


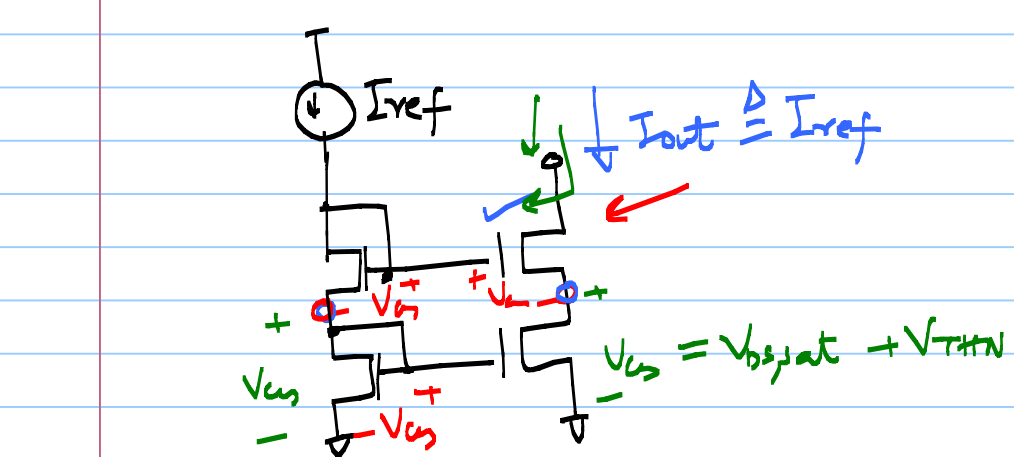
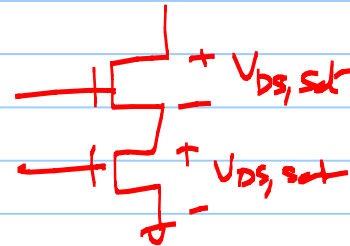


ECE 5411 - Lecture 10

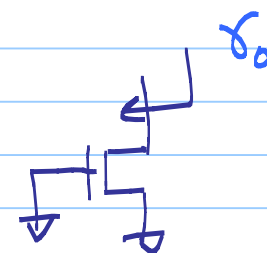
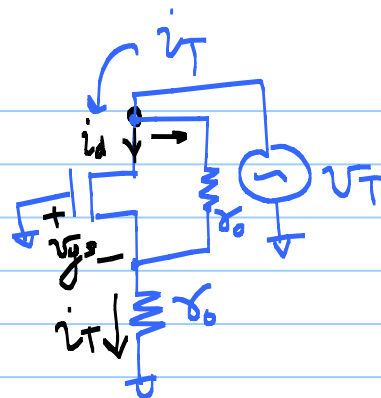
$$V_G \geq V_{GS} + V_{DS, \text{sat}} = 2V_{DS, \text{sat}} + V_{TH0V}$$



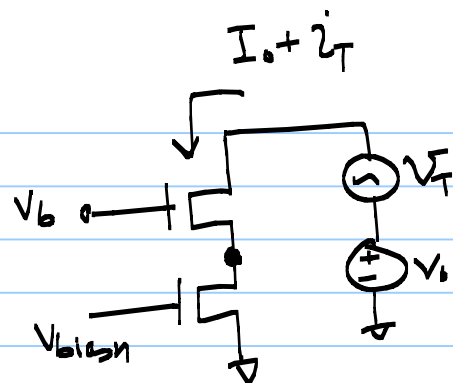

KVL: $v_{gs} + i_T r_o = 0 \Rightarrow v_{gs} = -i_T r_o \rightarrow \textcircled{1}$

KCL: $i_T - g_m v_{gs} - \frac{(v_T - (-v_{gs}))}{r_o} = 0 \rightarrow \textcircled{2}$

$$R_o = \frac{v_T}{i_T}$$

Eliminate v_{gs} :

$$v_{gs} = -i_T r_o$$

$$i_T + g_m r_o i_T - \frac{v_T}{r_o} + i_T = 0$$

$$\frac{v_T}{i_T} = (2 + g_m r_o) r_o = 2r_o + g_m r_o^2 \quad \text{if } g_m r_o \gg 1$$


$$\approx \boxed{g_m r_o^2} \leftarrow$$

$$= r_o (g_m r_o)$$

R_o is enhanced by $g_m r_o \gg 1$





Wide-Swing Cascode Current Mirrors

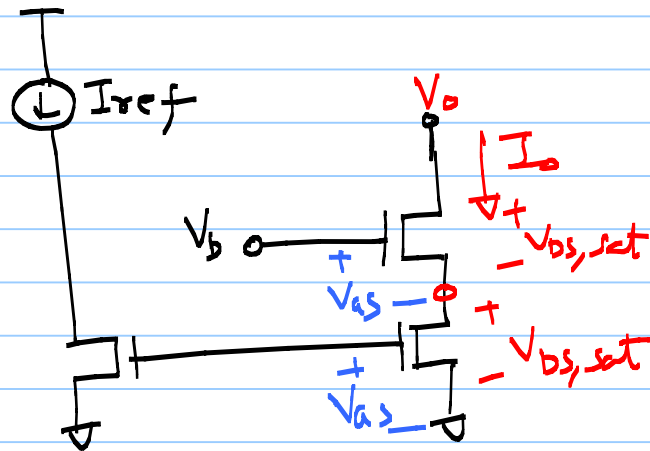

$$V_o \geq 2V_{ds,sat}$$
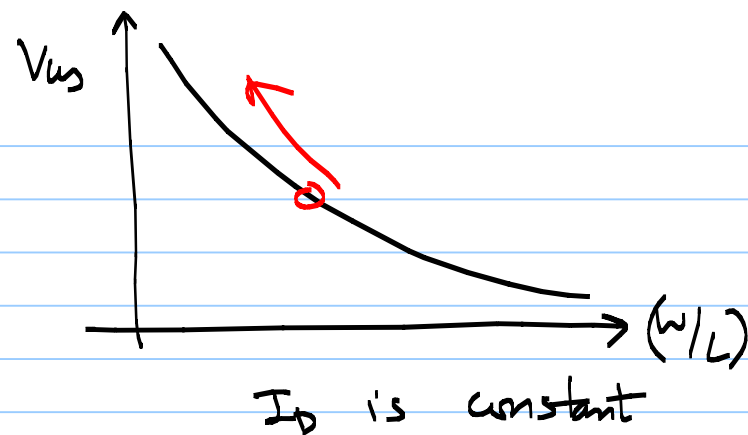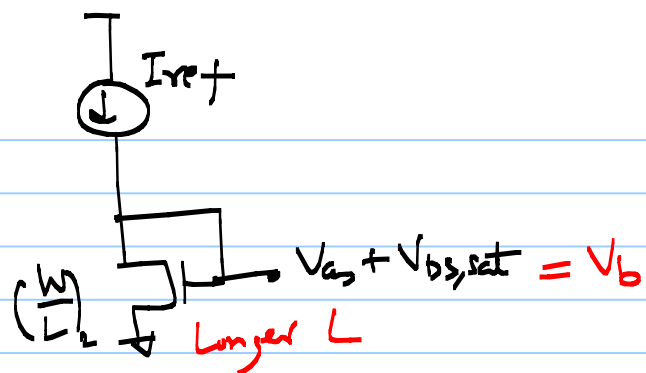
$$\begin{aligned} V_b &= V_{gs} + V_{ds,sat} \\ &= 2V_{ds,sat} + V_{thn} \end{aligned}$$




$$V_{gs} = \sqrt{\frac{2I_D}{K_L(\frac{W}{L})}} + V_{THN}$$

for higher V_{gs} for
same current

$$\left(\frac{W}{L}\right) \downarrow$$

$$\Rightarrow L \uparrow$$

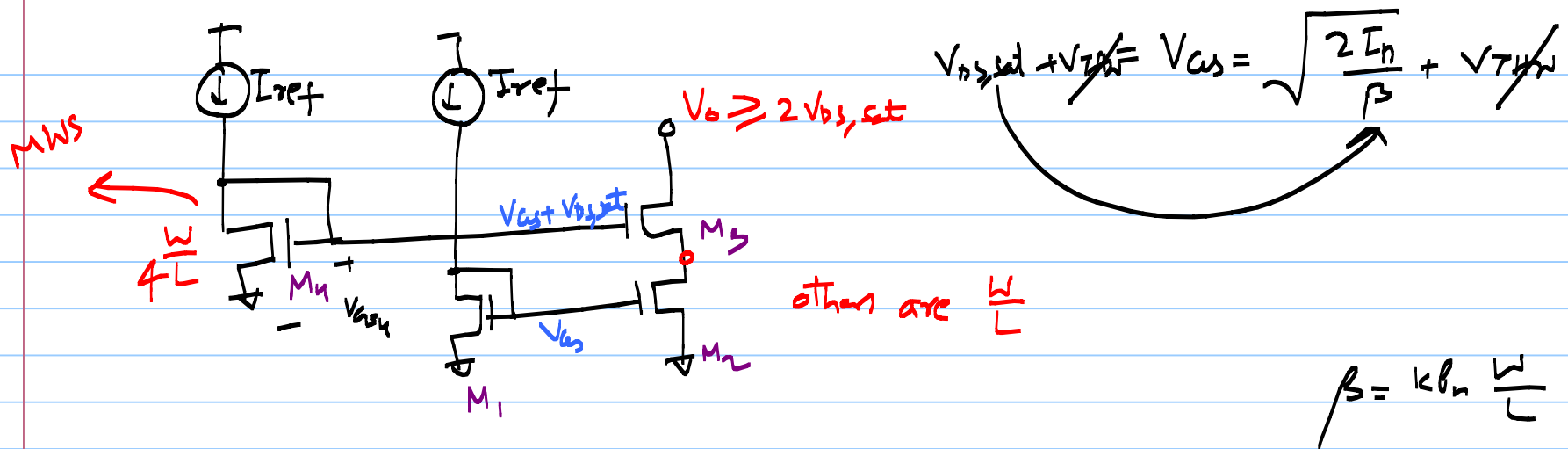

$$V_{gs4} = 2V_{ds,sat} + V_{thn} = \sqrt{\frac{2I_{ref}}{\beta_4}} + V_{thn}$$

find β_4


$$\Rightarrow 2\sqrt{\frac{2I_{ref}}{\beta}} = \sqrt{\frac{2I_{ref}}{\beta_4}}$$

$$\Rightarrow 2\sqrt{\beta_4} = \sqrt{\beta}$$


$$\Rightarrow \boxed{\beta_4 = \frac{\beta}{4}}$$

$$\Rightarrow \boxed{\left(\frac{W}{L}\right)_4 = \frac{W}{4L}}$$




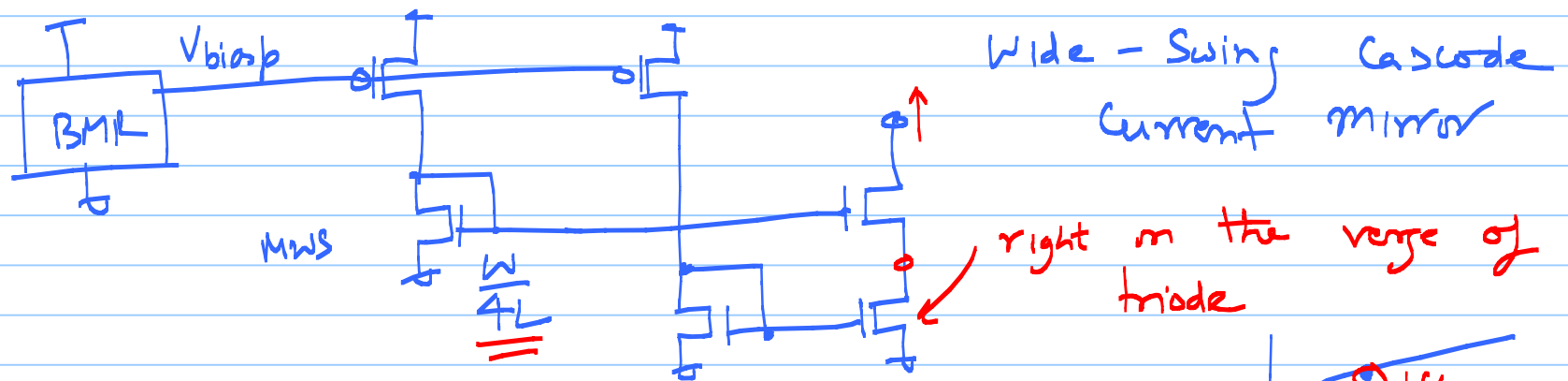
Long-L MWS device gives larger V_{GS4} for the same current.



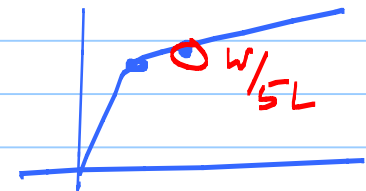$\frac{W}{SL}$ is better
 $\rightarrow$ slightly lower swing




* Matching

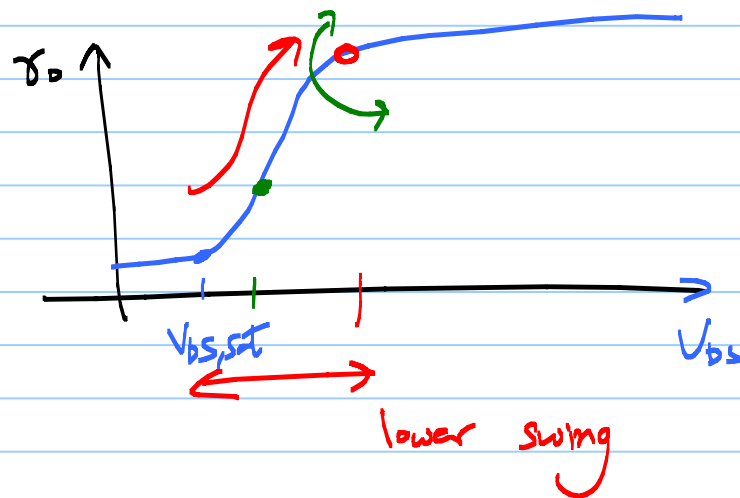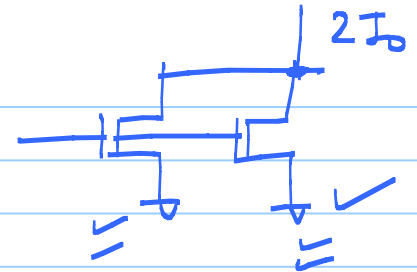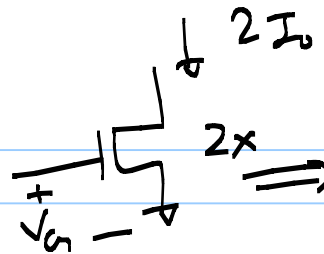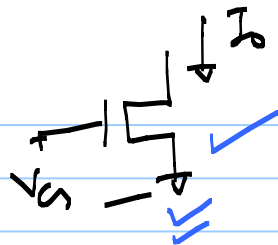


$$\left(\frac{W}{L}\right)_{MWS} = \frac{W}{2.5L} \quad \text{for } 50\text{nm}$$

* Bias the bottom device deeper into saturation
 $\Rightarrow$ larger 'L' in MWS device.


Short-channel Cascode Current Mirrors

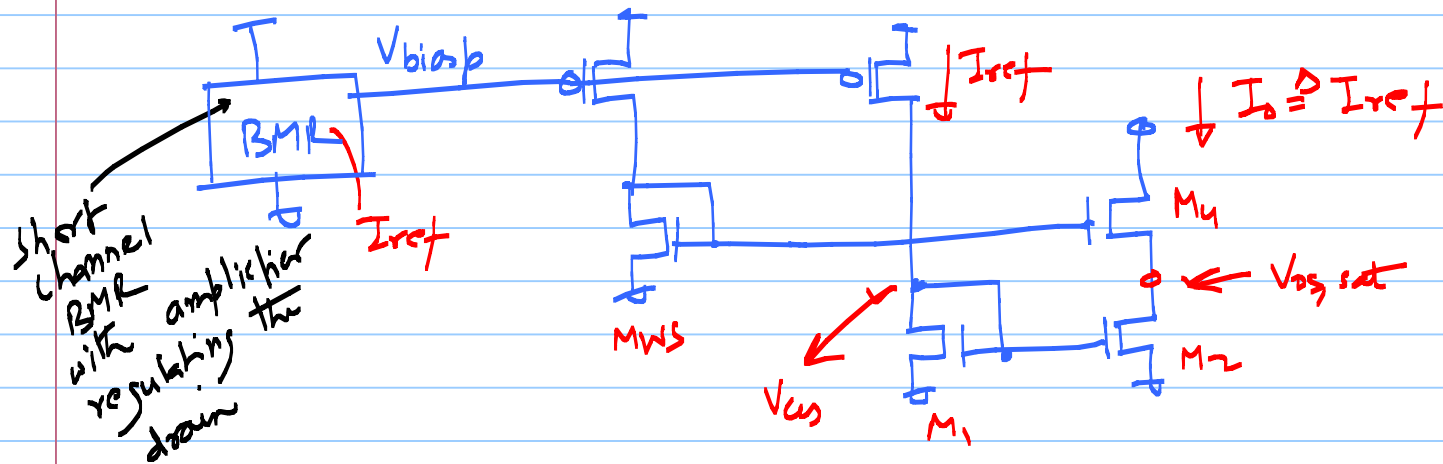


× V_{ds} of M_1 & M_2 are not the same.

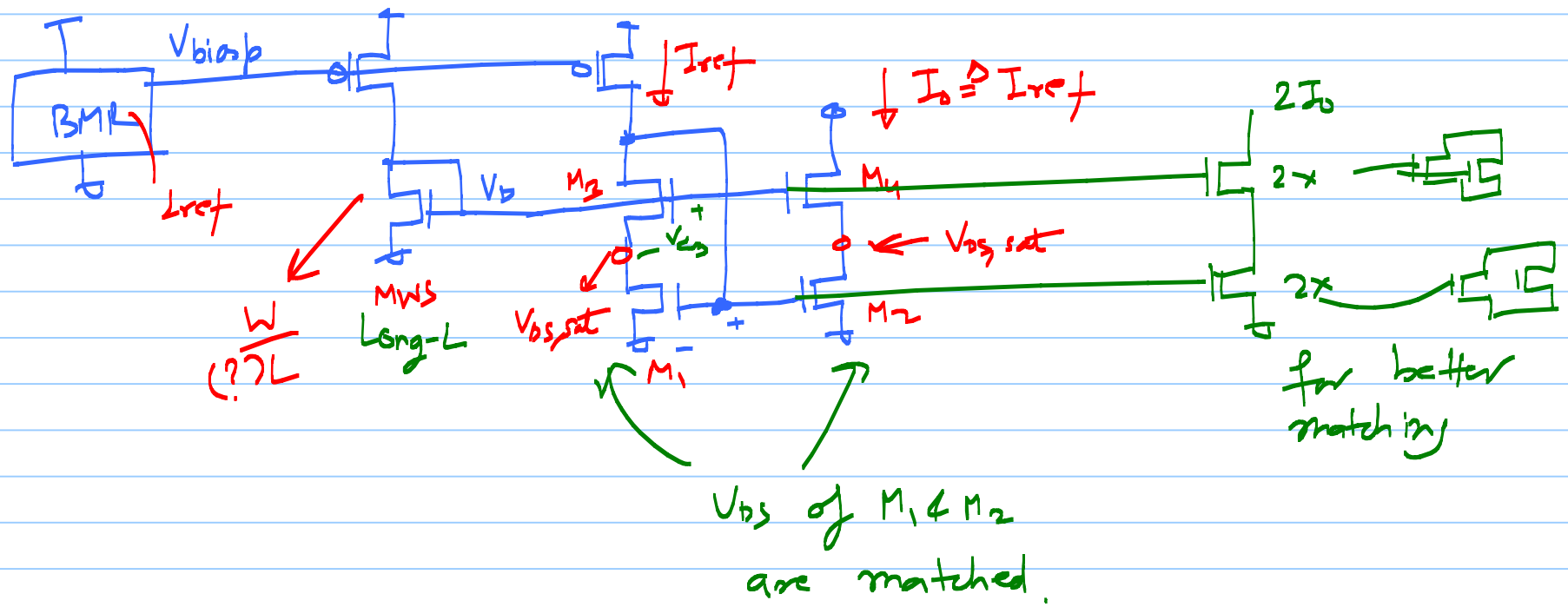

Regulated Drain Current Mirror :

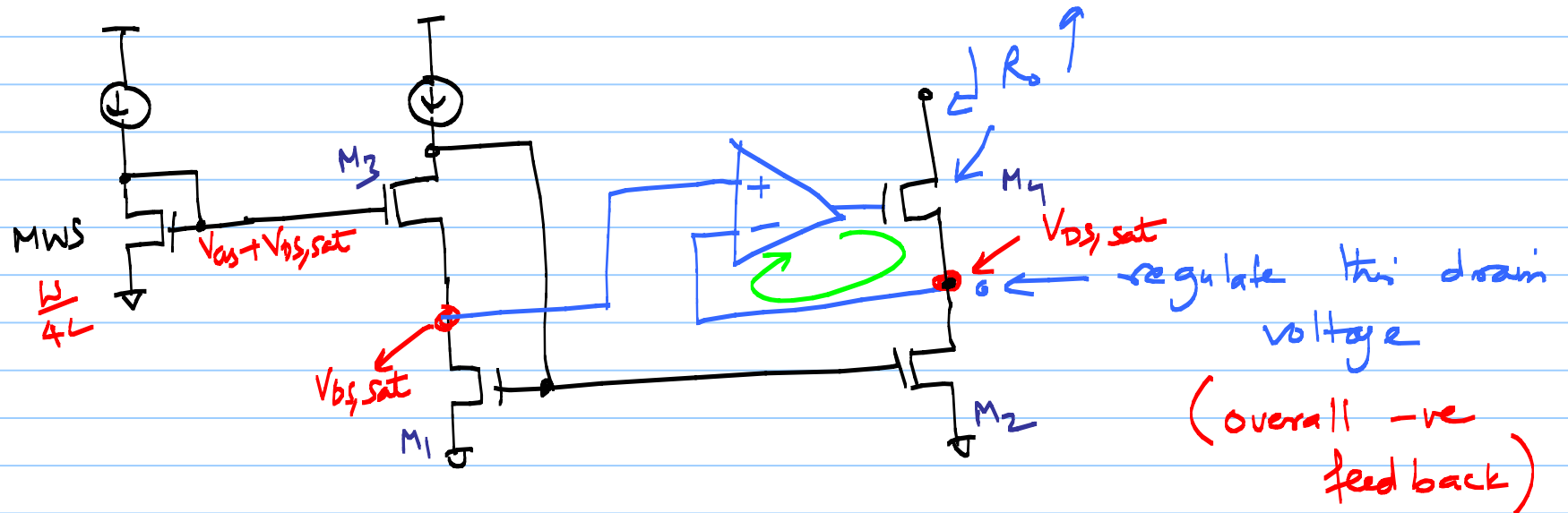

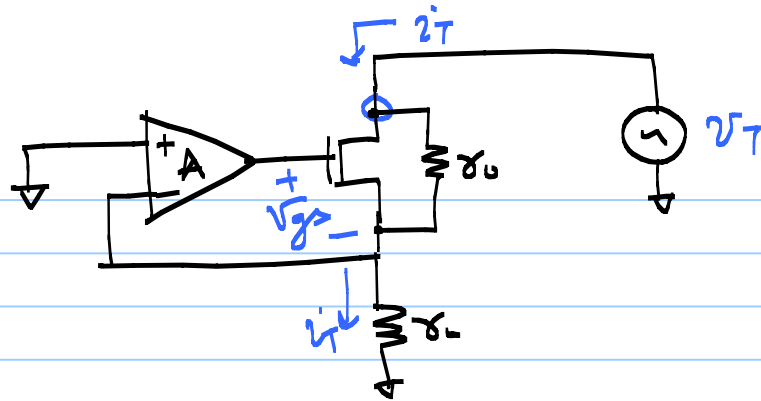If $A \rightarrow \infty$,
 $\Rightarrow V_{D2} = V_{D1} \Rightarrow R_D \rightarrow \infty$



$$(0 - i_T r_o) A = i_T r_o + v_{gs}$$

$$\Rightarrow -i_T r_o (A+1) = v_{gs} \longrightarrow \textcircled{1}$$

KCL:

$$i_T - g_m v_{gs} - \frac{(v_T - i_T r_o)}{r_o} = 0$$

$$\Rightarrow i_T + g_m r_o (A+1) i_T - \frac{v_T}{r_o} + i_T = 0$$

$$\Rightarrow \frac{v_T}{r_o} = i_T (2 + g_m r_o (A+1))$$

$$\Rightarrow R_o = \frac{v_T}{i_T} = (2 + g_m r_o (A+1)) r_o$$


$$= 2r_o + g_m r_o^2 (A+1)$$

$$\approx g_m r_o^2 A$$

$$A \gg 1$$

$$g_m r_o \gg 1$$

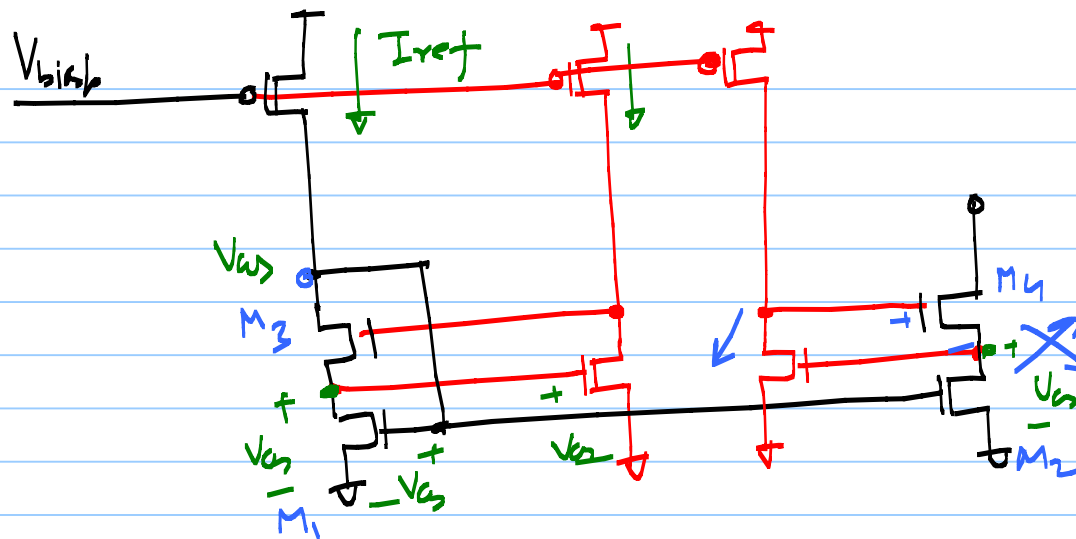$\Rightarrow$ output resistance is enhanced by the amplifier gain.





* Not a wide-swing
current mirror

"-ve feedback"

$$R_o = (g_m r_o^2) A \rightarrow \frac{g_m r_o}{2}$$

$$= \frac{g_m^2 r_o^3}{2}$$

Long-channel



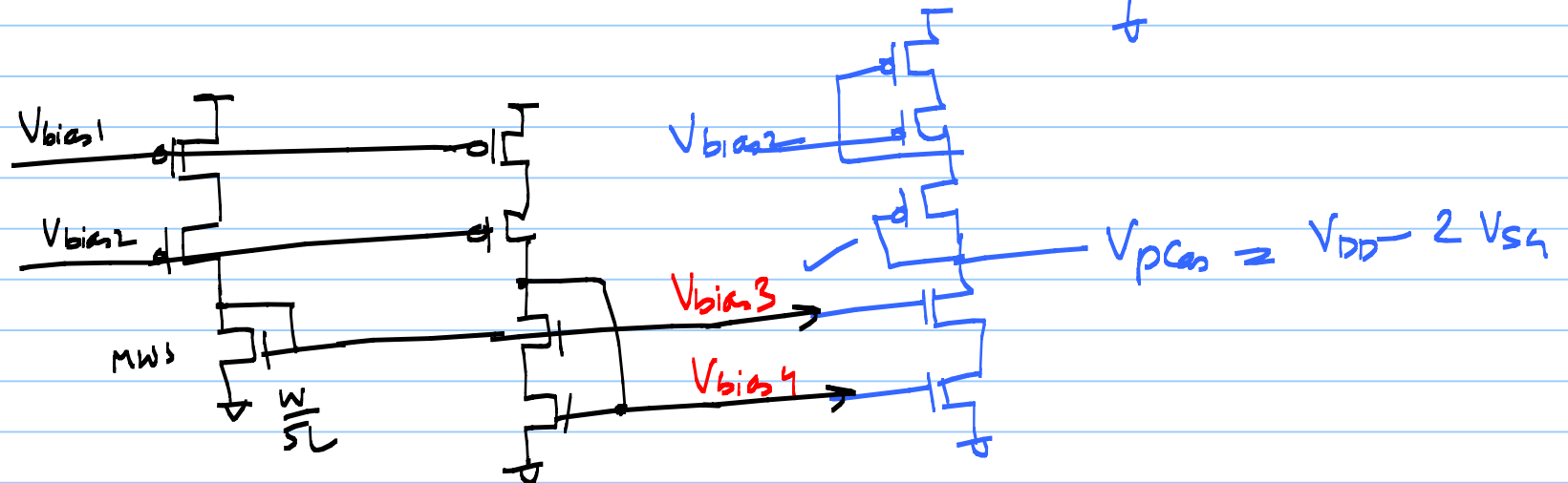
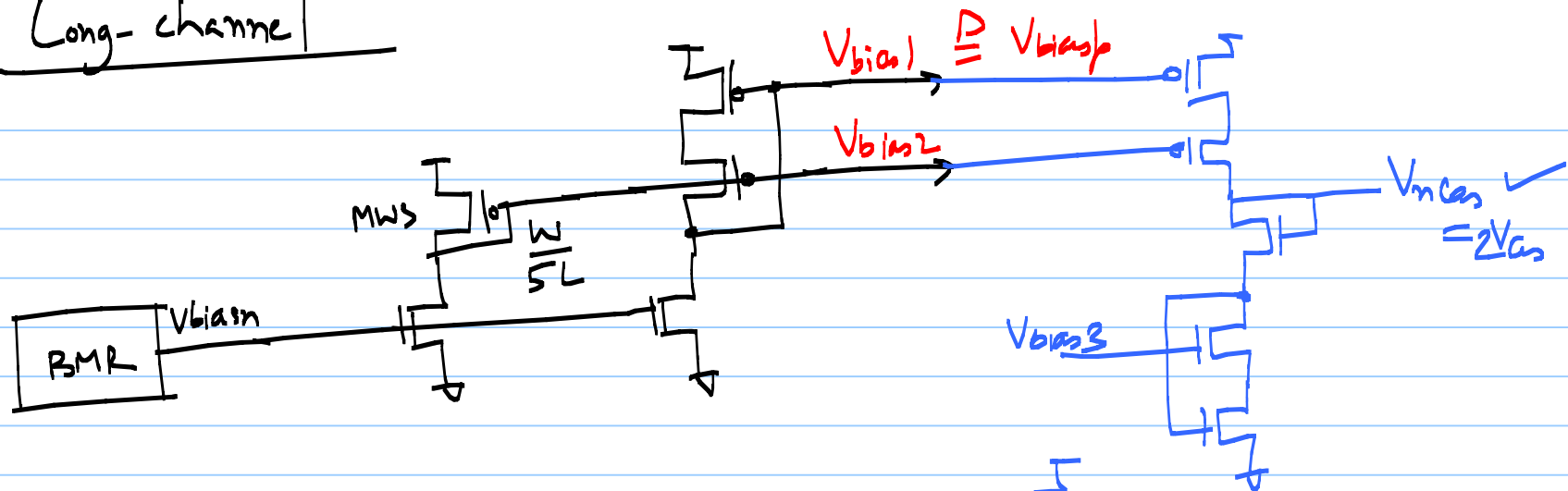




for short-channel

↳ use drain regulated BMR

↳ Adjust $\frac{W}{L}$ of the MOS devices.

ex. $50n \rightarrow \frac{W}{25L}$

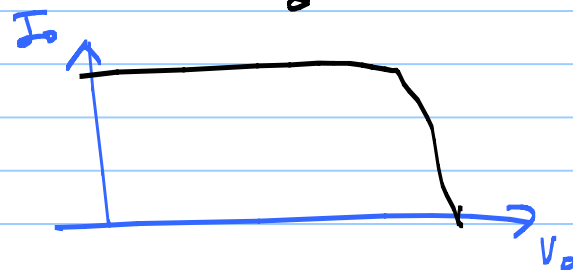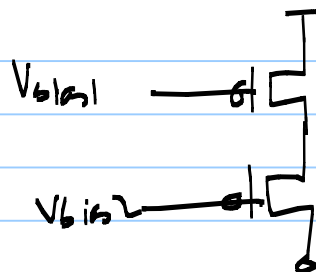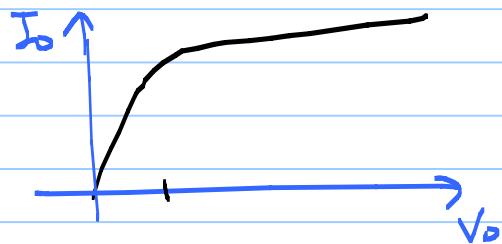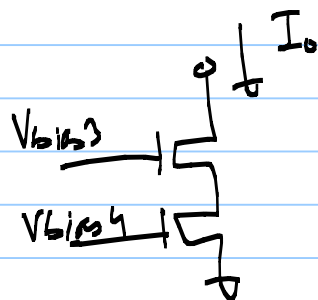

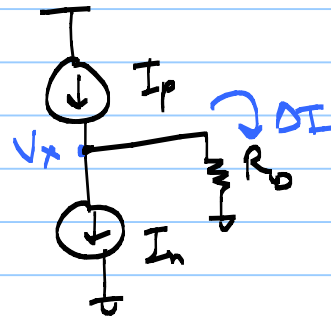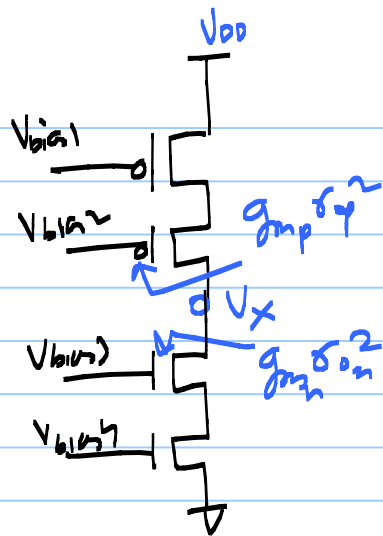

$$\Delta I = I_p - I_n$$



① $I_p > I_n$

* V_x keeps on increasing till I_p shuts down

② $I_p < I_n$

* V_x hits the ground rail

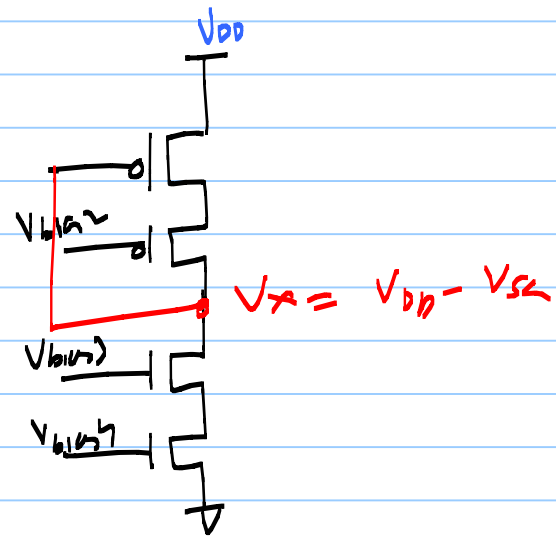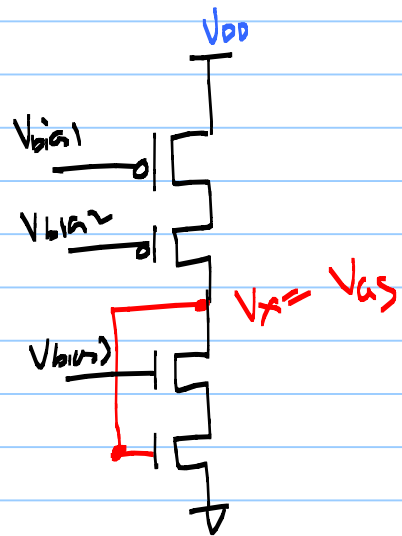* Cannot have two "independent" current sources fighting each other.



Floating Current Source

