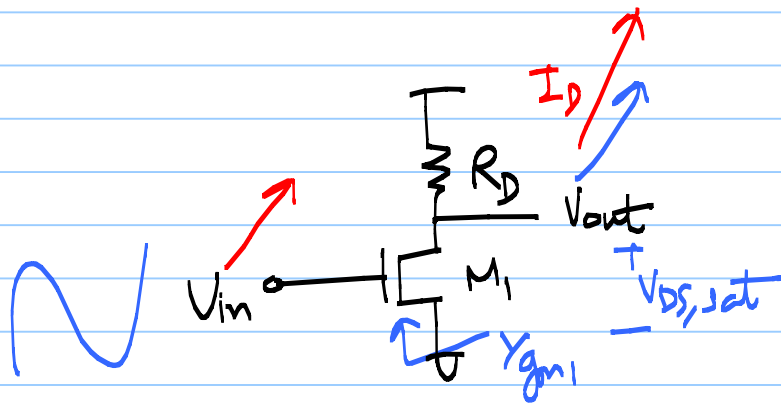


ECE541 - Lecture 12


Note Title


3/2/2011



$V_{in} \uparrow \Rightarrow I_D \uparrow$
 $g_m \uparrow$
 $g_m = f(V_{in})$

$$A_v = -g_{m1}(R_D || r_{o1})$$
$$= - \frac{(R_D || r_{o1})}{\frac{1}{g_{m1}}}$$

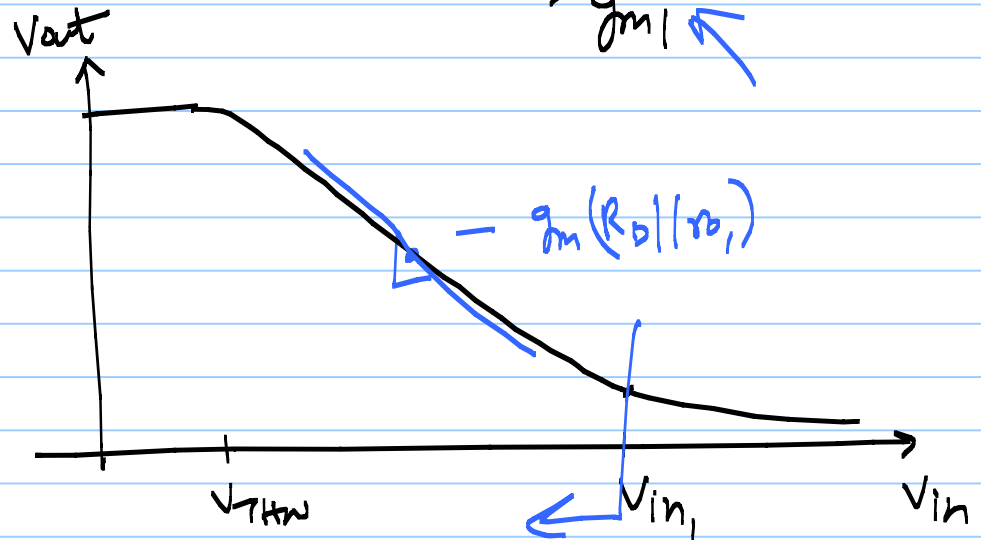


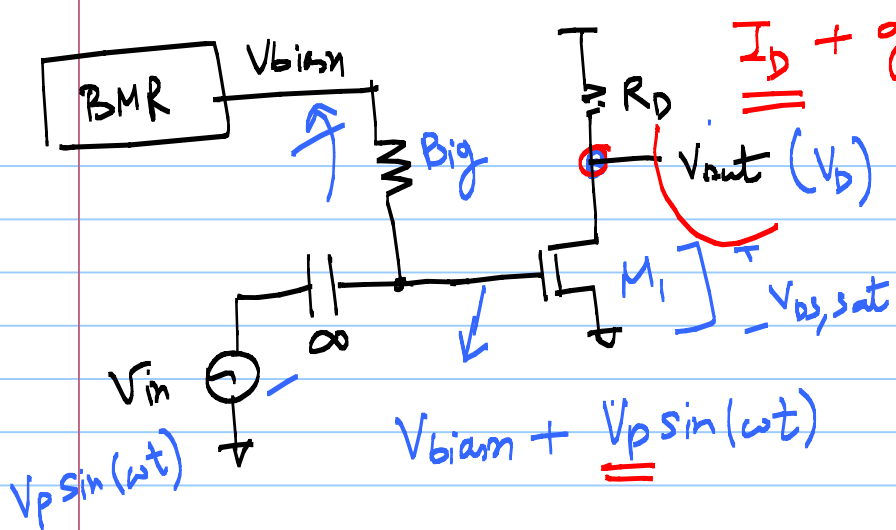

$$\underline{I_D} + g_m \underline{V_{in}} = \underline{i_D}$$

$$A_v = -g_{m1} (R_D || R_L || r_{o1})$$

$I_D \downarrow$

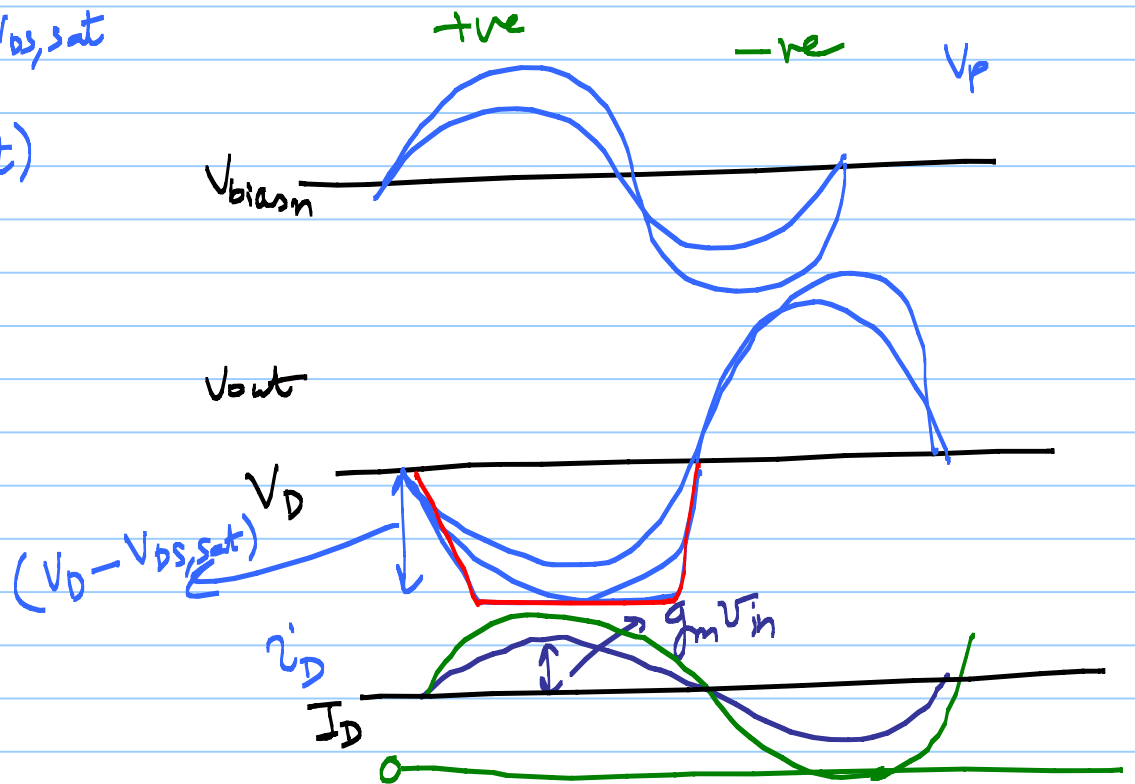

* +ve input cycle

* M_1 can enter triode


$$V_{pmax_1} \leq \frac{(V_{DS} - V_{DS,sat})}{|A_v| \rightarrow g_m (R_D || r_{o1})}$$


* -ve input cycle

* M_1 can enter cutoff $\Rightarrow v_a = -I_D$

$$V_{pmax_2} \leq \frac{I_D}{g_m}$$

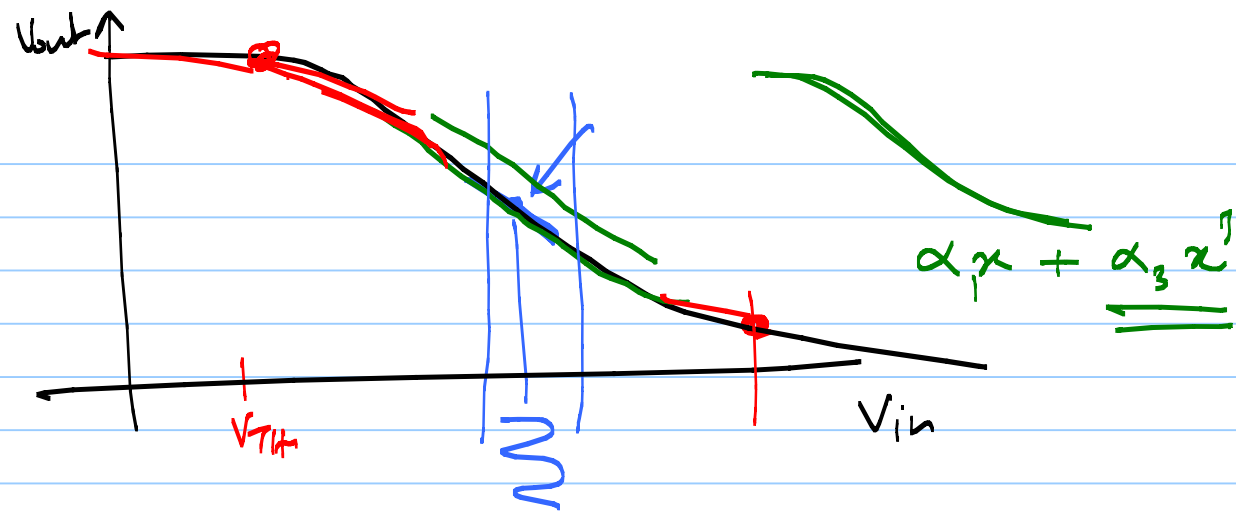* maximum permissible input signal amplitude
= $\min(V_{pmax_1}, V_{pmax_2})$



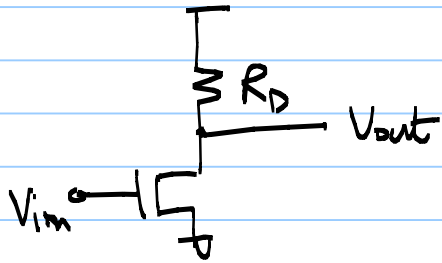




$$A_v = -g_m(R_D || r_{o1})$$

$$R_D \ll r_{o1}$$

$$\approx -g_m R_D$$

$$f_T \propto \frac{V_{ov}}{L}$$

$$g_{m,r} \propto \frac{L}{V_{ov}}$$

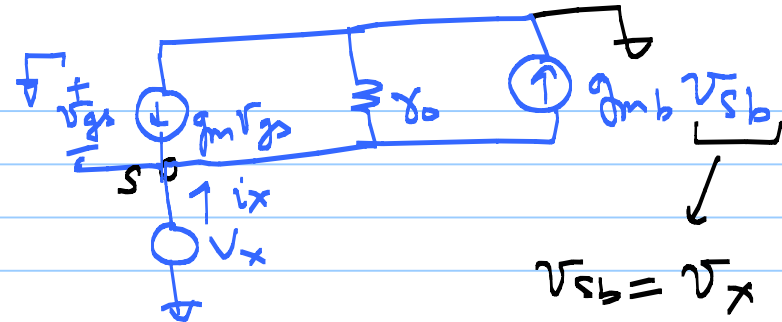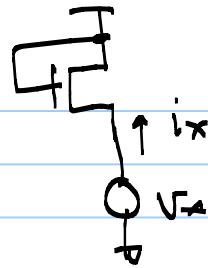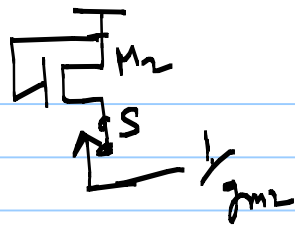

$$g_m v_{gs} - g_{mb} v_{sb} - \frac{v_x}{r_o} + i_x = 0$$

$$\frac{v_{gs} = -v_x}{v_{sb} = v_x}$$


$$-g_m v_x - g_{mb} v_x - \frac{v_x}{r_o} + i_x = 0$$

$$\left[-(g_m + g_{mb}) - \frac{1}{r_o} \right] v_x - i_x = 0$$

$$- \left[(g_m + g_{mb}) + r_o^{-1} \right] v_x - i_x = 0$$

$$R_{out} = \frac{v_x}{i_x} = \frac{1}{g_m + g_{mb} + r_o^{-1}}$$
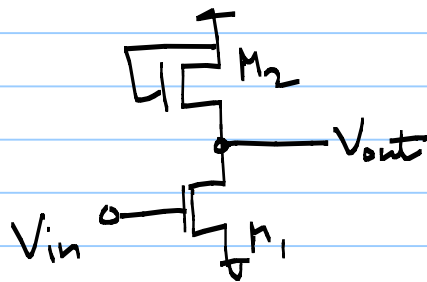
$$R_{out} \approx \frac{1}{g_m + g_{mb}} \quad \text{if } r_o \gg \frac{1}{g_m}$$



$$A_v = - \frac{\frac{1}{(g_{m2} + g_{mb2})}}{\frac{1}{g_{m1}}} = - \frac{g_{m1}}{g_{m2} + g_{mb2}} = - \frac{g_{m1}}{g_{m2}} \left(\frac{1}{\eta + 1} \right)$$

$g_{mb} = \eta g_m$

$$A_v = - \frac{g_{m1}}{g_{m2}} \left(\frac{1}{\eta+1} \right)$$



$$g_m = \sqrt{2\beta I_D}$$

$$= - \sqrt{\frac{(w/L)_1}{(w/L)_2}} \cdot \left(\frac{1}{\eta+1} \right)$$

$$\frac{g_{m1}}{g_{m2}} = \sqrt{\frac{(w/L)_1}{(w/L)_2}}$$

* Av gain is independent of bias currents & voltages

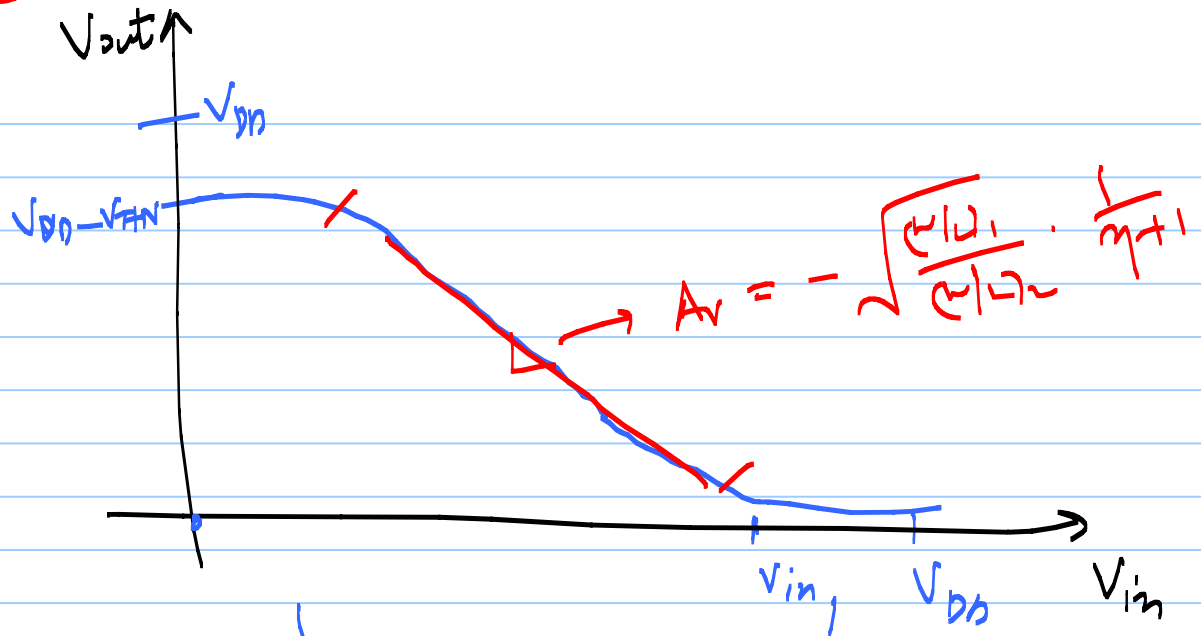
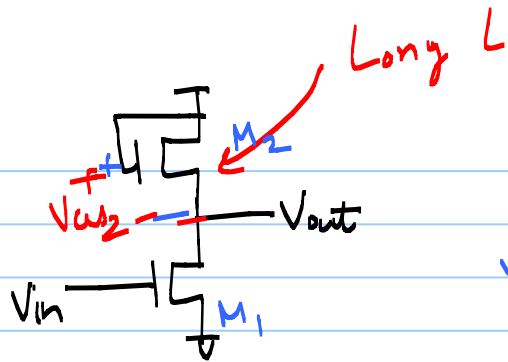
* if input signal varies, gain is constant






$$A_v = - \sqrt{\frac{(w/L)_1}{(w/L)_2}} \cdot \frac{1}{\eta + 1}$$

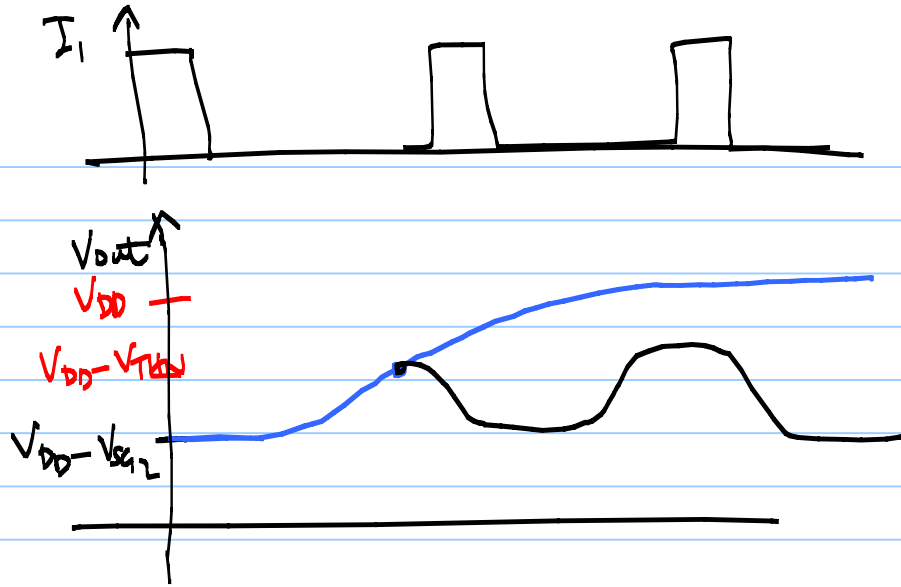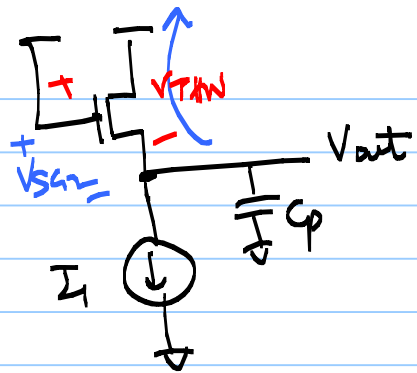0.8 ← $\frac{1}{\eta + 1}$

increase $A_v \Rightarrow$ make $(w/L)_2$ smaller $\Rightarrow V_{GS2} \uparrow$
 \hookrightarrow reduced output swing



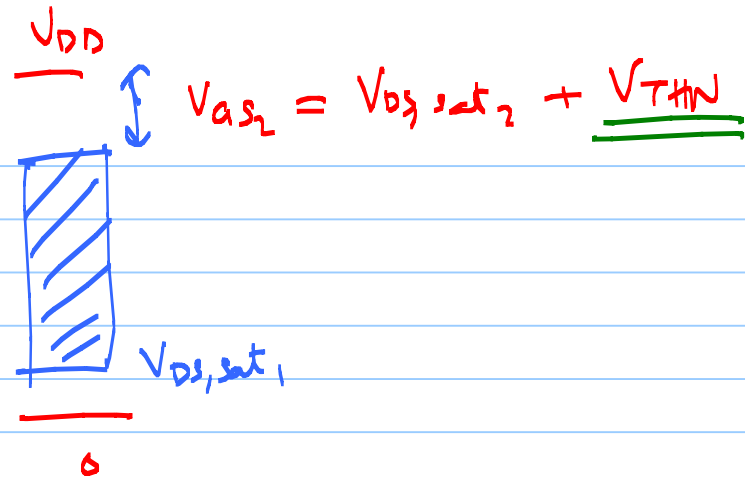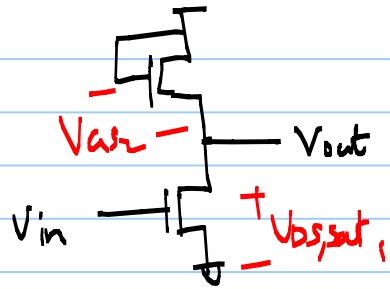


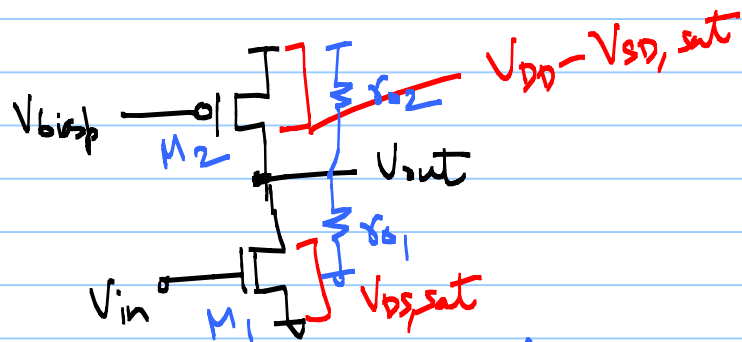


$$A_v = - \frac{(r_{o1} \parallel r_{o2})}{\frac{1}{g_{m1}}} = - g_{m1} (r_{o1} \parallel r_{o2})$$

* much larger gain

* better output swing / voltage headroom

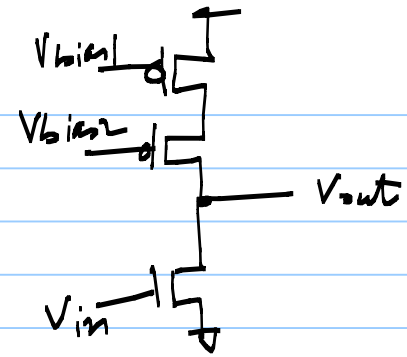

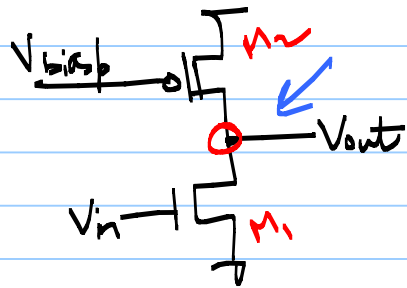* the output impedance value is no longer coupled with the drop across the load.




* output bias voltage in this circuit is not well defined

* Stage is reliably biased only in a feedback circuit.

$$-g_m(r_{o1} \parallel r_{o2}) \quad g_m r_o \propto \frac{L}{V_{ov}}$$

$$f_T \propto \frac{V_{ov}}{L}$$

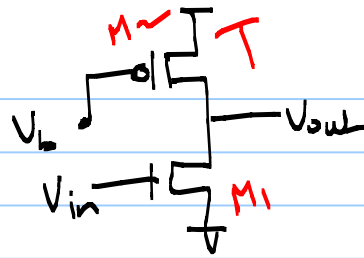

$$R_{ch} = \frac{1}{k_p \left(\frac{W}{L}\right)_p (V_{DD} - V_b - V_{THP})}$$


R_{ch} depends on P_T

↳ hard to design with P_T variations

CS with Source Degeneration

$\Rightarrow M_1 \rightarrow$ non-linear I-V characteristics

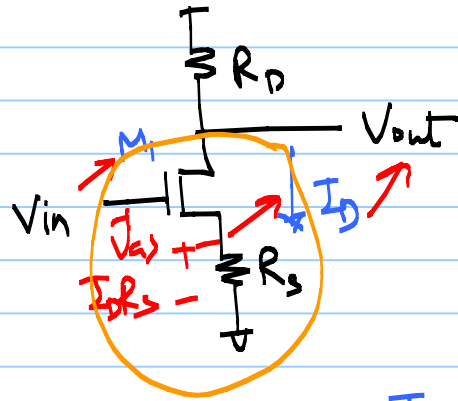
\hookrightarrow Can we use feedback to linearize this CS stage



$$I_D = \frac{V_{in} - V_{GS}}{R_S}$$

if $\Delta V_{GS} = 0$
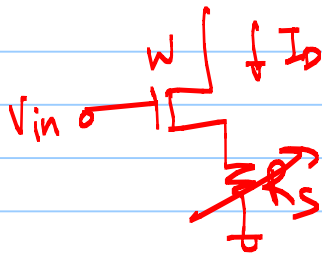
$$\Delta I_D = \frac{\Delta V_{in}}{R_S}$$



$$I_D \approx \frac{V_{in}}{R_S}$$

VGA

