
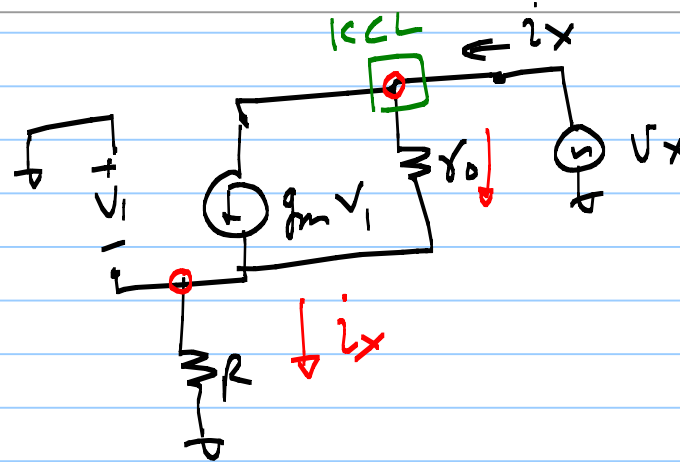


ECE 5411 - Lecture 13.

Note Title

3/7/2011

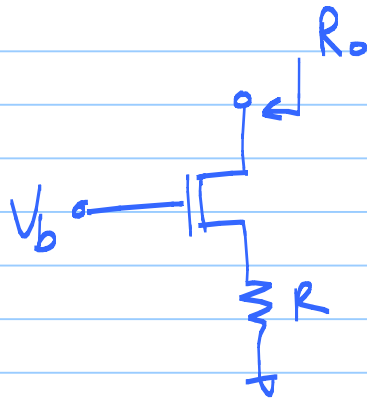

$$\underline{\underline{\frac{V_x}{i_x} = R_o}}$$

KCL $\Rightarrow$

$$i_x - g_m V_1 - \frac{V_x - i_x R}{r_o} = 0 \rightarrow (2)$$

$$i_x + g_m R i_x - \frac{V_x}{r_o} + i_x \frac{R}{r_o} = 0$$

$V_1 = -i_x R \rightarrow (1)$


$$i_x \left[1 + g_m R + \frac{R}{r_o} \right] = \frac{v_x}{r_o}$$

$$\Rightarrow \frac{v_x}{i_x} = \left[g_m R + 1 + \frac{R}{r_o} \right] r_o$$

$$= \boxed{g_m r_o R + R + r_o}$$


$$\approx g_m r_o R$$

$$g_m r_o \gg 1$$


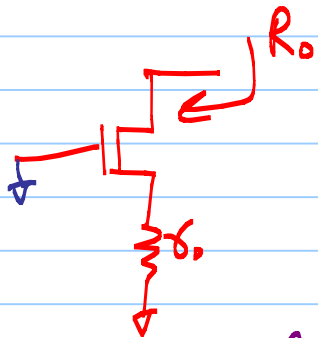


$$R_o \approx g_m r_o^2$$

$$= g_m r_o^2 + 2r_o$$

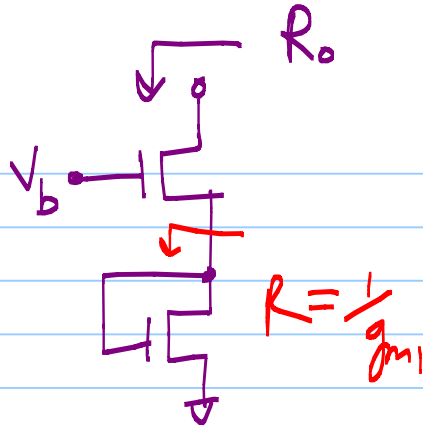

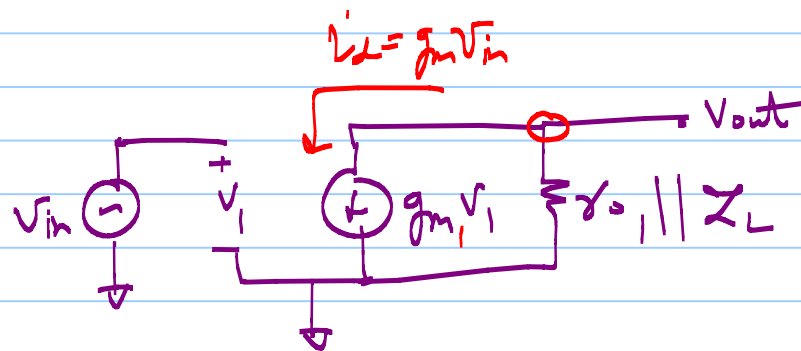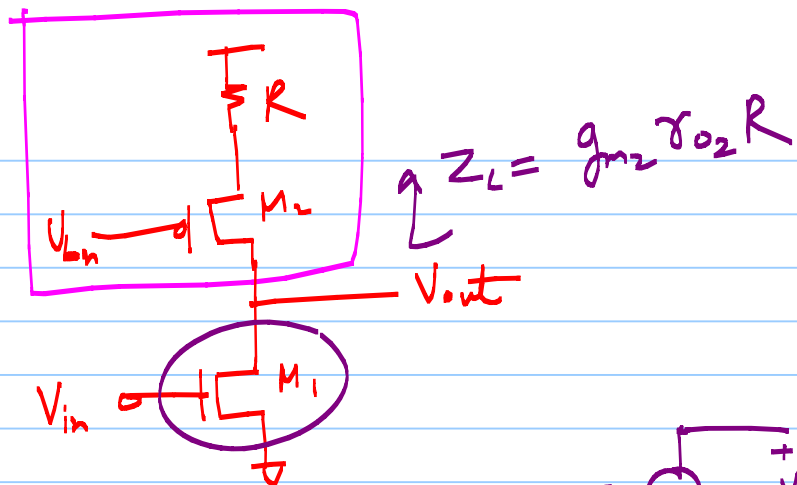
$$R_o = g_{m2} r_{o2} \frac{1}{g_{m1}} + \frac{1}{g_{m1}} + r_o$$



$$V_{out} = -g_{m1} V_{in} \cdot [r_{o1} \parallel (g_{m2} r_{o2} R)]$$

$$\Rightarrow A_v = \frac{V_{out}}{V_{in}} = -g_{m1} \times r_{o1} \parallel (g_{m2} r_{o2} R)$$



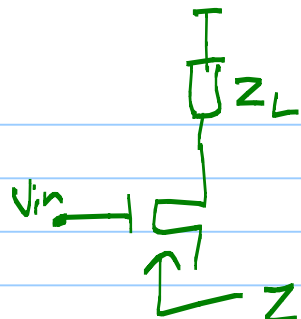
$$= - \frac{r_{o1} \parallel (g_{m2} r_{o2} R)}{\frac{1}{g_{m1}}} \leftarrow$$




$Z_{in} = \text{depends on } Z_L$

$\approx 1/g_m$ only if Z_L is small

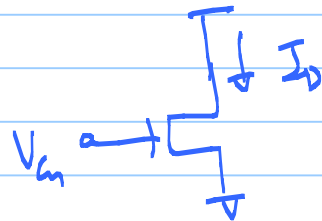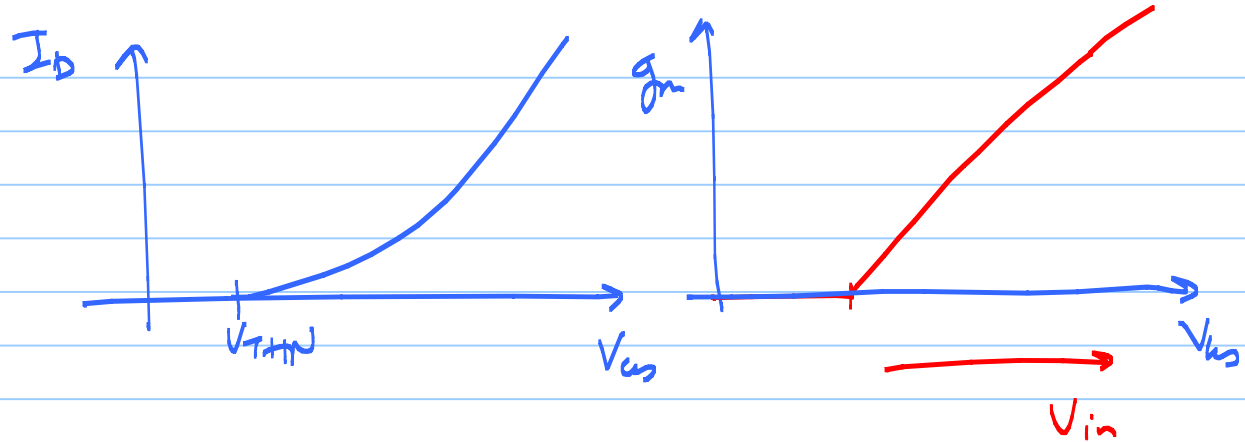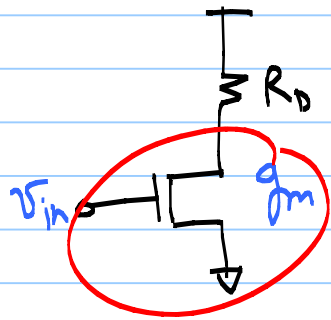Common - Source Amplifier with Source Degeneration



$$A_v = -g_m R_D$$
$$\Rightarrow$$

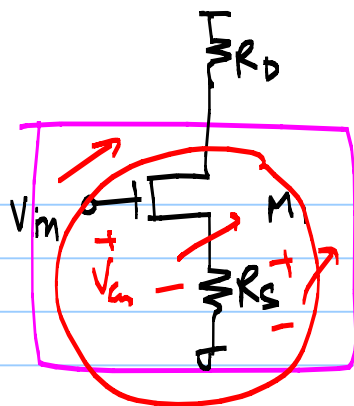


$I_D \uparrow$

V_{GS} is relatively constant



$$I_D = \frac{V_{in} - V_{GS}}{R_S}$$
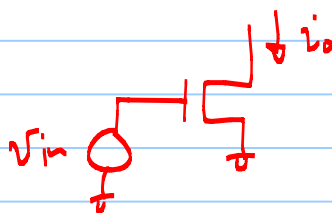
$$\Delta I_D \approx \frac{\Delta V_{in}}{R_S}$$



$$\frac{v_o}{v_{in}} = g_m$$

Assume $\Rightarrow \lambda = 0$

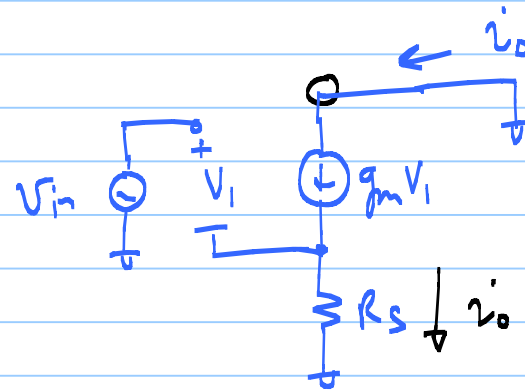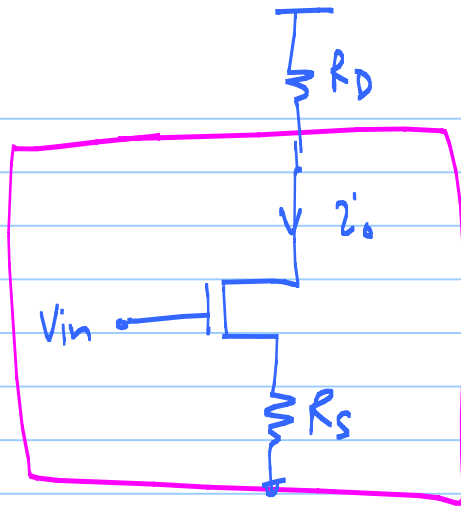


$$V_1 = V_{in} - i_o R_S \longrightarrow \textcircled{1}$$

$$i_o = g_m V_1 = g_m (V_{in} - i_o R_S)$$

$$\Rightarrow \frac{i_o}{V_{in}} = \frac{g_m}{1 + g_m R_S} = g_{m_{eff}}$$

$$i_o = \boxed{g_m} v_{in}$$

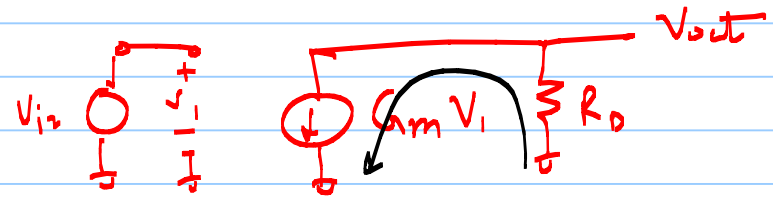

$$\begin{aligned} v_{out} &= -i_o R_D \\ &= -g_m v_{in} R_D \end{aligned}$$

$$\Rightarrow A = \frac{v_{out}}{v_{in}} = -\boxed{g_m} R_D$$

$$g_m = \frac{g_m}{1 + g_m R_S}$$

↳ g_m is smaller

$$g_m = \frac{1}{\frac{1}{g_m} + R_S} \quad \text{if } R_S \gg \frac{1}{g_m}$$

$$\approx \frac{1}{R_S}$$

↳ for $R_S \gg \frac{1}{g_m}$

↳ g_m becomes a weak function of g_m

$\Rightarrow$ the drain current is a 'linearized' function of the input voltage

$$\approx \frac{1}{R_S}$$

Cost $\Rightarrow$ lower gain
higher noise

$$\lambda \neq 0, g_{mb} \neq 0$$

$$g_m = \frac{g_m r_o}{R_S + [1 + (g_m + g_{mb}) R_S] r_o}$$




$\leftarrow$ Exercise


Set

$$g_{mb} = 0 \\ r_o \rightarrow \infty$$

$\Rightarrow \approx$

$$\frac{g_m}{1 + g_m R_S}$$

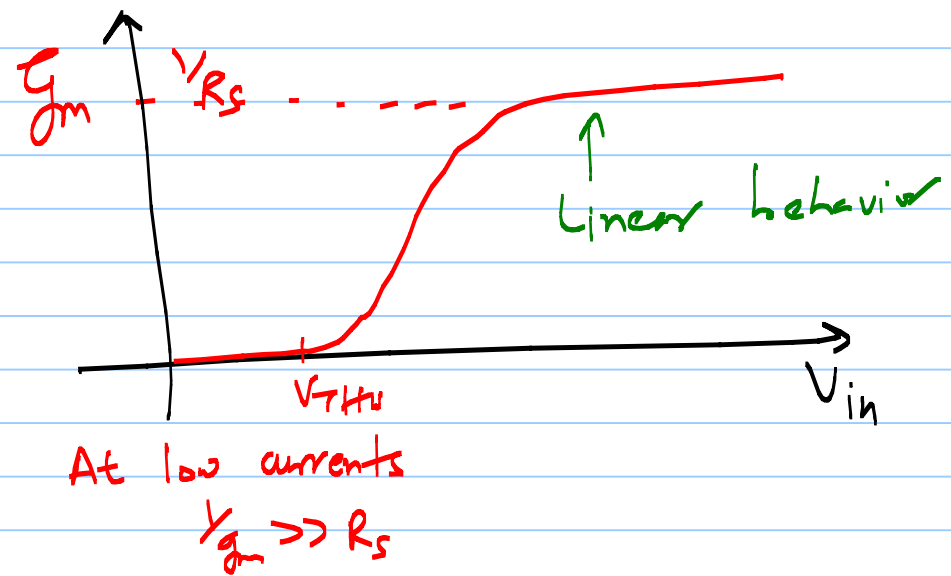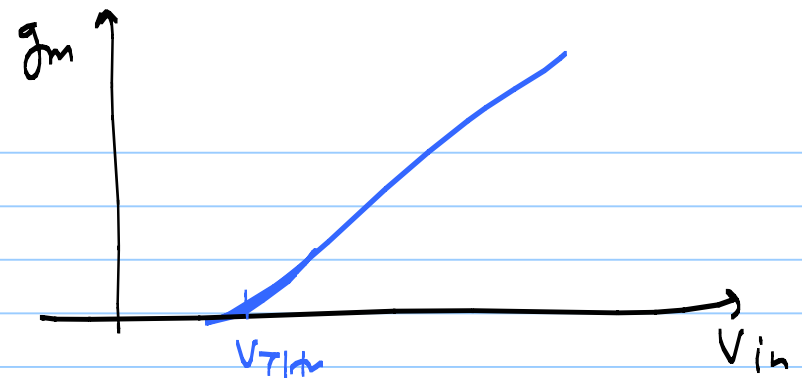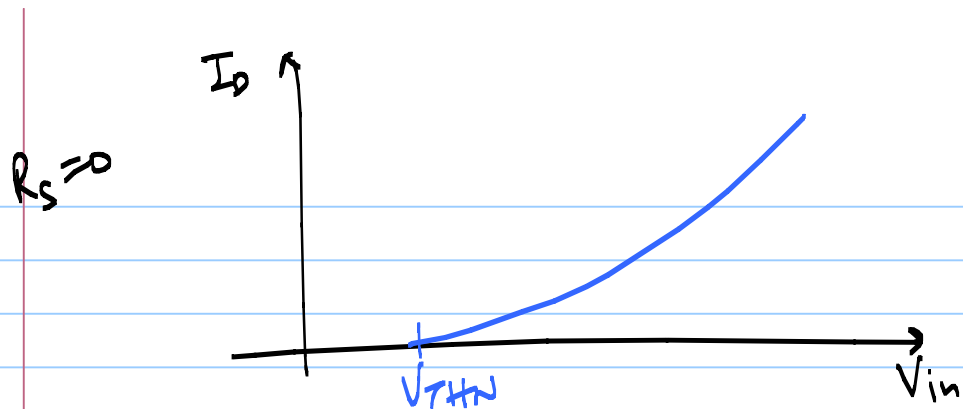

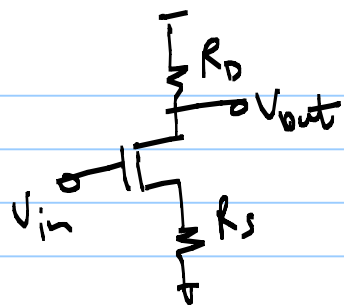

$$A_v = -g_m R_D$$


$$= - \frac{g_m R_D}{1 + g_m R_s}$$

$$= - \frac{R_D}{\frac{1}{g_m} + R_s}$$

if $R_D \gg \frac{1}{g_m}$

$$A_v \approx - \frac{R_D}{R_s}$$

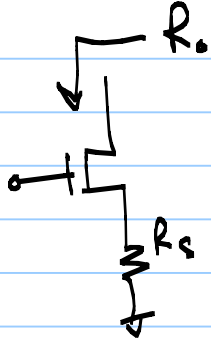* output impedance of CS with source degeneration




$$R_o \approx g_m r_o R_s = \underbrace{(g_m R_s)} r_o$$

$$R_o = [1 + (g_m + g_{mb}) R_s] r_o$$

R_{out} has "increased" by a factor of
 $1 + \underbrace{(g_m + g_{mb}) R_s}$

$$\lambda = 0$$

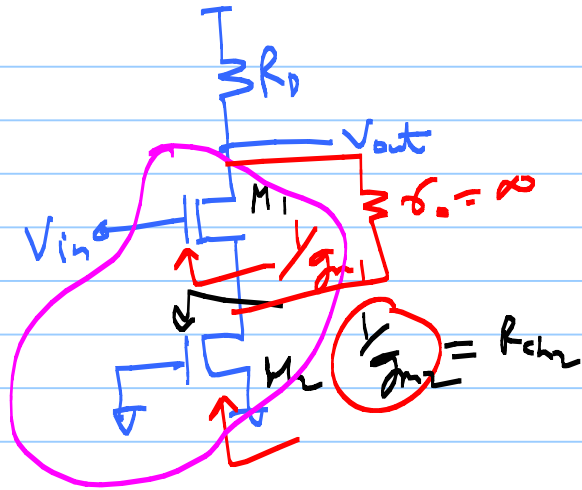


$$g_m = \frac{g_{m1}}{1 + g_{m1} \frac{1}{g_{m2}}}$$


$$\begin{aligned} A_v &= -g_m R_D \\ &= -\frac{g_{m1} R_D}{1 + \frac{g_{m1}}{g_{m2}}} \end{aligned}$$

$$A_v = - \frac{\text{Resistance seen in the drain}}{\text{total resistance seen in the source path}} = - \frac{R_D}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}}$$

Common Drain Amplifier (Source follower)


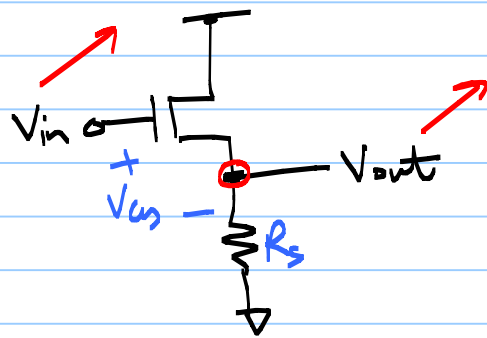


V_{SB}
 θ_{mb}

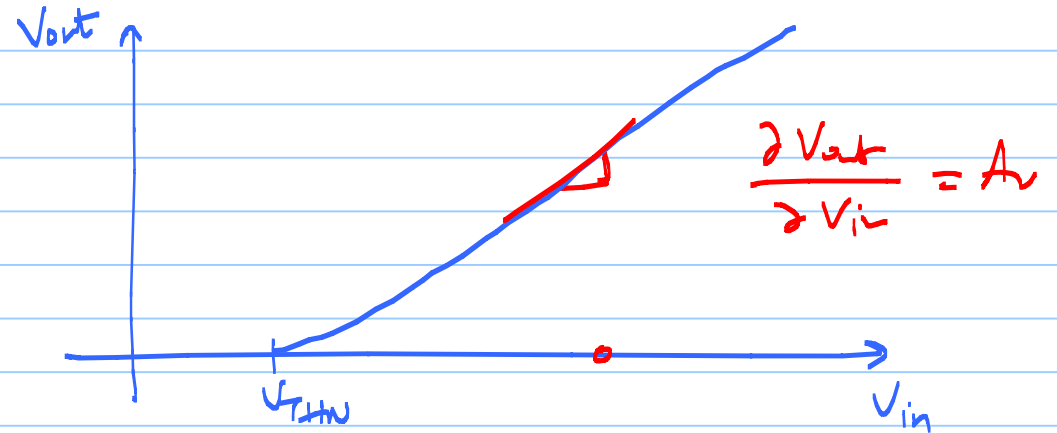

Small-signal analysis

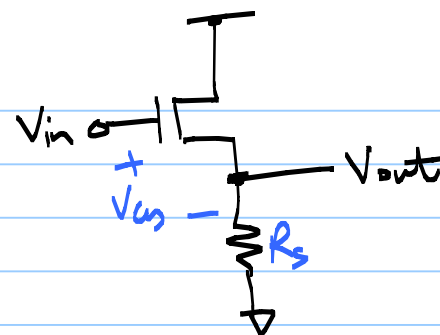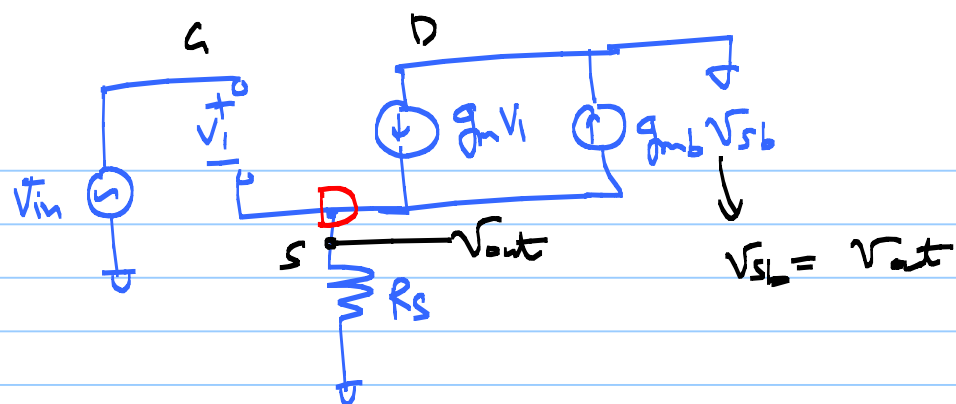$\lambda = 0 \Rightarrow r_o \rightarrow \infty$



$$V_{in} - V_1 = V_{out} \longrightarrow \textcircled{1}$$

$$KCL \Rightarrow g_m V_1 - g_{mb} V_{out} = \frac{V_{out}}{R_s} \longrightarrow \textcircled{2}$$

$$\Rightarrow g_m (V_{in} - V_{out}) - g_{mb} V_{out} = \frac{V_{out}}{R_s}$$

$$\Rightarrow V_{out} [(g_m + g_{mb}) + \frac{1}{R_s}] = g_m V_{in}$$

$\Rightarrow$

$$A_v = \frac{v_{out}}{v_{in}} = \frac{g_m R_s}{1 + (g_m + g_{mb}) R_s}$$


$\Rightarrow$ non-inverting gain

$$= \frac{g_m R_s}{1 + (\eta + 1) g_m R_s}$$





$$g_{mb} = \eta g_m$$

$$A_v = \frac{1}{(\eta + 1) + \frac{1}{g_m R_s}} < 1$$

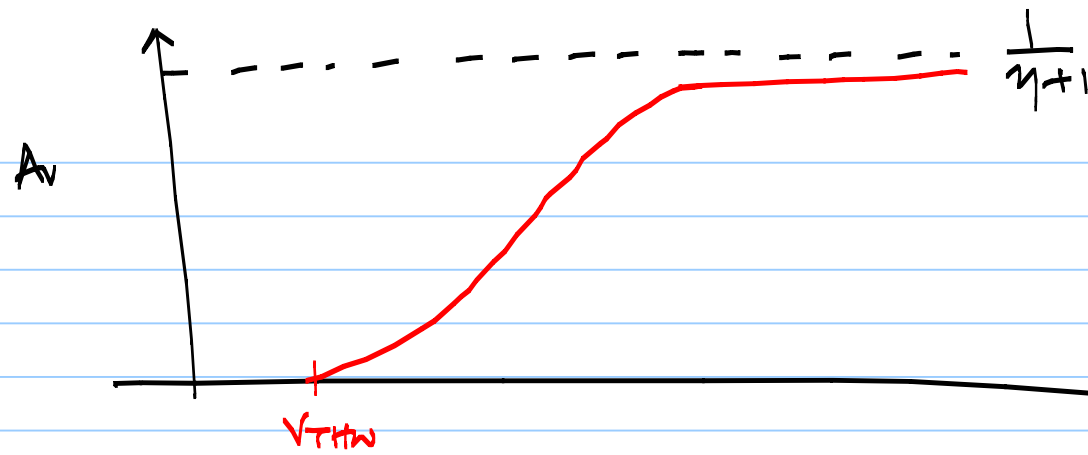
$$\approx \frac{1}{\eta + 1} \quad \text{when } g_m R_s \gg 1$$



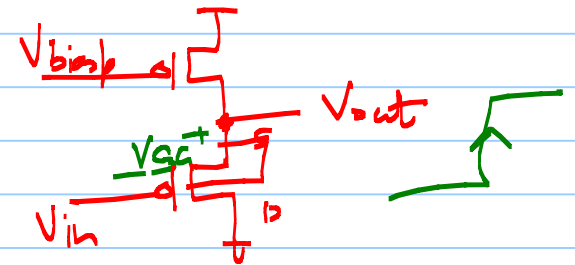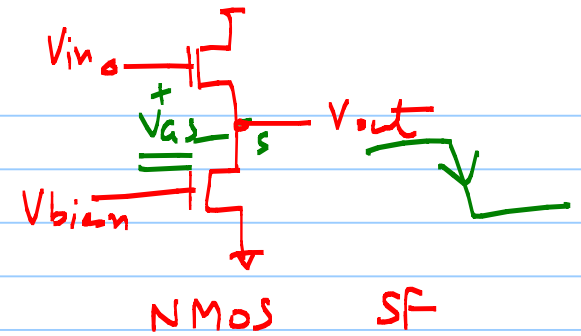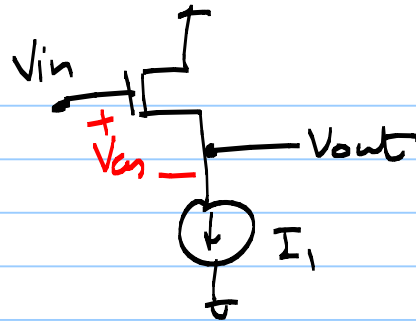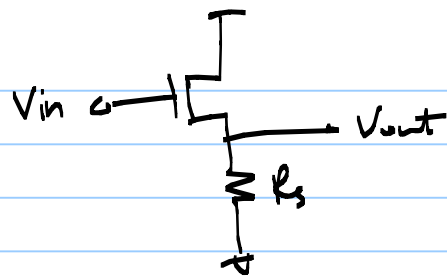$\Rightarrow$ gain monotonically increases with $V_{in} \Rightarrow g_m \uparrow \Rightarrow g_m R_s \uparrow$
 gain $\rightarrow \frac{1}{\eta+1} \gtrsim 1.0$



PMOS SF
"Level-shifting"

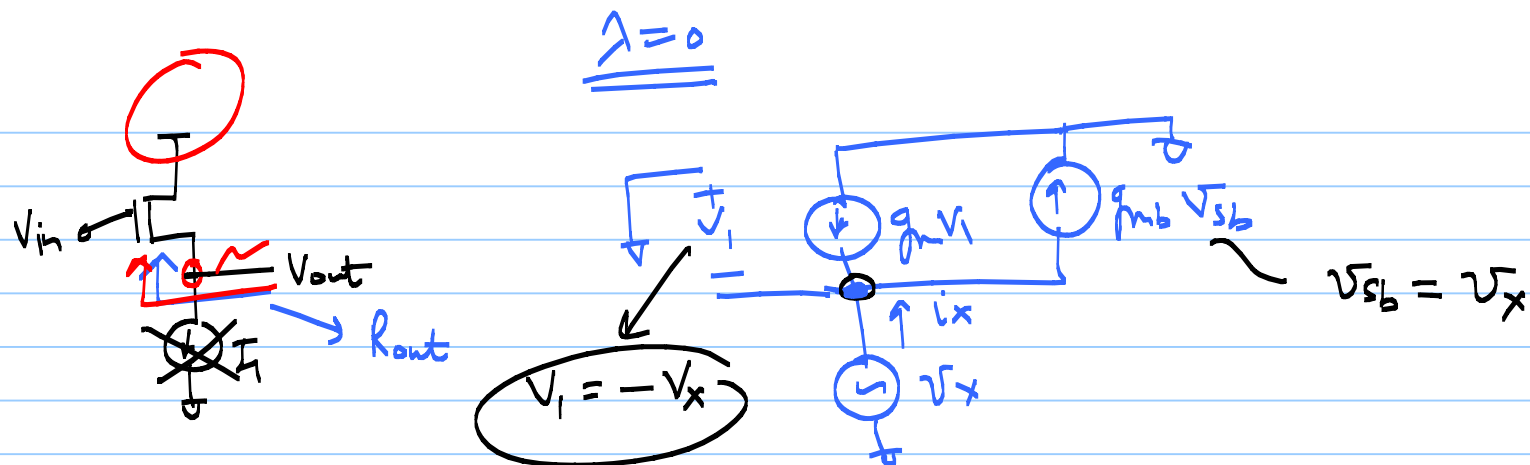


$$i_x + g_m V_1 - g_{mb} V_x = 0$$

$$\Rightarrow i_x - g_m V_x - g_{mb} V_x = 0$$

$$R_{out} = \frac{V_x}{i_x} = \frac{1}{g_m + g_{mb}} = \frac{1}{g_m (\eta + 1)}$$

$\Rightarrow$ Low- Z output from a SF.

Digression

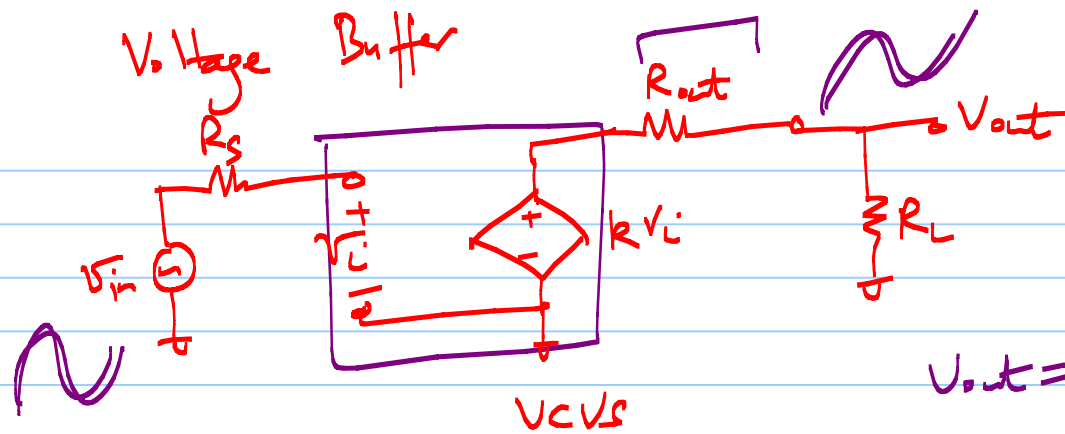

$$V_{out} = \frac{k v_i \cdot R_L}{R_L + R_{out}}$$

$$\underline{\underline{k=1}}$$

⇒ for good quality VB, we want $R_{out} \rightarrow 0$