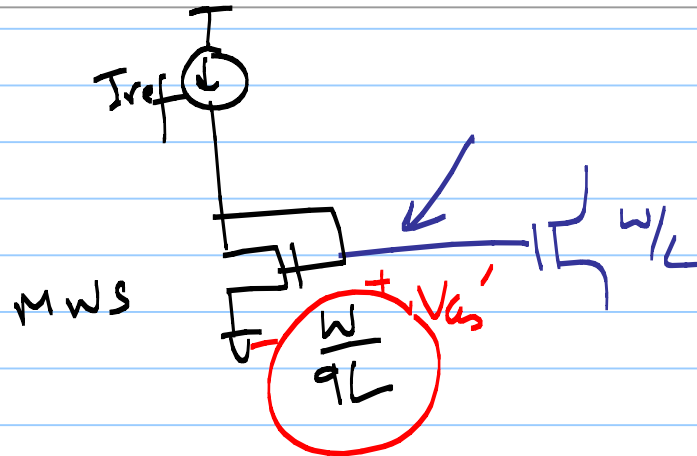


ECE 5411 - Lecture 14.


Note Title

3/14/2011




$$V_{gs}' = \sqrt{\frac{2I_D}{\beta'}} + V_{THN}$$
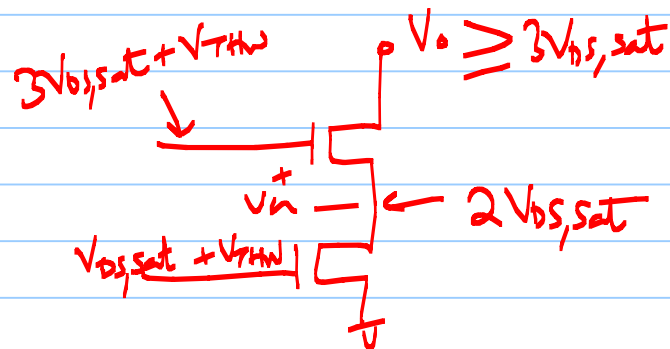
$$= \sqrt{\frac{2I_D}{\beta/g}} + V_{THN}$$



$$= 3 \left[\sqrt{\frac{2I}{\beta}} + V_{THN} \right] V_{DS,sat}$$




$$= \underline{3 V_{DS,sat} + V_{THN}}$$

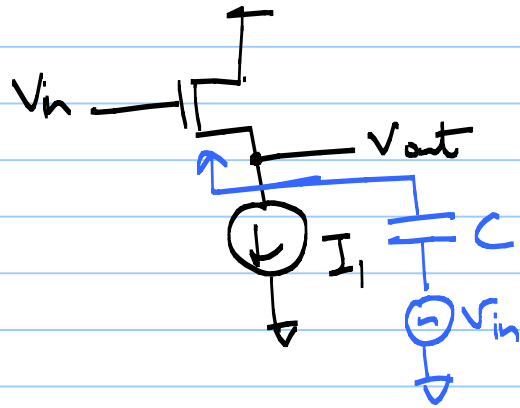


$$A_v = ? =$$

$$R_{out} = ?$$

$$\lambda = 0$$

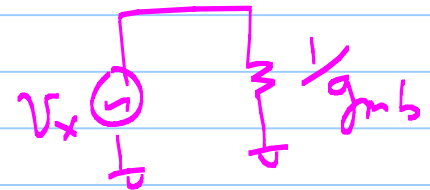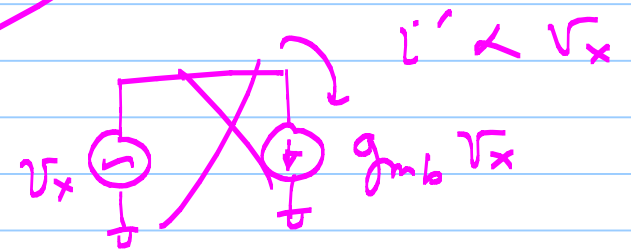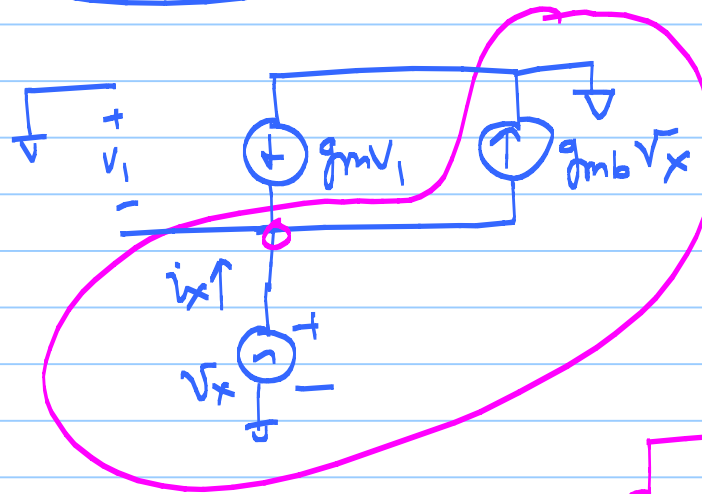

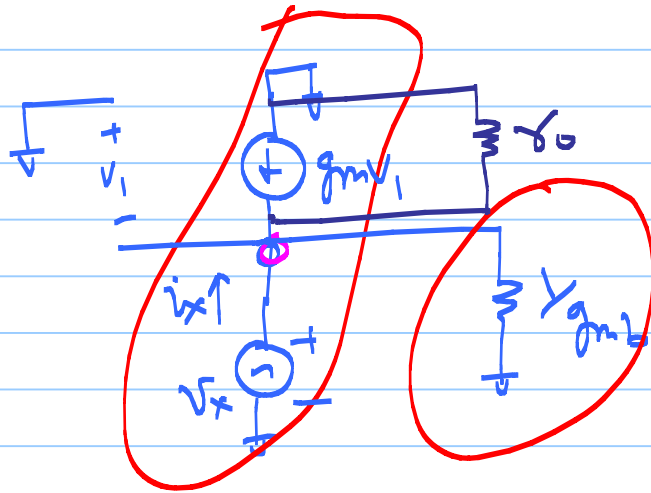

* Low-impedance output



$$i_x + g_m v_1 - g_{mb} v_x = 0$$

$$i_x = (g_m + g_{mb}) v_x$$

$$R_o = \frac{v_x}{i_x} = \frac{1}{g_m + g_{mb}} = \frac{1}{\frac{1}{g_m} \parallel \frac{1}{g_{mb}}}$$

$$R_o = \frac{1}{g_m + g_{mb} + 1/r_o} = \frac{1}{\frac{1}{g_m} \parallel \frac{1}{g_{mb}} \parallel r_o}$$

$$\frac{1}{g_m} \ll r_o$$

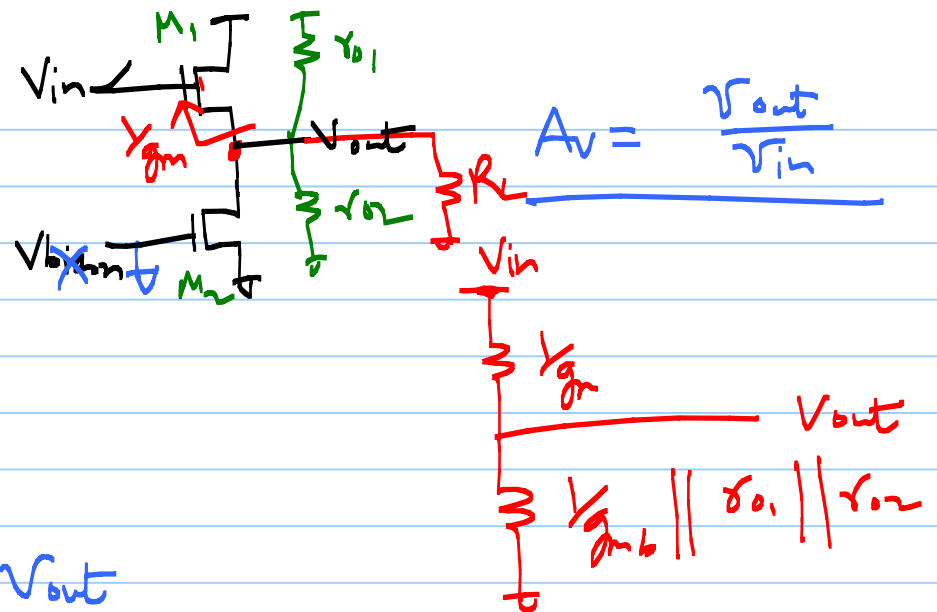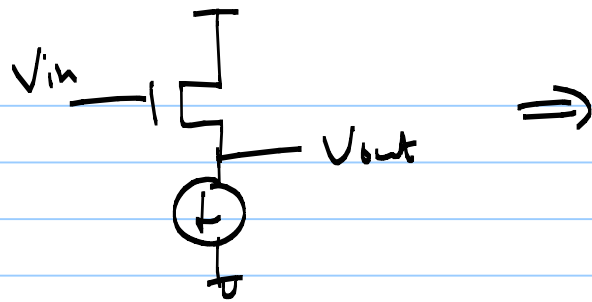


$$A_v = \frac{V_{out}}{V_{in}} = \frac{\frac{1}{g_m} \parallel r_{o1} \parallel r_{o2}}{\frac{1}{g_m} + \frac{1}{g_m} \parallel r_{o1} \parallel r_{o2}} =$$

$$A_v = \frac{\text{Resistance connected to the source}}{\text{Resistance looking into } + \quad (\checkmark) \text{ the source}}$$

→ resistance divider


$$\left. \begin{aligned} A &\leq 1 \\ R_o &\rightarrow \text{low} \\ R_{in} &\rightarrow \text{high} \end{aligned} \right\}$$

Voltage Buffer

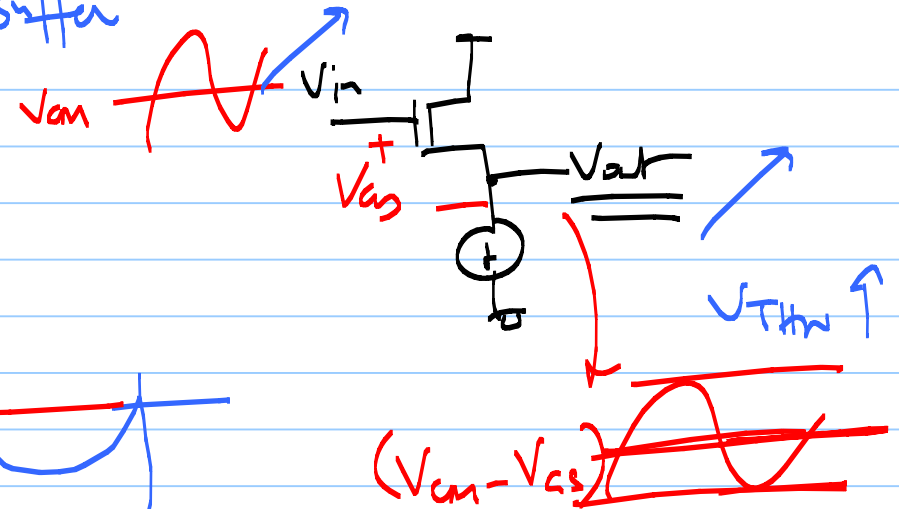


Issues:

① Body

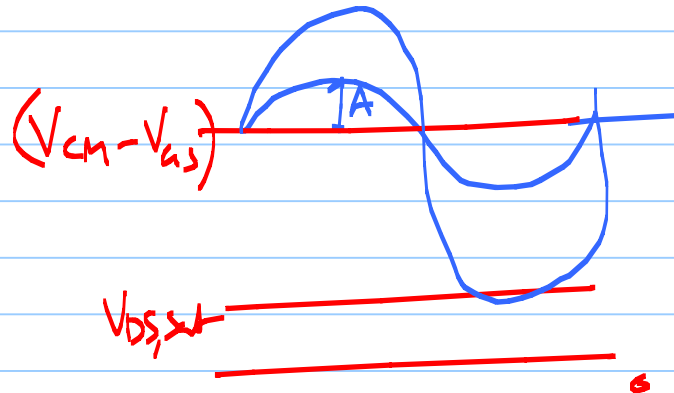





② Shift in DC value

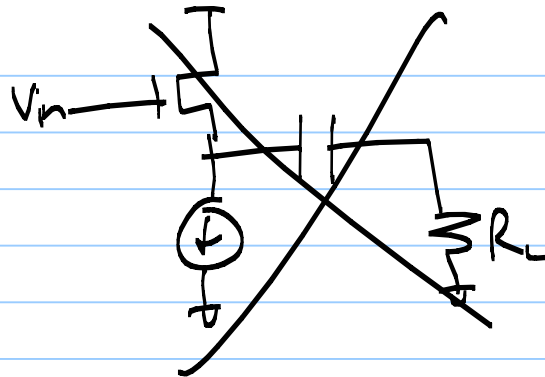
③ Loading $\Rightarrow A_v = \frac{\frac{1}{g_{mb}} \parallel r_{o1} \parallel r_{o2} \parallel R_L}{\frac{1}{g_m} + \frac{1}{g_{mb}} \parallel r_{o1} \parallel r_{o2} \parallel R_L} \approx \frac{R_L}{\frac{1}{g_m} + R_L}$



$\Rightarrow$ for low R_L , A_v can drop significantly.
 $\downarrow$
 $R_L \sim \frac{1}{g_m}$

Example:

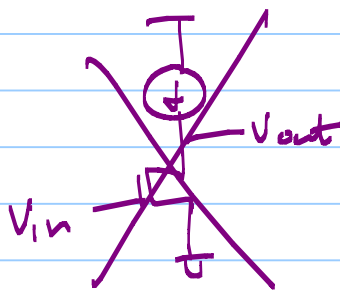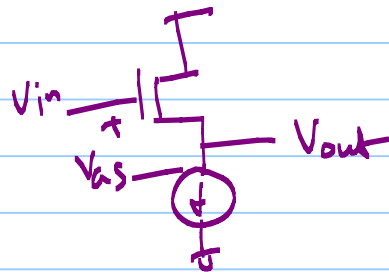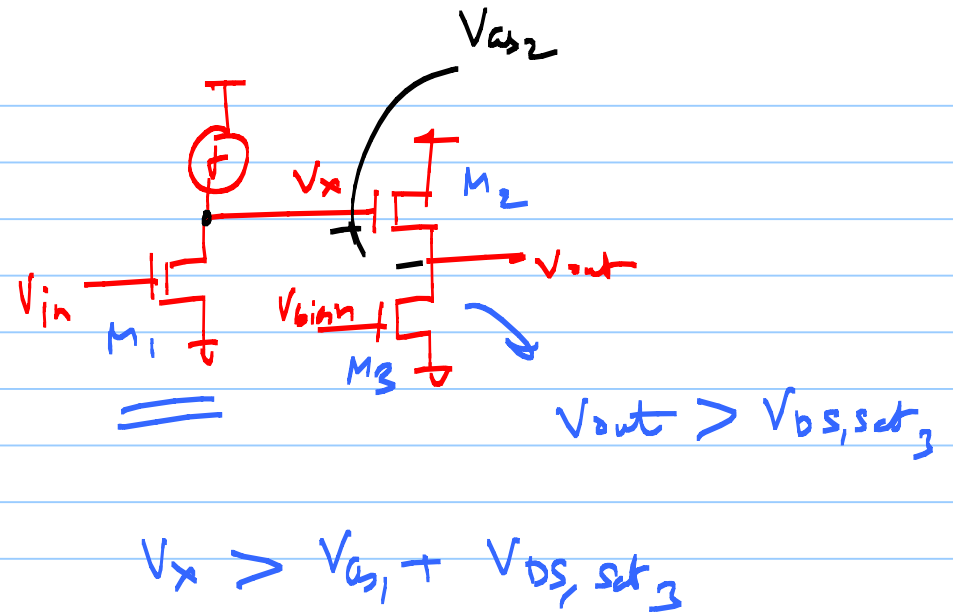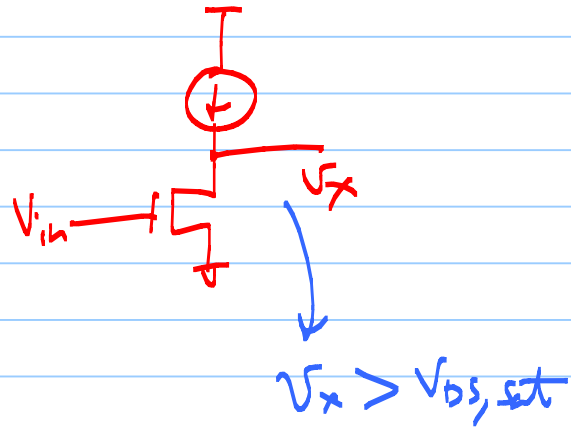

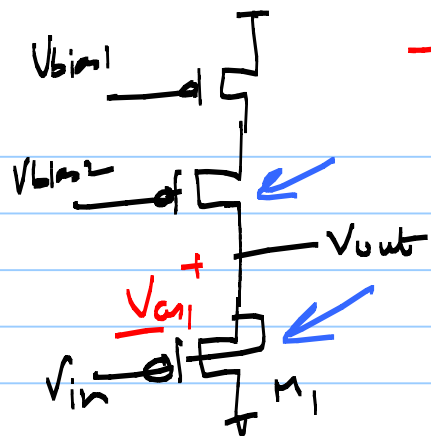

Level Shifter Example

$$V_{out} = V_{in} + V_{SG1}$$

for M_1 to be saturation

$$V_{out} = V_{DS} \geq V_{SG} - V_{THP}$$

$$\Rightarrow V_{out} \geq (V_{out} - V_{in}) - V_{THP}$$

$\Rightarrow$

$$\boxed{V_{in} \geq -V_{THP}}$$

$$V_{out} < V_{DD} - 2V_{SD,sat}$$


$$V_{in} + V_{SG}$$

$\Rightarrow$


$$\boxed{V_{in} < V_{DD} - 2V_{SD,sat} - V_{SG}}$$

Current mirror in saturation

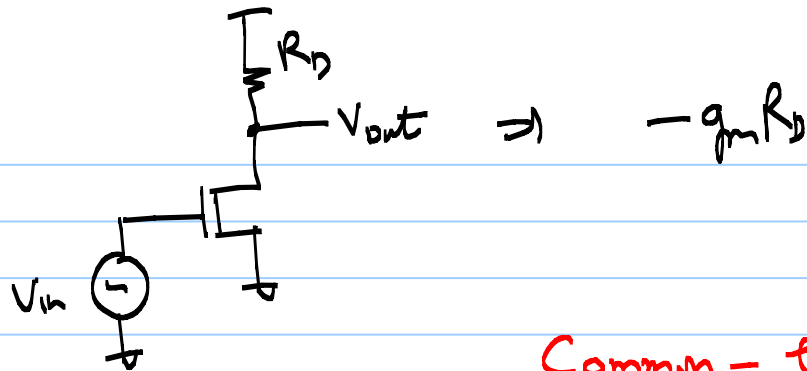
$$-V_{THP} \leq V_{in} \leq V_{DD} - 2V_{SD,sat} - V_{SC}$$




Common-gate Amplifier/Stage

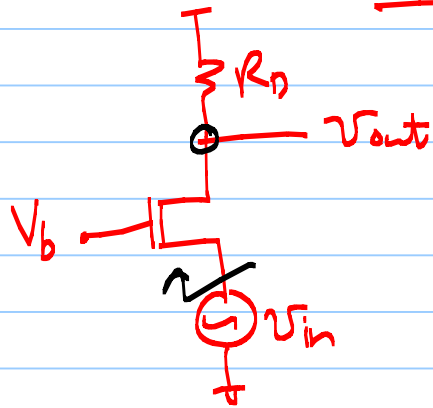



Direct coupling

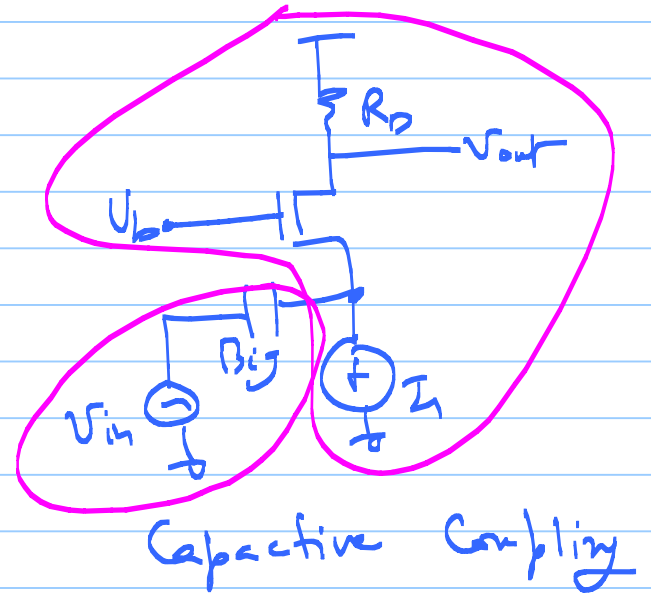

Capacitive coupling.

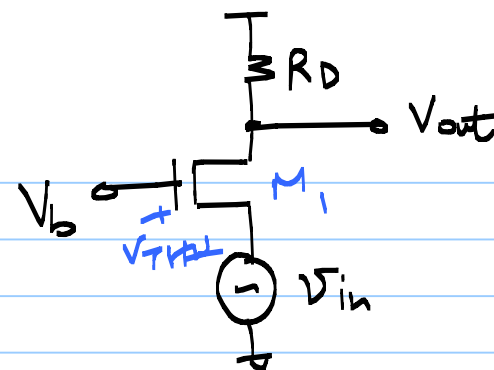

$$V_{DD} > V_b$$

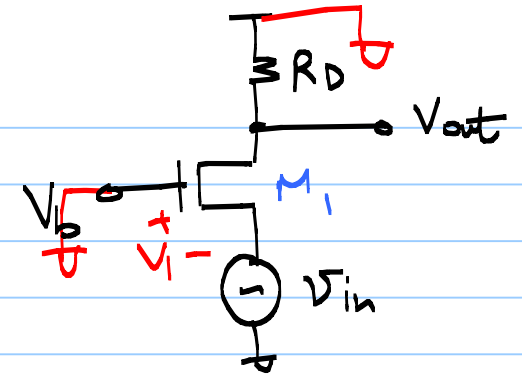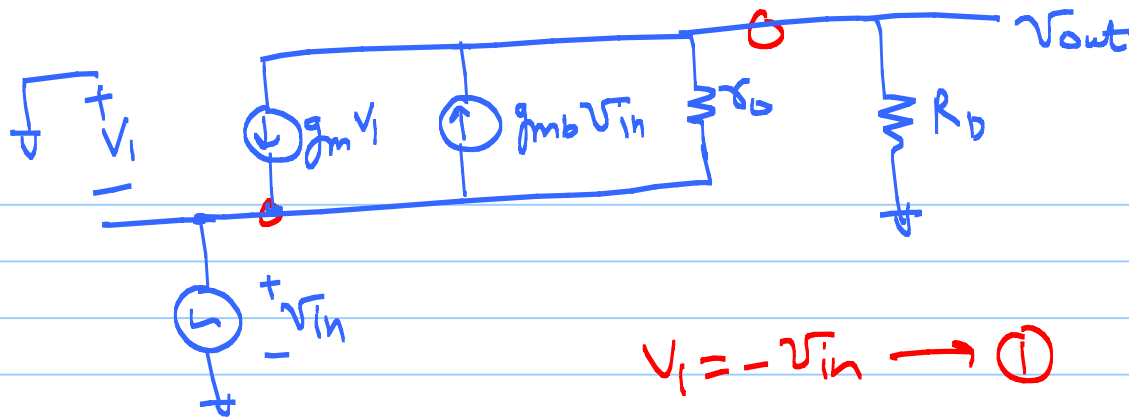

KCL:

$$-g_m v_1 + g_{mb} v_{in} - \frac{(v_{out} - v_{in})}{r_o} - \frac{v_{out}}{R_D} = 0$$

$$A_v = \frac{v_{out}}{v_{in}} = [(g_m + g_{mb}) + \frac{1}{r_o}] \times (R_D \parallel r_o)$$

$$\approx (g_m + g_{mb}) R_D$$

$$R_D \ll r_o$$



$$r_o \gg \frac{1}{g_m}$$

$$= (1+\mu) g_m R_D$$

* Body effect effectively increases g_m .

* Gain is +ve

Input impedance

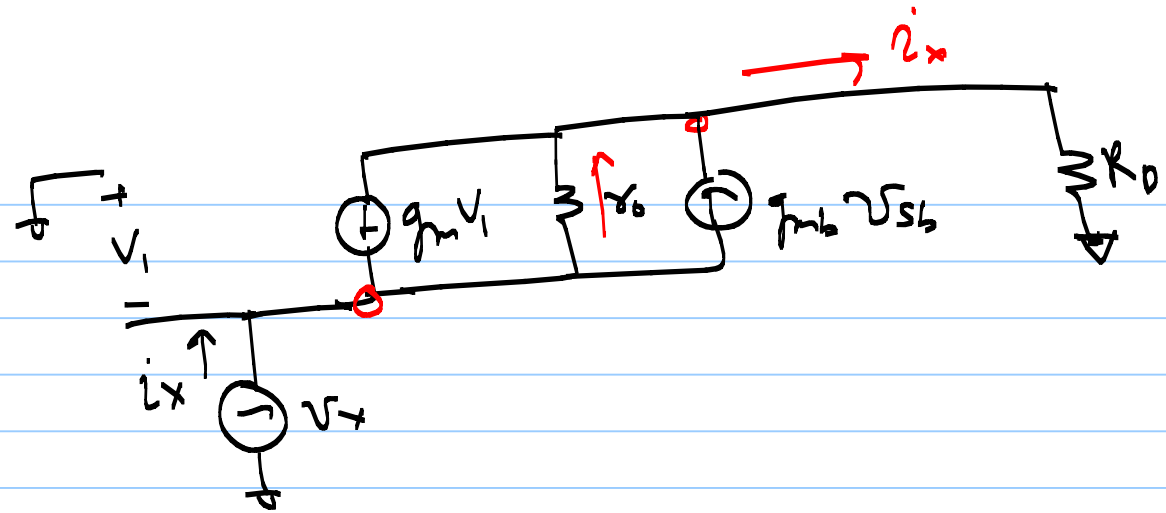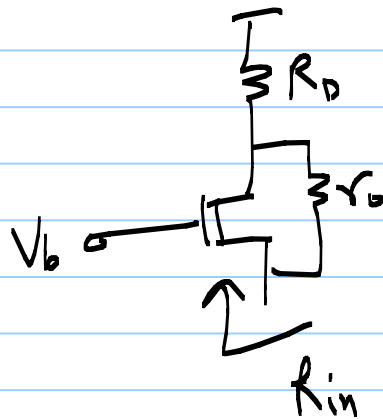

$$V_1 = -V_x$$

$$\Rightarrow \text{current through } r_o \Rightarrow i_x + g_m V_1 + g_{mb} V_1$$

$$= i_x - (g_m + g_{mb}) V_x$$

$\Rightarrow$ Adding up the voltages across r_o and R_D

$$R_D i_x + r_o (i_x - (g_m + g_{mb}) V_x) = V_x$$

$$\Rightarrow R_{in} = \frac{v_x}{i_x} = \frac{R_D + r_o}{1 + (g_m + g_{mb}) r_o}$$

$$\approx \frac{R_D}{\underbrace{(g_m + g_{mb}) r_o}} + \frac{1}{(g_m + g_{mb})}$$

* if $(g_m + g_{mb}) r_o \gg R_D \leftarrow R_D$ is low impedance

$$R_{in} \approx \frac{1}{g_m + g_{mb}}$$

* $R_D = g_{m2} r_{o2}^2$

$$\Rightarrow R_{in} = \frac{\cancel{g_{m2} r_{o2}^2} \cancel{r_{o1}}}{\cancel{(g_{m1} + g_{mb1}) r_{o1}}} + \frac{1}{(g_{m1} + g_{mb1})}$$

lets say
 $g_{m1} r_{o1} \approx g_{m2} r_{o2}$


$$\approx r_{o2} + \underbrace{\frac{1}{g_{m1}}}_{\text{if } R_D = r_o}$$

Special cases


① $R_D = 0$

$$R_{in} \approx \frac{R_D}{(g_m + g_{mb})R_D} + \frac{1}{(g_m + g_{mb})}$$

$$\approx \frac{1}{(g_m + g_{mb})}$$

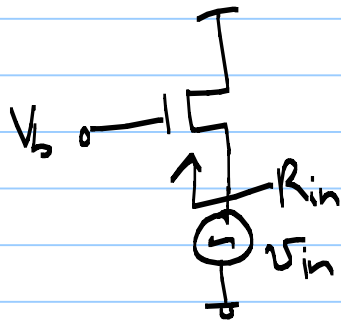

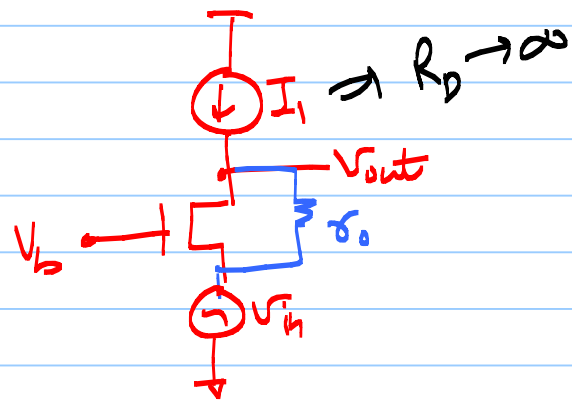② r_D is replaced by an ideal current source




$$R_{in} \rightarrow \infty$$


$$A_v = \frac{(g_m + g_{mb})r_o + 1}{r_o + (g_m + g_{mb})r_o R_s + R_s + R_D} \cdot R_D$$

$$R_D \rightarrow \infty$$
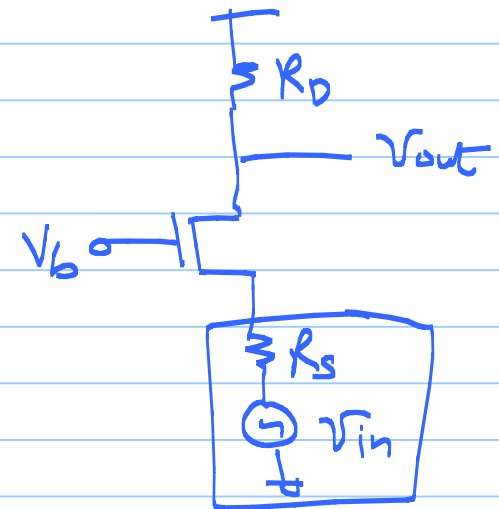
$$= A_v \approx (g_m + g_{mb})r_o + 1 \approx g_m r_o$$



Output impedance of CC stage

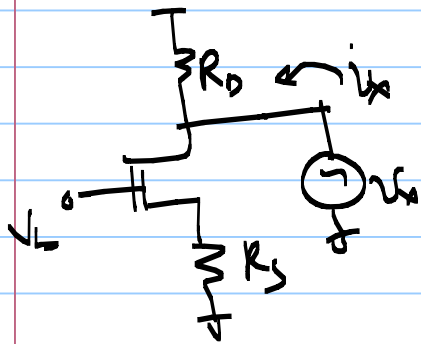

$$R_{out} = \left\{ \left[1 + (g_m + g_{m_e}) r_o \right] R_s + r_o \right\} \parallel R_D$$

→ same as CS with source degeneration