

ECE 5411 - Lecture 15.


Note Title

3/16/2011


Low frequency

Amplifier Stage	Gain	Z_{in}	Z_{out}	Application
CS	Large	∞	Moderate	Large Gain Amplifier
CS + SD	Moderate	∞	High	Linear, moderate Gain Amplifier (VGA)
CD / "SF"	Low (< 1)	∞	Low	Voltage Buffer (VBS, $A < 1$)
CG	Moderate / High	Low (moderate)	moderate / High	Current Buffer


* Voltage Buffer

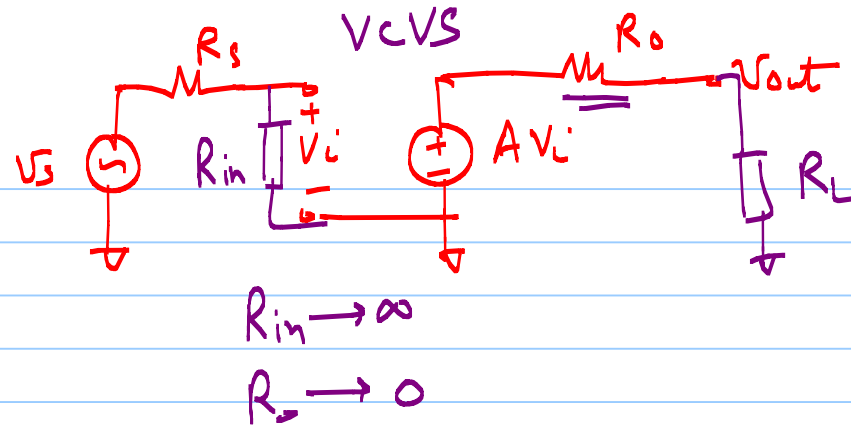

* Current Buffer

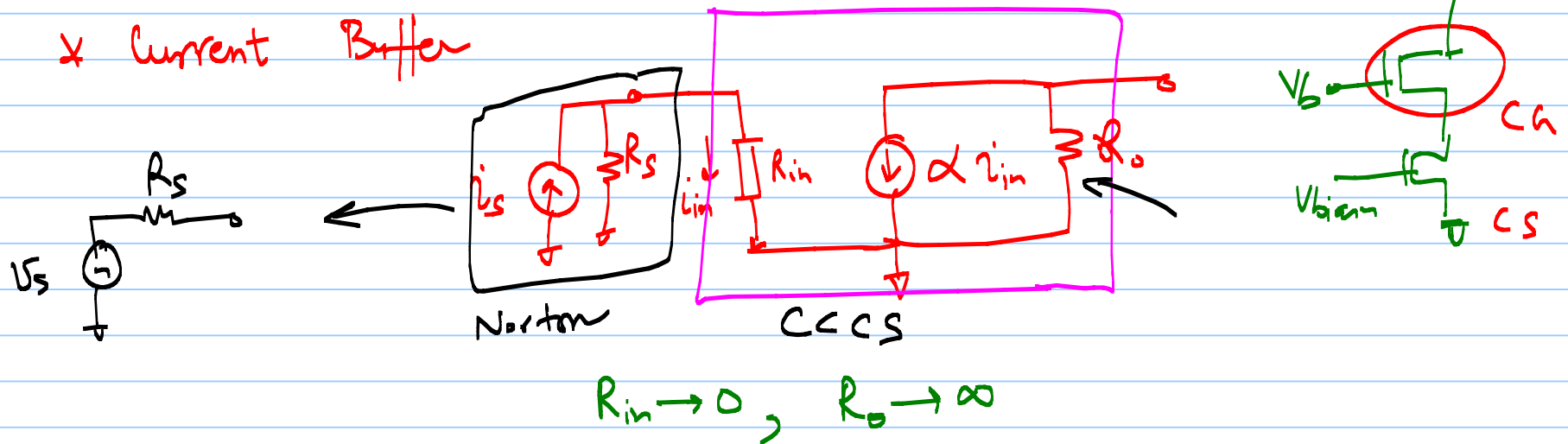


AC $\lambda \approx 0$

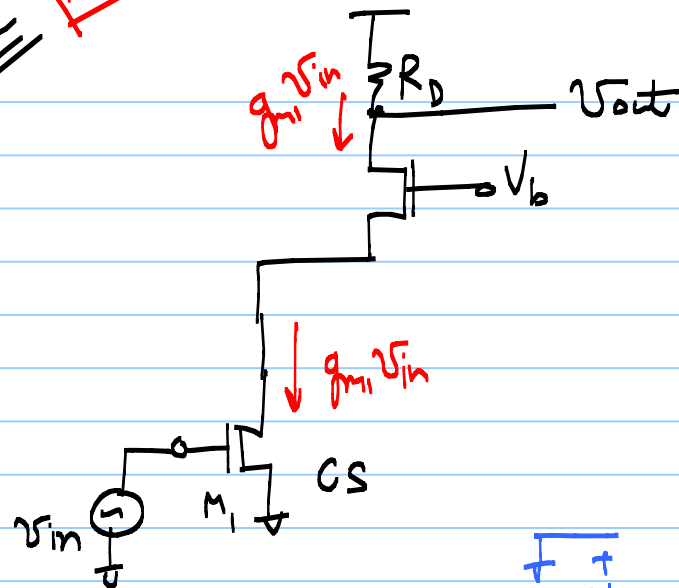

$(CS \Rightarrow)$ Converts v_{in} into
ac current $g_{m1} v_{in}$

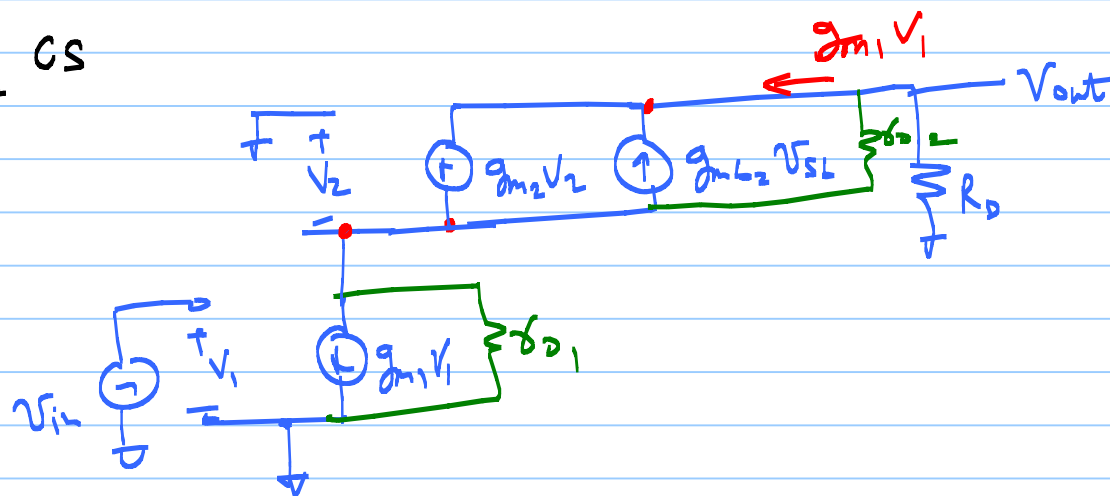$(C \Rightarrow)$ relaying this current
to R_D




Theorem: In a linear circuit, voltage gain = $-\frac{e}{g_m} R_{out}$


where,

$e \rightarrow$ denotes the electromotive force of the circuit when the output is shorted to ground.

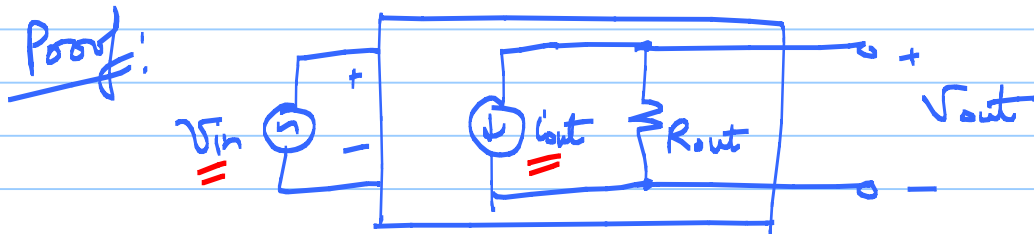$R_{out} \rightarrow$ output resistance of the circuit when the input is at zero.




ps

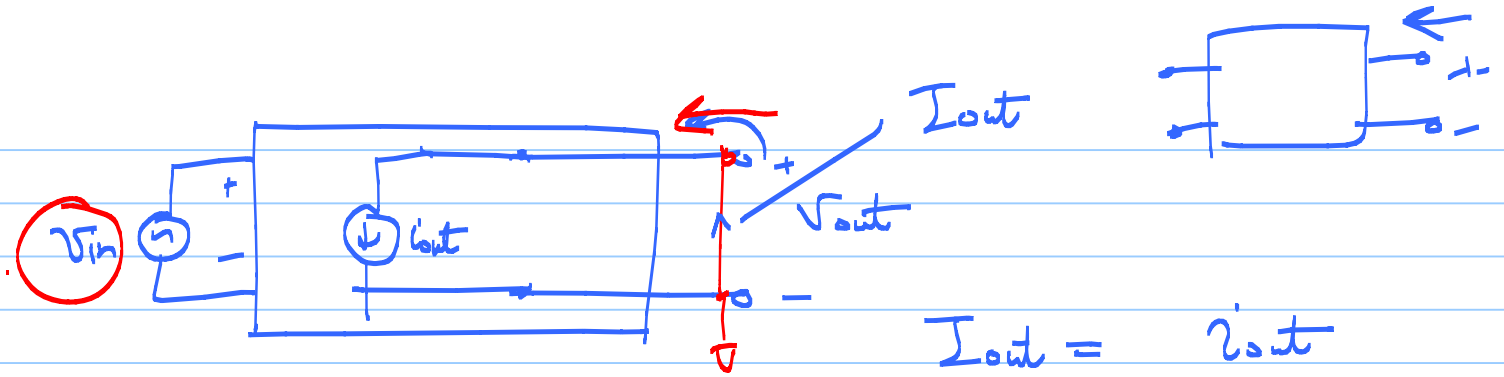


$$g_m = \frac{I_{out}}{V_{in}}$$


$$V_{out} = -g_m V_{in} R_{out}$$
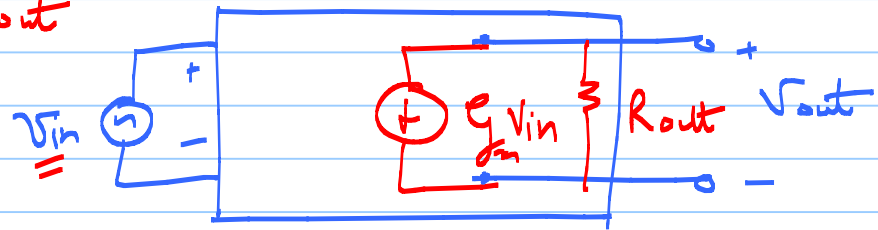
$$A_v = \frac{V_{out}}{V_{in}} = \boxed{-g_m R_{out}}$$



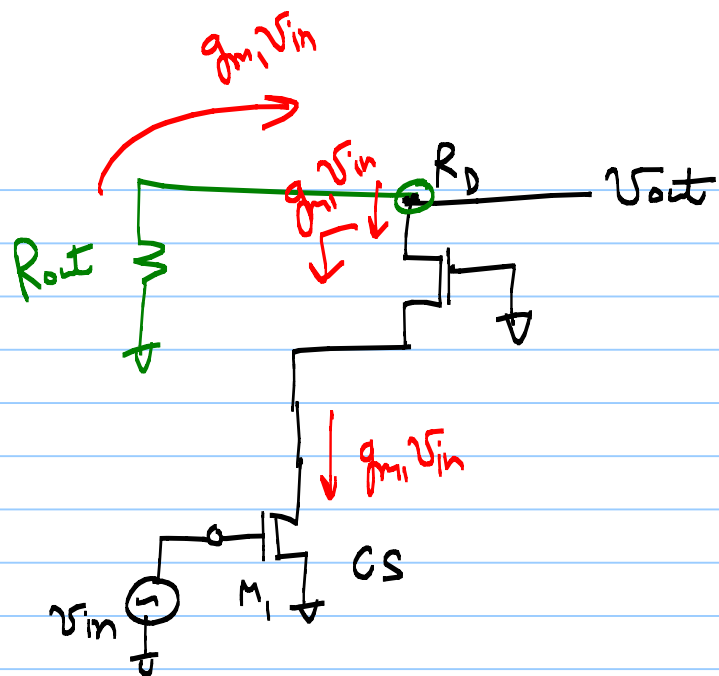
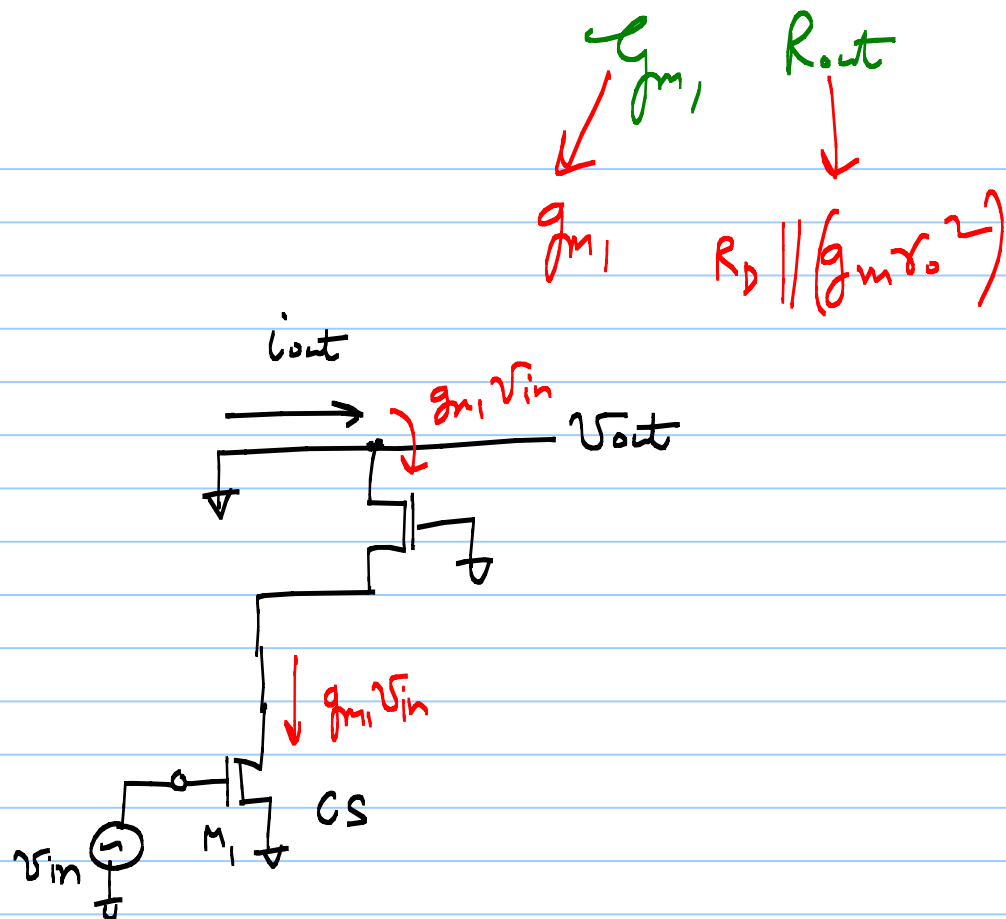
$$A_v = -g_{m1} \cdot (R_D \parallel g_{m1}r_{o2}^2)$$



$$g_m = \frac{g_{m1} r_{o1} [r_{o2} (g_{m2} + g_{m2b}) + 1]}{r_{o1} r_{o2} (g_{m2} + g_{m2b}) + r_{o1} + r_{o2}}$$

$$\xrightarrow{g_{m2} r_{o2} \gg 1} = \frac{g_{m1} \cancel{r_{o1}} \left[\frac{\cancel{g_{m2} r_{o2} + 1}}{g_{m2} r_{o2}} \right]}{\cancel{r_{o1}} + \frac{r_{o1} + r_{o2}}{\cancel{g_{m2} r_{o2}}}} \approx g_{m1}$$

$$R_{cas} = [1 + (g_{m2} + g_{m2b}) r_{o2}] r_{o1} + r_{o2}$$

$$\approx (g_{m2} + g_{m2b}) r_{o2} r_{o1} \approx g_{m2} r_{o2} r_{o1}$$

odd-order harmonics


$$i_A = g_{m1} v_{gs} + \cancel{g_{m3} v_{gs}^3}$$

Volterra Series
Analysis

$$A_v = -g_m R_{out} = -g_{m1} (R_{cm} \parallel R_D)$$

$$= -g_{m1} (g_{m2} r_{o2} r_{o1}) \text{ if } R_D \rightarrow \infty$$

*

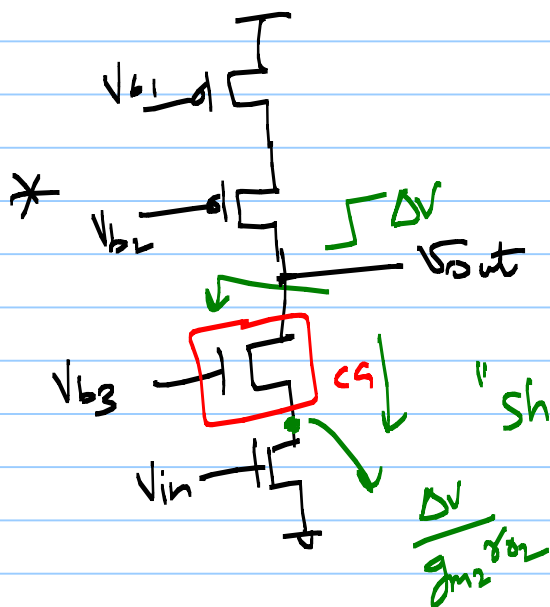

$$A_v = -g_{m1} \cdot R_{cm} \parallel R_{cap}$$

$$g_{m1} r_{o1}^2$$



$$g_{m2} r_{o2}^2$$

CC shields the drain of CS

↳ large R_{out}

$$R_o = (g_{m2} r_{o2}) r_{o1}$$


* current steering
DAC's

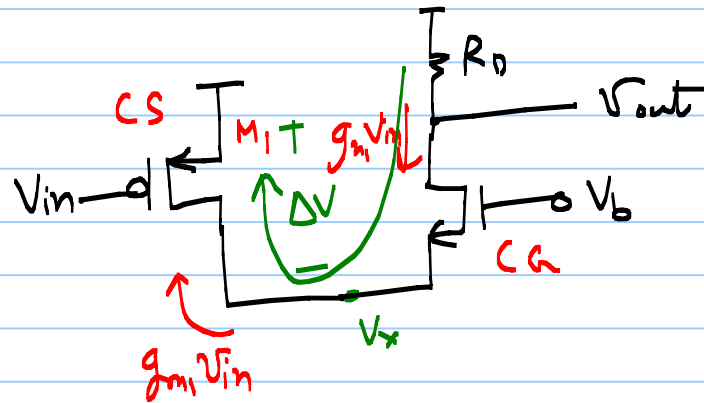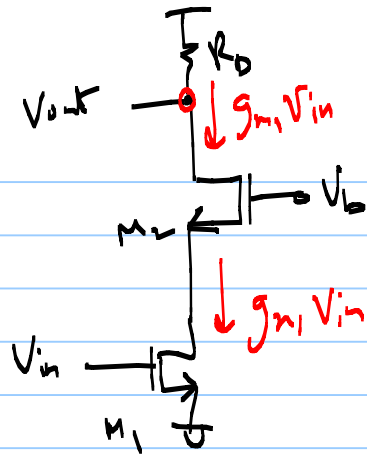


"Folded-Cascode"

[PMOS $\rightarrow$ CS
NMOS $\rightarrow$ CG]

performs the same
function as a
Cascode.

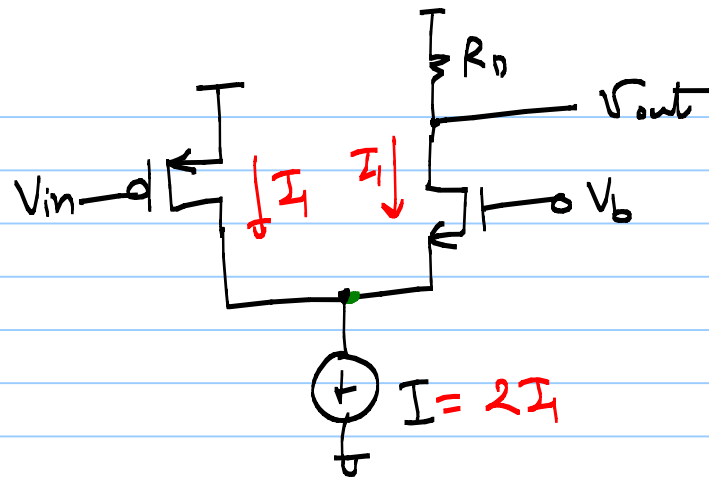


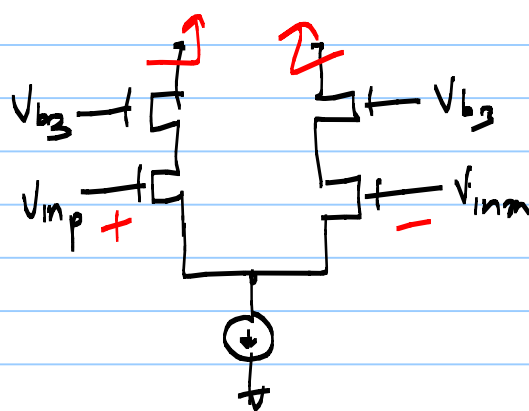x 2x bias current
 x better headroom
 with cascoded gain



NMOS half
 Telescopic diffamp.

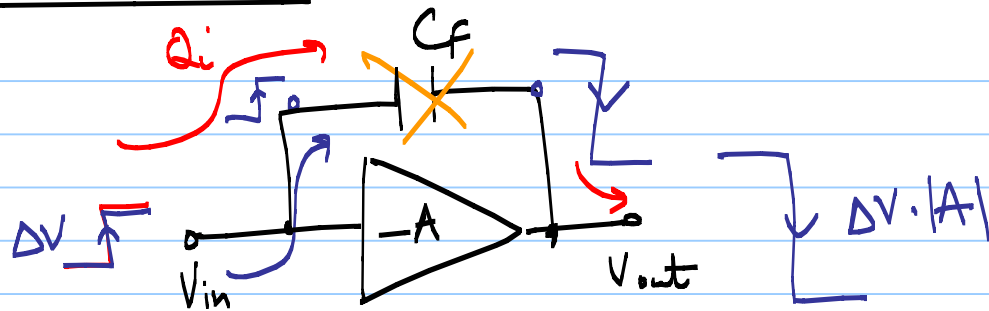Miller Effect (Capacitance multiplying effect)



$$A \gg 1$$


Net voltage change

across C_f

$$\Rightarrow (1 + |A|) \Delta V$$


$$\Rightarrow Q = C_f (1 + |A|) \Delta V$$

$$C_{in} = C_f (1 + |A|)$$

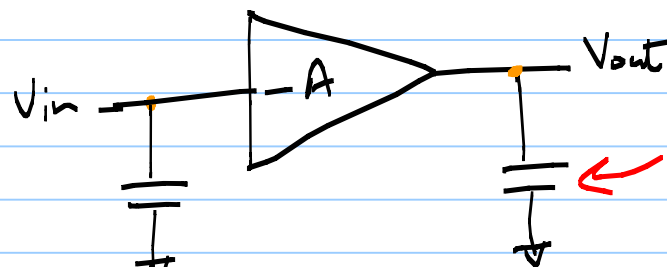

$$C_f (1 + |A|)$$

$$C_f (1 + \frac{1}{|A|})$$

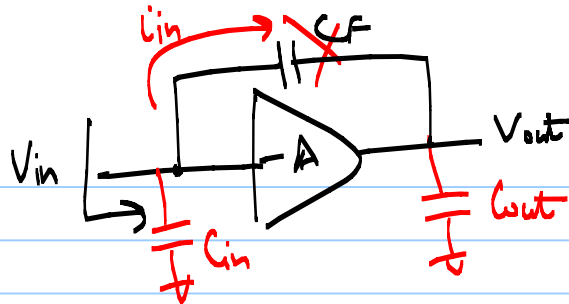

$$\begin{aligned}
 i_{in} &= \frac{V_{in} - V_{out}}{1/sC_f} = sC_f (V_{in} - V_{out}) \\
 &= sC_f (V_{in} - (-AV_{in})) \\
 &= sC_f V_{in} (1+A)
 \end{aligned}$$

$$|A| = A > 0$$

$$Z_{in} = \frac{V_{in}}{i_{in}} = \left[\underline{sC_f(1+A)} \right]^{-1} = \underline{\left[sC_{in} \right]^{-1}}$$

$C_{in} = C_f (1+|A|)$

$$\begin{aligned}
 i_{out} = -i_{in} &= -sC_f (v_{in} - v_{out}) \\
 &= sC_f \left(\frac{1}{|A_1|} + 1 \right) v_{out}
 \end{aligned}$$

$$\Rightarrow Z_{out} = \frac{v_{out}}{i_{out}} = \left[sC_f \left(1 + \frac{1}{|A_1|} \right) \right]^{-1} = \left[sC_{out} \right]^{-1}$$

$$C_{out} = \left(1 + \frac{1}{|A_1|} \right) C_f \approx C_f$$