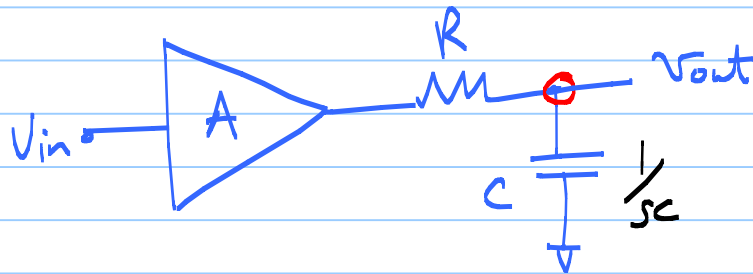


ECE 5411 - Lecture 16.


Note Title


3/21/2011



$$\frac{v_{out}}{v_{in}}(s) = \frac{A}{1 + sRC} = \frac{A}{1 + s/\omega_p}$$

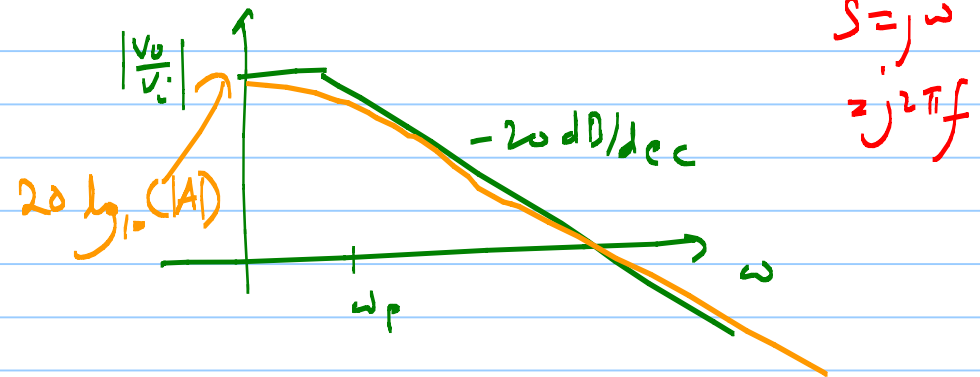
$$\omega_p = \frac{1}{RC} = \frac{1}{\tau}$$



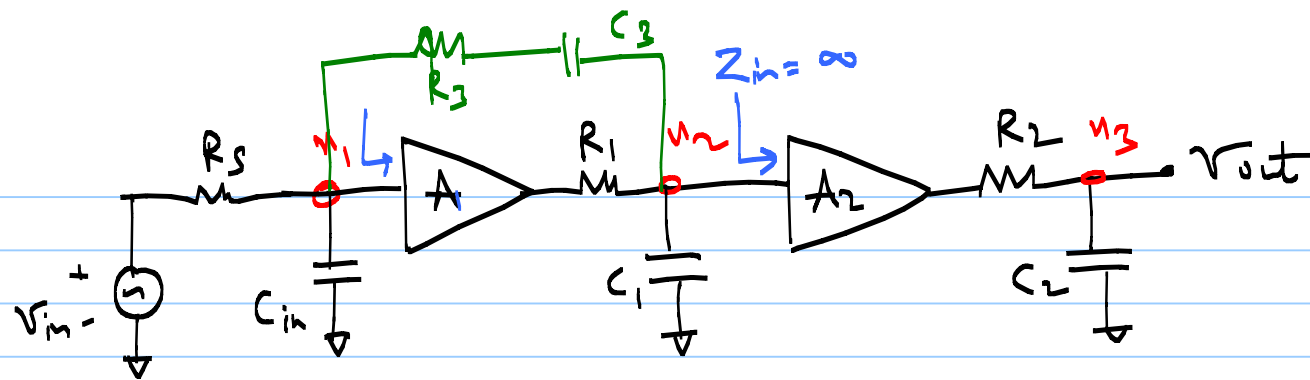


$$\frac{V_{out}}{V_{in}}(s) = \frac{1}{1 + s \underbrace{R_S C_{in}}_{\tau_1}} \cdot \frac{A_1}{1 + s \underbrace{R_1 C_1}_{\tau_2}} \cdot \frac{A_2}{1 + s \underbrace{R_2 C_2}_{\tau_3}}$$

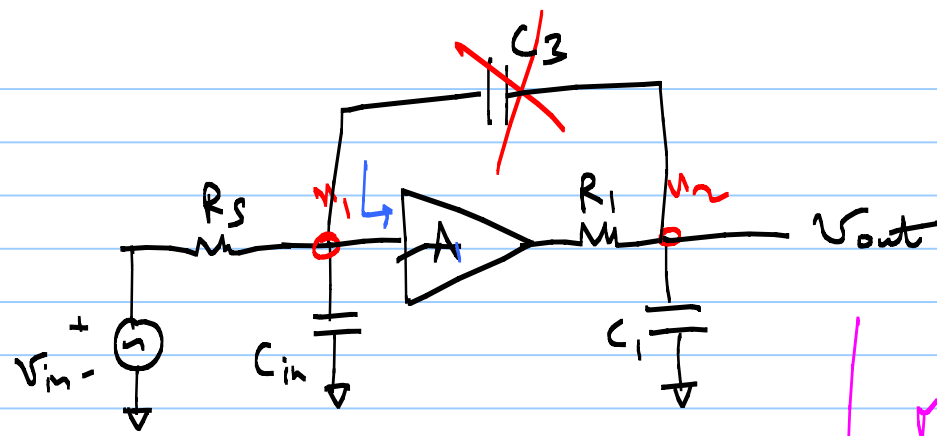← All poles in a circuit are contributed by all the nodes.






Miller transformation

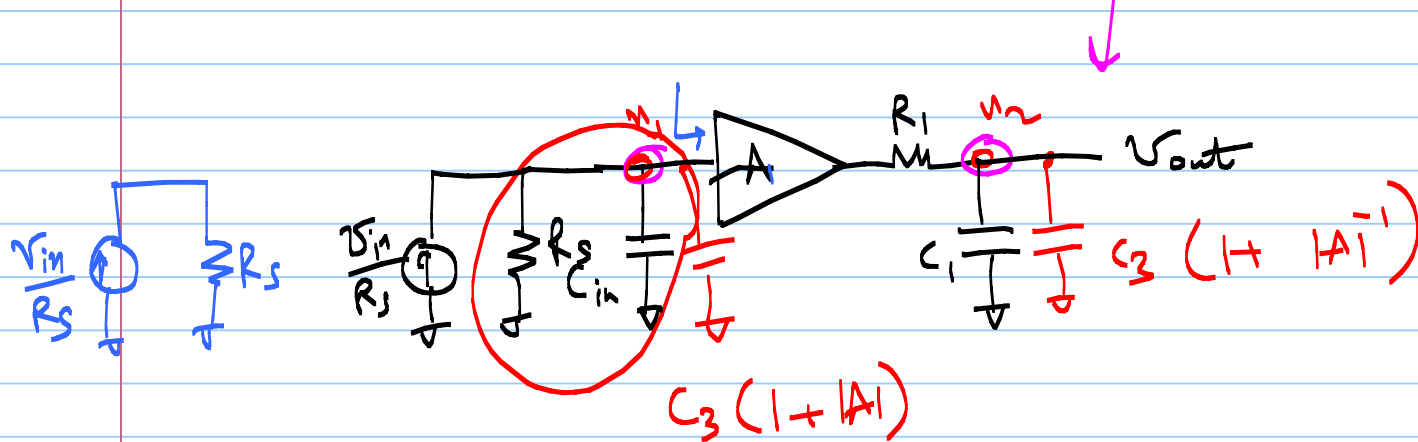


$$\omega_{in} = \frac{1}{R_s [C_{in} + C_3(1+|A|)]}$$

$$\omega_{out} = \frac{1}{R_f (C_1 + C_3)}$$

are
devices in saturation
r

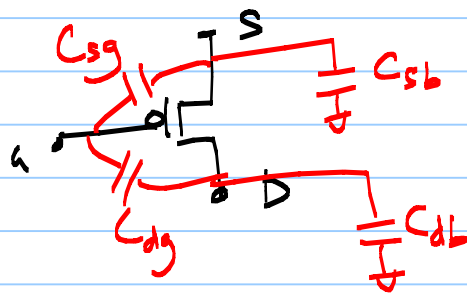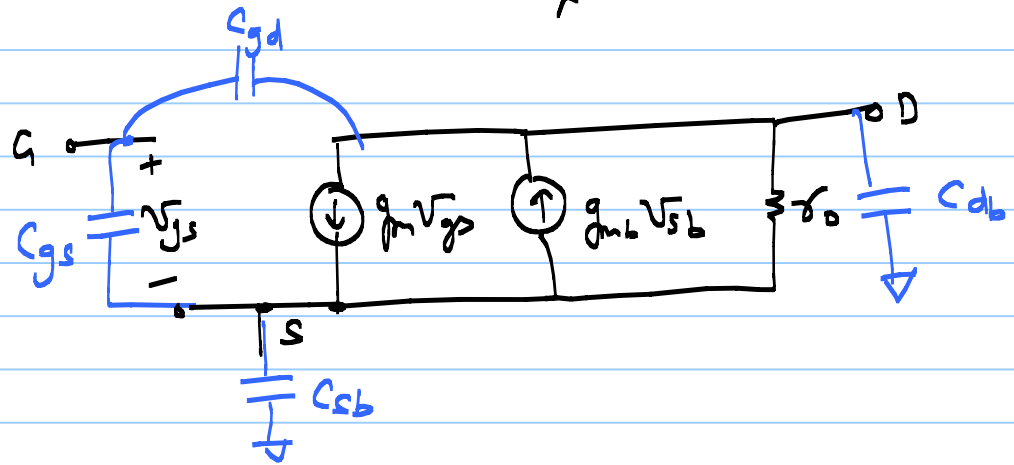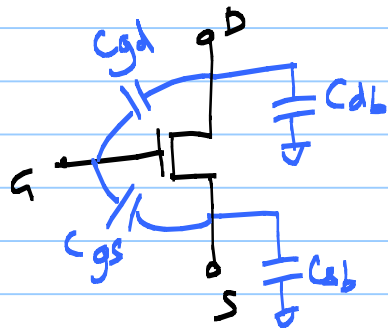


CS Stage

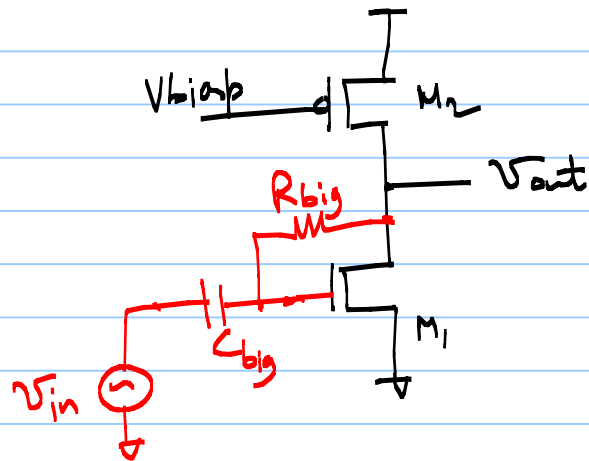

$$\omega_{DC} = \frac{1}{R_{big} C_{big}} \ll \omega_{in}$$

As picture

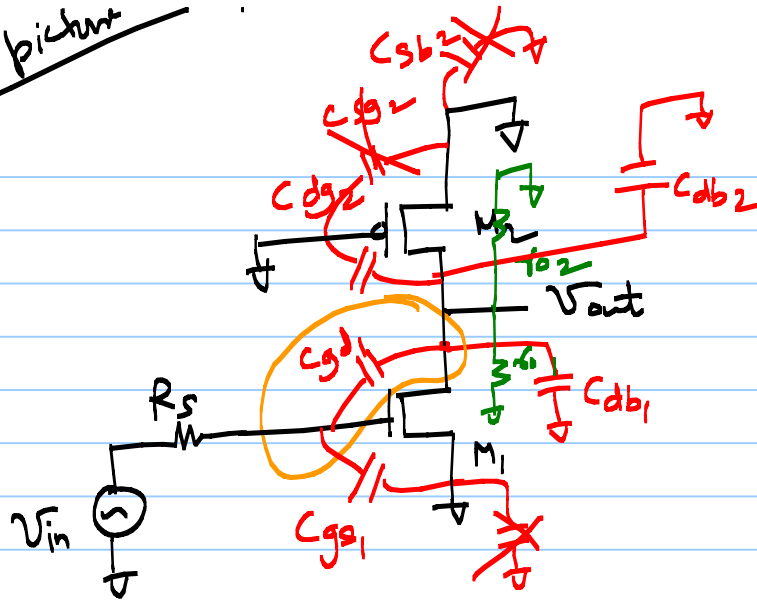


$$A_v = -g_{m1} (r_{o1} \parallel r_{o2}) \quad \text{Low-freq gain}$$

"Grounded Caps"

$C_{gs1}, C_{db1}, C_{gd2}, C_{db2}$

$C_{gd1} \Rightarrow$ between input and output

Approach 2

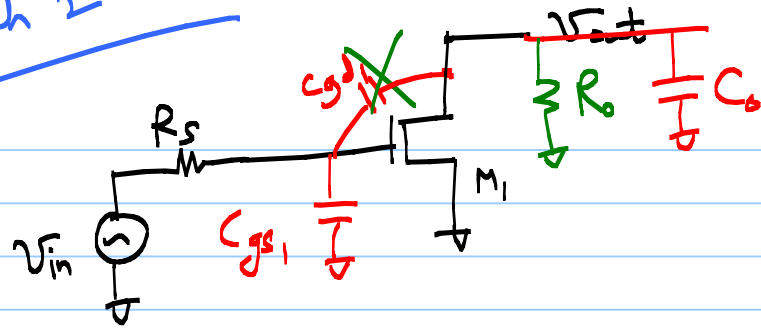


$$C_{db} = C_{db1} + C_{db2}$$

$$R_o = r_{o1} \parallel r_{o2}$$

$$C_o = C_{db} + C_{dg2}$$

$$|A| = g_{m1}(r_{o1} \parallel r_{o2})$$

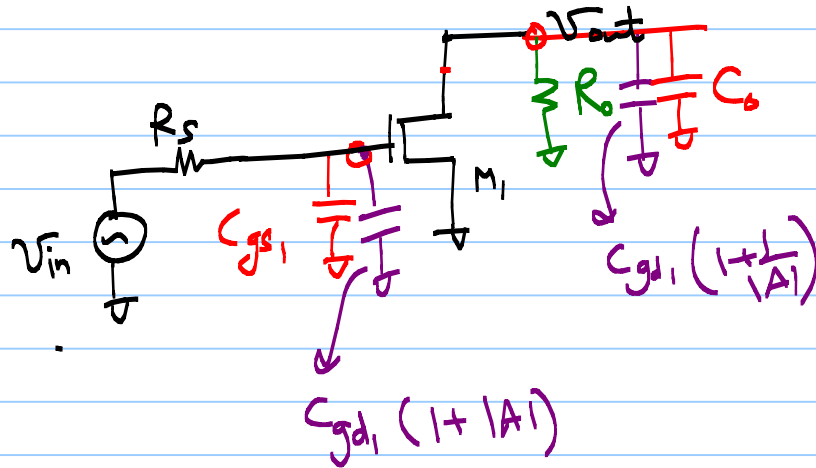

$$\omega_{in} = \frac{\text{poles}}{R_s [C_{gs1} + (1 + |A|) C_{gd1}]}$$

$$\omega_{out} = \frac{1}{R_o C_o} = \frac{1}{(r_{o1} \parallel r_{o2}) [C_{gd1} + C_o]}$$


$$\frac{V_{out}(s)}{V_{in}} = \frac{A_v}{(1 + s/\omega_{in})(1 + s/\omega_{out})}$$

$$f_{in} = \frac{\omega_{in}}{2\pi}$$

$$f_{out} = \frac{\omega_{out}}{2\pi}$$

* Error in estimating the zero location.

Approach 2

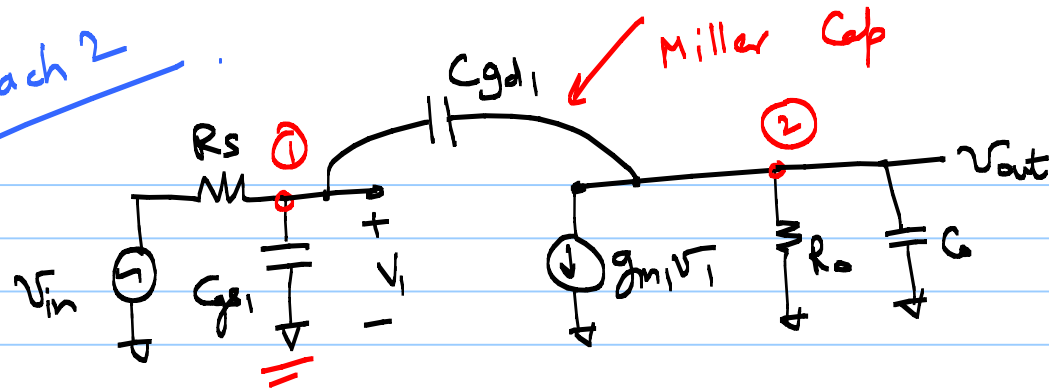

$$R_o = r_{o1} \parallel r_{o2}$$

$$C_o = C_{ab} + C_{dg2}$$

Nodal analysis

$$\textcircled{1} \Rightarrow \frac{V_x - V_{in}}{R_s} + V_x C_{s1} s + (V_x - V_{out}) C_{gd1} s = 0$$

$$\textcircled{2} \Rightarrow (V_{out} - V_x) C_{gd1} s + g_{m1} V_x + V_{out} \left(\frac{1}{R_o} + C_o s \right) = 0$$

Solve for V_x and substitute in $\textcircled{2}$

$$v_x = - \frac{v_{out} (C_{gd} s + \frac{1}{R_o} + s C_o)}{g_{m1} - s C_{gd}}$$

$$\frac{v_{out}}{v_{in}}(s) = \frac{(C_{gd} s - g_{m1}) R_o}{R_s R_o \underbrace{\zeta}_{=} s^2 + [R_s (1 + g_{m1} R_o) C_{gd} + R_s C_{gs} + R_o (C_{gd} + C_o)] s + 1}$$

$$\zeta = C_{gs} C_{gd} + C_{gs} C_o + C_{gd} C_o$$

$$N = (s C_{gd} - g_{m1}) R_o = 0$$

$$\omega_z = \frac{g_{m1}}{C_{gd}}$$

RHP zero

$$f_z = \frac{\omega_z}{2\pi} = \frac{g_{m1}}{2\pi C_{gd}}$$

$$D = \underline{R_S R_O} s^2 + [R_S (1 + g_{m1} R_O) C_{gd1} + R_S C_{gs1} + R_O (C_{gd1} + C_o)] s + 1 \rightarrow (3)$$

Assume that $|\omega_{p1}| \ll |\omega_{p2}| \Rightarrow \frac{1}{|\omega_{p1}|} \gg \frac{1}{|\omega_{p2}|}$

$$D = \left(\frac{s}{\omega_{p1}} + 1 \right) \left(\frac{s}{\omega_{p2}} + 1 \right)$$

$$= \frac{s^2}{\omega_{p1} \omega_{p2}} + \left(\frac{1}{\omega_{p1}} + \frac{1}{\omega_{p2}} \right) s + 1 \rightarrow (4)$$

Coeffⁿ of 's'

$$\omega_{p1} = \frac{1}{R_S (1 + \underbrace{g_{m1} R_O}_{|A|}) C_{gd1} + R_S C_{gs1} + \underbrace{R_O (C_{gd1} + C_o)}}_{\leftarrow \text{Miller gain in } C_{gd1}}$$

with Miller appx. $\Rightarrow \omega_{in} = \frac{1}{R_s C_{gs1} + (1 + |A|) R_s C_{gd1}}$

2nd pole:

$$\omega_{p2} = \frac{1}{\omega_{p1}} \times \frac{1}{R_s R_o}$$

} $\rightarrow \chi_i$
k sai

$$= \frac{1}{\omega_{p1}} \times \frac{1}{R_s R_o [C_{gs1} C_{gd1} + C_{gs1} C_o + C_{gd1} C_o]}$$

$$= \frac{R_s (1 + g_{m1} R_o) C_{gd1} + R_s C_{gs1} + R_o (C_{gd1} + C_o)}{R_s R_o [C_{gs1} C_{gd1} + C_{gs1} C_o + C_{gd1} C_o]}$$

$$\Rightarrow \omega_p = \frac{R_s \cancel{(1 + g_m R_o)} C_{gd1} + \cancel{R_s} C_{gs1} + \cancel{R_o} (C_{gd1} + C_o)}{\cancel{R_s R_o} [C_{gs1} C_{gd1} + C_{gs1} C_o + \cancel{C_{gd1} C_o}]}$$

Assumption

$$* \text{ If } \underline{C_{gs1}} \Rightarrow (1 + g_m R_o) C_{gd1} + \frac{R_o}{R_s} (C_{gd1} + C_o)$$

↳ Miller Cap is very small compared to C_{gs1}

$$\omega_p \approx \frac{1}{R_o (C_{gd1} + C_o)}$$

Same as ω_{out}


↳ Valid only when C_{gs1} dominates the response

↳ otherwise not!

$$\Rightarrow \omega_z = \frac{g_{m1}}{C_c} \quad |\omega_{p1}| \ll |\omega_{p2}|$$

$$\omega_{p1} = \frac{1}{R_s [(1+|A_v|)C_c + C_{gs1}] + R_o [C_c + C_o]}$$
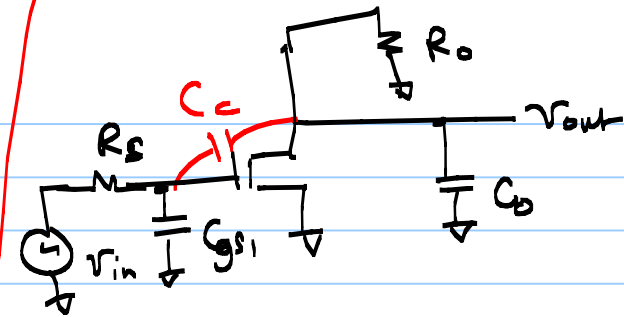
$$\omega_{p2} = \frac{R_s (1 + g_{m1} R_o) C_c + R_s C_{gs1} + R_o [C_c + C_o]}{R_s R_o [C_{gs1} C_c + C_{gs1} C_o + C_c C_o]}$$



$$C_c = C_{gd1} + C_c'$$

* for $C_c \approx 0$, and a large C_o

$$\omega_{p1} \approx \frac{1}{R_s C_{gs1} + R_o C_o}$$

$$\omega_{p2} = \frac{\cancel{R_s C_{gs1}} + \cancel{R_o C_o}}{\cancel{R_s R_o} \cdot \cancel{C_{gs1} C_o}} \approx \frac{1}{R_o C_o}$$

* Now, increase C_c

Consider when, $C_c \gg C_{gs1}$

$$\omega_{p1} \approx \frac{1}{R_S(1+|A|)C_c + R_o(C_c + C_o)}$$

$$\omega_{p2} \approx \frac{\cancel{R_S}(1+g_{m1}R_o)\cancel{C_c}}{\cancel{R_S}R_o\cancel{g_c}[C_o + C_{gs1}]} \approx \boxed{\frac{g_{m1}}{C_o + C_{gs1}}}$$

$$C_c = 0$$

Typical Case

$$C_c \gg C_{gs1}, \quad C_c \approx C_o$$

ω_{p1}

$$\approx \frac{1}{R_s C_{gs1} + R_o C_o}$$

$$\approx \frac{1}{\underline{R_s (1 + |A|) C_c + R_o [C_c + C_o]}} \quad \downarrow$$

ω_{p2}

$$\approx \frac{1}{\underline{R_o C_o}}$$

$$\approx \frac{g_{m1}}{C_o + C_{gs1}} \Rightarrow \frac{g_{m1}}{C_o} = \underline{\underline{g_{m1} R_o}} \left[\underline{\frac{1}{R_o C_o}} \right] \quad \uparrow$$

ω_z

$$\approx \frac{g_m}{C_{gd1}}$$

$$\frac{g_m}{C_c}$$

Pole Splitting

s plane

$C_c \uparrow$

