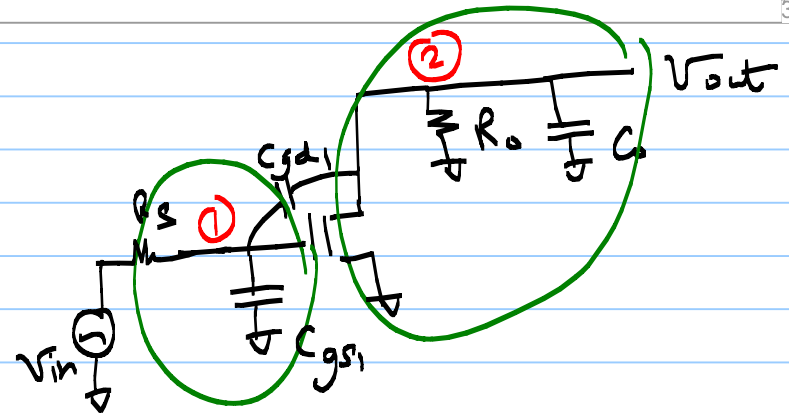



ECE 5411 - Lecture 17

Note Title

3/23/2011



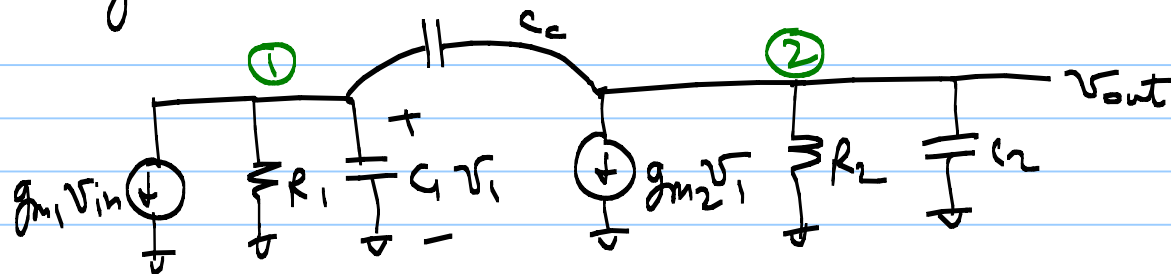Generic Model for CS $\rightarrow$ 2nd order



Example

21.6 - 21.10

$$A_V = + g_{m1} R_1 g_{m2} R_2 \leftarrow \text{DC gain}$$

$$\omega_{p1} = \frac{1}{R_2 (C_2 + C_c) + R_1 (C_1 + C_c (1 + g_{m2} R_2))}$$

$$\omega_{p2} = \frac{1}{g_{m2} R_2 R_1 C_c}$$

Ex 21.6


$$\omega_{p1} \approx \frac{g_{m2} C_c}{\underline{C_c C_1} + \underline{C_1 C_2} + C_c C_2}$$

$$\propto \frac{g_{m2}}{\underline{C_2}} \quad \text{if } C_2 \approx C_c \gg C_1$$

$$\omega_z = \frac{g_{m2}}{C_c}$$

$$A_v(s) = \frac{A_{v0} (1 + s/\omega_z)}{(1 + s/\omega_{p1}) (1 + s/\omega_{p2})}$$





open-loop
small-signal
transfer function

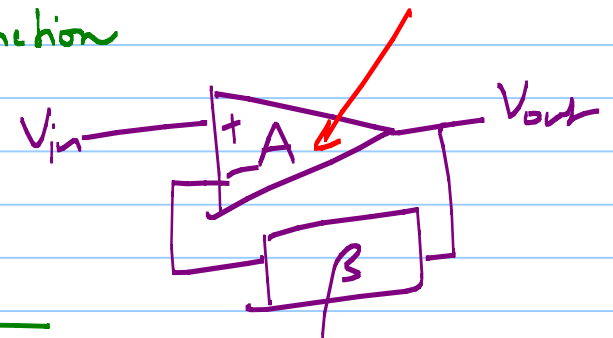




RHP zero $\rightarrow \tan^{-1}\left(\frac{-\omega/\omega_z}{1}\right) = -\tan^{-1}\left(\frac{\omega}{\omega_z}\right)$



LHP zero $\rightarrow \tan^{-1}\left(\frac{+\omega/\omega_z}{1}\right) = +90^\circ$

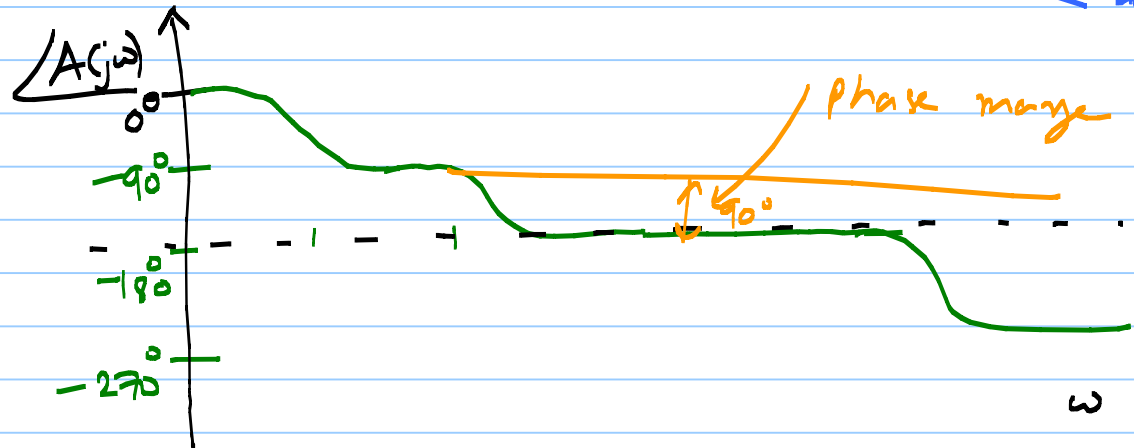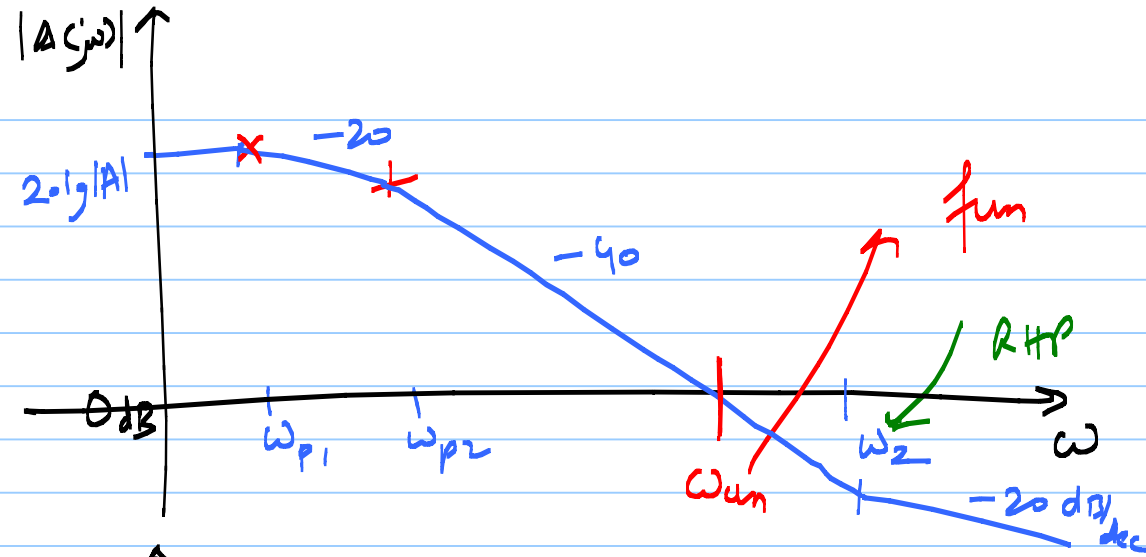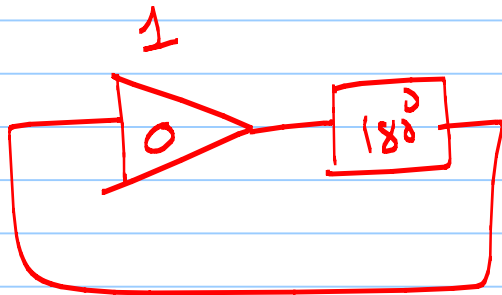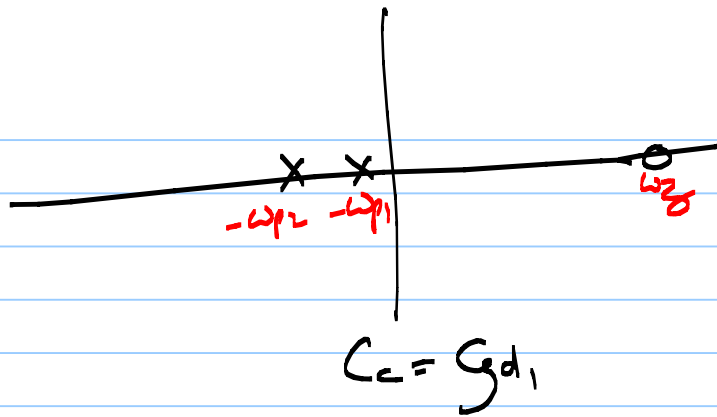
$$\frac{\omega_z}{10} < \omega < 10 \omega_z$$



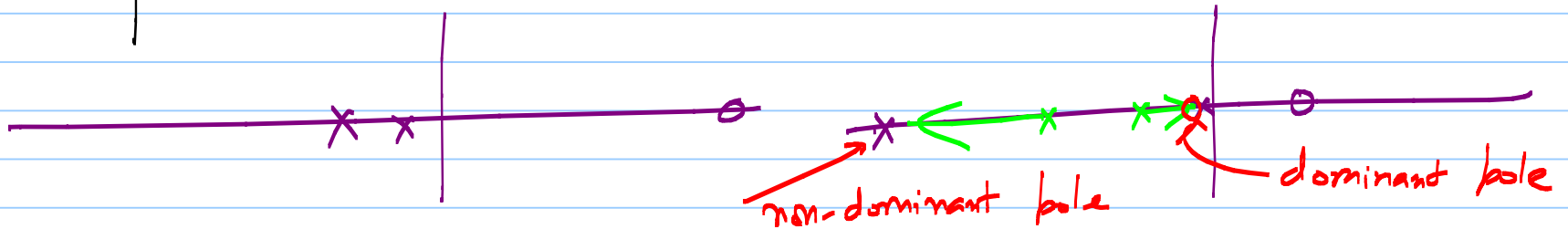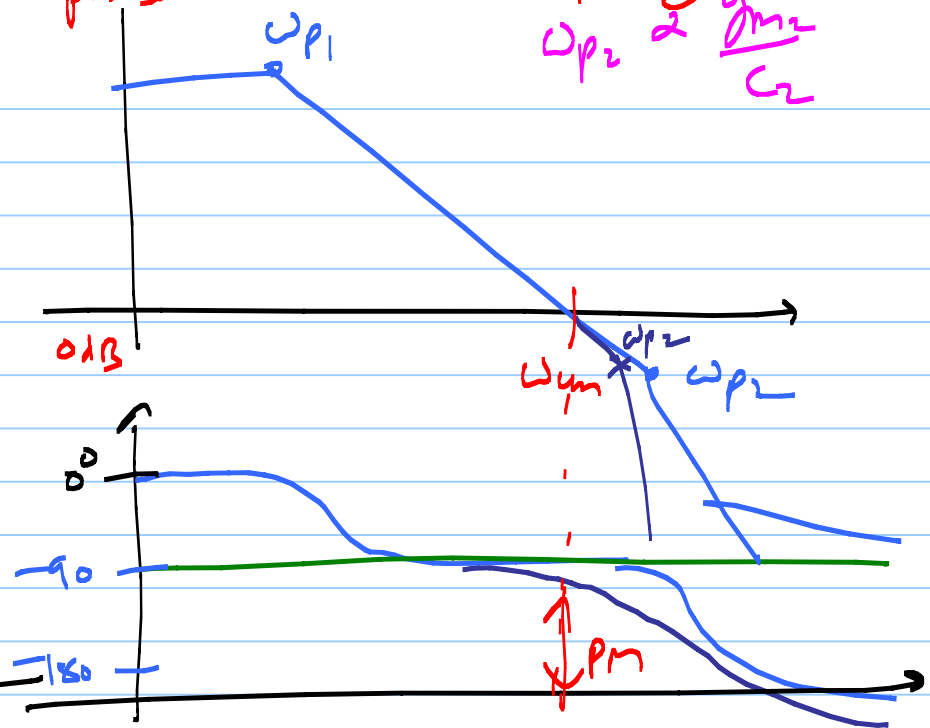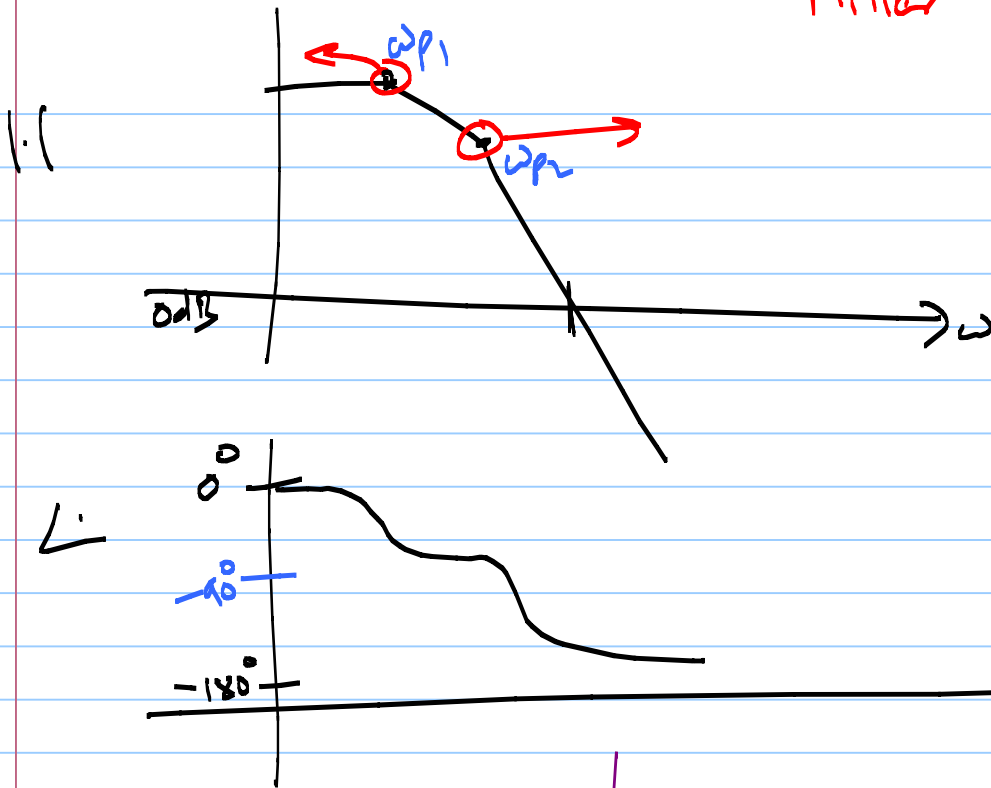Miller Compensation $\Rightarrow$ Pole splitting
 $\omega_{p2} \propto \frac{g_{m2}}{C_2}$



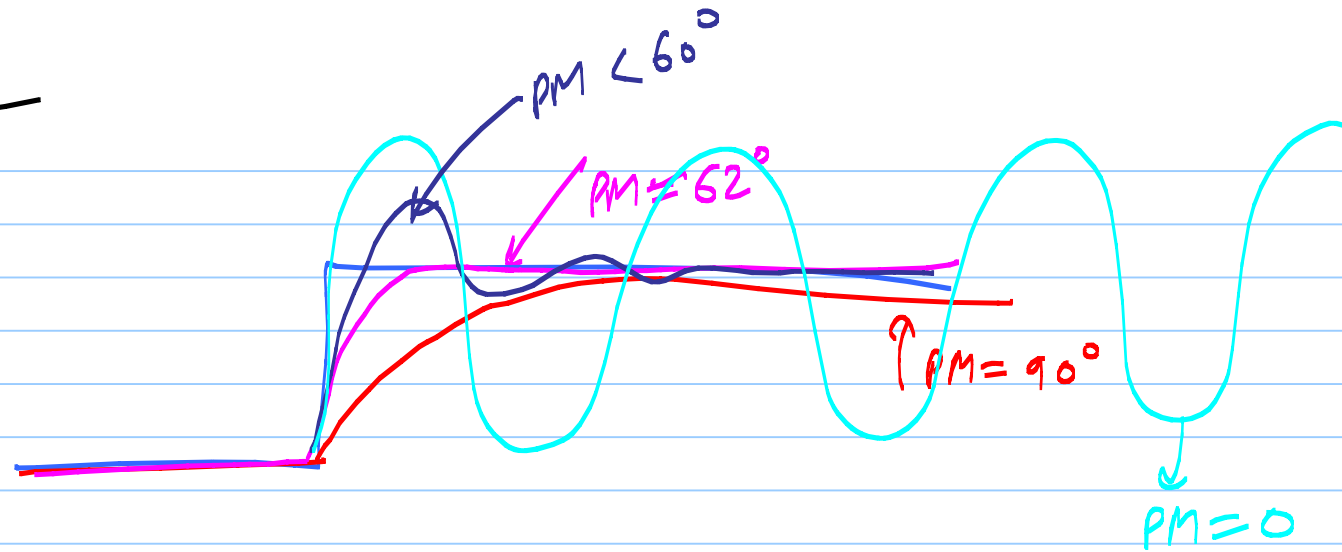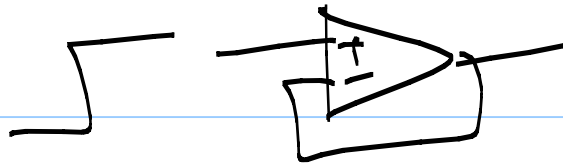

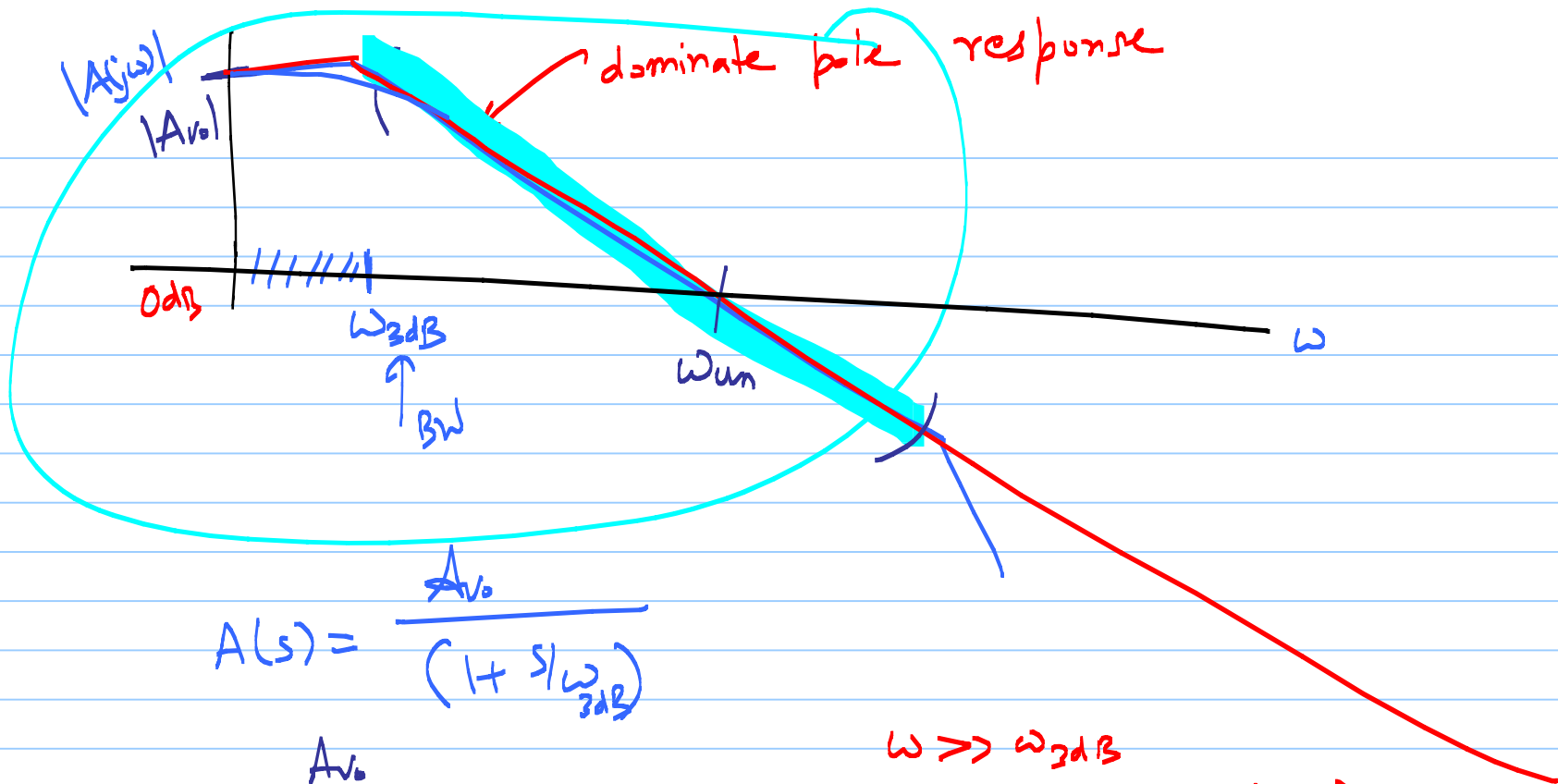

$$A(s) = \frac{A_{vo}}{(1 + s/\omega_{3dB})}$$

$$A(j\omega) = \frac{A_{vo}}{1 + \frac{j\omega}{\omega_{3dB}}}$$

$$\omega \gg \omega_{3dB}$$

$$|A(j\omega)| \approx \frac{A_{vo}}{\omega/\omega_{3dB}} = \frac{A_{vo} \cdot \omega_{3dB}}{\omega} =$$

@ $\omega = \omega_{um}$

$$\frac{A_{v0} \cdot \omega_{3dB}}{\omega_{um}} = 1$$

$$\Rightarrow \omega_{um} = \underbrace{A_{v0}} \cdot \underbrace{\omega_{3dB}}$$

$$f_{um} = A_{v0} \cdot f_{3dB}$$



unity gain frequency

$$\omega_{um} \approx A_{v0} \cdot \omega_{p1}$$



$$= g_{m1} R_1 / g_{m2} R_2 \times \frac{1}{g_{m2} R_2 R_1 C_c}$$

$$\boxed{\omega_{um} \approx \frac{g_{m1}}{C_c}}$$

$$\omega_z = \frac{g_{m2}}{C_c}$$

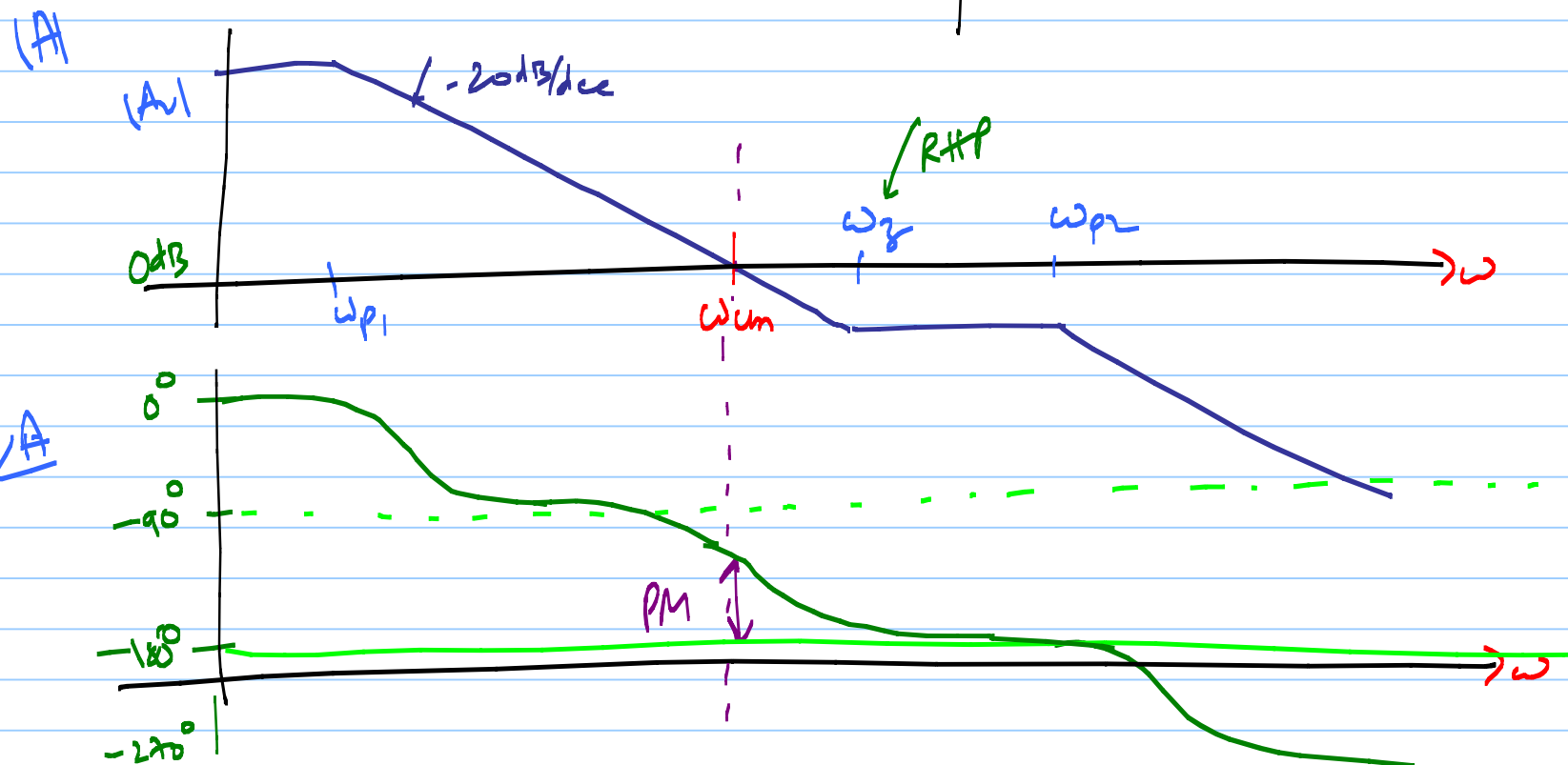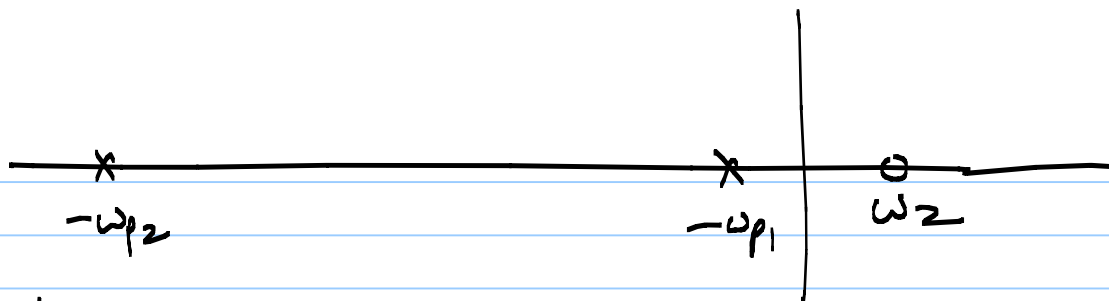

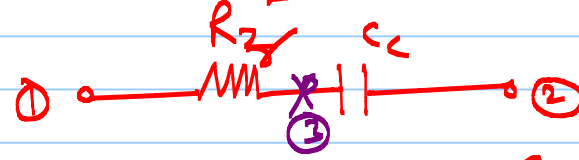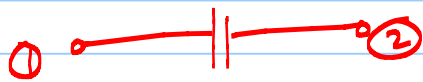Miller Cap RHP zero is Undesired $\rightarrow$ near ω_{dom}
 Compensation Cap $\rightarrow$ zero nulling resistor





$$\omega_z = \frac{1}{C_c \left[\frac{1}{g_{m2}} - R_z \right]}$$

$$+ \frac{g_{m2}}{C_c} = \frac{1}{C_c \frac{1}{g_{m2}}}$$



* $R_z = \frac{1}{g_{m2}} \leftarrow$ RHP zero nulling

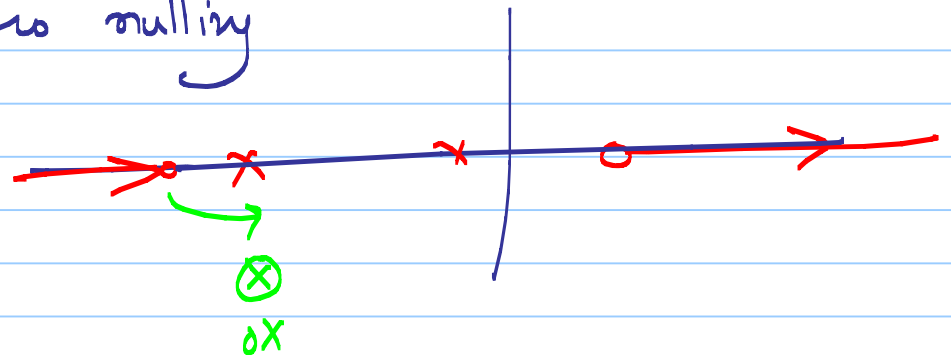* $R_z > \frac{1}{g_{m2}} \leftarrow$ LHP zero



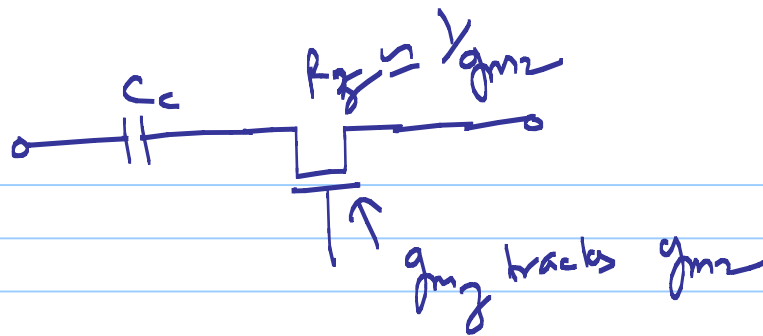


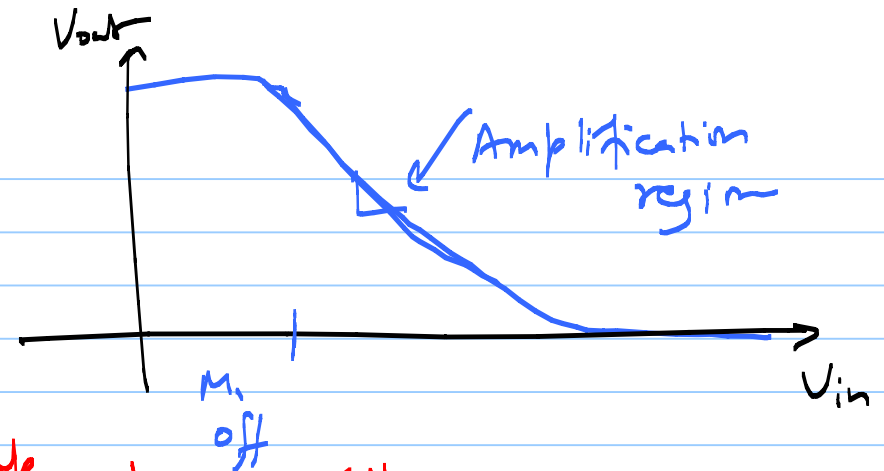
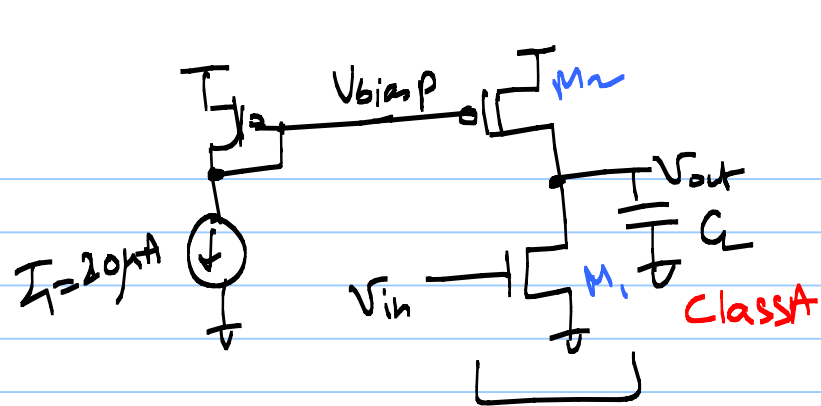
$$R_z = \frac{1}{g_{m2}} \approx \frac{1}{g_{m2}}$$



Class A $\rightarrow$ Both Pull-up device are ON
pull-down

Class B $\rightarrow$ only one is ON

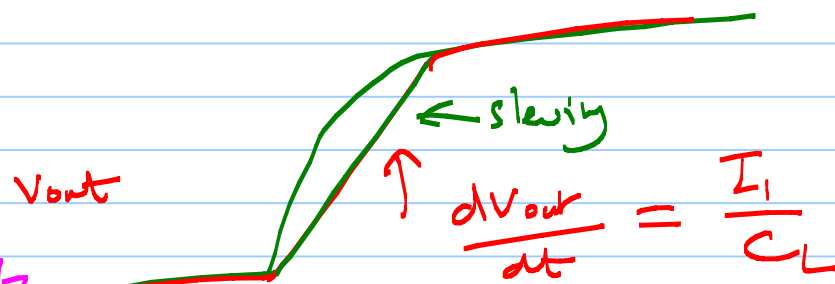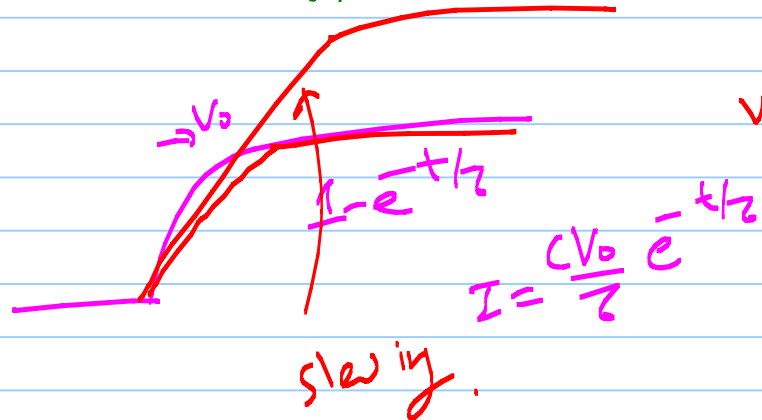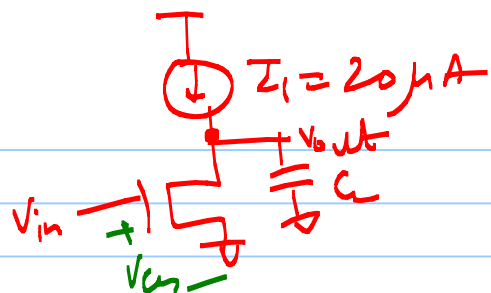Class AB $\rightarrow$ both are ON during the transition



the slew-rate limitation

