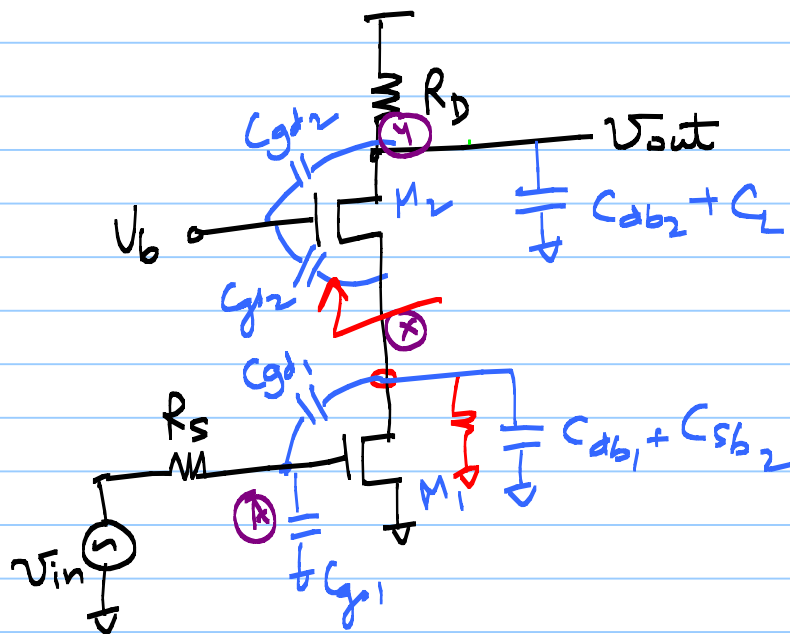


ECE 511 - Lecture 18

Note Title

4/4/2011



$$A_v = -g_{m1} (R_D \parallel g_{m1} r_{o2})$$

gain from (A) to (X)

↳ Assuming low value of R_D

$$-g_{m1} \times \left(\frac{1}{g_{m2} + g_{m2b}} \parallel r_{o1} \right)$$

$$\approx -\frac{g_{m1}}{g_{m2}} \approx -1$$

→ C_{gd1} is only multiplied by 2x, instead of $|A_v|$

→ Miller effect is less significant in cascode amplifiers.


$$\omega_{PA} = \frac{1}{R_S \left[C_{gs1} + \left(1 + \frac{g_{m1}}{g_{m2} + g_{mb2}} \right) C_{gd1} \right]} \rightarrow \textcircled{1}$$



$$\omega_{hg} = \frac{1}{R_D [C_{db2} + C_L + C_{gd2}]}$$


* pole @ node (x)

$$C_x = 2C_{gd1} + C_{db1} + C_{sb2} + C_{s2}$$
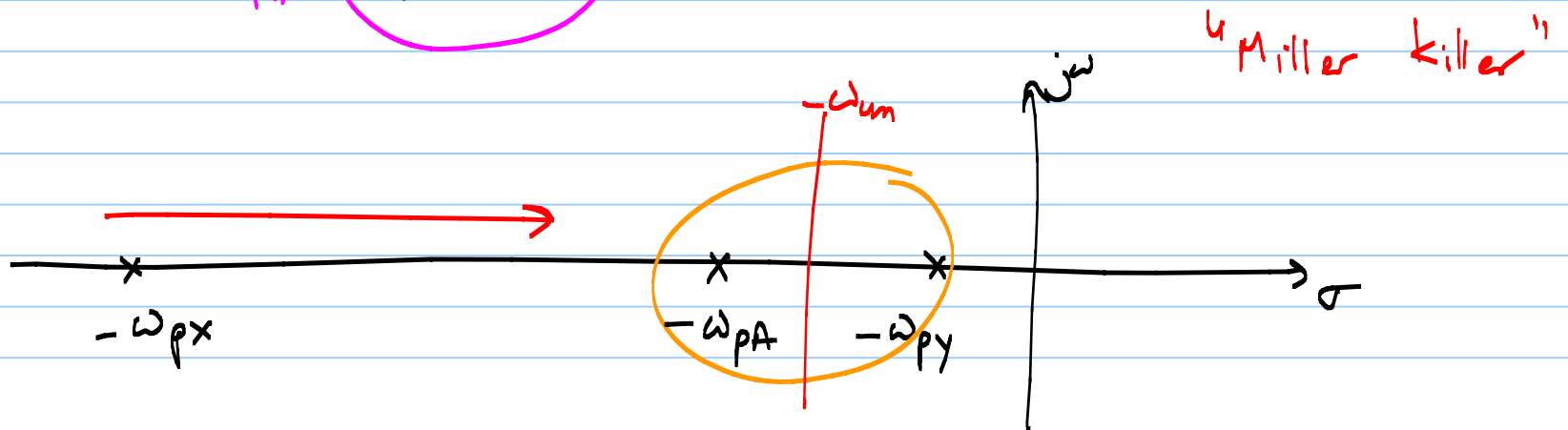
$$\omega_{px} = \frac{1}{R_x \left(\frac{1}{g_{m2} + g_{m2}} \right) [2C_{gd1} + C_{db1} + C_{sb2} + C_{s2}]}$$



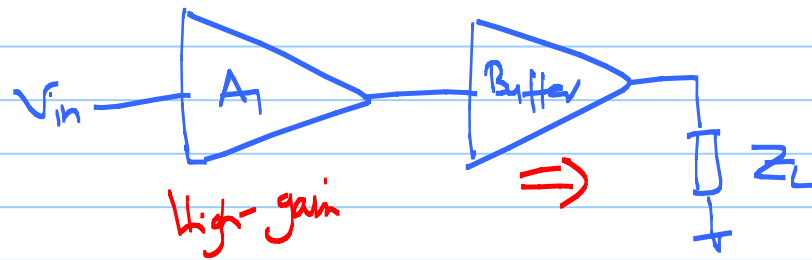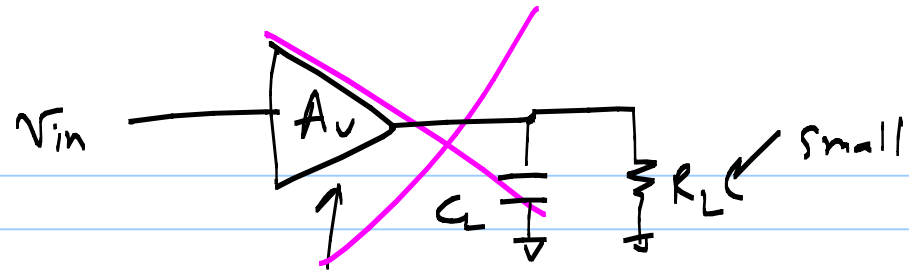

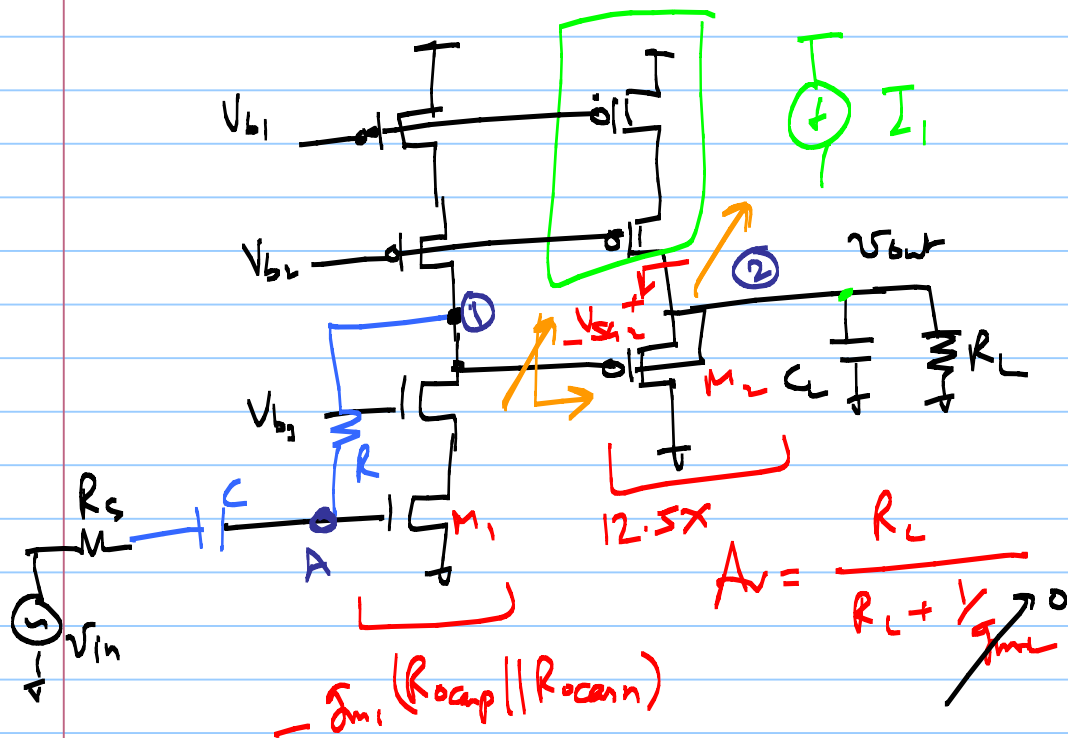

$$\frac{I_1}{C_L}$$

$$C_{gs}(1-A)$$

Class-A

$$R_L \gg \frac{1}{g_{m2}}$$


$$\omega_{in} = \frac{1}{R_s C_{in}}$$

$$\omega_1 \Leftarrow$$



$$R_{eq} \cdot C_{small}$$

$$\omega_2 \Leftarrow \frac{1}{R_{low} \cdot C_L}$$

$$\frac{1}{g_{m2}}$$

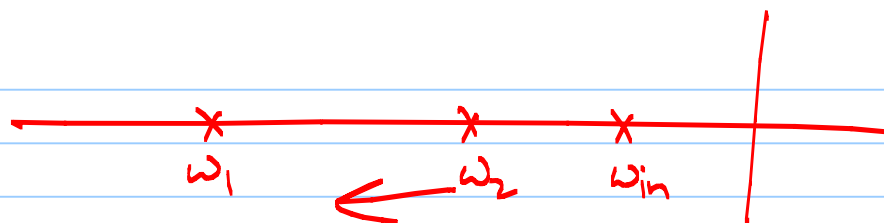



Page 698.

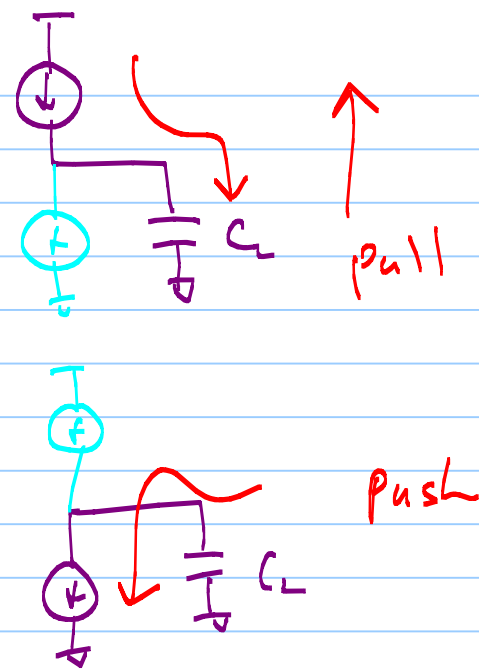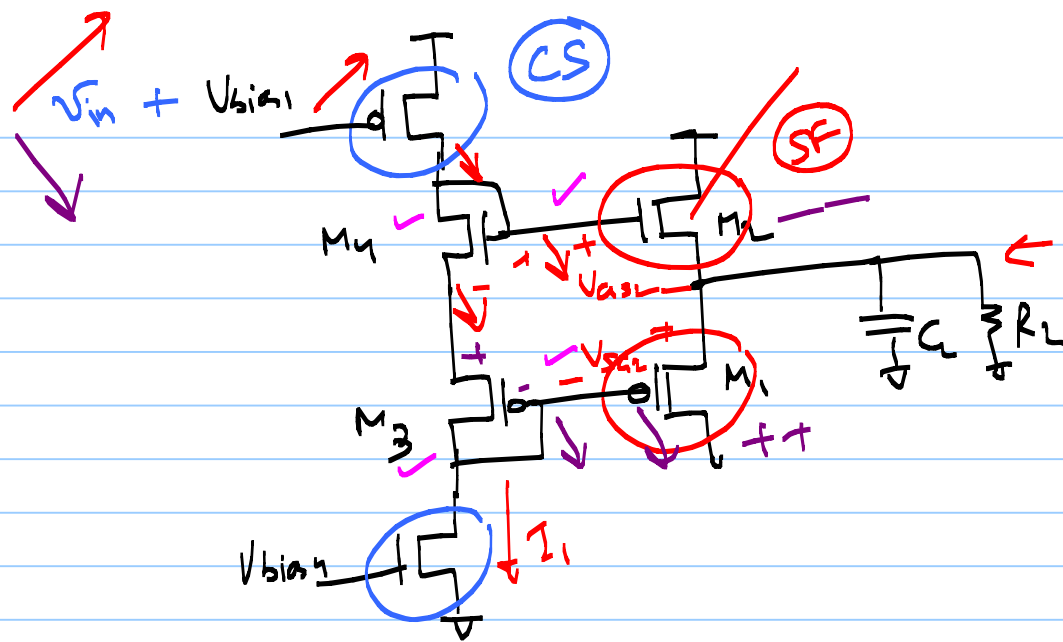

Class-AB

Push-pull Amplifier

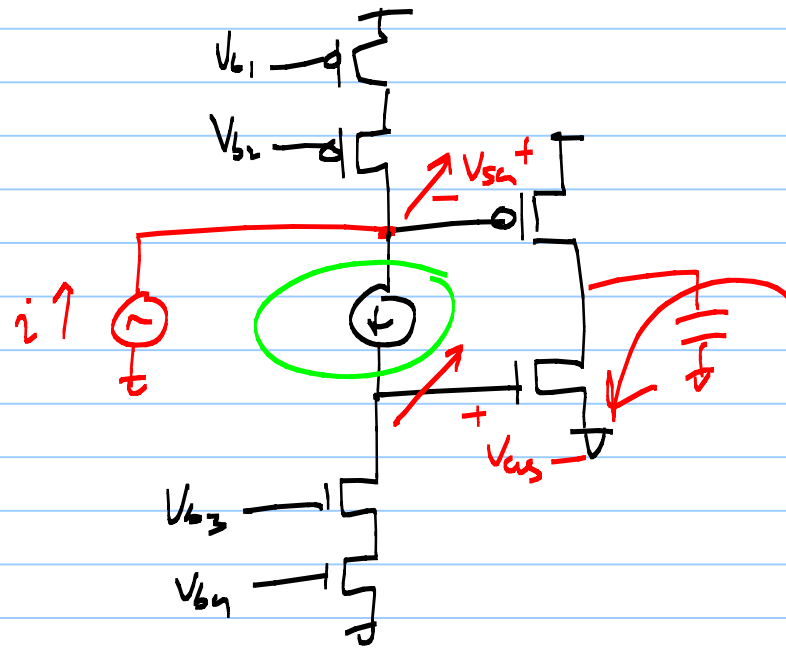

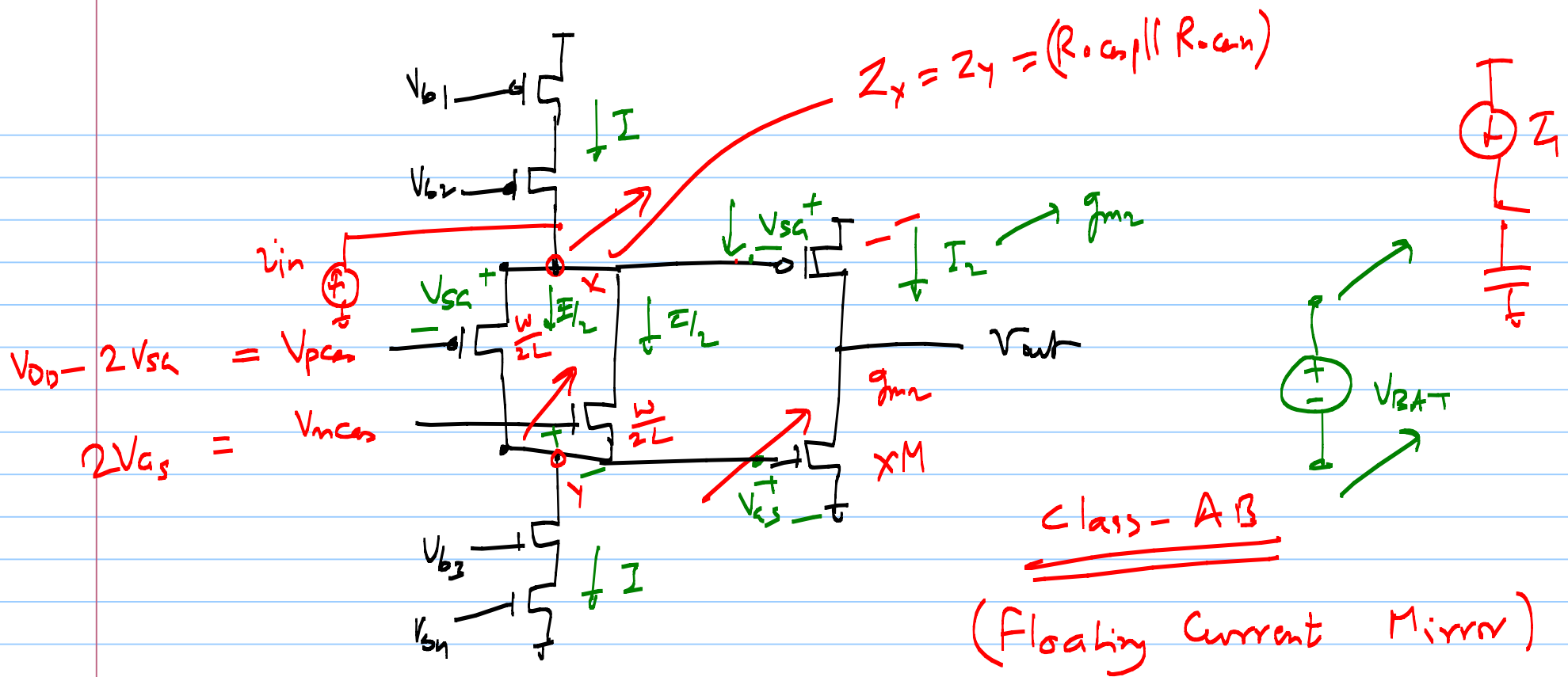


$$PCE = \frac{P_{load}}{P_{VDD}} \times 100\%$$

Class A $\rightarrow$ 12.5%


Class-AB $\rightarrow$ 100%

Class-B $\rightarrow$ "Switcher distribution"

"Differential Amplifiers"

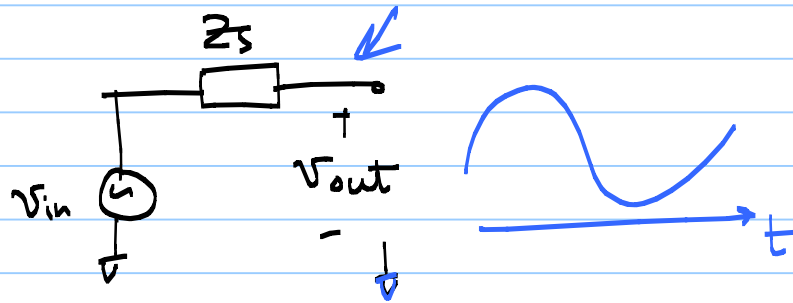


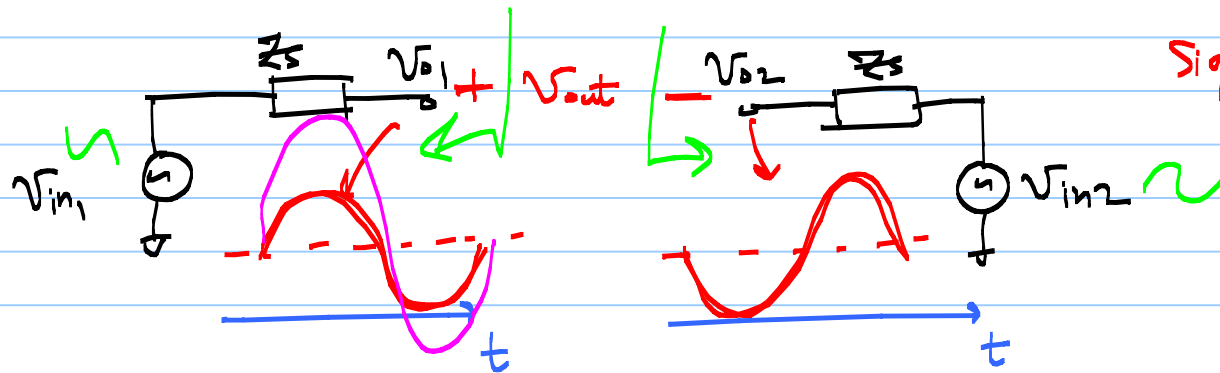Single-ended is referenced to a fixed voltage $\rightarrow$ ground.



$\Rightarrow$ The center potential in differential

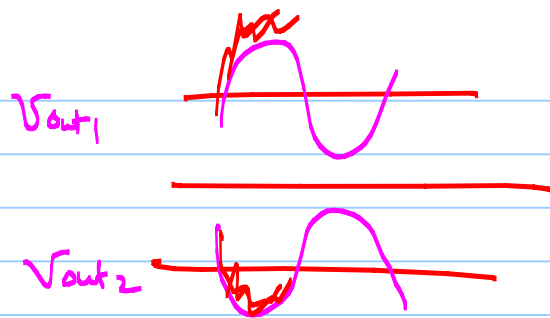
signaling is called
"Common-mode"
CM-level.






$$V_{cm} = \frac{V_{out1} + V_{out2}}{2}$$

$$V_d = V_{out} = (V_{out1} - V_{out2})$$

$$V_{out} = V_{out1} - V_{out2}$$

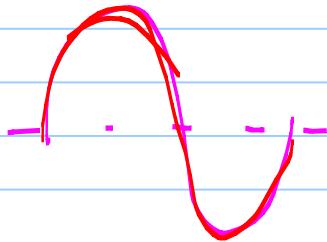

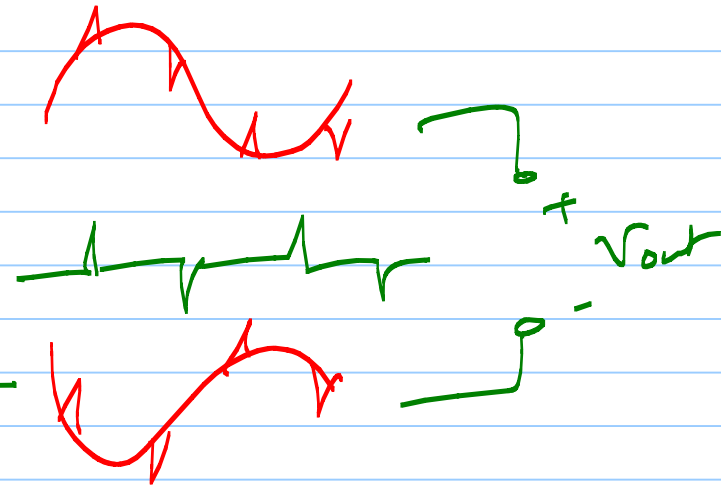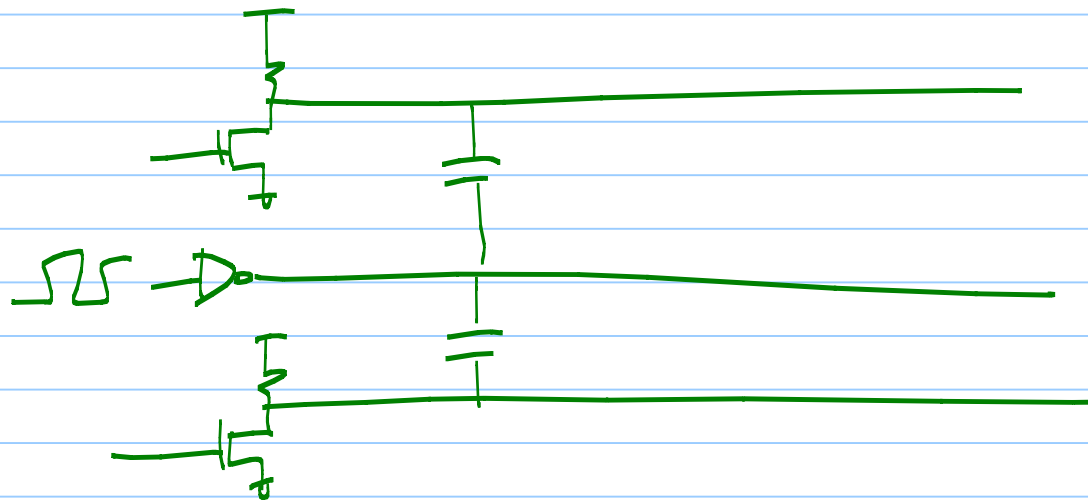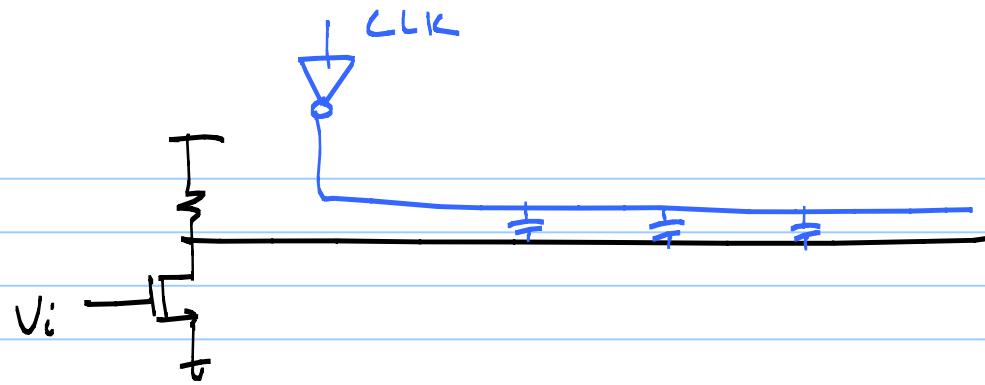

⇒ Comm-mode disturbance rejection


↳ differential output is still intact

⇒ CM-level is disturbed.



* Supply noise is rejected.

* Swing is effectively doubled. !

SE

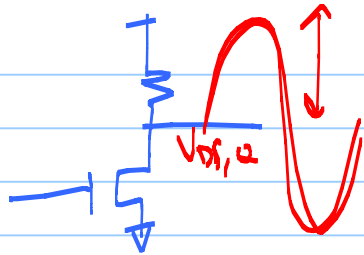

$$\frac{(V_{DD} - V_{DS,sat})}{2} = A$$

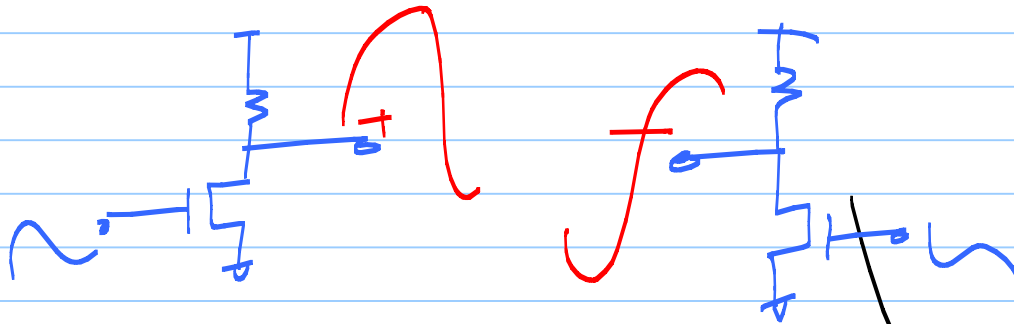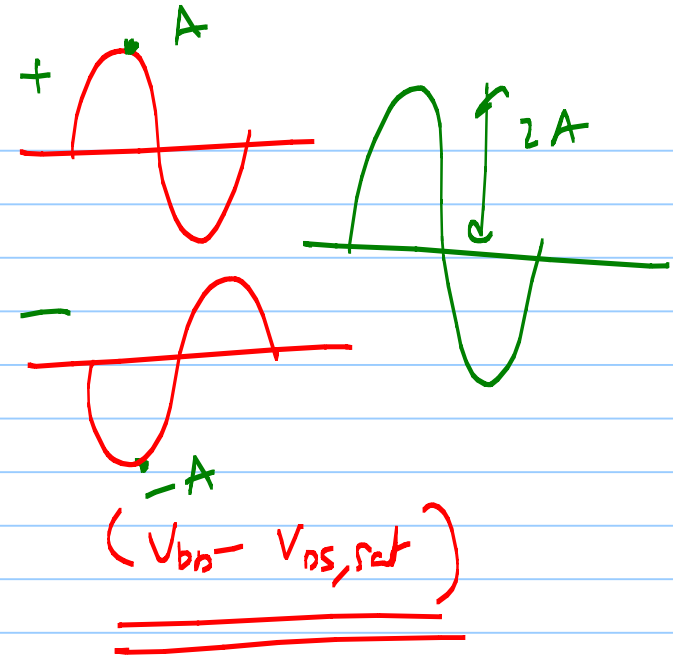

* Biasing is simplified.