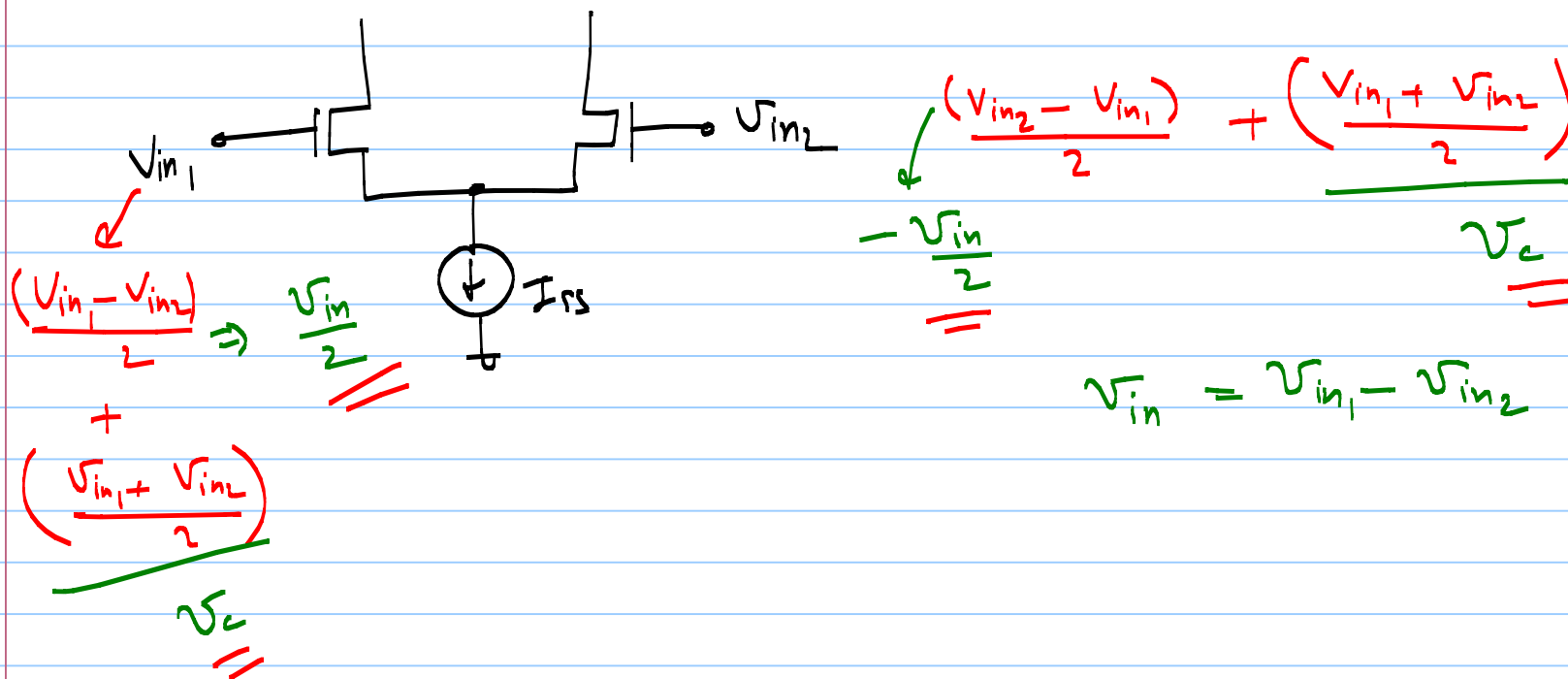


ECE 5411 - Lecture 20


Note Title

4/13/2011




DM


(A)

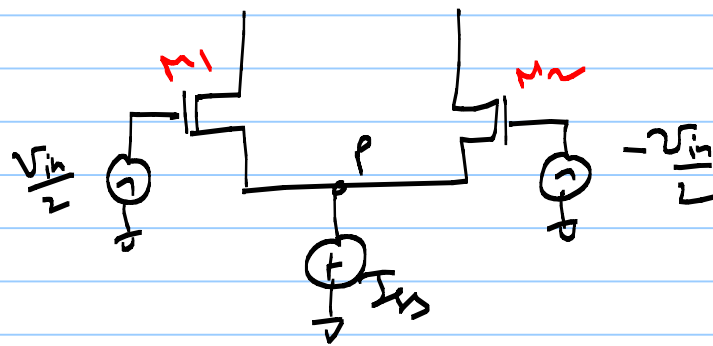

CM


(B)

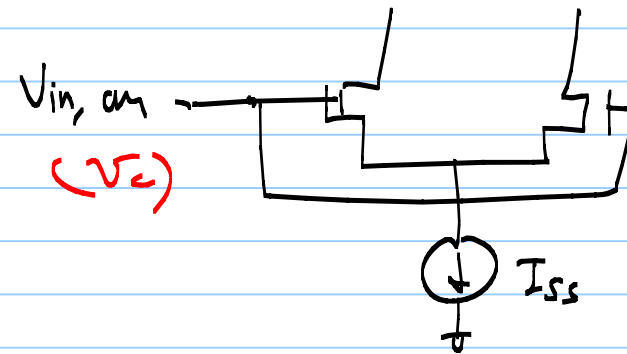

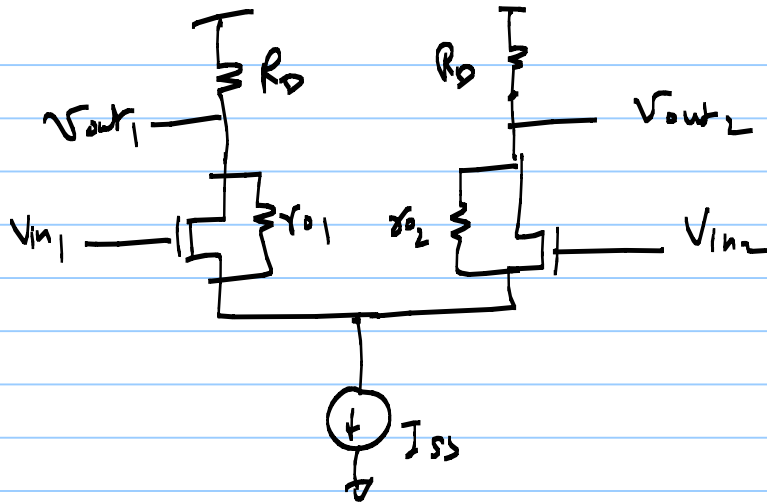

$$V_{in} = V_{in1} - V_{in2}$$

DM

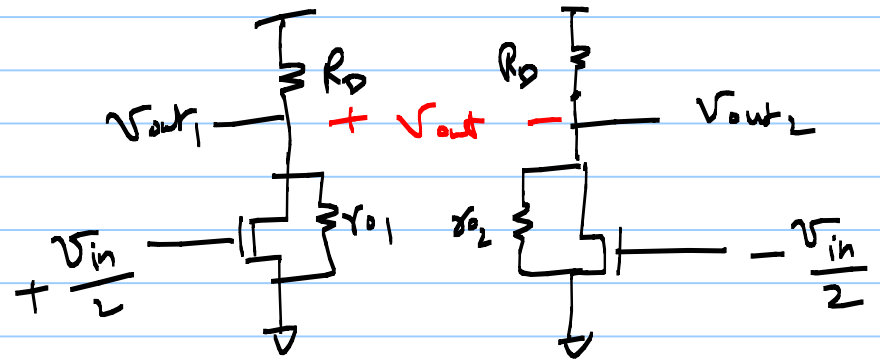


$$V_{out1} = -g_{m1} \frac{V_{in}}{2} \cdot (R_D \parallel r_{o1})$$


$$V_{out2} = -g_{m2} \left(-\frac{V_{in}}{2}\right) \cdot (R_D \parallel r_{o2})$$

$$V_{out} = V_{out1} - V_{out2} = -g_{m1} V_{in} (r_o \parallel R_D) = A_{v,DM}$$

Common Mode Response

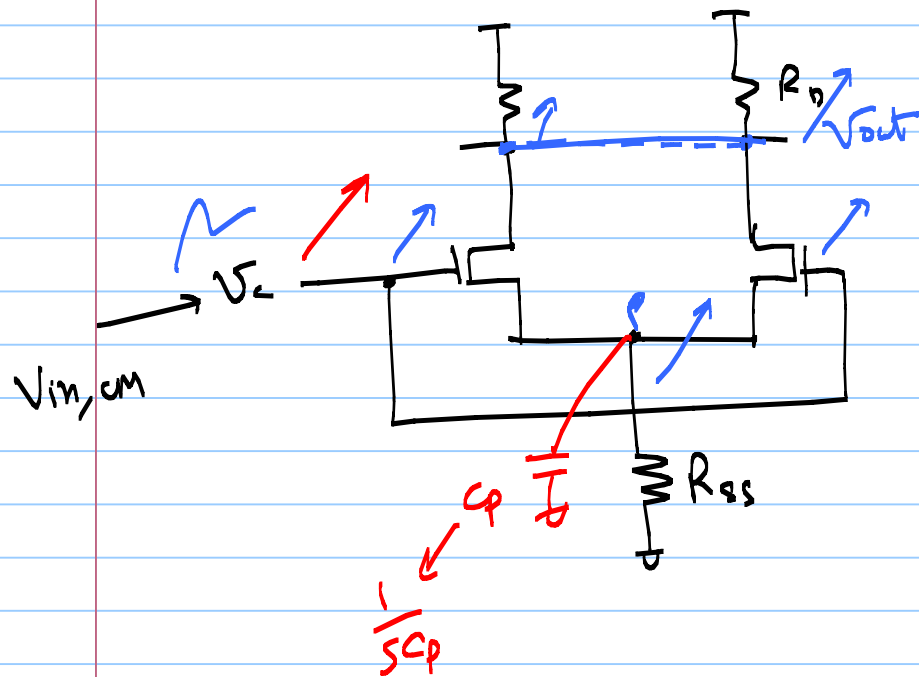

$\Rightarrow$

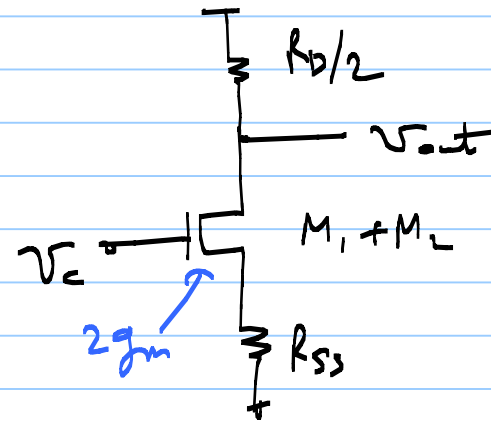

CM equivalent circuit

$$\frac{v_{out}}{v_c} = - \frac{R_D/2}{1/2g_m + R_{SS}} = A_{V,cm}$$


Common Mode Rejection Ratio (CMRR)

$$CMRR = \left| \frac{A_{v, DM}}{A_{v, CM}} \right| \leftarrow \text{dB}$$

∞
 0

$$R_D \ll r_{o1,2}$$

$$= \left| \frac{\frac{g_{m1,2} (r_{o1,2} \parallel R_D)}{R_D/2}}{\frac{1}{2g_{m1,2}} + R_{SS}} \right| = \frac{1}{2} + g_{m1,2} \underline{\underline{R_{SS}}}$$

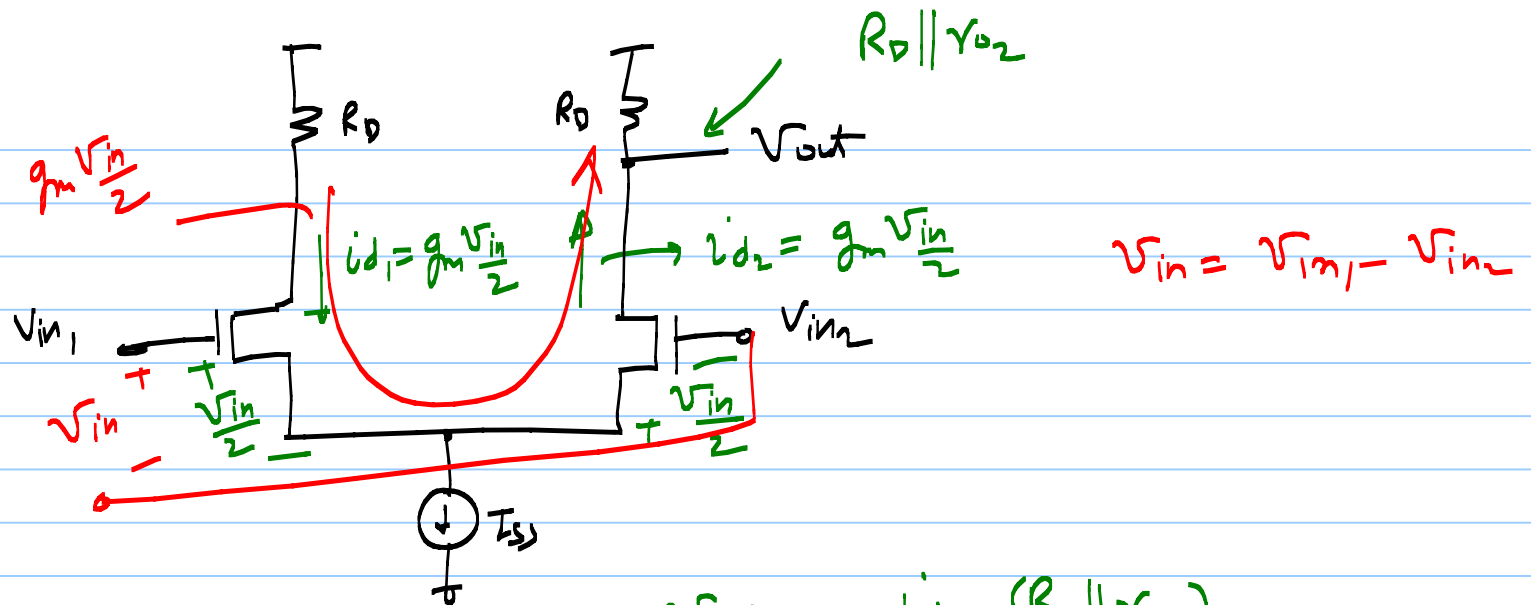

$$\begin{aligned}
 v_{out} &= i_{d2} (R_D || r_{o2}) \\
 &= g_m \frac{v_{in}}{2} (R_D || r_{o2})
 \end{aligned}$$


$$A_{v,DM} = \frac{g_m}{2} (R_D || r_{o2})$$

$$* \quad g_{m1} = g_{m2} + \Delta g_m$$


$$* \quad R_{D1} = R_{D2} + \Delta R_D$$

* for g_m mismatch

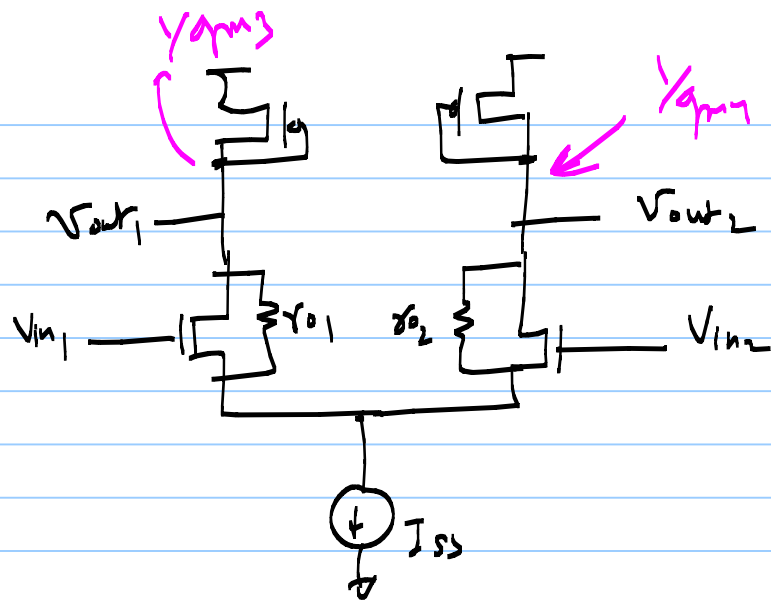
$$CMRR \approx \frac{g_m}{\Delta g_m} (1 + 2g_m R_{SS})$$



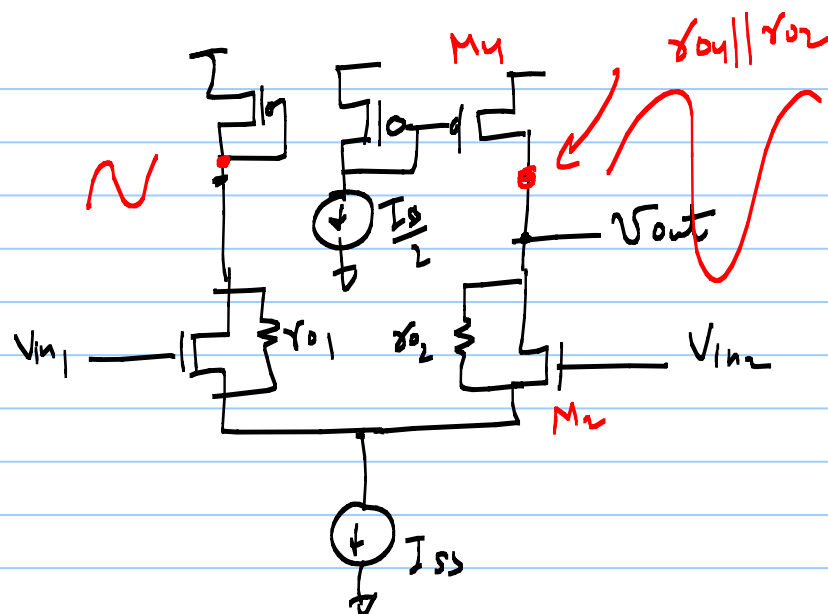
$$g_{m1,2} \left(\frac{1}{g_{m3,4}} \right)$$



$$A_v = + \frac{g_{m1,2}}{2} (R_D || r_{o1,2}) =$$

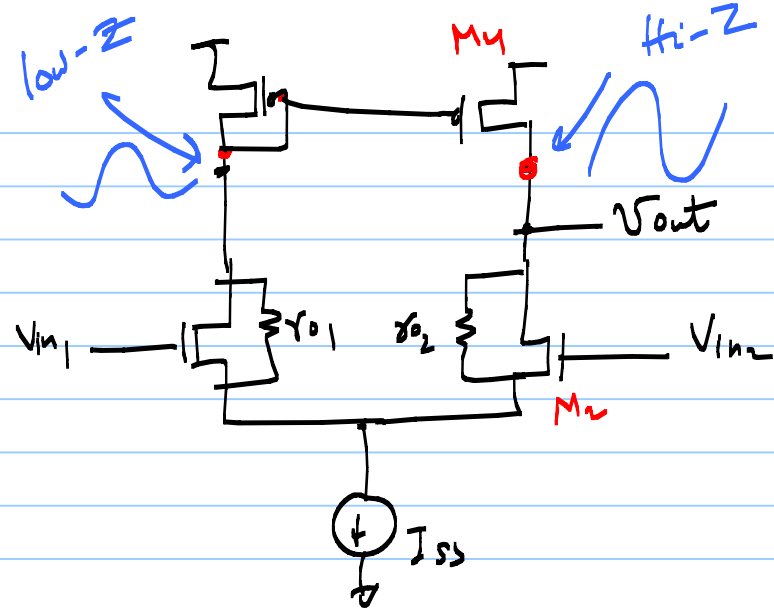



Diff amp with CM load

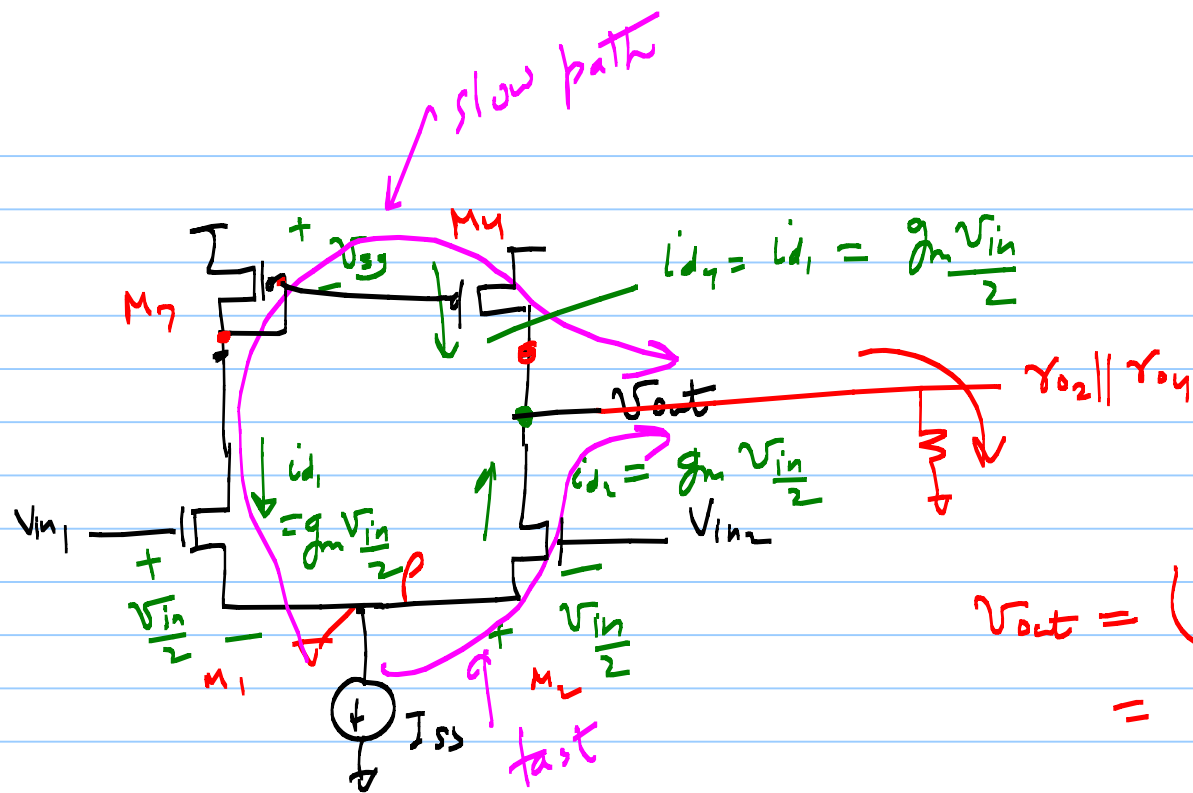

$$V_{out} = (i_{d2} + i_{d4}) (r_{o2} || r_{o4})$$

$$= g_m V_{in} (r_{o2} || r_{o4})$$


$$A_{DM} = + \underline{\underline{g_{m,2}}} (r_{o2} || r_{o4})$$

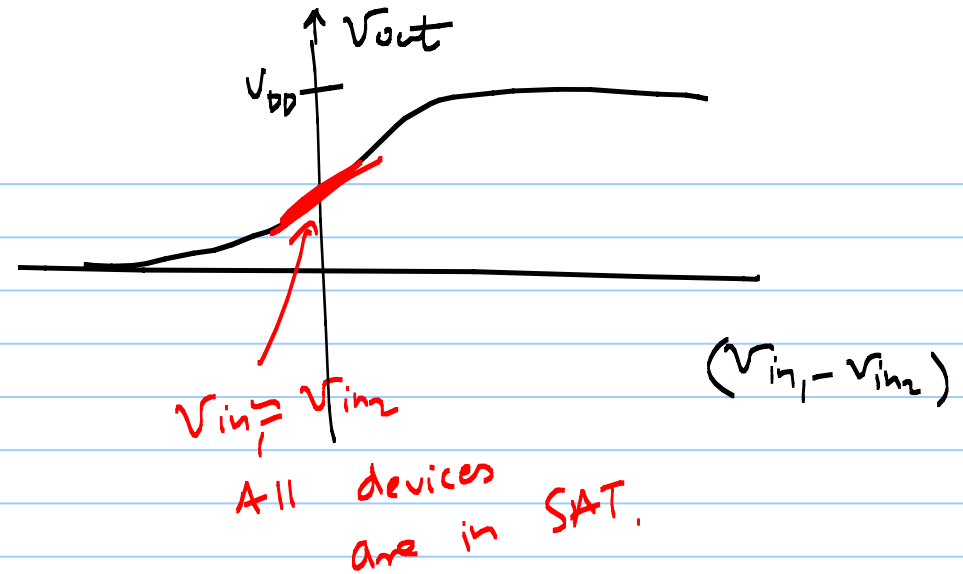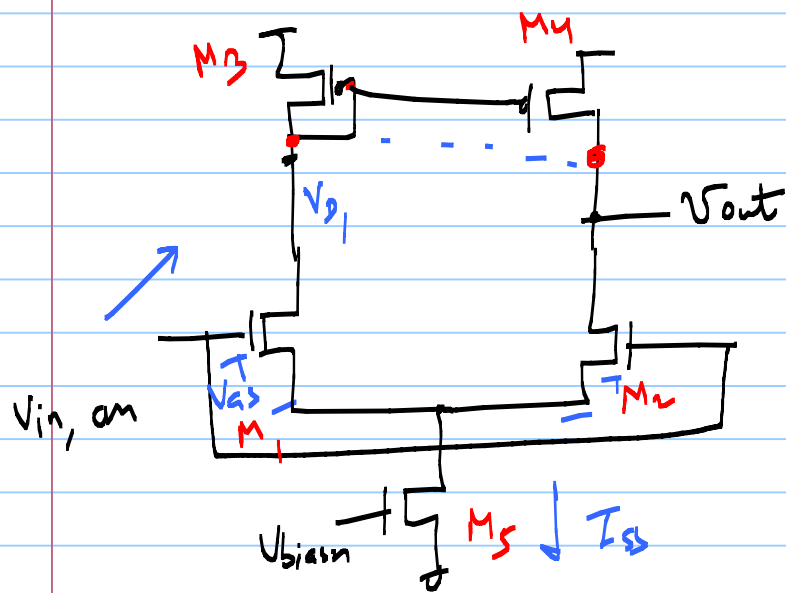

$$V_{in,cm} \geq \underline{V_{GS,1,2} + V_{DS,sat5}}$$

$$V_{in,cm} \leq V_{THN} + V_{D1} = \underline{\underline{V_{DD} - V_{SG2} + V_{THN}}}$$

$(\lambda \neq 0)$

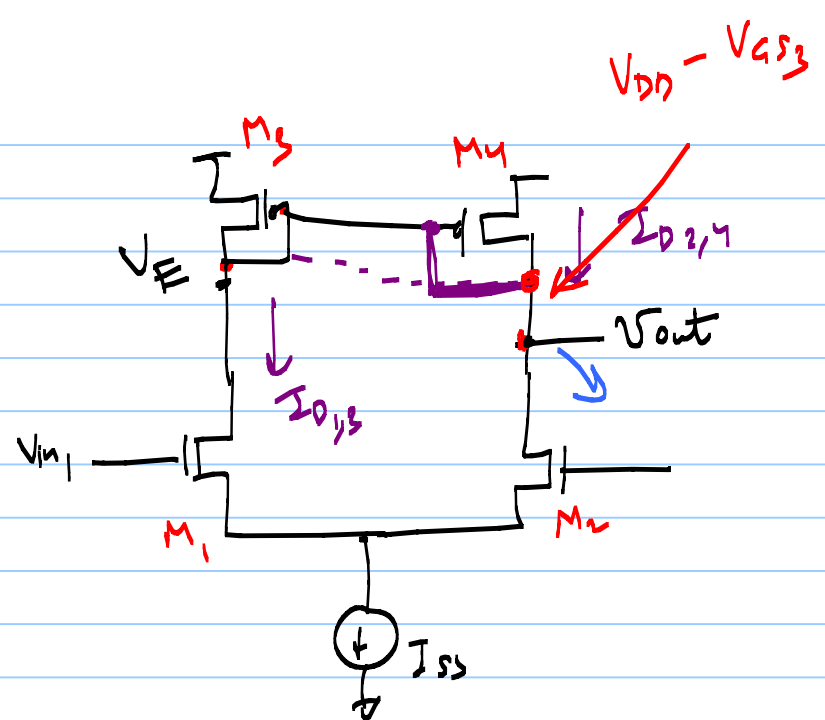

Let's assume

$$V_{out} < V_E$$

$$I_{D1} > \frac{I_{SS}}{2}$$


$$I_{D2} < \frac{I_{SS}}{2}$$

$$I_{D3} > \frac{I_{SS}}{2}$$

$$I_{D4} > \frac{I_{SS}}{2} \Rightarrow I_{D2} > \frac{I_{SS}}{2}$$

Contradiction

$$V_{out} = V_E$$

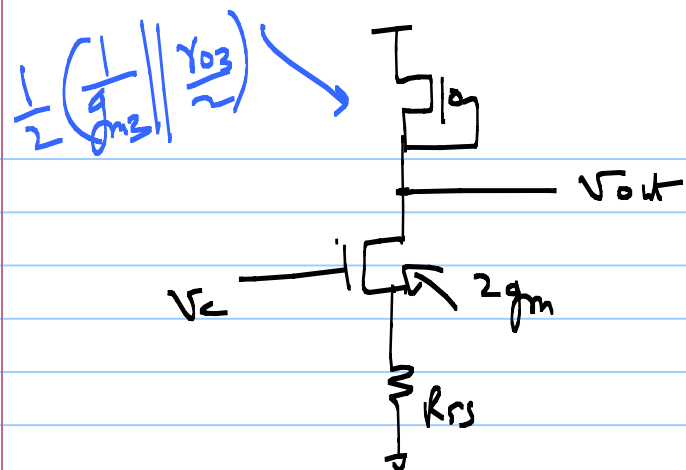


cm equivalent circuit

$$A_{v,cm} = \frac{-\frac{1}{2g_{m3,4}} \parallel \frac{r_{o3,4}}{2}}{\frac{1}{2g_{m1,2}} + R_{ss}}$$


$$= -\frac{1}{2g_{m3,4} R_{ss}}$$

$$CMRR = \left| \frac{A_{v,dm}}{A_{v,cm}} \right| = g_{m1,2} (r_{o1,2} \parallel r_{o3,4}) \cdot 2g_{m3,4} R_{ss}$$

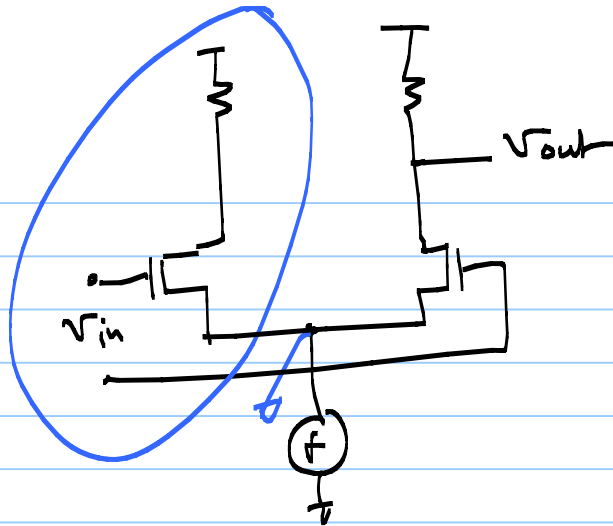


CS



$R_s = 0$

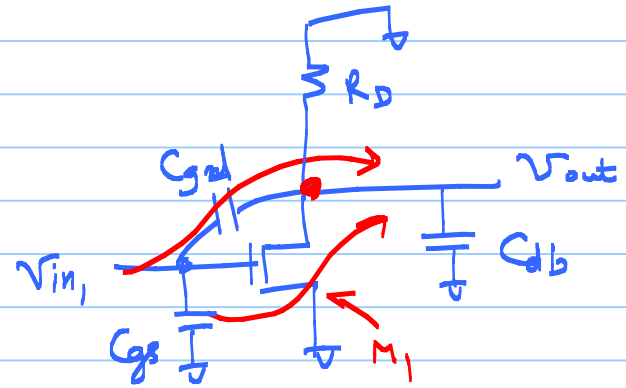

$$\omega_p = \frac{1}{(r_o \parallel R_D) C_L} \quad \text{---} \quad C_{gd} + C_{db}$$
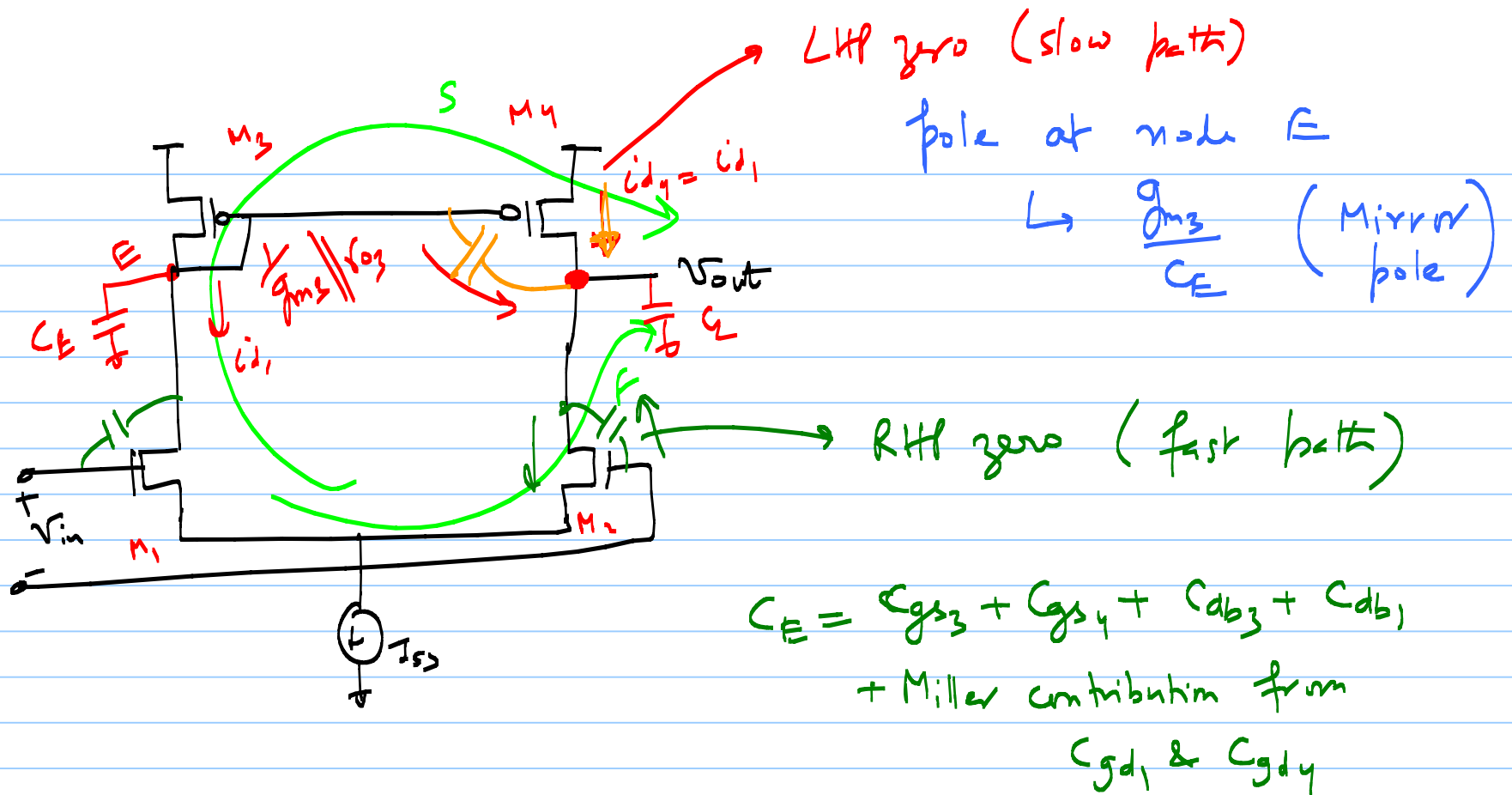
$$\omega_{z1} = + \frac{g_{m1}}{C_{gd}} \quad (\text{RHP})$$



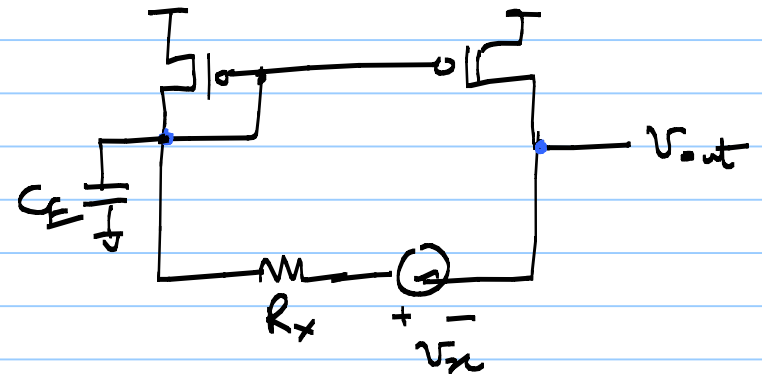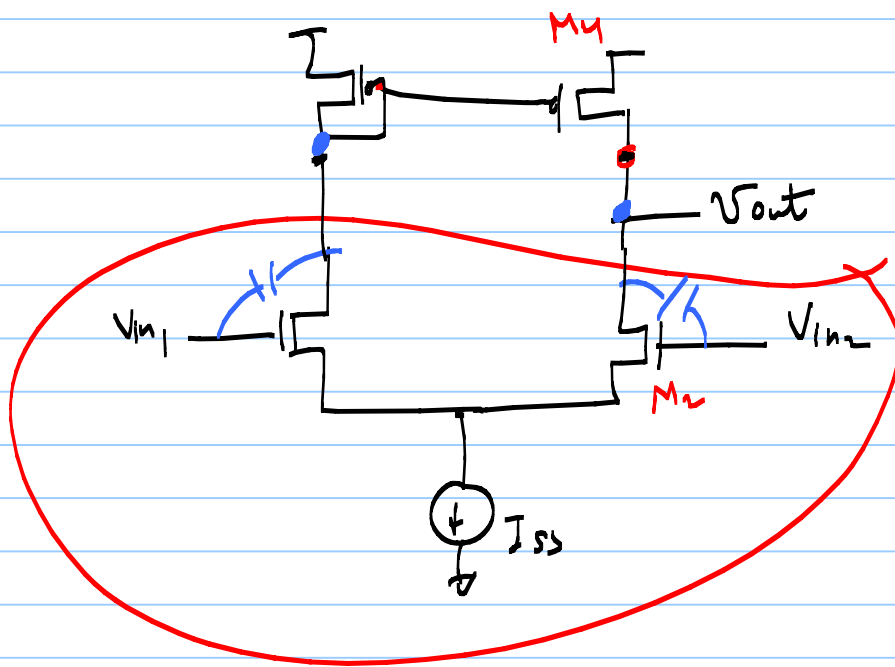

$$\frac{V_{out}}{V_{in}}(s) = \frac{g_{mn} r_{on} (2g_{mp} + sC_E)}{2r_{op}r_{on}C_EC_Ls^2 + [(2r_{on}+r_{op})C_E + r_{op}(1+2g_{mp}r_{on})C_L]s + 2g_{mp}(r_{on}+r_{op})}$$

LHP zero @ $\omega_{z1} = -\frac{2g_{mp}}{C_E}$

ω_{p1}, ω_{p2}

$$\omega_{p1} = \frac{1}{(r_{on} || r_{op}) C_L}$$

$$\omega_{p2} = \frac{g_{mp}}{C_E}$$

LHP

$$\omega_{z1} = -\frac{2g_{mp}}{C_E} = 2\omega_{p2}$$

$$\omega_{z2} = \frac{g_{mn}}{C_{Lm}} \quad \text{RHP}$$

