

ECE 5411 - Lecture 21.

Note Title

4/18/2011



Operational Amplifiers (Opamps)



* opamp $\rightarrow$ high-gain Diff amplifier

$10^1 \rightarrow 10^5$


* LM741

* IC - opamps

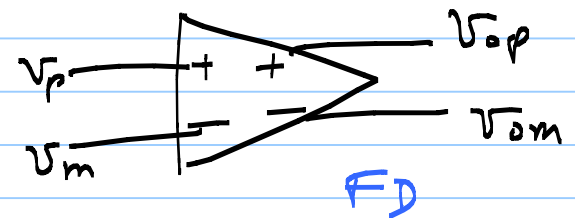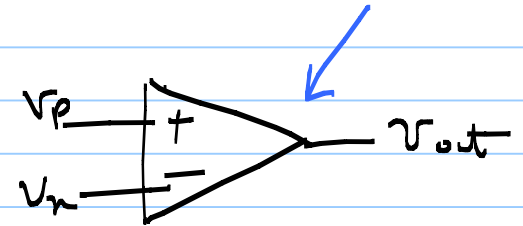

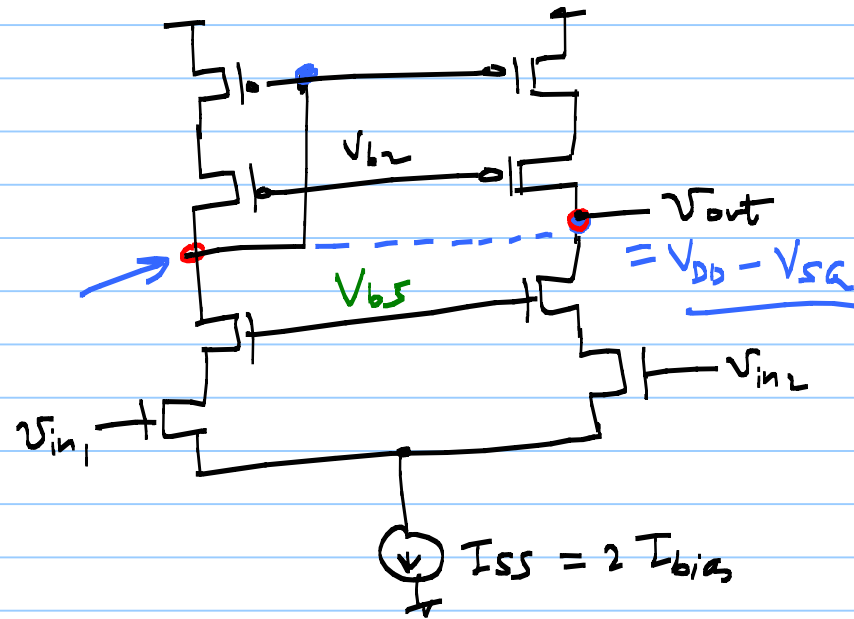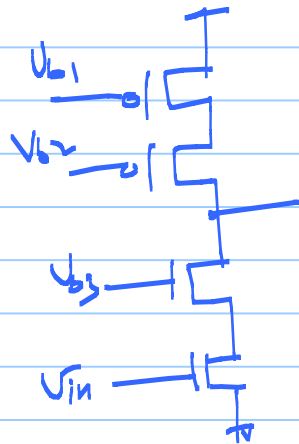


CM picture

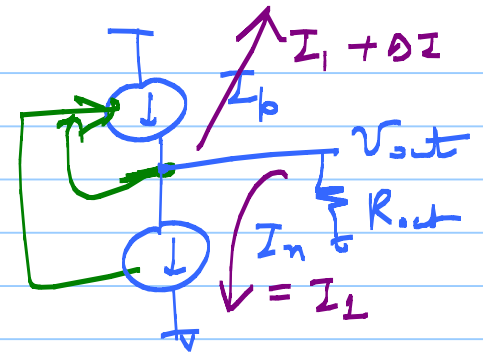


$$V_{CM0} = \frac{V_{out1} + V_{out2}}{2}$$

$$V_{CM} = \frac{V_{DD}}{2}$$

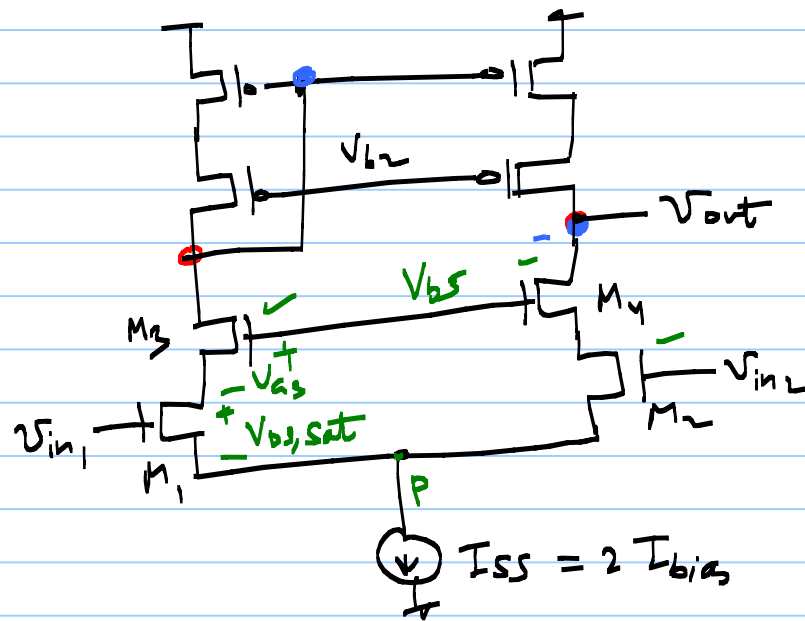


$$V_{b5} \geq V_p + V_{gs} + V_{ds,sat}$$

Telescopic

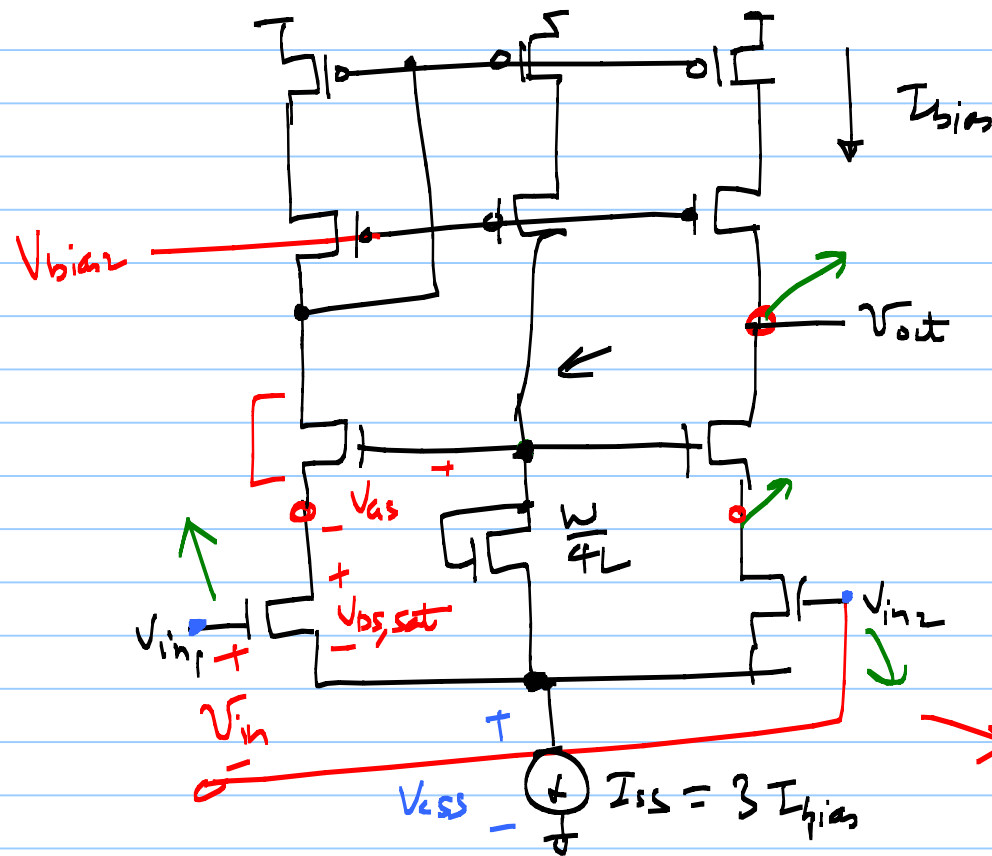

Cascode Diffamp
"Telescopic"

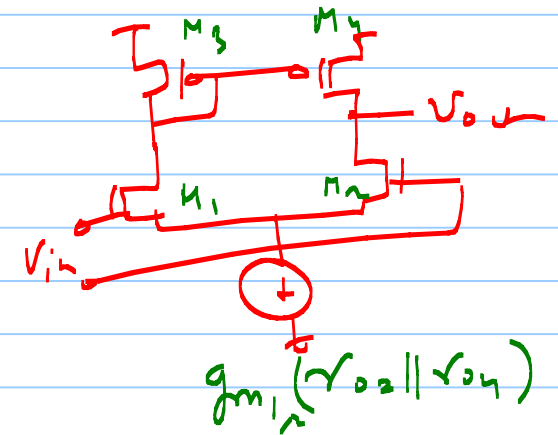

$$+ g_{m1,2} (R_{o,cas,p} \parallel R_{o,cas,n})$$

$$* \quad V_{cm, in} \geq V_{GS, 1/2} + \frac{V_{CSS}}{2V_{DS, sat}}$$

$$* \quad V_{cm, max} = ?$$

$$V_{D1,2} \leq V_{DD} - V_{SG} - \frac{V_{DS, sat}}{2} + V_{THN}$$


$$V_{cm, in} \leq V_{DD} - V_{SG} - V_{DS, sat} + V_{THN}$$

$$V_{cm, in} \in \left[\underbrace{V_{GS, 1/2} + V_{CSS}}_{}, \underbrace{V_{DD} - V_{SG} - V_{DS, sat} + V_{THN}}_{} \right].$$

$$\underline{\underline{V_{in,cm} - V_{THN} + V_{DS,sat} \leq V_{out} < V_{DD} - 2V_{SD,sat}}}$$

Performance Parameters:

① Gain:

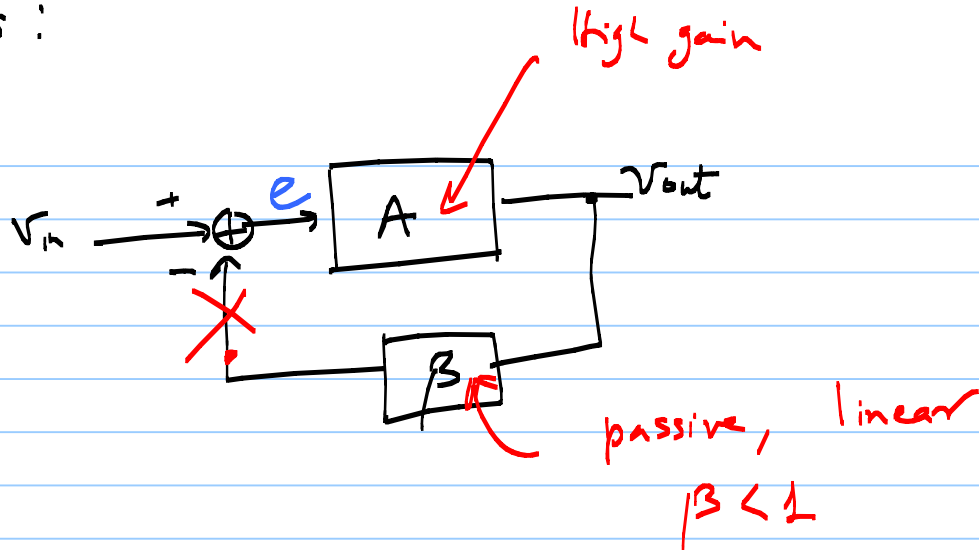

$$\underline{\underline{\frac{V_{out}}{V_{in}} = \frac{A}{1+A\beta}}}$$

$$e(t) \rightarrow 0$$

$$A\beta \gg 1$$

$A\beta \rightarrow$ open "loop gain"

$\frac{A}{1+A\beta} \rightarrow$ closed loop gain

$$\frac{V_{out}}{V_{in}} = \frac{A}{1+A\beta} \approx \frac{A}{A\beta} \approx \frac{1}{\beta}$$

$$= \frac{1}{\beta} \cdot \frac{1}{\frac{1}{A\beta} + 1}$$

$$= \underbrace{\frac{1}{\beta}} \left[1 - \underbrace{\frac{1}{A\beta}} \right]$$


relative error

$$A_{CL} = \frac{1}{\beta} = 10$$

< 1% relative error in gain

$$\frac{1}{A\beta} < \frac{1}{10}$$

$$A_{CL} = 10$$

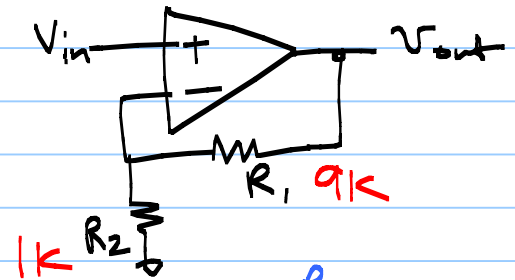

$$\beta = \frac{R_2}{R_1 + R_2} < 1$$



$$\frac{1}{1+x} \approx 1 - x + x^2 - x^3 + \dots$$

$$= 1 - x$$

$$|x| \ll 1$$

$$\frac{1}{A} < \frac{1}{1000} \Rightarrow A > 1000 \rightarrow 60 \text{ dB}$$

② Small-Signal Bandwidth:

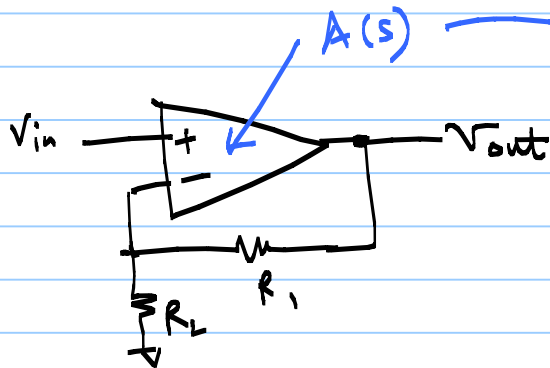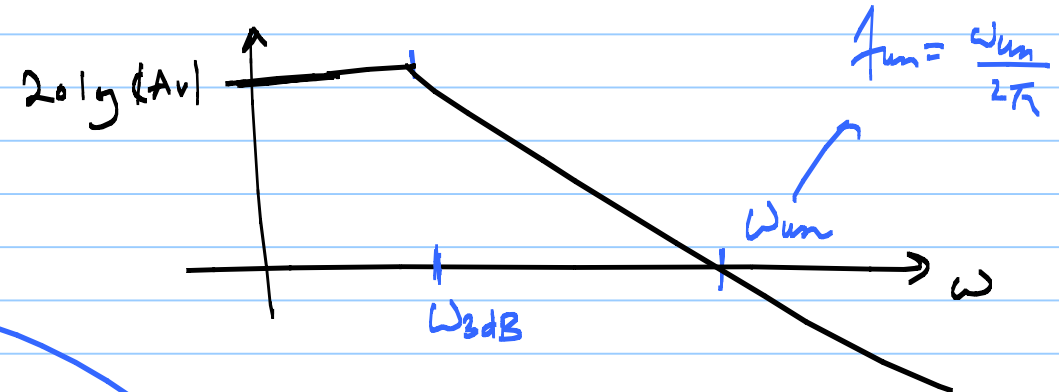

$$A(s) = \frac{A_0}{(1 + s/\omega_0)}$$

$$\frac{V_{out}}{V_{in}}(s) = \frac{A(s)}{1 + A(s)\beta}$$


$$= \frac{\frac{A_0}{(1+s/\omega_0)}}{1 + \frac{\beta A_0}{(1+s/\omega_0)}} = \frac{A_0}{1 + s/\omega_0 + \beta A_0}$$



$$= \frac{A_0}{(\beta A_0 + 1) + s/\omega_0} = \frac{\boxed{\frac{A_0}{1 + \beta A_0}}}{1 + \frac{s}{\omega_0(1 + \beta A_0)}}$$

$$= \frac{A_{CL}}{1 + \frac{s}{\omega_{2dB}}}$$

$\frac{A_0}{1 + \beta A_0}$
 $\omega_0(1 + \beta A_0)$

$$\frac{1}{\beta} = 10$$

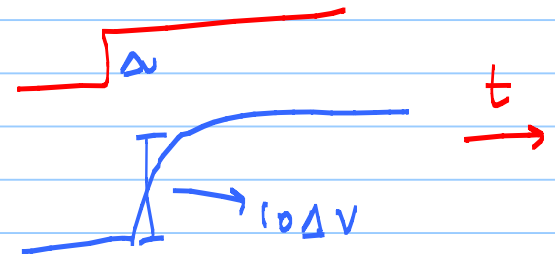

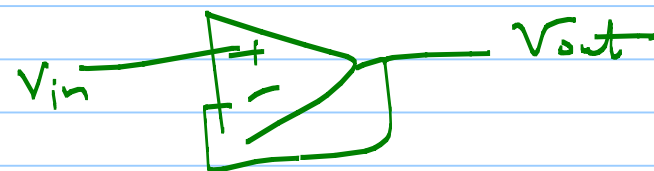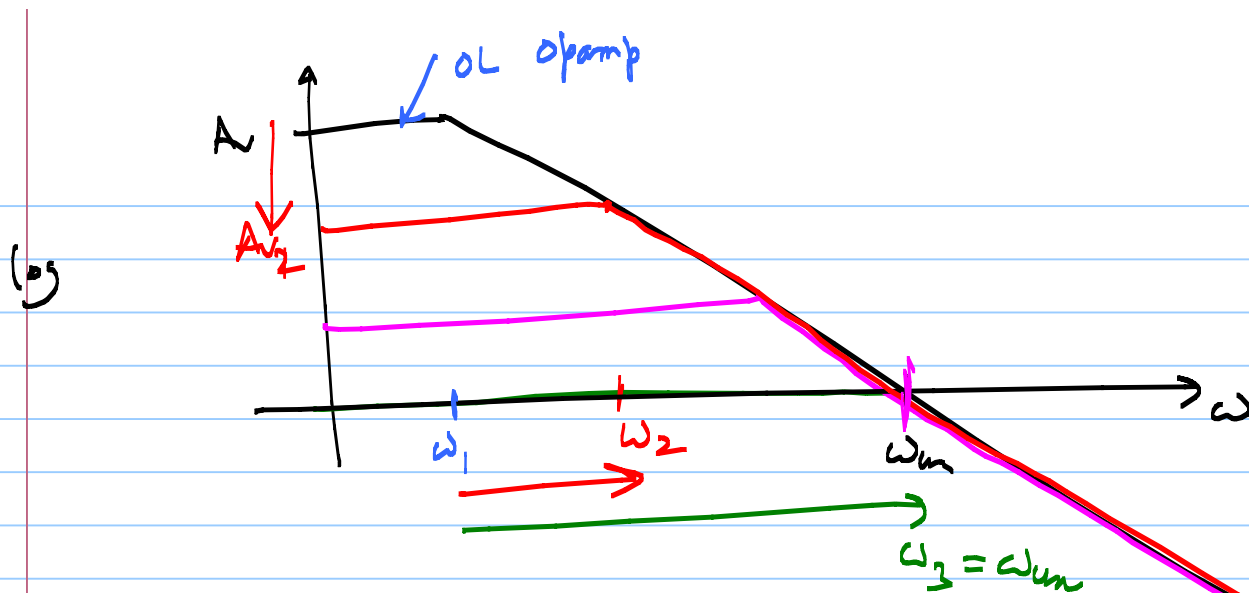

Gain-BW trade off

* Assuming Dominant pole response

$$\frac{V_{out}}{V_{in}} = \frac{A_{CL}}{1 + sZ} = \frac{A_u}{1 + s/\omega_{3dB}}$$

$$Z = \frac{1}{\omega_0(1 + A_0\beta)}$$

$$\omega_{3dB} = \omega_0(1 + A_0\beta)$$

$$\approx \omega_0 A_0 \beta$$

$$= \omega_{un} \cdot \beta$$

$$= \omega_{un} \cdot \frac{1}{A_{CL}}$$

$$\Rightarrow \boxed{\omega_{3dB} \times A_{CL} = \omega_{un}} \quad \begin{array}{l} \text{GB} \\ \text{Trade off} \end{array}$$


$$V_{in} \quad \text{[step function]} \quad = a u(t) \quad \xleftrightarrow{\quad} \quad \frac{a}{s}$$

$$A_{cc}(s) = \frac{A_{cc}}{(1 + s\tau)} \quad \rightarrow \quad \tau = \frac{1}{\omega_0(1 + A_0\beta)}$$

$$V_{out}(s) = A_{cc}(s) \cdot \frac{a}{s}$$

$$= \frac{a A_{cc}}{s(1 + s\tau)}$$
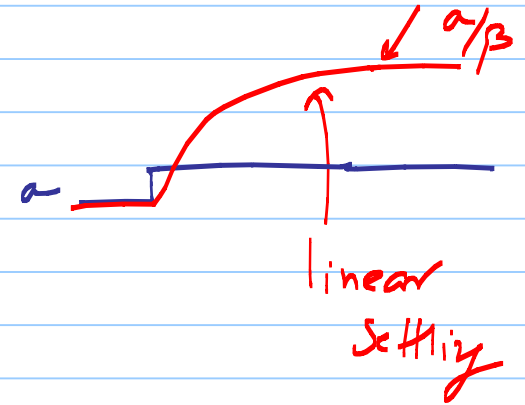
$$V_{out}(t) = \mathcal{L}^{-1}(\quad) = \underbrace{a \cdot \frac{1}{\beta}}_{\text{final value}} (1 - e^{-t/\tau}) u(t)$$



for 1% settling

$$t_{1\%} = 4.6\tau = 5ns \quad \text{with} \quad \frac{1}{\beta} = 10$$





$\rightarrow \omega_{24\beta} = 1.09ns$

$$\omega_{um} = \omega_{3dB} \times A_{cl}$$

$$= 10 \times \frac{1}{1.09 \text{ ns}}$$

$$= 9.2 \times 10^9 \text{ rad/s} \xrightarrow{\frac{1}{2\pi}} \underline{f_{um} = 1.47 \text{ GHz}}$$


③ Large Signal Bandwidth $au(t)$

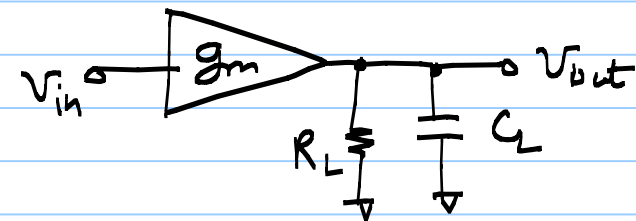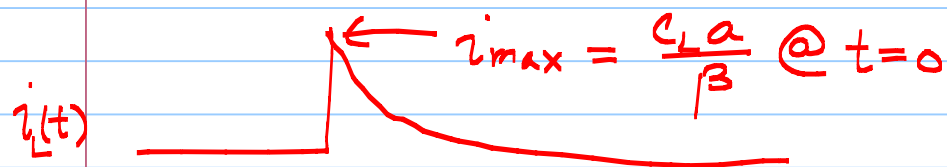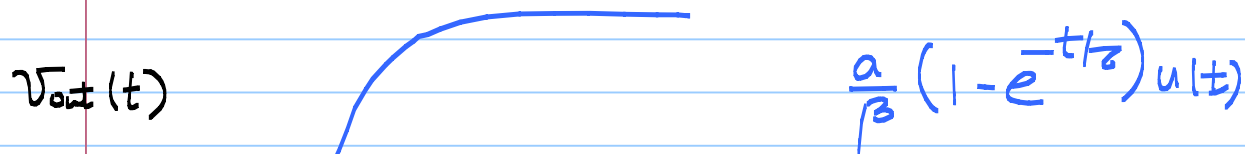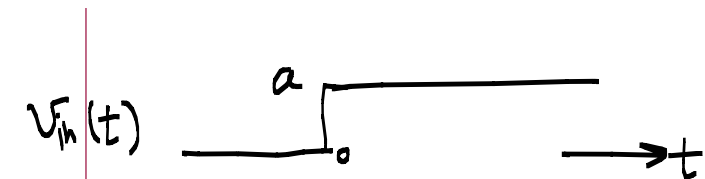

If the max current needed to drive the load $i_{max} > I_L$, the max current sourced/sunk by the amplifier $\Rightarrow$ slewing occurs.

$$i_L(t) = C_L \frac{dV_{out}}{dt}$$
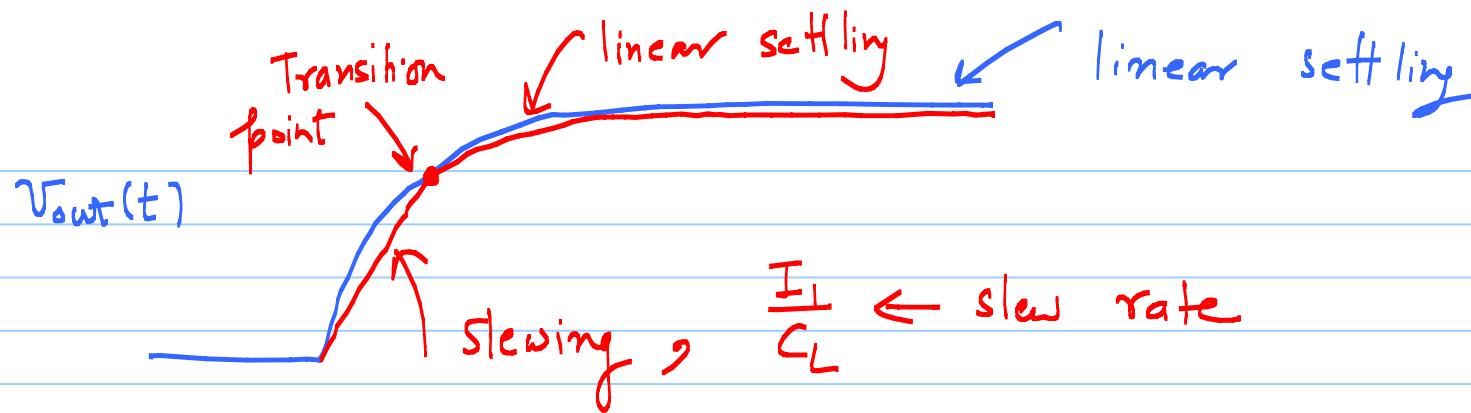
$$= C_L \frac{a}{\beta} e^{-t/\tau} \cdot u(t)$$



* Slewing is a non-linear behavior

↳ leads to distortion in output signal.

↳ mandates experience and careful simulations.

④ Output Swing -

trades-off with device size, overdrive, bias currents & speed.

↳ fully-differential circuits

⑤ Linearity:

- ① Use fully-diff implementation to suppress even-order harmonics
- ② Allow efficient open-loop gain so that the closed-loop system achieves reasonable linearity.

⑥ Noise & offset:

The input noise and offset of opamps determine the minimum signal level, which can be with reasonable quality.

↳ noise analysis

⑦ Power Supply rejection:

supply noise leaks into the signal path

↳ use fully-differential opamps.