

ECE 5411 - Lecture 22

Note Title



4/20/2011

Ex.

$$V_{DD} = 3V$$

$$V_{THN} = V_{THP} = 0.7V$$

$$V_{ov} = V_{DS,sat} = 0.3V$$

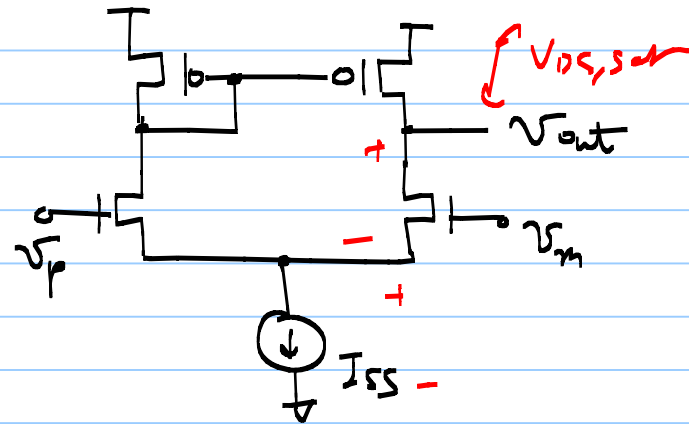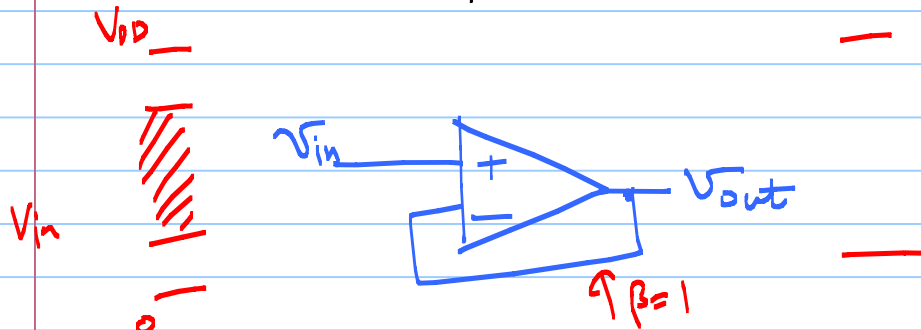

* What is the input CMR = ?


* Closed-loop output impedance

$$V_{in, cm} \in [V_{GS1,2} + V_{DS,sat}, V_{DD} - V_{SG3} + V_{THN}]$$
$$= [1.3, 2.7]$$
$$\quad \quad \quad \underbrace{\hspace{1cm}}_{1.4V}$$

$$R_{o,CL} = \frac{R_{o,OL}}{1 + \text{loop-gain}}$$

$$= \frac{r_{op} || r_{on}}{g_{m1/2}}$$

$$\frac{1}{g_{m1,2}}$$

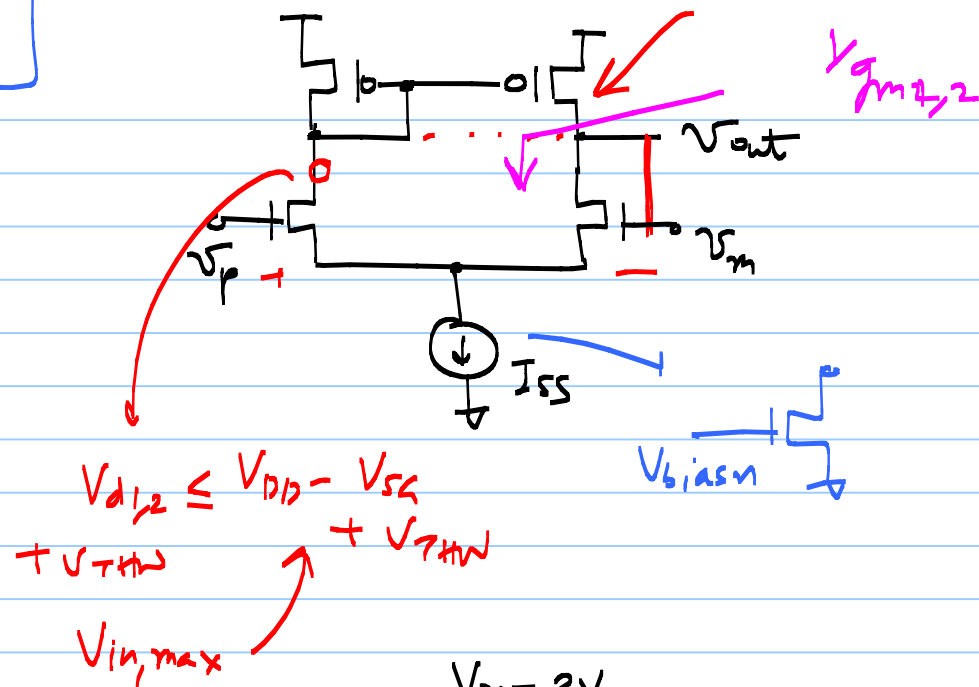

$$V_{DD} = 3V$$

$$V_{THN} = V_{THP} = 0.7 \text{ V}$$


$$V_{OV} = V_{DS,sat} = 0.3V$$

x Both M_2 & M_4 must be in SAT.

$$V_{out} \leq V_x + V_{THN} \longrightarrow \textcircled{1}$$

$$V_{out} \approx V_{b5} - V_{THN} \longrightarrow (2)$$

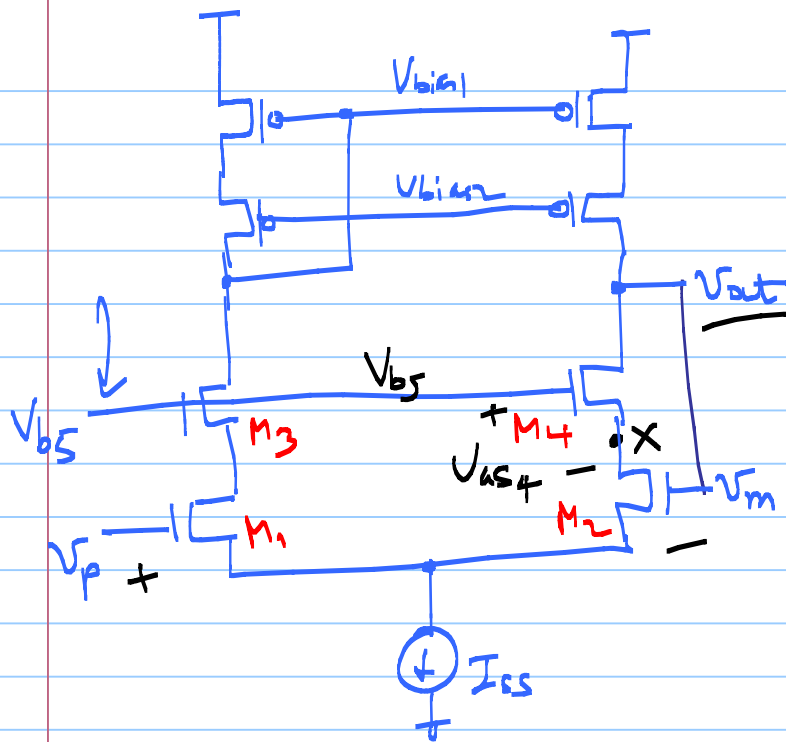
$$V_x = V_{b5} - V_{a5} \longrightarrow (3)$$




$$\underbrace{V_{b5} - V_{THN}}_{V_{o,min}} \leq V_{out} \leq \underbrace{V_{b5} - V_{asq} + V_{THN}}_{V_{o,max}}$$

$$V_{\text{max}} - V_{\text{min}} = 2V_{\text{THN}} - V_{\text{asy}} = V_{\text{THN}} - V_{\text{ouy}}$$

NMOS Cascode

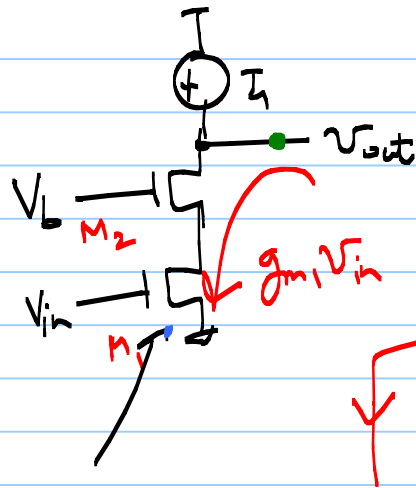



Folded Cascode

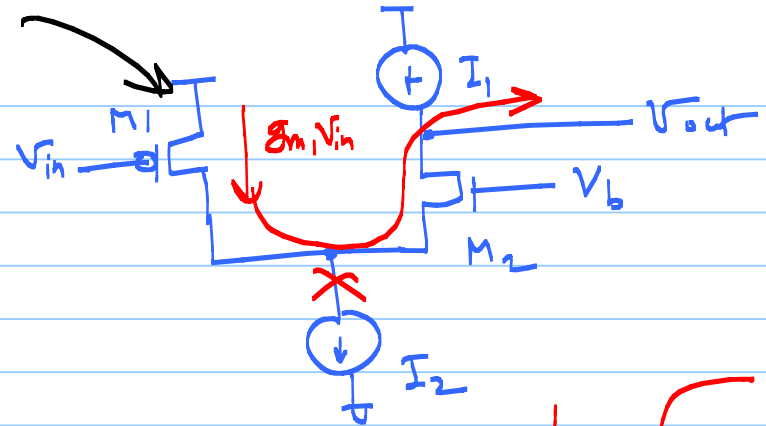


* input device is replaced by the opposite

* Small-signal current $g_{m1}v_{in}$ is folded up through M_2
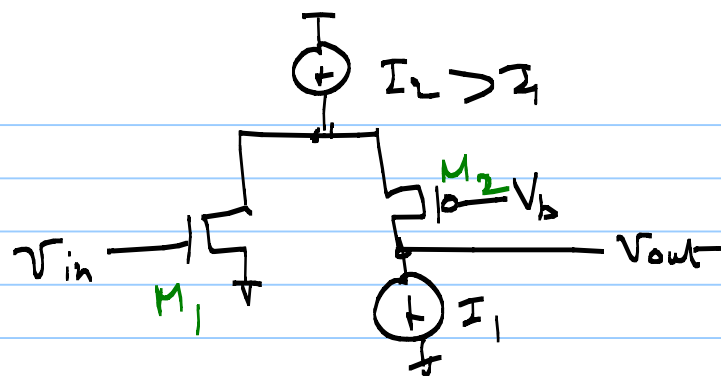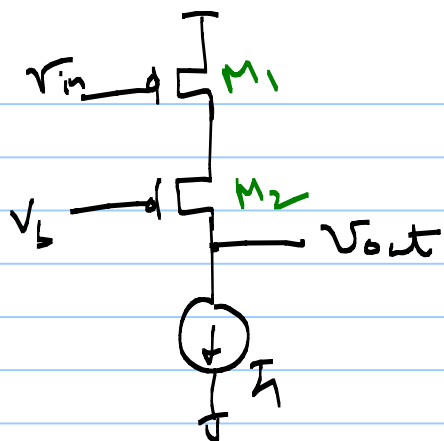
$$* A = -g_m R_{out} = -g_{m1} (g_{m2} r_{o2} r_{o1})$$



FD representation CMFB not shown

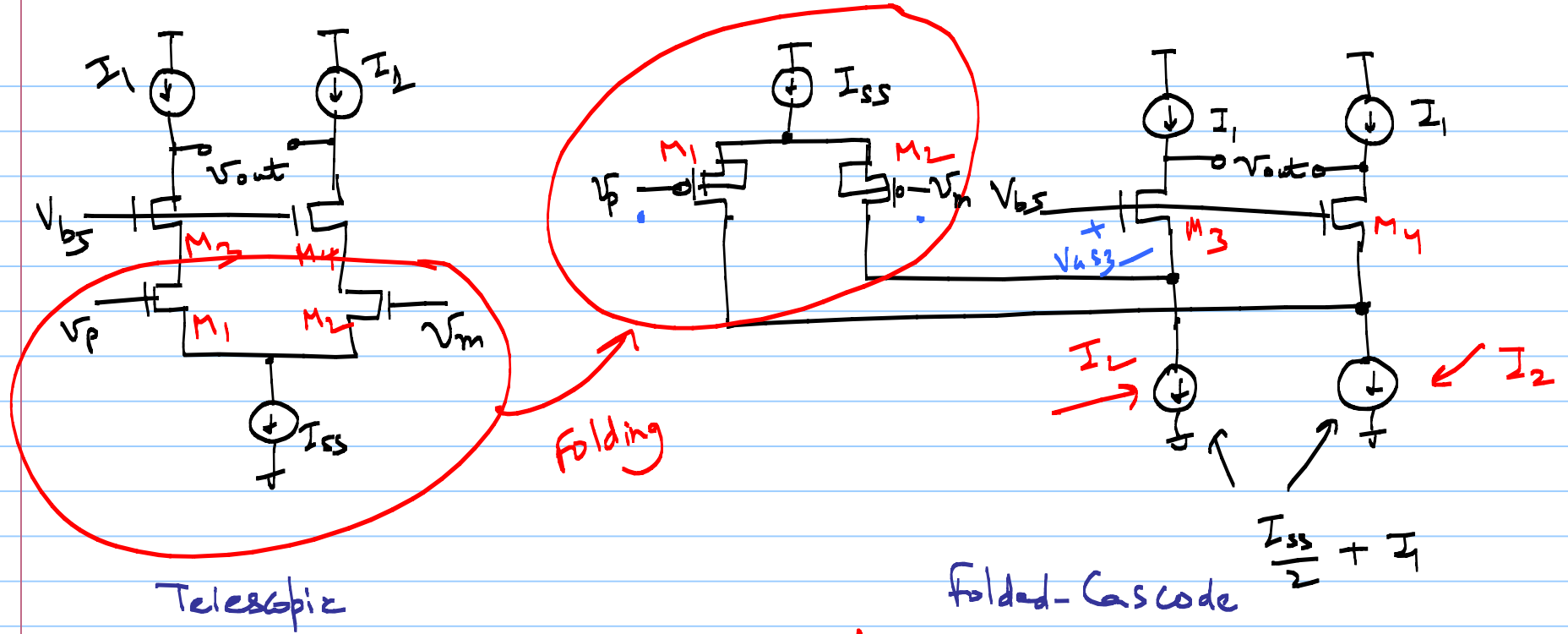


$$\underline{\underline{V_{in,min} \leq V_{b5} - V_{as} + V_{THN} = V_{in,max}}}$$

$$V_{in,min} = ?$$

$$V_{in,min} \geq V_{b5} - V_{as3} - V_{THP} \leftarrow$$

$\Rightarrow$ possible to short Input & Output

Single-Ended folded-Cascode Diffamp.

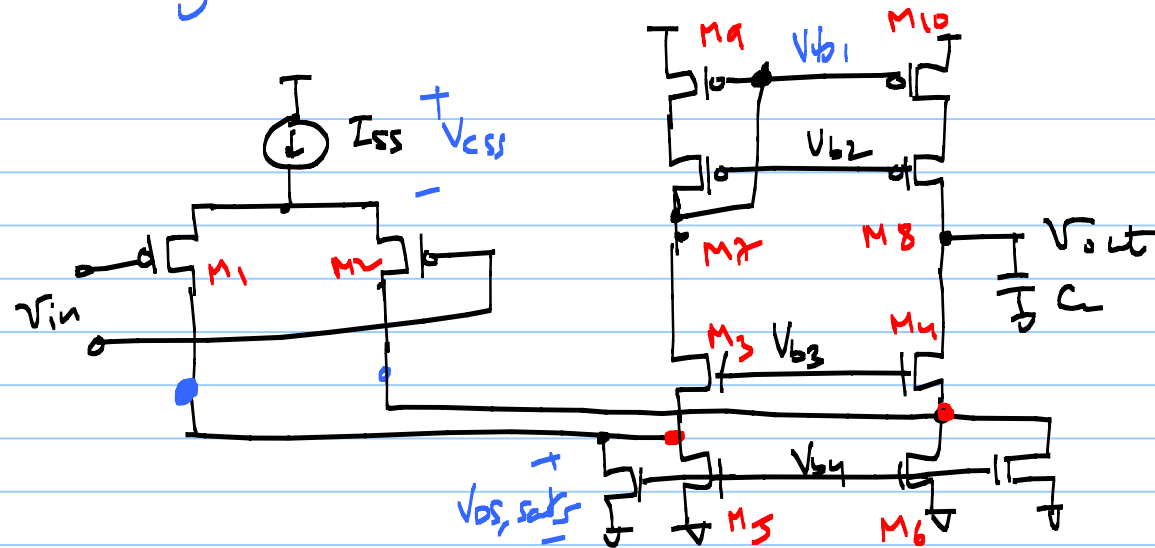

$$I_{bias} = \frac{I_{SS}}{2}$$



$$V_{cm,in} \leq V_{DD} - V_{CSS} - V_{SG1,2}$$

$$V_{d1} \geq V_{DS,sat5} - V_{THP}$$

$$V_{cm,in} \geq V_{DS,sat5} - V_{THP} < 0$$

$$V_{cm,in} \in [V_{DS,sat} - V_{THP}, V_{DD} - \underline{V_{SS}} - \underline{V_{SG,2}}]$$
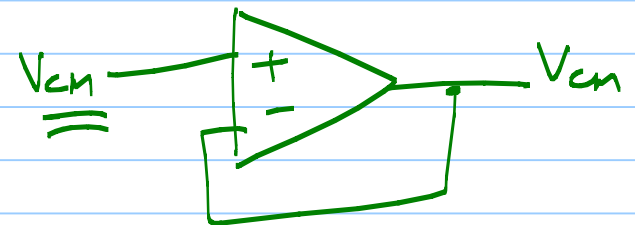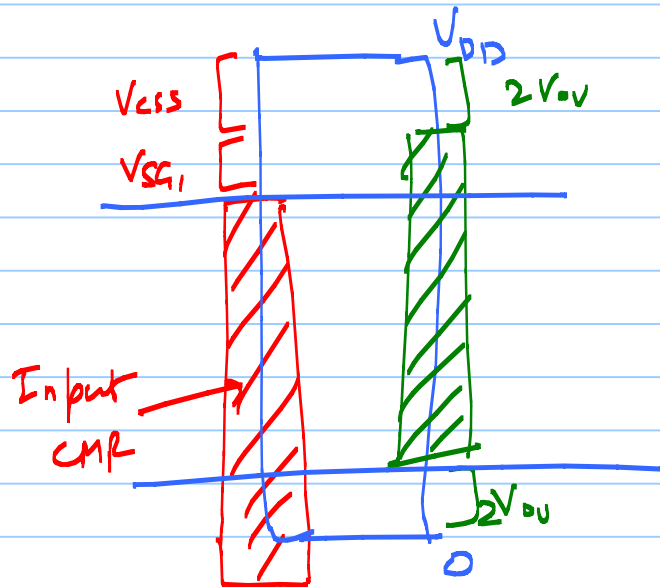
$$V_{out} \in [2V_{DS,sat}, V_{DD} - 2V_{SD,sat}]$$



fully - Diff Circuits

odd function

$$y = \frac{f(x) - f(-x)}{2}$$

$x=a$

$$= \cancel{f(a)} + \frac{f'(a)(x-a)}{1} + \frac{f''(a)(x-a)^2}{2} + \dots$$

$$- \left[\cancel{f(a)} - \frac{f'(a)(x-a)}{1} + \frac{f''(a)(x-a)^2}{2} \right]$$


$$= (x-a), \frac{(x-a)^3}{1 \cdot 3}, \dots$$

$\Rightarrow$ only odd order terms remain in the output


(a)

$$R_{out} = g_{m2} r_{o2} r_{o1}$$

(b)

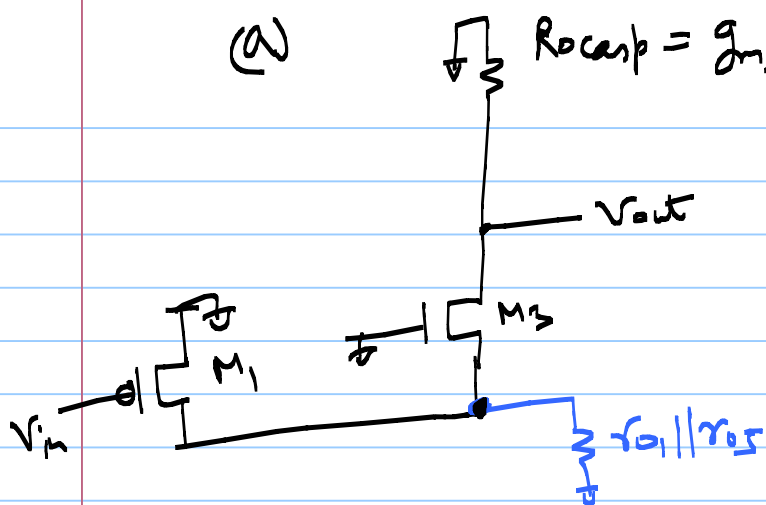

$$C_{in} = g_{m1}$$

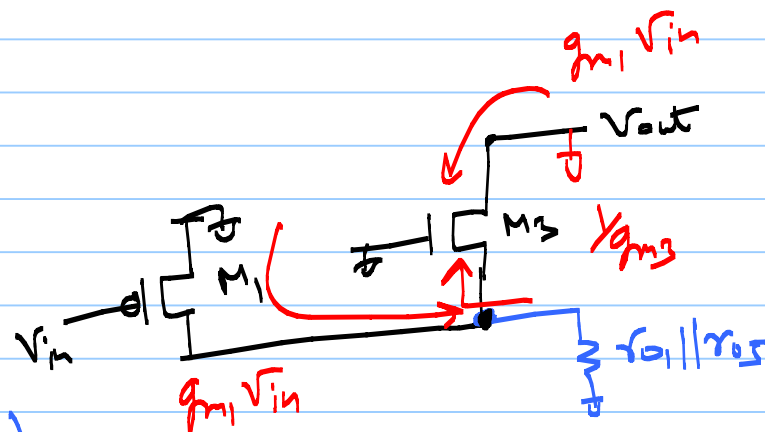

$$(c) R_{out} = \underbrace{(g_{m2} r_{o2} r_{o1})}_{g_{mp} r_{op}^2} \parallel g_{m3} r_{o3} (r_{o1} \parallel r_{o5})$$

$$1/g_{m3} \ll r_{o1} \parallel r_{o5}$$

$$A_v = + g_{m1} R_{out}$$

$$A_v = \underline{\underline{g_{m1}}} \left\{ \underbrace{g_{m3} r_{o3} (r_{o1} \parallel r_{o5})}_{g_{mn} r_{on} \parallel \frac{r_{on}}{2}} \parallel g_{m7} r_{o7} r_{o9} \right\}$$



$$< g_{mn} r_{on}^2$$

↳ gain is roughly 2-3x lower than Telescopic Diffamp.

Pole location.

* Output pole $\Rightarrow \omega_{p1} = \frac{1}{R_{out} C_L}$ ← roughly the same as Telescopic

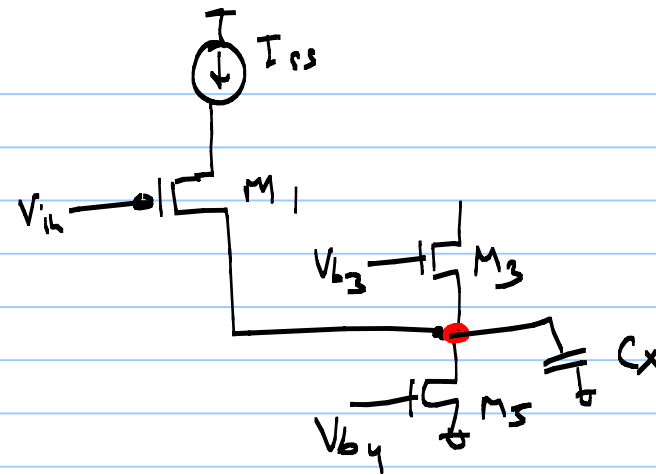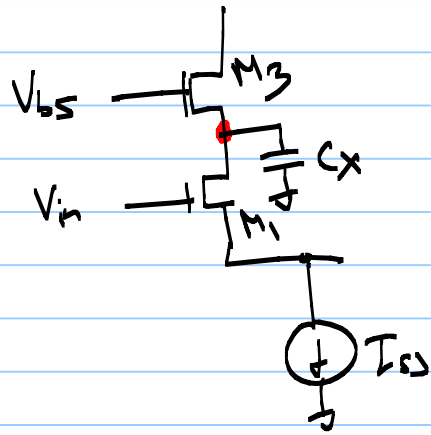* Mirror pole $\Rightarrow \omega_{p2} \Rightarrow$ same



* ω_{px} is lower for fc