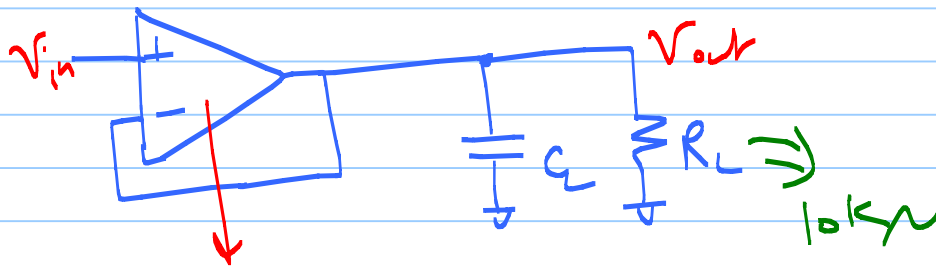


ECE 5410 - Lecture 23.

Note Title



4/25/2011




$$A \approx -g_m \underline{R_{out}}$$

A green arrow points from the underlined R_{out} in the equation to the text $10M\Omega$.


heavy load
Large Cap
Small Resistor

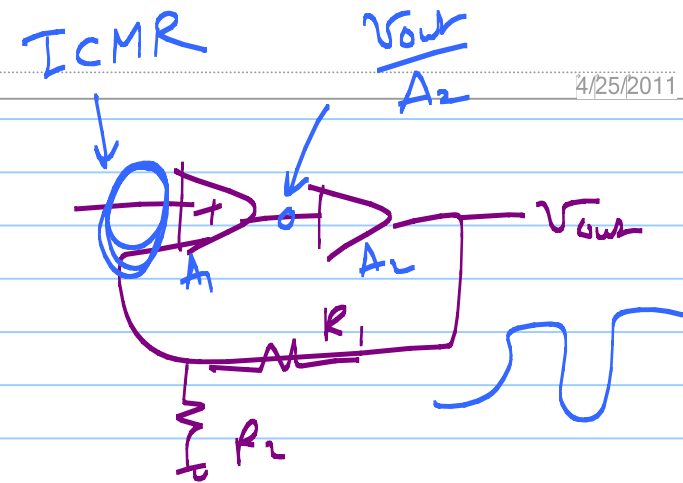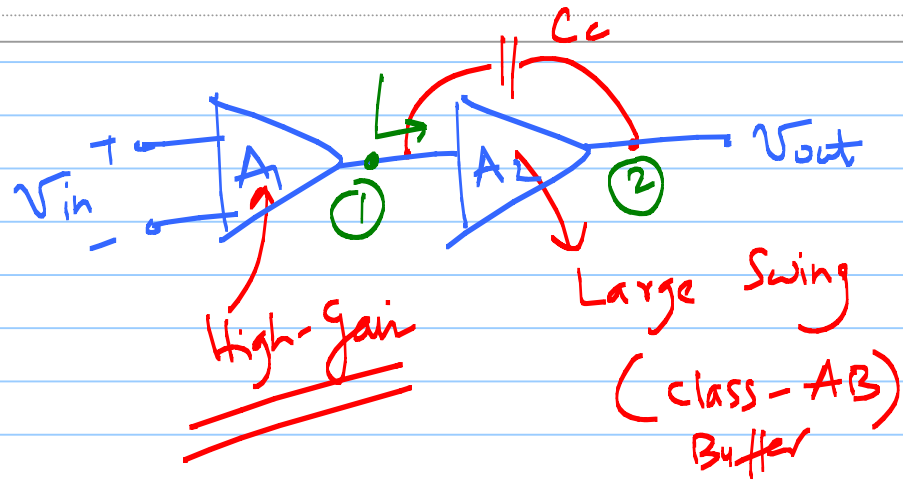

CMRR

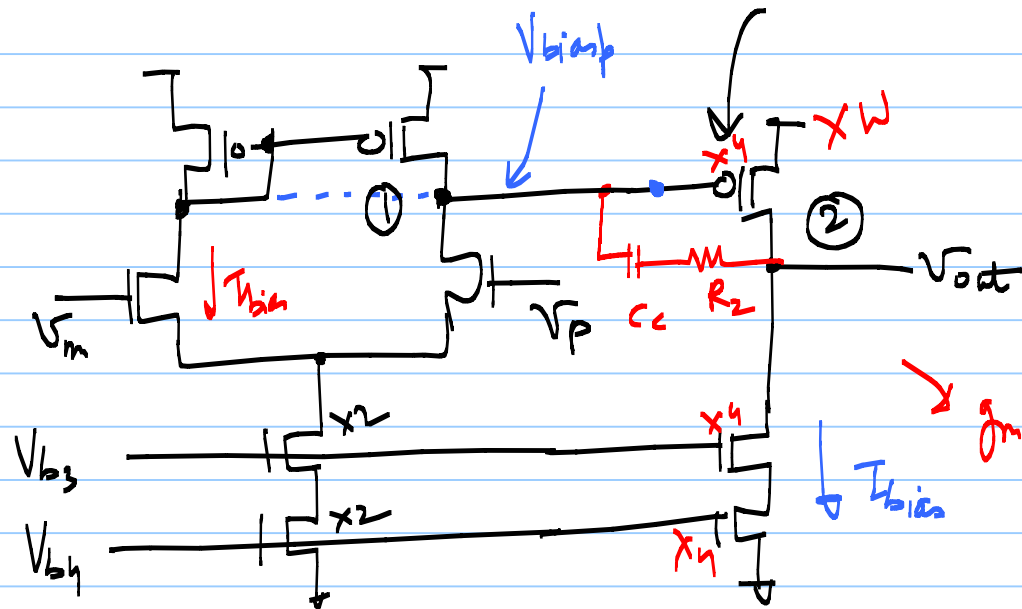

$$A_1 = g_{m1} R_1$$

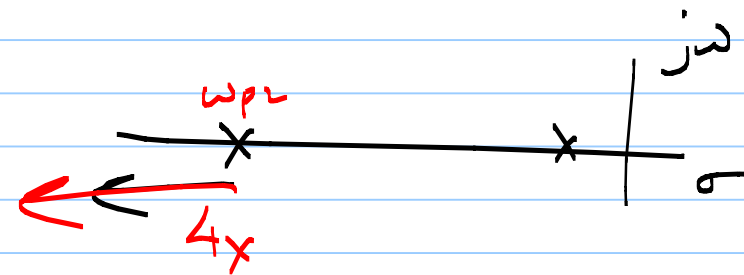

$$\rightarrow g_{m2} = 4g_{m1}$$

$$\underline{\underline{f_{un} = \frac{g_{m1}}{2\pi C_o}}}$$

$\omega_{p2} \uparrow \uparrow$

Cascode Compensation
(Indirect)

* LHP zero

* $\omega_{p2} = \frac{g_{m2} (g_{mca} R_1)}{C_c}$

→ High-Speed Compensation

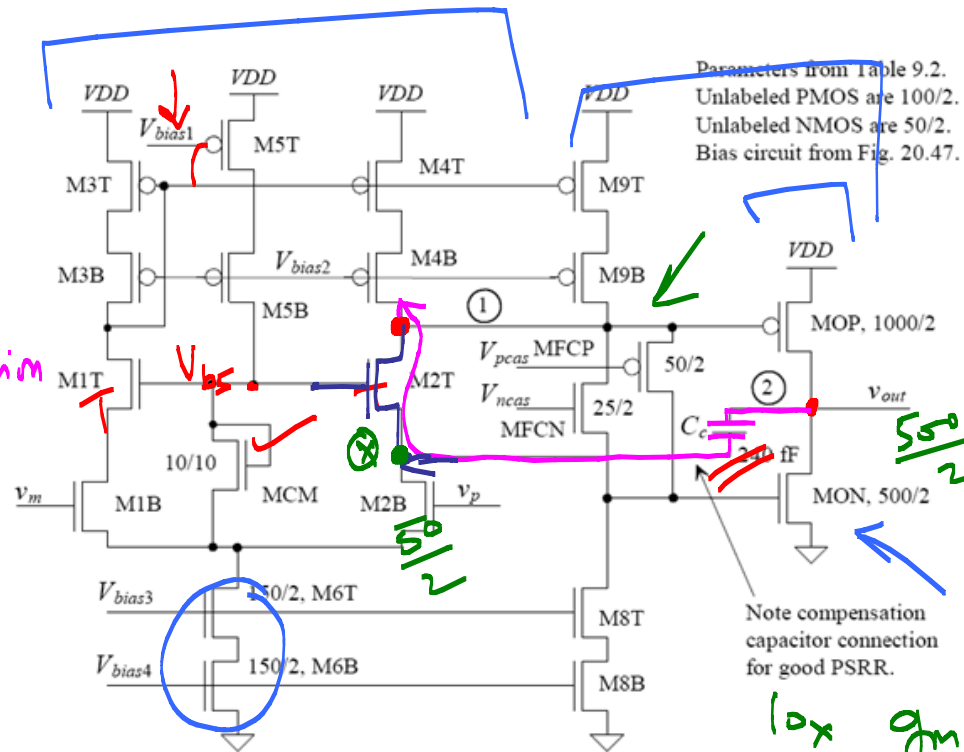


Figure 24.29 A CMOS op-amp with output buffer.

* Not Miller Compensated!

Class-AB output stage

$\omega_{p2} \approx g_{m2}$


* Smaller $C_c \rightarrow f_{un} \uparrow \uparrow$

* Be careful about ω_{px}

$$\omega_m = \frac{g_m}{C_c}$$

closed-loop response
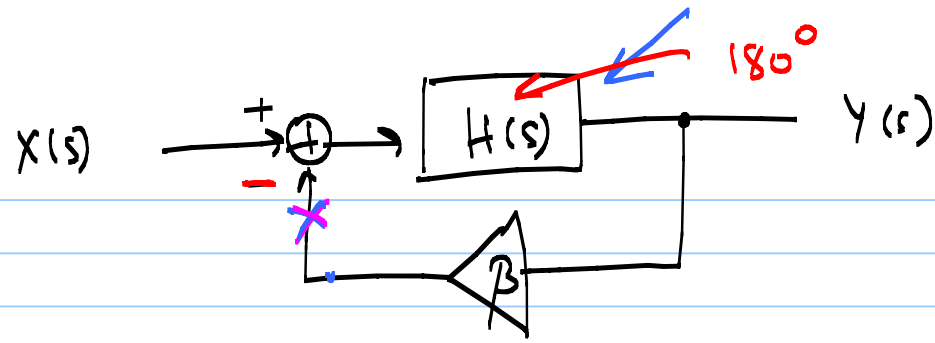
$$\frac{Y(s)}{X(s)} = \frac{H(s)}{1 + \beta H(s)}$$




open-loop response

$\beta < 1$, constant

if $\beta H(s) = -1 \Rightarrow$ closed-loop gain $= \infty$

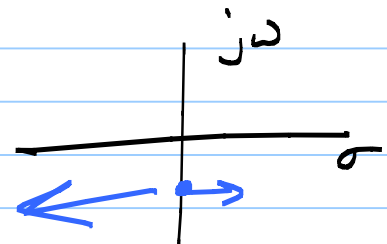→ circuit can amplify its own noise
& start oscillation.







$$\begin{cases} |\beta H(j\omega_1)| = 1 \\ \angle \beta H(j\omega_1) = -180^\circ \end{cases}$$

← Barkhausen's Criterion



$$|\beta_H(j\omega)| \geq 1$$


→ overall 360° phase-shift
in the loop

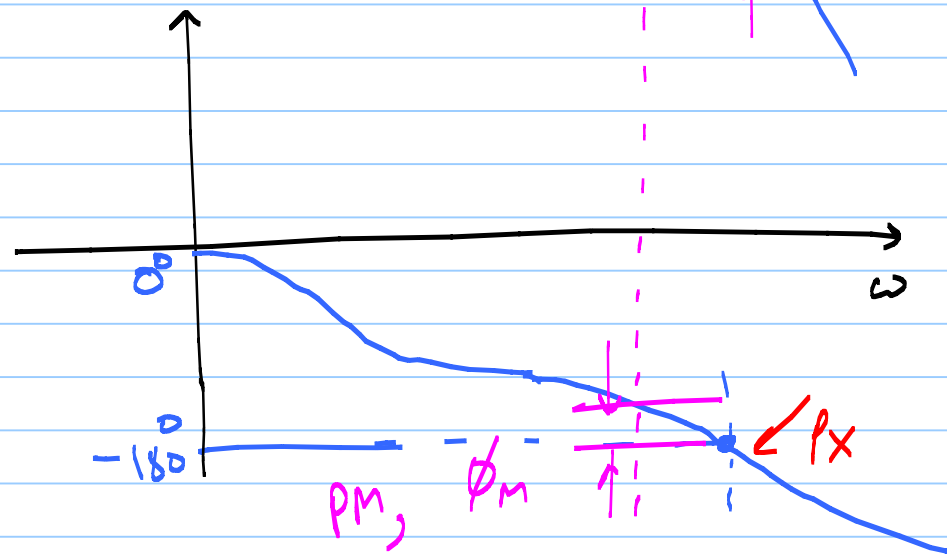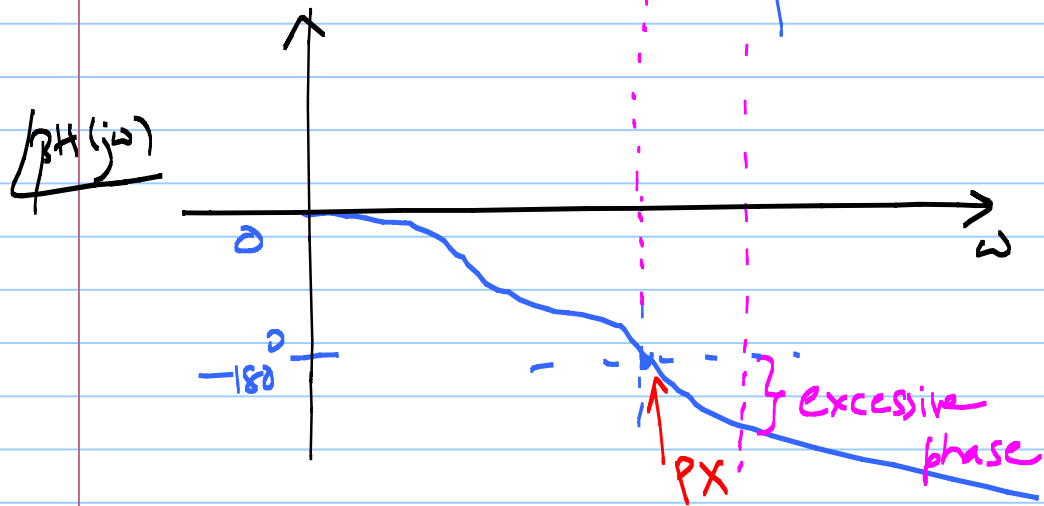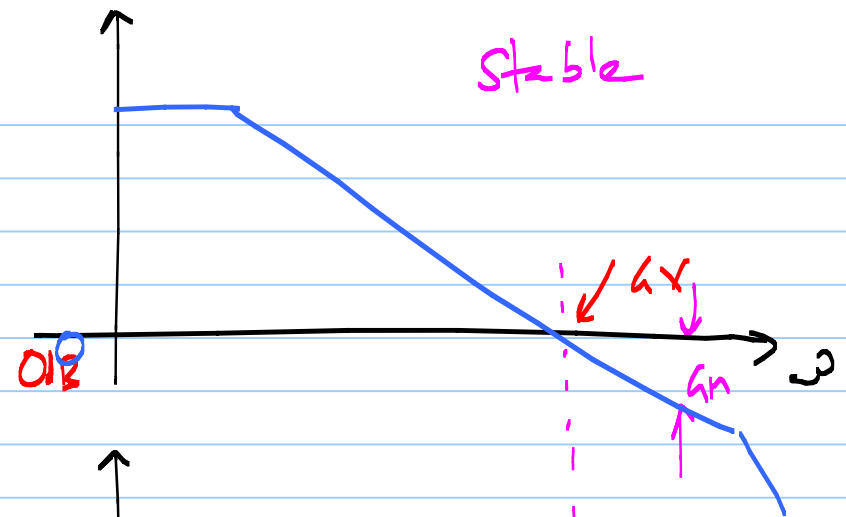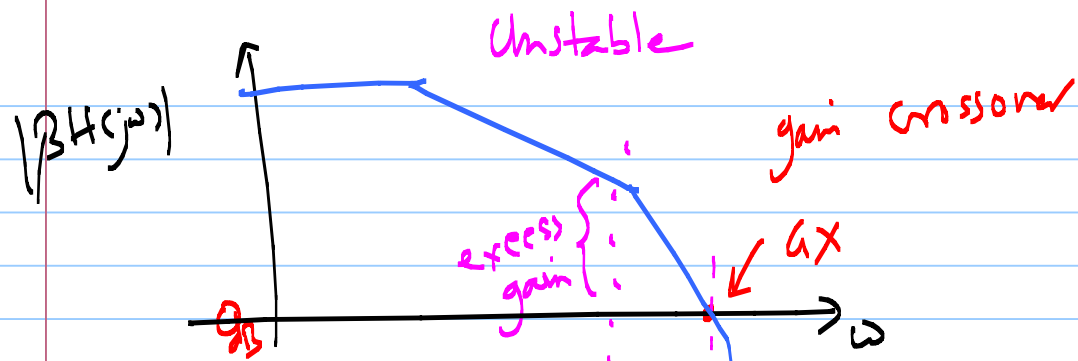


* for stable system G_X should occur before P_X .


$$\beta \in [0, 1]$$

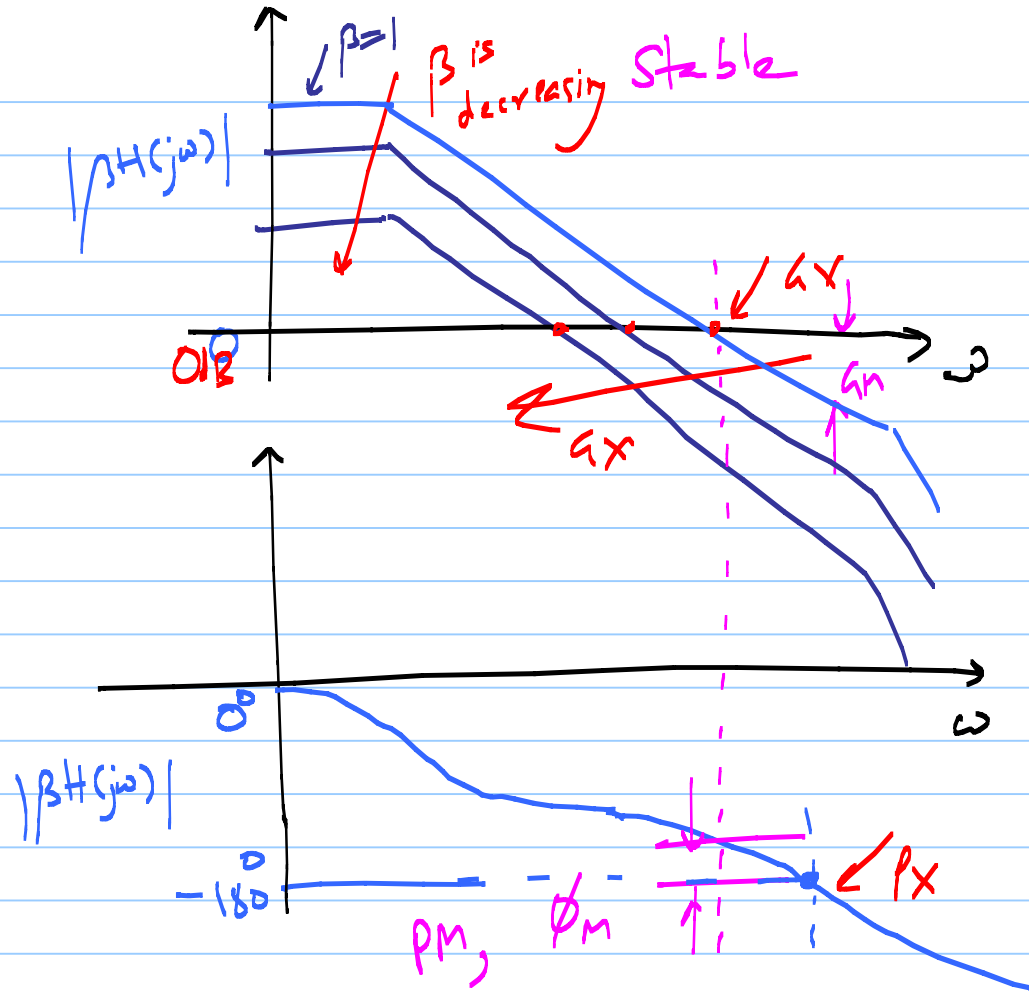→ Looking for $\beta=1$ is sufficient to test stability



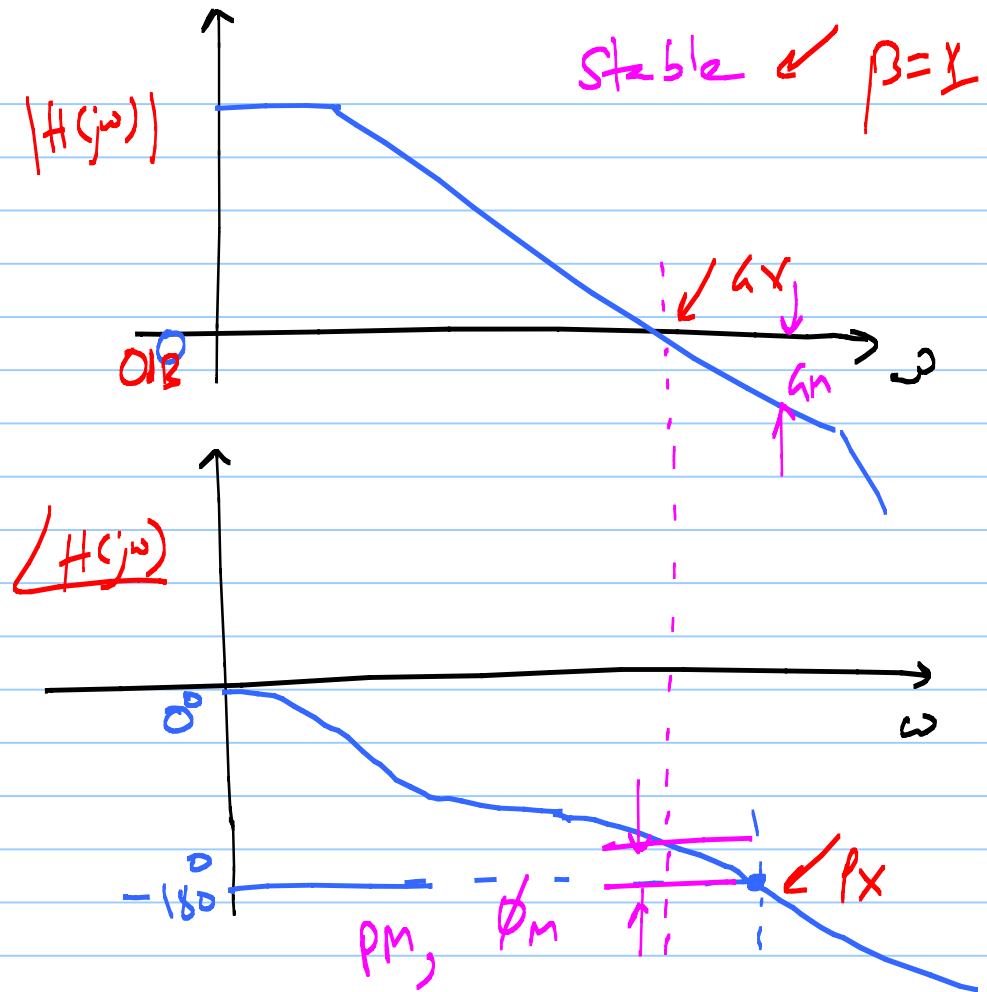* The worst case stability is for $\beta = 1$.



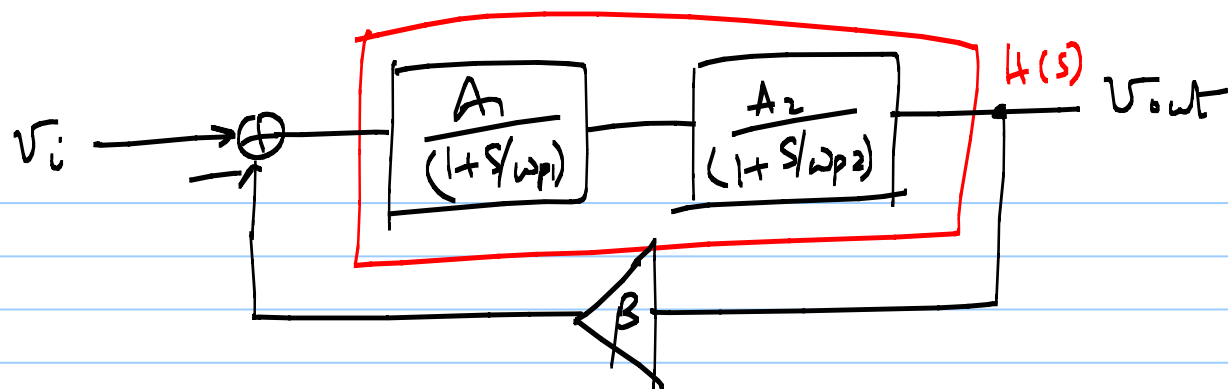


$$A_0 = A A_2$$

ω_{p1}
 ω_{p2} } Open loop poles

$$\frac{V_o}{V_i}(s) = \frac{k}{1 + \frac{k}{A_0} + s\left(\frac{1}{\omega_{p1}} + \frac{1}{\omega_{p2}}\right) + \frac{s^2}{\omega_{p1}\omega_{p2}} \cdot \frac{k}{A_0}}$$



$$\text{DC gain} = \frac{k}{1 + k/A_0} \rightarrow k \text{ as } \frac{A_0}{k} \gg 1$$

$$\beta A_0 \gg 1$$

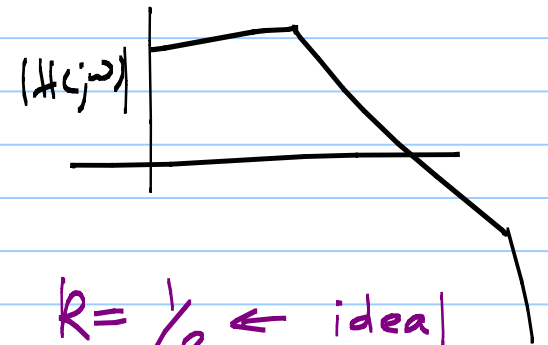

$k = 1/\beta \leftarrow$ ideal closed-loop gain

Root locus

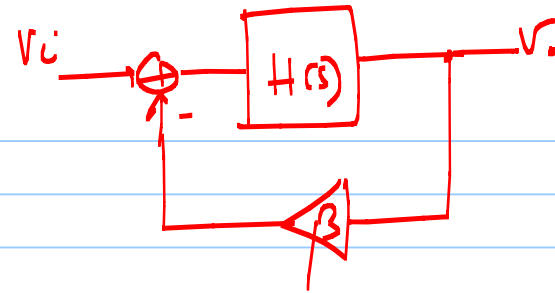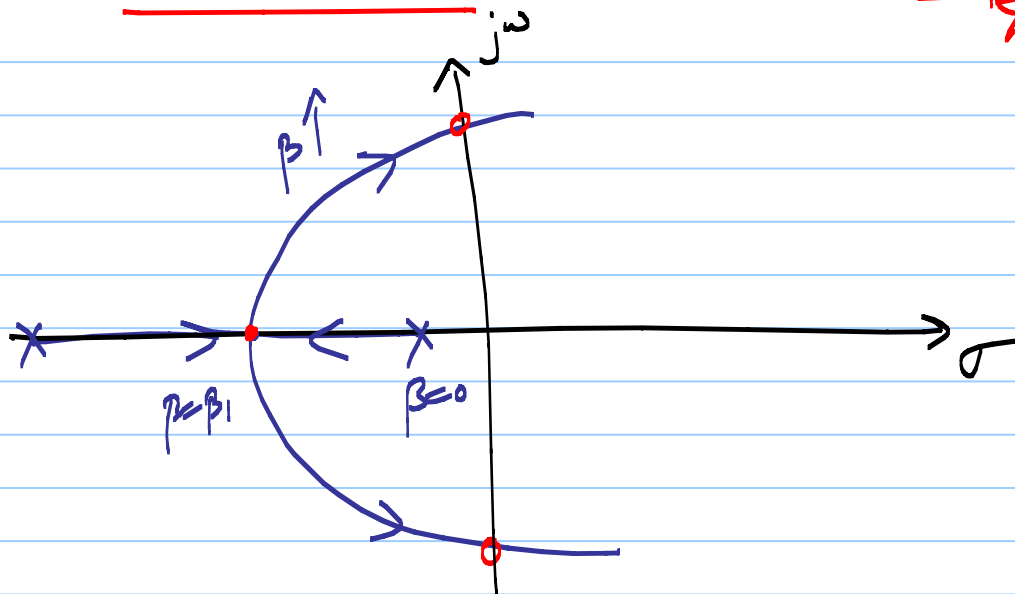

↑
locus of the roots of
the closed loop
system as β is
varied.

$$\frac{V_o}{V_i}(s) = \frac{k}{1 + \frac{k}{A_o} + s\left(\frac{1}{\omega_{p1}} + \frac{1}{\omega_{p2}}\right) + \frac{s^2}{\omega_{p1}\omega_{p2}} \cdot \frac{k}{A_o}}$$

$$\frac{V_o}{V_i}(s) = \frac{k}{\left(\frac{s}{\omega_o}\right)^2 + \left(\frac{s}{\omega_o Q}\right) + 1} = \frac{k}{\left(\frac{s}{\omega_o}\right)^2 + 2\zeta\left(\frac{s}{\omega_o}\right) + 1}$$

damping factor $\leftarrow \zeta = \frac{1}{2Q} \leftarrow$ pole Quality factor $\hat{=} \frac{Y}{X} = \frac{\sigma_n}{\omega_n}$


$\omega_o = \sqrt{\omega_{p1}\omega_{p2}} \leftarrow$ natural frequency

$$\zeta = \frac{1}{2} \sqrt{\frac{k}{A_0}} \left[\sqrt{\frac{\omega_{p2}}{\omega_{p1}}} + \sqrt{\frac{\omega_{p1}}{\omega_{p2}}} \right] \quad \leftarrow \text{Damping factor}$$

$\zeta > 1 \leftarrow$ overdamped

$\zeta = 1 \leftarrow$ critically damped

$\zeta < 1 \leftarrow$ underdamp

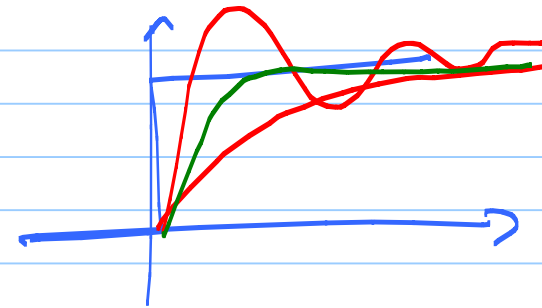

* $\zeta = \frac{1}{\sqrt{2}}$ (fastest)
Best settling time

$$\omega_{p2} = \frac{2 A_0 \omega_{p1}}{k}$$

$$= 2 \omega_{un}$$

$$\phi_m \approx 90^\circ - \tan^{-1} \left(\frac{\omega_{un}}{\omega_{p2}} \right)$$

$$= \underline{\underline{63.5^\circ}}$$

if $\phi_m = 60^\circ \Rightarrow \zeta = 0.66$

$$\underline{\underline{45^\circ - 65^\circ}}$$