

ECE 5411 → Lecture 24


Note Title

4/27/2011


$$\Rightarrow \phi_M = 63.5^\circ$$

$$\zeta_y = \frac{1}{\sqrt{2}}$$


t_{settle} is minimize

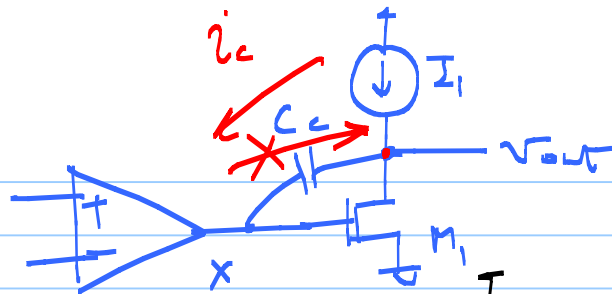

Miller

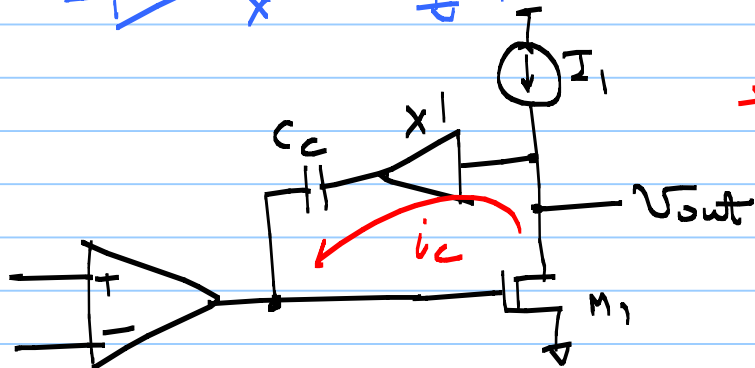


* No RHP zero

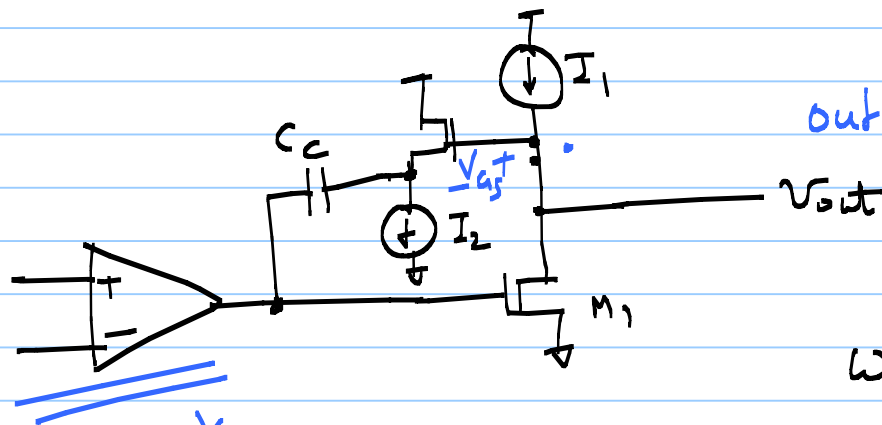

output swing is less.
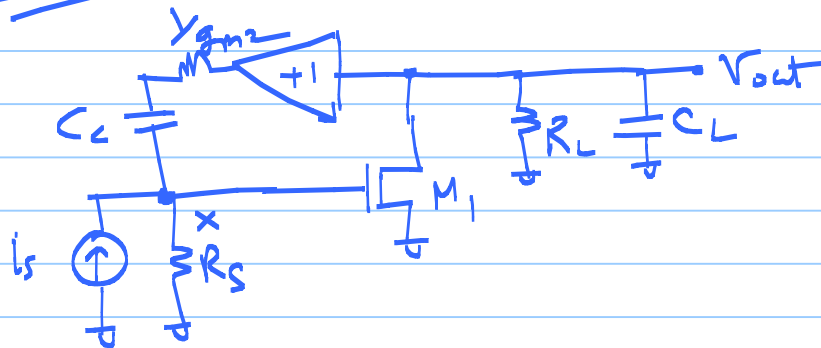
$$\omega_{p1} \approx \frac{1}{g_{m1} R_L R_S C_c}$$




$$\omega_{p2} \approx \frac{g_{m1}}{C_L}$$


$$\omega_z = -\frac{g_{m2}}{C_c} \leftarrow \text{LHP zero}$$

Use a CG Stage

"1983 Ahuja Compensation"

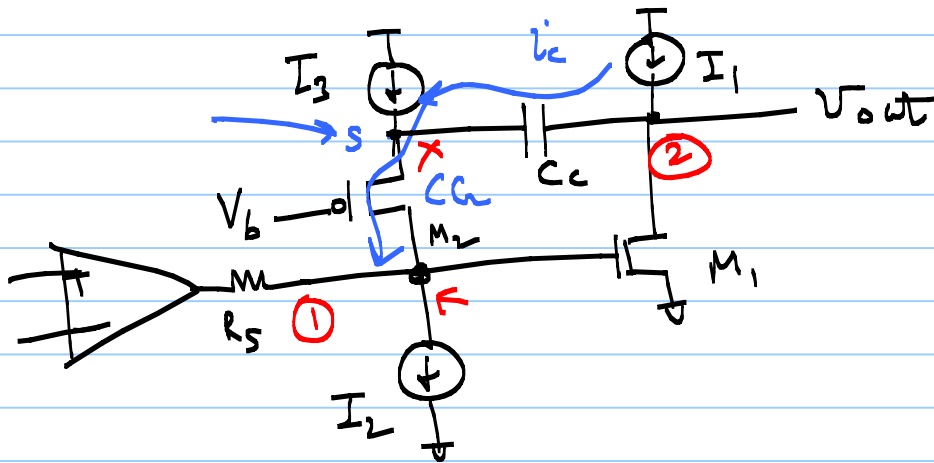

Assume $\lambda = \gamma = 0$

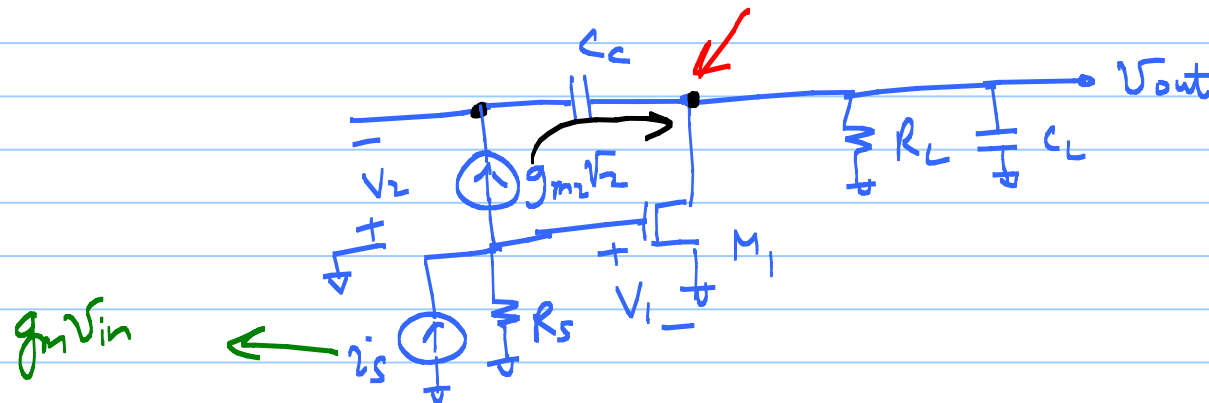

$$KVL \Rightarrow V_{out} + \frac{g_{m2} V_2}{sC_c} = -V_2$$

$$\Rightarrow V_2 = -V_{out} \frac{sC_c}{g_{m2} + sC_c} \rightarrow (1)$$

$$KCL @ V_{out} \Rightarrow g_{m1} V_1 + V_{out} (R_L^{-1} + sC_c) = g_{m2} V_2 \rightarrow (2)$$

$$KCL @ input \Rightarrow i_{in} = \frac{V_1}{R_s} + g_{m2} V_2 \rightarrow (3)$$

$$\frac{V_{out}}{i_s} = \frac{-g_{m1} R_s R_L (g_{m2} + sC_c)}{R_L C_L C_c s^2 + [(1 + g_{m1} R_s) g_{m2} R_L C_c + C_c + g_{m2} R_L C_L] s + g_{m2}}$$

$$\omega_z = - \frac{g_{m2}}{C_c} \quad \leftarrow \text{CA Device} \quad \leftarrow \text{Can use to improve } \phi_m$$

$$\omega_{p1} = \frac{1}{g_{m1} R_L R_S C_c} \quad \leftarrow \text{Same as Miller}$$


$$\omega_{p2} = (g_{m2} R_S) \frac{g_{m1}}{C_L} \quad \leftarrow \underbrace{(g_{m2} R_S)}_{\text{CA}} \times \omega_{p2, \text{Miller}}$$

$\Rightarrow \omega_{p2}$ gets pushed away by a large factor

$\times \quad \omega_{p2} \uparrow$ for lower C_c


$$\Rightarrow \text{gain } \uparrow \uparrow = \frac{g_{m1}}{4\pi C_c}$$

$\leftarrow$ Look out for ω_{px}


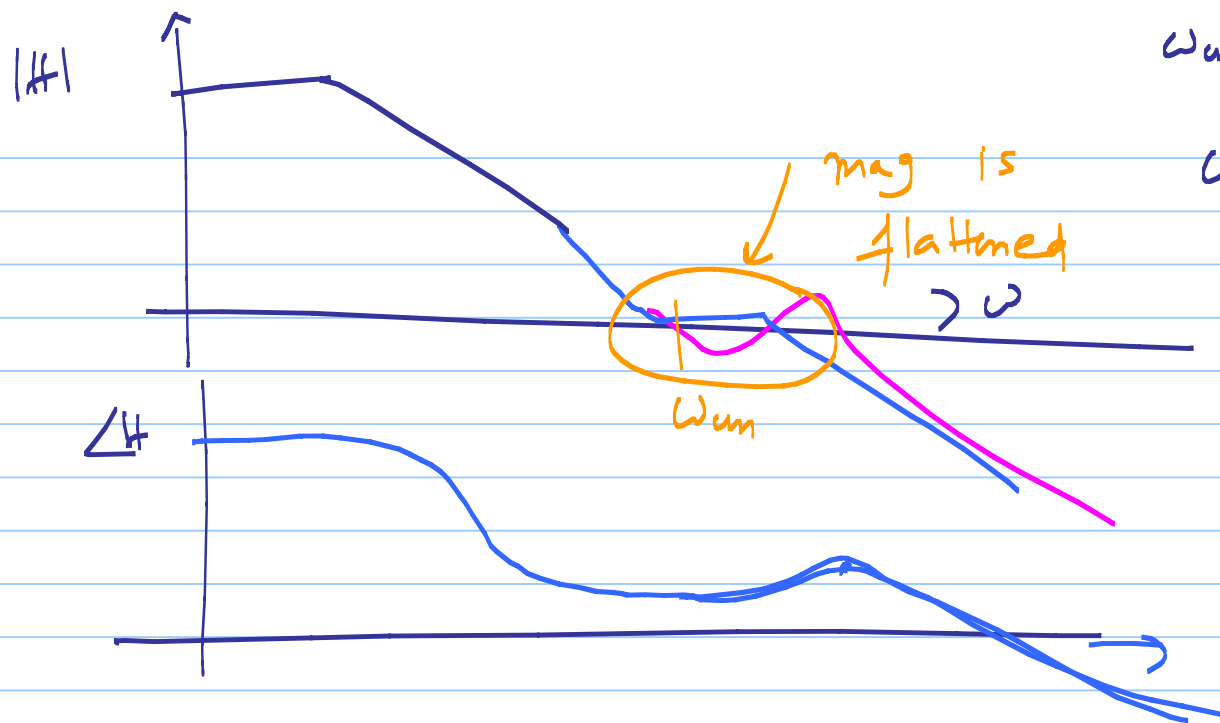


$$\omega_{um} = -\frac{g_{m1}}{C_c}$$
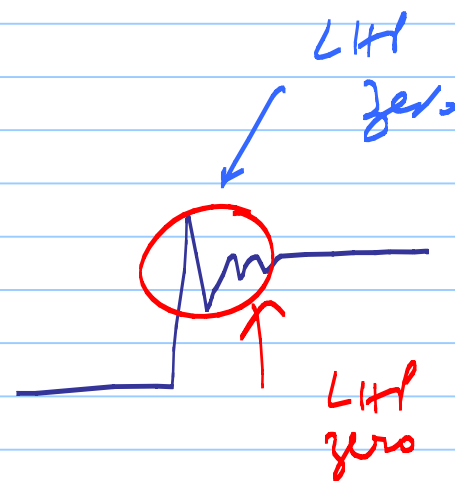
$$\omega_z = -\frac{g_{m, \text{EB}}}{C_c}$$



Cascode Compensation

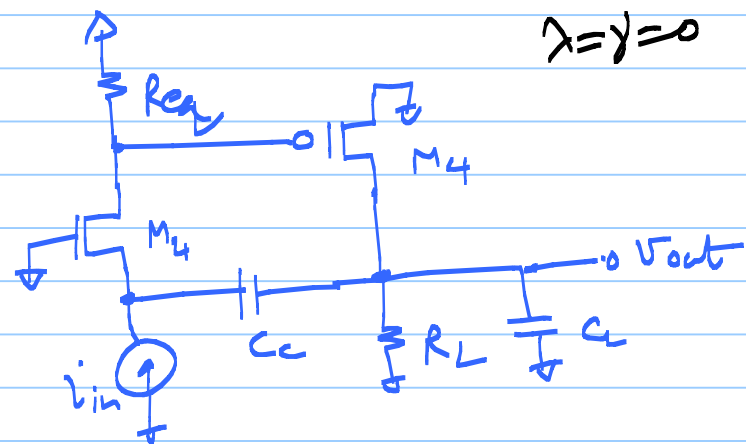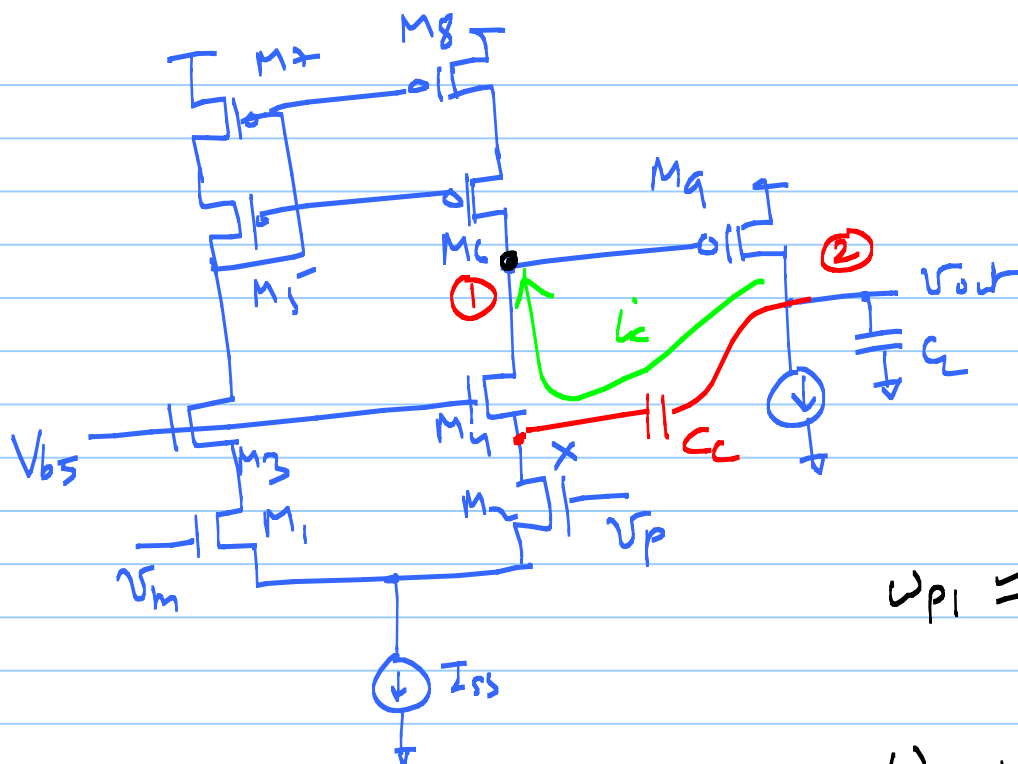

$$\omega_{p1} = \frac{1}{R_{eq} g_m R_L C_L}$$

$$\omega_p \approx (g_{m2} R_{eq}) \frac{g_{mq}}{C_L}$$

$$\omega_3 = - (g_{m4} R_{eq}) \frac{g_{m1}}{C_c} \gg \frac{g_{m4}}{C_c}$$

→ nano-CMOS

① $V_{DD} \downarrow$

$V_{THN,P} \leftrightarrow$

$\Rightarrow$ headroom is shrinking



(-)

② $\sigma_{\Delta V_{THN}} \propto \frac{1}{\sqrt{WL}} \rightarrow \text{offsets}$

③ $g_m r_o \downarrow$


(+) $f_T \uparrow \uparrow$

(+) $(CL) \downarrow \downarrow$

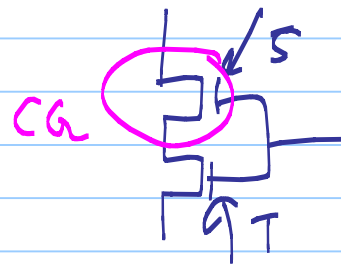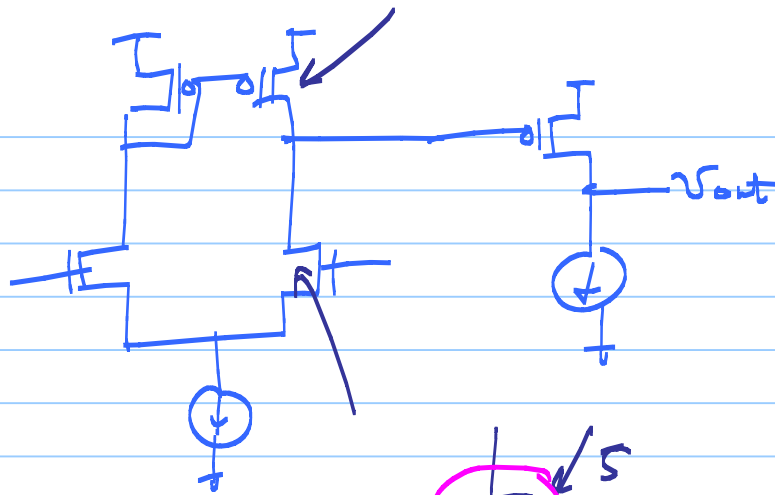

Split-Length Compensation

Low- V_{DD}

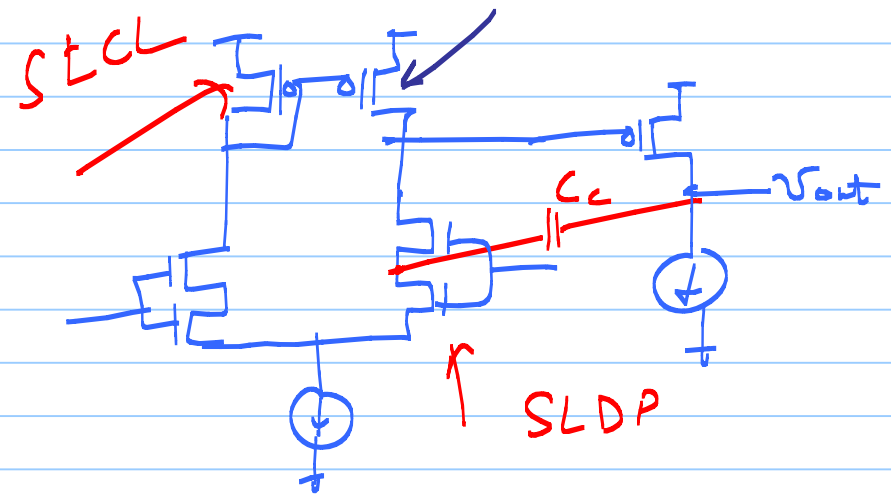


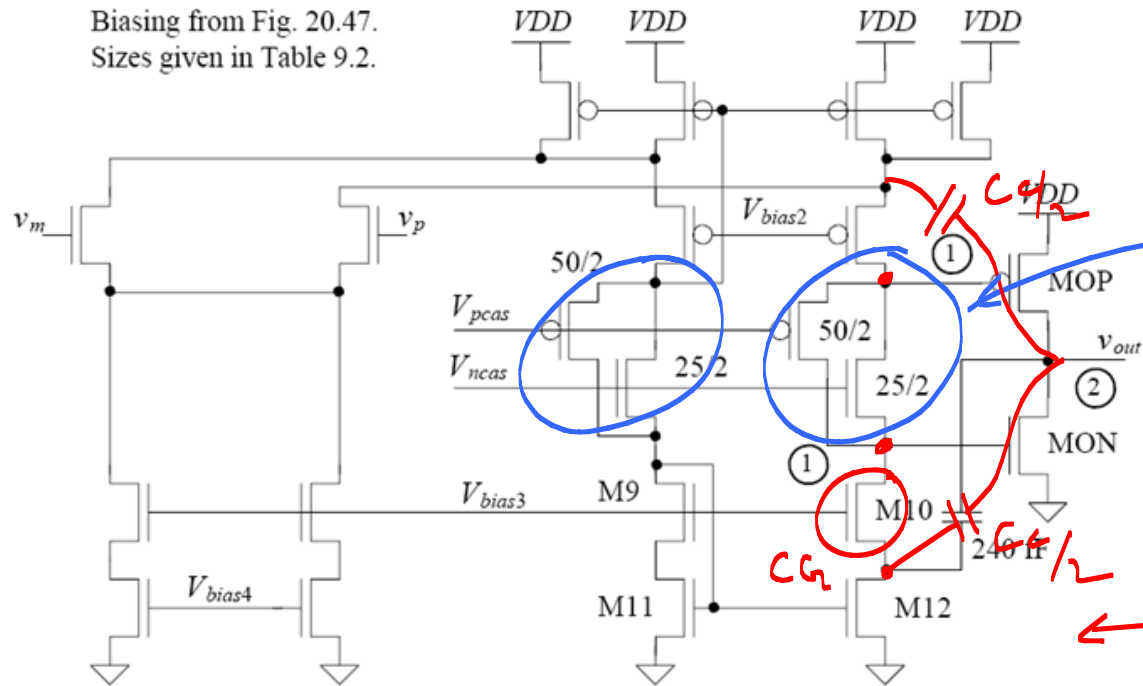


Figure 24.44 Folded-cascode op-amp with class AB output buffer.

Floating CM
 is embedded
 into FC
 structure

indirect
 (cascode)

compensated.

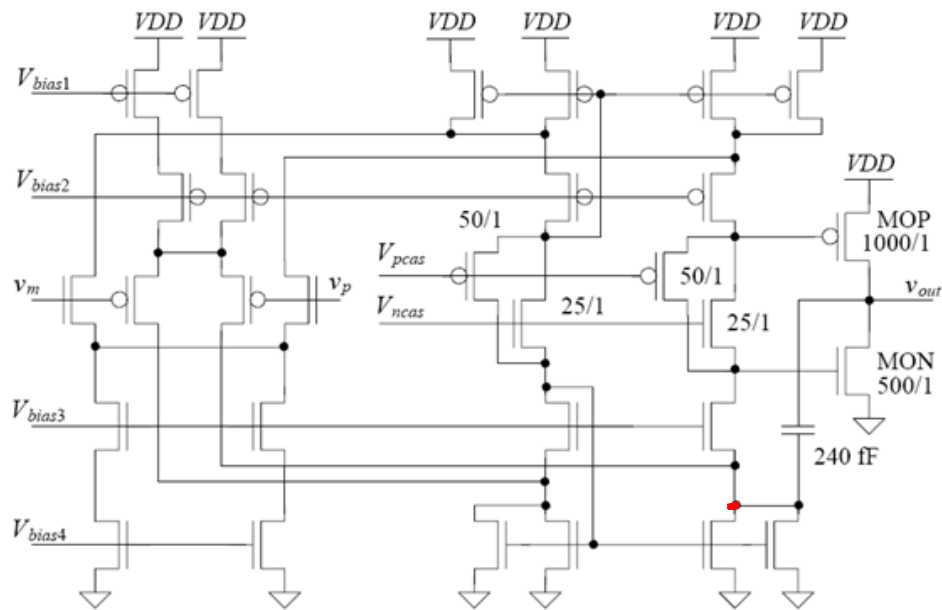



Biasing from Fig. 20.47.
Unlabeled NMOS are 50/1.
Unlabeled PMOS are 100/1.

Figure 24.48 An op-amp with an input common-mode range that extends beyond the power supply rails and that can drive heavy loads.

Rail-to-Rail
operation



Gain Boosting / Enhancement

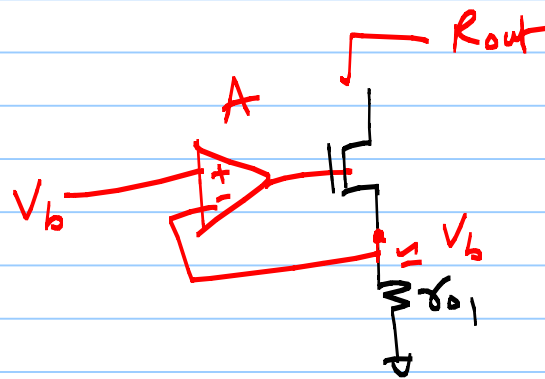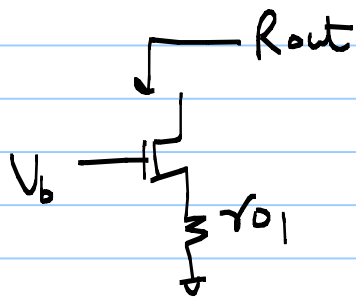

$$\approx A g_{m2} r_{o2} r_{o1}$$

Razavi Sec 9.8

Biasing using Fig. 20.47.
 Unlabeled NMOS are 50/1.
 Unlabeled PMOS are 100/1.



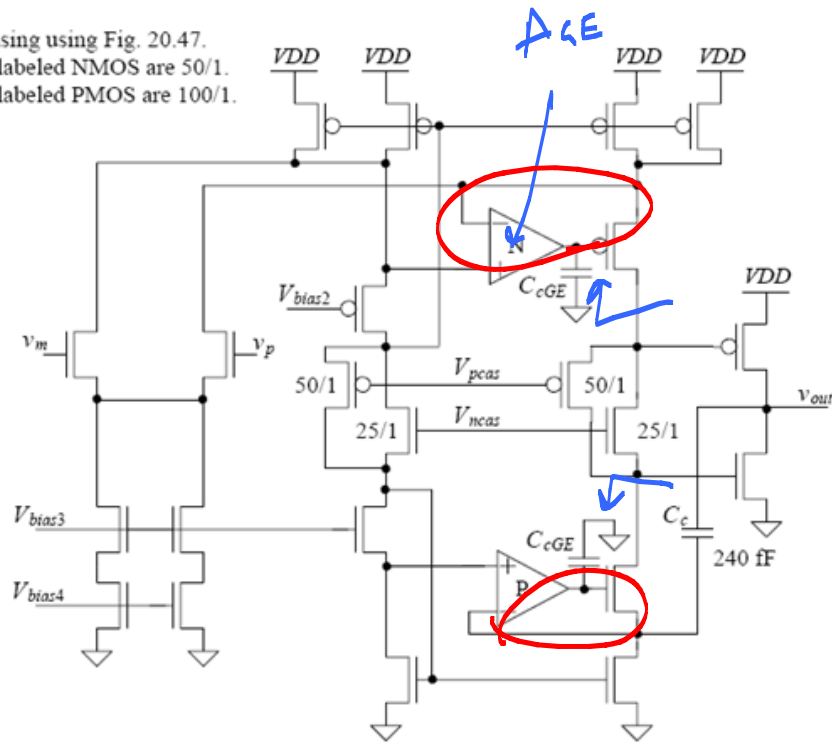


Figure 24.51 Folded-cascode op-amp with class AB output buffer and gain-enhancement.

$$A_{OL} = A_{OL1} \cdot A_{GE}$$

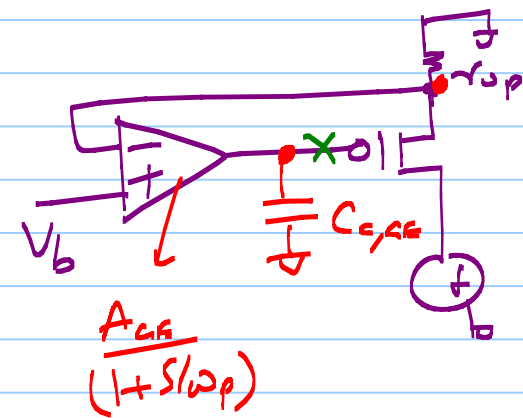

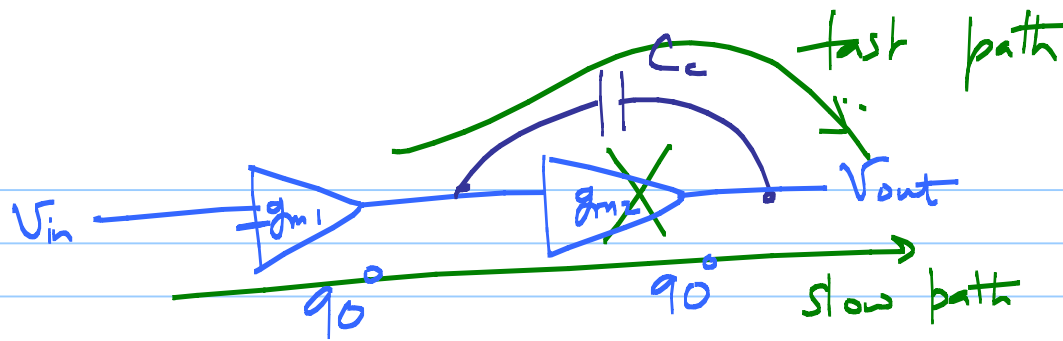


$$A = g_{m1} r_{o1} \cdot g_{m2} r_{o2}$$

@ high frequency

$$SR = \frac{I_{ss}}{C_c}$$



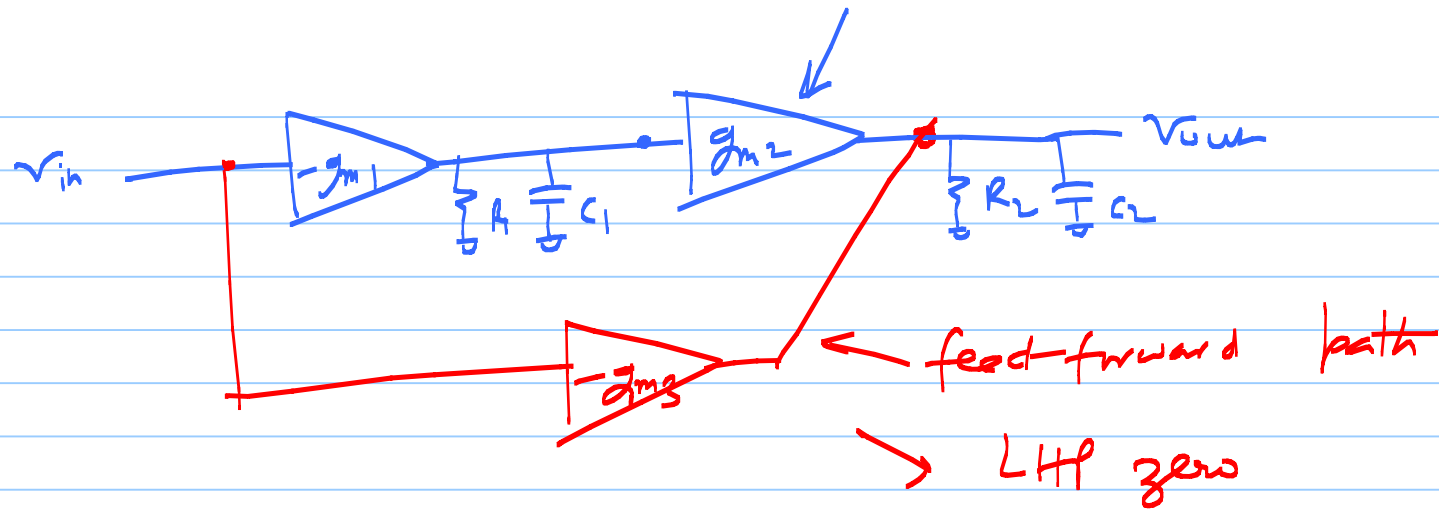

$$\frac{v_o}{v_i}(s) = \frac{-(A_{v1}A_{v2} + A_{v3}) \left[1 + \frac{A_{v3}s}{(A_{v1}A_{v2} + A_{v3})\omega_{p1}} \right]}{(1 + s/\omega_{p1})(1 + s/\omega_{p2})}$$

$\omega_{p2} = \omega_z$

$$A_{v_k} = g_{m_k} R_k$$

$$\omega_z = \omega_{p1} \left[1 + A_{v1} \frac{g_{m2}}{g_{m3}} \right]$$

