

ECE 511 - Lecture 2

Note Title

1/24/2011



SAT

$$V_{DS} > V_{GS} - V_{THN}$$


NMOS ←

$$V_{SD} > V_{SG} - V_{THP}$$

PMOS ←

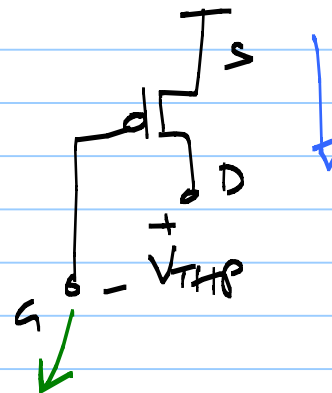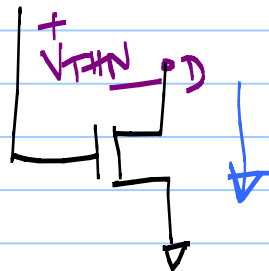

DIODE CONNECTED MOSFET

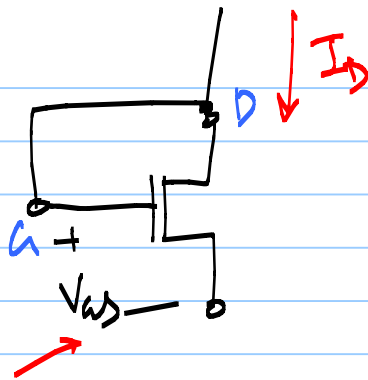


$$I_D = f(V_{gs}, V_{ds}) \leftarrow$$

$$V_{gs} = V_{ds}$$

$$I_D = f(V_{gs}) \leftarrow$$

$$V_{ds} > V_{gs} - V_{THN}$$
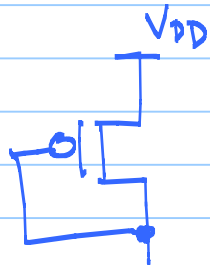
$$V_{gs} > V_{THN} \quad (\text{Always})$$






$$I_D = \frac{\beta_n}{2} (V_{gs} - V_{THN})^2$$

G-D connected
Diode Connected
MOSFET


* Always in
"SATURATION"
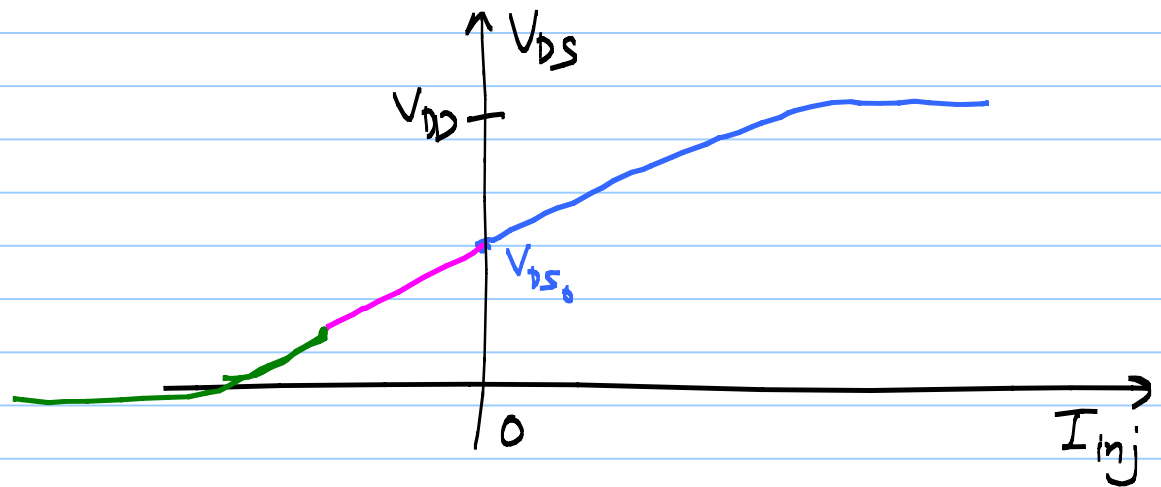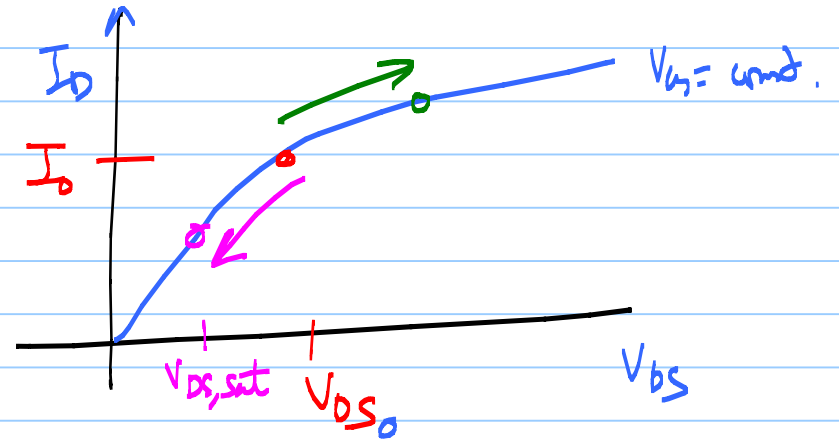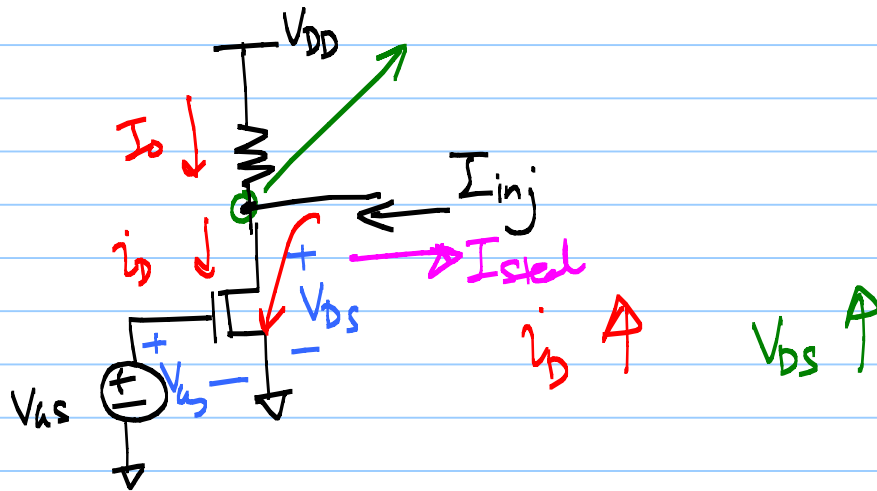
$$V_{OV} = V_{GS} - V_{THN} \triangleq V_{DS, sat} \leftarrow \text{OVERDRIVE}$$




Body Effect :

$$V_{THN}(V_{SB}) = V_{TH0} + \gamma_n \left(\sqrt{2|V_{fp}| + V_{SB}} - \sqrt{2|V_{fp}|} \right)$$

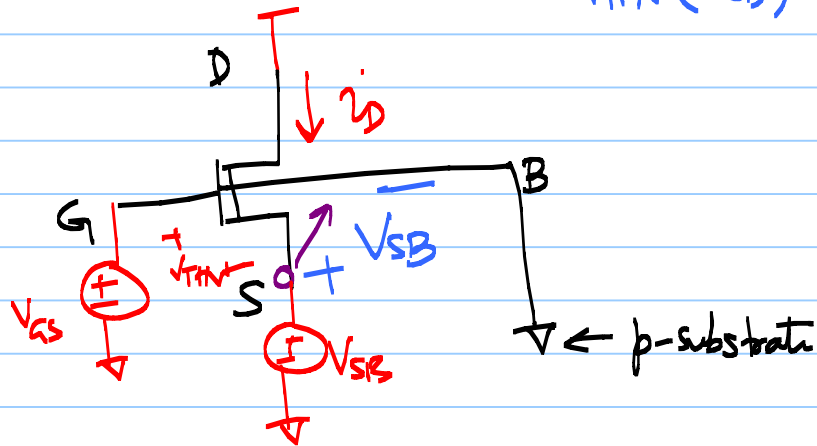

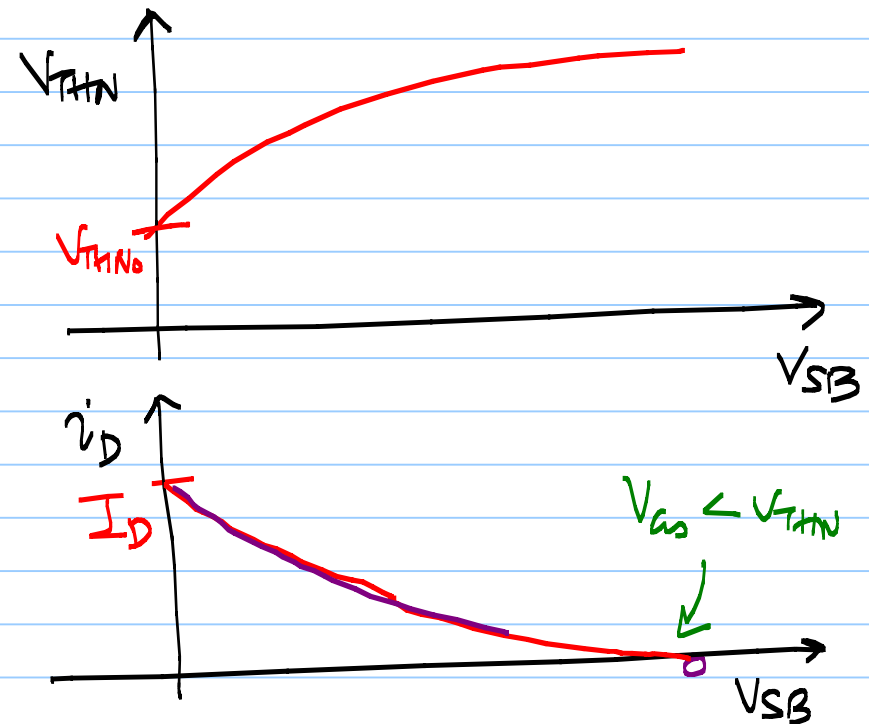$V_{SB} \uparrow \Rightarrow V_{THN} \uparrow$
 $\Rightarrow i_D \downarrow$






Subthreshold Region

$$I_D = I_{D0} \cdot \frac{W}{L} e^{\frac{V_{GS} - V_{THN}}{nV_T}} \leftarrow V_{D1}$$

$$I_D \propto e^{\frac{V_{ov}}{nV_T}}$$


"EKV model"

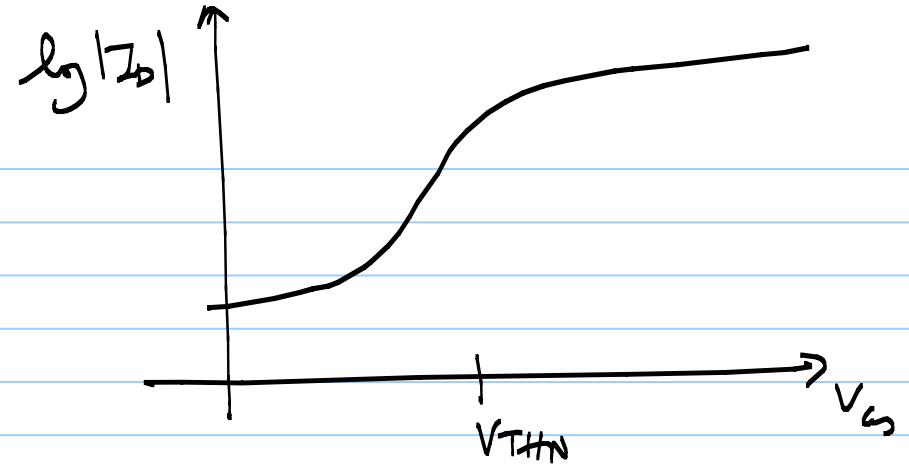

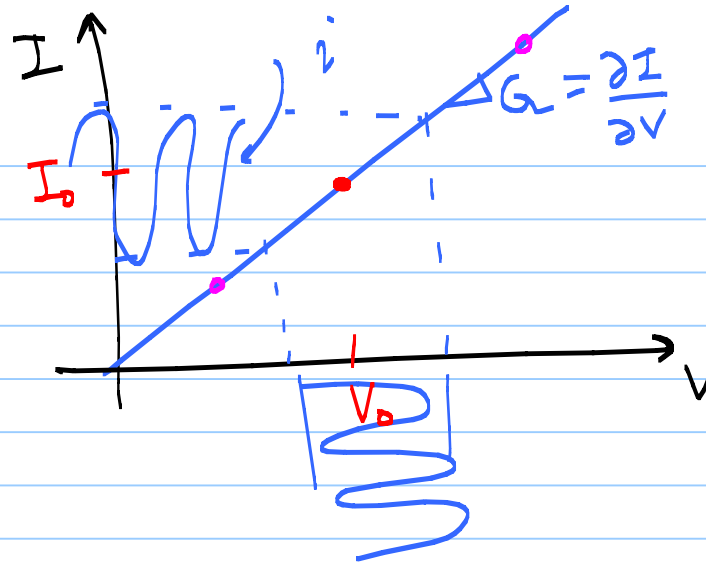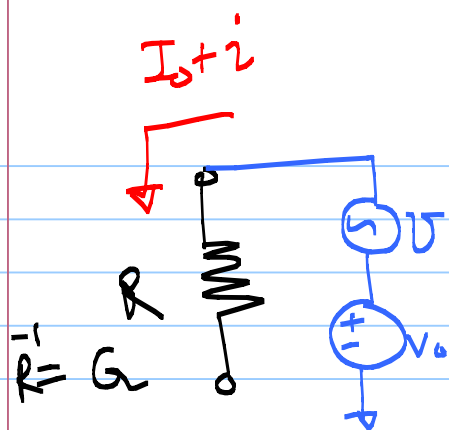

"Bias"

Linear Device

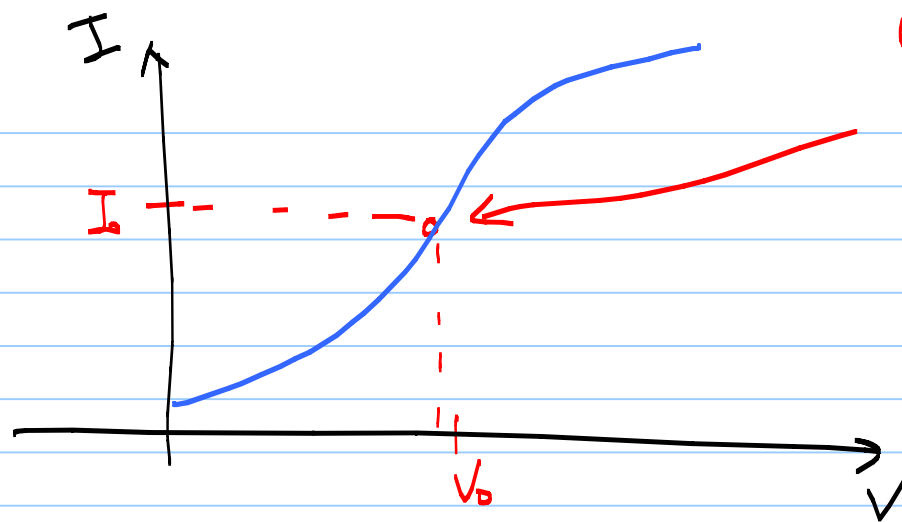

Q-point
Bias point
DC operating point

$$I = f(V)$$

$$I = f(V) \rightarrow \underline{V_0 + v}$$

$$I = f(V_0) + \frac{f'(V_0)}{1} \underbrace{(V - V_0)}_v + \cancel{\frac{f''(V_0)}{2} \underbrace{(V - V_0)^2}_{v^2}} + \cancel{\frac{f'''(V_0)}{6} \underbrace{(V - V_0)^3}_{v^3}} + \dots$$

$(I_0 + i)$

As signal ' v ' is sufficiently small

$v^2, v^3 \leftarrow$ neglect


$$I = \underbrace{f(v_0)}_{I_0} + \underbrace{f'(v_0)}_g v$$

$g \rightarrow$ Small Signal Conductance


$$I - I_0 = g \cdot v$$

$$\boxed{i = g \cdot v}$$


$g = \left. \frac{dI}{dv} \right|_{v=v_0}$ $\rightarrow$ Small signal parameter is found at the Bias point

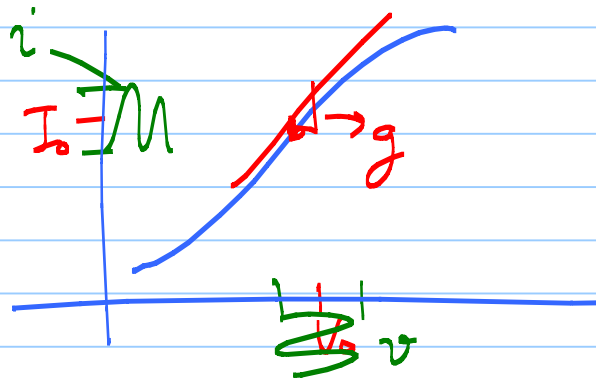

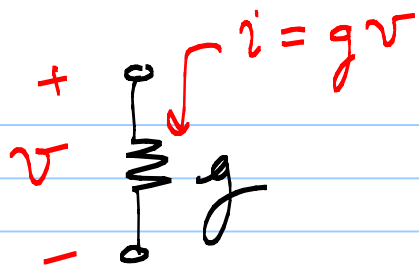$i = g \cdot v \leftarrow$ linearized around Bias point


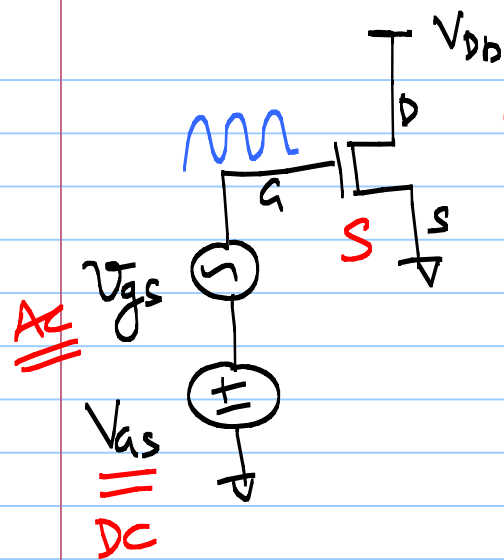
$$\boxed{i = g_1 v} + \underbrace{g_2 v^2 + g_3 v^3 + \dots}_{\text{distortion terms}}$$



$$v_D = I_D + v_d$$


Total DC AC

$$v_{as} = v_{as} + v_{gs}$$

DC AC

$$v_D = I_D + v_d$$

Neglect CLM

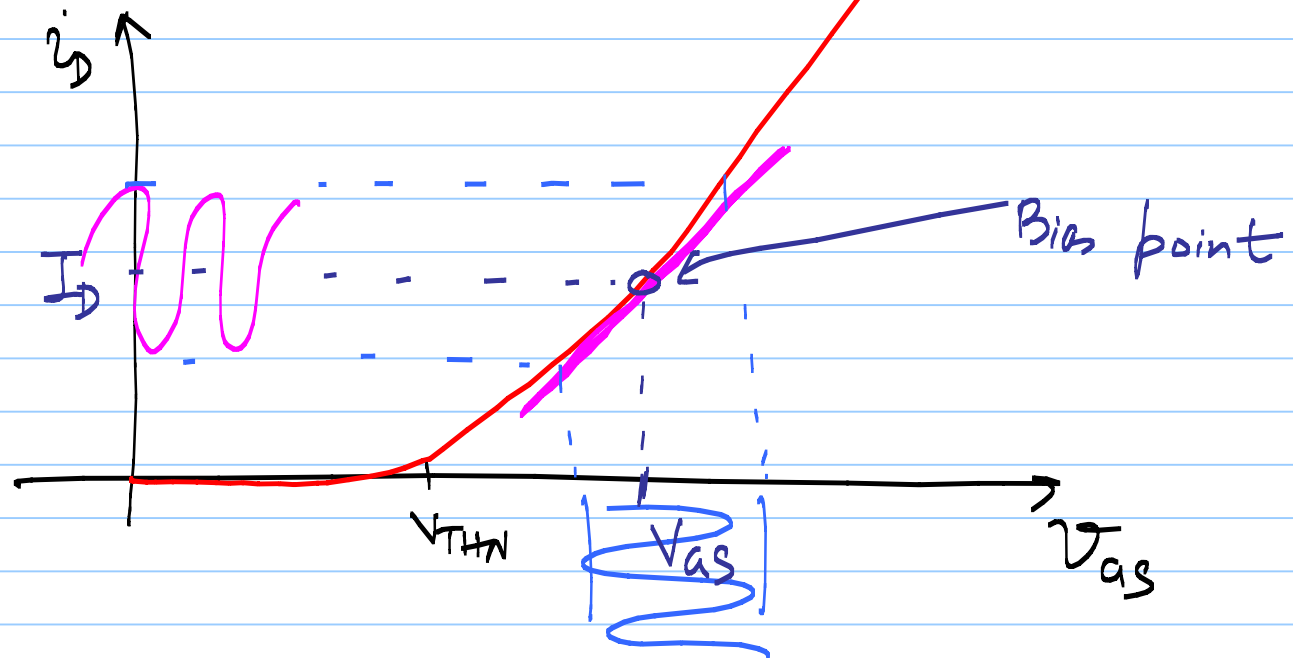

$$i_D = \frac{K_P}{2} \frac{W}{L} (\underline{V_{as}} - V_{THN})^2 \leftarrow$$


$$I_D + \underline{i_d} = \frac{K_P}{2} \frac{W}{L} (V_{as} + \underline{V_{gs}} - V_{THN})^2$$

g_m = transconductance


$$\rightarrow i_d = g_m \cdot V_{gs}$$

$$g_m = \left. \frac{\partial i_D}{\partial V_{as}} \right|_{V_{as}=V_{as}} = \frac{K_P}{2} \frac{W}{L} \cdot 2(V_{as} - V_{THN}) \Big|_{V_{as}=V_{as}}$$
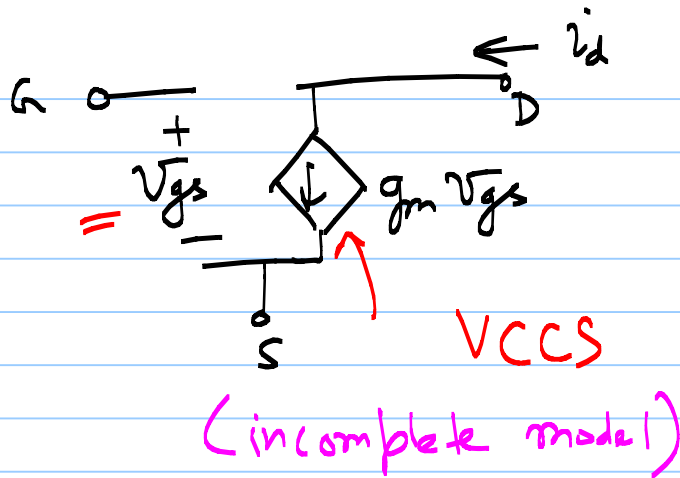
$$g_m = K_P \cdot \frac{W}{L} (\underbrace{V_{as} - V_{THN}}_{V_{ov}})$$



$$i_d = g_m v_{gs}$$

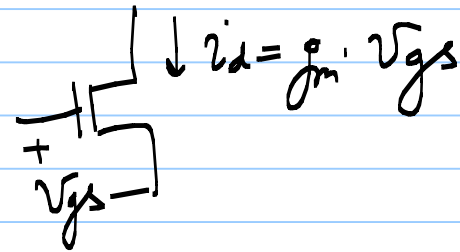

$$g_m = \underbrace{K_n \cdot \frac{W}{L}}_{\beta_n} (V_{GS} - V_{THN})$$

$$g_m = \beta_n (V_{GS} - V_{THN}) \longrightarrow \textcircled{1}$$

$$= \sqrt{2 \beta_n I_D} \longrightarrow \textcircled{2}$$


$$= \frac{2 I_D}{(V_{GS} - V_{THN})} \longrightarrow \textcircled{3}$$

$$I_D = \frac{\beta_n}{2} (V_{GS} - V_{THN})^2$$

$$(V_{GS} - V_{THN}) = \sqrt{\frac{2 I_D}{\beta_n}} \longrightarrow \textcircled{2}$$


$$\beta_n = \frac{2 I_D}{(V_{GS} - V_{THN})^2}$$

$$g_m = \beta_n (V_{GS} - V_{THN})$$

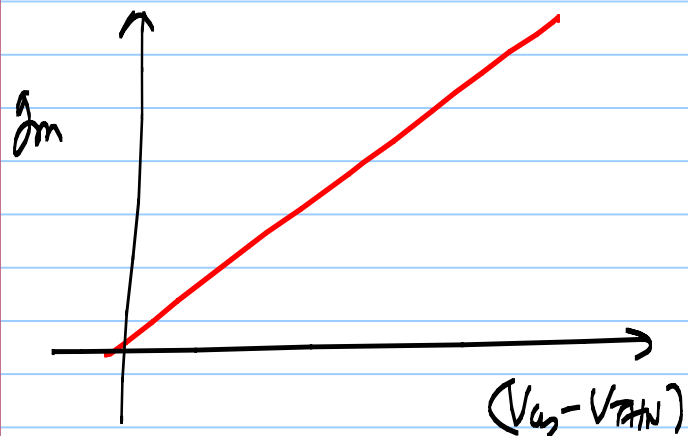


$\frac{W}{L}$ constant

$$g_m = \sqrt{2\beta I_D}$$

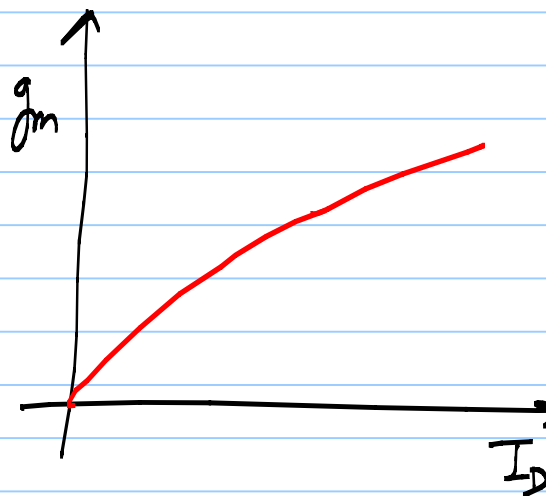



$\frac{W}{L}$ constant

$$g_m = \frac{2I_D}{V_{GS} - V_{THN}}$$

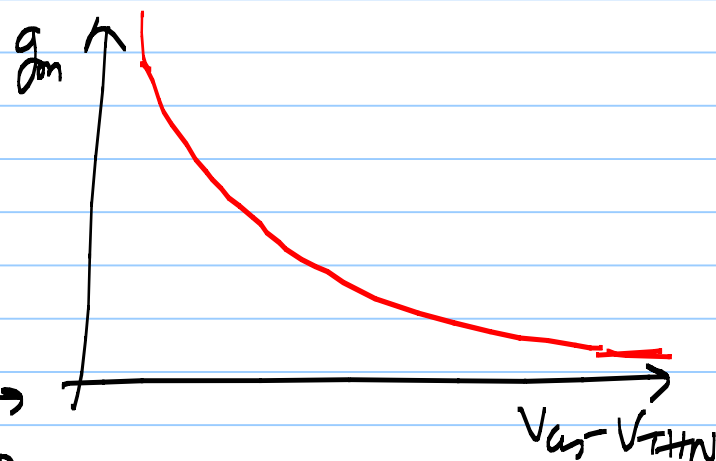

I_D constant

$$xy = c$$

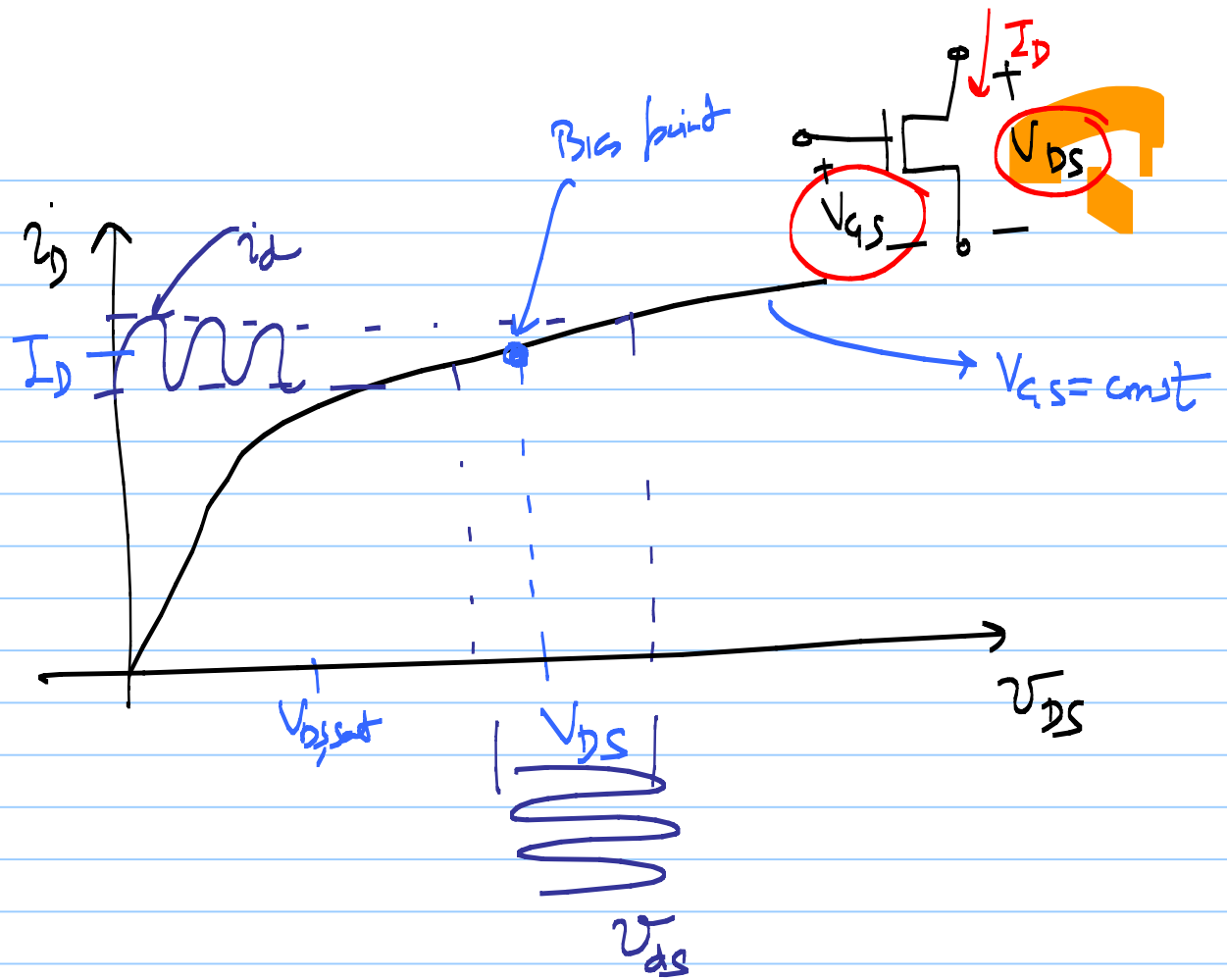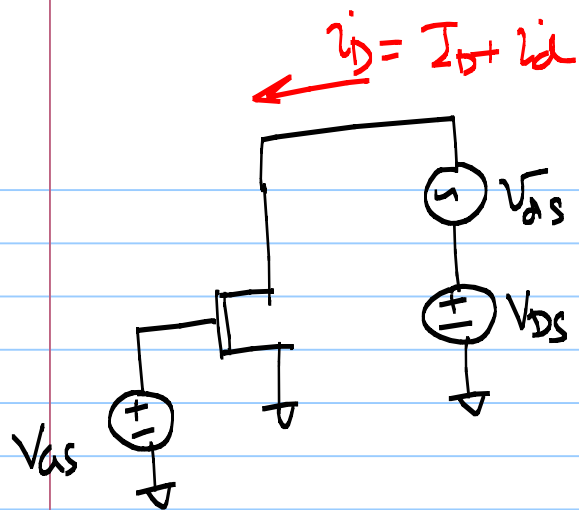

$$\underbrace{i_D}_{I_D + i_d} = \frac{K_p}{2} \frac{W}{L} (V_{GS} - V_{THN})^2 \left[1 + \lambda \underbrace{(V_{DS} - V_{DS,sat})}_{V_{DS} + V_{dS}} \right]$$

$$i_d = g_o \cdot V_{dS} = \frac{V_{dS}}{r_o}$$

Output conductance g_o, g_{DS}

output resistance

$$g_o = r_o^{-1} = \left. \frac{\partial i_D}{\partial V_{DS}} \right|_{\substack{V_{GS} = V_{DS} \\ V_{GS} = \text{const}}} = \lambda \cdot I_{Dsat}$$

$$\boxed{r_o = \frac{1}{\lambda I_{Dsat}}}$$

