
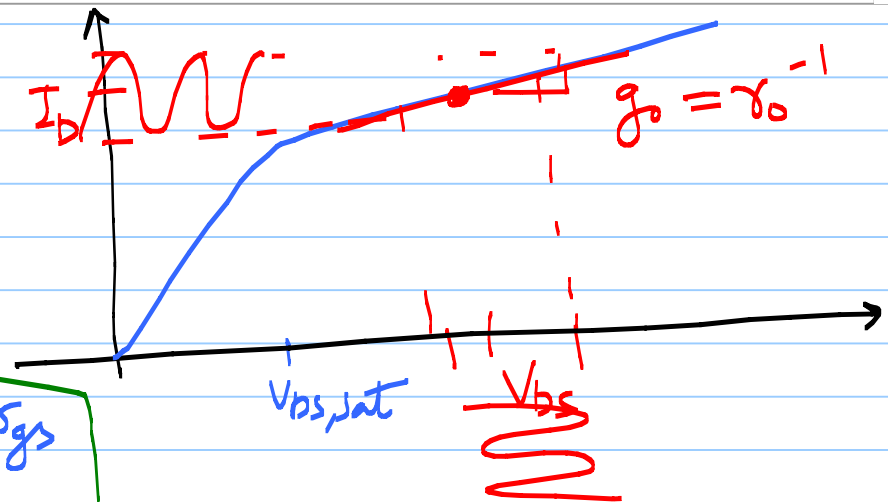
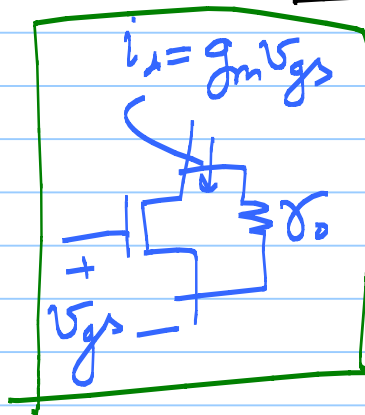




EE 5411 : Lecture 3.

Note Title

1/26/2011

$$r_o = \frac{1}{\lambda I_{D,sat}}$$

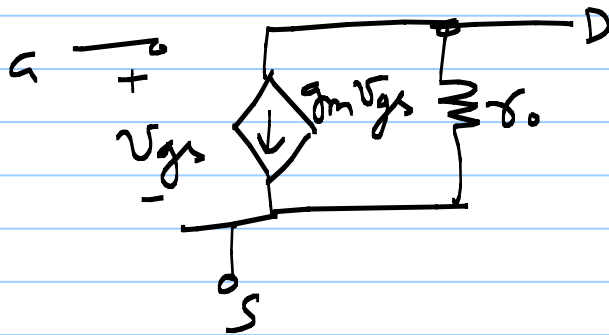

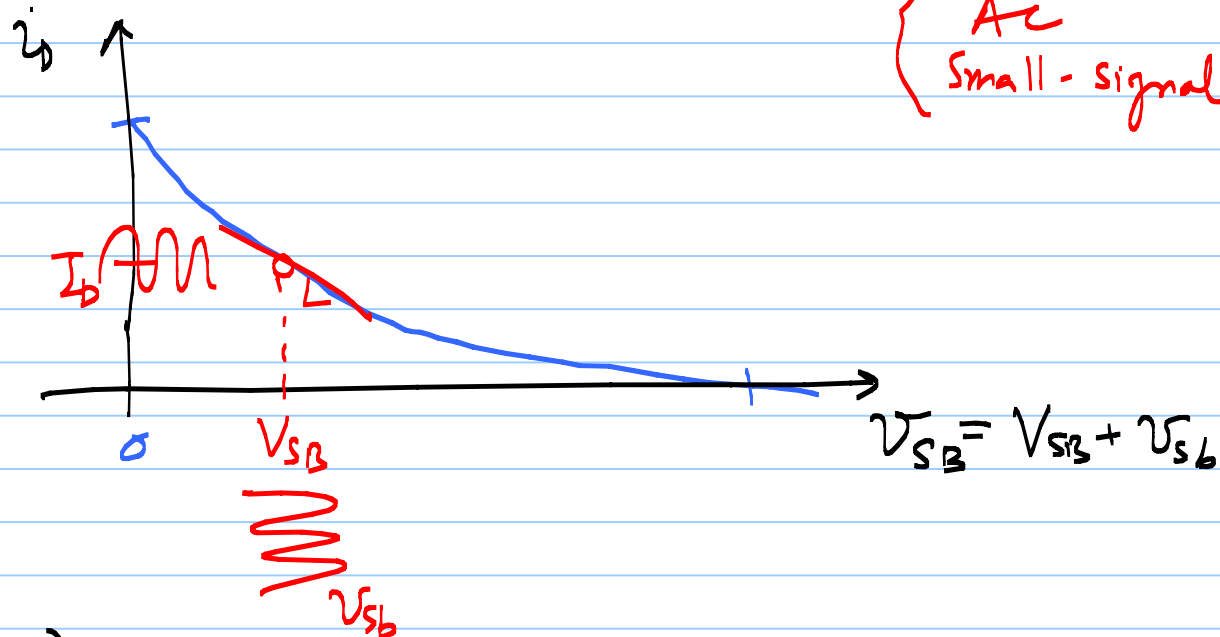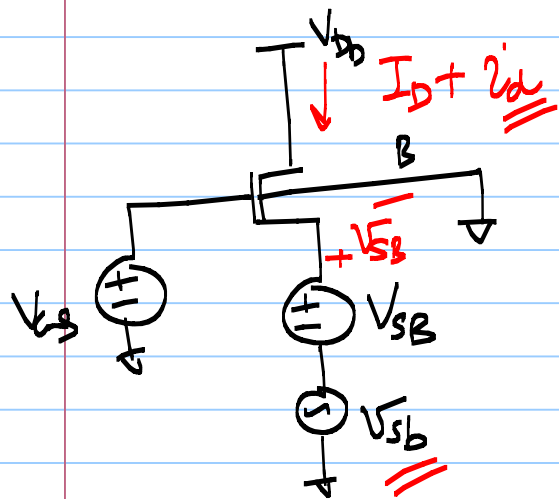

incremental
AC
Small-signal

$$i_D = f(V_{SB})$$

$\downarrow$ $I_D + i_d$ $\downarrow$ $V_{SB} + v_{sb}$ $\left. \begin{matrix} V_{GS} \\ V_{DS} \end{matrix} \right\} \text{const}$

$$V_{SB} = V_{SB} + v_{sb}$$

$$i_d = g_{mb} v_{sb} \rightarrow \text{small-signal parameter } (g_{mb})$$

$$g_m = \left. \frac{\partial i_d}{\partial v_{sb}} \right|_{v_{sb} = V_{SB}}$$

$$= \frac{\partial}{\partial v_{sb}} \left[\frac{K_n}{2} \frac{W}{L} (V_{GS} - V_{THN})^2 \right] \bigg|_{v_{sb} = V_{SB}}$$

$$= \frac{K_n}{2} \cdot \frac{W}{L} \cdot 2(V_{GS} - V_{THN}) \cdot \left(-\frac{\partial V_{THN}}{\partial v_{sb}} \right) \bigg|_{v_{sb} = V_{SB}}$$

$$= g_{m0} \cdot \left(-\frac{\partial V_{THN}}{\partial v_{sb}} \right)$$

$$V_{THN} = f(v_{sb})$$

$$= g_m \cdot \underbrace{\left[-\frac{\partial}{\partial} (|2V_{fp}| + V_{SB})^{-1/2} \right]}_{\eta}$$


$$\eta < 0$$

$$|\eta| < 1$$

$$\boxed{g_{mb} = \underline{\underline{|\eta|}} g_m}$$

$$\underline{\underline{\eta}} = -\frac{\gamma}{2} \frac{1}{\sqrt{|2V_{fp}| + \underline{\underline{V_{SB}}}}}$$

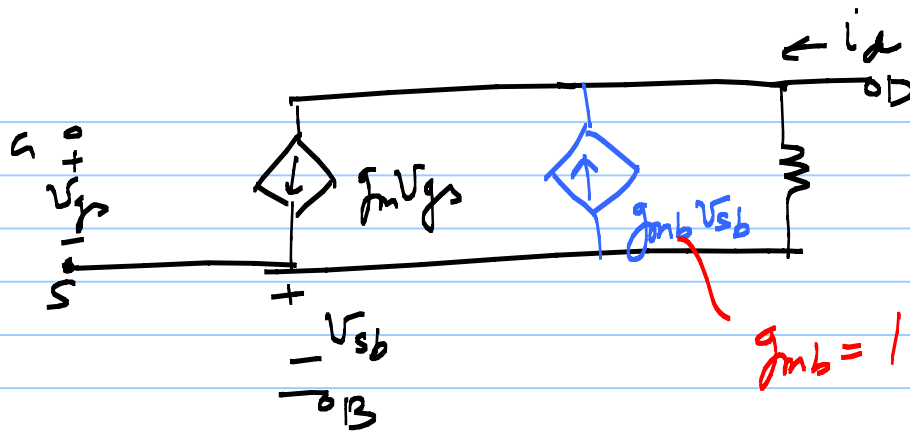* -ve sign in $\eta \Rightarrow$ indicates that g_{mb} is opposing ' $\underline{\underline{g_m}}$ '



Small signal model
for small frequencies

$$g_{mb} = | \eta | g_m$$


Small-signal parameters

* g_m

* r_o, g_{ds}

* g_{mb}

Diode connected MOSFET

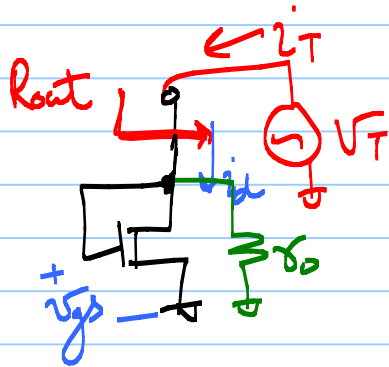


$$\frac{1}{g_m} \parallel r_o \approx \frac{1}{g_m}$$



* Apply a AC test voltage
* find the AC current

$$\frac{v_T}{i_T} = R_{out}$$

$$R_{out} = \frac{v_T}{i_T} = ?$$
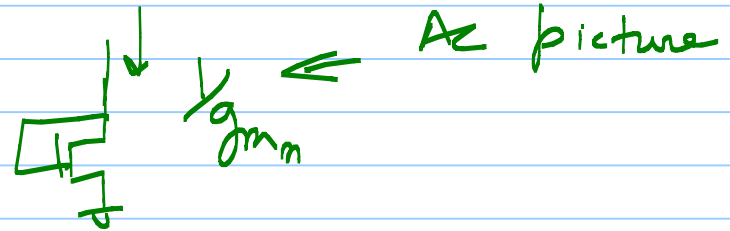
$$= \frac{v_{gs}}{i_d} = \frac{v_{gs}}{g_m v_{gs}} = \frac{1}{g_m}$$



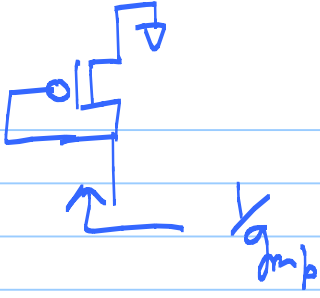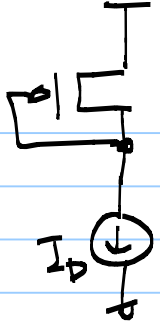

Steps for small-signal analysis

- ① Given a circuit, draw the DC picture
- ↳ Short AC voltage sources
 - ↳ Open AC current sources.

Find Bias points for all the devices

- ② Use the DC operating point from ①,
- ↳ find small-signal parameters ($g_m, r_o, \dots$)
- [linearization around the bias point]


③ Draw the AC picture for the circuit

↳ replace devices by their small-signal models

↳ short DC voltage sources

↳ open DC current sources

Solve for AC values in this circuit.

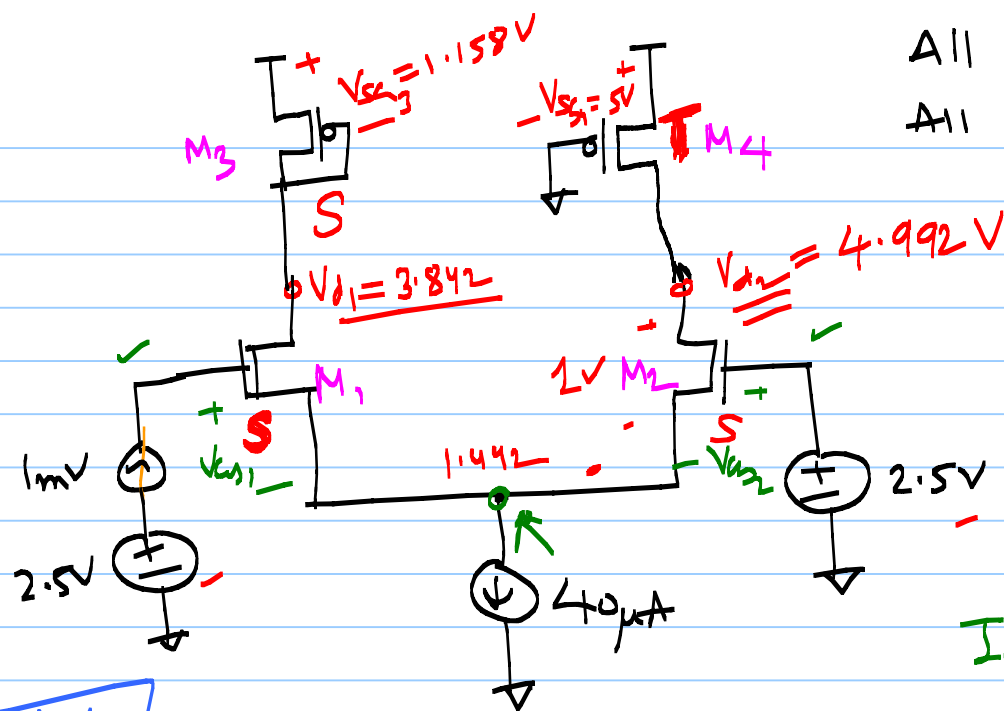

All NMOS are $10/2$
All PMOS are $30/2$

$1\mu\text{m}$ process (Table 6.2)

$$V_{DD} = 5V$$

$$V_{THN} = 0.8$$

$$V_{THP} = 0.9$$

$$K_{Pn} = 120 \frac{\mu A}{V^2}$$

$$K_{Pp} = 40 \frac{\mu A}{V^2}$$

$$I_{D1} = I_{D2} = 20\mu A$$

M_1 & M_2

Solve for $V_{G1} = V_{G2} = \sqrt{\frac{2I_D \cdot L}{K_{Pn} W}} + V_{THN}$

$$= \sqrt{\frac{40}{120} \cdot \frac{2}{10}} + 0.8 = 1.058V$$

$$V_{DS,sat} = V_{DS1} - V_{THN} = 250 \text{ mV}$$

$$V_{S1} = V_{S2} = 2.5 - 1.058 = \boxed{1.442 \text{ V}}$$

M_3 $V_{SG3} = \sqrt{\frac{2 \cdot 20}{40} \cdot \frac{2}{30}} + 0.9 = \boxed{1.158 \text{ V}} \Rightarrow \boxed{V_{SD,sat} = 250 \text{ mV}}$

* M_1 was indeed in Saturation:

M_4 $V_{SG} = 5 \text{ V} \Rightarrow$ most likely M_4 is in Triode

for M_4 to be in Saturation

$$\Rightarrow V_{SD} \geq V_{SG} - V_{THP}$$

$$V_S - V_D \geq V_S - V_G - V_{THP}$$

$$0 = V_G \geq V_D - V_{THP}$$

$$\Rightarrow \underline{V_{D4} \leq 0.9 \text{ V}}$$


Find $V_{D2} = V_{D4}$

$$M_4 \Rightarrow 20\mu = 40\mu \cdot \frac{30}{2} \left[(5 - 0.9)V_{SD} - \frac{V_{SD}^2}{2} \right]$$

$$\Rightarrow \boxed{V_{SD4} = 8.13 \text{ mV}}$$

$$\Rightarrow V_{D4} = V_{D2} = V_{DD} - V_{SD4} = \underline{4.992 \text{ V}}$$


$\times$ M_2 is in Saturation indeed.

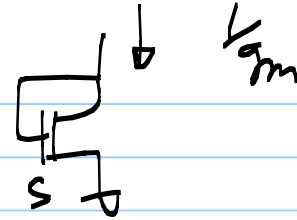

$$R_{ch} = \frac{1}{K P_n \frac{W}{L} (V_{as} - V_{THN})}$$

$$= \frac{1}{g_m}$$

Very Small

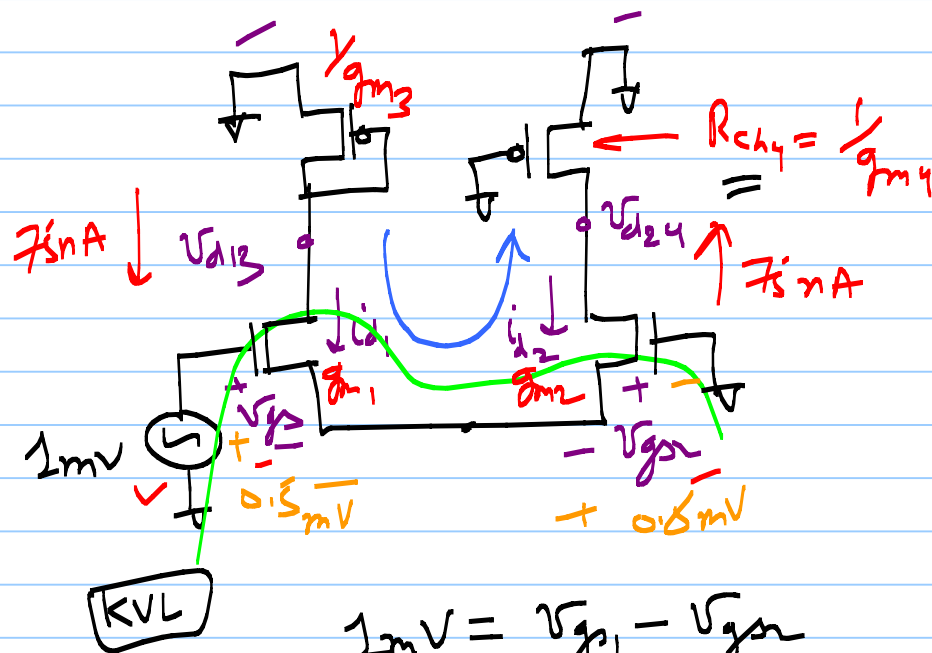

$$1mV = v_{gs1} - v_{gs2}$$

$$M_4 \quad R_{ch4} = 407 \Omega$$

$$M_1, M_2$$

$$g_{m1} = g_{m2} = \sqrt{2\beta_n I_0} = 150 \frac{\mu A}{V}$$

$$M_3 \quad \frac{1}{g_{m3}} = 6.67 k\Omega$$

$$i_{d1} + i_{d2} = 0$$

$$i_{d2} = -i_{d1}$$

$$v_{gs2} = g_{m2} i_{d2} = -g_{m1} i_{d1} = -v_{gs1}$$


$$\boxed{v_{gs2} = -v_{gs1}} = 0.5 \text{ mV}$$

$$i_{d1} = -i_{d2} = g_{m1} v_{gs1} = \boxed{75 \text{ nA}}$$

$$i_{D1} = \overset{\text{DC}}{I_{D1}} + \overset{\text{AC}}{i_{d1}} = [20 + 0.075 \cdot \sin(\omega t)] \mu\text{A}$$

$$i_{D2} = I_{D2} + i_{d2} = [20 - 0.075 \cdot \sin(\omega t)] \mu\text{A}$$

$$i_{D1} + i_{D2} = 40 \mu\text{A}$$

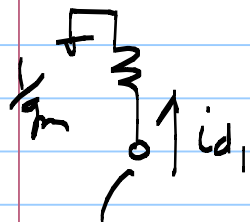

$$v_{d1} = v_{d3} = -i_{d1} \cdot \frac{1}{g_{m3}} = -0.5 \text{ mV}$$

$$v_{d2} = v_{d4} = -i_{d4} \cdot R_{C4} = 0.03 \text{ mV}$$

(neglected all
\$v_{b's}\$)

$$v_{b1,3} = [3.842 - 0.5 \times 10^{-3} \sin(\omega t)] \text{ V}$$

$$v_{b2,4} = [4.792 \text{ V} + 0.03 \times 10^{-3} \sin(\omega t)] \text{ V}$$