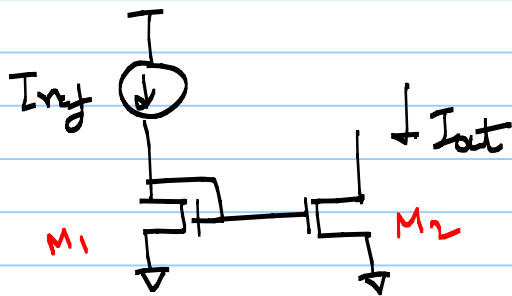


ECE 5411 - Lecture 7

Note Title

2/9/2011



$$\Delta\left(\frac{W}{L}\right), \Delta V_{THN}$$

Fig 20.4

$$y = f(x_1, x_2, \dots)$$

$$\Delta x_1, \Delta x_2$$

$$\Delta y = \frac{\partial f}{\partial x_1} \cdot \Delta x_1 + \frac{\partial f}{\partial x_2} \cdot \Delta x_2 + \dots$$

multivariable
Taylor Series

$$I_D = \frac{K P_n}{2} \left(\frac{W}{L}\right) (V_{GS} - V_{THN})^2$$

$$\Delta\left(\frac{W}{L}\right)$$

$$\Delta V_{THN}$$

$$\Delta I_D = \frac{\partial I_D}{\partial \left(\frac{W}{L}\right)} \Delta\left(\frac{W}{L}\right) + \frac{\partial I_D}{\partial (V_{GS} - V_{THN})} \Delta(V_{GS} - V_{THN})$$

$$= \underbrace{\frac{K P_n}{2} (V_{GS} - V_{THN})^2}_{\Delta\left(\frac{W}{L}\right)} - \underbrace{K P_n \left(\frac{W}{L}\right) (V_{GS} - V_{THN})}_{\Delta V_{THN}}$$

normalize for comparison

$$\delta_{I_D} = \frac{\Delta I_D}{I_D} = \underbrace{\frac{\Delta(W/L)}{W/L}}_{\Delta V_{THN}} - \underbrace{\frac{2 \Delta V_{THN}}{(V_{GS} - V_{THN})}}_{\Delta V_{THN}}$$

∝ To minimize current mismatch
↳ larger overdrive ($V_{GS} - V_{THN}$)

* big problem in sub- V_T designs.

* With CMOS scaling

$$\sigma_{\Delta V_{THN}} \propto \frac{1}{\sqrt{WL}} \quad \leftarrow$$

$\frac{\sigma(W/L)}{(W/L)}$ is larger for smaller devices


↳ could use larger devices *

Effect channel length modulation
($\lambda > 0$)


$$\frac{I_{D2}}{I_{D1}} = \frac{(W/L)_2}{(W/L)_1} \cdot \frac{1 + \lambda (V_{D2} - V_{D1, \text{sat}})}{1 + \lambda (V_{D1} - V_{D1, \text{sat}})}$$

If $V_{D2} \neq V_{D1} = V_{as}$

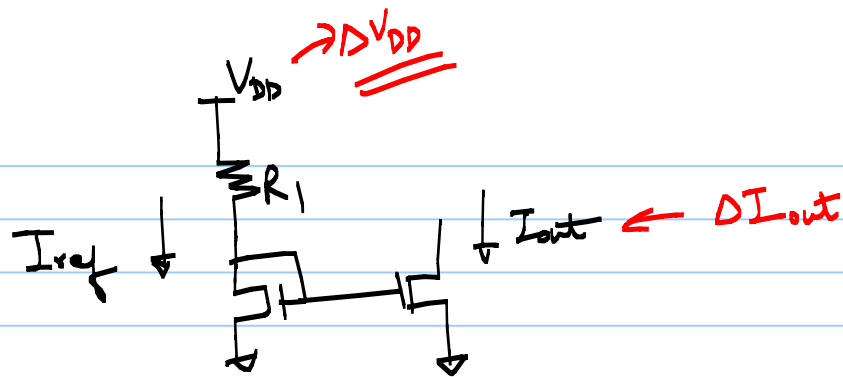↳ current mismatch
↳ dominant source of mismatch




"AC picture"

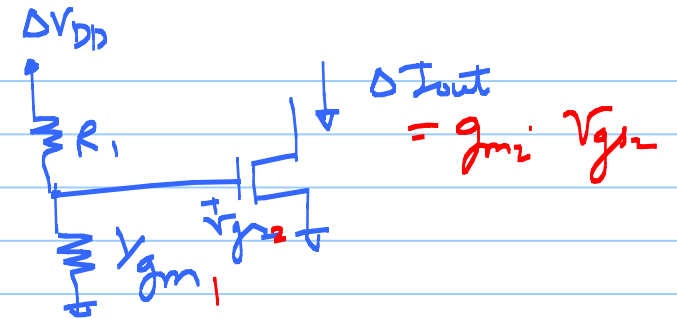

$$\Delta I_{out} = \frac{\Delta V_{DD}}{R_1 + \frac{1}{g_{m1}}} \cdot \left(\frac{g_{m2}}{g_{m1}} \right) = \frac{\Delta V_{DD}}{R_1 + \frac{1}{g_{m1}}} \cdot \frac{(W/L)_2}{(W/L)_1}$$

$$\frac{100 \times 10^{-3}}{10 \times 10^3}$$

$$10 \mu A$$

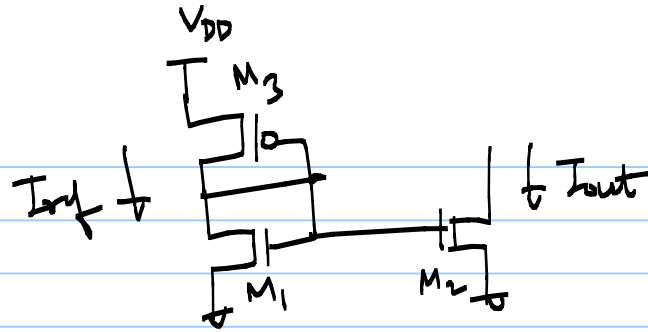

$$V_{DD} = V_{GS1} + V_{SD3}$$


$$V_{DD} = \sqrt{\frac{2I_{ref}}{\beta_n}} + V_{THN} + \sqrt{\frac{2I_{ref}}{\beta_p}} + V_{THP}$$

$$I_{ref} = \frac{(V_{DD} - V_{THN} - V_{THP})^2}{(\sqrt{2/\beta_n} + \sqrt{2/\beta_p})^2}$$

In order to get rid of V_{DD} sensitivity, the circuit must bias itself

$\Rightarrow I_{ref}$ must be derived from I_{out}

($\nabla = 0$)

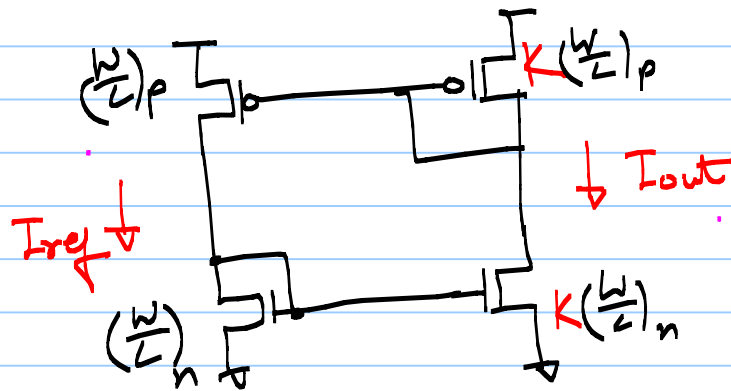

~~$$I_{out} = I_{ref}$$~~


$$I_{out} = k \cdot I_{ref}$$

Since both I_{ref} & I_{out} feed from a current source,
both are independent of V_{DD} .

This circuit can sustain any value of I_{ref} .

* How do we set the values of I_{ref} & I_{out} .

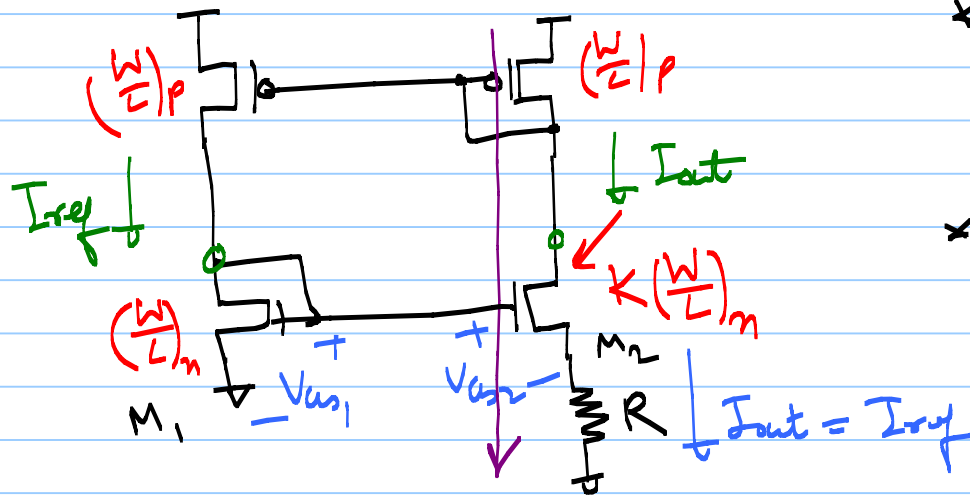$\rightarrow$ add some constant to the circuit.



* Pmos devices force
 $I_{ref} = I_{out}$

* R decreases V_{gs} of M_2
 $\hookrightarrow$ increase width of M_2
 by K-times.

$$V_{gs1} = V_{gs2} + I_{out} \cdot R \quad \leftarrow$$

$$\sqrt{\frac{2I_{out}}{Kp_n \left(\frac{W}{L}\right)_1}} + \cancel{V_{THN1}} = \sqrt{\frac{2I_{out}}{Kp_n \cdot K \left(\frac{W}{L}\right)_1}} + \cancel{V_{THN2}} + I_{out} \cdot R$$

* neglect body effect $\rightarrow$ keep this in mind

$$\sqrt{I_{out}} \cdot \left[\frac{2}{\sqrt{K P_n (W/L)_1}} \left(1 - \frac{1}{\sqrt{K}} \right) \right] = I_{out} \cdot R$$

Solve for $I_{out} = I_{ref} =$ $\begin{cases} 0, \text{ degenerate solution} \\ \frac{2}{K P_n (W/L)_1} \cdot \frac{1}{R^2} \left(1 - \frac{1}{\sqrt{K}} \right)^2 \end{cases}$

* $V_{THN1} \neq V_{THN2}$ leads to some error

* Supply independent biasing


* Beta multiplier reference (BMR)

* not Temperature independent

Let $K=4$

$$I_{ref} = \frac{2}{2K\mu_n(\frac{W}{L})_1} \cdot \frac{1}{R^2} \left(\frac{1}{4} \right)$$

*

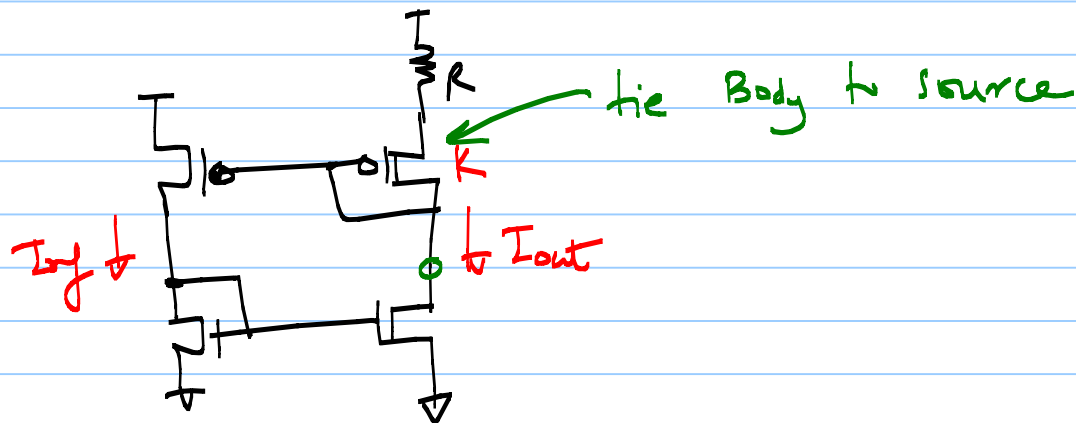

* For $\lambda > 0$

↳ lead to some V_{DS} dependence

↳ use longer 'L' devices

$$\lambda \propto \frac{1}{L}$$

* for lower sensitivity to V_{DD} noise

↳ use a locally regulated V_{DD} for generating
 $I_{ref} = I_{out}$.

See Fig 20.10
Fig 20.16