

MidTerm 2 - Review Session

Note Title

4/9/2011

Chapter 21 → Amplifiers

→ CS, CS - source degeneration
cascode amplifier

CG → current buffer

SF → level shifting

Input impedance

* Miller Effect

* Analyse simple AC equivalent circuit
↳ transfer function

* frequency response of CS amplifiers

↳ pole-splitting

↳ RHP zero

* Dominant pole compensation → ω_{un} , f_{un}




↳ Bode Plots


x Cascade CS amplifier
↳ poles, (Miller approximation).

x Class-A $\leftarrow$ slew limitation

x Class AB $\rightarrow$ output buffer (floating current mirror biasing)
(push-pull amplifier)

$\Rightarrow$ HW6, HW7, HW8

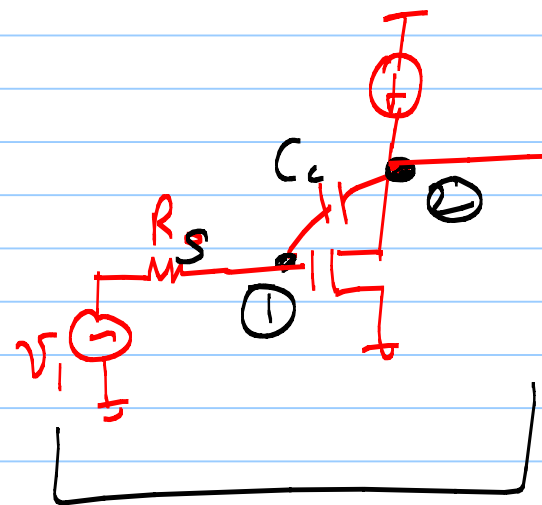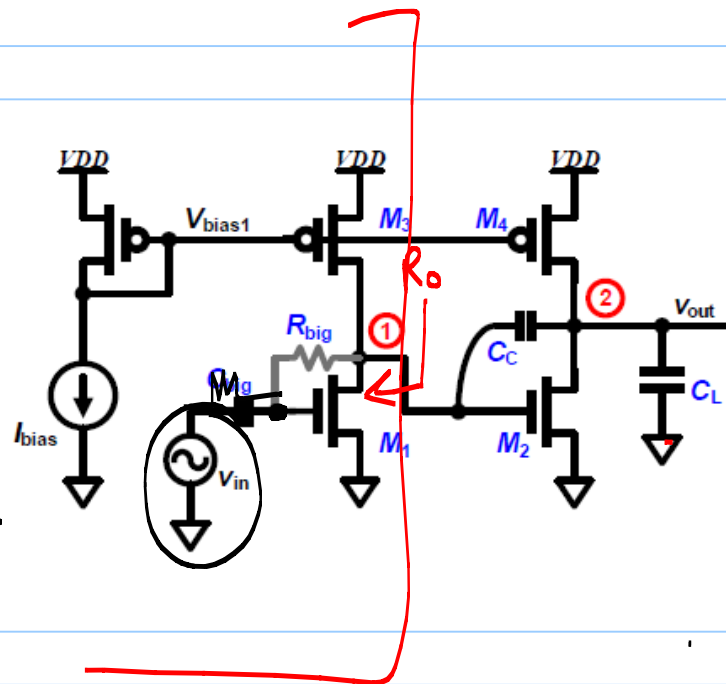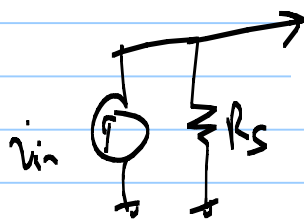

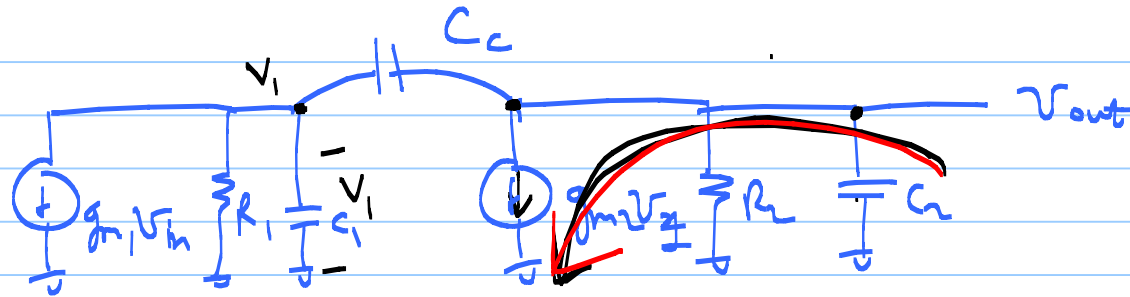

(-)


RHP zero

$$\underline{H(s)} = \frac{(1 - \frac{s}{\omega_z})}{D(s)} = 0$$

$$s = s_z \leftarrow j\omega_z$$

$$\frac{v_{out}}{v_{in}}(s_z) = 0$$

@ $s = s_z$
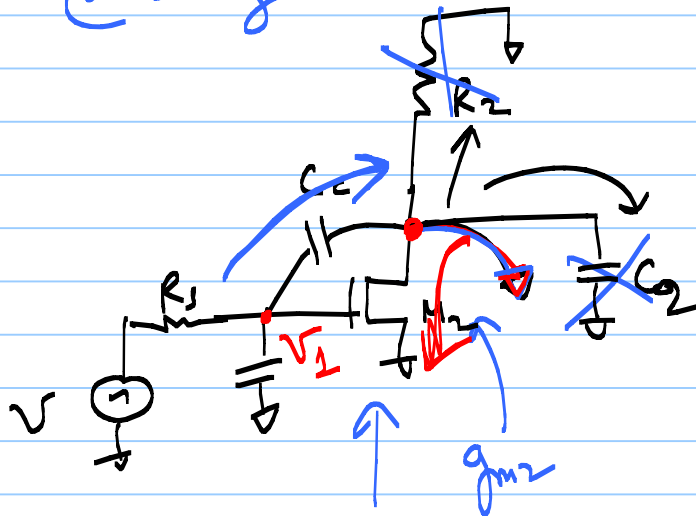
$$S = S_z \leftarrow j^w z$$


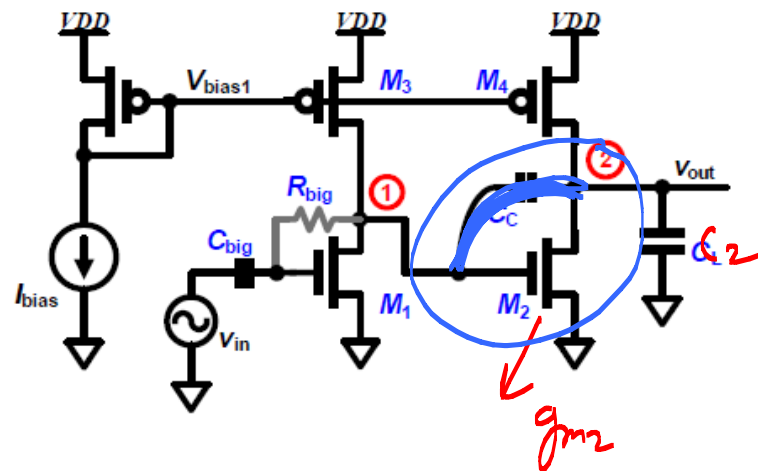
$$\frac{v_1}{1/s_c} \Big|_{s=s_z} = g_2 v_1$$

$$\Rightarrow \cancel{v_1} s_z C_c = g_{m2} \cancel{v_1}$$

→ $s_3 = \frac{g_{m2}}{C_c}$

$j\omega_3$ →

$$|\omega_3| = \left| \frac{g_{m2}}{C_c} \right|$$



$$\omega_{p2} \approx \frac{g_{m2}}{C_2}$$

$$\frac{1}{R \parallel \frac{1}{g_{m2}}} \approx \frac{g_{m2}}{C_2}$$


$$H(s) = \frac{A_{v0}}{(1 + s/\omega_{p1})}$$

$$\approx \frac{A_{v0}}{s/\omega_{p1}}$$

$$= \frac{\omega_{p1} \cdot A_{v0}}{s} = \frac{\omega_{un}}{s}$$

$$s \gg \omega_{p1}$$

$$\omega_{un} = \frac{g_{m1}}{C_c} =$$

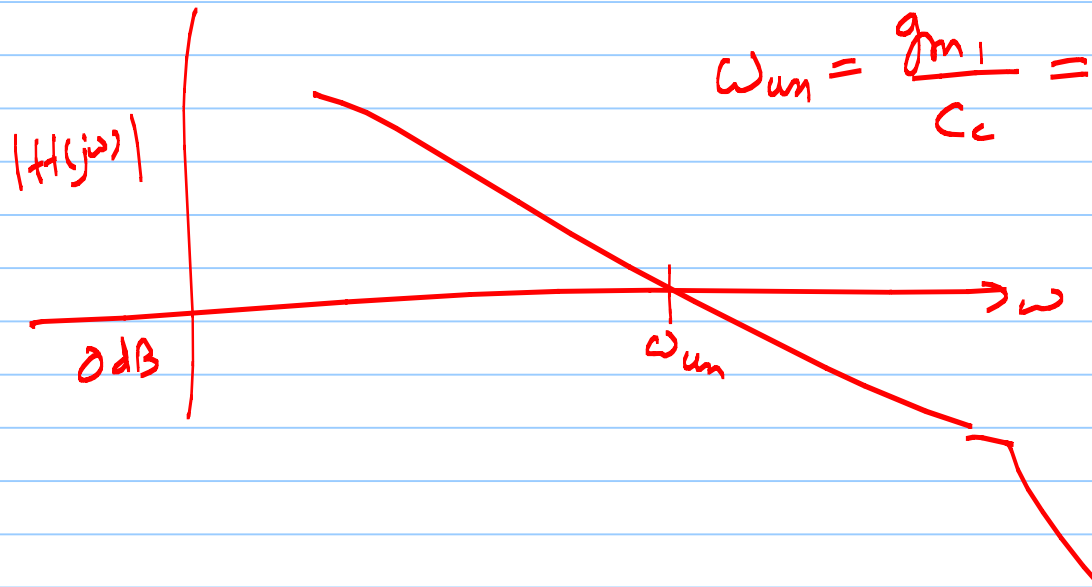

⇒ class A → +ve slow rate limitation

$$\sim \frac{I_{bias}}{C_L}$$

no -ve slow rate limitation

