## Homework 8

## ECE 5411 - CMOS Analog IC Design (Spring 2012)

Due on Monday, Apr 2, 2011.

**Note**: Use Cadence schematic capture, layout and Spectre simulation tools, available on the AMS servers for the homework problems.

- **Problems A1:** Understand examples 21.6-21.10 in the textbook. Do problems A21.19 and A21.20. Simulate them using Spectre. Use the provided MATLAB script (*CommonSourceFreqResp1.m*) to generate frequency and pole-zero plots to augment your understanding.
- **Problems A2:** Do problems A21.21 and A21.23. Simulate them using Spectre. Use the provided MATLAB script to generate frequency and pole-zero plots.
- **Problems A3:** Using the method used in class, show that the zero location in a common-source amplifier is given by  $\omega_z = \frac{g_{m2}}{C_c}$ . Similarly, derive the expression for the zero location when a zero-nulling resistor  $R_z$  is added in series with  $C_c$ . Modify the MATLAB file *CommonSource-FreqResp1*, to account for  $R_z$  and demonstrate zero-nulling and LHP zero creation with this script.

**Problem B1:** For the amplifier shown in the figure below:



 $V_{THN} = 0.7V$ , and  $KP_n = 200 \frac{\mu A}{V^2}$  $V_{THP} = 0.8V$ , and  $KP_p = 50 \frac{\mu A}{V^2}$ 

 $\gamma = 0$ 

- a) Determine the operating points of all the devices in the circuit. For this part, neglect channel length modulation  $(\lambda = 0)$ .
- b) All transistors in the circuit have finite  $r_o$ , such that for any transistor  $g_m r_o = 100$ . Draw the small signal equivalent circuit of the amplifier, and determine the small signal gain  $(\frac{v_{out}}{v_{in}})$ . Also determine the input and output resistances of the amplifier (Perform lowfrequency analysis only).



**Problem B2:** Repeat problem B1 for the amplifier shown in the figure below.

**Problem B3:** Estimate the poles of each circuit shown in the figure below (symbolic answers). Assume that the current sources are ideal. For part (a) use  $\lambda \neq 0$ , and for part (b) assume  $\lambda = 0$ 

