



Practice Problem Set 1 (Dittamjes)

Note Title


4/14/2011

- ① Do problems A22.1 – A22.4, A22.9 from the additional textbook problem set.

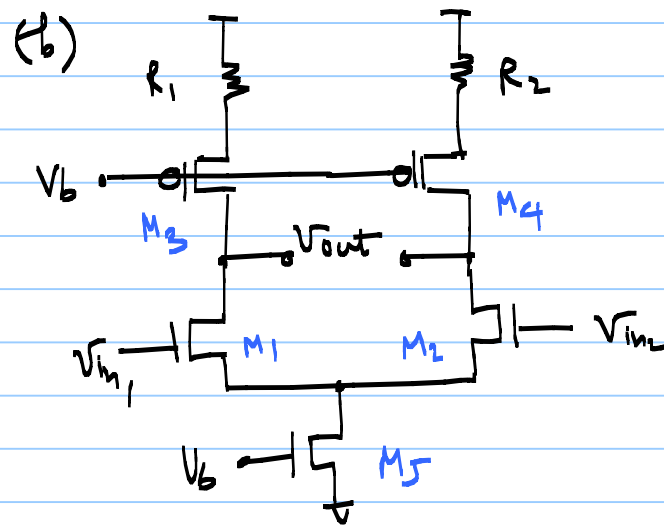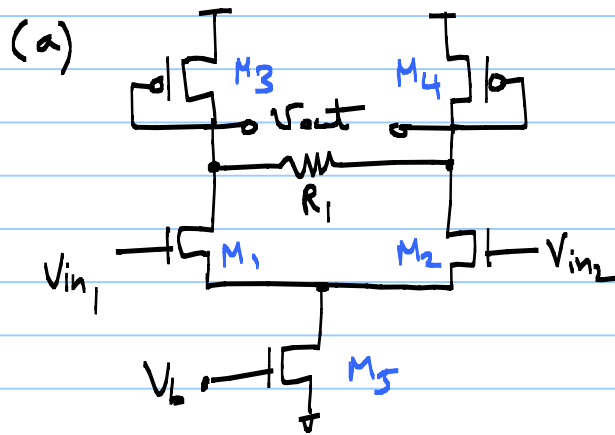
② Assuming all the circuits shown below are symmetric, calculate the small-signal differential voltage gain of each circuit. ($\lambda \neq 0$)




(c)

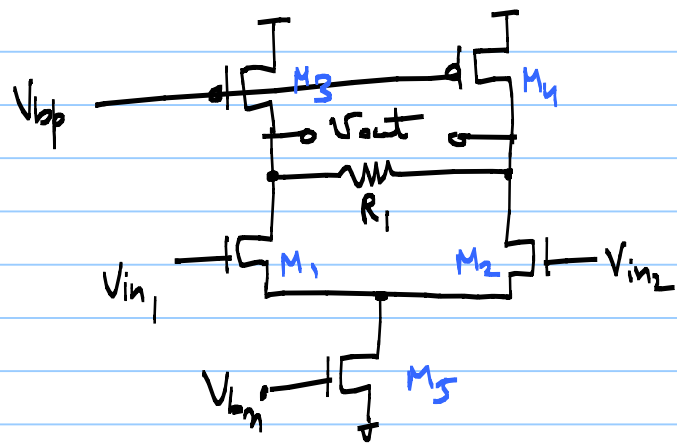


(d)

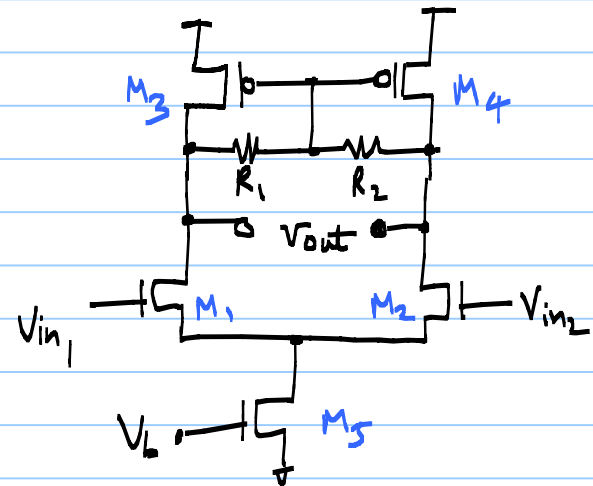

(e)

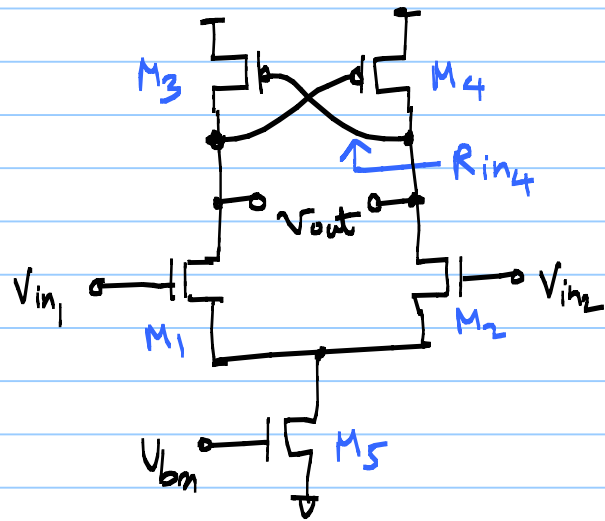


(f)

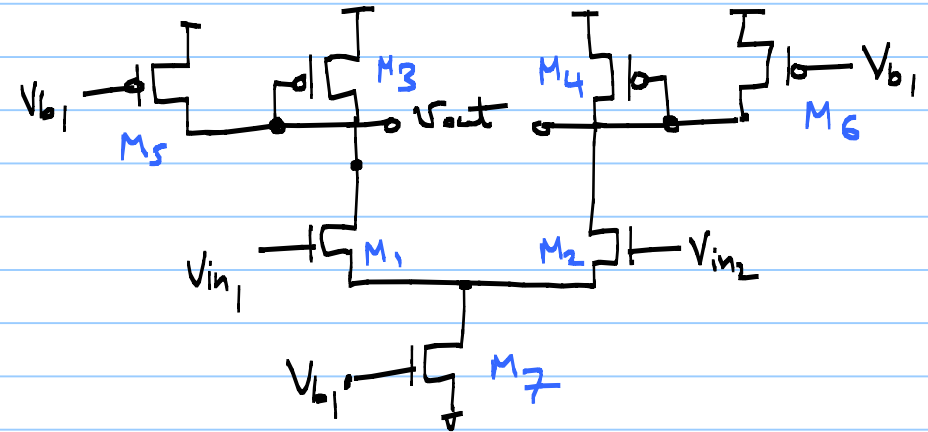


Hint: find the impedance R_{in4} first.

(g)

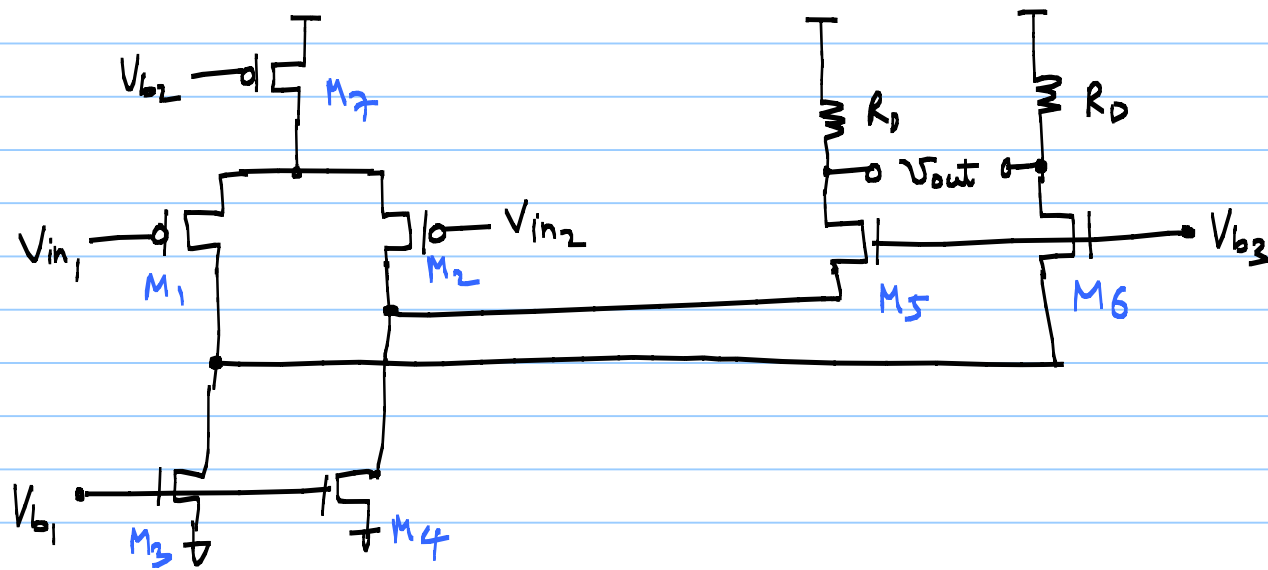


③ Consider the circuit shown below:

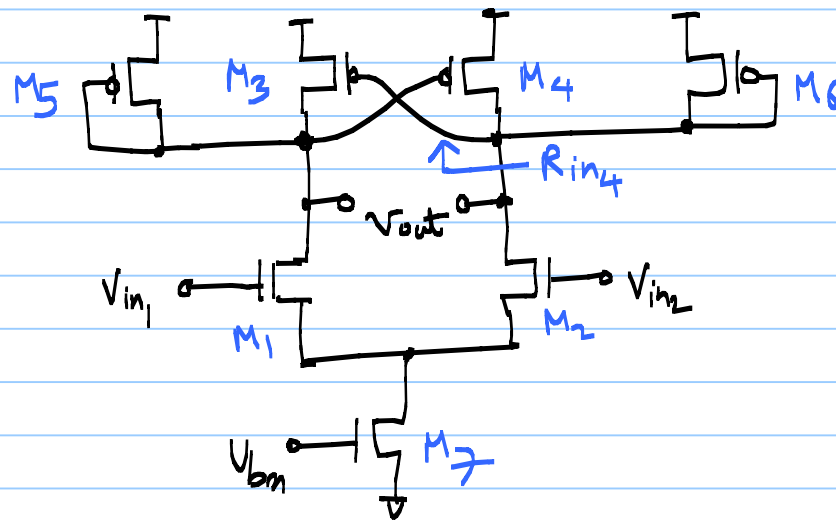- (a) sketch v_{out} as V_{in1} & V_{in2} vary differentially from 0 to V_{DD}
- (b) if $\lambda=0$, obtain an expression for voltage gain. What is the voltage gain when $W_{3,4} = 0.8 W_{5,6}$




④ Calculate gain of the following circuits.



(a)

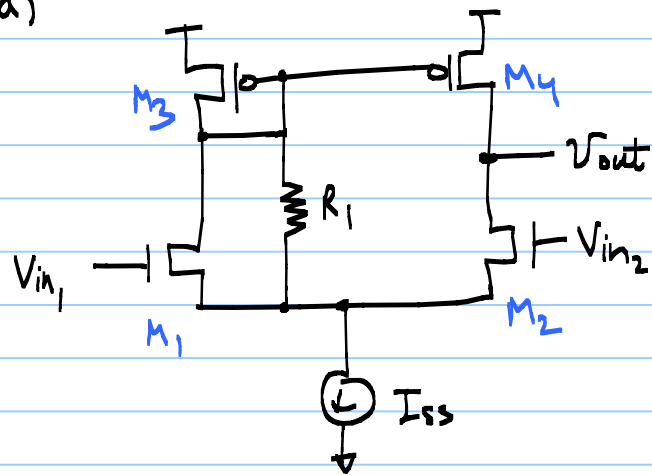


(b)

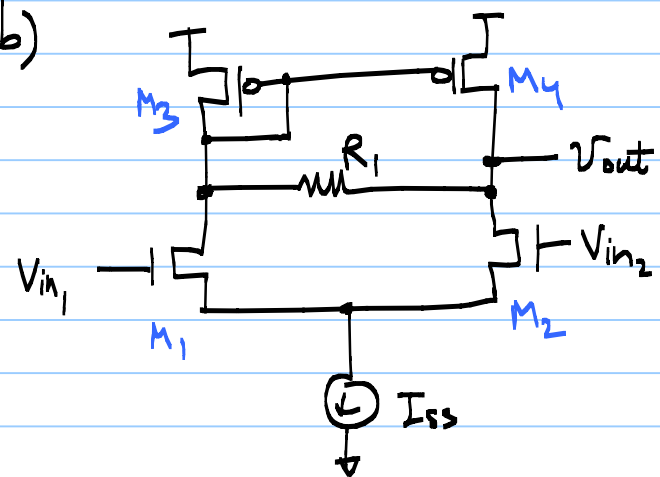

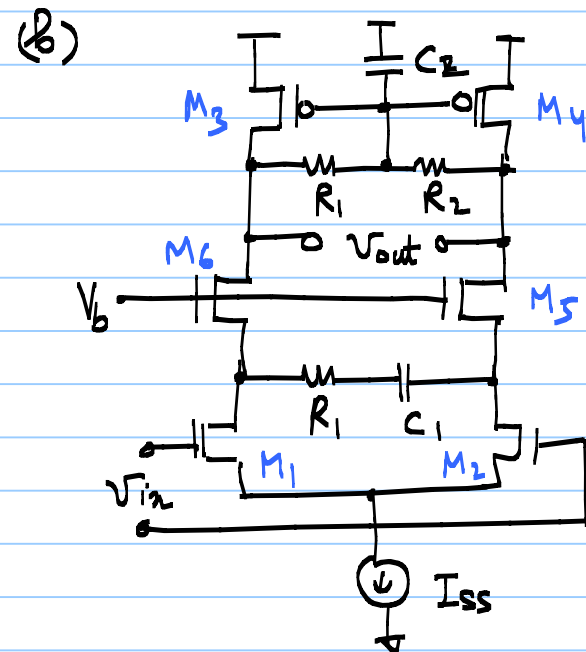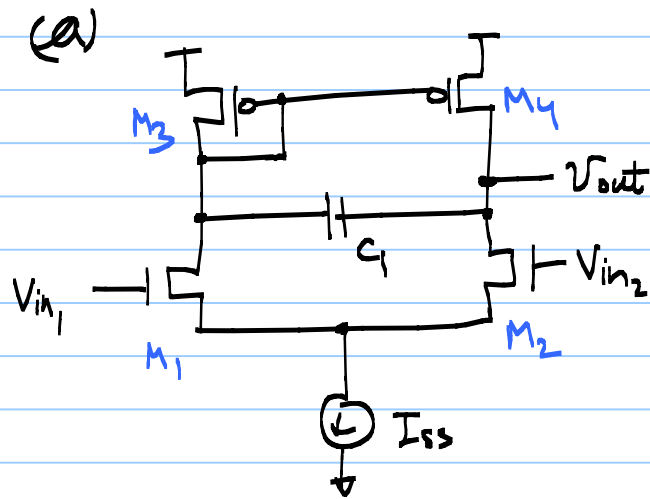- ⑤ Calculate the gain of each circuit at very low and very high frequencies. Neglect all other capacitances and assume $\lambda = \gamma = 0$.



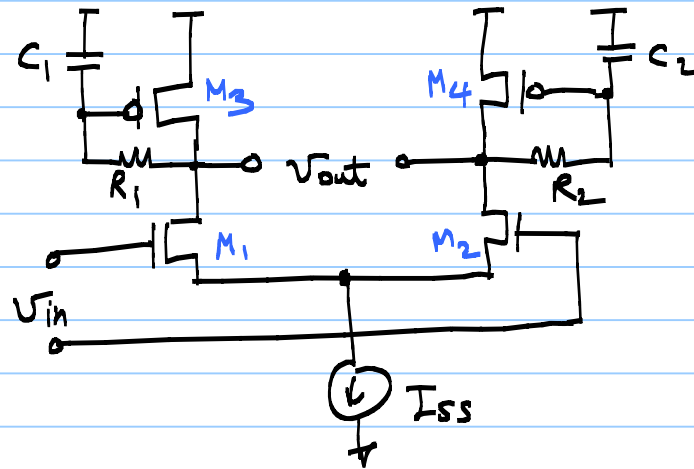- ⑥ For the circuit below, neglecting other capacitances, determine the transfer function. Explain under what conditions the load exhibits an inductive behavior.



Given:

$$K_{lp} = 50 \frac{\mu A}{V^2}$$

Unless specified for a device, assume $\lambda = 0$.

Unless specified for a device, assume $\lambda = 0$.

