
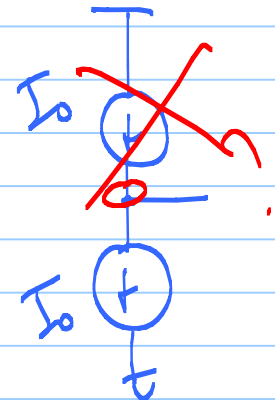
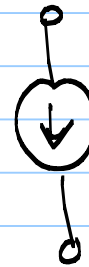


ECE 511 - Lecture 10.

Note Title


2/27/2012

floating current source

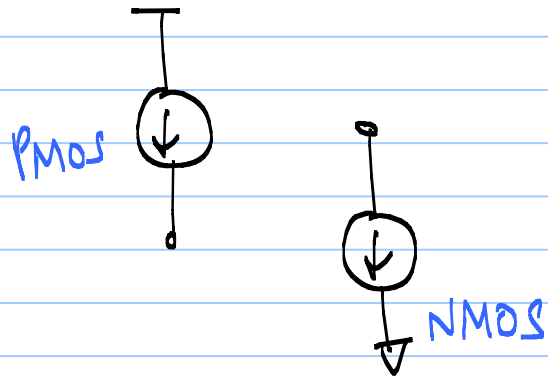


Monticelli Biasing scheme
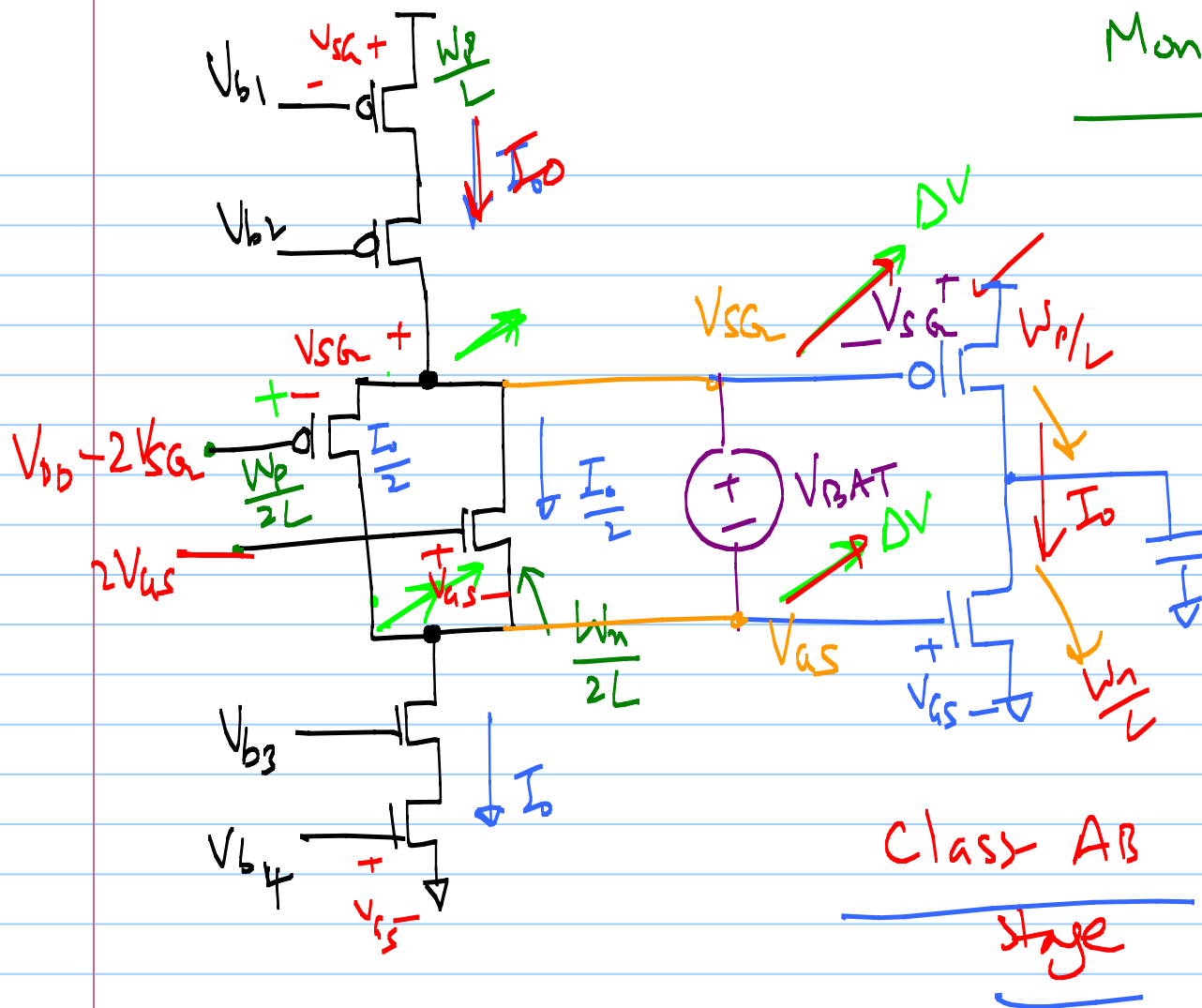
$$V_{BAT} = (V_{DD} - V_{SG}) - (V_{GS})$$



Class AB
stage

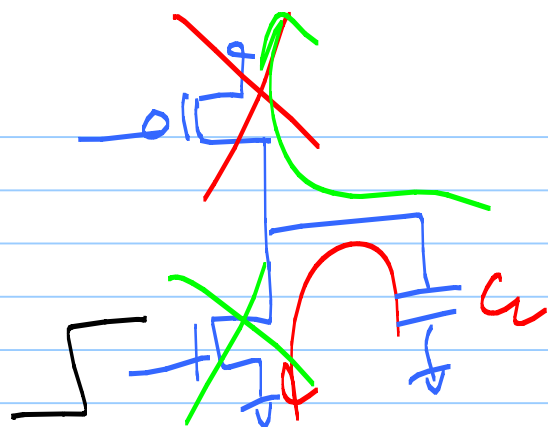


chapter 21 - Amplifiers

* low-frequency small-signal behavior

*


LNA


opamp.

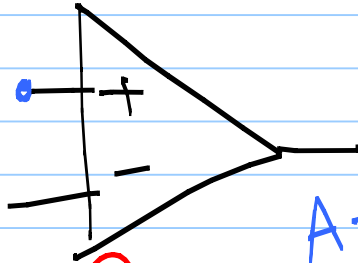

$A \rightarrow \infty$
 $R_{in} \rightarrow \infty$
 $R_{out} \rightarrow 0$

Signal processing

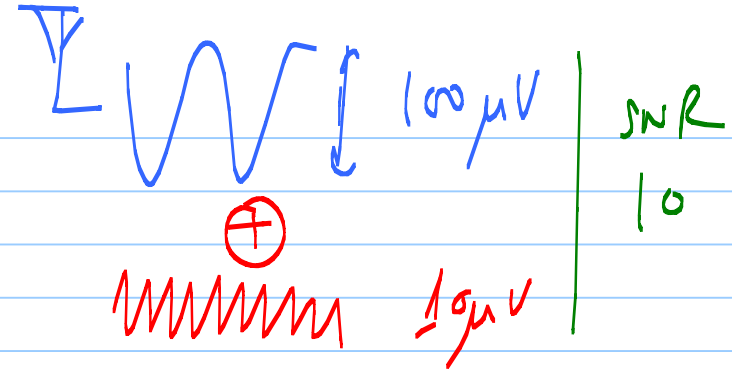

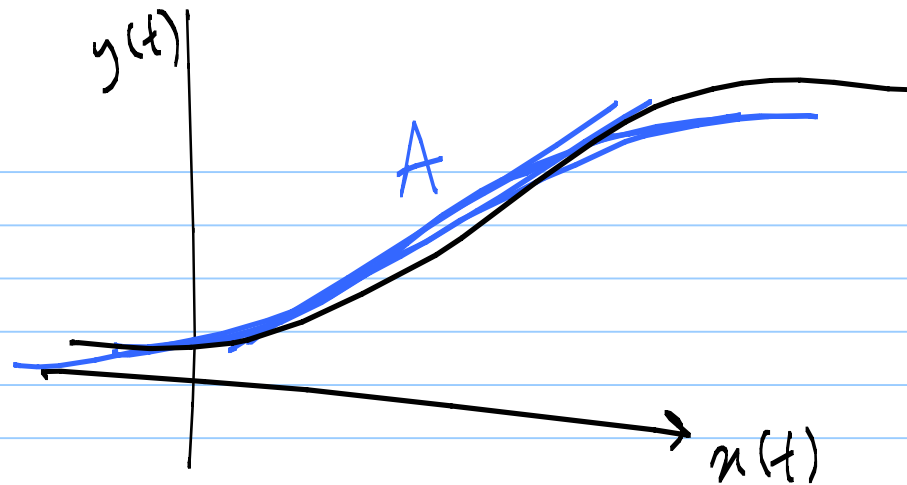

$$y(t) = \alpha_0 + \alpha_1 x(t) + \alpha_2 \cancel{x^2(t)} + \alpha_3 x^3(t) + \cancel{\dots};$$

for small $x(t)$

$$y(t) \approx \alpha_0 + \alpha_1 x_1(t)$$

DC operating point
 Small-signal gain

$$x(t) \uparrow \Rightarrow \cancel{x^2(t)}, \underline{\underline{x^3(t)}}$$

non-linearity


$\Rightarrow$ the feedback to improve linearity






non-linearity metrics $\rightarrow$ HD_3

RF system $\rightarrow$


IIP_3, IM_3

Trade-offs

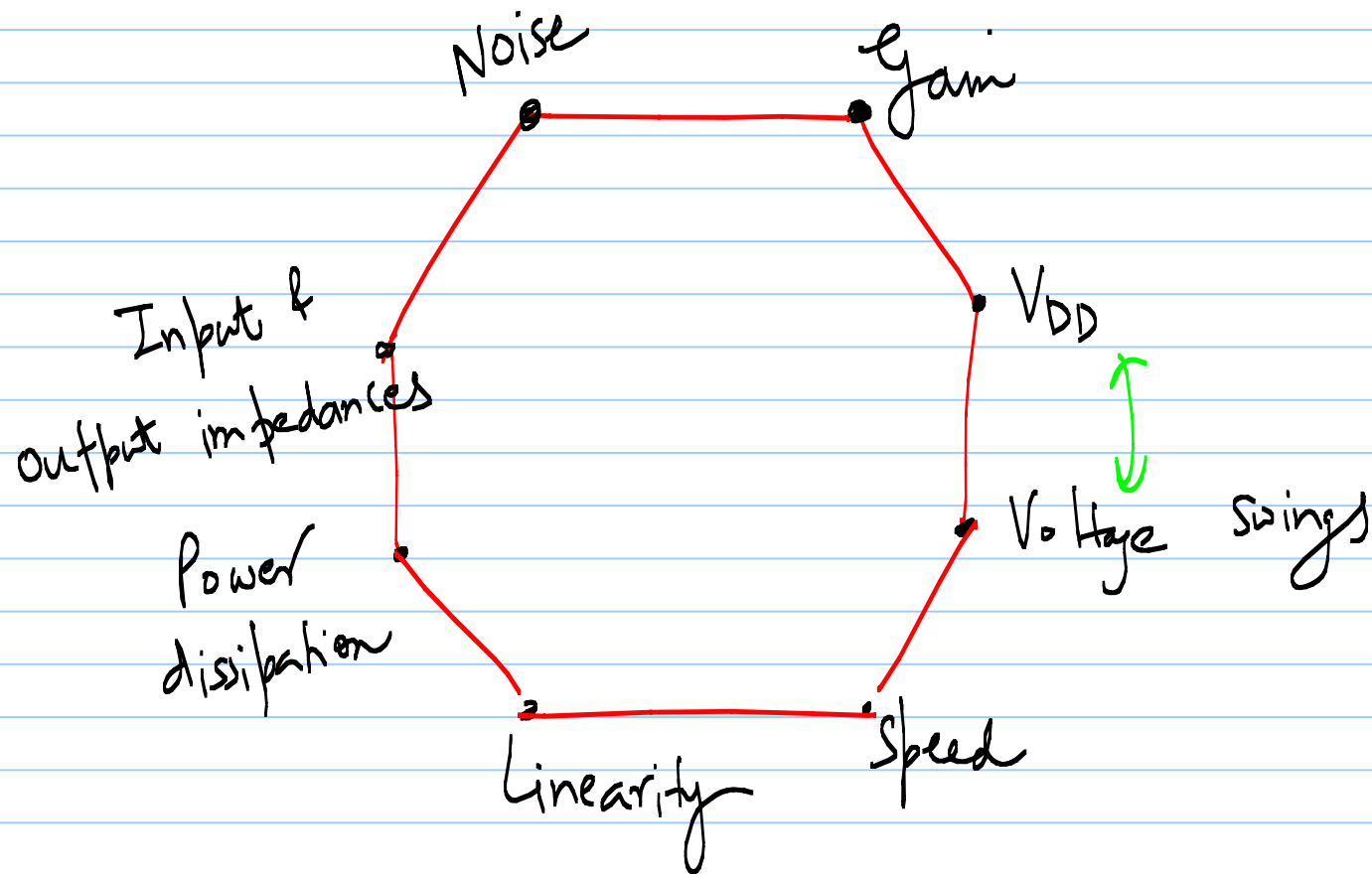


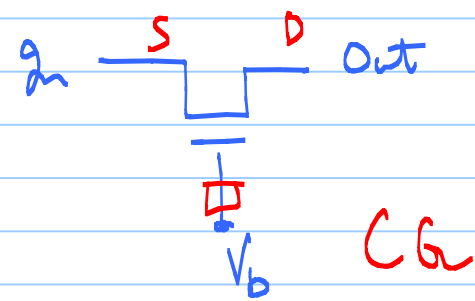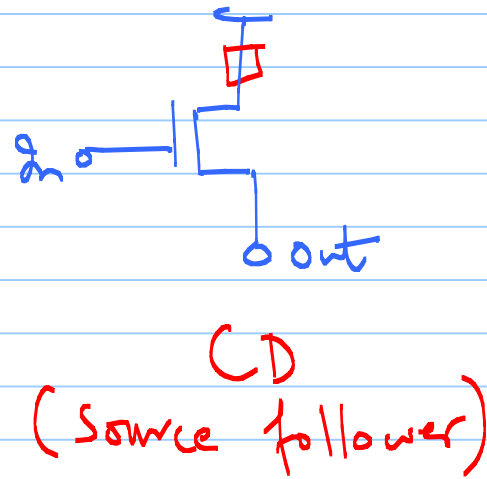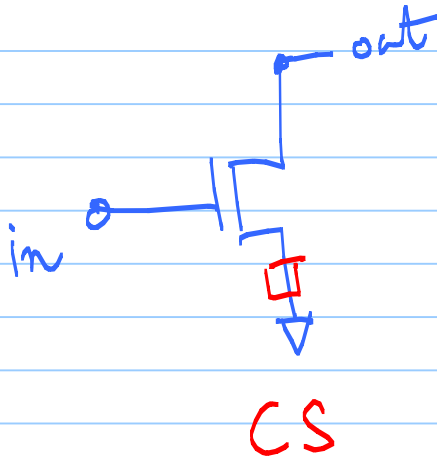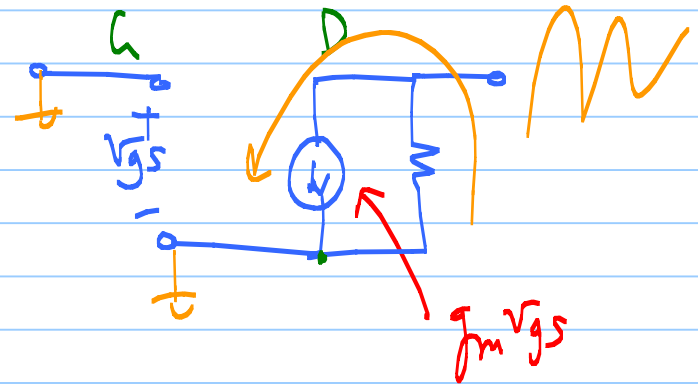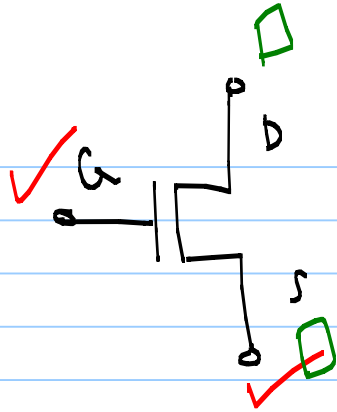

Common Source Amplifier (Stage)

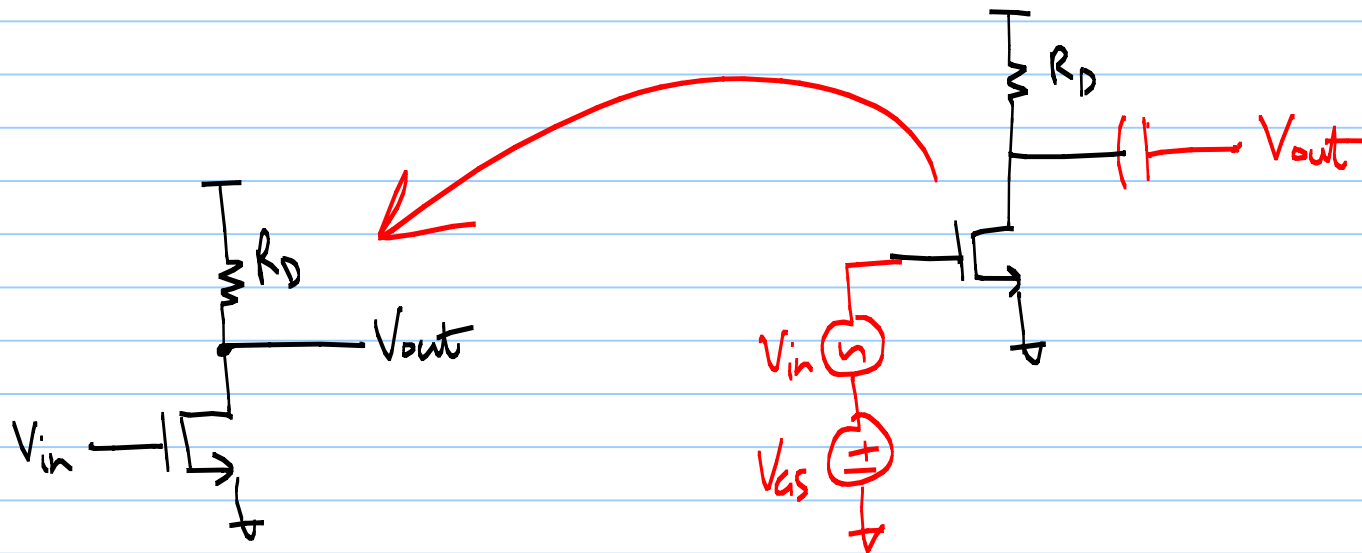

Small signal
equivalent

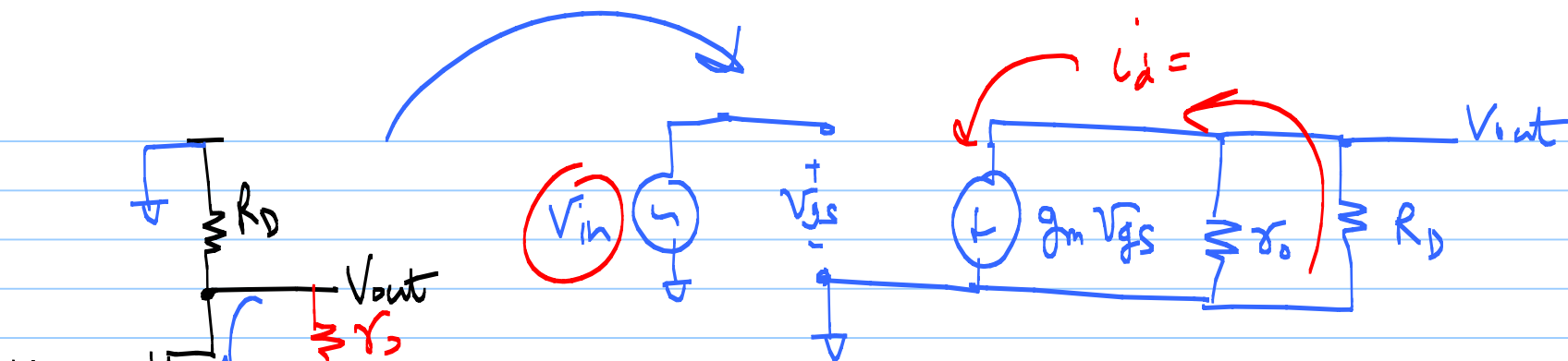




$$V_{out} = -i_d (R_D \parallel r_o)$$

$$= -g_m v_{gs} (R_D \parallel r_o)$$

$$\Rightarrow \boxed{\frac{V_{out}}{V_{in}} = -g_m (R_D \parallel r_o)}$$


$$R_D \ll r_o$$

$$A_v = \frac{V_{out}}{V_{in}} \approx -g_m R_D$$
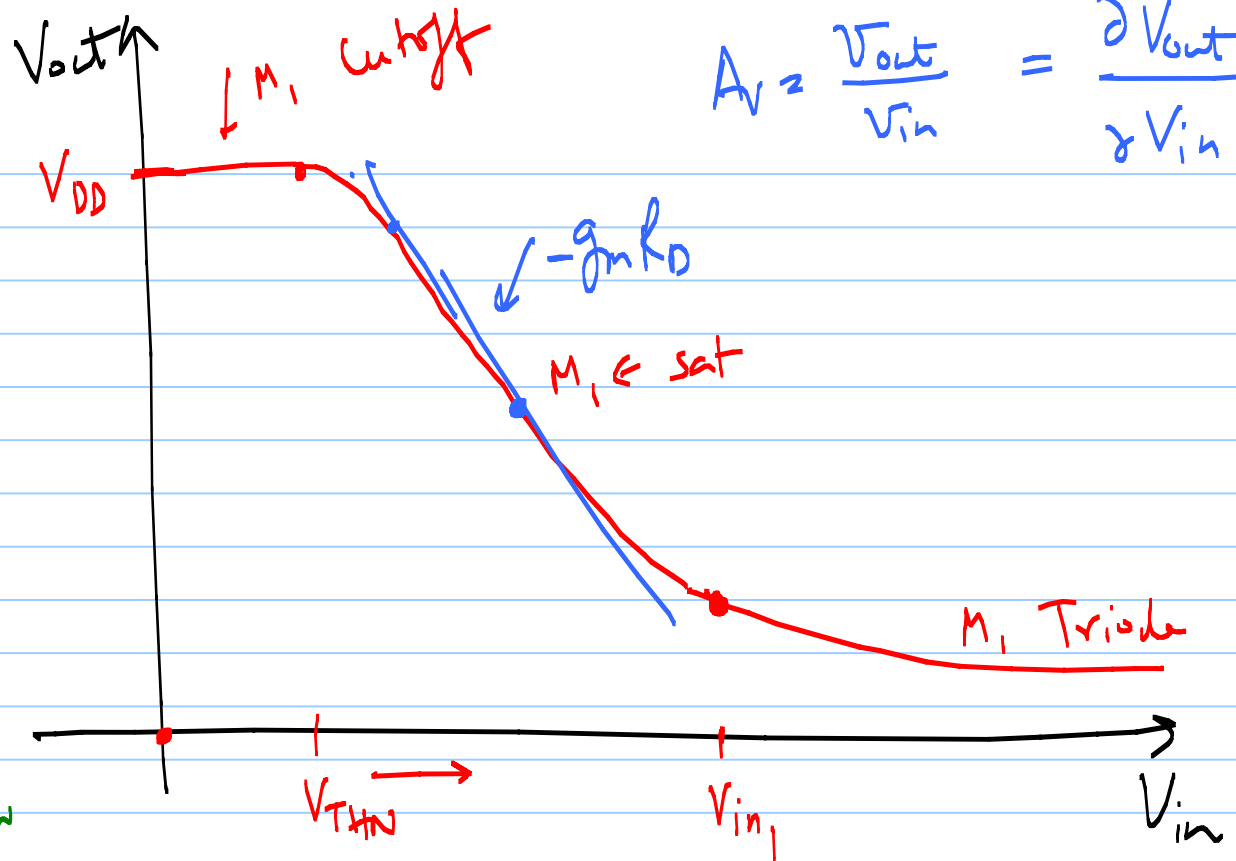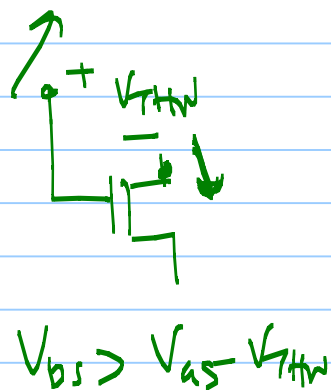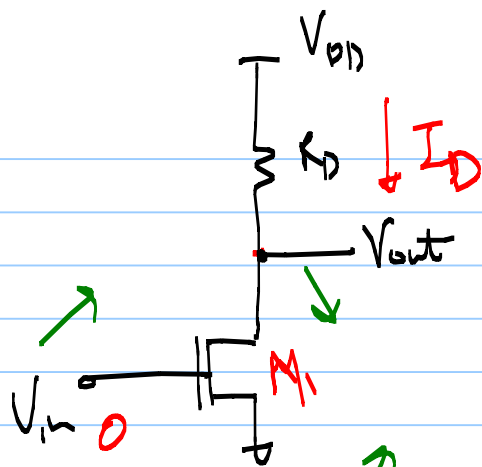
$$A_v = \frac{V_{out}}{V_{in}} = \frac{\partial V_{out}}{\partial V_{in}}$$

Large signal
behavior

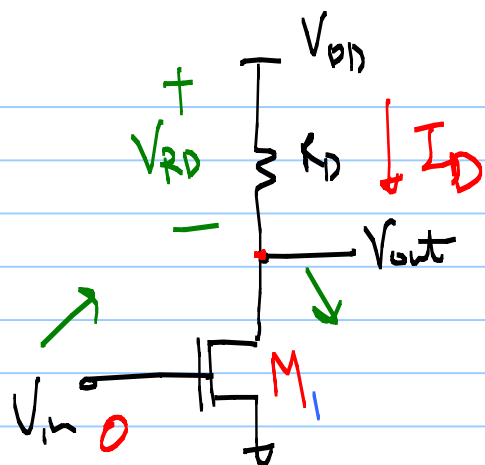

$$V_{out} = V_{DD} - I_D \cdot R_D$$

$$V_{out} = V_{DD} - \frac{K_P n}{2} \frac{W}{L} \cdot R_D (V_{in} - V_{THn})^2$$

$$A_v = \frac{\partial V_{out}}{\partial V_{in}} = - \boxed{\frac{K_P n}{2} \frac{W}{L} (V_{in} - V_{THn})} R_D$$

$$= \boxed{- g_m R_D}$$

$$A_v = -g_m R_D$$

$$g_m = \sqrt{2\beta I_D}$$

$$= -\sqrt{2K_p \frac{W}{L} I_D} \cdot R_D$$

$$\frac{V_{RD}}{I_D}$$

$$A_v = -\sqrt{2K_p \left(\frac{W}{L}\right)} \cdot \frac{V_{RD}}{\sqrt{I_D}}$$

$A_v \uparrow \Rightarrow$

• $\left(\frac{W}{L}\right) \uparrow$

• $V_{RD} \uparrow \Rightarrow$

• $I_D \downarrow \Rightarrow$


Swing $\downarrow$

~~lower speeds~~


$g_m R_D$

$R_D \uparrow$

$V_{RD} \uparrow$

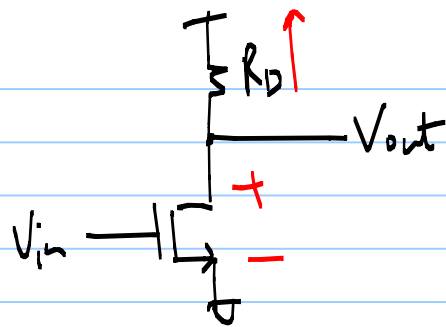

Diode-connected load


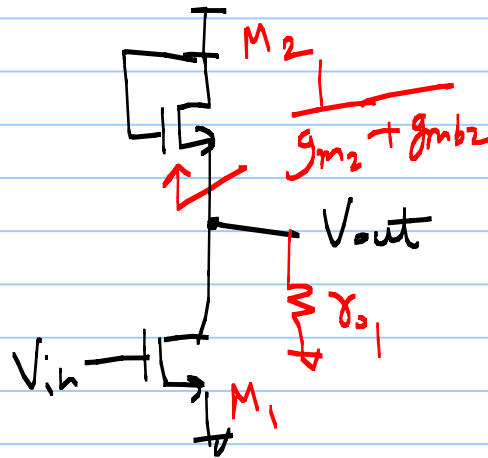


$$A = -g_{m1} \left(\frac{1}{g_{m2} + g_{mb2}} \parallel r_{o1} \right)$$

$$\approx -\frac{g_{m1}}{g_{m2} + g_{mb2}}$$

$$= -\frac{g_{m1}}{g_{m2}(1+\eta)} = \frac{\sqrt{2\beta_1 I_D}}{\sqrt{2\beta_2 I_D}} \frac{1}{(1+\eta)}$$

$$g_{mb2} = \eta g_{m2}$$

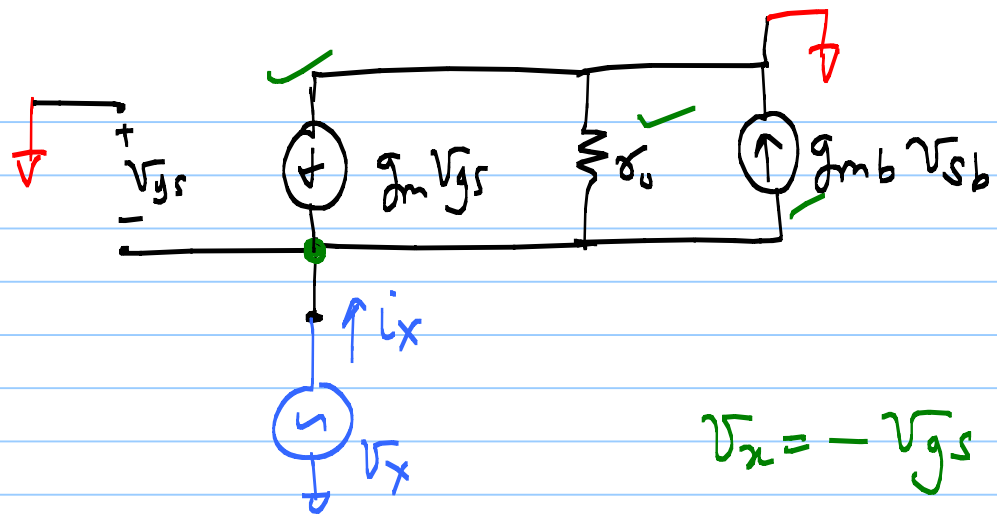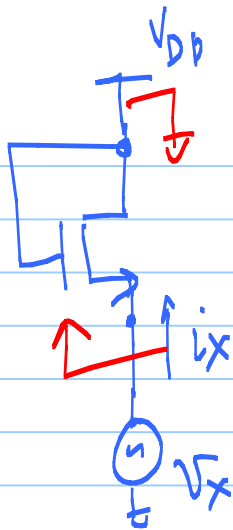


$$V_{gs} = -V_x$$

$$V_{sb} = V_x$$

$$(g_m + g_{mb})V_x + \frac{V_x}{r_o} = i_x$$


$$\frac{V_x}{i_x} = \frac{1}{g_m + g_{mb} + r_o^{-1}} \approx \frac{1}{g_m + g_{mb}}$$
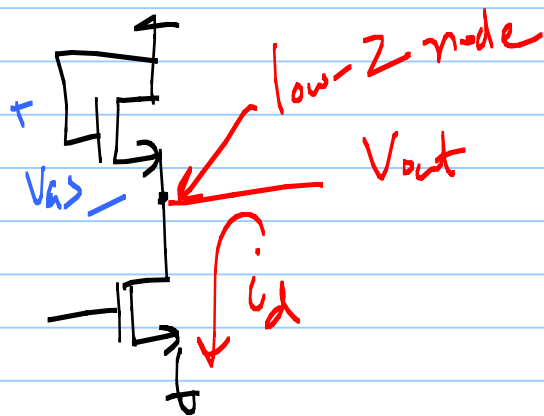
$$A_v = - \sqrt{\frac{(W/L)_1}{(W/L)_2}} \cdot \frac{1}{(\eta+1)}$$



$$V_{out} = - i_d \cdot R_D$$

$$= - g_m v_{in} R_D$$

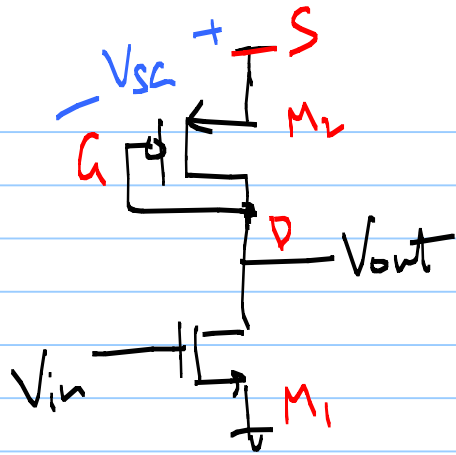

$$A_v = - \frac{g_{m1}}{g_{m2}} = - \frac{\sqrt{(\mu/L)_1}}{\sqrt{(\mu/L)_2}}$$

