



ECE 511 - Lecture 12

Note Title

3/5/2012

SF


Find R_{out} ?

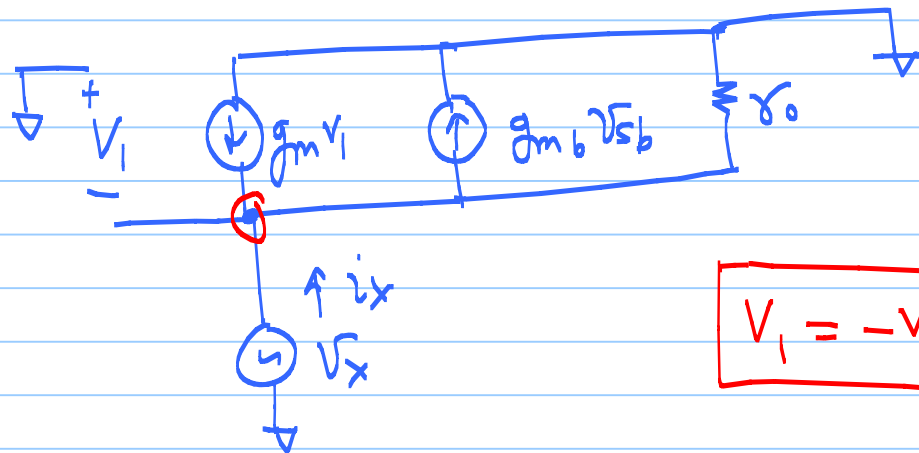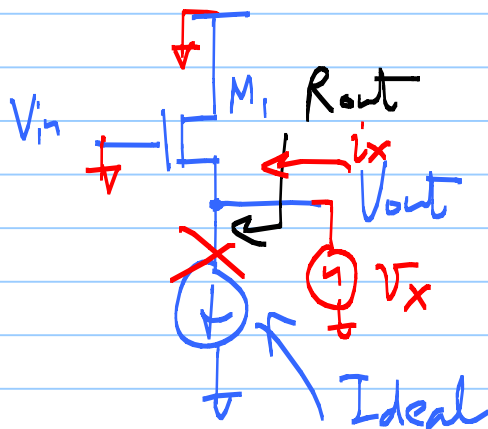

$$V_1 = -V_x$$



$$i_x - g_m v_x - g_{m_b} v_x + \frac{v_x}{r_o} = 0$$

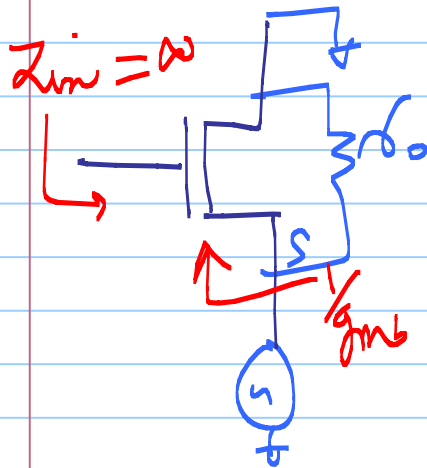
$$\boxed{R_{out}} = \frac{v_x}{i_x} = \frac{1}{g_m + g_{mb} + \frac{1}{r_o}} = \frac{1}{g_m} \parallel \frac{1}{g_{mb}} \parallel r_o \approx \boxed{\frac{1}{g_m}}$$





resistance
looking into
the source

$\Rightarrow$ Low- Z

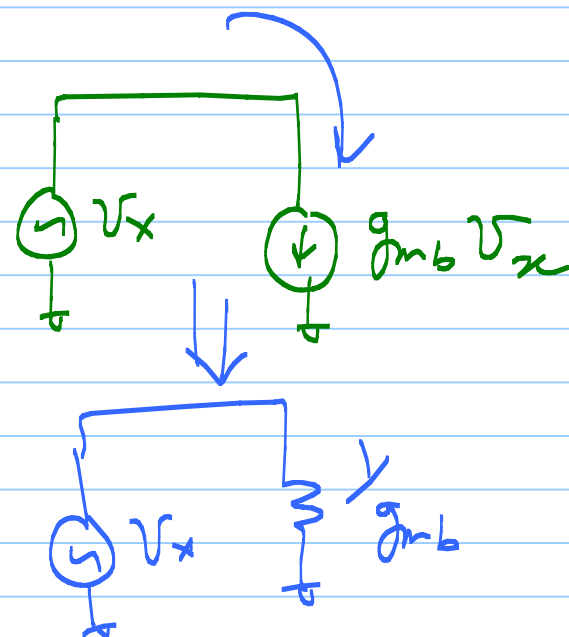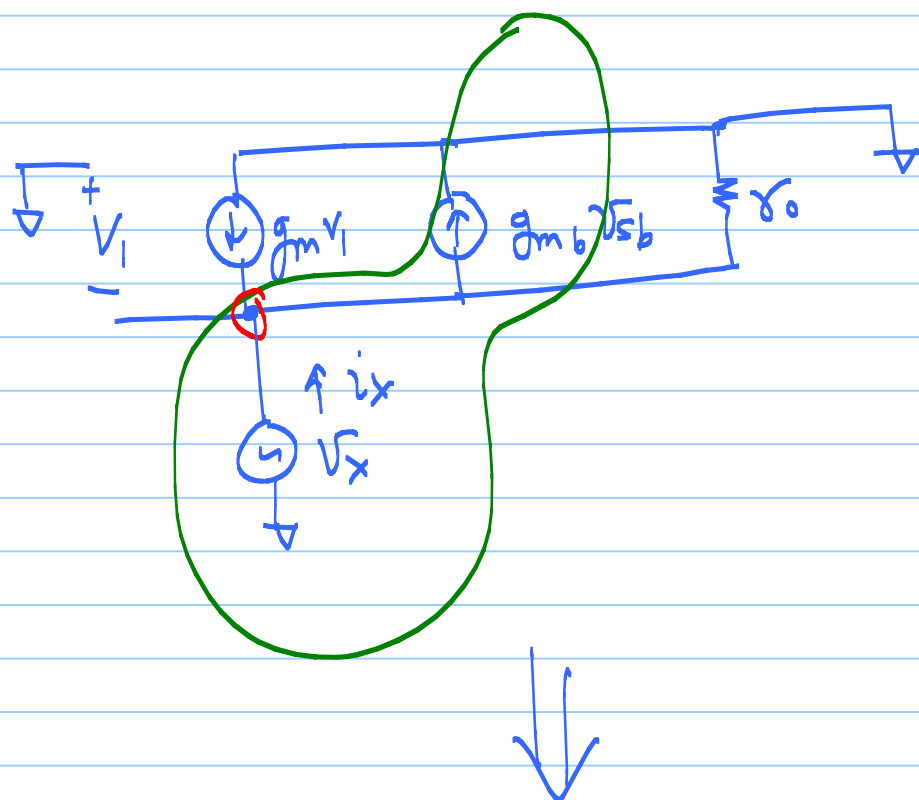

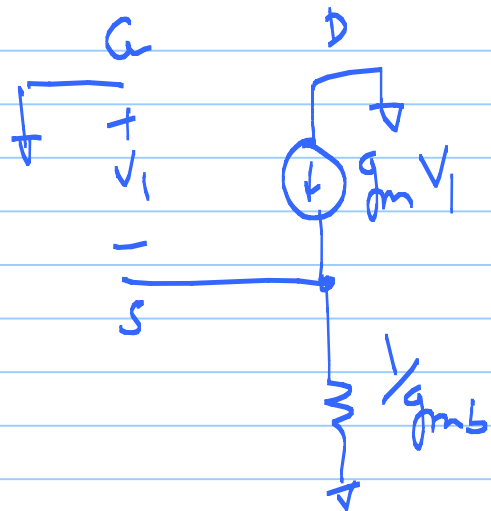


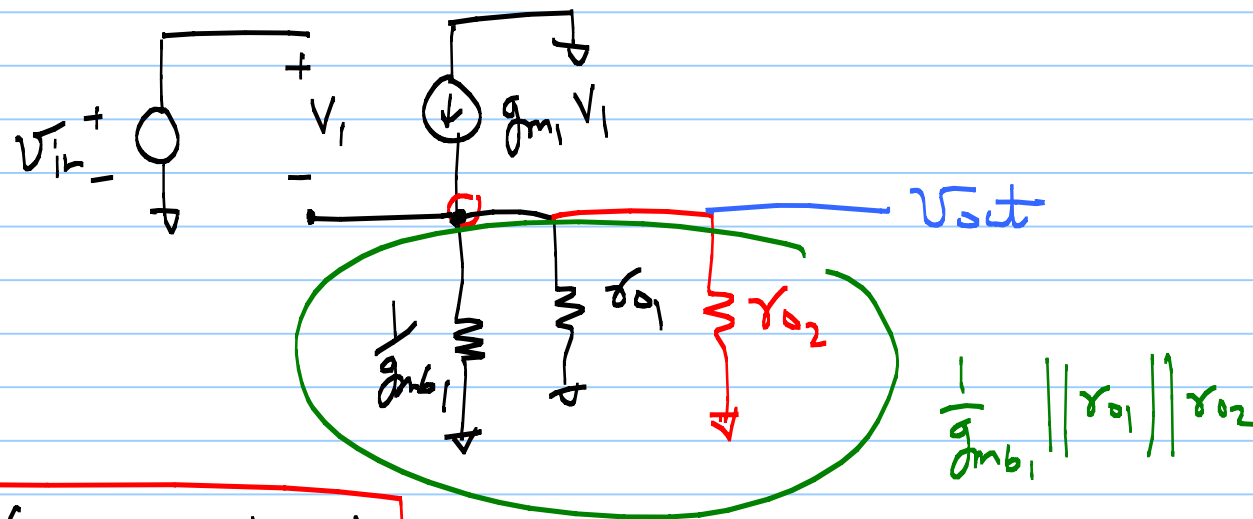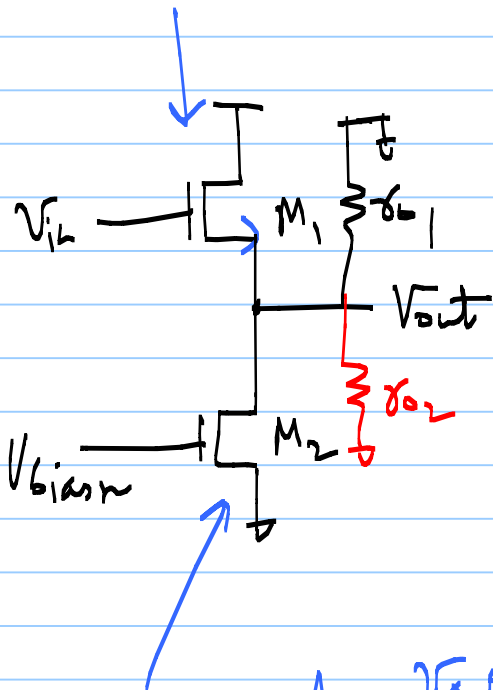

$$A = \frac{V_{out}}{V_{in}} = \frac{\left(\frac{1}{g_{m1}} \parallel r_{o1} \parallel r_{o2} \right)}{\frac{1}{g_{m1}} + \left(\frac{1}{g_{m1}} \parallel r_{o1} \parallel r_{o2} \right)}$$

resistance looking into the source

resistance connected to the source

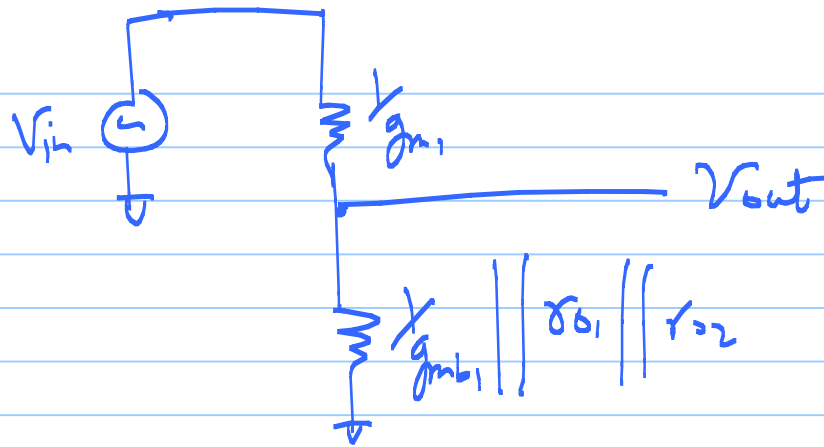

$$\frac{1}{g_{mb1}} \parallel g_{o1} \parallel r_{o2} \approx \frac{1}{g_{mb1}}$$


$\Rightarrow$

$$A_v =$$

$$\frac{\frac{1}{g_{mb1}}}{\frac{1}{g_{m1}} + \frac{1}{g_{mb1}}} = \frac{g_{m1}}{g_{mb1} + g_{m1}} = \frac{1}{\eta + 1}$$



$\downarrow \eta g_{m1}$

Voltage Buffer

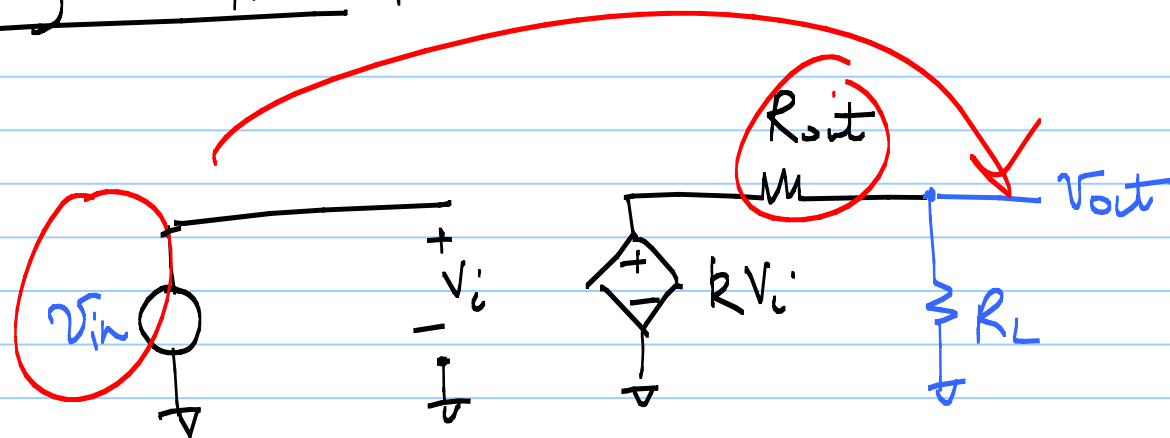

$$V_{out} \leq V_{in}$$
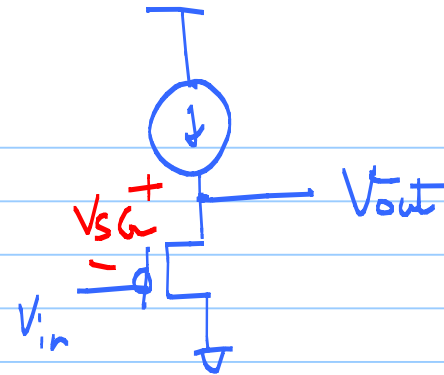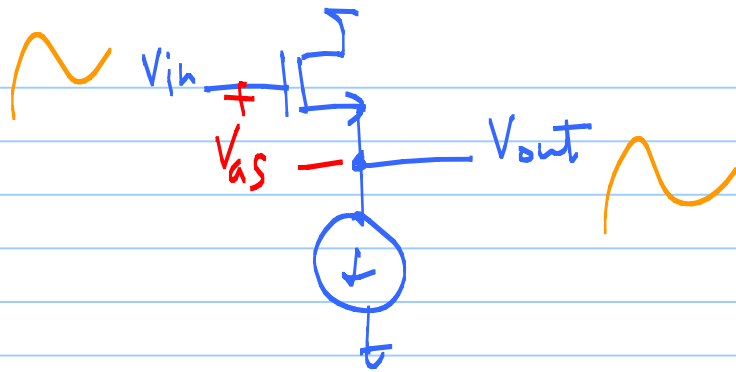
$$\frac{V_{out}}{V_{in}} = \frac{R_L}{R_{out} + R_L} = \frac{1}{\left(\frac{R_{out}}{R_L}\right) + 1} \rightarrow 0$$



① SF $\Leftarrow$ "Voltage" Buffer

② Level shifting


$$A_v \approx \frac{1}{\eta + 1}$$

⊖ Body effect $\Rightarrow V_{TH}$ depends V_{source}



⊖ low R_L

$$A_v = \frac{R_L}{R_{out} + R_L}$$

Example:

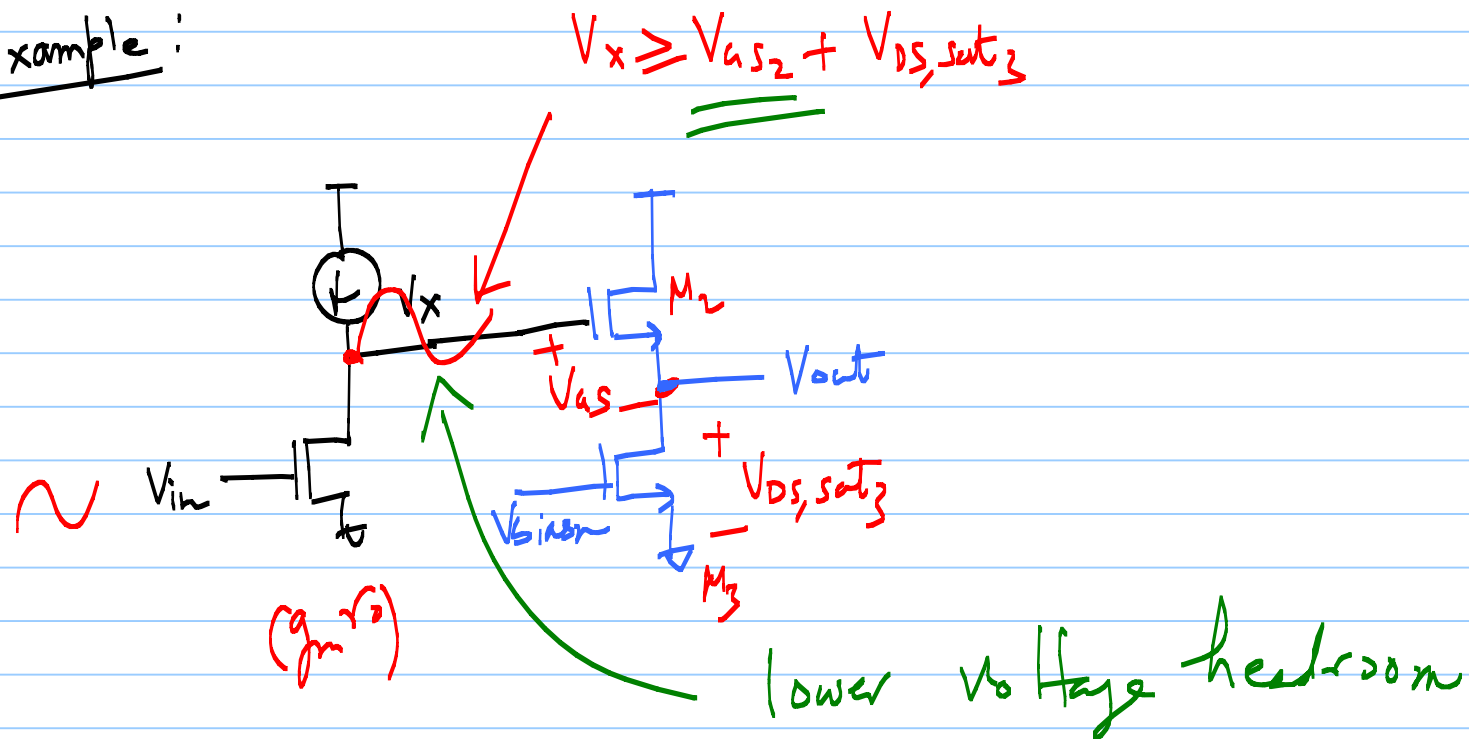

Example

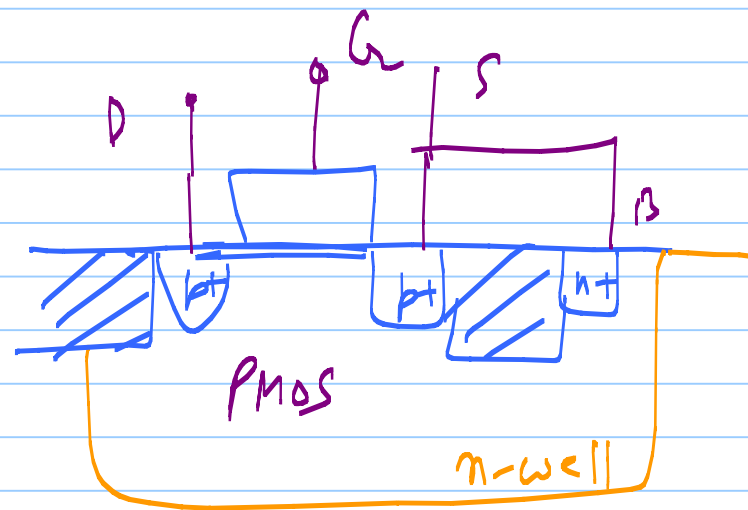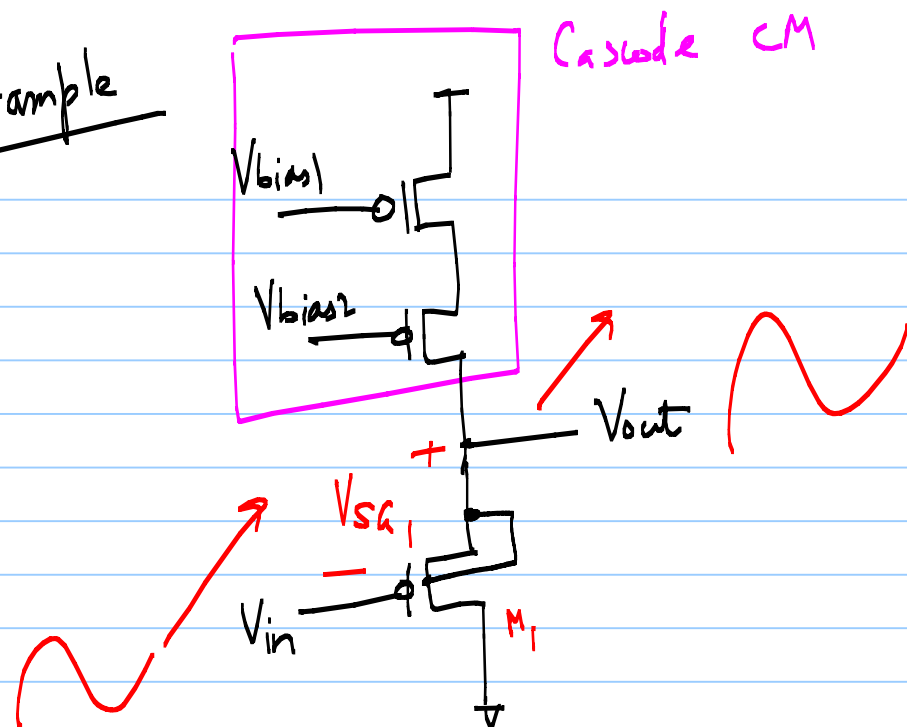

- ① M_1 is in saturation as long as
- $$V_{SD} = V_{out} \geq V_{SG} - V_{THP}$$

$$\Rightarrow \cancel{V_{out}} \geq \cancel{V_{out}} - V_{in} - V_{THP}$$

$$\Rightarrow \underline{\underline{V_{in} \geq -V_{THP}}} \quad \text{for } V_{in} \in [0, V_{DD}]$$

not a problem

$$\textcircled{2} \quad V_{out} < V_{DD} - 2V_{SD, sat}$$


$$\Rightarrow V_{in} + V_{SG1} < V_{DD} - 2V_{SD, sat}$$

$$\Rightarrow \boxed{V_{in} < V_{DD} - 2V_{SD, sat} - V_{SG1}}$$


$$-V_{THP} \leq V_{in} \leq V_{DD} - 2V_{SO,sat} - V_{SG1}$$

↑ input range for the level-shifter



Common-gate Stage

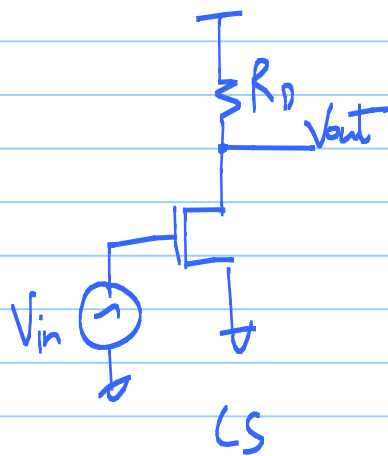

$\Rightarrow$

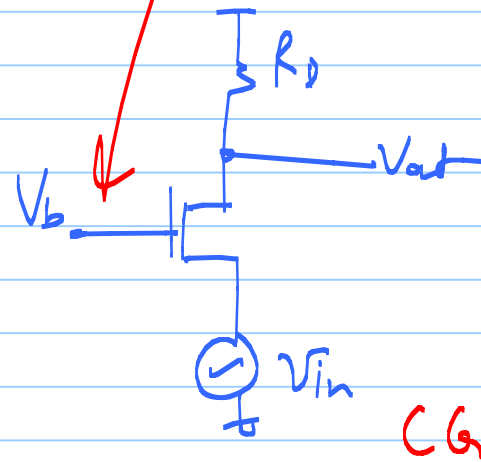


Gate is biased

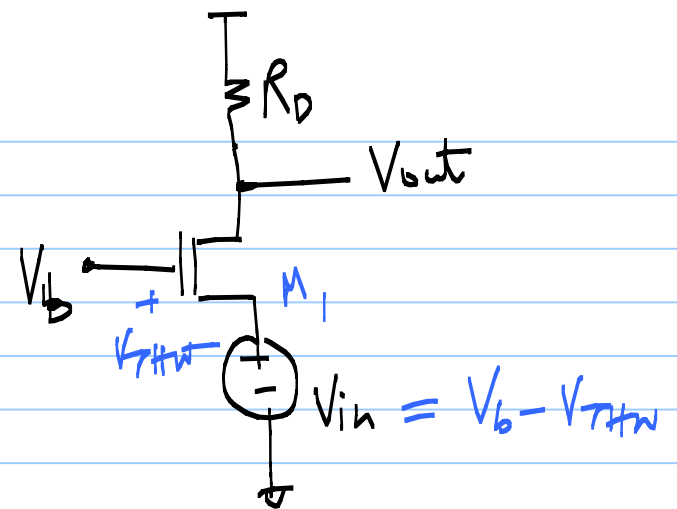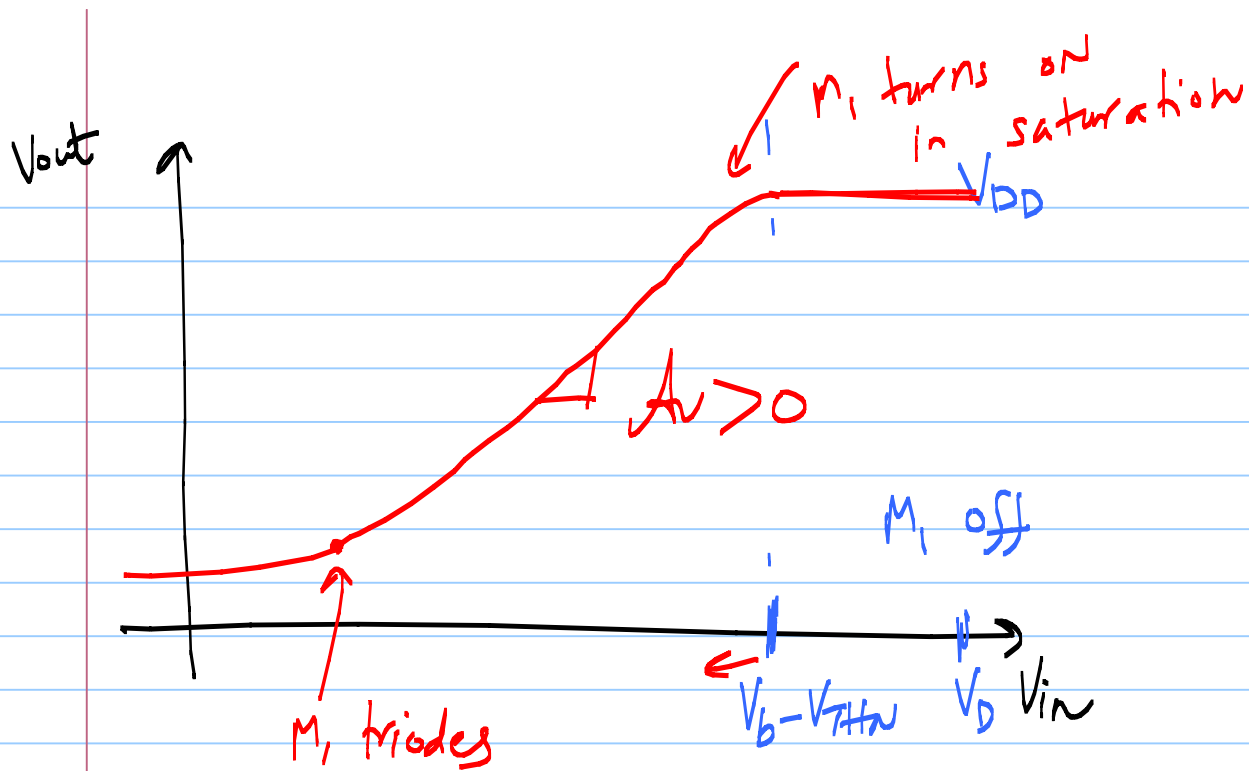

M_1 is in saturation
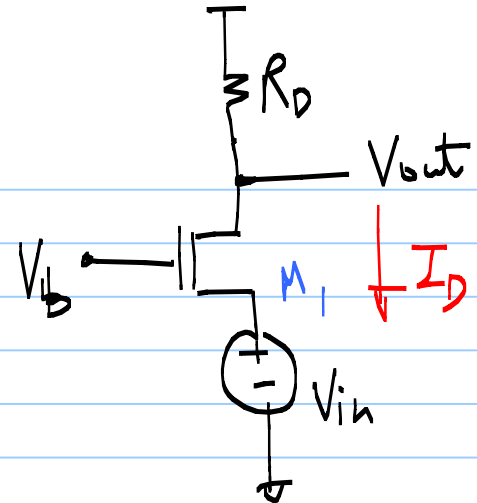
$$I_D = \frac{K_{Pn}}{2} \frac{W}{L} (\underbrace{V_b - V_{in}}_{V_{as}} - V_{THN})^2 \longrightarrow (1)$$



$$V_{out} = V_{DD} - I_D \cdot R_D$$

$$V_{out} = V_{DD} - \frac{K_{Pn}}{2} \frac{W}{L} (V_b - \underline{V_{in}} - V_{THN})^2 R_D$$

$$A_v = \frac{\partial V_{out}}{\partial V_{in}} = -K_{Pn} \frac{W}{L} (V_b - V_{in} - V_{THN}) \cdot \left(-1 - \frac{\partial V_{THN}}{\partial V_{in}} \right) R_D$$


$\nearrow$


$$\Rightarrow A_v = K P_n \frac{w}{L} (V_b - V_{in} - V_{THn}) (1 + \eta) R_D$$

$$A_v = + g_m R_D (1 + \eta)$$

+ve gain

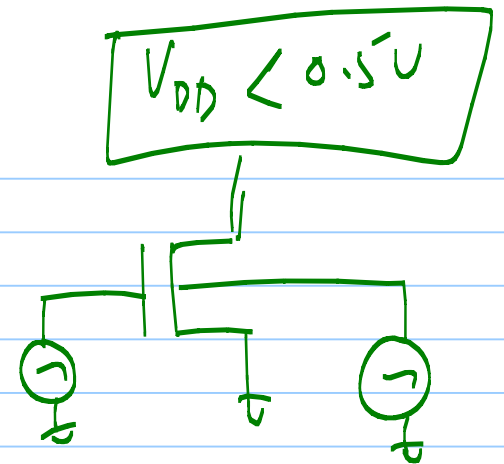
$(1 + \eta) \leftarrow$ more gain due to body effect



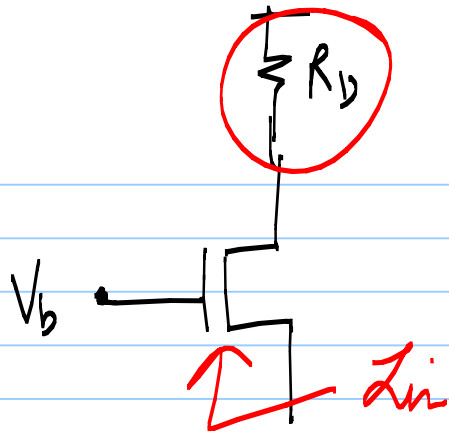


$$R_D \ll r_o$$

$$z_{in} \approx \frac{1}{g_m}$$

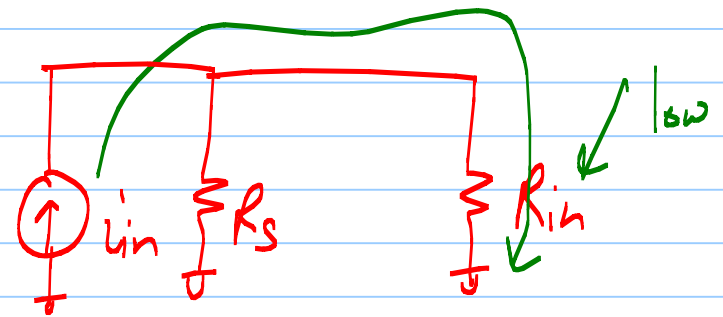

$$R_{in} \ll R_S$$

* CG makes a good current input stage

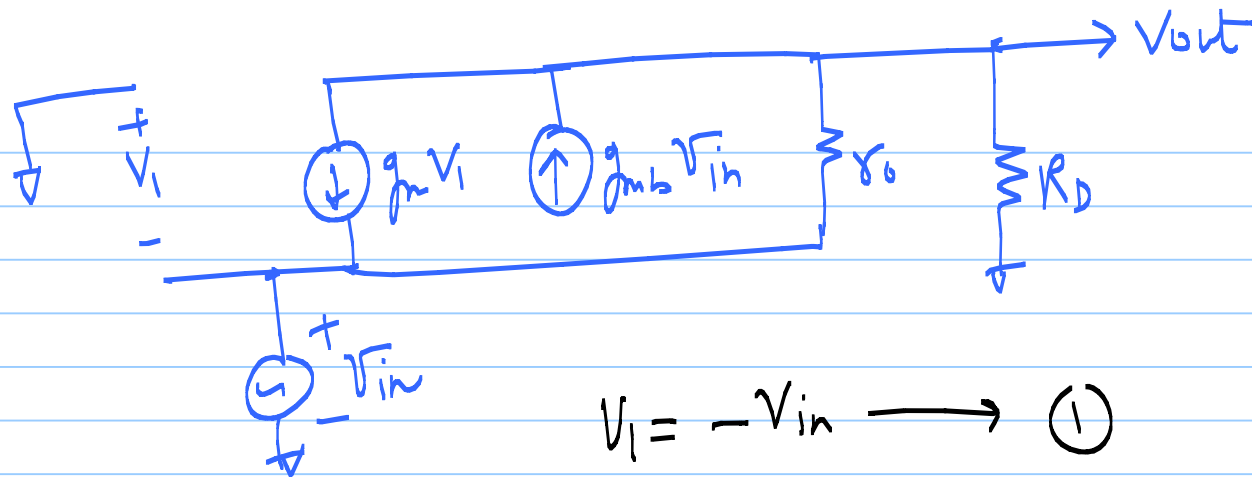



$$V_1 = -V_{in} \longrightarrow (1)$$

$$-g_m V_1 + g_m b V_{in} - \frac{(V_{out} - V_{in})}{r_o} - \frac{V_{out}}{R_D} = 0$$

$$A_v = \left[(g_m + g_m b) + \frac{1}{r_o} \right] \cdot (R_D \parallel r_o)$$

for $r_o \gg R_D$

$$A_v \approx (\eta + 1) g_m R_D$$

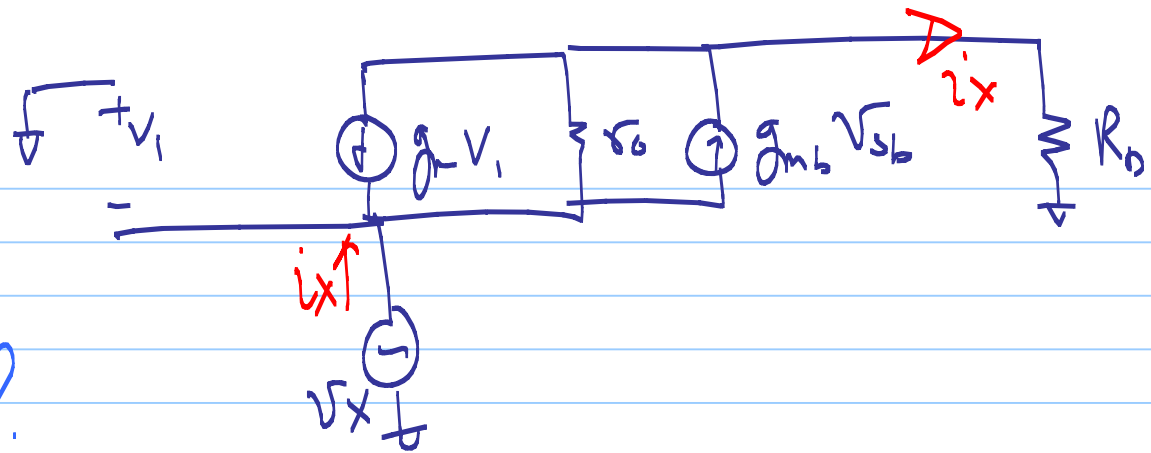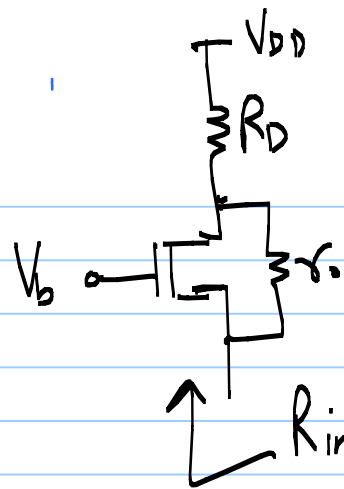

$$R_{in} = \frac{v_x}{i_x} = \frac{R_D + r_o}{1 + (g_m + g_{mb}) r_o}$$

$$\text{for } (g_m + g_{mb}) r_o \gg 1$$



$$\approx \frac{R_D}{(g_m + g_{mb}) r_o} + \frac{1}{(g_m + g_{mb})}$$

Special Case (A) $R_D = 0$

$$R_{in} = \frac{1}{g_m + g_{mb}}$$

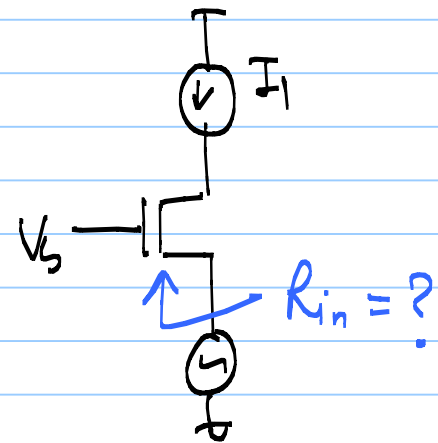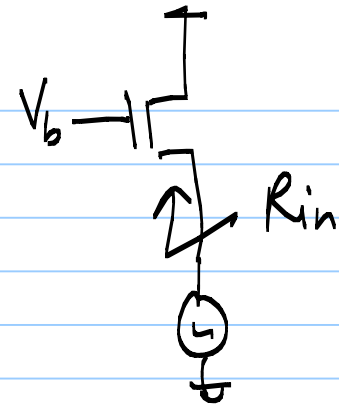(B) $R_D \leftarrow$ Ideal Current Source

$$R_{in} = \frac{R_D}{(g_m + g_{mb})r_o} \rightarrow \infty$$



② $R_D = g_{m2} r_{o2}^2$ ← Cascode Current Source

$$R_{in} = \frac{g_{m2} r_{o2}^2}{(g_{m1} + g_{mb}) r_{o1}} + \frac{1}{(g_{m1} + g_{mb})}$$


$$g_{m2} = g_m$$

$$r_{o2} = r_o$$

$$\approx r_o + \frac{1}{g_{m1} + g_{mb}}$$


$$\approx r_o$$

$$\approx$$

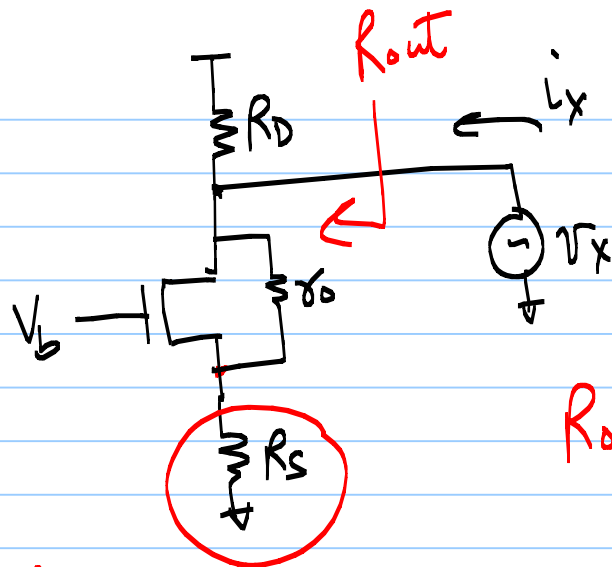

looks similar to the R_{out} of
SD-CS
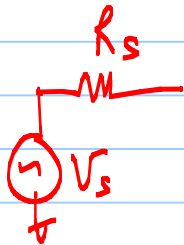
$$R_{out} = \left\{ \underbrace{[1 + (g_m + g_{mb})r_o]R_s + r_o}_{g_m r_o R_s} \right\} \parallel R_D$$



$R_{out} \Rightarrow$ moderate to high impedance

$R_{in} \Rightarrow$ Low if $R_D \approx r_o$