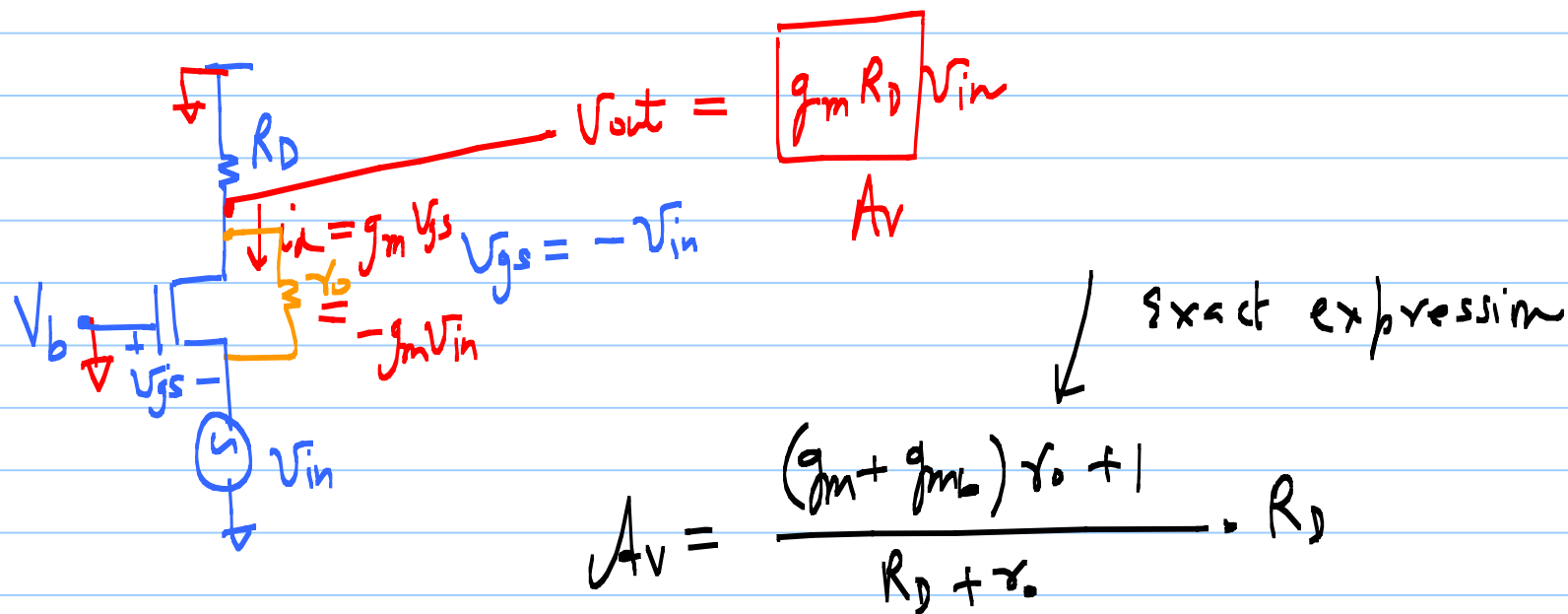


ECE 511 - Lecture 13


Note Title

3/7/2012



For $r_0 \gg R_D$

$\approx \underline{(1 + \eta) g_m R_D}$

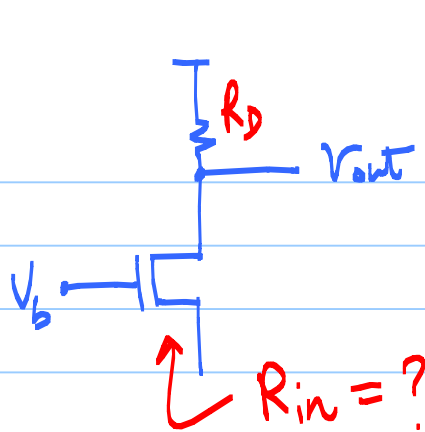


$$R_D \leq r_o \Rightarrow R_{in} = \frac{1}{g_m + g_{mb}} \approx \frac{1}{g_m}$$

$$R_D \gg r_o \Rightarrow R_{in} = \frac{R_D}{(g_m + g_{mb}) r_o} \approx \frac{R_D}{g_m r_o}$$

$$R_D = g_m r_o^2$$

$$\hookrightarrow R_{in} \approx r_o$$

$$R_{in} \ll \infty$$

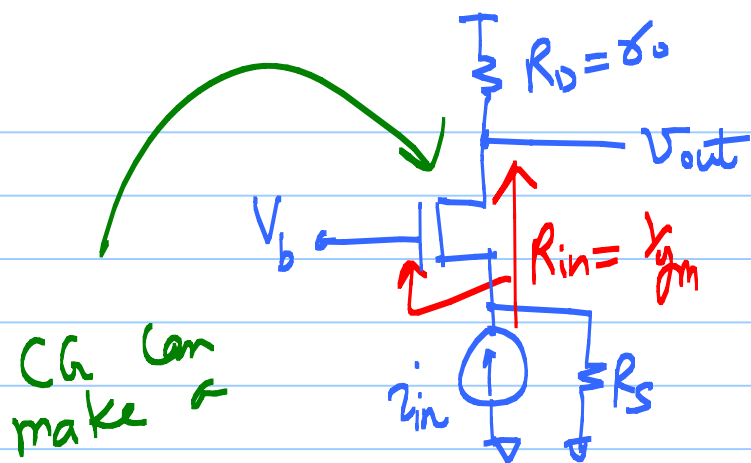

CG can
make a

good
current buffer

$$\frac{1}{g_m} \ll R_s$$

Application $\rightarrow$ Transimpedance amplifier

	gain	@ Low-f Z_{in}	@ Low-f Z_{out}	
CS	Large	∞	Moderate (r_o)	→ Amplifier
CS-SD	Medium	∞	High	→ Linear amplifier
SF	(<1) Low	∞	* Low ($= 1/g_m$)	→ Voltage Buffer
CG	Medium/high	Low *	Moderate/high	→ Current Buffer

CASCODE Amplifier

$$V_{out} = -i_d (R_D \parallel R_{cas})$$

$$= -g_m (R_D \parallel R_{cas}) V_{in}$$


$$A_v = -g_m (R_D \parallel R_{cas})$$



$$A_v = -g_m R_{cas}$$

$$= -g_m (g_m r_o^2)$$



$$A_v = -g_m r_o$$


$$R_{out} = r_o$$

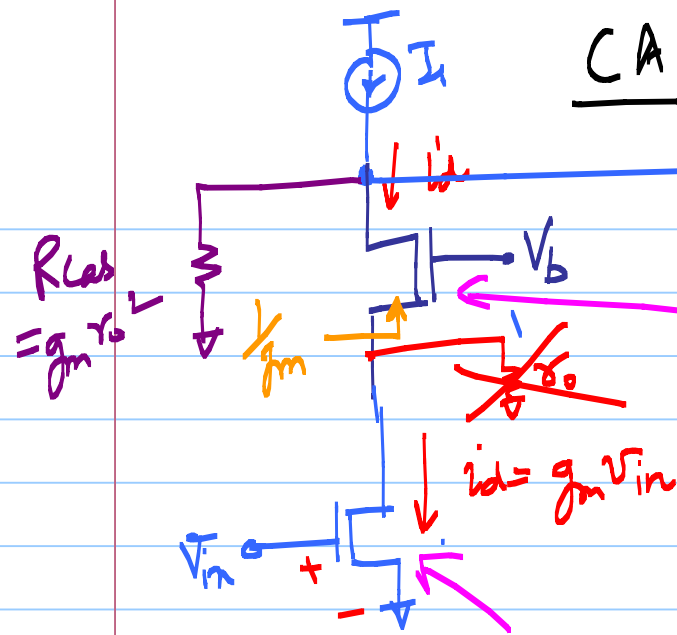

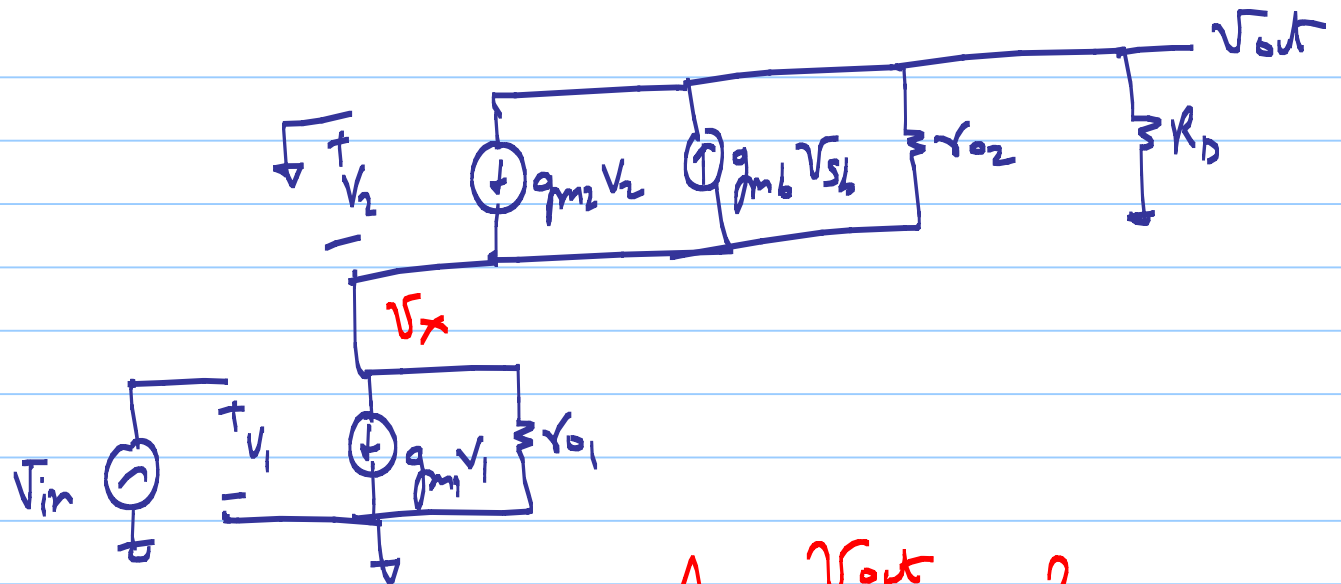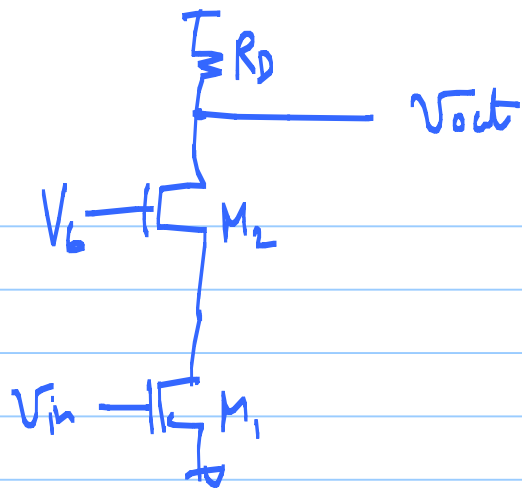


$$A = \frac{V_{out}}{V_{in}} = ?$$

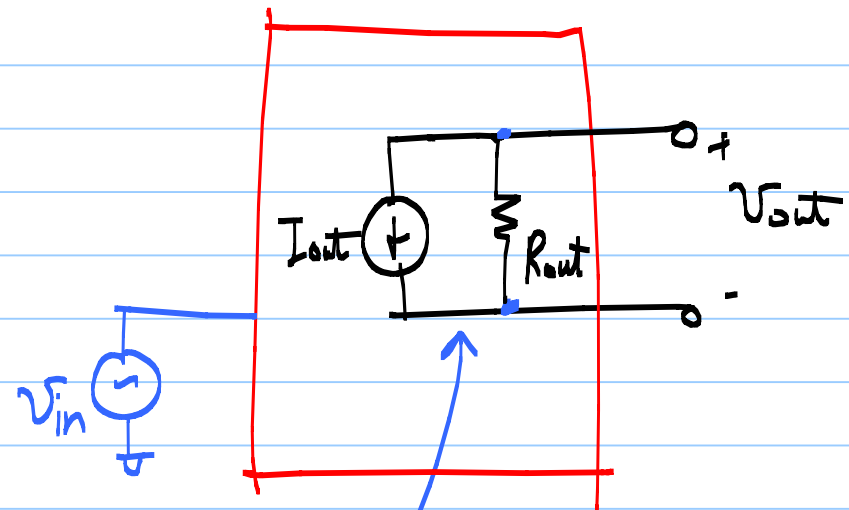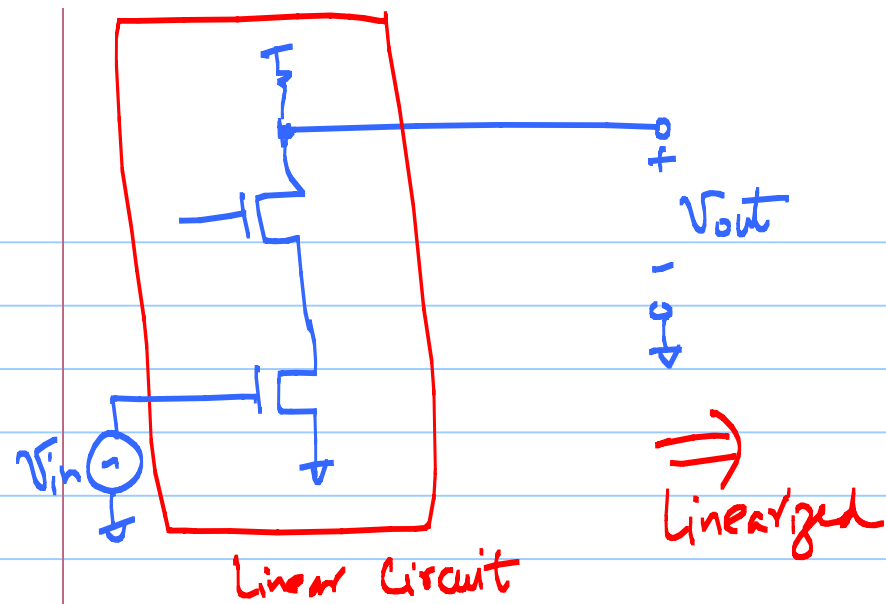

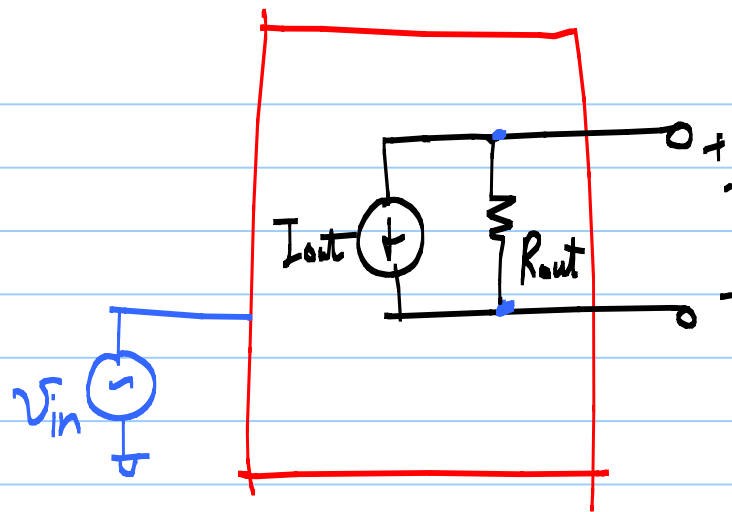

open circuit output ?

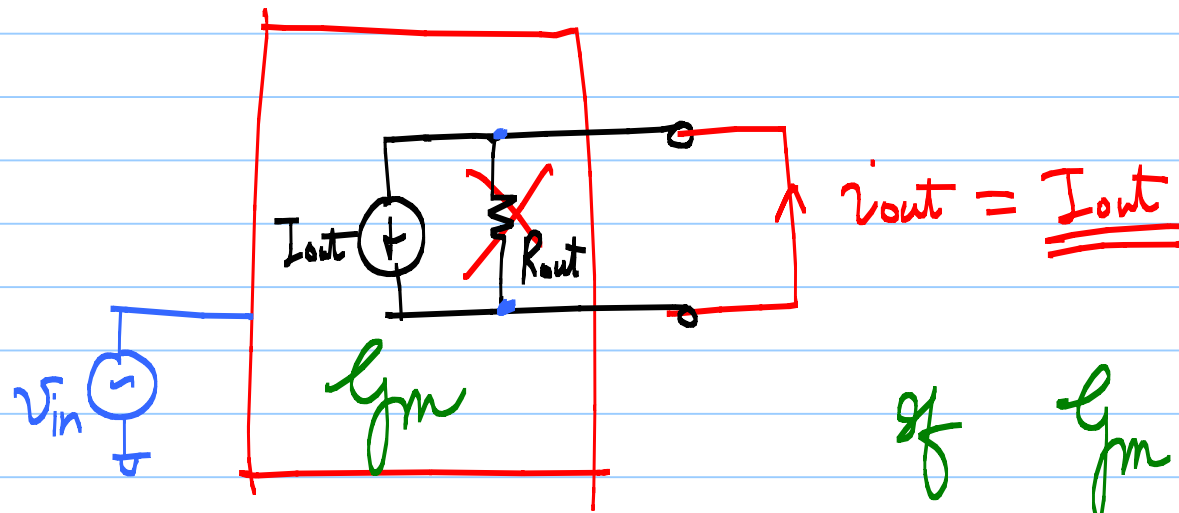
$$V_{out} = -I_{out} \cdot R_{out} \longrightarrow \textcircled{1}$$



$$\text{of } g_m \triangleq \frac{I_{out}}{v_{in}} \rightarrow \textcircled{2}$$

$$V_{out} = - I_{out} R_{out} = - (g_m R_{out}) v_{in}$$
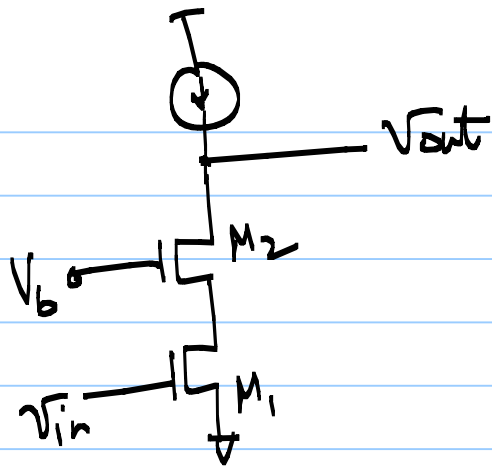
$$\Rightarrow A_v = \frac{V_{out}}{v_{in}} = - g_m R_{out}$$




$$A_v = -g_m R_{out}$$

$$i_{out} = g_{m1} v_{in}$$

??

$$\approx (g_{m2} + g_{m2b}) r_{o2} r_{o1}$$

$$\approx g_m r_o^2$$

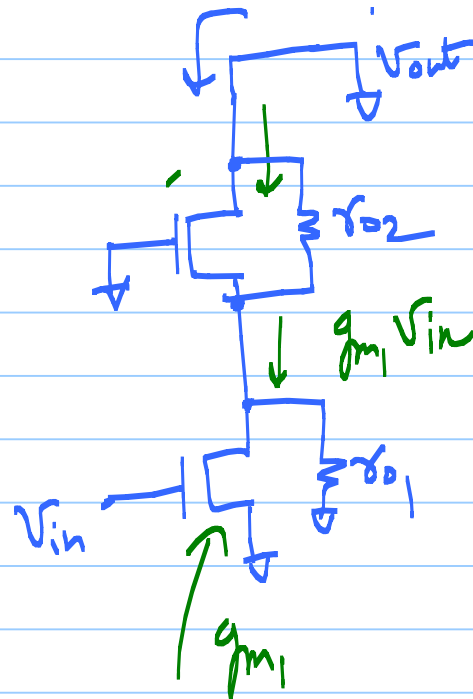

$$g_m = \frac{i_{out}}{v_{in}}$$

$$g_m = \frac{g_{m1} r_{o1} [\cancel{r_{o2}} (g_{m2} + \cancel{g_{m2} b}) + 1]}{\cancel{r_{o1}} \cancel{r_{o2}} (g_{m2} + \cancel{g_{m2} b}) + r_{o1} + r_{o2}}$$

$$\eta = \gamma = 0$$

$$= g_{m1} r_{o1} \left[\frac{\cancel{g_{m2} r_{o2} + 1}}{\cancel{g_{m2} r_{o2}}} \right]^1$$

$$\underline{g_{m2} r_{o2} \gg 1}$$

$$\cancel{r_{o1}} + \frac{(r_{o1} + r_{o2})}{g_{m2} r_{o2}}$$


$$= \frac{\cancel{g_{m1} r_{o1}}}{\cancel{r_{o1}} + \cancel{r_{o2}}} = \underline{\underline{g_{m1}}} \leftarrow \text{Approximation}$$

$$A_v \approx -g_m R_{out}$$


$$= -g_{m1} \cdot (g_{m2} + g_{m2b}) r_{o1} r_{o2}$$

$$= -g_{m1} \cdot (g_{m2} r_{o1} r_{o2}) \stackrel{\Delta}{=} -g_m^2 r_{o1}^2$$

Cascode

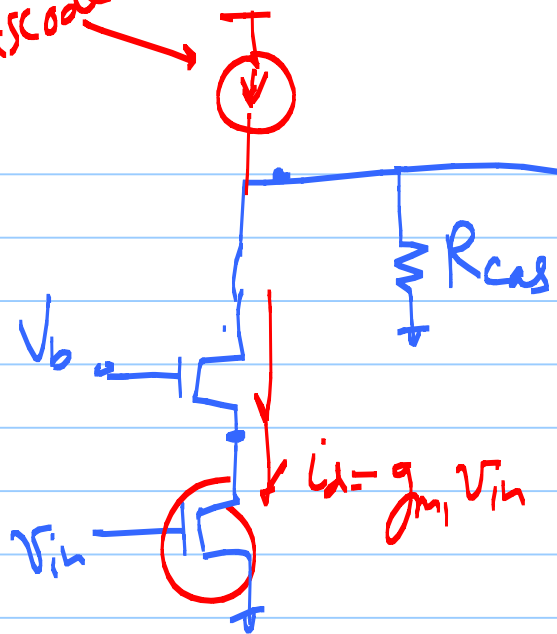
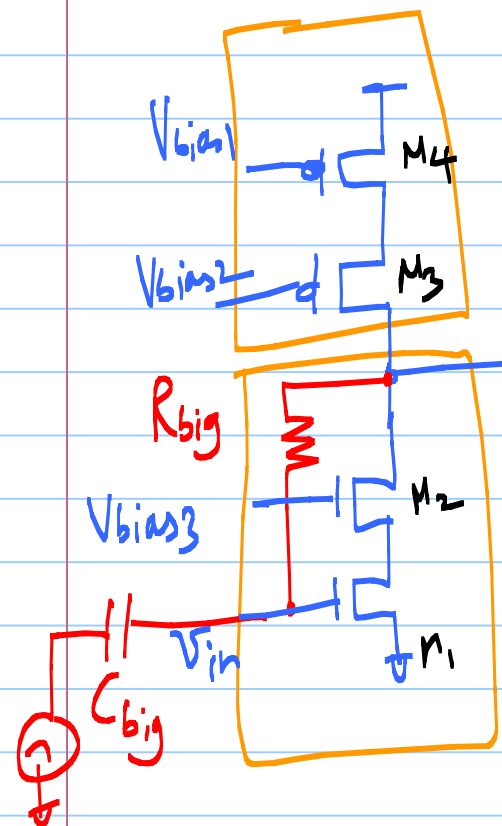
$$V_{out} = - \underbrace{g_{m1} R_{cas}} \cdot V_{in}$$



$$R_{\text{cas}} = g_{m3} r_{o3} r_{o4} = g_{m3} r_{o3}^2 r_{o4}$$

Fig 21.35


$$A_v = -g_{m1} \cdot R_{\text{out}}$$

$$= -g_{m1} \cdot (g_{m1} r_{o1} r_{o2} \parallel g_{m3} r_{o3} r_{o4})$$


$$\Delta = -g_{m1} (g_{m1} r_{o1}^2 \parallel g_{m3} r_{o3}^2)$$

$$= -\frac{g_{m1}^2 r_{o1}^2}{2}$$

Cascode

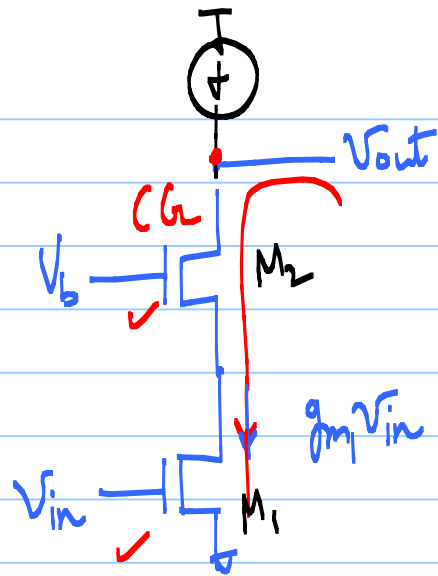


Folded-Cascode

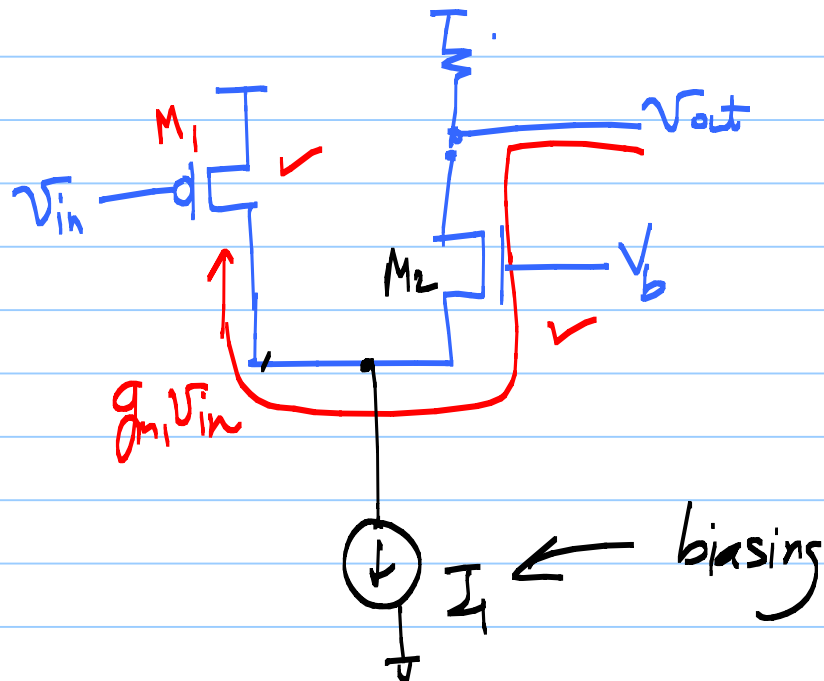

Small-signal current is folded up
 $\Rightarrow$ 2x bias current


Miller Effect :

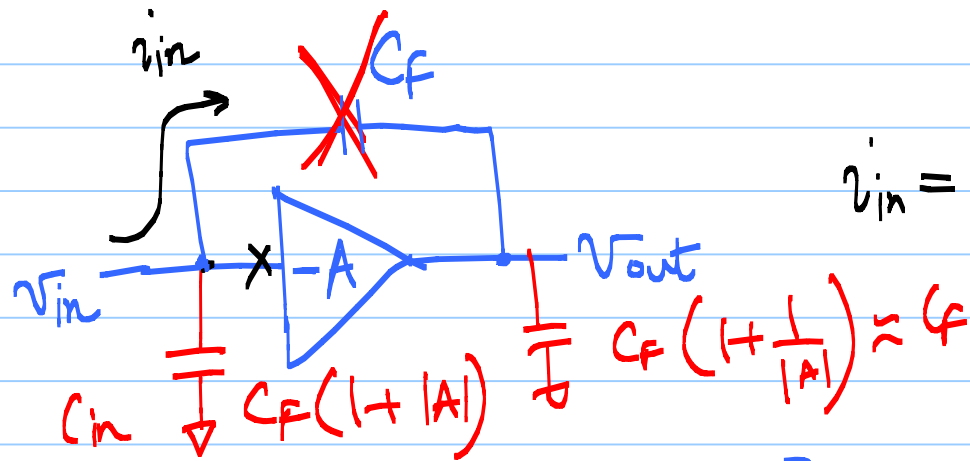

$$i_{in} = \frac{V_{in} - V_{out}}{\frac{1}{sC_f}} = sC_f(V_{in} - V_{out})$$

$$i_{in} = sC_f[V_{in} - (-|A|V_{in})] = sC_f(1 + |A|)V_{in}$$

$$\begin{aligned} i_{out} &= -i_{in} = -sC_f(V_{in} - V_{out}) \\ &= -sC_f\left(-\frac{V_{out}}{|A|} - V_{out}\right) = +sC_f\left(1 + \frac{1}{|A|}\right)V_{out} \end{aligned}$$

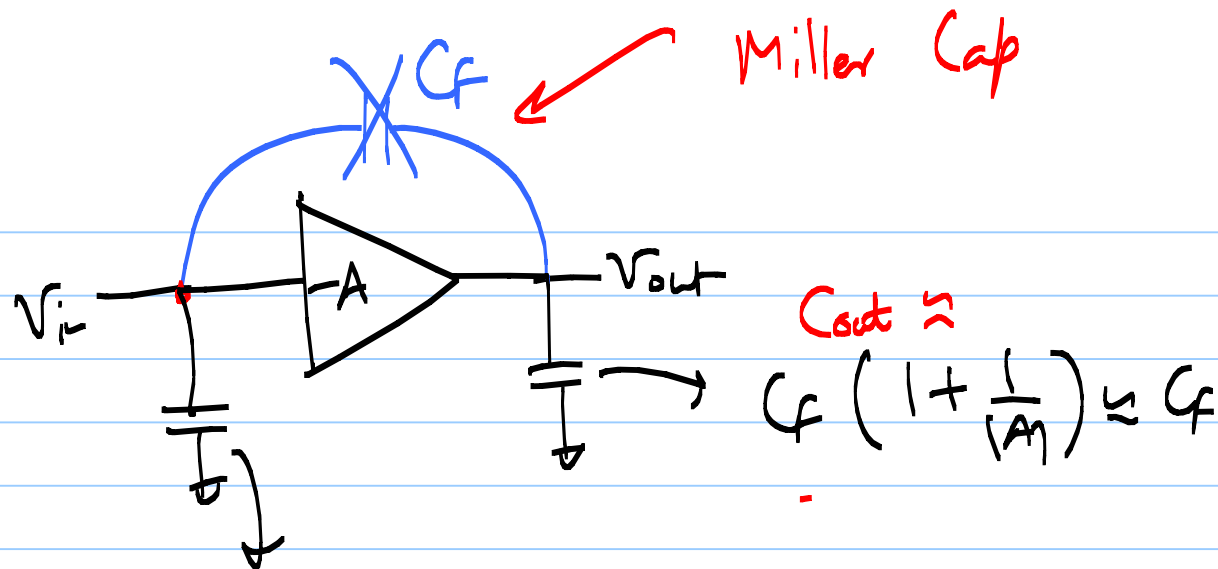

$C_{out} \approx$

$$C_f \left(1 + \frac{1}{|A|} \right) \approx C_f$$

$$C_{in} = C_f (1 + |A|)$$

$$|X_c| = \left| \frac{1}{j\omega C} \right| = \frac{1}{2\pi f C}$$

$$f \rightarrow \infty \quad |X_c| \rightarrow 0$$