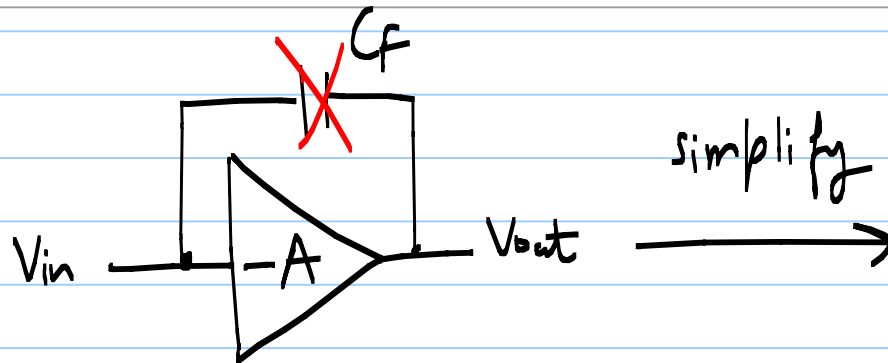


ECE 511 - Lecture 14


Note Title




3/14/2012




simplify

Miller Effect

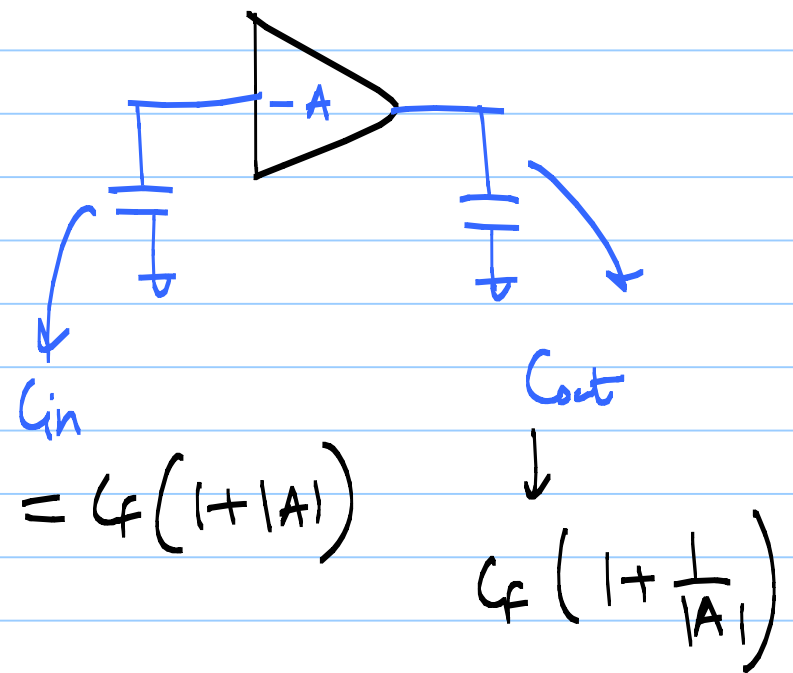


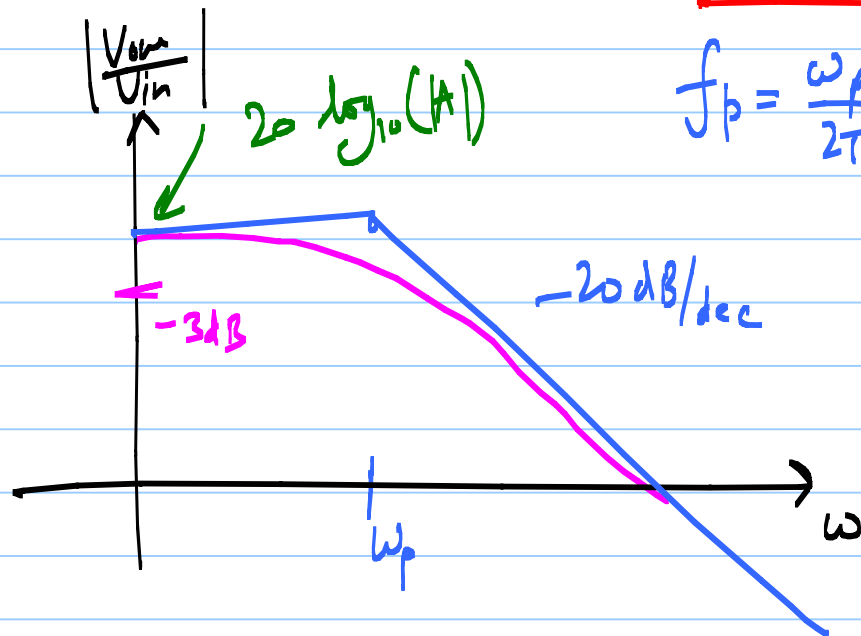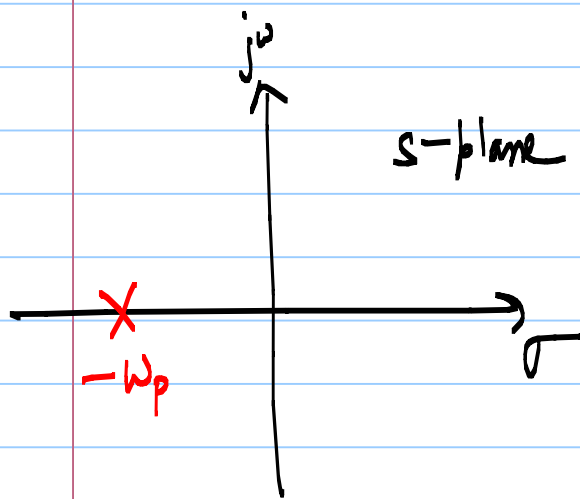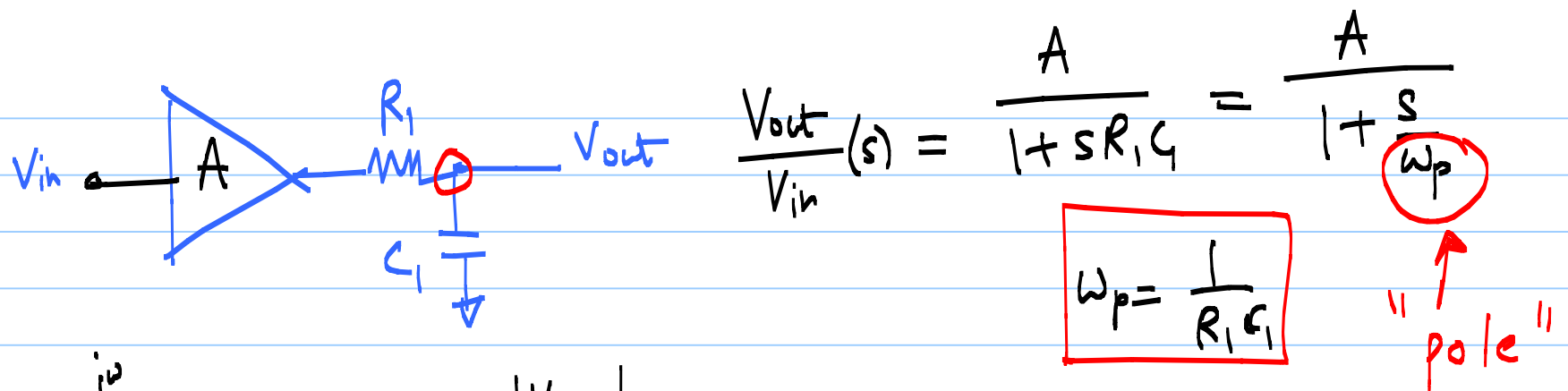

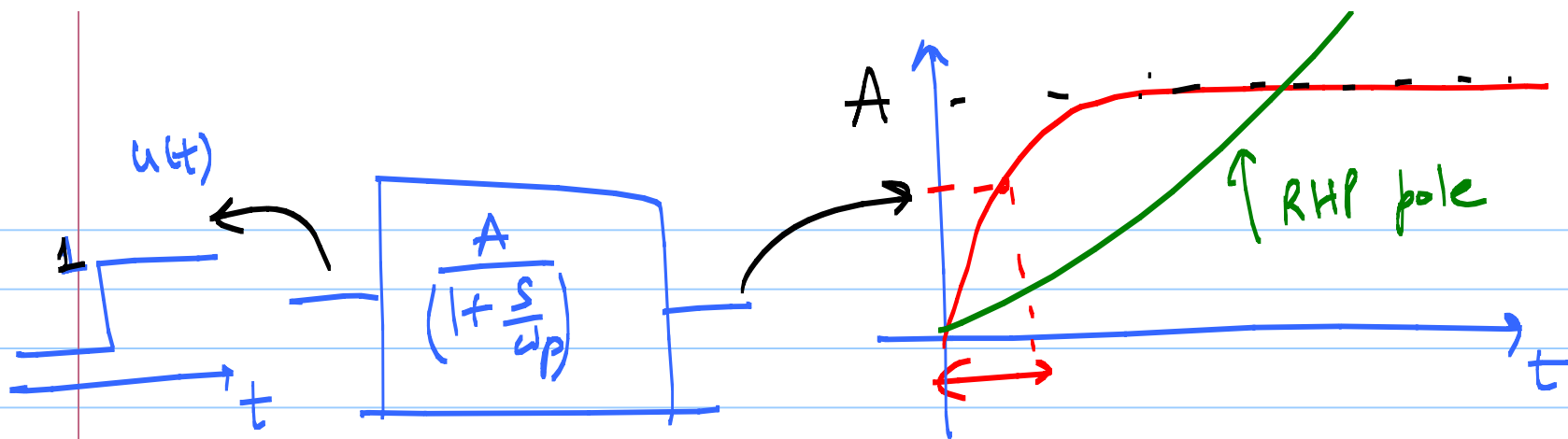
$$f_p = \frac{\omega_p}{2\pi} = \frac{1}{2\pi R_1C_1}$$



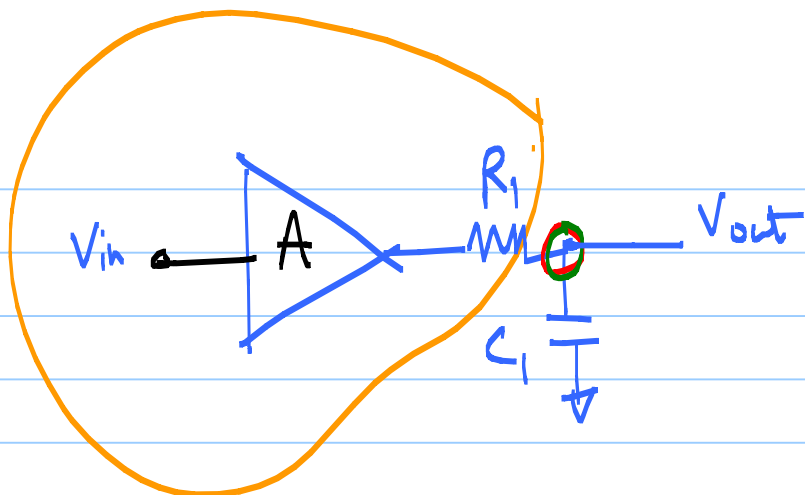
$$RC = \tau = \frac{1}{\omega_p} = \frac{1}{2\pi f_p}$$



$\Rightarrow$

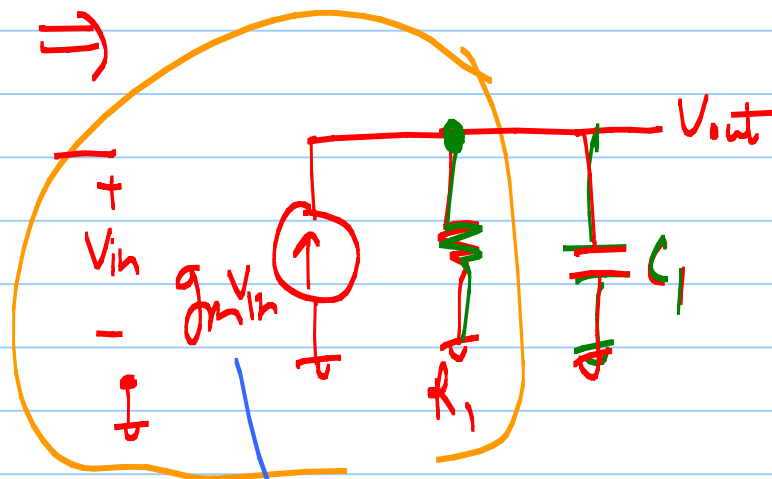

$$A = g_m R_1$$

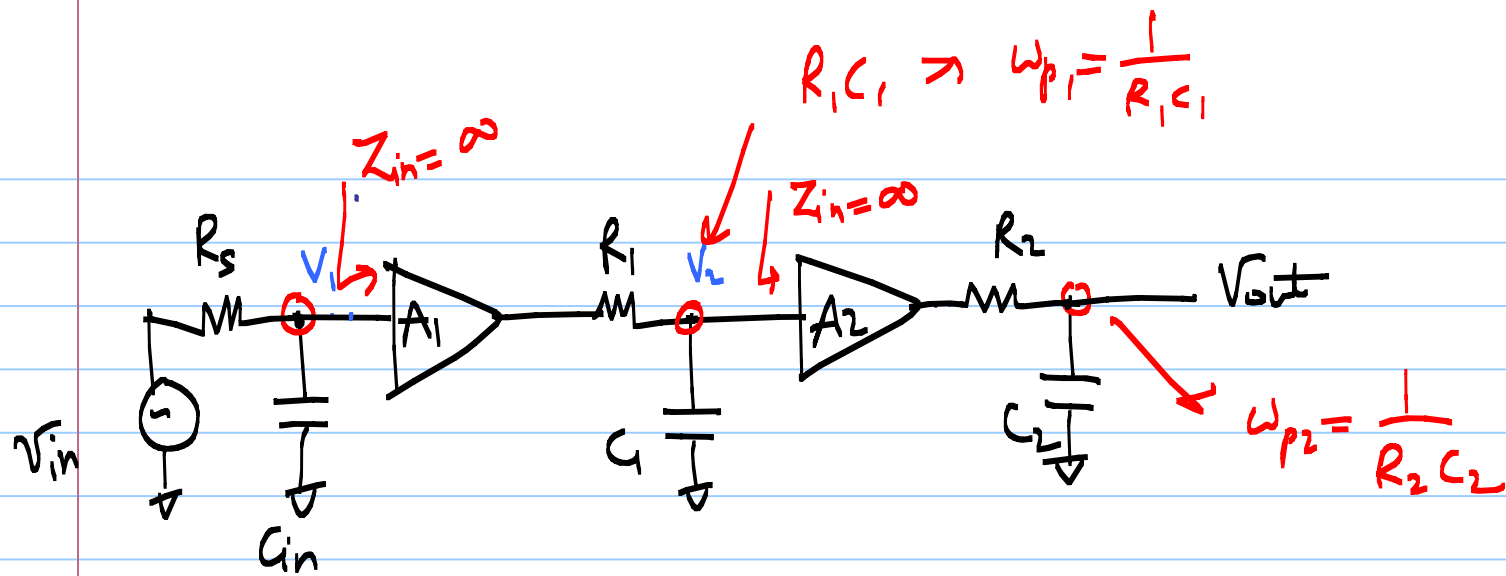


$$\frac{V_{out}}{V_{in}}(s) = \frac{1}{(1 + sR_s C_{in})} \cdot \frac{A_1}{(1 + sR_1 C_1)} \cdot \frac{A_2}{(1 + sR_2 C_2)}$$

3 poles

3 poles $\rightarrow$ determined by total cap to gnd $\times$ total R to gnd at any node

for every i^{th} node $\Rightarrow \omega_{p_i} = \frac{1}{R_i C_i} = \frac{1}{\tau_i}$
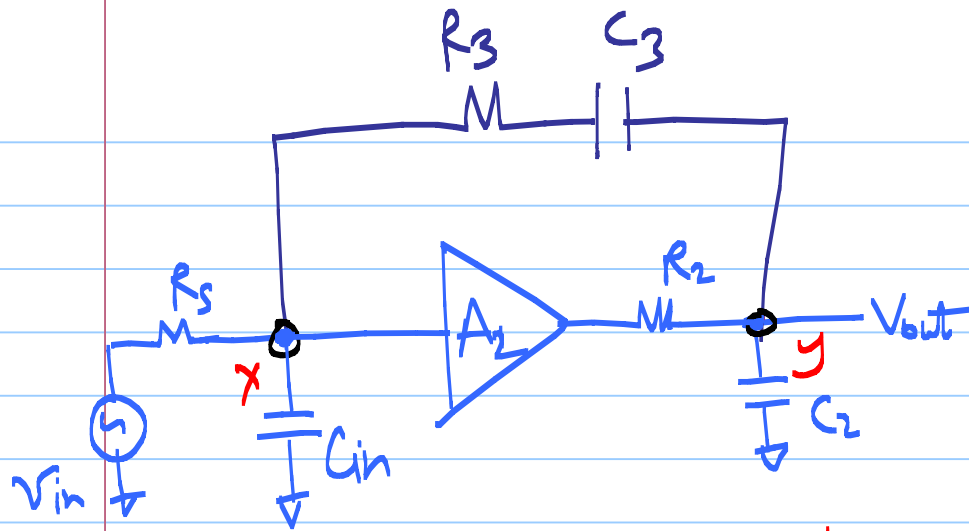
$$\text{Node}_i \Rightarrow \omega_{p_i} = \frac{1}{R_i C_i}$$





x & y are interacting thru R_2 - C_2 path

~~$$\omega_{p1} = \frac{1}{R_3 C_{in}}$$~~

~~$$\omega_{p2} = \frac{1}{R_2 C_2}$$~~

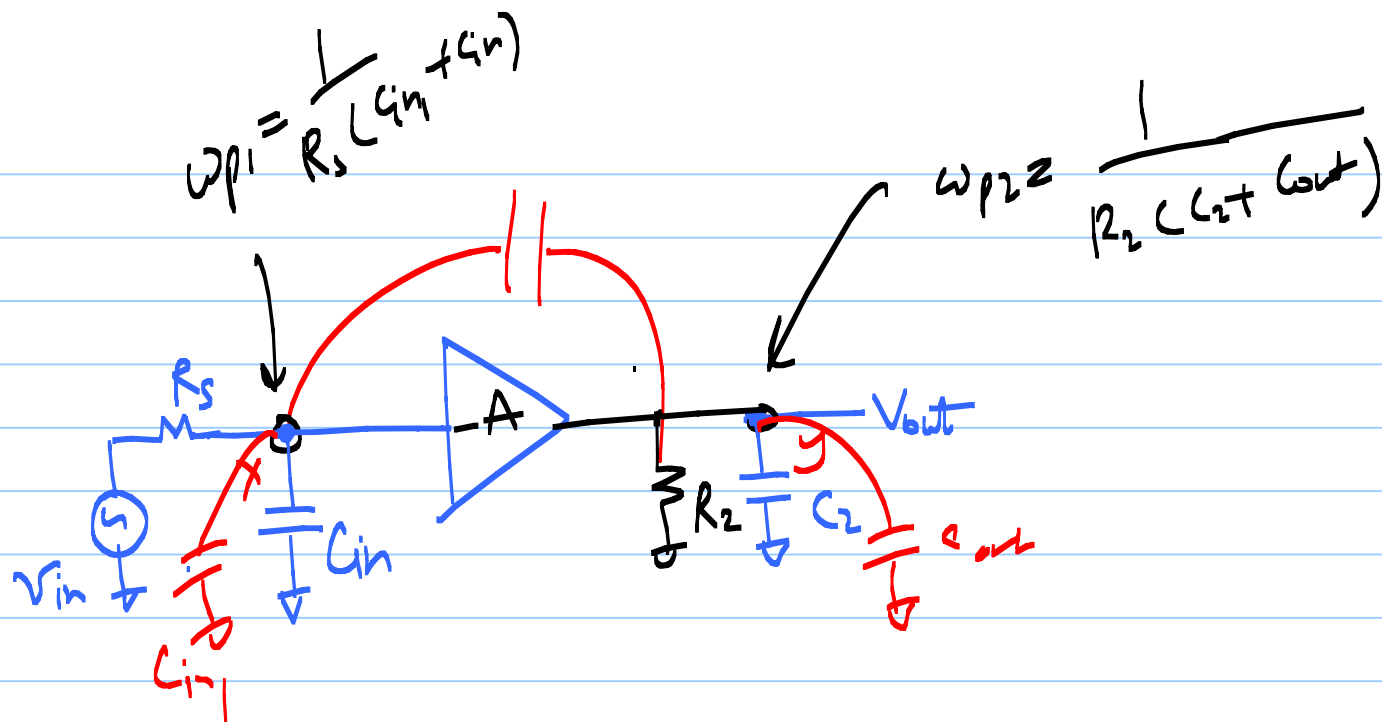* All poles are contributed by all the nodes in the circuit



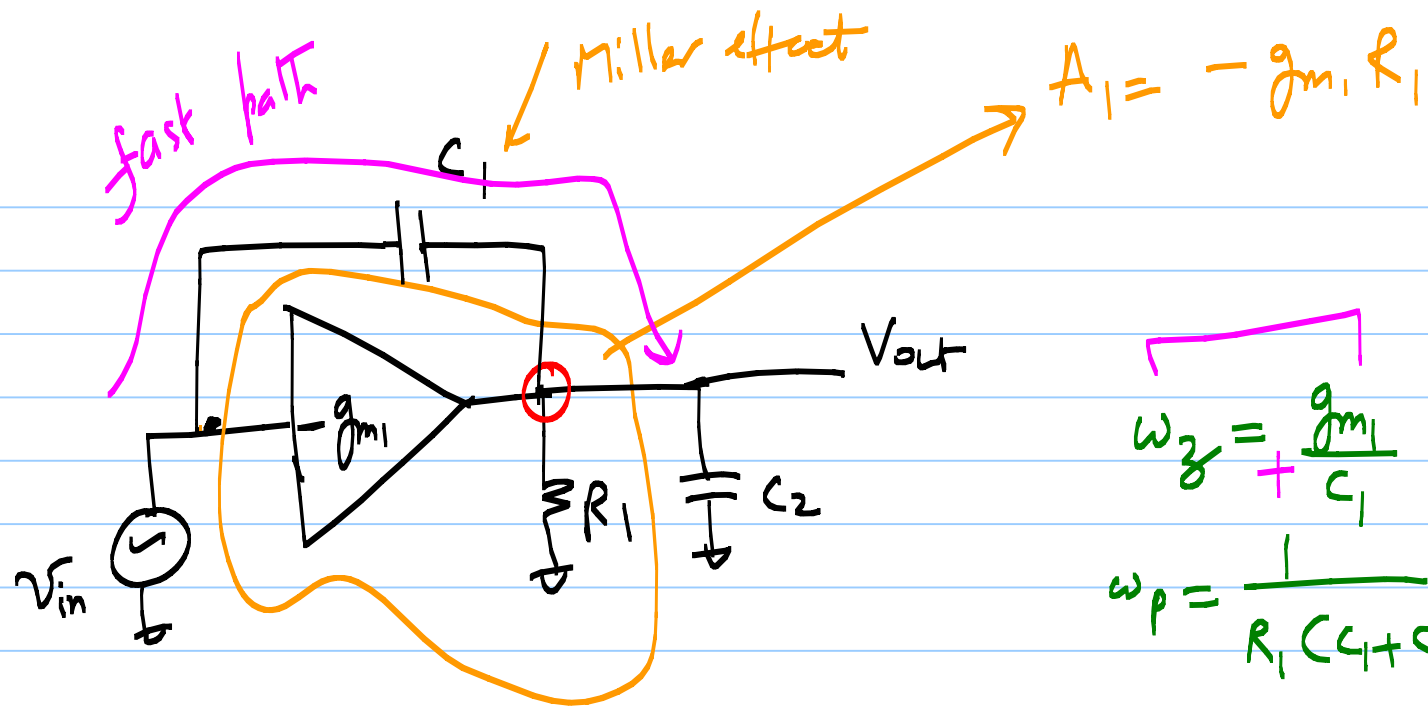

$$\omega_z = +\frac{g_{m1}}{C_1} \quad \text{RHP}$$

$$\omega_p = \frac{1}{R_1(C_1 + C_2)}$$

$$-g_{m1} V_{in} - \frac{V_{out}}{1/sC_2} - \frac{V_{out}}{R_1} - \frac{(V_{out} - V_{in})}{1/sC_1} = 0$$

$$(-g_{m1} + sC_1)v_{in} = v_{out} [1/R_1 + sC_2 + sC_1]$$

$$\Rightarrow \frac{v_{out}}{v_{in}} = - \frac{(g_{m1} - sC_1)}{1/R_1 + s(C_1 + C_2)}$$

$$= \underbrace{-g_{m1}R_1}_{A_v} \cdot \frac{\left(1 - \frac{sC_1}{g_{m1}}\right)}{(1 + sR_1(C_1 + C_2))}$$

$\swarrow \omega_z$

$\nwarrow \omega_p$




$$= \frac{A_v (1 - s/\omega_z)}{(1 + s/\omega_p)}$$

$\longleftarrow$ zero

$\longleftarrow$ pole

$$\omega_z = \frac{g_{m1}}{C_1}$$

$$\omega_p = \frac{1}{R_1(C_1 + C_2)}$$

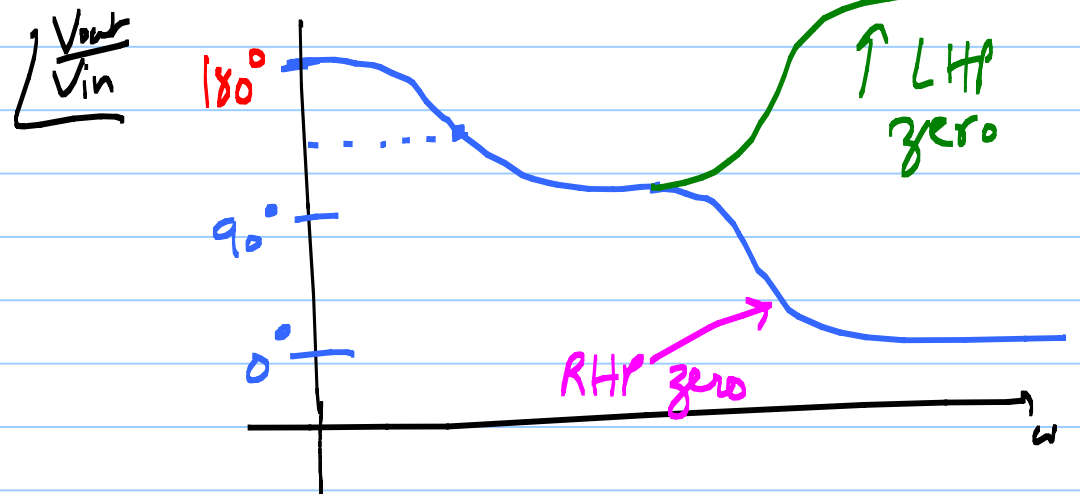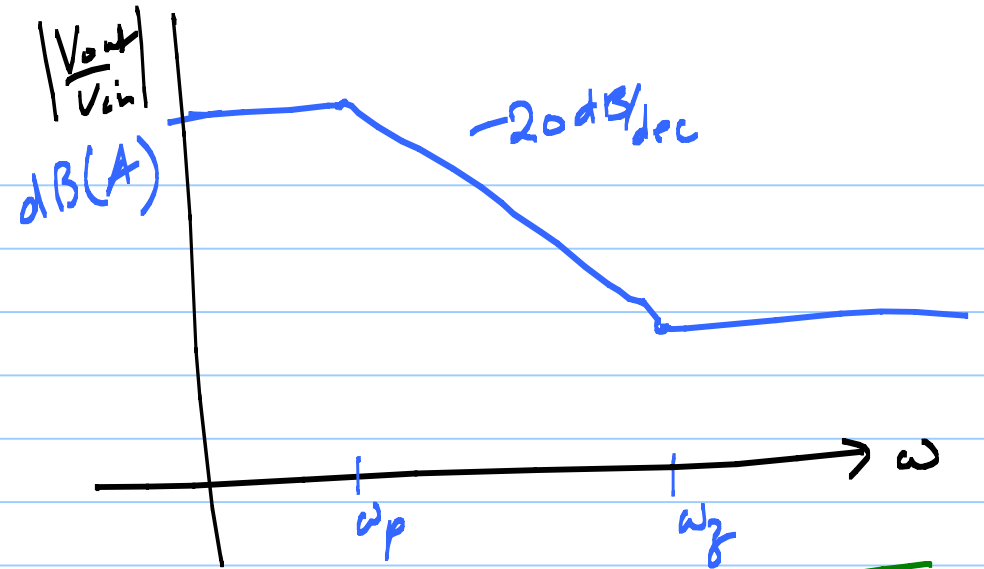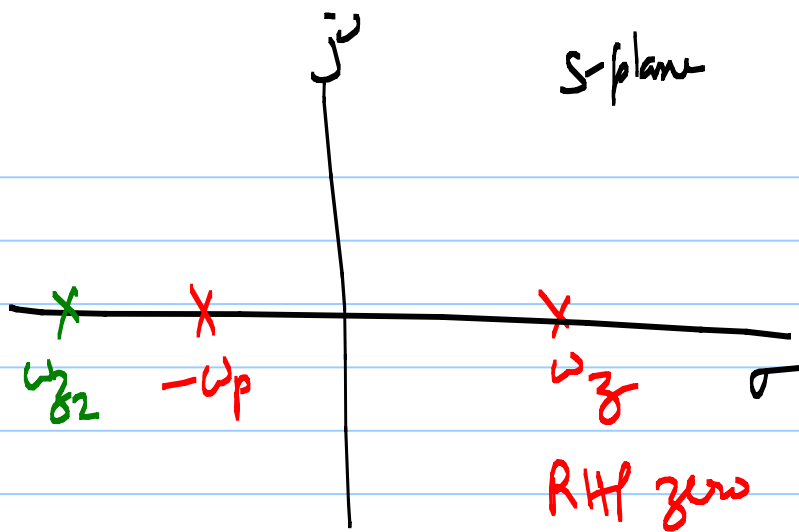

$$A_v \frac{(1 - s/\omega_z)}{(1 + s/\omega_p)}$$



$$\sum_i \tan^{-1}\left(\frac{\omega}{\omega_{zi}}\right) - \sum_j \tan^{-1}\left(\frac{\omega}{\omega_{pj}}\right)$$

$$\angle \frac{V_{out}}{V_{in}} = \tan^{-1}\left(\frac{\omega}{\omega_z}\right) - \tan^{-1}\left(\frac{\omega}{\omega_p}\right)$$


RHP zero pulls the phase down
by total of 90°

High-frequency small-signal Model


NMOS

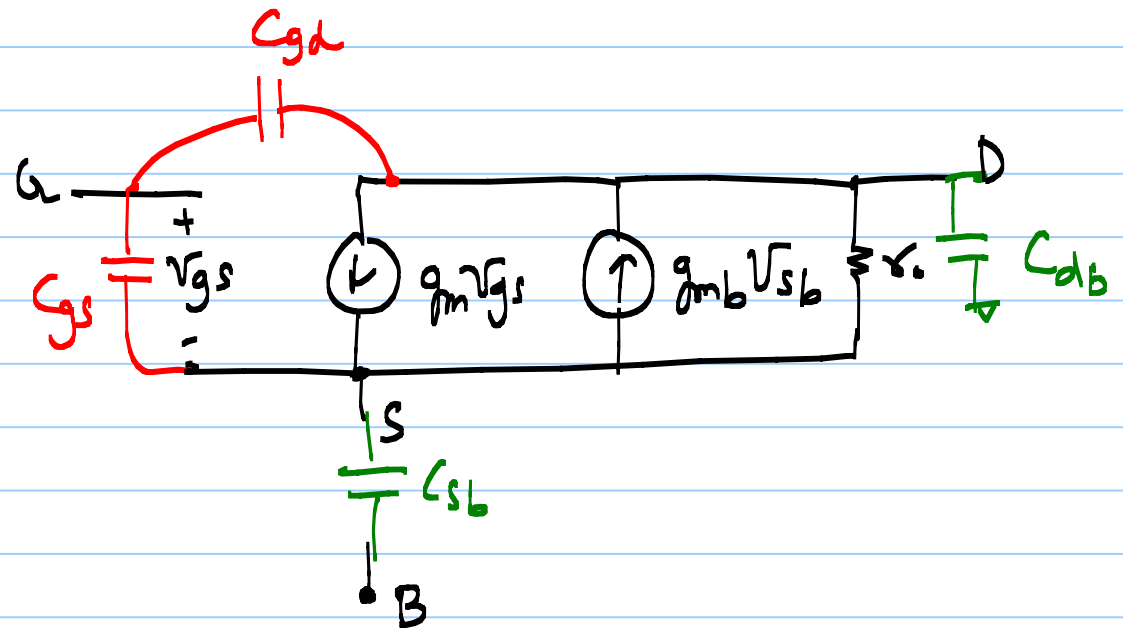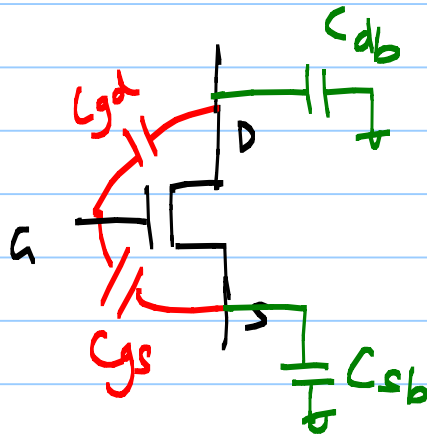

CS Stage

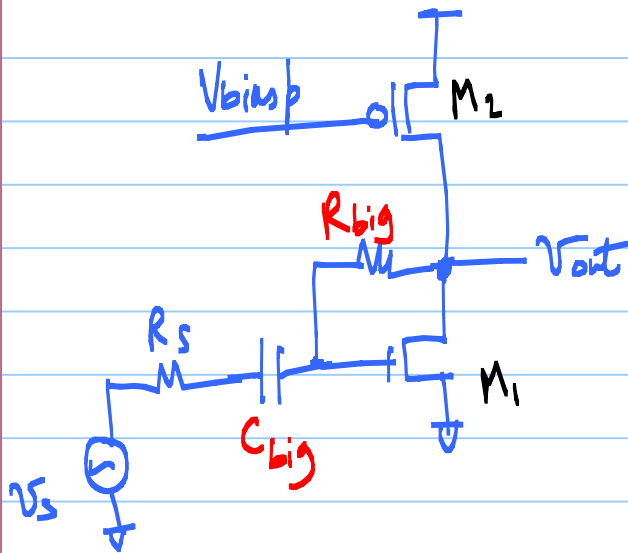

Ac picture with parasitics

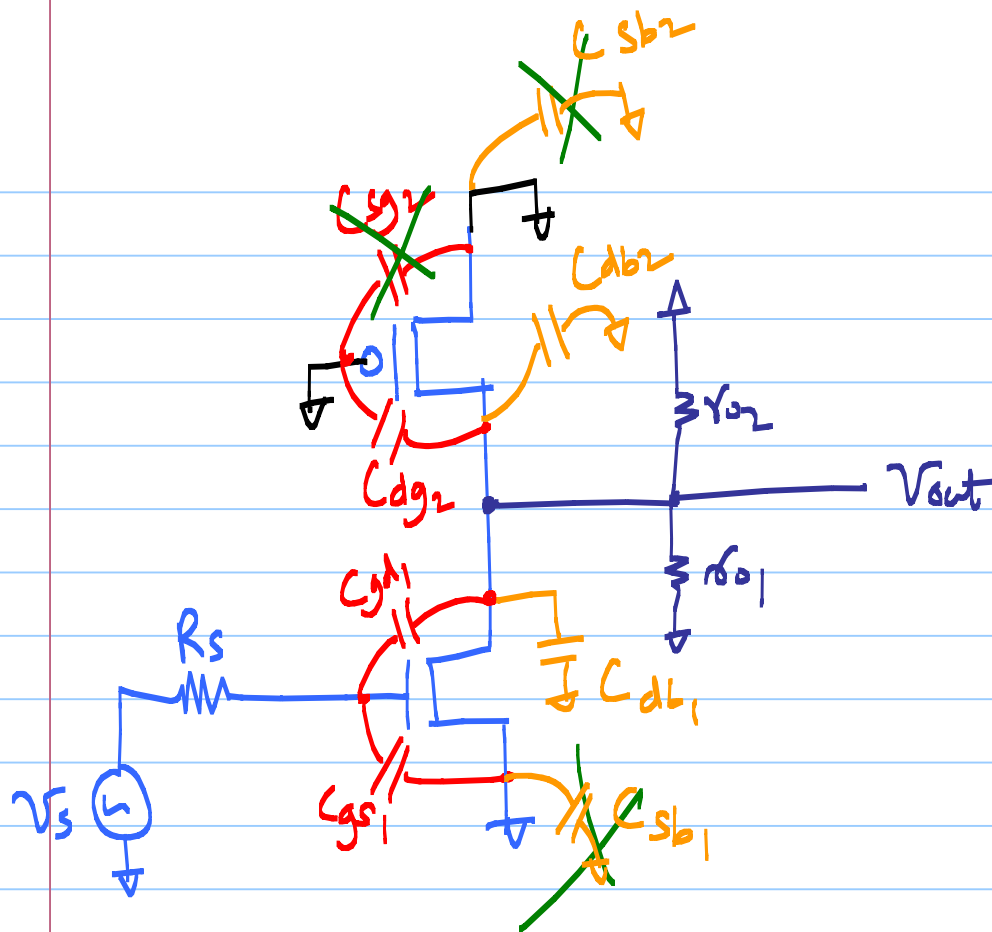

grounded caps



$C_{gs1}, C_{db1}, C_{dg2}, C_{db2}$

C_{gd1} ← between input & output

$$A_v = -g_{m1}(r_{O1} || r_{O2})$$

Let's use Miller's Theorem

(A)

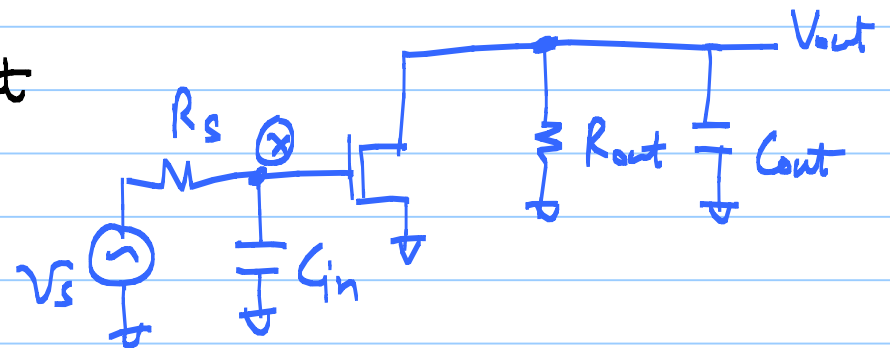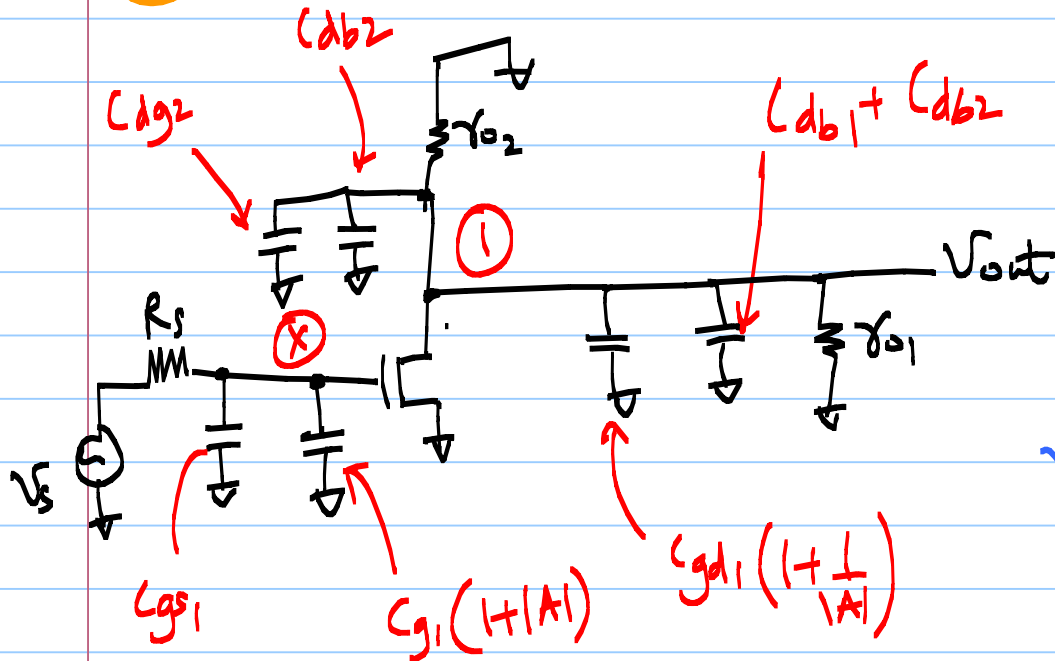

$$R_{out} = r_{o1} \parallel r_{o2}$$

$$C_{in} = C_{gs1} + C_{gd1}(1+|A|)$$

$$C_{out} = C_{gd1}\left(1+\frac{1}{|A|}\right) + (C_{db1} + C_{db2})$$

$$\rightarrow \omega_{in} = \frac{1}{R_s C_{in}} = \frac{1}{R_s [C_{gs1} + (1+|A|) C_{gd1}]} \leftarrow$$


$$\rightarrow \omega_{out} = \frac{1}{R_{out} C_{out}} = \frac{1}{(r_{o1} || r_{o2}) [C_{gd1} + C_{db}]} \leftarrow$$

$$\frac{V_{out}}{V_{in}}(s) = A_v \cdot \frac{1}{(1 + s/\omega_{in}) (1 + s/\omega_{out})}$$

$\uparrow$
 $\uparrow$

$$\rightarrow \omega_z = ??$$

(A)

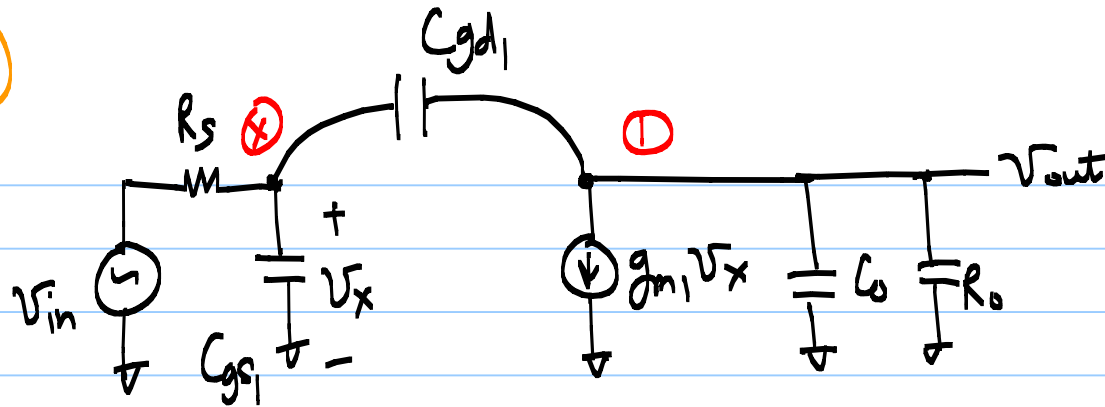

$$R_o = r_{o1} || r_{o2}$$

$$C_o = C_{db} + C_{dg2}$$

$$\frac{V_{out}}{V_{in}}(s) = ?$$

(X) $\frac{V_x - V_{in}}{R_s} + V_x C_{gs1}s + (V_x - V_{out}) C_{gd1}s = 0$ ← solve for V_x

(1) $(V_{out} - V_x) C_{gd1}s + g_{m1}V_x + V_{out} \left(\frac{1}{R_o} + C_o s \right) = 0$ ← substitute here

$$v_x = - \frac{v_{out} (C_{gd1} s + \frac{1}{R_o} + C_o s)}{(g_{m1} - s C_{gd1})}$$

$$\frac{v_{out}}{v_{in}}(s) = \frac{(C_{gd1} s - g_{m1}) R_o}{R_s R_o \xi [s^2] + [R_s (1 + g_{m1} R_o) C_{gd1} + R_s C_{gs1} + R_o (C_{gd1} + C_{db})] [s] + [1]}$$

$$\xi = C_{gs1} \cdot C_{gd1} + C_{gs1} C_o + C_{gd1} \cdot C_o$$