

ECES11 - Lecture 15

Note Title


3/19/2012

$$\frac{V_{out}}{V_{in}}(s) = \frac{(C_{gd1}s - g_{m1})R_o}{R_s R_o \zeta s^2 + [R_s(1 + g_{m1}R_o)C_{gd1} + R_s C_{gs1} + R_o(C_{gd1} + C_{d1})]s + 1}$$

$\omega_z = +\frac{g_{m1}}{C_{gd1}} \quad (R+P)$

$\zeta = C_{gs1}C_{gd1} + C_{gs1}C_o + C_{gd1}C_o$

2^{nd} order D^r

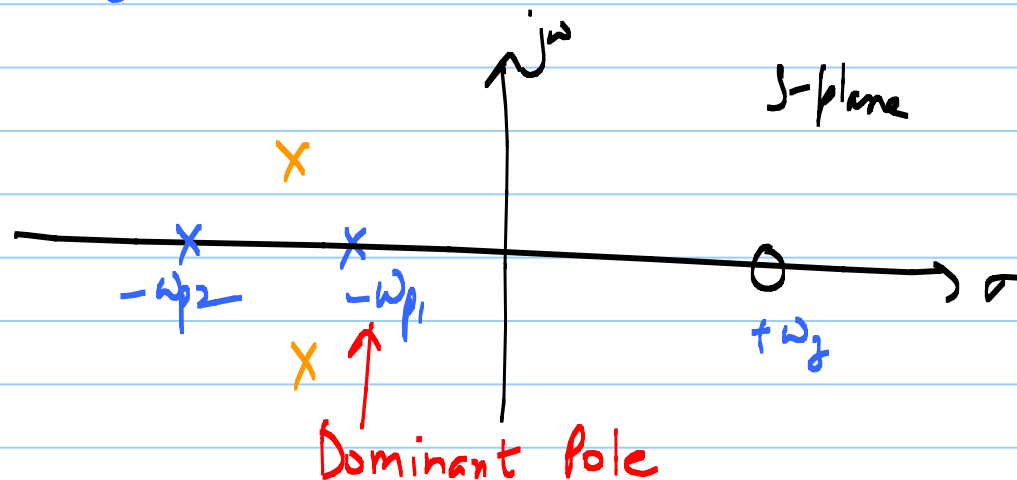

Assume

$$|\omega_{p1}| \ll |\omega_{p2}|$$

$$\Rightarrow \boxed{\frac{1}{\omega_{p1}} \gg \frac{1}{\omega_{p2}}}$$

$$D(s) = \left(\frac{s}{\omega_{p1}} + 1\right) \left(\frac{s}{\omega_{p2}} + 1\right) = \frac{s^2}{\omega_{p1}\omega_{p2}} + \underbrace{\left(\frac{1}{\omega_{p1}} + \frac{1}{\omega_{p2}}\right)}_{\text{coeff}^n \text{ of 's'} \rightarrow \frac{1}{\omega_{p1}}} s + 1$$

coeffⁿ of 's' $\rightarrow \frac{1}{\omega_{p1}}$

$$\omega_{p1} \approx \frac{1}{R_s(1 + \underline{g_{m1} R_o}) \underline{C_{gt1}} + R_s \underline{C_{gs1}} + \boxed{R_o(C_{gt1} + C_o)}} \quad \leftarrow \text{contribution from output node}$$

Compare with "Miller Analysis"

$$\omega_{in} = \frac{1}{R_s \underbrace{C_{g1}} + (1 + |A|) \underbrace{R_s C_{gd1}}}$$

$\uparrow$
 $|g_m R_o|$

Coeffⁿ of "s²"

$$\omega_{p2} = \frac{1}{\omega_{p1}} \times \frac{1}{R_s R_o \epsilon}$$

$$= \frac{1}{\omega_{p1}} \cdot \frac{1}{R_s R_o [C_{gs1} C_{gd1} + C_{gs1} C_o + C_{gd1} C_o]}$$

$$\omega_{p2} = \frac{R_s(1+g_m R_o)C_{gd1} + R_s C_{gs1} + R_o(C_{gd1} + C_o)}{R_s R_o [C_{gs1} C_{gd1} + C_{gs1} C_o + C_{gd1} C_o]}$$

Let $C_{gs1} \gg (1+g_m R_o)C_{gd1} + \frac{R_o}{R_s}(C_{gd1} + C_o)$

$$\omega_{p2} \approx \frac{1}{\underline{R_o}(\underline{C_{gd1}} + \underline{C_o})}$$


Same as in Miller analysis

only valid when C_{gs} dominates the input cap

"Zero"


$$\omega_z = + \frac{g_{m1}}{C_{gd1}} \Rightarrow (RHP)$$

$$(V_{GS1} - V_{out}) s C_{gd1}$$

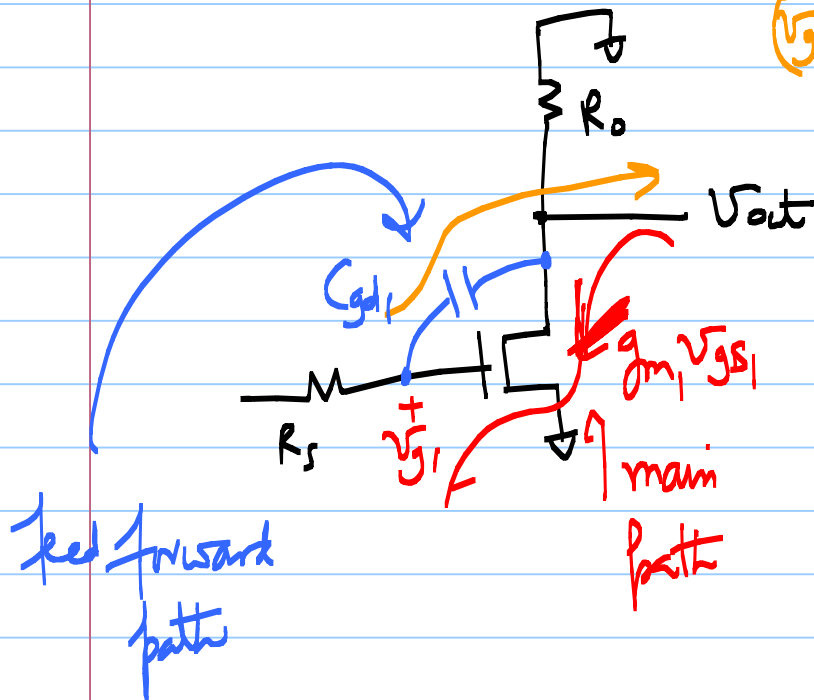

* Feedforward path causes gain filtering by $+20 \text{ dB/dec}$

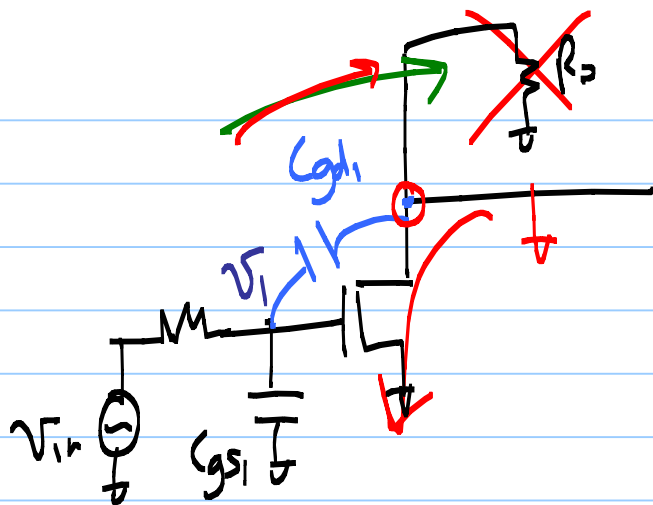* RHP zero reduces phase @ high-f
 $\therefore$ signal through C_{gd1} adds in opposite phase to $g_m V_{GS1}$.



V_{out}

@ $S = S_z$

$\Rightarrow V_{out}(S_z) = 0$

$\Rightarrow$

$$V_1 \cdot S_z C_{gd1} + (-g_{m1} V_1) = 0$$

$\Rightarrow$

$$S_z \cdot C_{gd1} = g_{m1}$$

$\Rightarrow$

$$S_z = \frac{g_{m1}}{C_{gd1}}$$


RHP zero.

$$A(s) = A_v \cdot \frac{(1 - s/\omega_z)}{(1 + \frac{s}{\omega_{p1}})(1 + s/\omega_{p2})}$$

① $\omega_z = + \frac{g_{m1}}{C_c}$

② $\omega_{p1} = \frac{1}{R_s [(1 + |A|C_c) + C_{gs1}] + R_o (C_c + C_o)}$

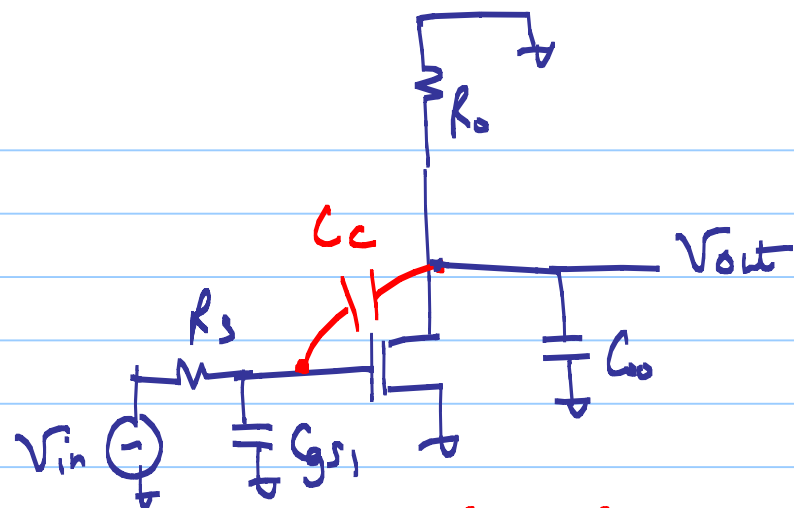③ $\omega_{p2} = \frac{R_s (1 + g_{m1} R_o) C_c + R_s C_{gs1} + R_o (C_c + C_o)}{R_s R_o [C_{gs1} C_c + C_{gs1} C_o + C_c C_o]}$




$C_c = C_{gd1}$
"Miller Cap"

Case I: $C_c \approx 0$ & C_o is large

$$\omega_{p1} \approx \frac{1}{R_s C_{gs1} + \underline{R_o C_o}} \quad \leftarrow$$

$$\omega_{p2} \approx \frac{1}{\underline{R_o C_o}}$$

$$\omega_z \Rightarrow \infty$$

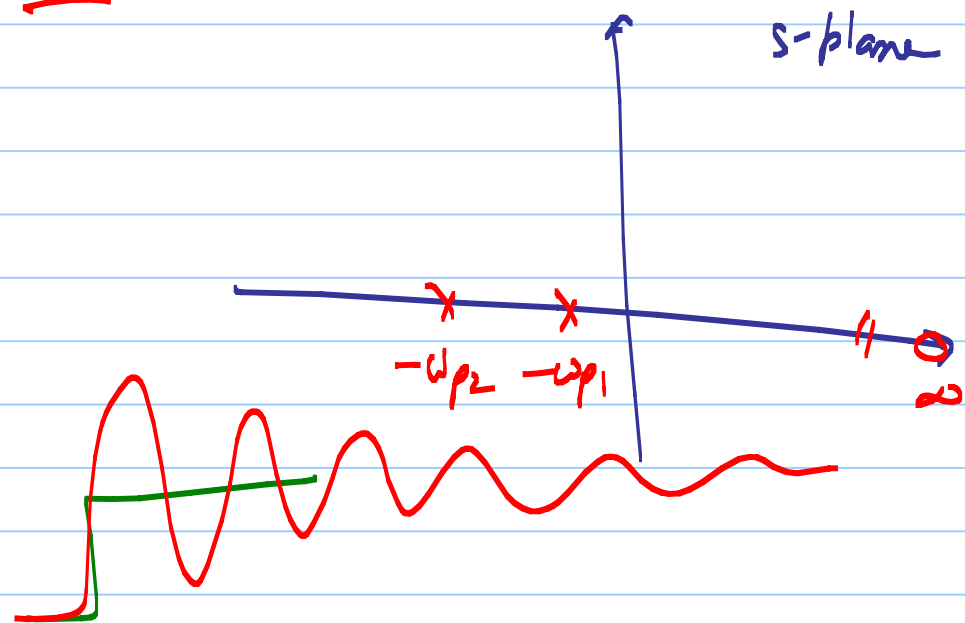


✗ increase C_c

$$\Rightarrow \underline{C_c \gg C_{gs1}}$$

$$\omega_{p1} \approx \frac{1}{R_S (1 + |A_v|) C_c + R_o (C_c + C_o)} \quad \leftarrow$$

$$\omega_{p2} \approx \frac{\cancel{R_S} (1 + \cancel{g_{m1} R_o}) \cancel{C_c} + \cancel{R_o} (\cancel{C_c} + C_o)}{\cancel{R_S R_o} \cancel{C_c} [C_o + C_{gs1}]}$$
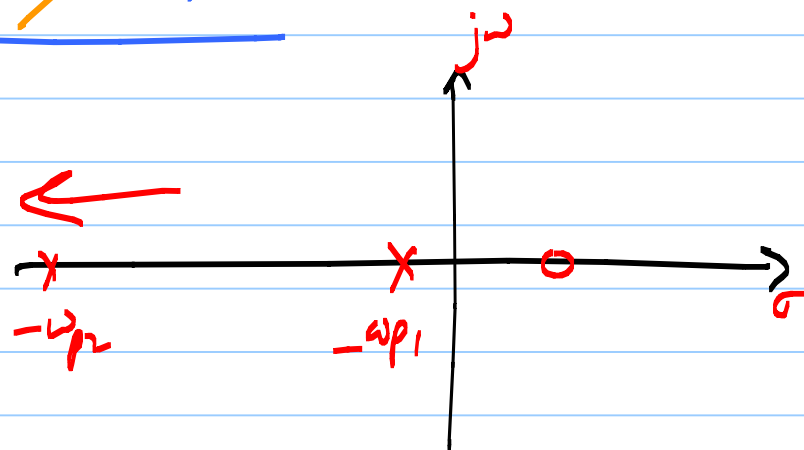
$$\approx \boxed{\frac{g_{m1}}{C_o + C_{gs1}}}$$



$$C_c = 0$$

ω_{p1}

$$\approx \frac{1}{R_s C_{gs1} + R_o C_o}$$

ω_{p2}

$$\approx \left(\frac{1}{R_o C_o} \right)$$

ω_z

$$\frac{g_{m1}}{C_{gs1}}$$


$$C_c \gg C_{gs1}$$

$$\approx \frac{1}{R_s (1 + |A|) C_c + R_o (C_c + C_o)}$$

ω_{p1} is smaller


$$\approx \frac{g_{m1}}{C_o + C_{gs1}} \approx \frac{g_{m1}}{C_o} = \underbrace{(g_{m1} R_o)}_{\text{gain}} \left[\left(\frac{1}{R_o C_o} \right) \right]$$

$$\frac{g_{m1}}{C_c}$$

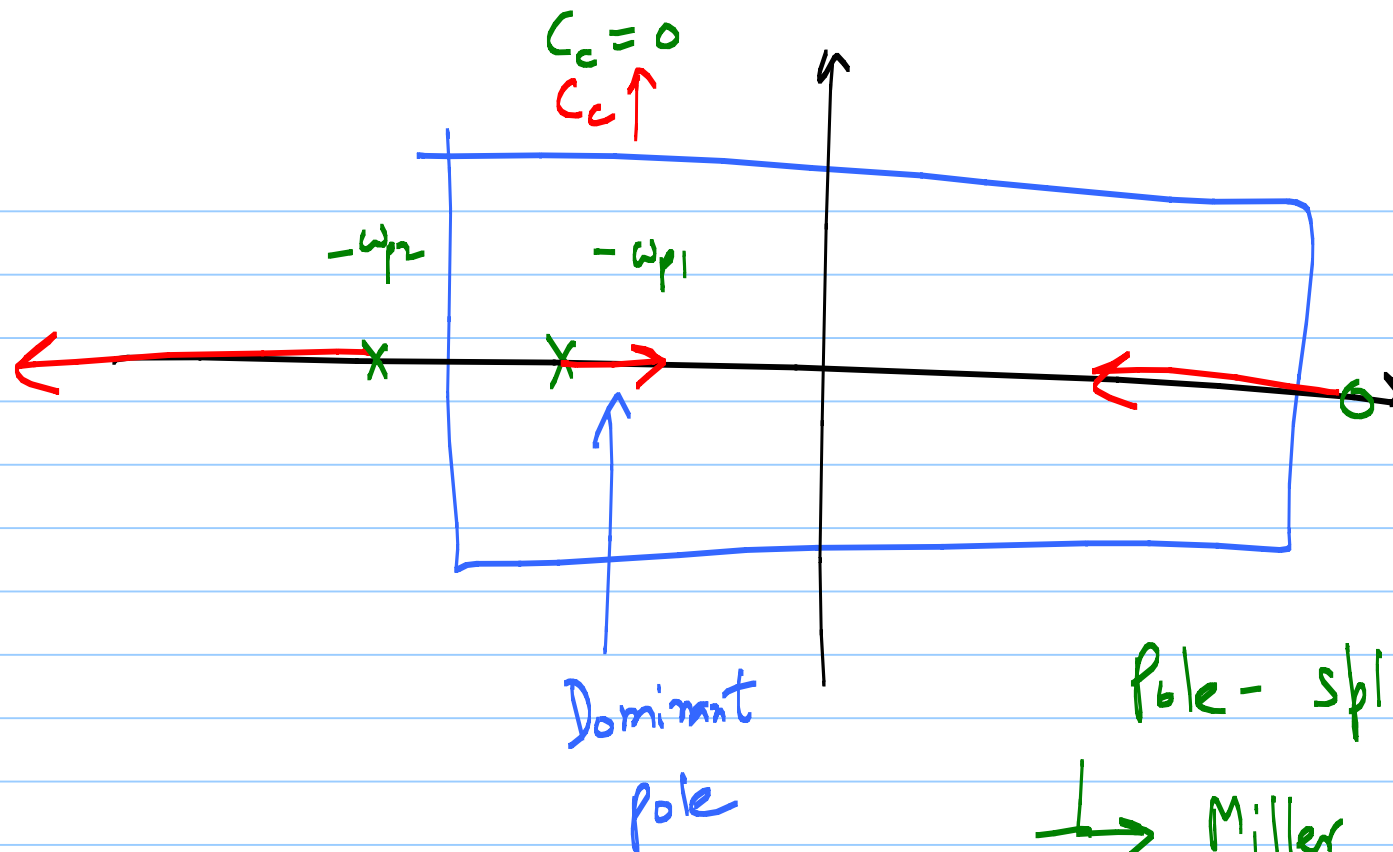


Pole-splitting
→ Miller Compensation
→ stabilize two-pole
amplifier

* Explanation for ω_{p2}

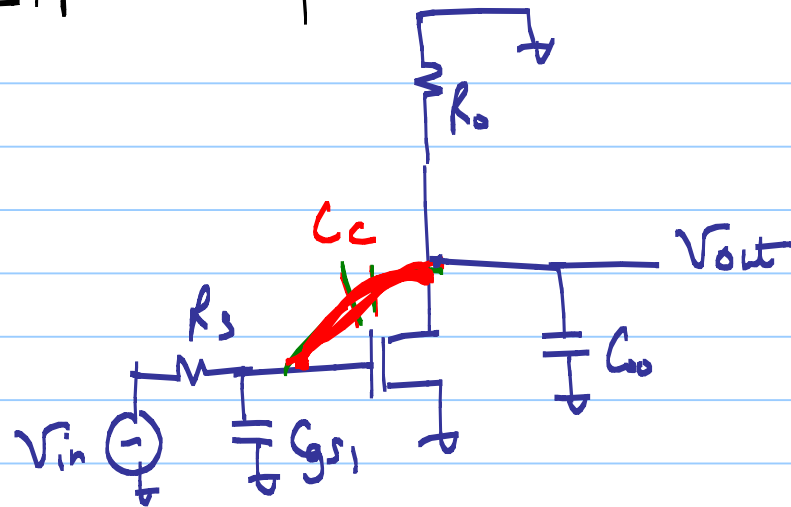

@ very high frequency

$$\omega \geq \omega_{p2}$$

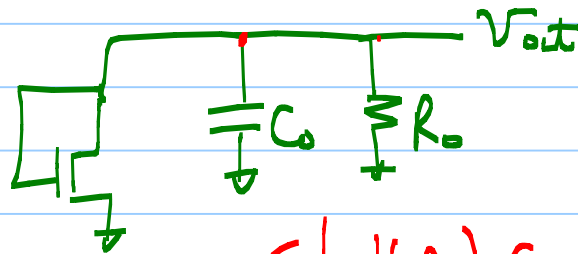


$$Z_{out} = \left(\frac{1}{g_{m1}} \parallel R_o \right) C_o \approx \frac{C_o}{g_{m1}}$$

$$\Rightarrow \omega_{p2} \approx \frac{g_{m1}}{C_o}$$

pole splitting Summary

generic model for "2nd order" amplifier.

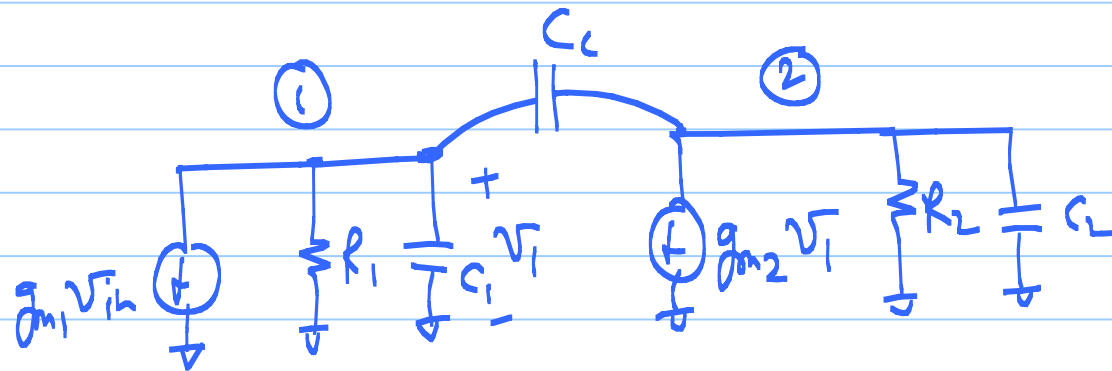

$$A(s) = A_v \frac{(1 - s/\omega_z)}{(1 + s/\omega_{p1})(1 + s/\omega_{p2})}$$

$$A_v = g_{m1} R_1 \cdot g_{m2} R_2$$

$$\omega_{p1} \approx \frac{1}{R_2 (C_c + C_2) + R_1 (C_1 + C_c (1 + g_{m2} R_2))} \approx \frac{1}{g_{m2} R_2 R_1 C_c}$$

$$\omega_{p2} \approx \frac{g_{m2} C_c}{C_c C_1 + C_1 C_2 + C_c C_2} \propto \frac{g_{m2}}{C_2} \quad \text{for } C_c \approx C_2 \gg C_1$$

$$\omega_{un} = \frac{g_{m1}}{C_c} \quad \text{or unity-gain frequency}$$

$$A(s) = \frac{A_v (1 - s/\omega_z)}{(1 + s/\omega_{p1})(1 + s/\omega_{p2})}$$


$$A(s) \approx \frac{A_v}{(1 + s/\omega_{p1})}$$

Compensated

$$\omega_{p1} \ll \omega_{p2}$$

↑ dominant pole response

$$\omega_z \rightarrow \infty$$

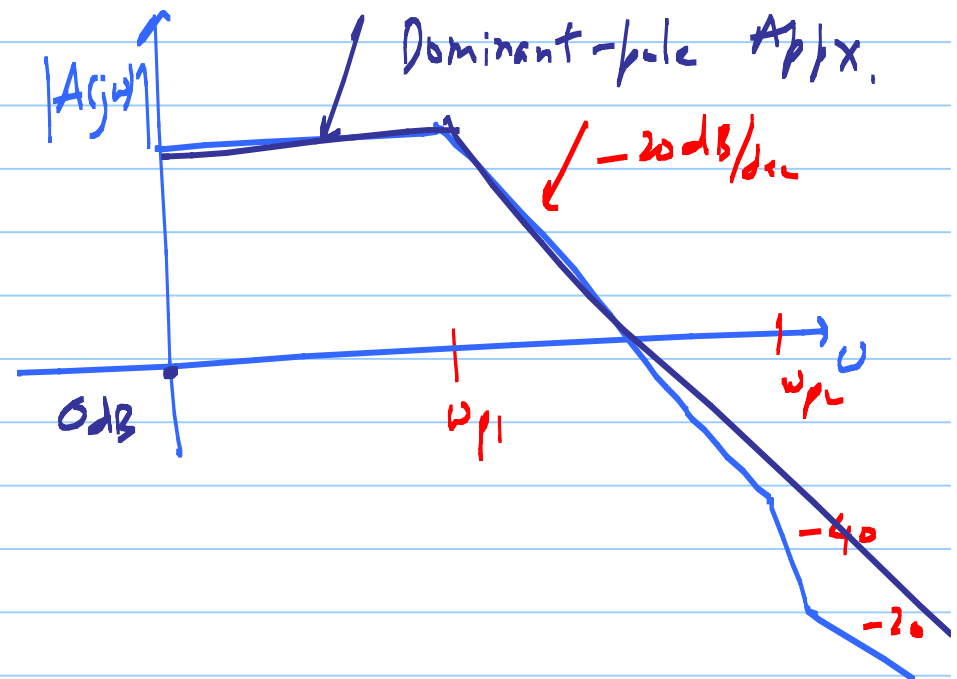

$$A(s) = \frac{A_v}{(1 + s/\omega_{p1})}$$

$$\omega_{p1} \Rightarrow \omega_{3dB}$$

$$\approx \frac{A_v}{1 + s/\omega_{3dB}}$$

$\swarrow$ DC gain
 $\nwarrow$ 3dB-BW

$$A_v = \overbrace{g_{m1} R_1} \overbrace{g_{m2} R_2}$$

$$\omega_{3dB} = \frac{1}{g_{m2} R_2 R_1 C_c} \Rightarrow f_{3dB} = \frac{\omega_{3dB}}{2\pi} = \frac{1}{2\pi g_{m2} R_2 R_1 C_c}$$


$$A_v \cdot \omega_{3dB} = \frac{g_{m1}}{C_c}$$

for $\omega \gg \omega_{3dB}$


$$\frac{A_v}{1 + s/\omega_{3dB}}$$

$$\approx \frac{A_v}{s/\omega_{3dB}} = \frac{A_v \omega_{3dB}}{s} = \frac{\omega_{um}}{s}$$

$$\omega_{um} = \frac{g_{m1}}{C_c}$$

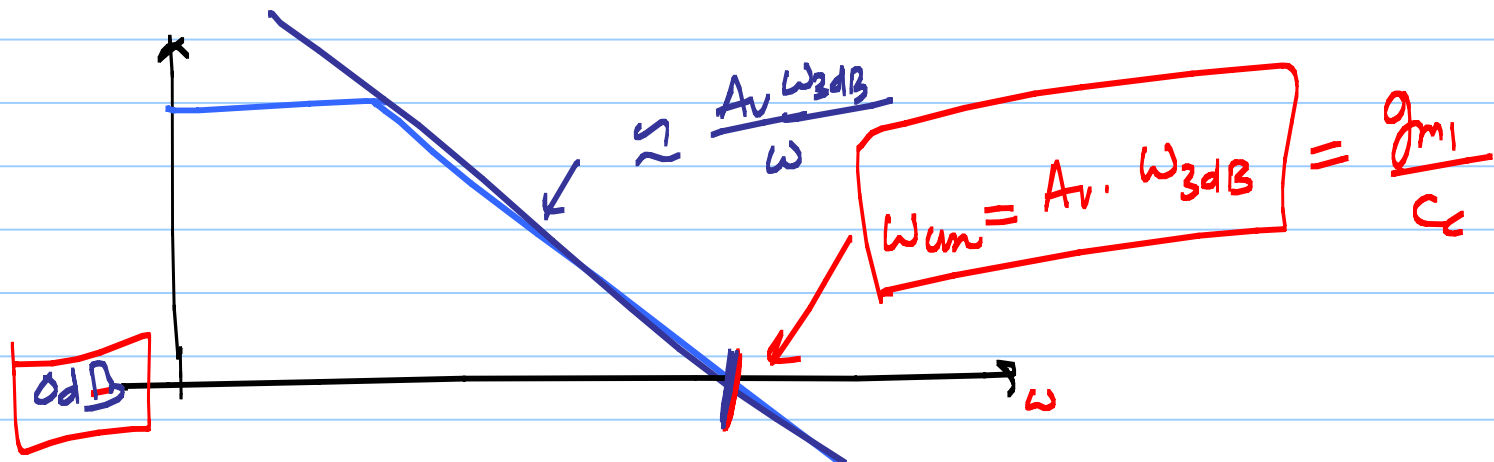

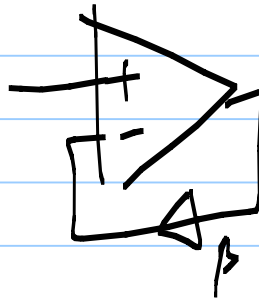constant
↓
 ω_{um} = $A_v \cdot \omega_{3dB}$ ← Gain-BW trade-off for the amplifier



$\omega_{p2} \gg \omega_{um}$ ← ω_{p1} ← dominant pole response

