
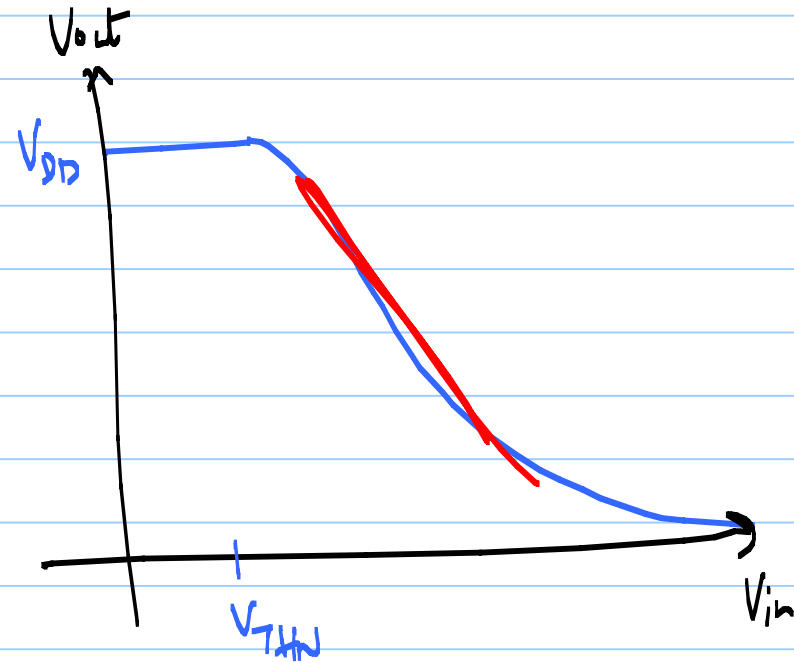


ECE 511 - Lecture 17




Note Title


4/2/2012

CS Amplifier:

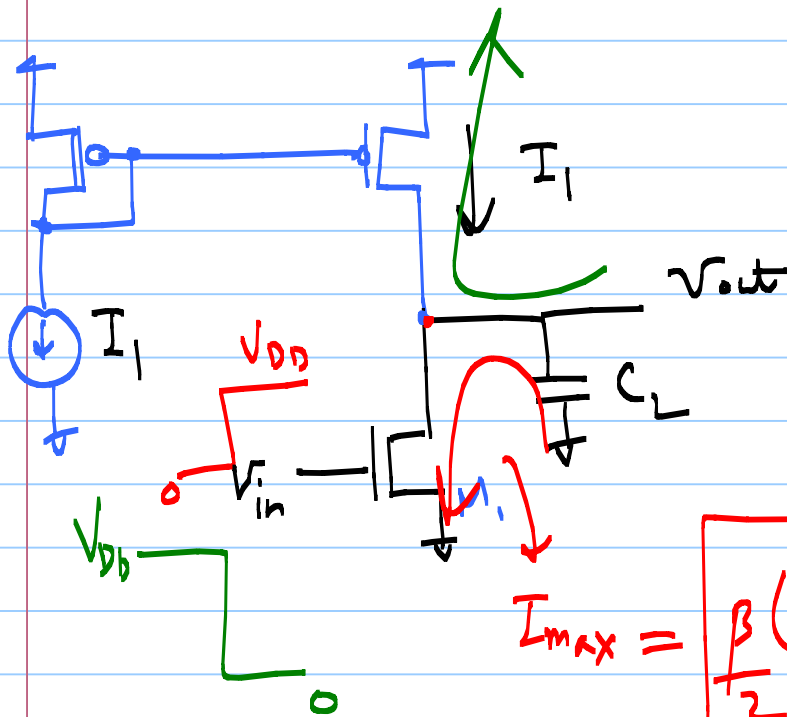

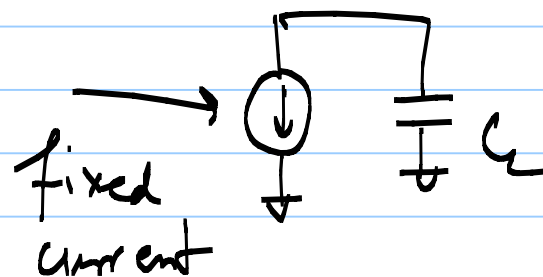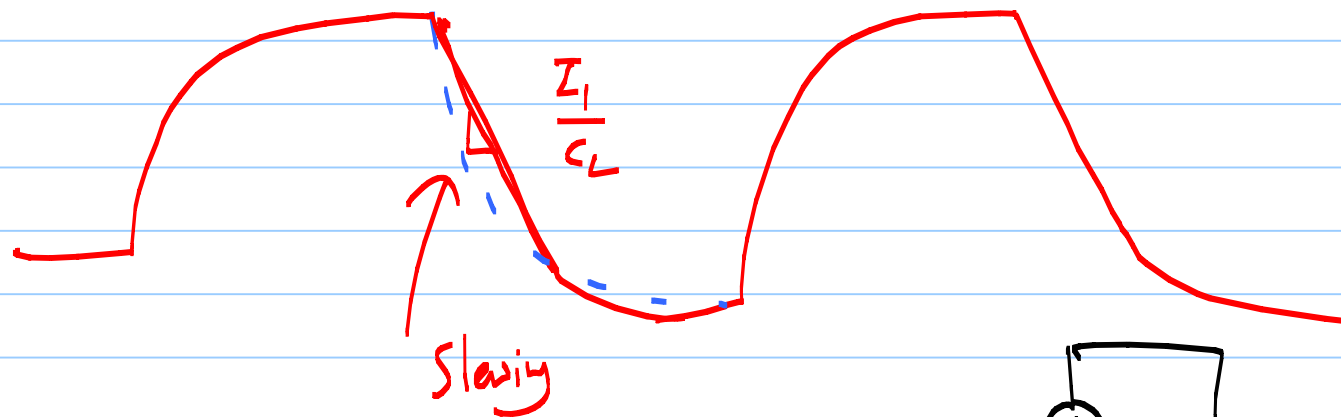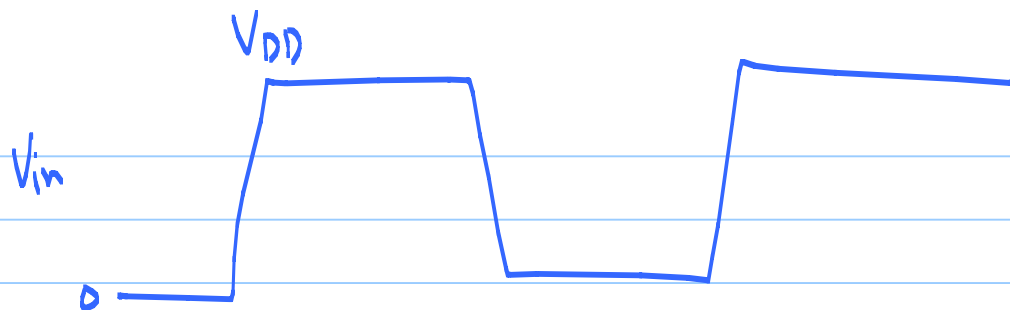
$$I_{max} = \frac{\beta (V_{DD} - V_{THN})^2}{2}$$



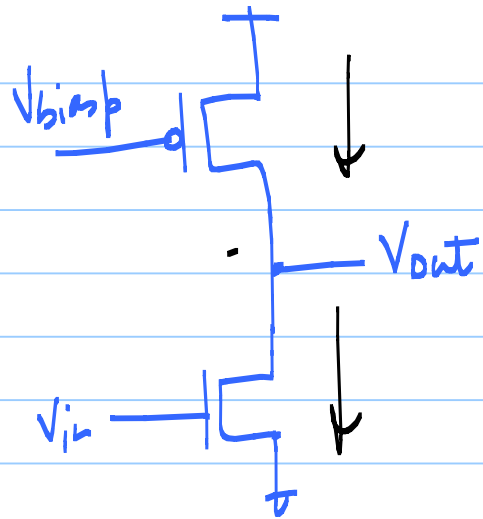

Class-A
stage

* both conduct at the same
time

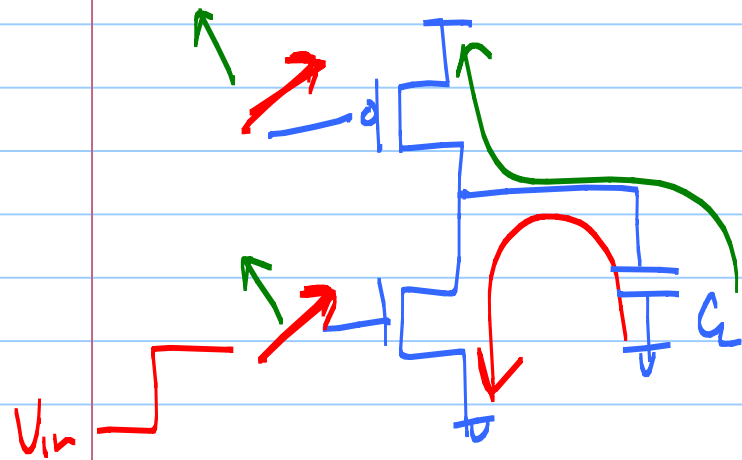


Class AB stage

Smooth transition from
one device to another

↳ output stage of an amplifier

* In class B → only one device is on at a time

Floating Current Mirror

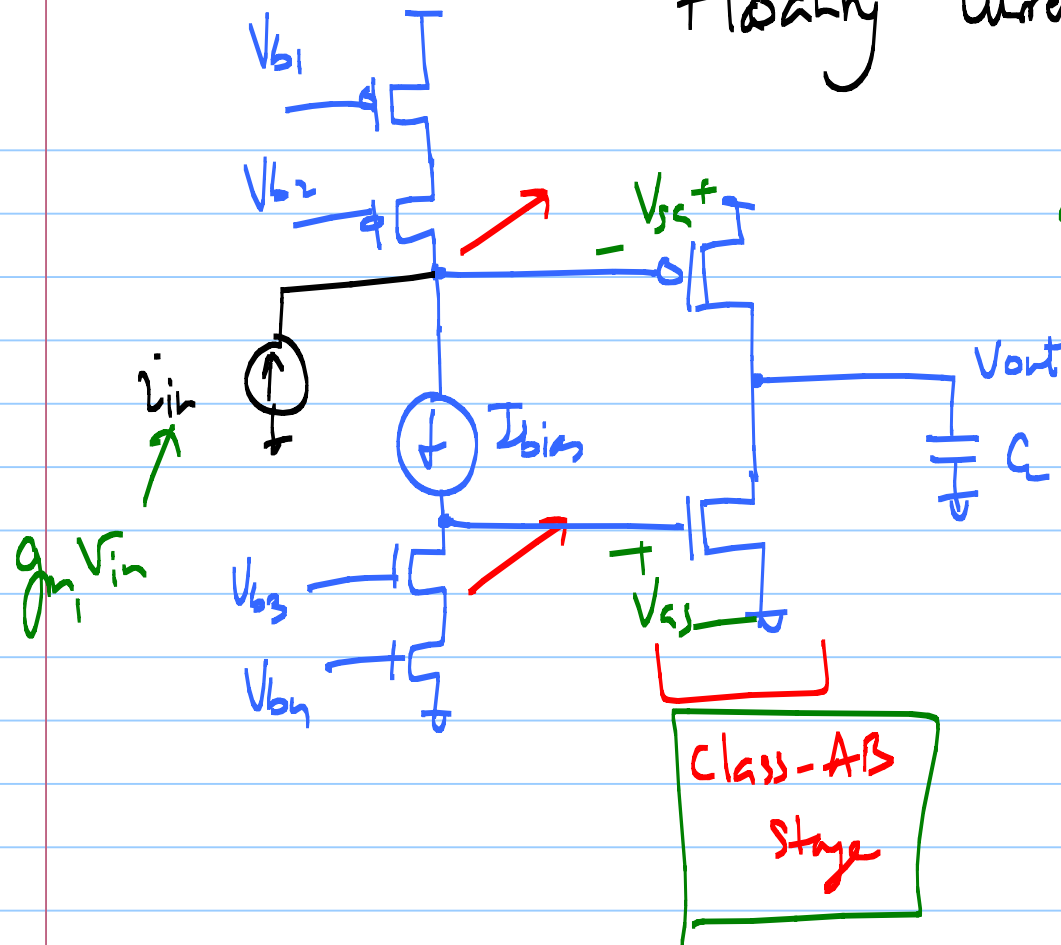


← Chapter 20

← o/p stage for an opamp.


Chapter 22 - Differential Amplifiers

* Single-ended signal

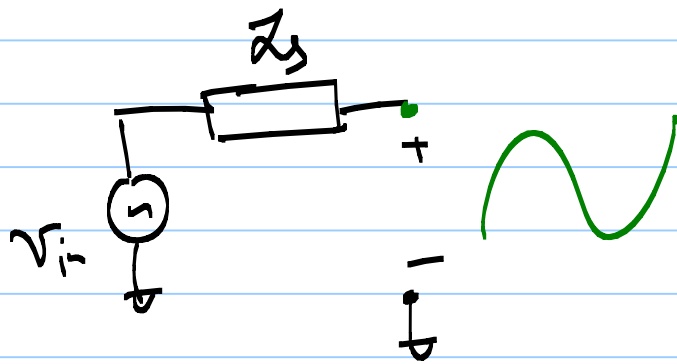


one wire wrt the ground.

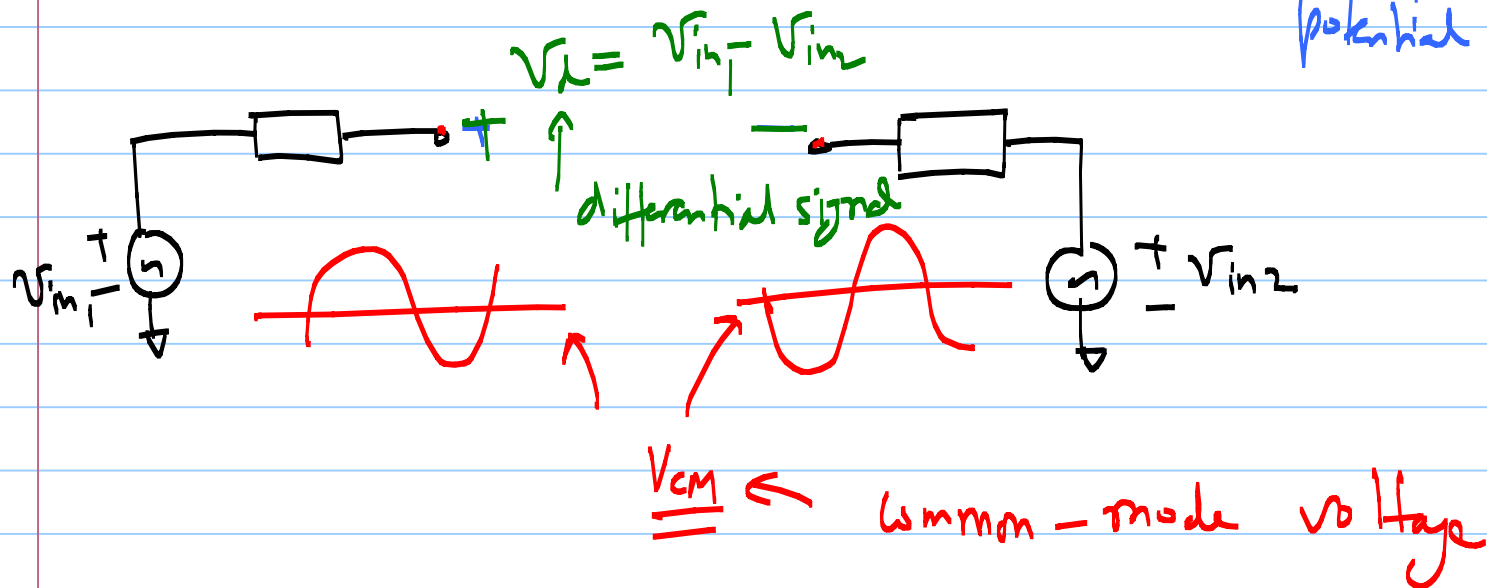
* Differential signal $\rightarrow$ measured b/w 2 nodes, which have equal and opposite signal excursions around a fixed potential



$$V_d = V_{in1} - V_{in2} \quad \leftarrow \text{DM signal}$$

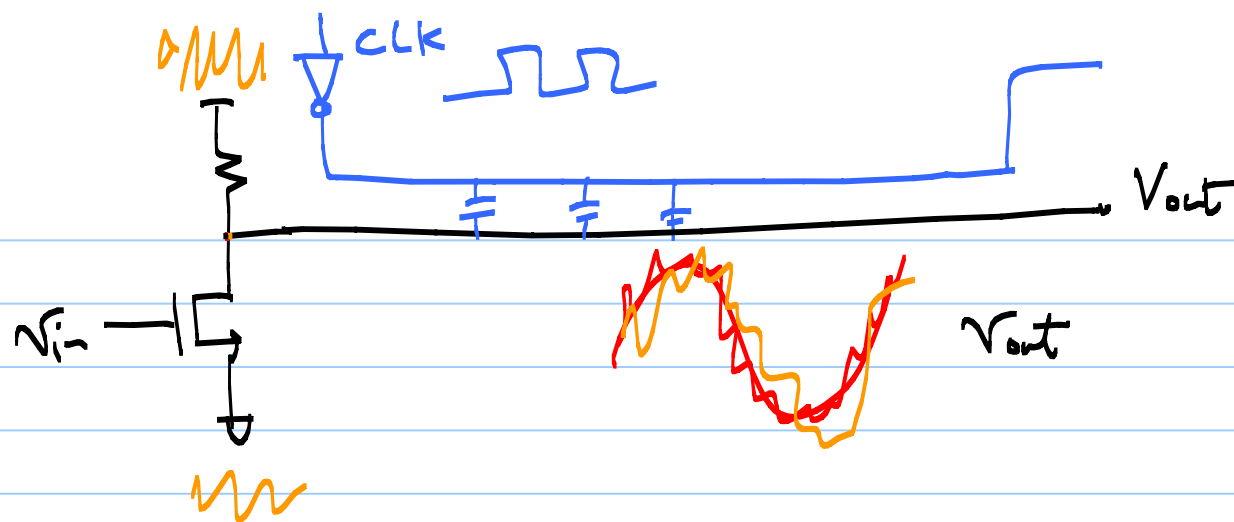
$$V_{cm} = \frac{V_{in1} + V_{in2}}{2} \quad \leftarrow \text{CM signal}$$



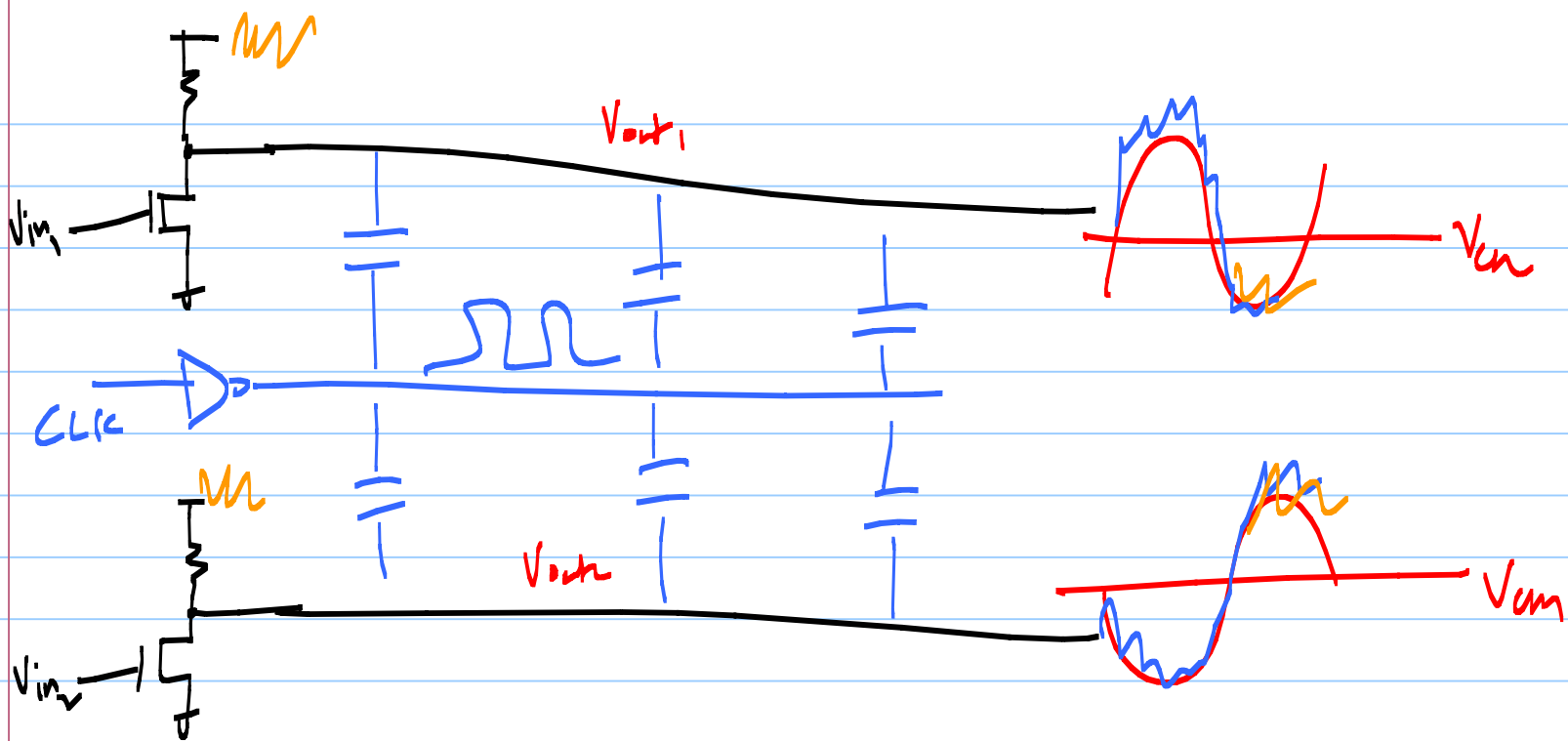





$$V_{dm} = V_{out1} - V_{out2} =$$
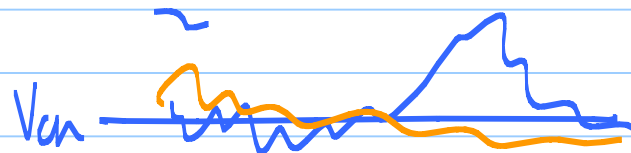
$$V_{av} = \frac{V_{out1} + V_{out2}}{2}$$




Differential sigals/circuits

↳ reject CM disturbances.

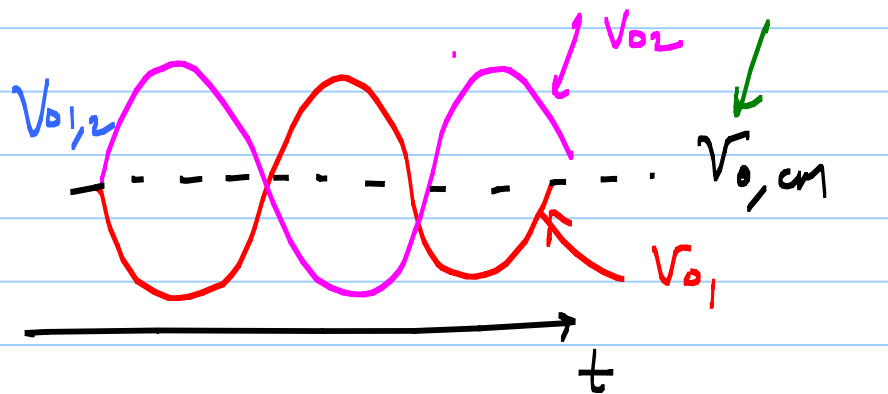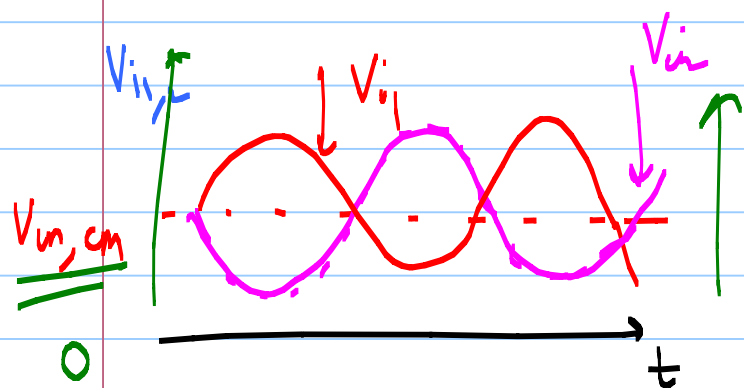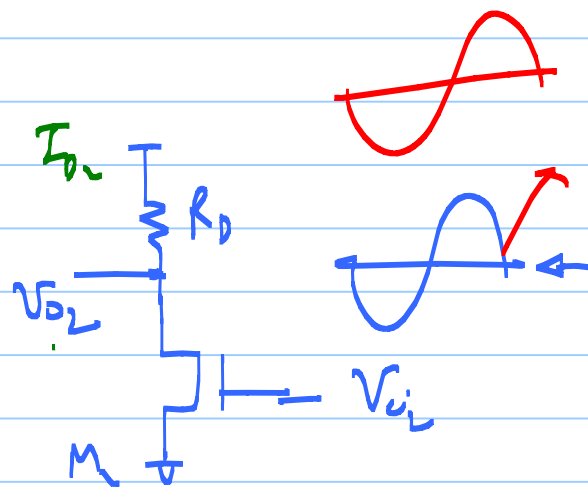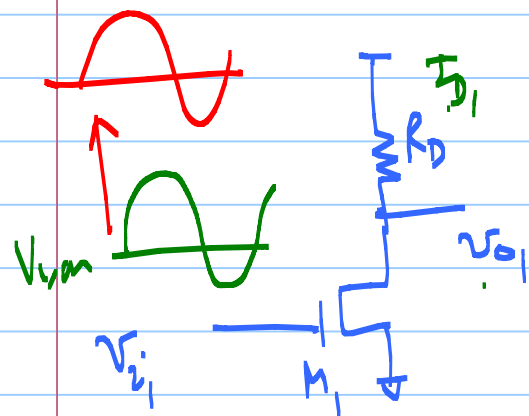

* Bias currents I_{D1}, I_{D2} $\leftrightarrow$ depend upon the input cm voltage

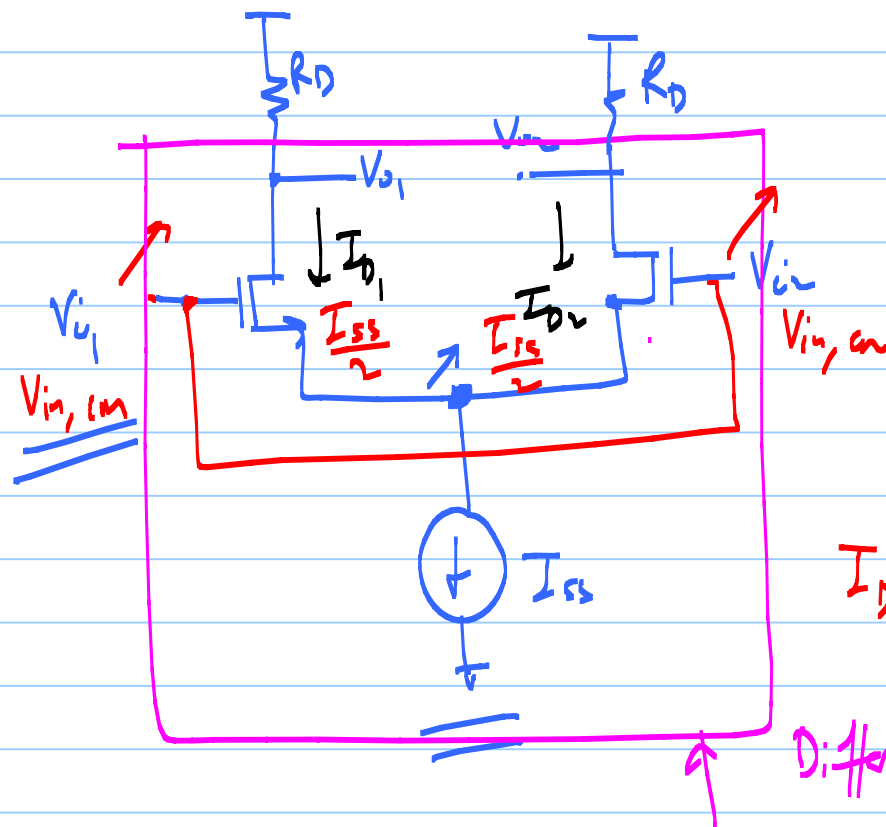* Somehow make I_{D1} & I_{D2} independent of $V_{in, cm}$ voltage




$$\boxed{I_{D1} + I_{D2} = I_{SS}}$$



↑
independent of $V_{in,cm}$

$$I_{D1} = I_{D2} = \frac{I_{SS}}{2}$$


Differential pair


$$\boxed{I_{D1} + I_{D2} = I_{SS}}$$



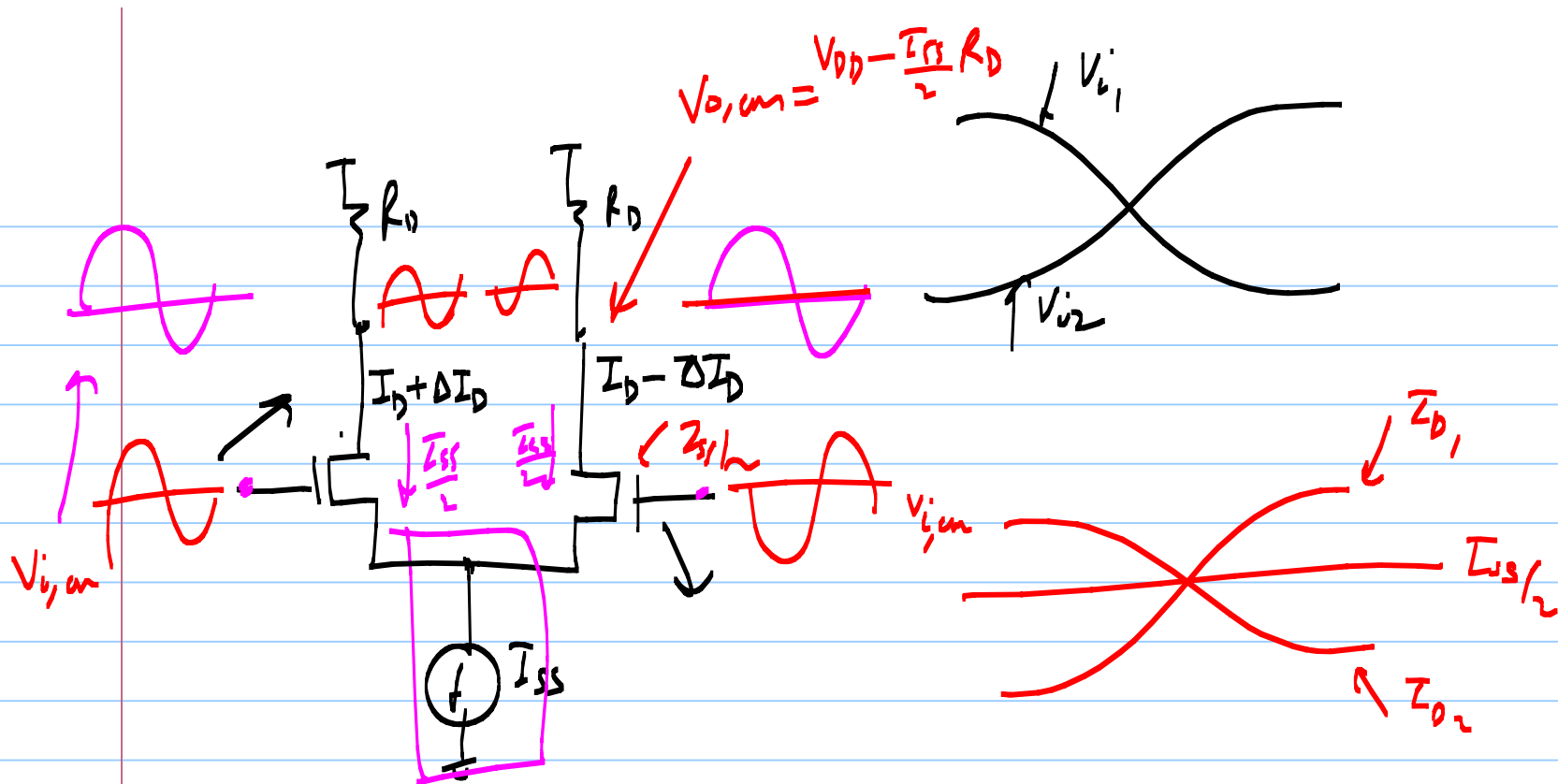


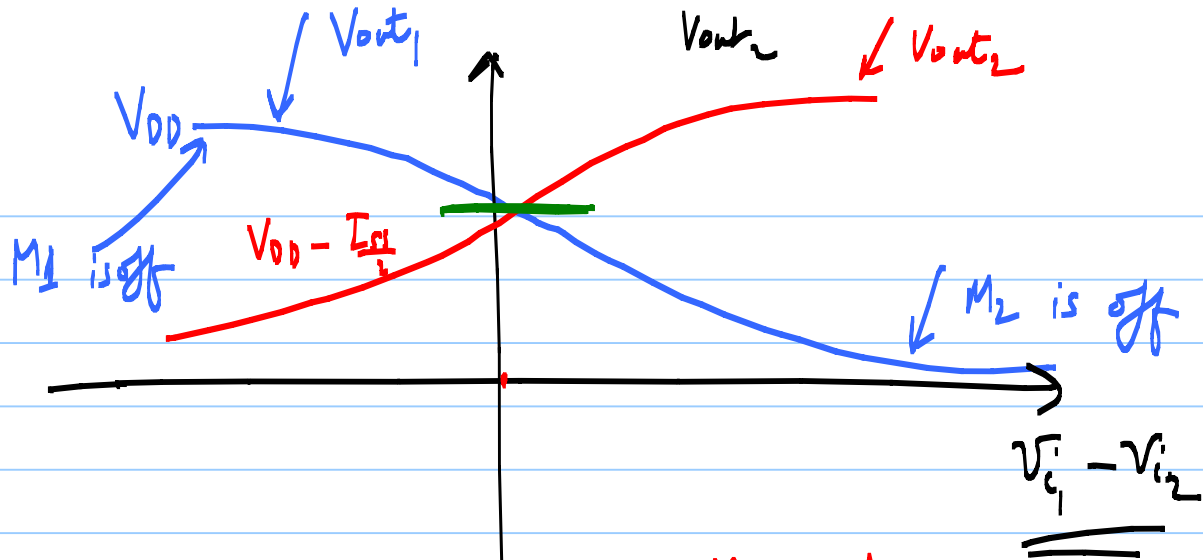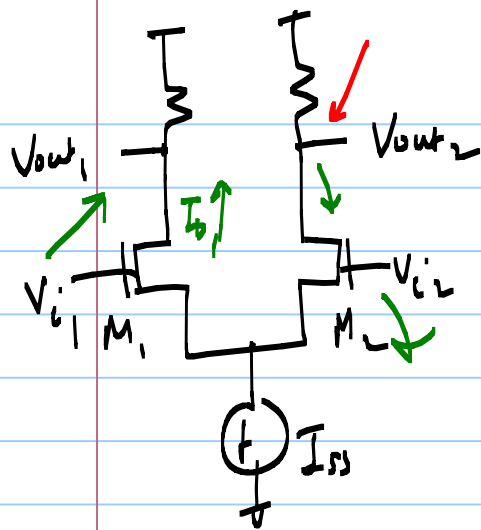

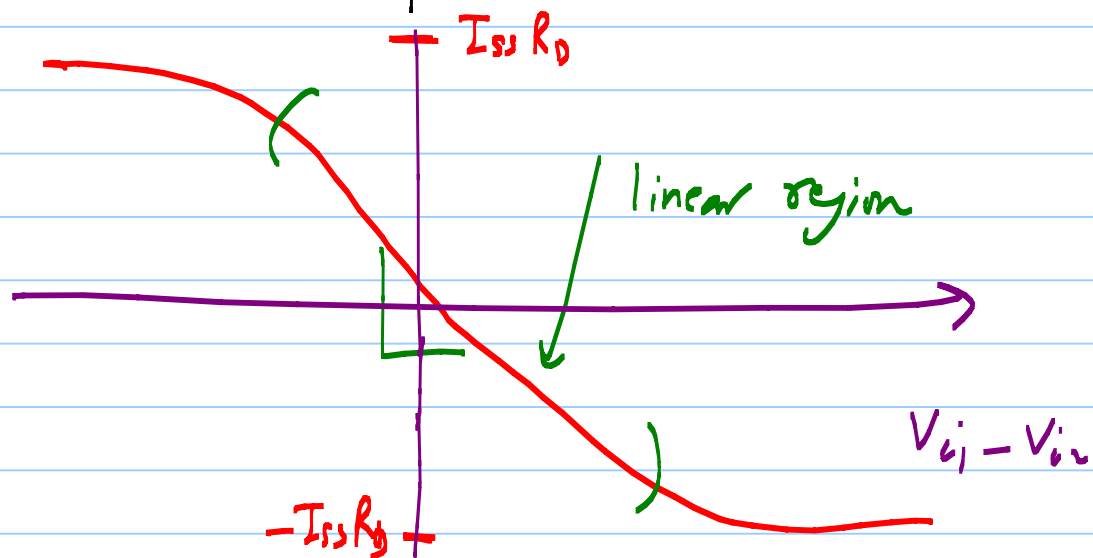$V_{out} = V_{out1} - V_{out2}$ ← DM output



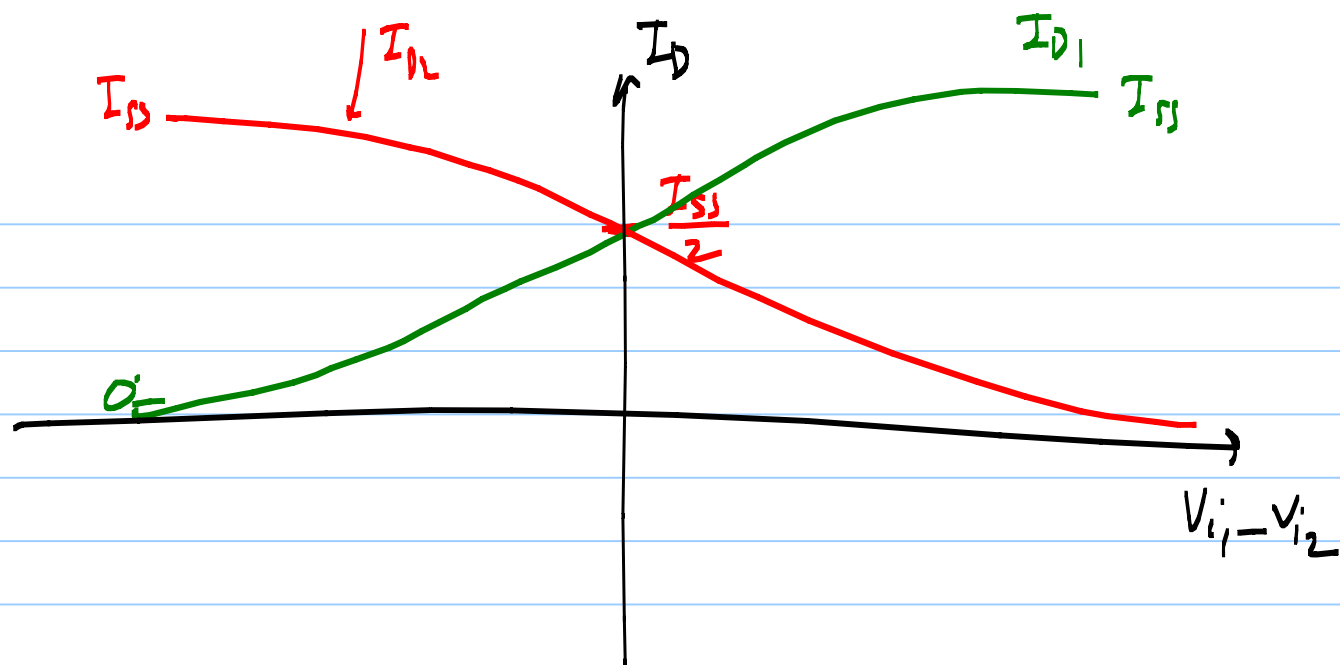

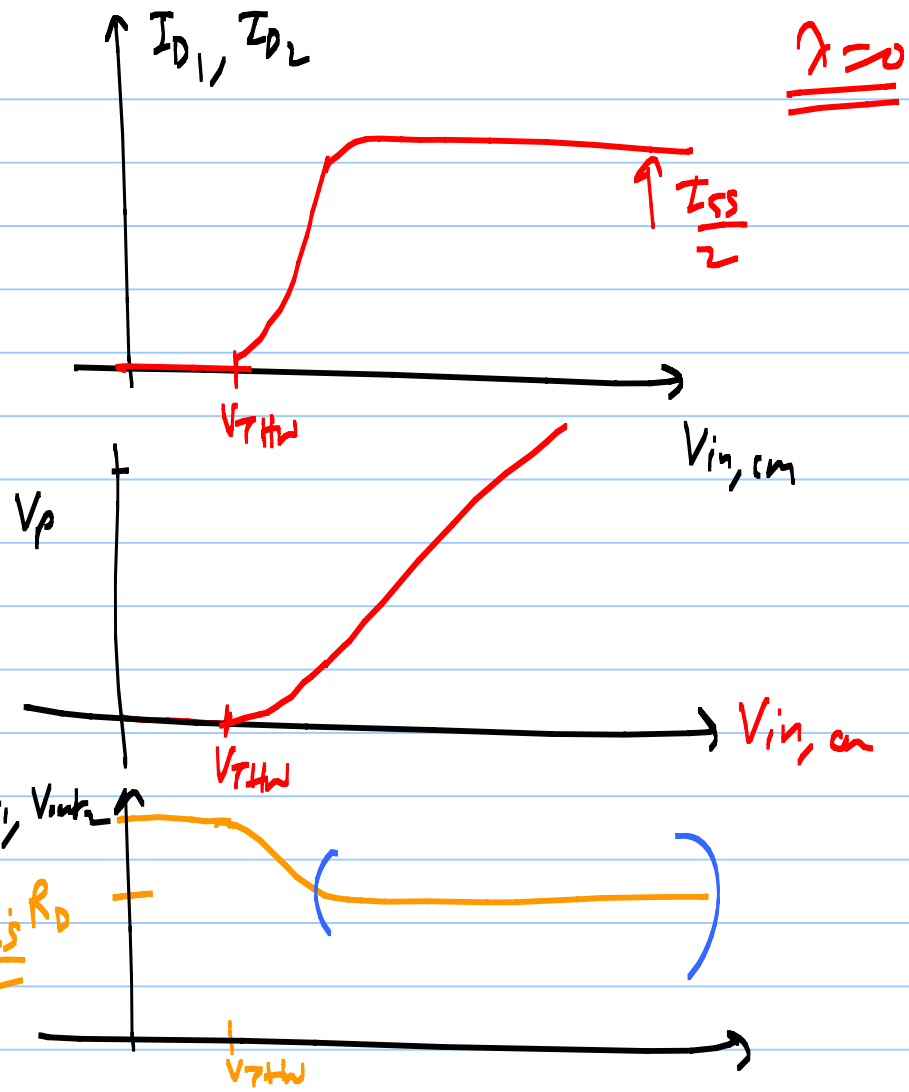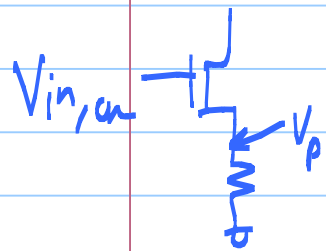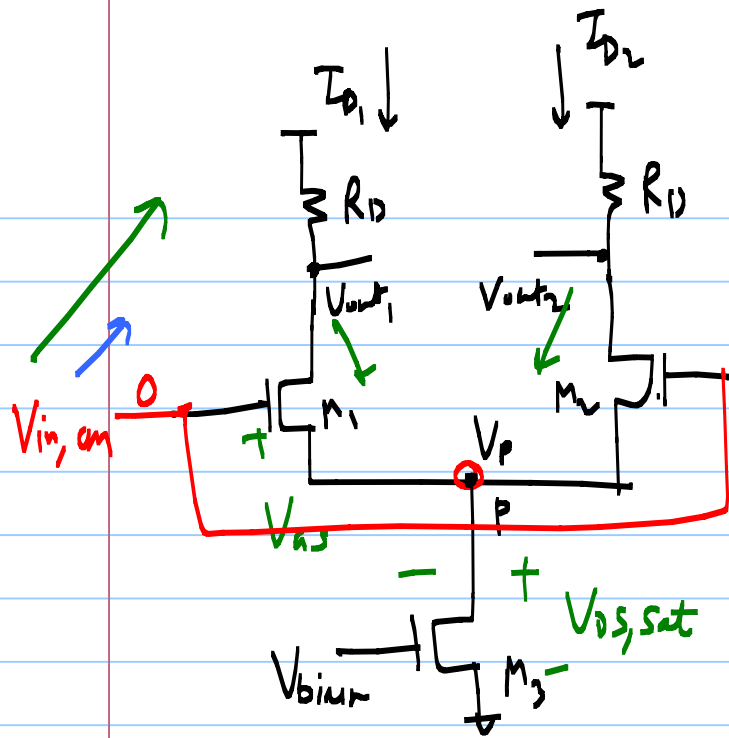

$$\underline{\underline{V_{in,cm}}} \geq V_{DS,sat3} + V_{GS1,2} \quad \text{M}_{1,2,3} \text{ are all in SAT}$$

M₁ & M₂ enter Triode

$$V_{in,cm} > V_{out1} + V_{THN}$$

$$V_{DS1} < V_{GS1} - V_{THN}$$

$$\uparrow$$

$$(V_{in,cm} - V_P) < (V_{out1,2} - V_P) - V_{THN}$$

$$V_{in, cm} > V_{out, cm} + V_{THN}$$

$$V_{in, cm} > \underline{V_{DD} - \frac{I_{SS} R_D}{2} + V_{THN}}$$

$$V_{GS1} + V_{OS, sat3} < \underbrace{V_{in, cm}} < V_{DD} - \frac{I_{SS} R_D}{2} + V_{THN}$$

↑ Allowed input common-mode range

Input CMR