



ECE 511 - lecture 18

Note Title


4/4/2012

* Diff amp

ICMR

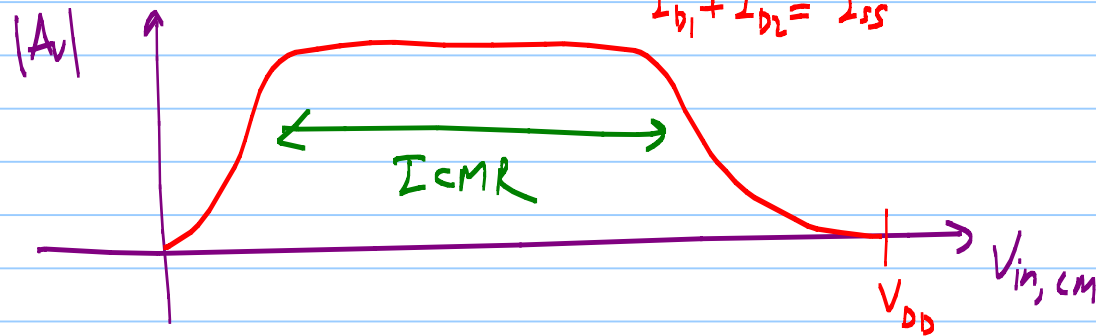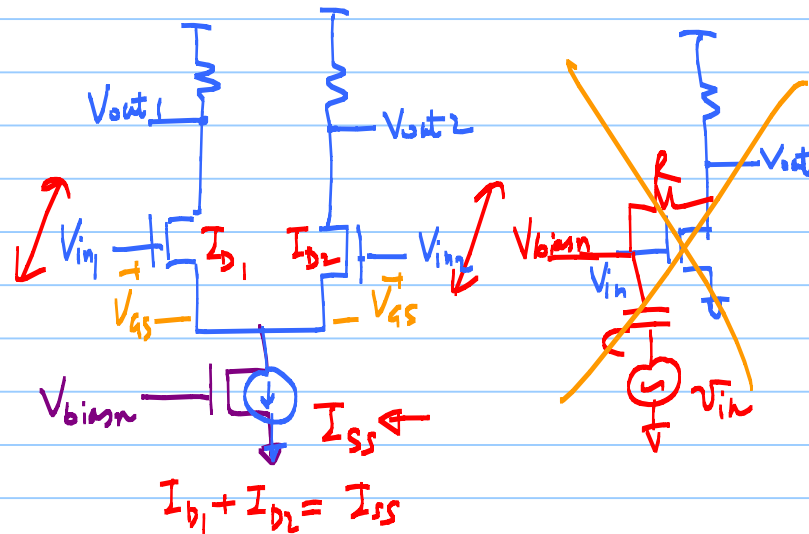


Output Swing?

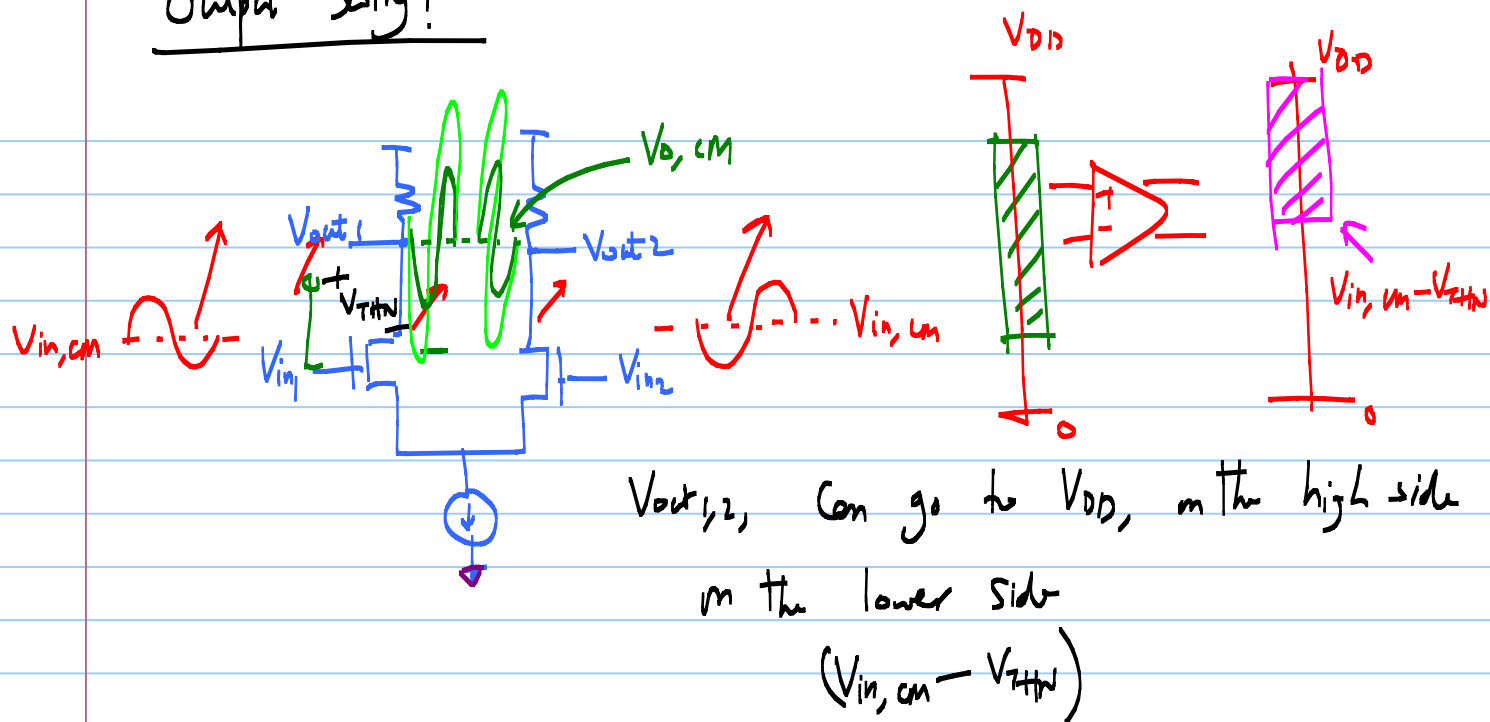

Assume symmetric, & $\lambda = 0$
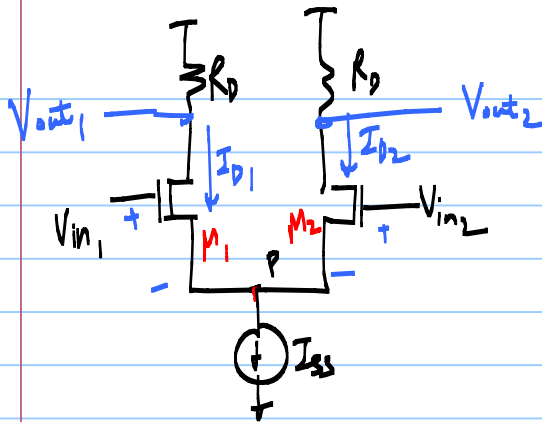
$$V_{out1} - V_{out2} = R_D (I_{D2} - I_{D1}) \rightarrow \textcircled{1}$$




$$V_{in1} - V_{in2} = V_{GS1} - V_{GS2}$$


$$= \left(\sqrt{\frac{2I_{D1}}{\beta}} + \cancel{V_{thn}} \right) - \left(\sqrt{\frac{2I_{D2}}{\beta}} - \cancel{V_{thn}} \right)$$

$$V_{in1} - V_{in2} = \sqrt{\frac{2}{\beta}} \left(\sqrt{I_{D1}} - \sqrt{I_{D2}} \right) \rightarrow \textcircled{2}$$

$$I_{D1} + I_{D2} = I_{SS} \rightarrow \textcircled{3}$$
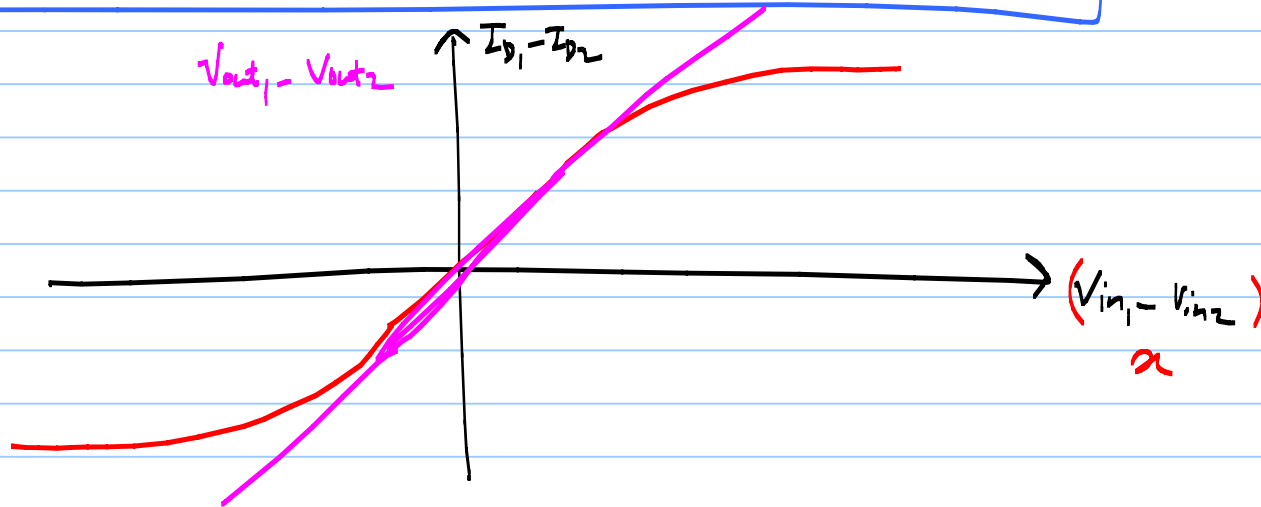
$$I_{D1} - I_{D2} = \frac{\beta}{2} \underbrace{(V_{in1} - V_{in2})}_{\propto} \sqrt{\underbrace{\frac{4I_{SS}}{\beta}}_{V_{ov}^2} - \underbrace{(V_{in1} - V_{in2})^2}_{\propto^2}}$$




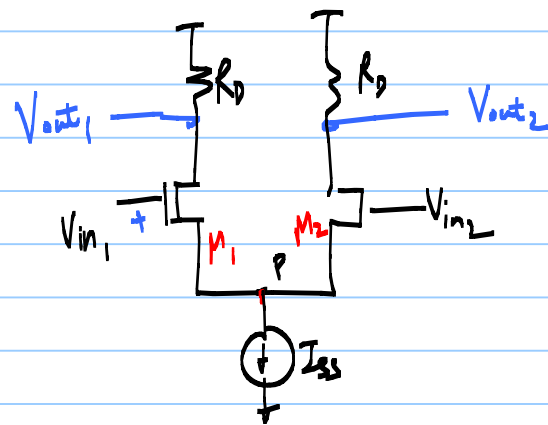


Differential Small-signal gain

$$A_{DM} = \frac{(V_{out1} - V_{out2})}{(V_{in1} - V_{in2})}$$


Half-Circuit Method

Symmetric Circuit

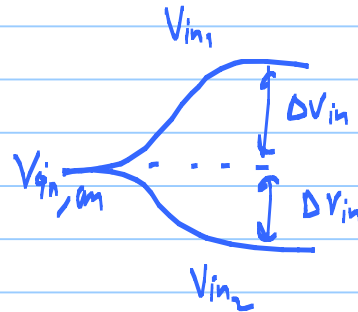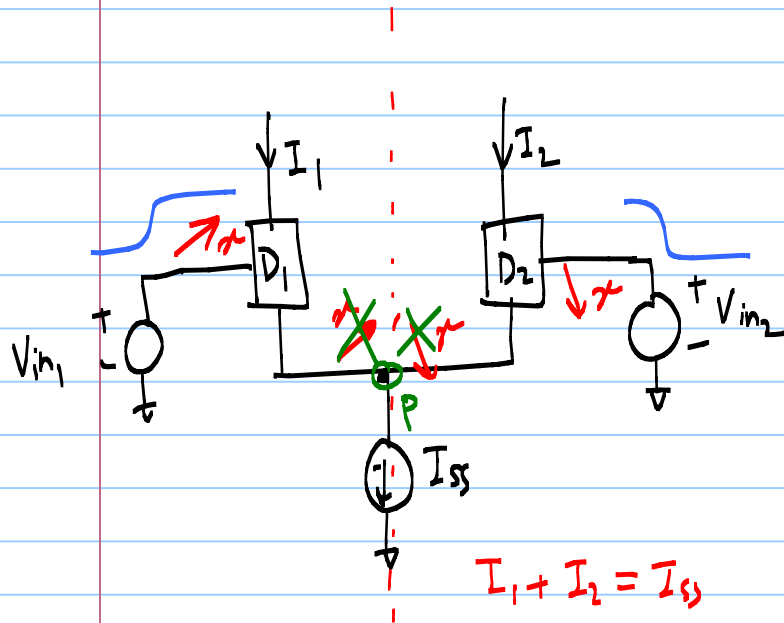


By symmetry node $P \leftarrow$ fixed
DC voltage

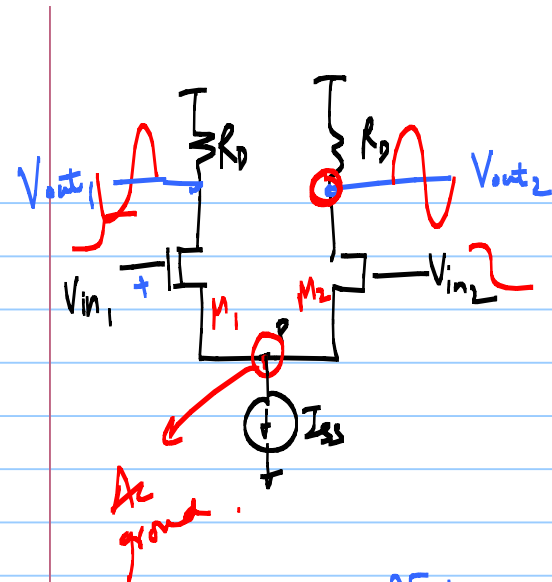$\hookrightarrow$ Node "P" is an "AC ground"



AC Picture

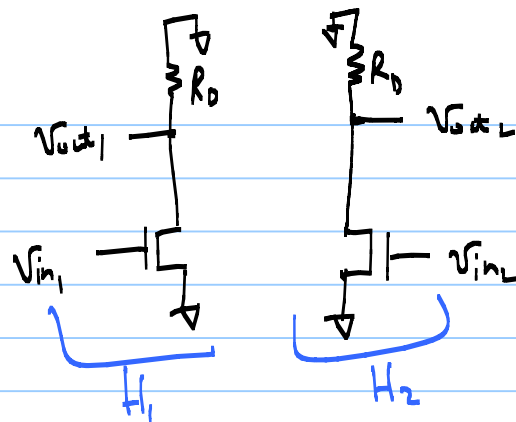

Two Half Circuits

$$H_1: \frac{V_{out1}}{V_{in1}} = -g_{m1}(R_D \parallel r_{o1})$$

$$H_2: \frac{V_{out2}}{V_{in2}} = -g_{m2}(R_D \parallel r_{o2})$$




$$g_{m1} = g_{m2}$$

$$r_{o1} = r_{o2}$$

$$\frac{V_{out1} - V_{out2}}{V_{in1} - V_{in2}} = -g_m(R_D \parallel r_o) \leftarrow \text{Differential mode gain}$$

$$= \frac{V_{out2}}{V_{in1} - V_{in2}} = \frac{g_m (R_D || r_{o2})}{2}$$

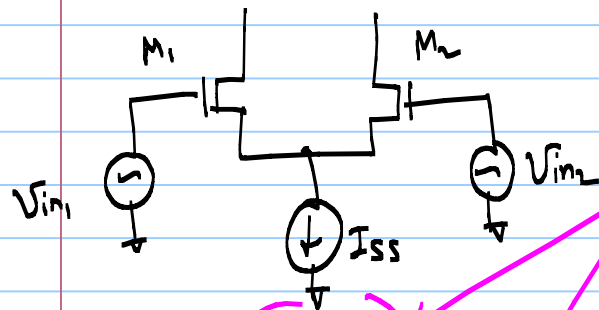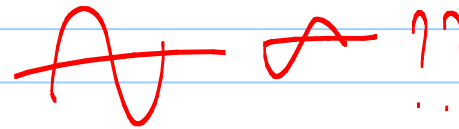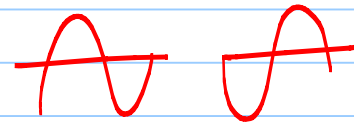* What if the inputs are not differential





Differential mode term $f(x)$

$$V_{in1} = \frac{(V_{in1} - V_{in2})}{2} + \frac{(V_{in1} + V_{in2})}{2}$$

$$V_{in2} = \frac{(V_{in2} - V_{in1})}{2} + \frac{(V_{in1} + V_{in2})}{2}$$



$$= \underbrace{\left(\frac{f(x) + f(-x)}{2} \right)}_{\text{Even}} + \underbrace{\left(\frac{f(x) - f(-x)}{2} \right)}_{\text{Odd}}$$

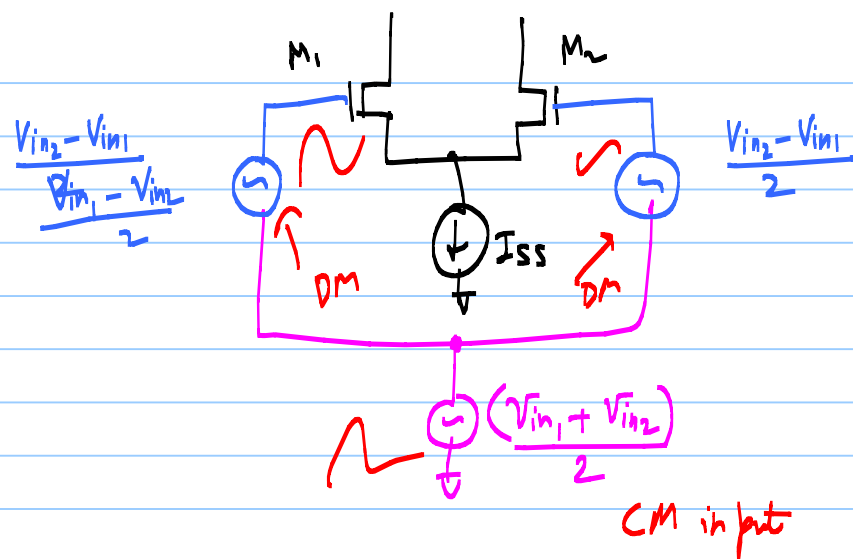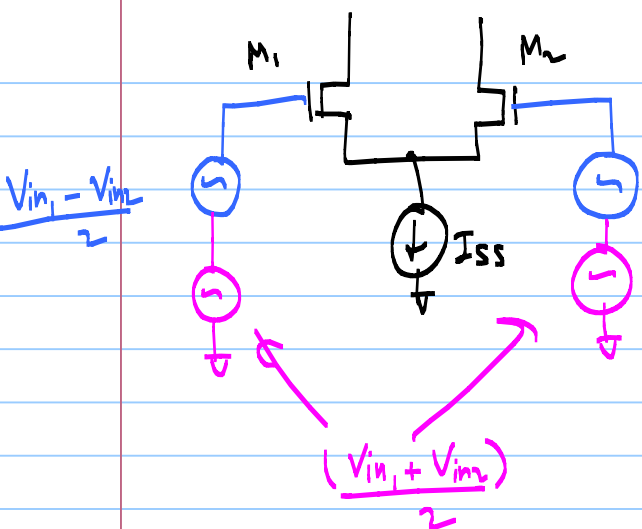Common mode term $\leftarrow$ NOT DC here



By Superposition


⊕

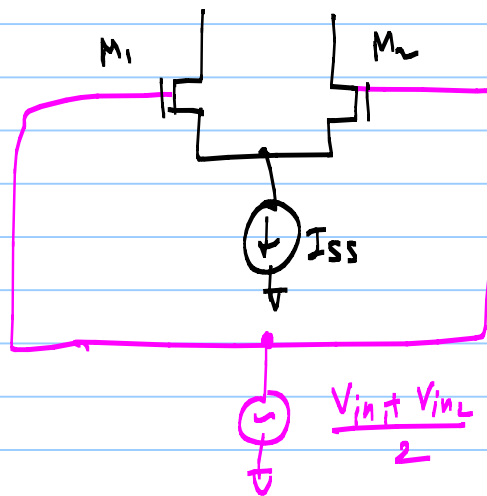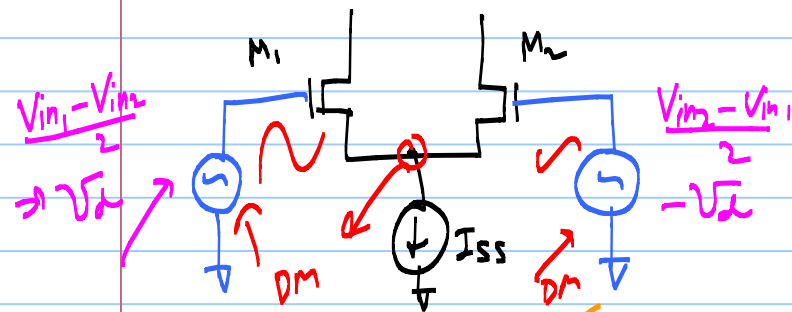

DM Equivalent

(Half Circuit Method)



CM Equivalent circuit

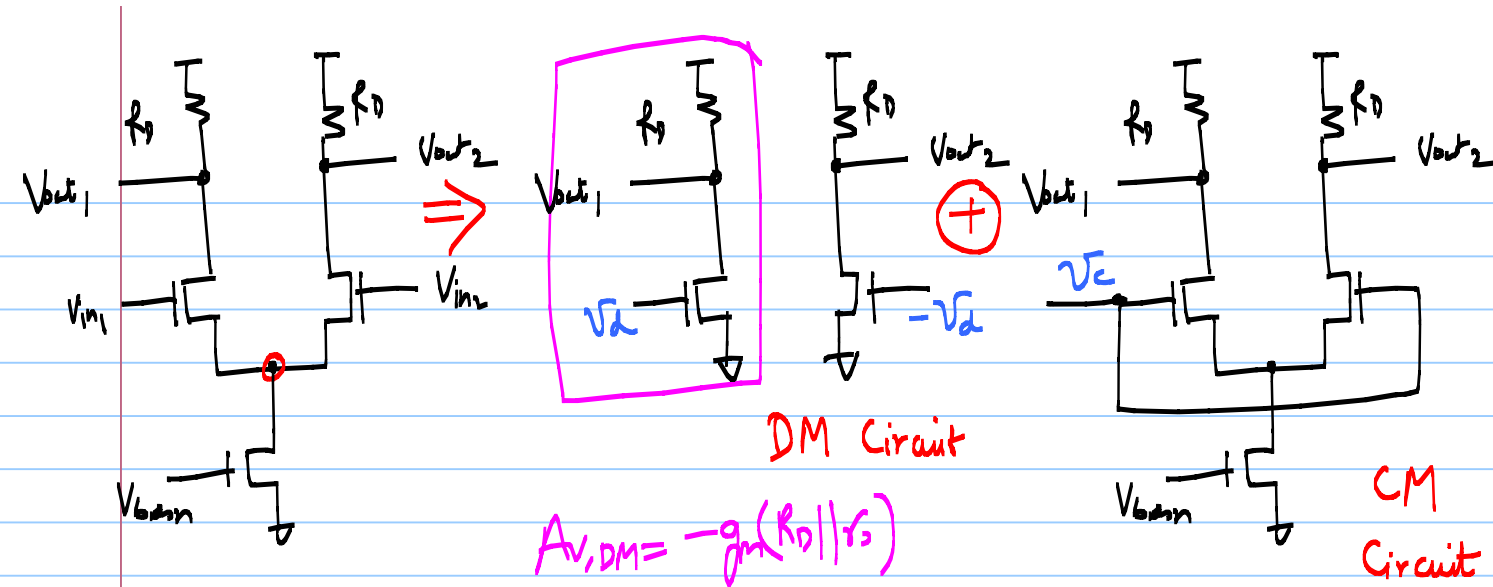

$$A_{v,DM} = -g_m(R_D || r_o)$$

$v_d = v_{in1} - v_{in2} \leftarrow$ differential input
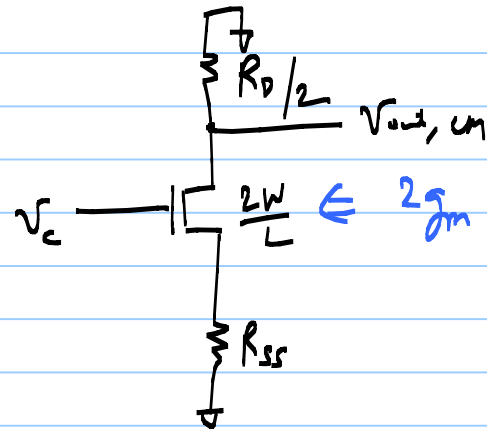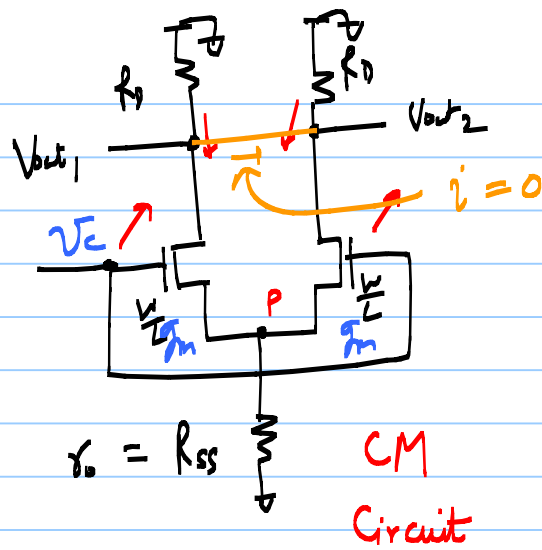
$$v_c = \left(\frac{v_{in1} + v_{in2}}{2} \right)$$



Equivalent CM circuit

Common mode gain $A_{v,cm} = \frac{v_{out,cm}}{v_c} = \frac{-R_D/2}{1/2g_m + R_{SS}}$

$$A_{v,DM} = -g_m(R_D || r_o) \quad \text{Maximize}$$

$$A_{v,CM} = \frac{-R_D/2}{\left(\frac{1}{2g_m}\right) + R_{SS}} \quad \text{Minimize}$$

Ideal tail CM

$$R_{SS} \rightarrow \infty$$

$$A_{v,CM} = 0$$

AC output

$$V_{out,L} = V_{out,L,DM} + V_{out,L,CM}$$


$$= A_{v,DM} \left(\frac{V_d}{2} \right) + A_{v,CM} (V_c)$$

$$\frac{V_{in1} + V_{in2}}{2}$$

$$\frac{V_{in1} - V_{in2}}{2}$$

Common-mode
rejection ratio

$$CMRR = \left| \frac{A_{v, DM}}{A_{v, CM}} \right| \rightarrow \infty$$

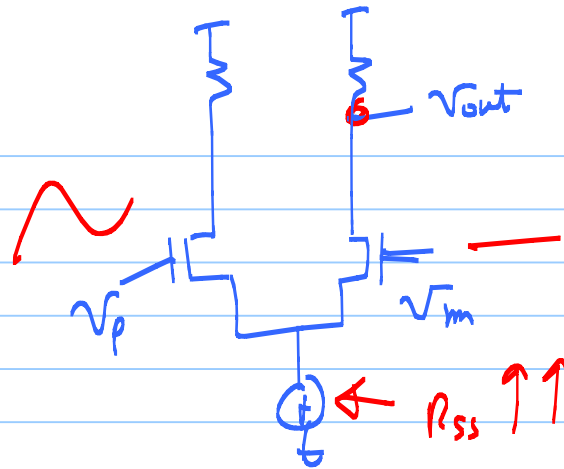



$$= \frac{g_m R_D / 2}{\left(\frac{g_m R_D}{1 + 2g_m R_{SS}} \right)}$$

$$\approx \frac{1}{2} + g_m R_{SS}$$

$$\approx \underline{\underline{g_m R_{SS}}}$$


R_{SS} should be as
large as possible

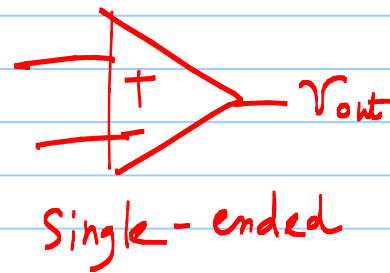

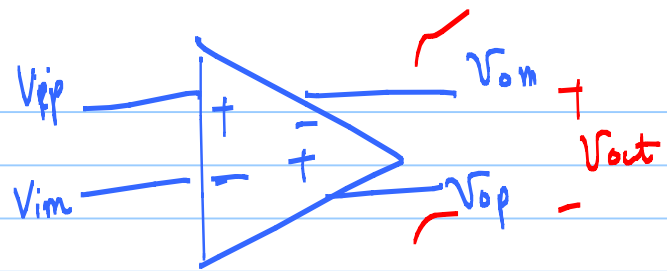


Diode Connected PMOS load

↳ 100 gain

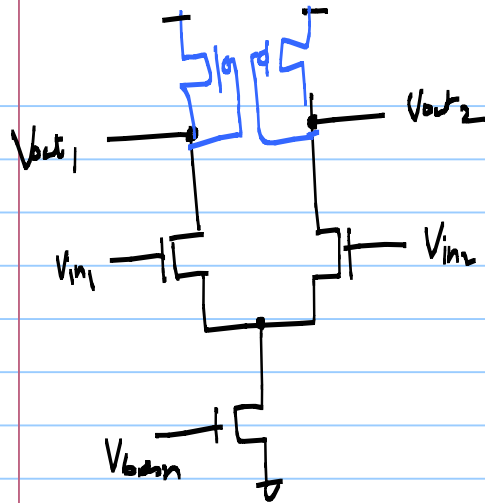

$$g_m(r_{o1} || r_{o3})$$

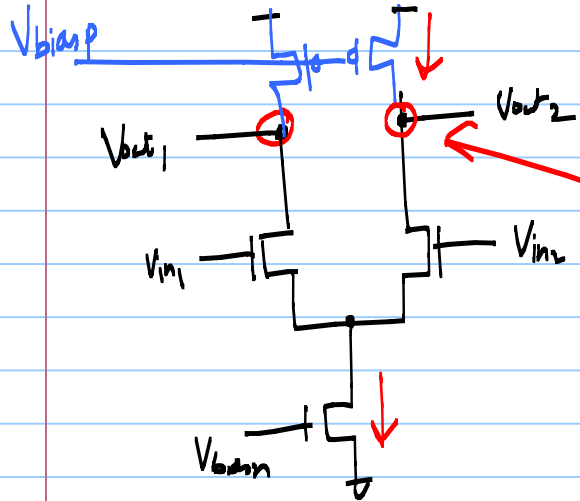

output CM-level
is not defined