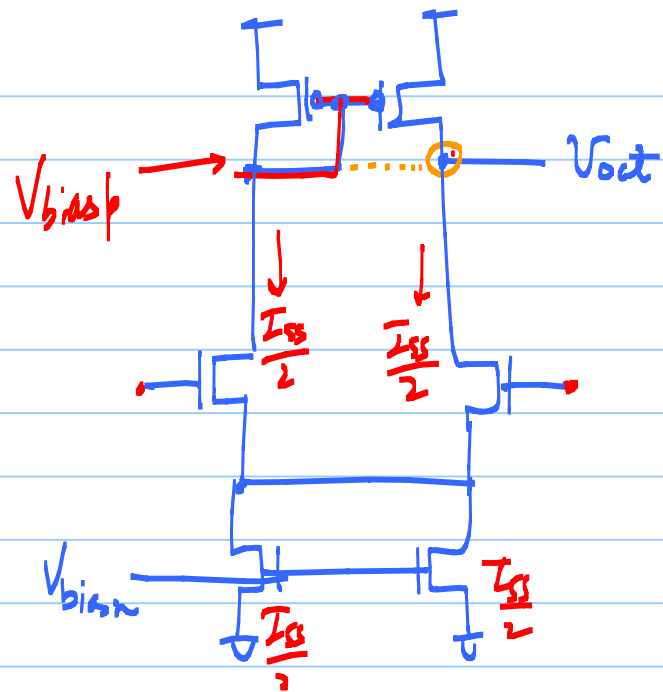



Note Title

Differential outputs



Single-Ended Diffamp (CM load)



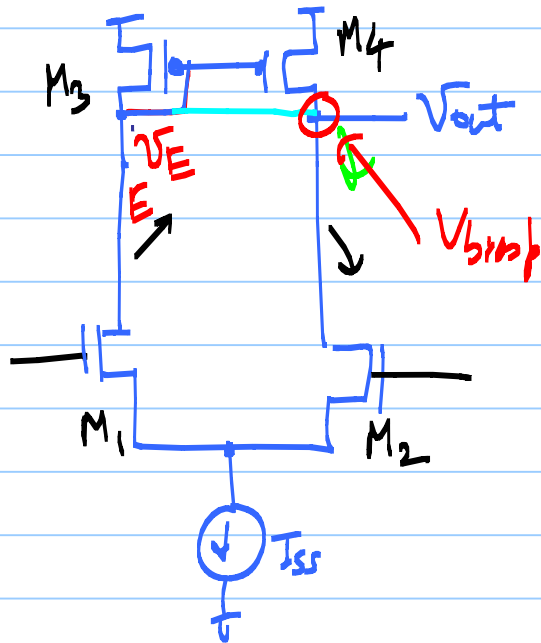

Let $V_{out} < V_E$



① $I_{D1} > I_{D2}$ $\Rightarrow I_{D1} > \frac{I_{SS}}{2}$
 $I_{D2} < \frac{I_{SS}}{2}$

$I_{D3} > \frac{I_{SS}}{2}$


$\Rightarrow I_{D4} < \frac{I_{SS}}{2}$

② $I_{D4} > \frac{I_{SS}}{2}$ $\Rightarrow$ Contradiction

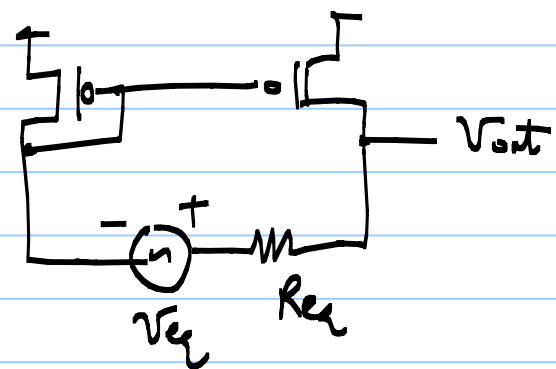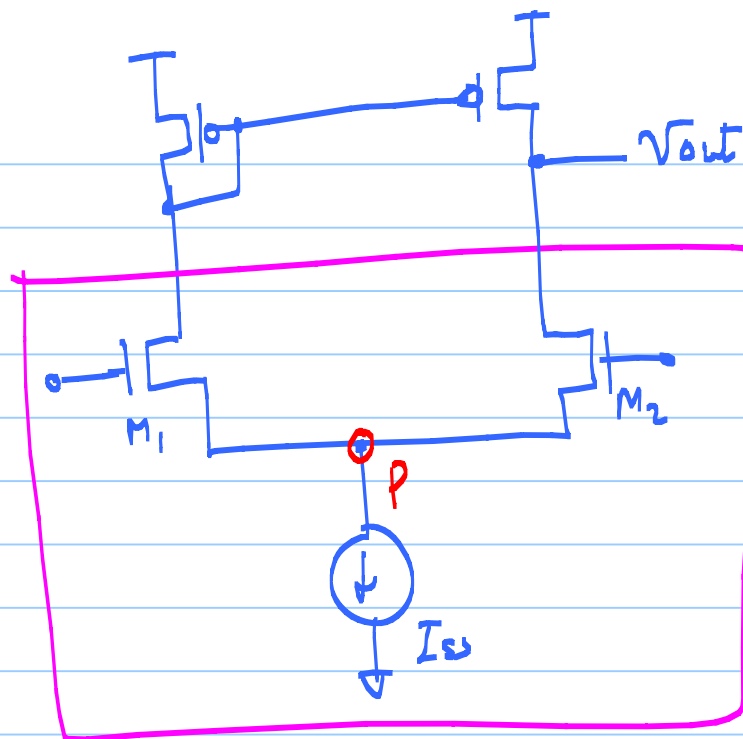$V_{out} \triangleq V_E = V_{bipolar}$
 Proof by contradiction




↑ Look at the posted
notes online

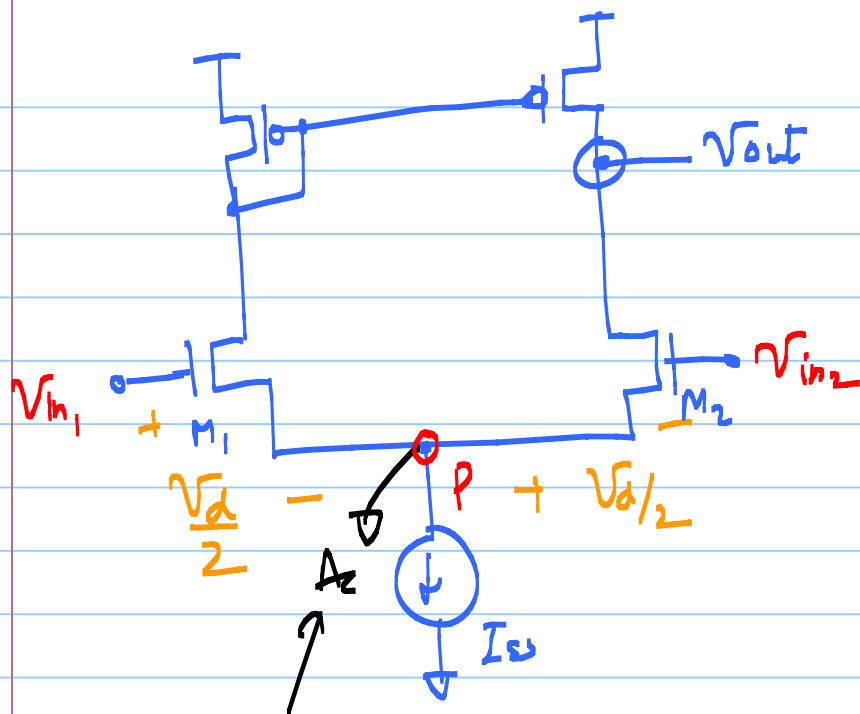

$$V_d = V_{in1} - V_{in2}$$


Assumption

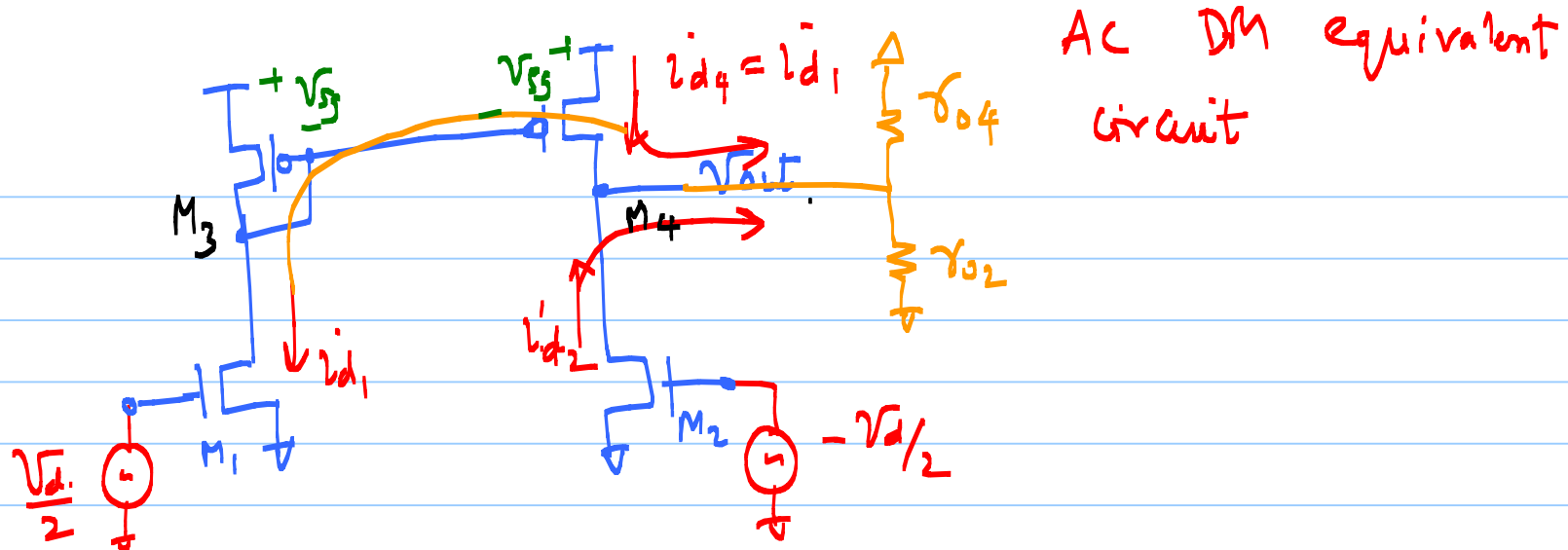

$$\begin{aligned}
 V_{out} &= + (i_{d2} + i_{d4}) (r_{o2} \parallel r_{o4}) \\
 &= 2 i_{d2} (r_{o2} \parallel r_{o4}) = 2 \cdot \underbrace{i_{d2}}_{g_m \frac{V_d}{2}} (r_{o2} \parallel r_{o4}) \\
 &= \boxed{g_m (r_{o2} \parallel r_{o4})} V_d
 \end{aligned}$$

$$A_{v,DM} = + g_{m,2} (r_{o2} \parallel r_{o4})$$

Common-mode analysis



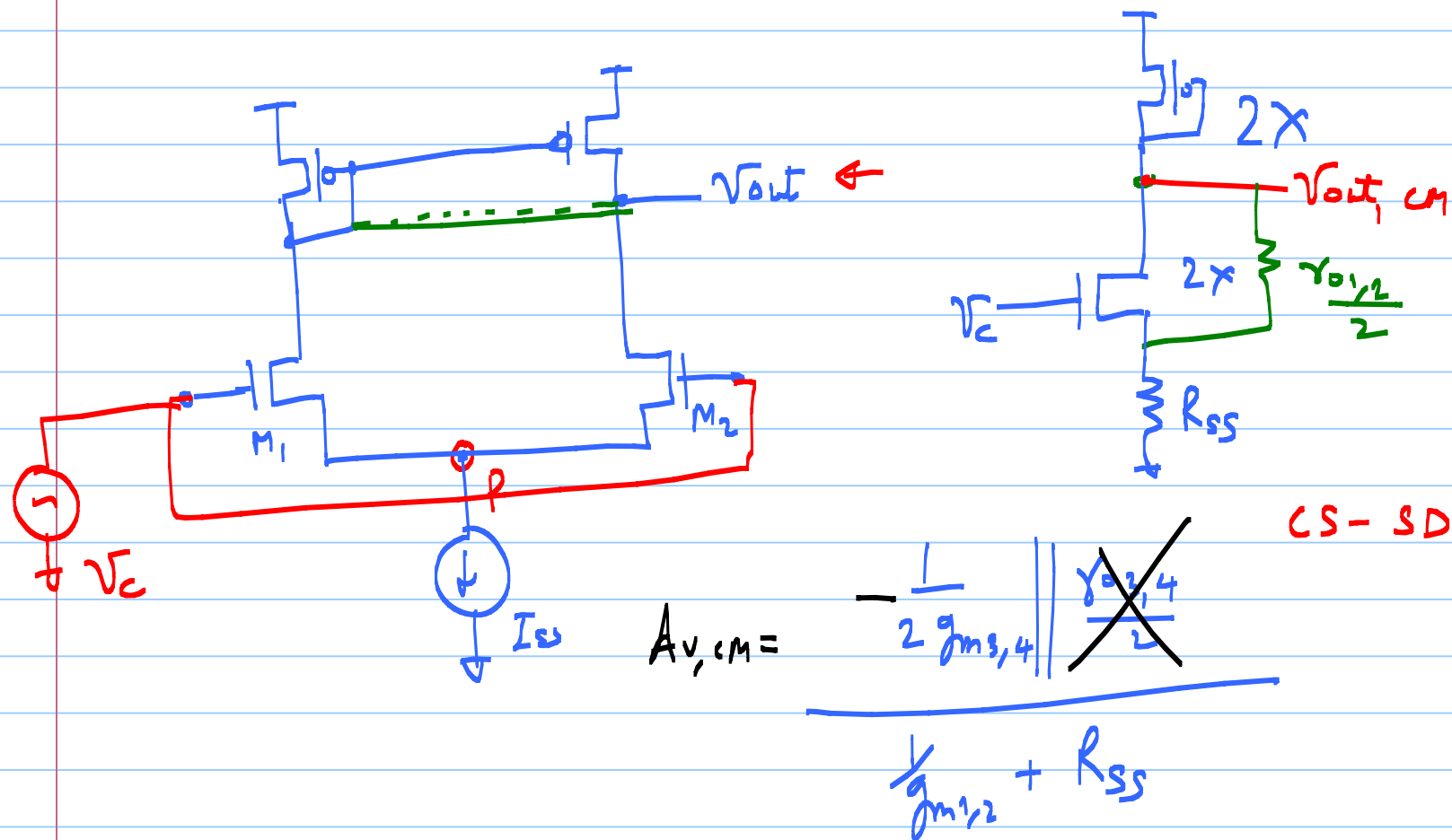


$$A_{v,cm} = \frac{-1}{1 + 2 g_{m1,2} R_{SS}} \cdot \frac{g_{m1,2}}{g_{m3,4}}$$

$$\approx \frac{-1}{2 g_{m3,4} \cdot R_{SS}}$$

$$CMRR = \left| \frac{A_{v,dm}}{A_{v,cm}} \right| = g_{m1,2} (r_{o1,2} || r_{o3,4}) \cdot \underbrace{2 g_{m3,4} \cdot R_{SS}}$$


DM AC Response

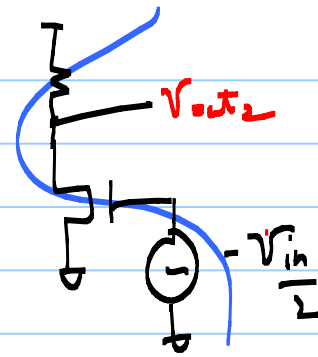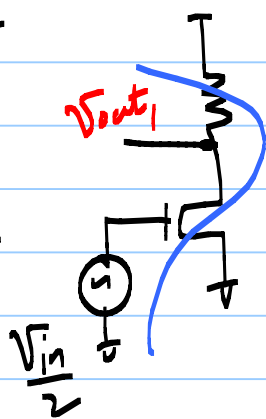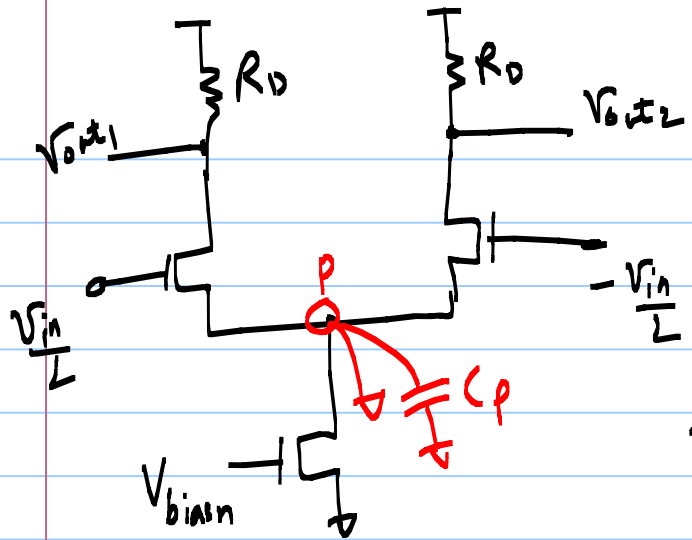

1 pole
1 RHP zero

$$\omega_{p1} = \frac{1}{(r_{ds} || R_D) C_L}$$

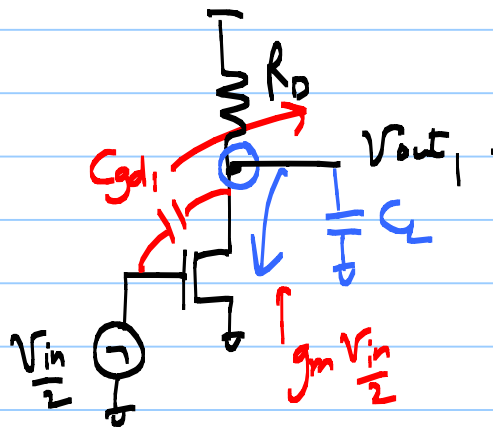
$$\omega_z = + \frac{g_{m1,2}}{C_{gd1,2}}$$




$$\frac{V_{out}}{V_{in}}(s) = - \frac{A_{vo} (1 - s/\omega_z)}{(1 + s/\omega_{p1})}$$

$$A_{vo} \Rightarrow g_{m1,2} (r_{o2} \parallel r_{o4})$$

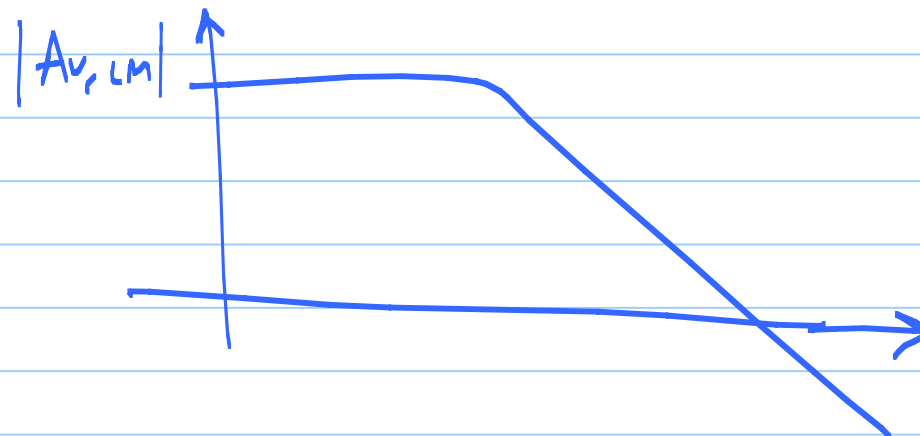
$$A_{v,cm} = - \frac{\frac{R_D}{2} \parallel \frac{1}{sC_L}}{\frac{1}{2g_{m1,2}} + r_{o3} \parallel \left(\frac{1}{s\varphi}\right)}$$



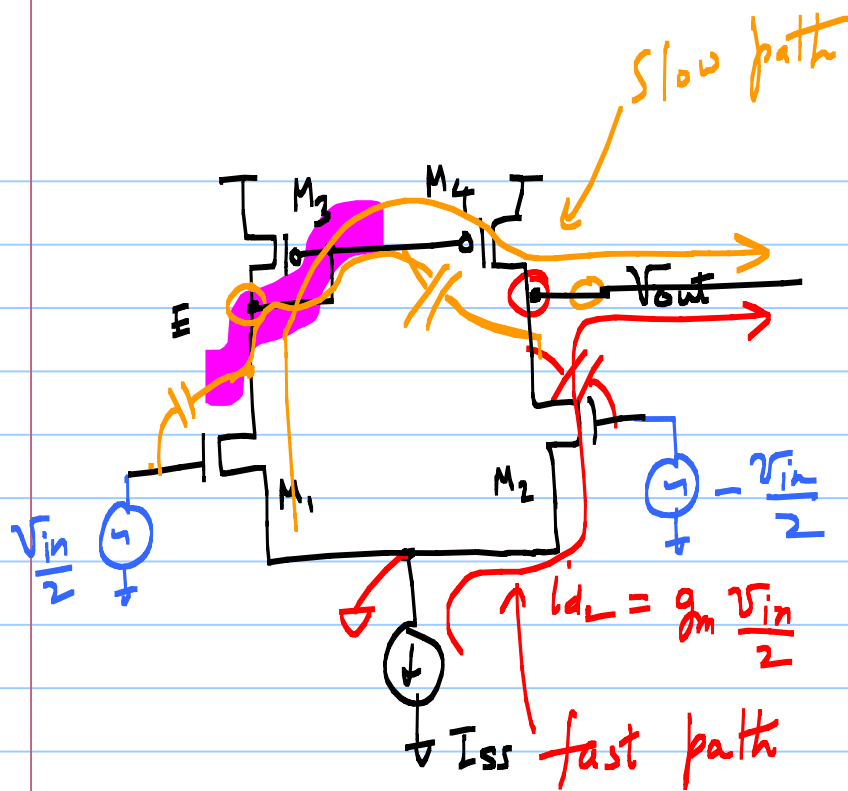


$V_{out} \rightarrow$ Dominant pole
 $E \Rightarrow$ Mirror pole

RHP zero

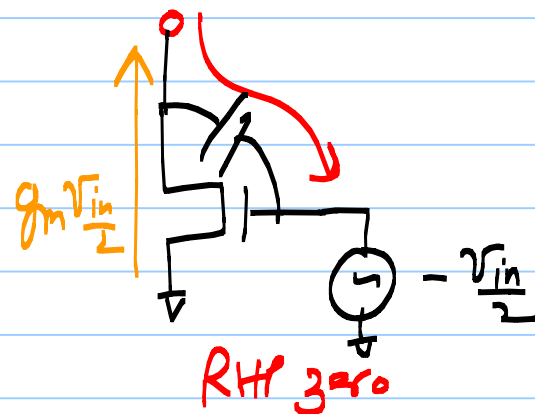

(fast path zero)

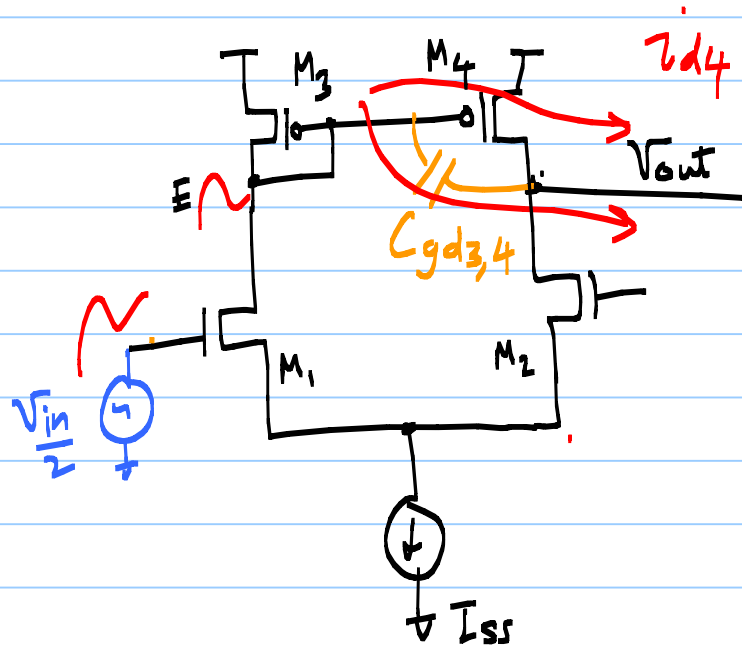

LHP zero

$$\frac{g_{m4}}{C_{gd3,4}}$$

