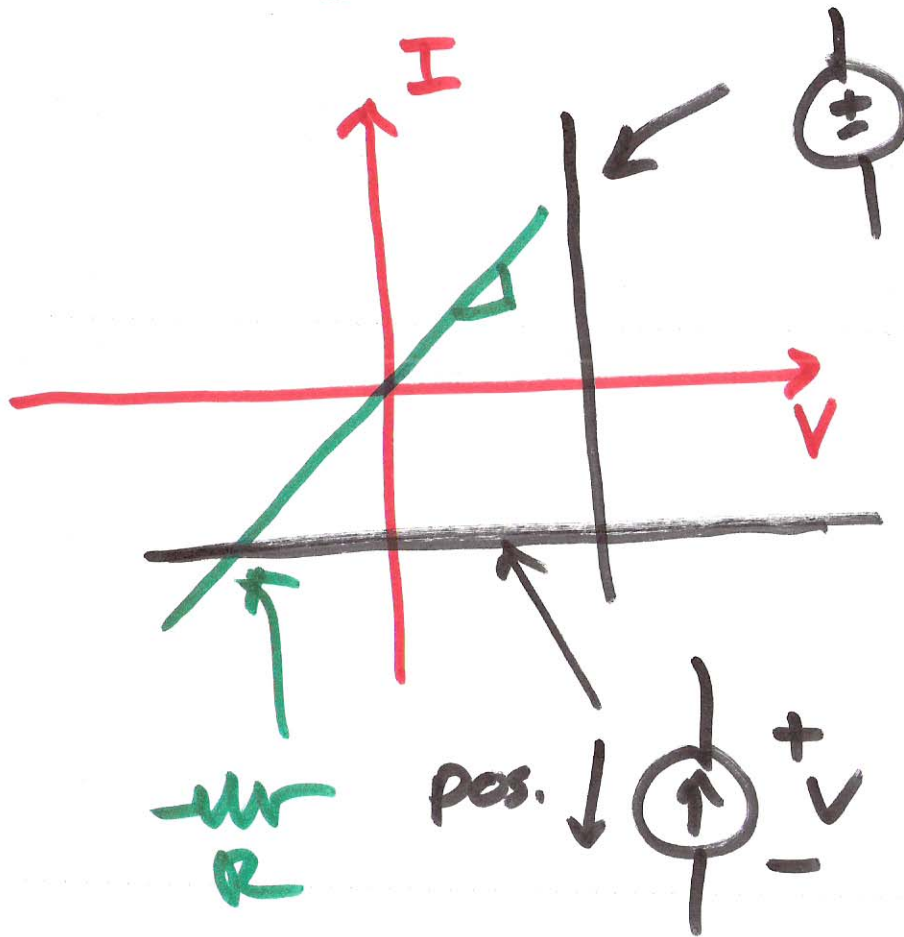


Lecture 1


JAN. 18, 2012

Start Ch. 9




H.W. due Monday


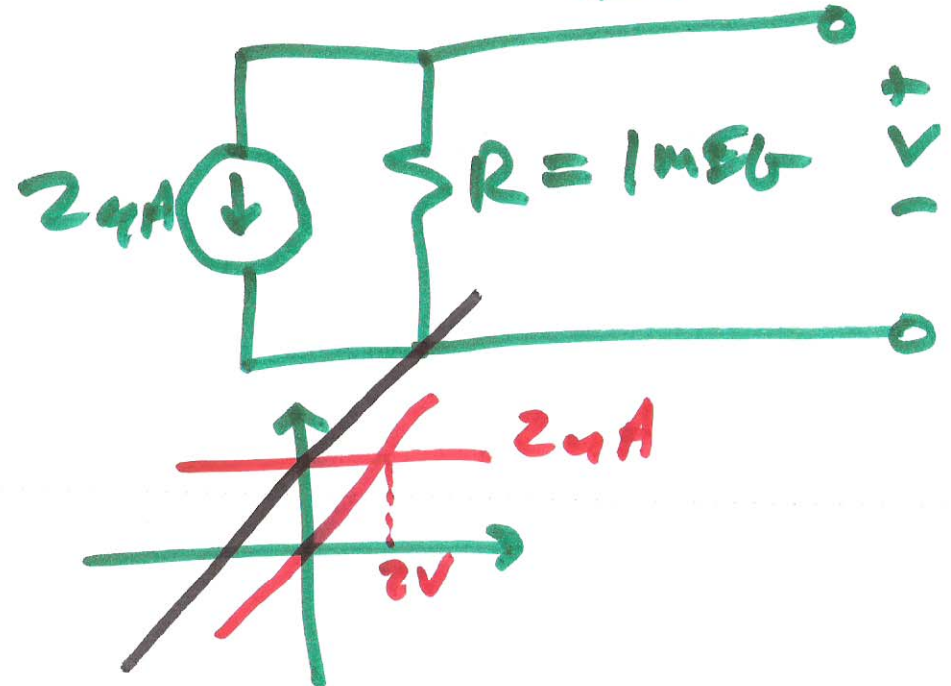
$$\text{slope} = \frac{\Delta I}{\Delta V} = \frac{1}{R}$$






1)

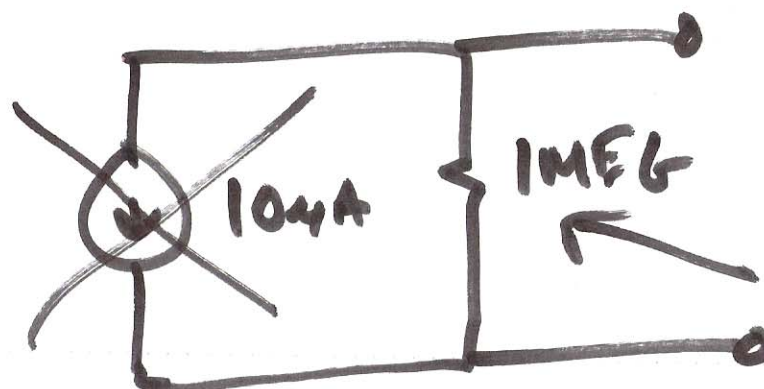
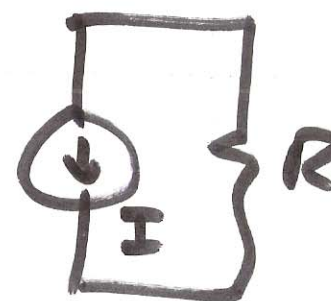
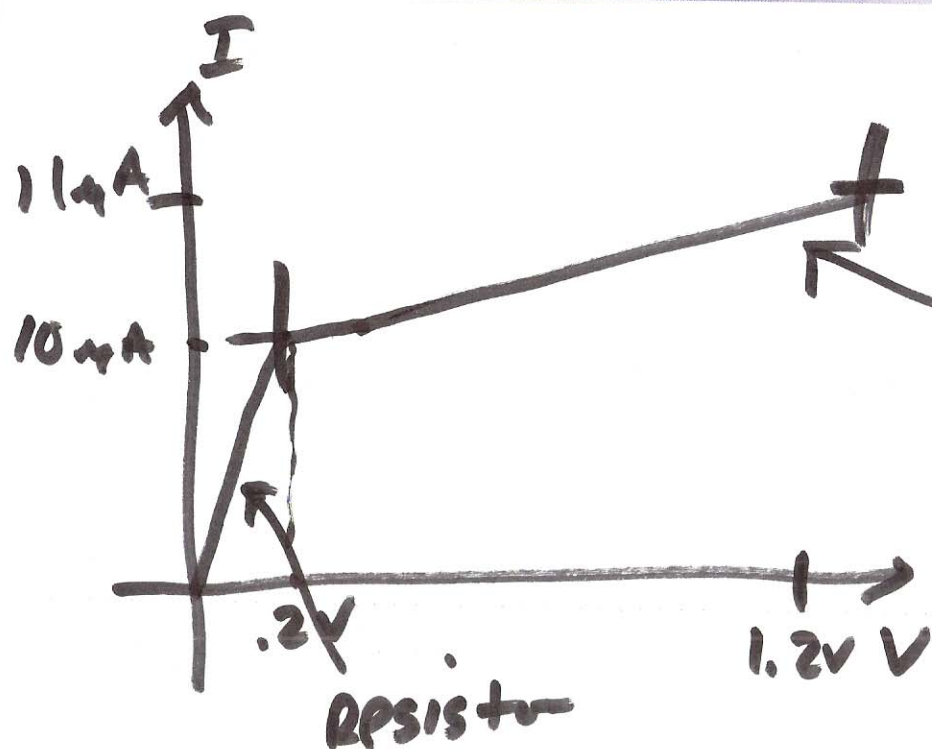


Resistor for
Small-signal
Analysis.

IV curves of a MOSFET

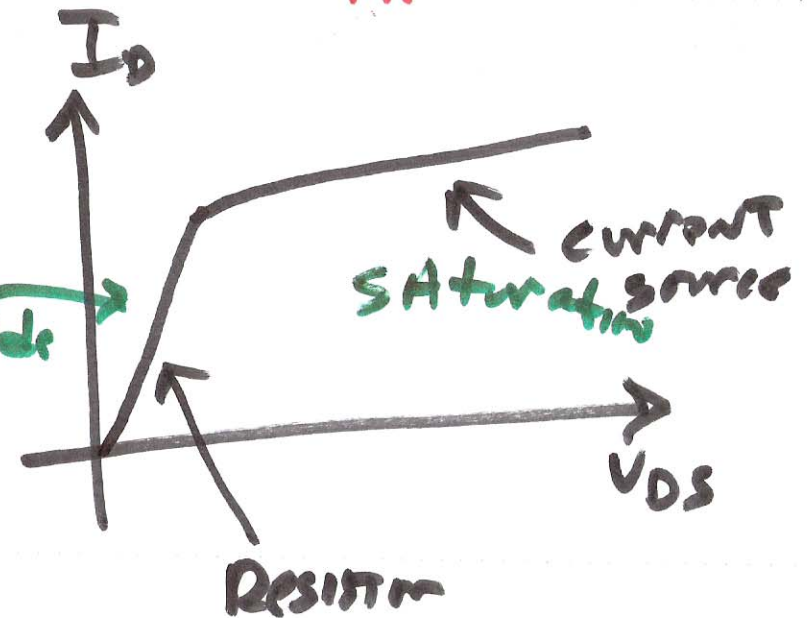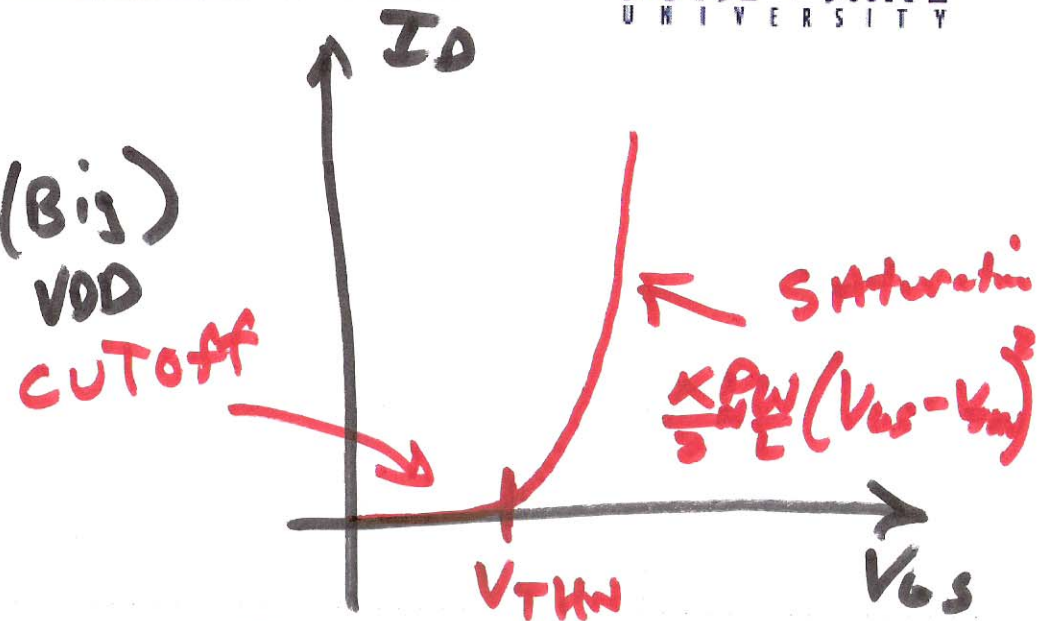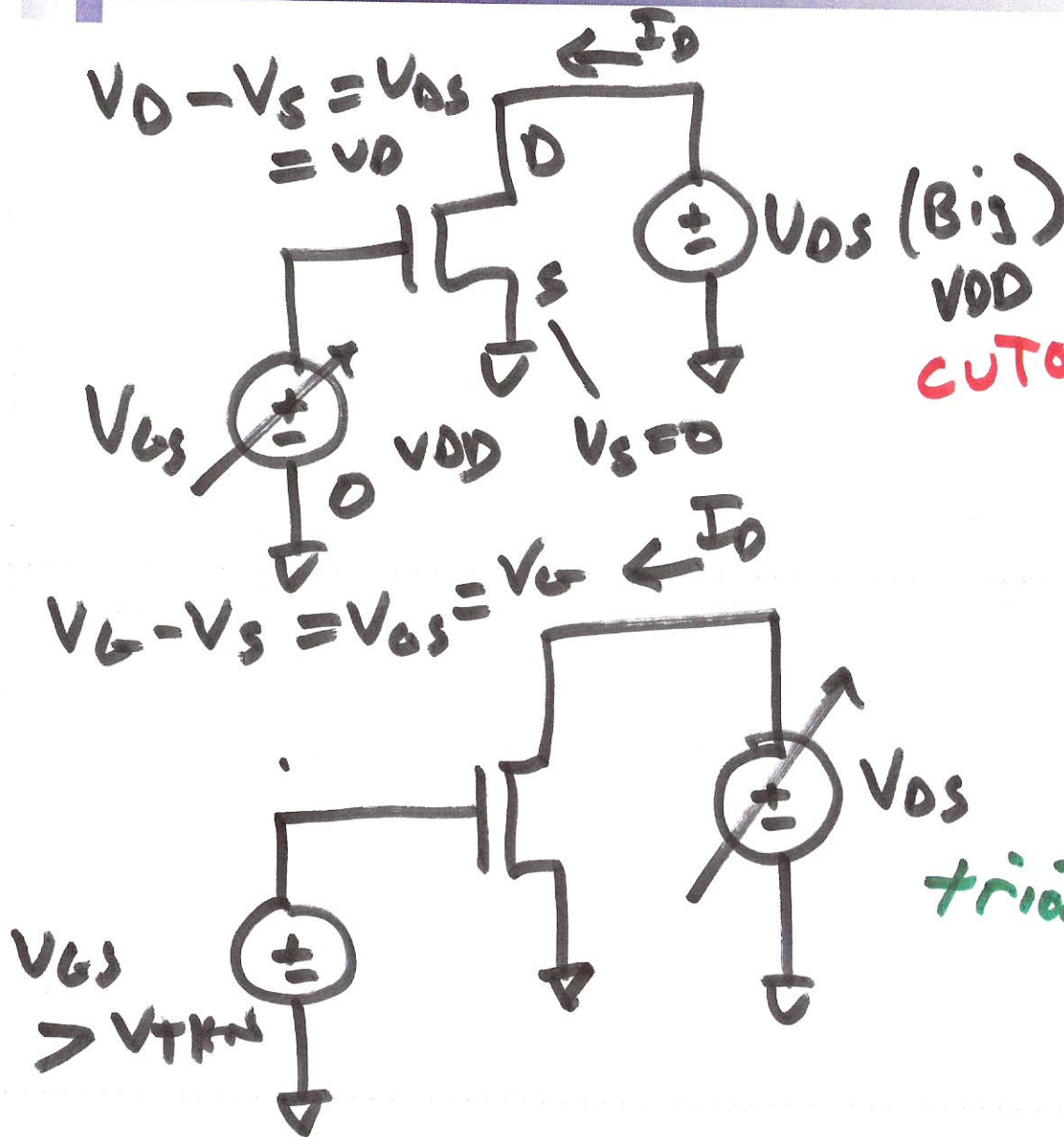



$$V_S - V_G = V_{SG}$$

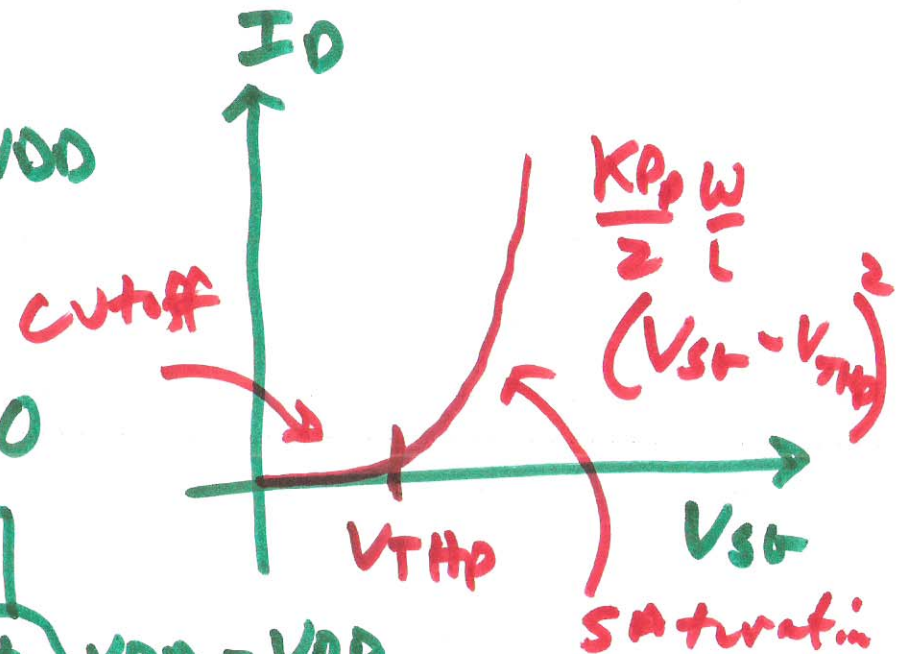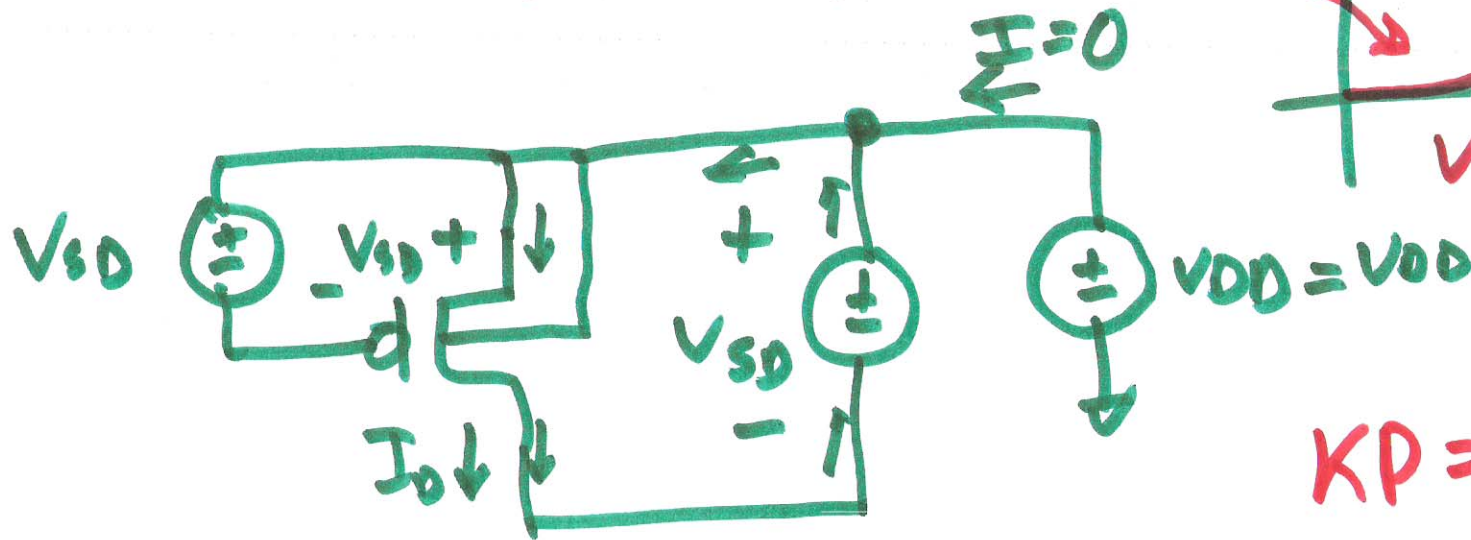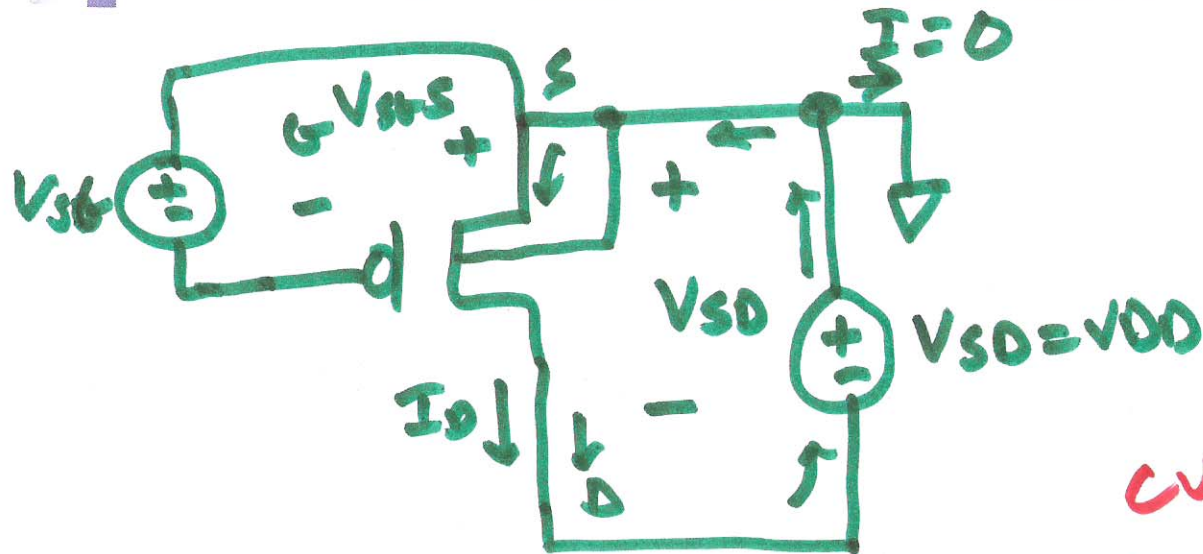



$K_P = \text{transconductance parameter}$


K_{PN}
 K_{PP}

4)

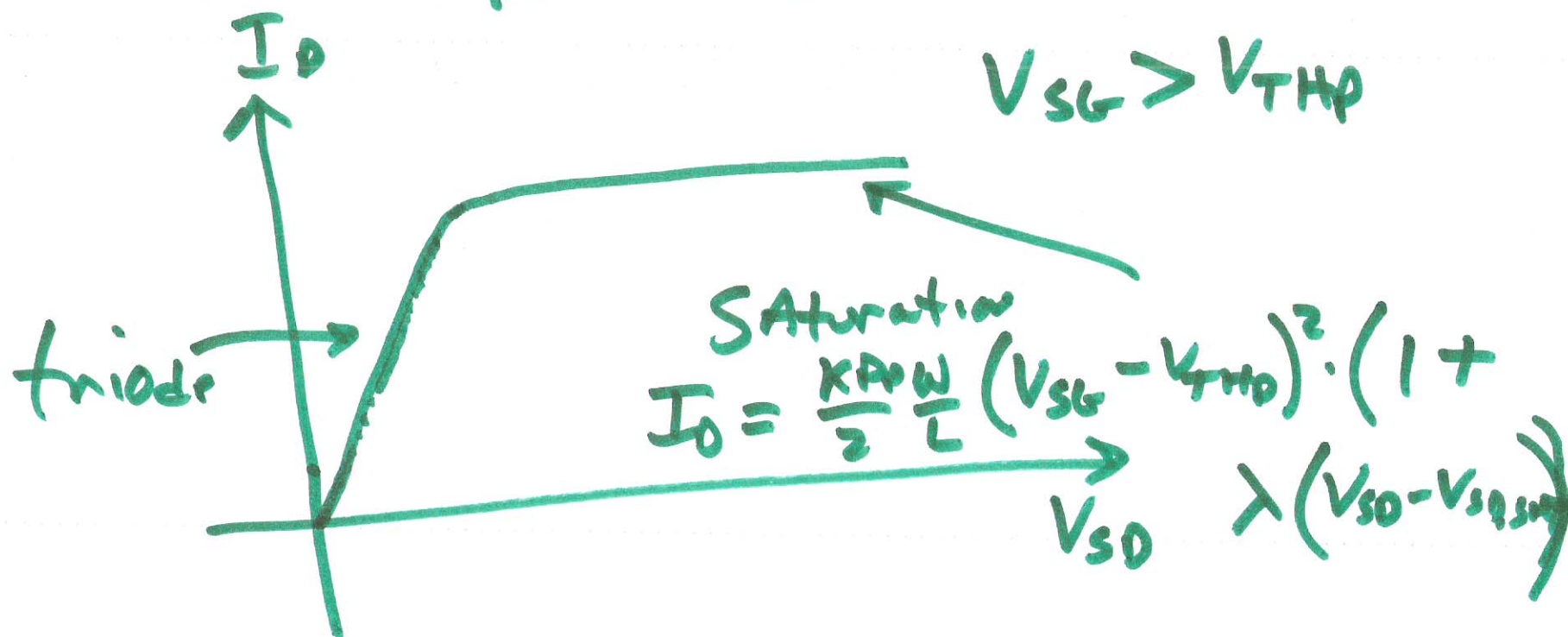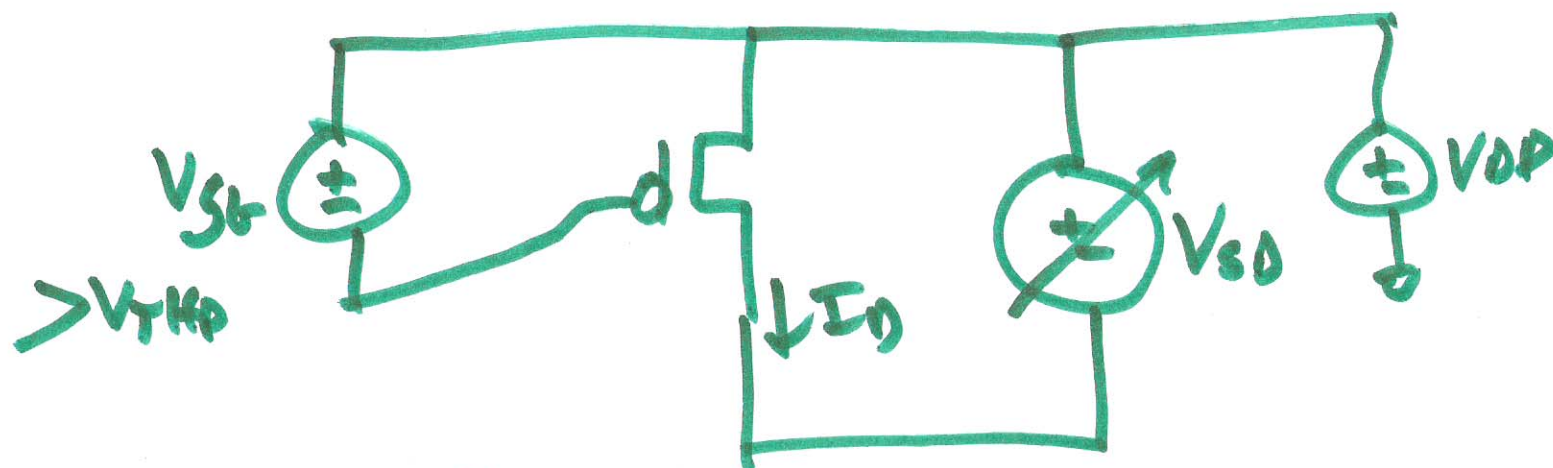


5)

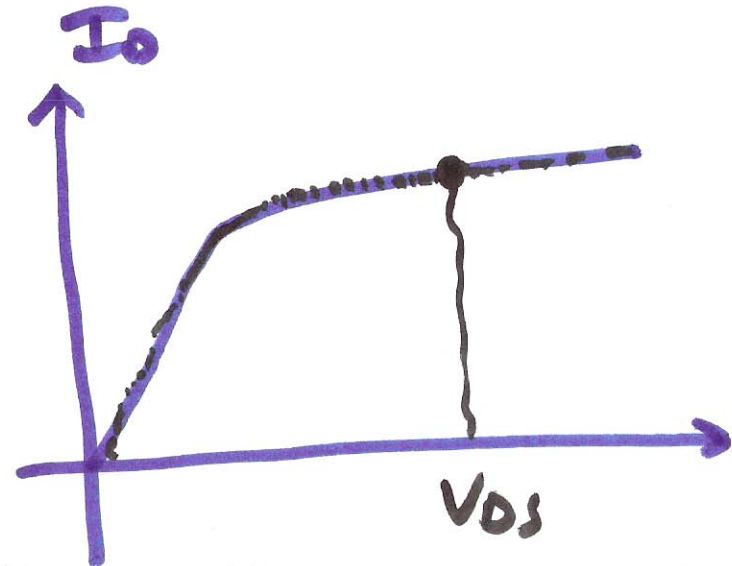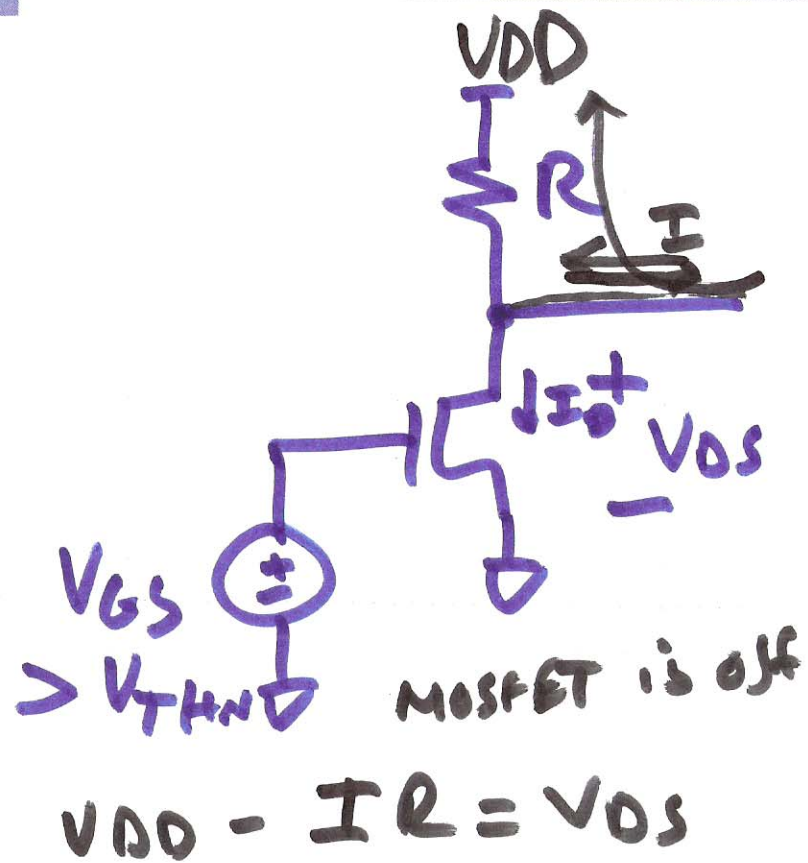


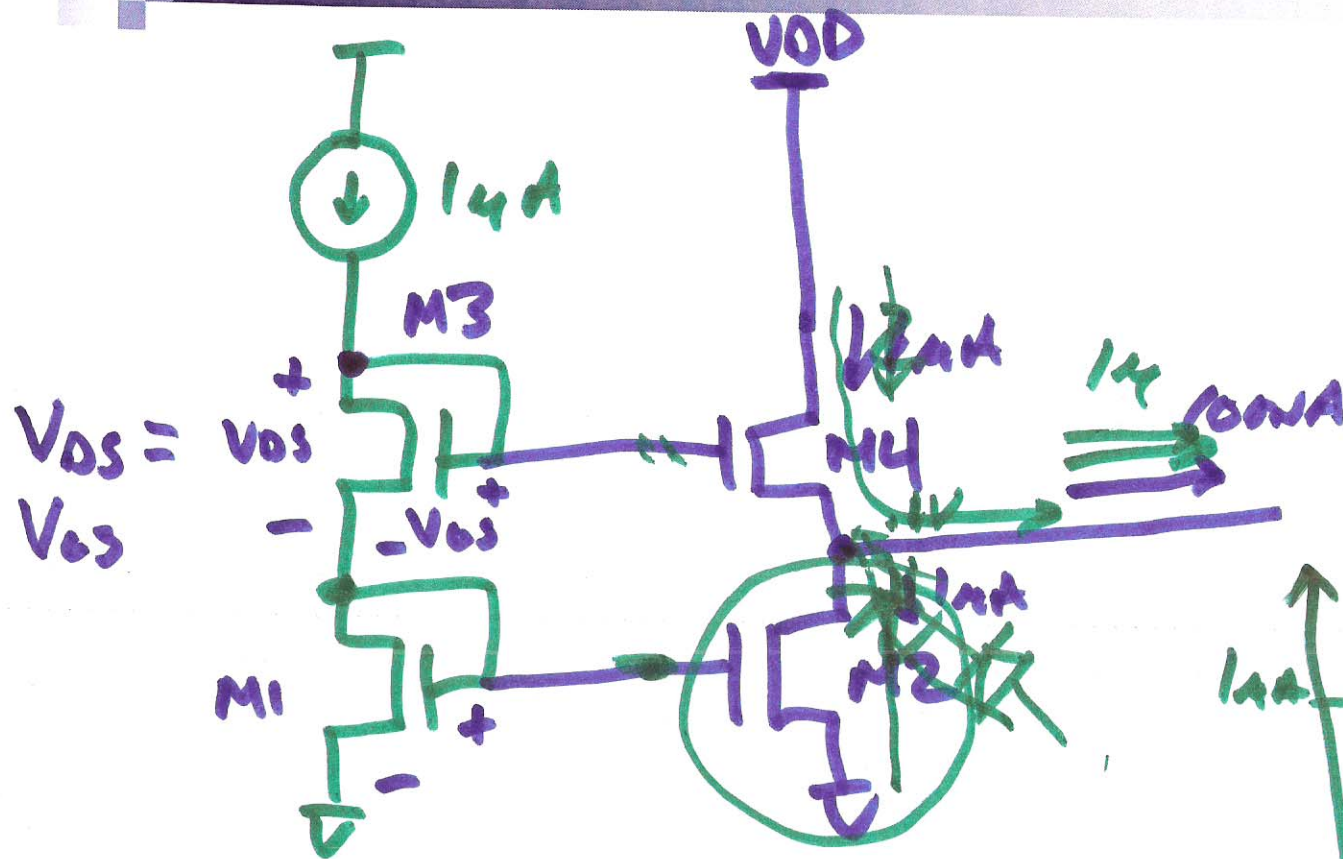


$$I_D = \frac{K_P}{2} \frac{W}{L} (V_{GS} - V_{THN})^2$$
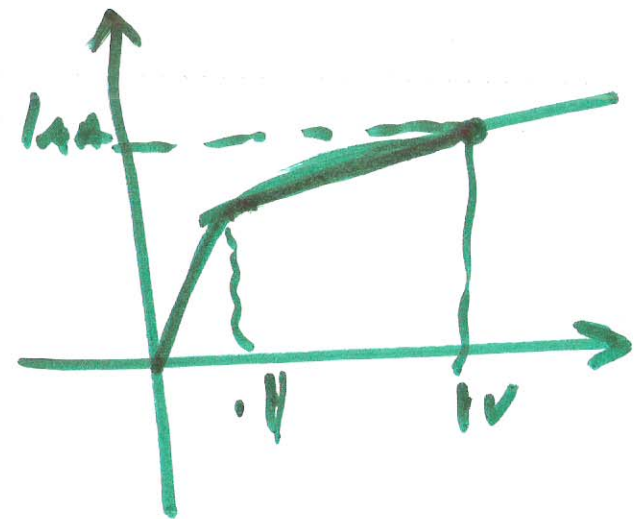
$$V_{GS} = \sqrt{\frac{2I_D L}{K_P W}} + V_{THN}$$



→

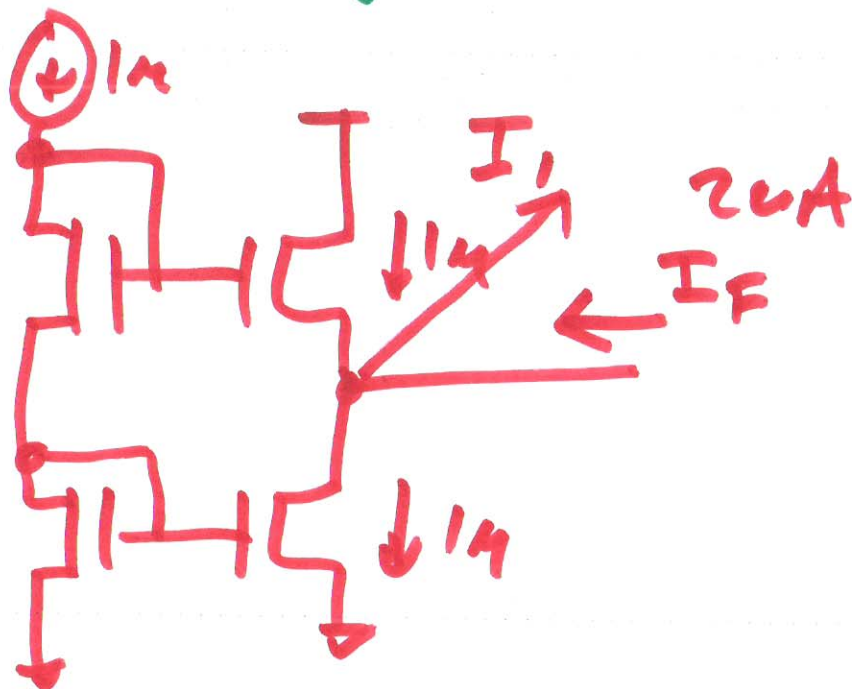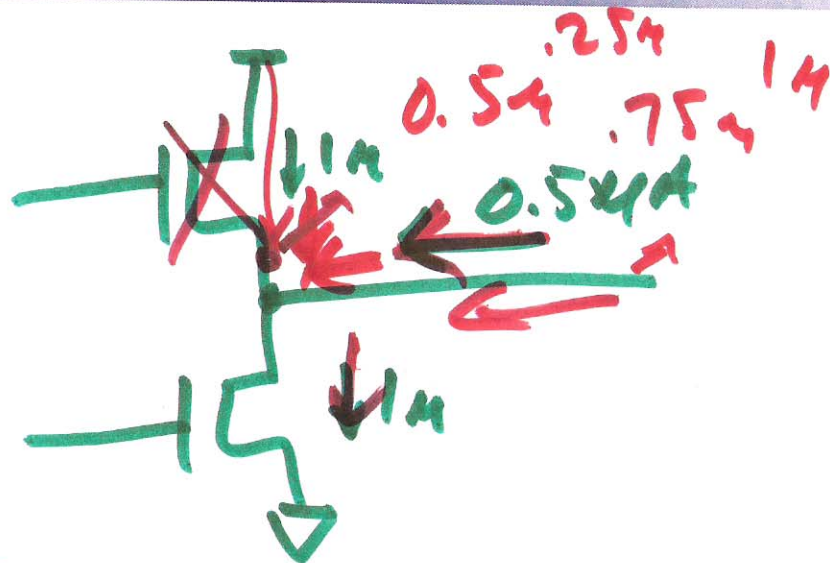


$$I_1 + I_F = 1\text{mA}$$

$$\frac{1}{2}\text{mA} + \frac{1}{2}\text{mA} = 1\text{mA}$$

$$0 + 1\text{mA} = 1\text{mA}$$

$$+ 2\text{mA} = 1\text{mA}$$

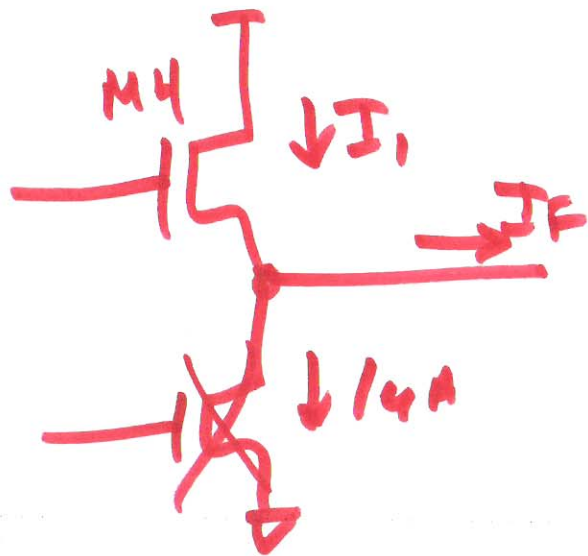

$$I_1 \approx I_F + 14A$$

$$I_1 = 14A + 14A = 28A$$


$$I_F \gg 14A$$

$$I_1 \approx I_F$$


TRANS CONDUCTANCE

$$i_D = \underbrace{I_D}_{DC} + \underbrace{i_d}_{AC}$$
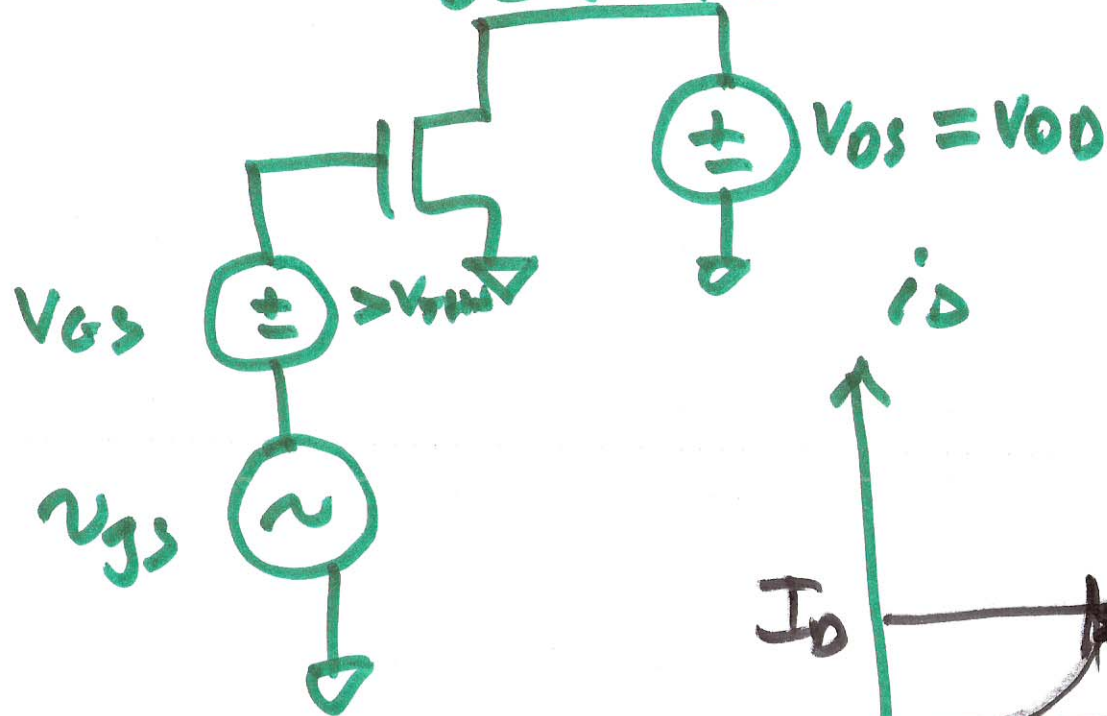
$$v_{GS} = \underbrace{v_{GS}}_{AC} + \underbrace{V_{GS}}_{DC}$$




$$v_{GS, AC} \ll V_{GS, DC}$$

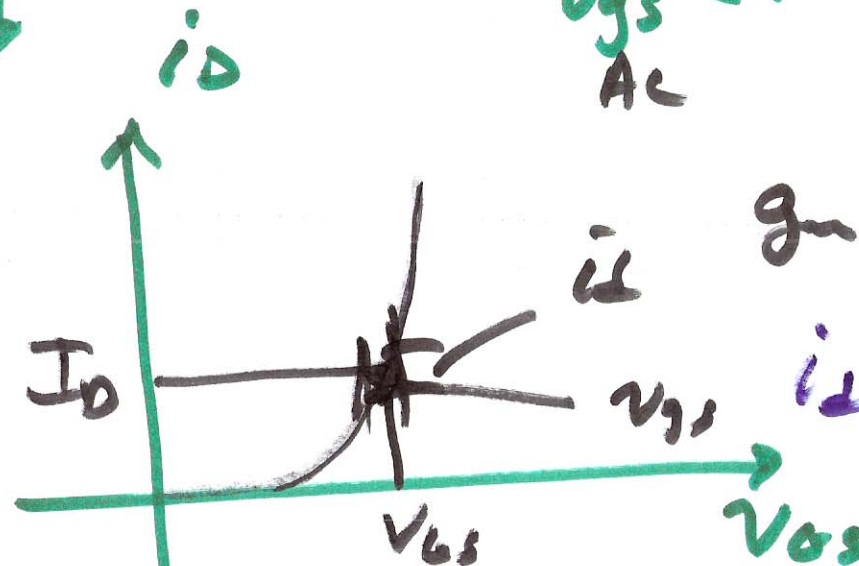

$$g_m = \frac{i_d}{v_{gs}}$$

$$i_d = g_m v_{gs}$$

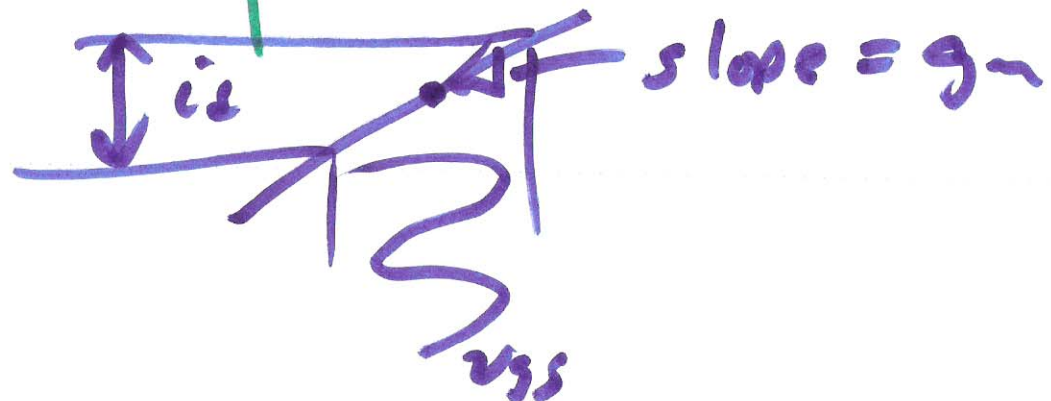

$$\frac{K_P}{2} \cdot \frac{W}{L} \underbrace{(V_{GS} + v_{gs} - V_{TH})}_{v_{GS}}^2 = I_D + i_d = i_D$$

$$\beta_N = K_P \cdot \frac{W}{L}$$

$$g_m = \frac{\partial i_D}{\partial v_{GS}} \bigg|_{\substack{I_D = \text{CONST} \\ V_{GS} = \text{CONST}}} = K_P \cdot \frac{W}{L} (V_{GS} - V_{TH}) \cdot 1 \approx V_{GS} \nearrow V_{GS} \gg v_{gs} = g_m$$


$$I_D = \frac{\beta}{2} (V_{GS} - V_{TH})^2$$

$$g_m = K_P \cdot \frac{W}{L} (V_{GS} - V_{TH}) = \beta (V_{GS} - V_{TH})$$

$$= \sqrt{\frac{2I_D}{\beta}} = \sqrt{\frac{2I_D}{K_P \cdot \frac{W}{L}}}$$

11)

Long channel

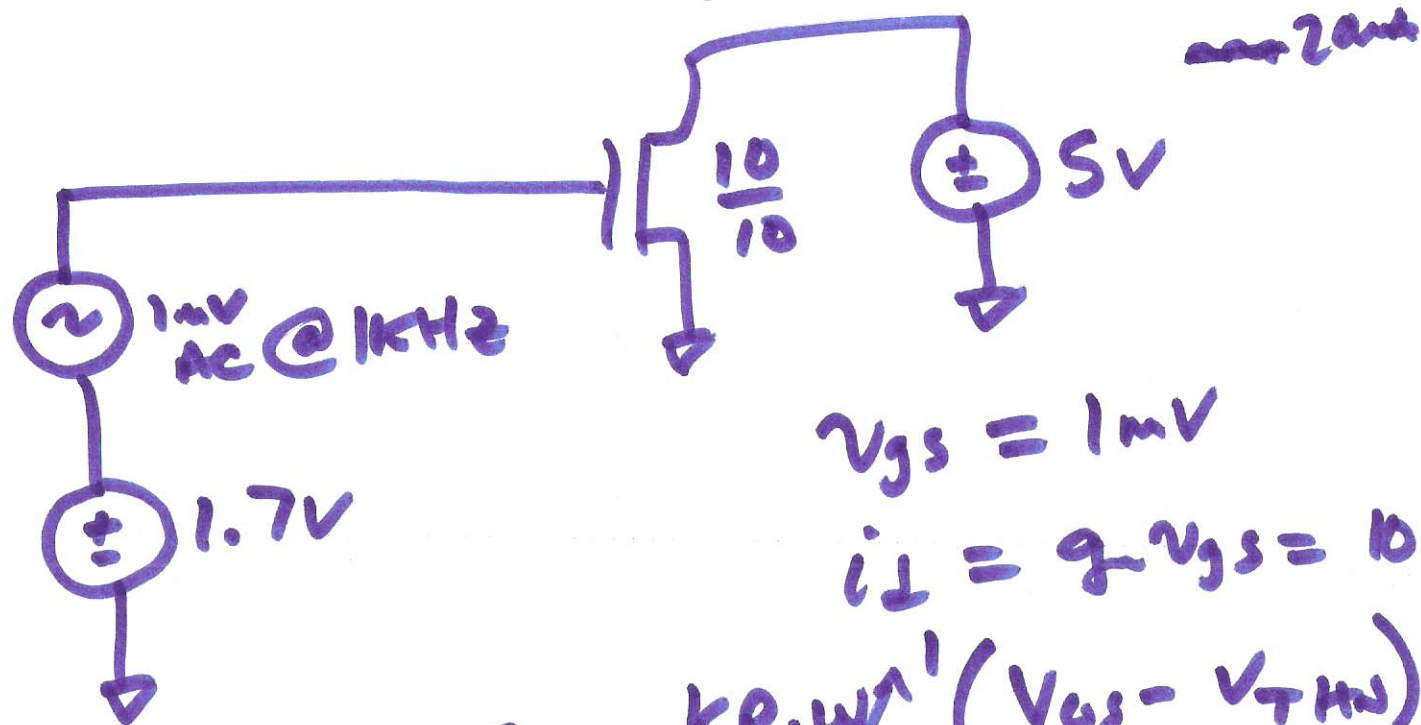

$$V_{gs} = 1\text{mV}$$

$$i_d = g_m V_{gs} = 108\frac{\mu\text{A}}{\text{V}} \cdot 1\text{mV}$$

$$g_m = k_p \frac{W}{L} (V_{gs} - V_{TH}) = 108\frac{\mu\text{A}}{\text{V}}$$

$$= 120\frac{\mu\text{A}}{\text{V}} (1.7 - .8)$$

$$= 108\frac{\mu\text{A}}{\text{V}}$$