
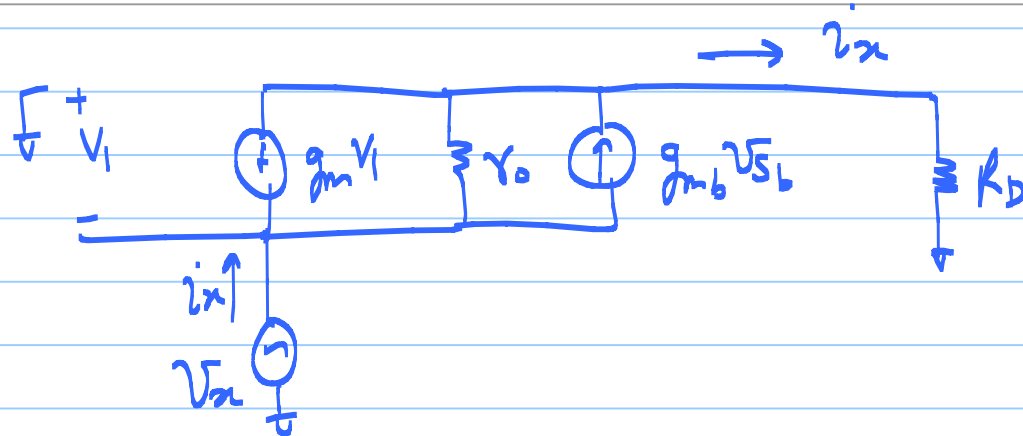


ECE 511 — Lecture 20

Note Title

4/11/2012

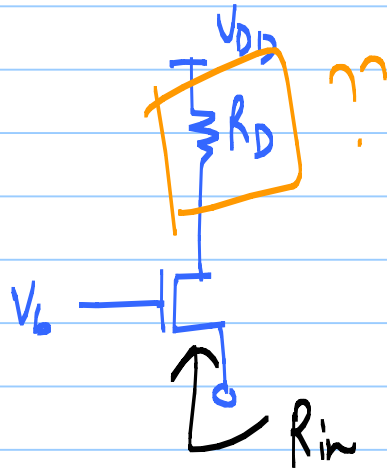

$$R_{in} = \frac{V_x}{i_x} = \frac{R_D + r_o}{1 + (g_m + g_{mb}) r_o}$$

$$\approx \frac{R_D}{(g_m + g_{mb}) r_o} + \frac{1}{g_m + g_{mb}}$$

$$\textcircled{1} \quad R_D \leq r_o$$

$$R_{in} = \frac{1}{(g_m + g_{m_b})} + \frac{1}{g_m} \approx \frac{1}{g_m}$$


$$\textcircled{2} \quad R_D \leq g_m r_o^2$$

$$R_{in} = \frac{g_m r_o^2}{g_m r_o} + \frac{1}{g_m} \approx r_o$$

Opamps


Opamp
(operational amplifier)


VCVS

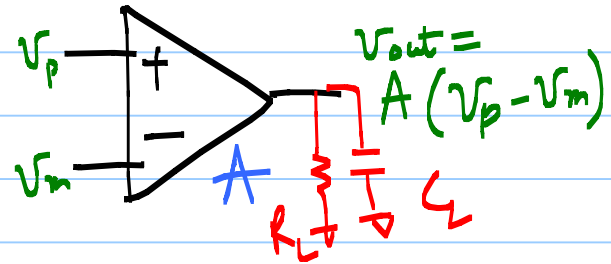

OTA
(operational transconductance amplifier)

VCES

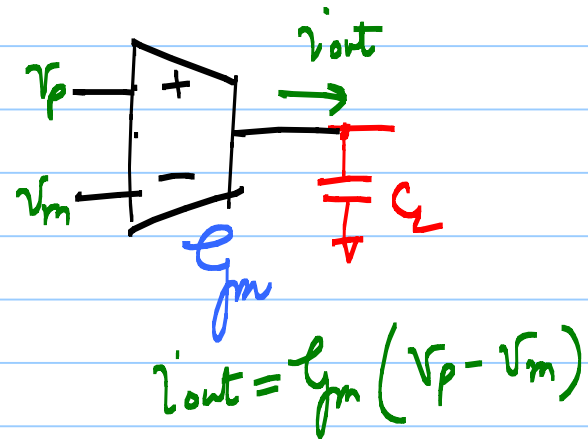


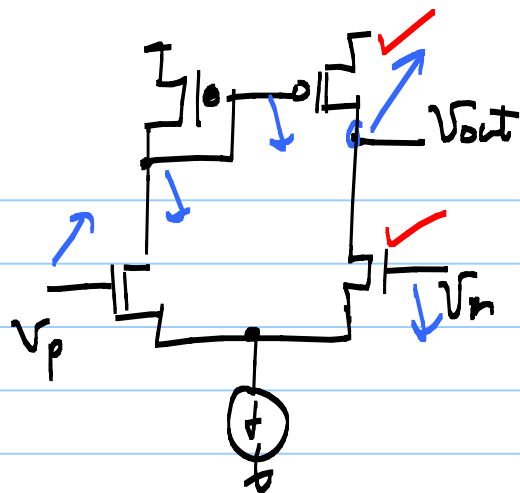



$$+ g_m(\overline{V_{op}} \parallel \overline{V_{in}}) \approx g_m r_o$$

more gain $\rightarrow$ Cascode

Telescopic Amplifier

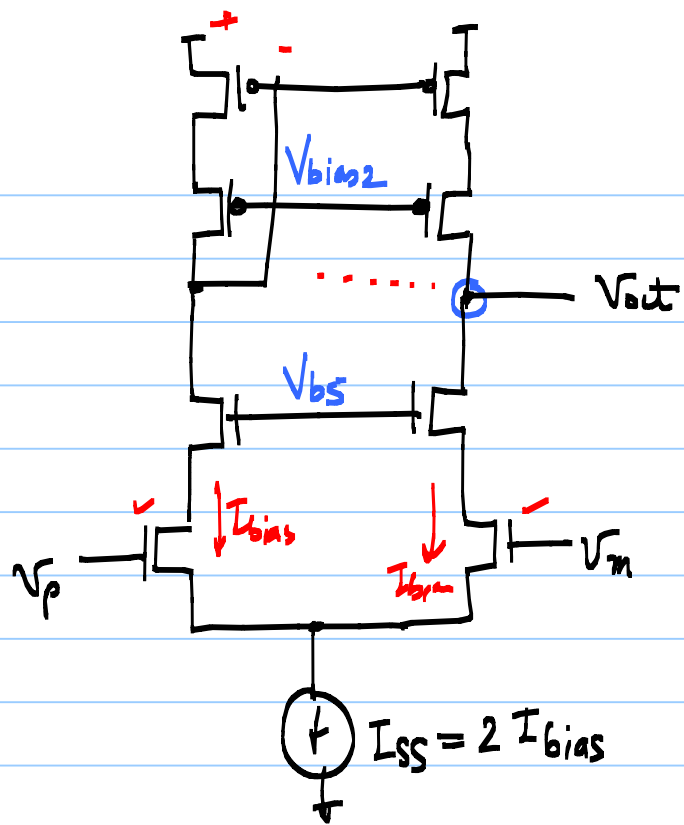


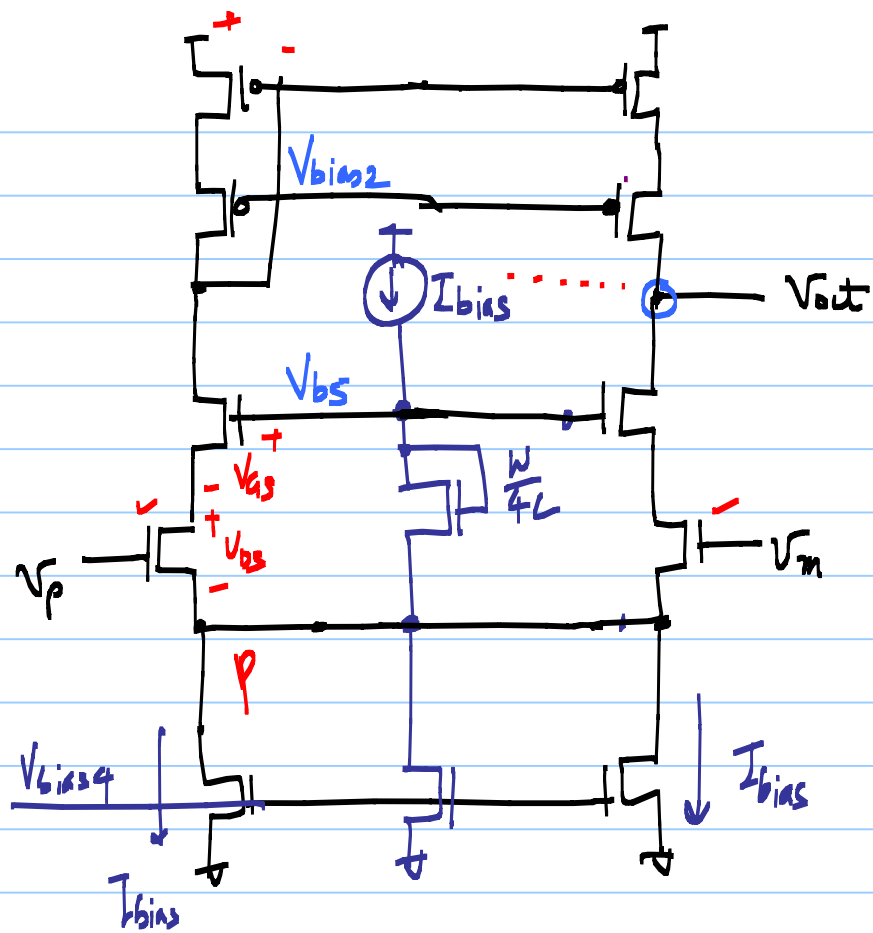

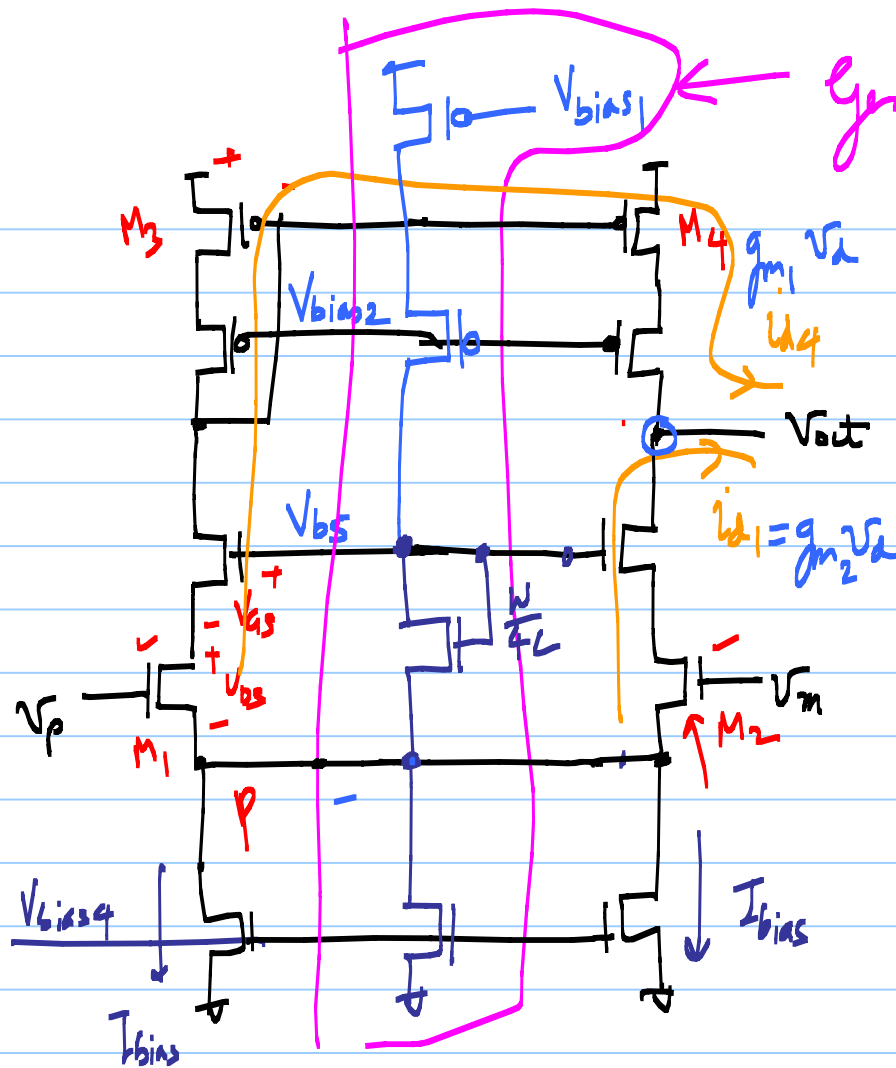

$$A_{V,DM} = g_{m1,2} \cdot \left(\frac{g_{m_n} v_{in}^2}{g_{m_p} v_{in}^2} \right) \parallel \left(\frac{R_{nCas}}{R_{pCas}} \right)$$


Ac → Differential Mode

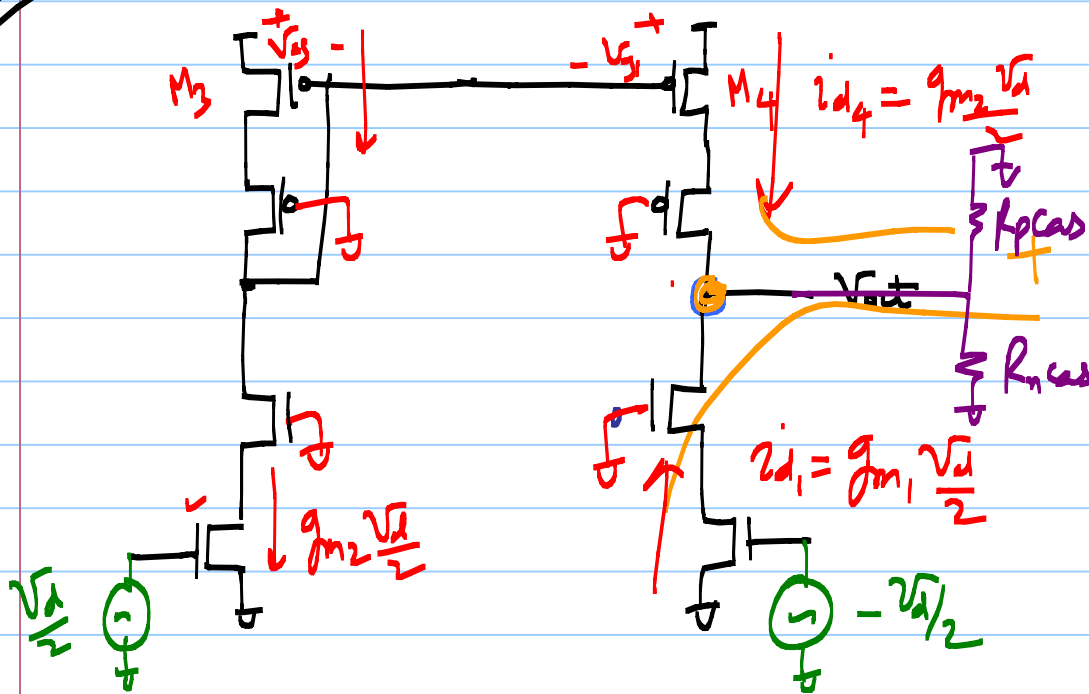



$$v_d = v_p - v_m$$

$$g_m v_d$$

$$v_{out} = g_m v_d (R_{p, cas} || R_{L, cas})$$

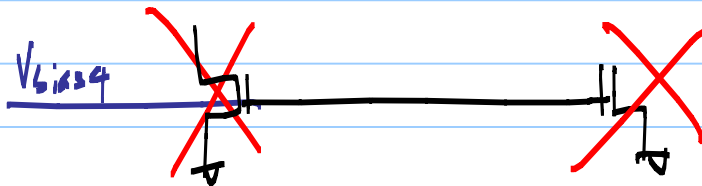


Ac → Comm-mode

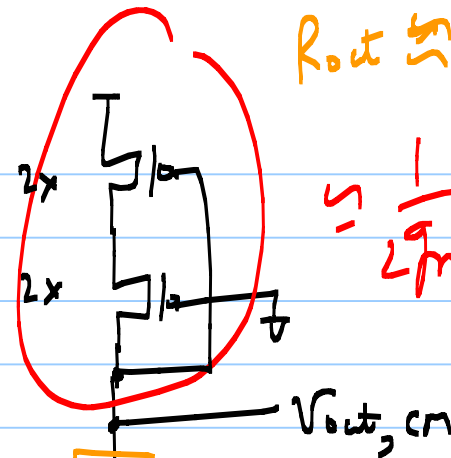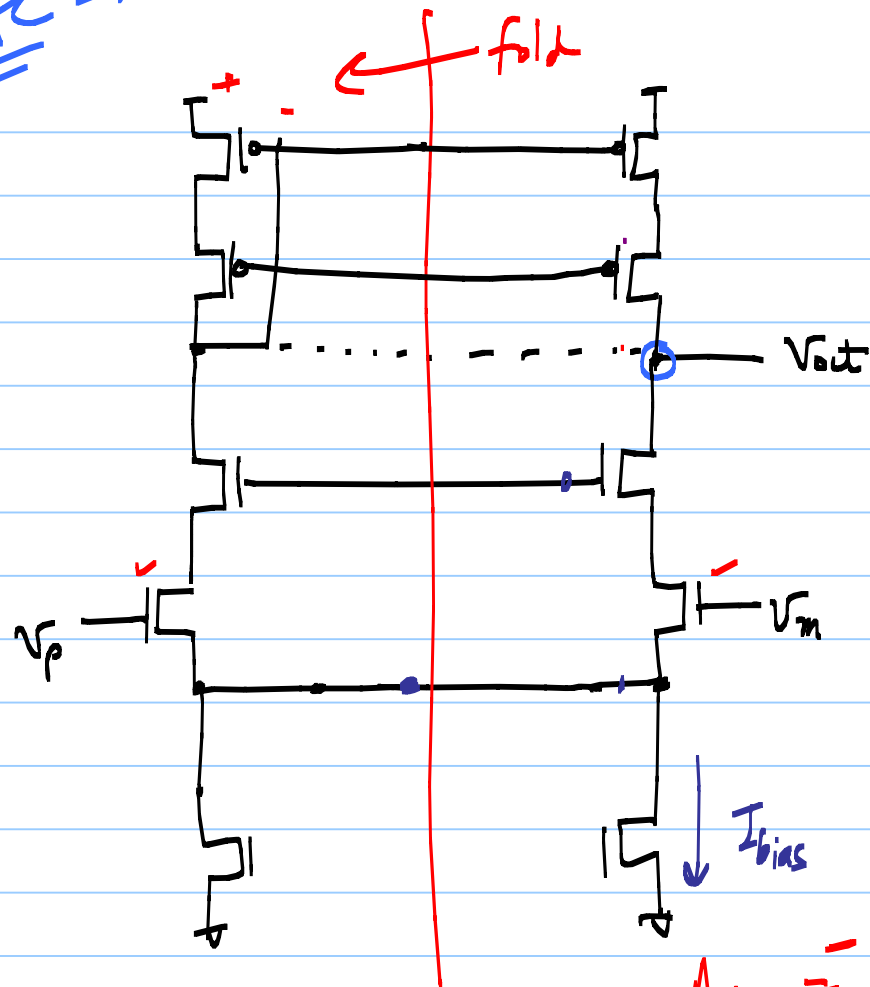

$$R_{out} \approx \frac{1}{2g_{mp}}$$

$$\approx \frac{1}{2g_m}$$

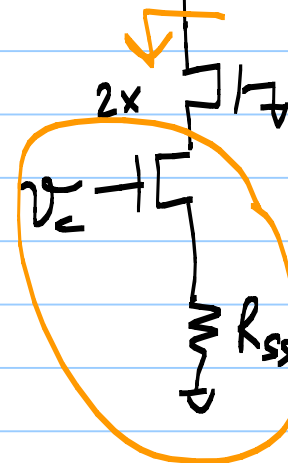

$$g_m = \frac{2g_{mn}}{1 + 2g_{mn} R_{ss}}$$


$$A_{v,cm} = -g_m \cdot R_{out} = -\frac{2g_{mn}}{1 + 2g_{mn} R_{ss}} \cdot \frac{1}{2g_{mp}}$$

$$CMR = 20 \log_{10} \left| \frac{A_{v, on}}{A_{v, cm}} \right|$$

$$V_{cm,in} < V_{DS} + V_{THN}$$

$$= (V_{DD} - V_{SL}) - (V_{DS,sat}) + V_{THN}$$
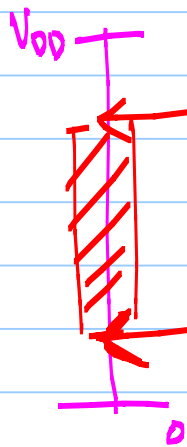
$$I_{CMR} \in \left[V_{GS} + \underbrace{2V_{DS,sat}}, \quad V_{DD} - V_{SL} - \underbrace{V_{DS,sat}} + V_{THN} \right]$$




lower I_{CMR} & output swing

Output Swing


$$(V_{in,cm} - V_{THN} + V_{DS,sat}) \leq V_{out} \leq (V_{DD} - 2V_{DS,sat})$$


Performance Parameters :

① Gain :

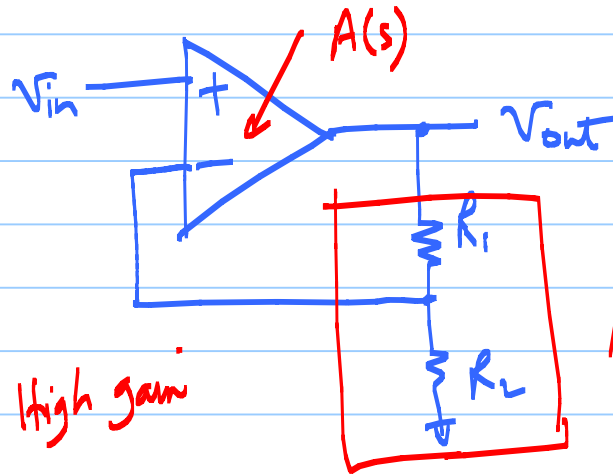

$$\beta = \frac{R_2}{R_1 + R_2} < 1$$

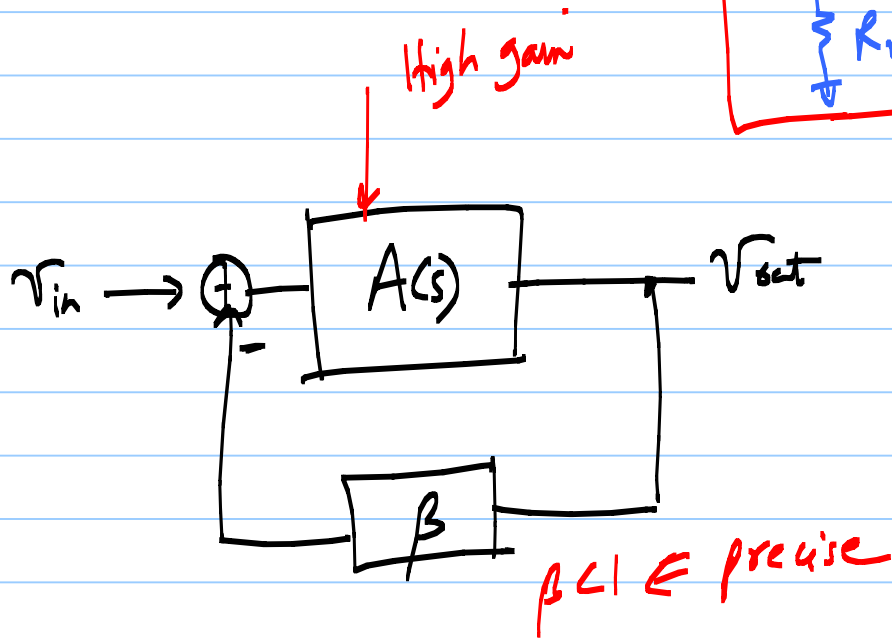

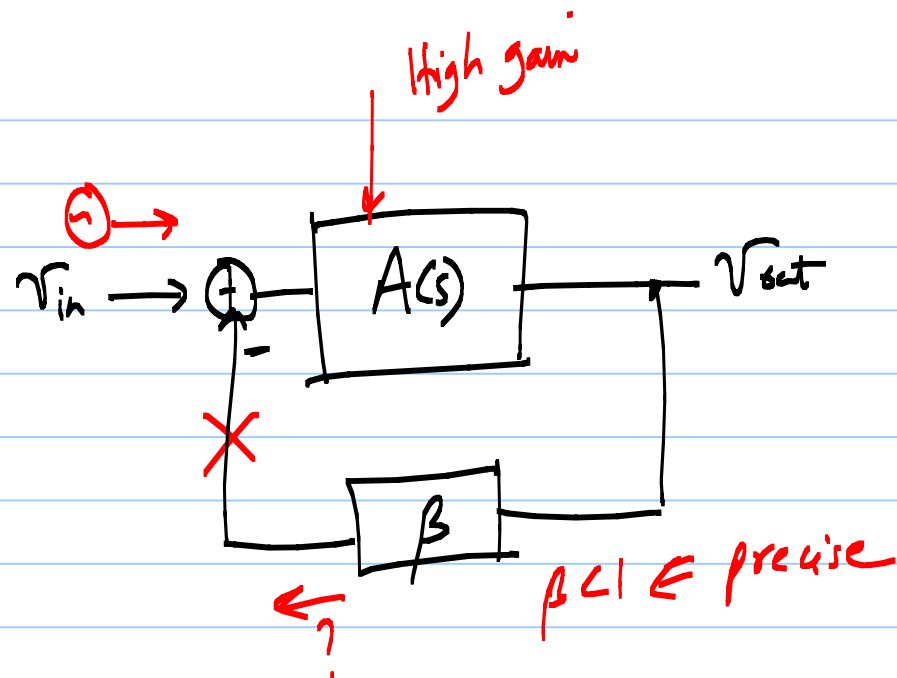

$A\beta \leftarrow \text{open-loop response} \rightarrow \text{loop-response}$

$$(v_{in} - \beta v_{out}) A(s) = v_{out}$$

$$\frac{V_{out}}{V_{in}}(s) = \frac{A(s)}{(1+A\beta)s} = \frac{A}{1+A\beta} \leftarrow A_{CL}(s)$$

closed-loop
response

Assume $A(s) = A$

$$A_{CL} = \frac{V_{out}}{V_{in}} = \frac{A}{1+A\beta} = \frac{1}{\beta} \cdot \frac{1}{(1 + \frac{1}{A\beta})}$$

$$A_{CL} = \frac{1}{\beta} \left[1 - \frac{1}{A\beta} \right] \approx \frac{1}{\beta} \leftarrow$$

if $A\beta \gg 1 \leftarrow$ loop gain is ∞

$$|x| < 1$$

$$\frac{1}{1+x} \approx 1-x$$

$$A_{CL} = \frac{1}{\beta} \left[1 - \underbrace{\frac{1}{A\beta}}_{\text{relative gain error}} \right] = A_{CL, \text{ideal}} \underbrace{\left(1 - \epsilon \right)}_{\text{gain error}}$$

ideal A_{CL}

$$\epsilon \downarrow \Rightarrow A\beta \uparrow \Rightarrow A \uparrow$$

fr

$$\epsilon < 1\%$$

$$\Rightarrow A > 1000 = 60 \text{ dB}$$

② $A(s) = \frac{A}{(1 + \frac{s}{\omega_0})}$ $\leftarrow$ Dominant pole model