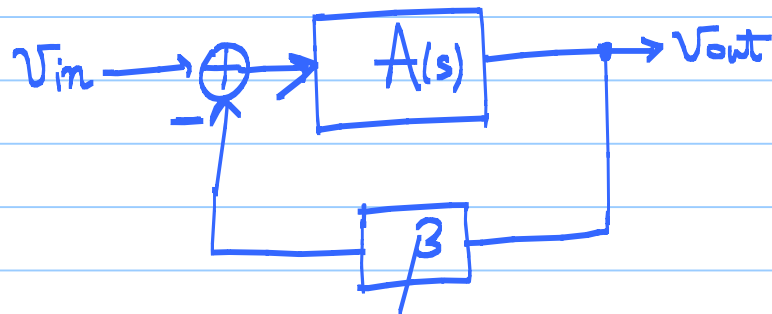


ECE 511 - Lecture 21

Note Title

4/18/2012



loop-gain $\rightarrow A\beta$

Ideal CL gain $\rightarrow A_{CL} = \frac{1}{\beta}$ $\leftarrow$ when $|A\beta| \gg 1$

finite 'A' $\Rightarrow A_{CL} = \frac{1}{\beta} (1 - \epsilon)$ $\swarrow$ gain error
 $\uparrow$ $\frac{1}{A\beta}$

Saturday (4/21)


Project Help
Session

MEC 206

3 PM $\rightarrow$ 4 PM

②
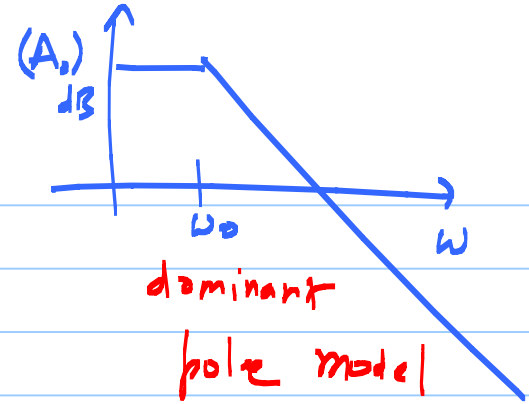
$$A(s) = \frac{A_0}{\left(1 + \frac{s}{\omega_0}\right)}$$



$$\frac{V_{out}}{V_{in}}(s) = \frac{A(s)}{1 + \beta A(s)}$$

$$= \frac{A_0}{(1 + \beta A_0) + \frac{s}{\omega_0}}$$

$$= \frac{\left(\frac{A_0}{1 + \beta A_0}\right)}{1 + \frac{s}{\omega_0(1 + \beta A_0)}}$$

$$\approx \frac{1}{\beta} \text{ for } A_0\beta \gg 1$$

$$= \frac{A_{CL}}{\left(1 + \frac{s}{\omega_0(1 + \beta A_0)}\right)}$$

closed loop pole (ω_{CL})

$$\omega_{3dB} = (1 + \beta A_0) \omega_0$$

$$\approx \beta A_0 \omega_0$$

$$= \frac{1}{A_{CL}} \cdot \omega_{un}$$



Constant
for the
opamp


$$\omega_{un} = \omega_{3dB} \cdot A_{CL}$$





$\uparrow$ $\downarrow$ $\uparrow$
 $2\pi f_{un}$

gain-BW
trade off

$$A_0 \beta \gg 1$$

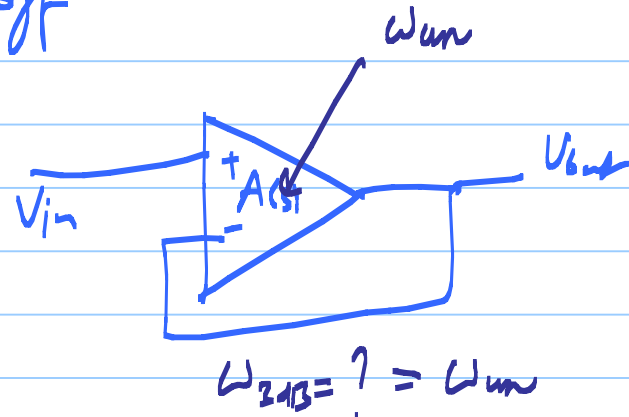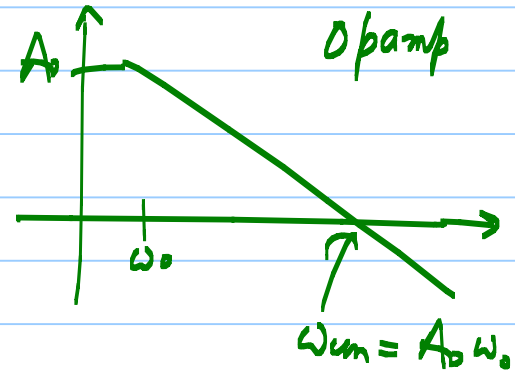

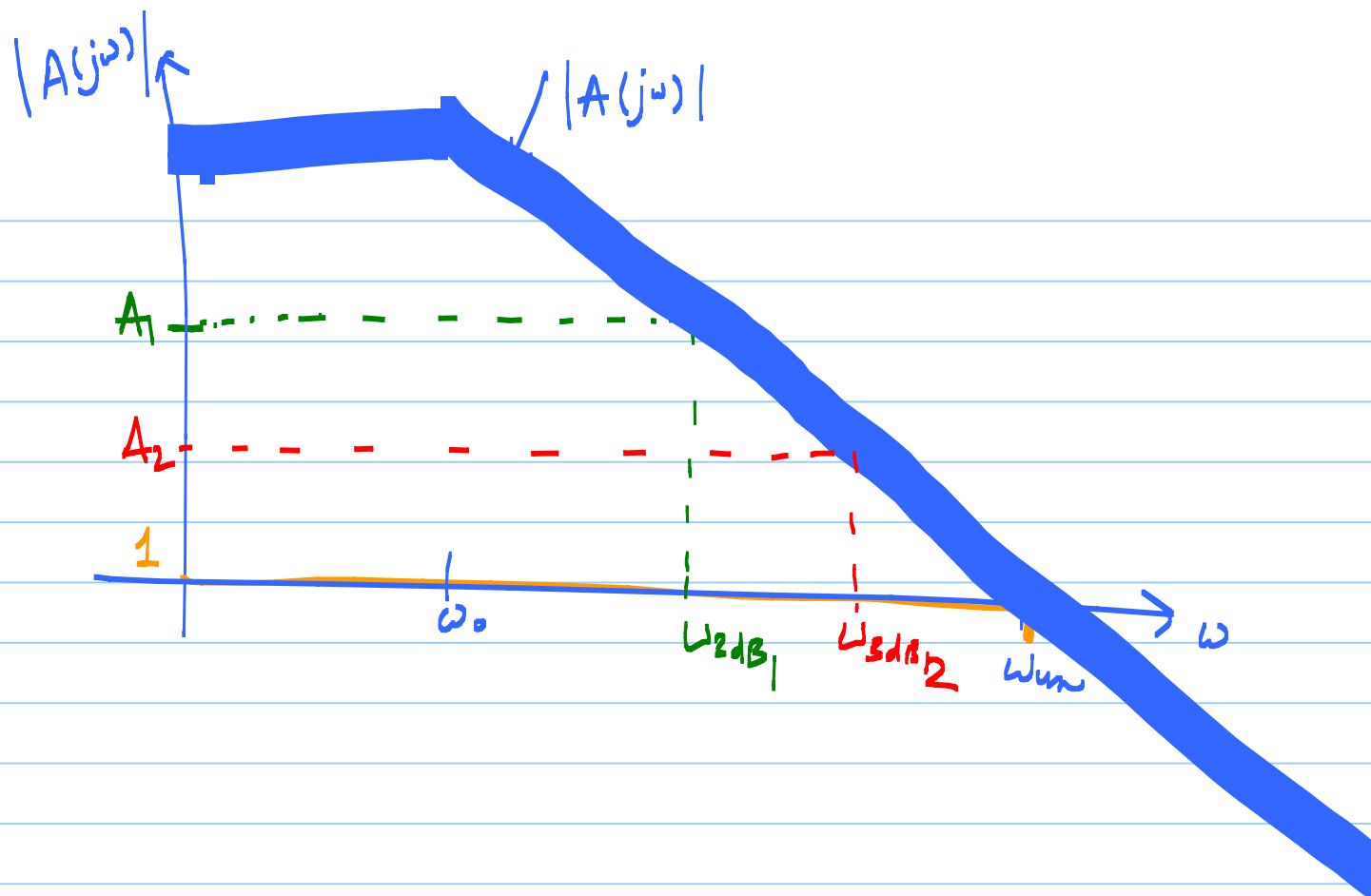

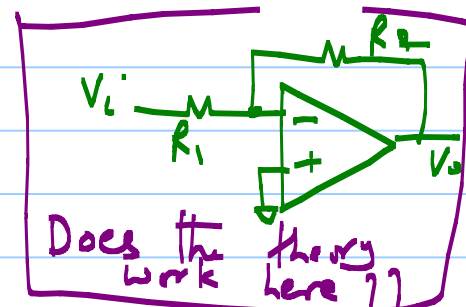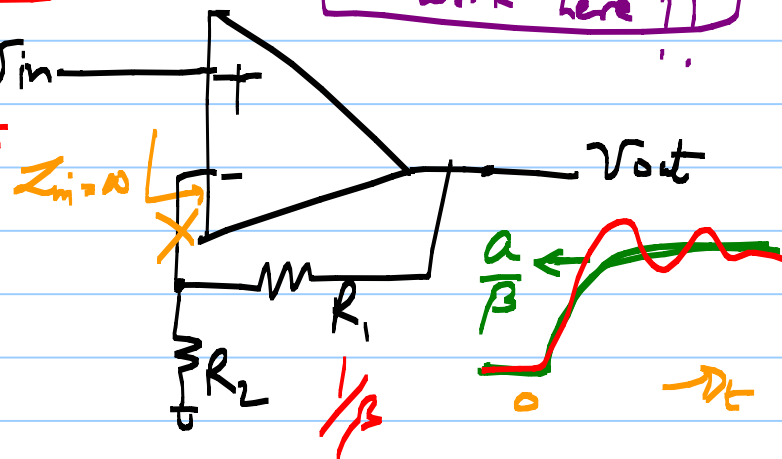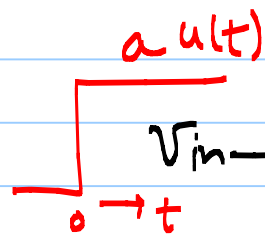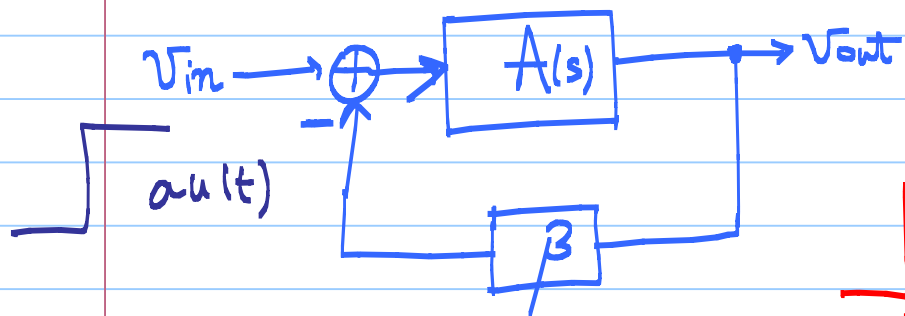


$$\beta = \frac{R_2}{R_1 + R_2}$$

$$V_{in}(t) = a u(t) \leftrightarrow \frac{a}{s}$$

$$V_{out}(t) = \mathcal{L}^{-1} \left(\frac{a}{s} \cdot \frac{1}{\beta} \cdot \frac{1}{(1 + s/\omega_{3dB})} \right)$$

$$= \frac{a}{\beta} \left[1 - e^{-t/\tau} \right] u(t)$$
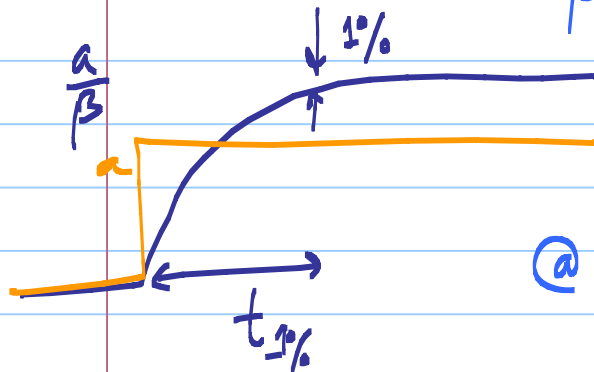
$$\tau = \frac{1}{\omega_{3dB}} = \frac{1}{\omega_{uni} \cdot 1/\beta}$$



Linear settling
'1st order system'
↳ Single-pole opamp
model

$$@ t = t_{1\%}$$

$$1 - e^{-t/\tau} = 0.99$$

$$\Rightarrow \boxed{t_{1\%} = 4.6 \tau}$$

$$\approx 5 \cdot \tau \quad \begin{matrix} \nearrow \omega_{3dB} \\ \downarrow \omega_{uni} \end{matrix}$$

for 1% settling of S_{ns}



$$\frac{1}{\beta} = 10$$

$$\omega_{um} = \frac{1}{\beta} \cdot \omega_{3dB} \quad \leftarrow \frac{1}{2}$$

$$= \frac{1}{\beta \tau} \quad \tau = \frac{S_{ns}}{4.7} = 1.09 \text{ ms}$$

$$= 9.21 \times 10^9 \text{ rad/s}$$

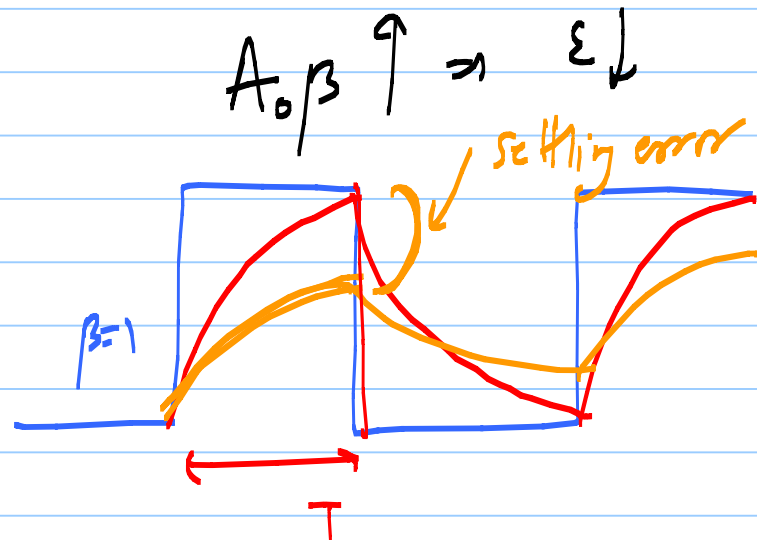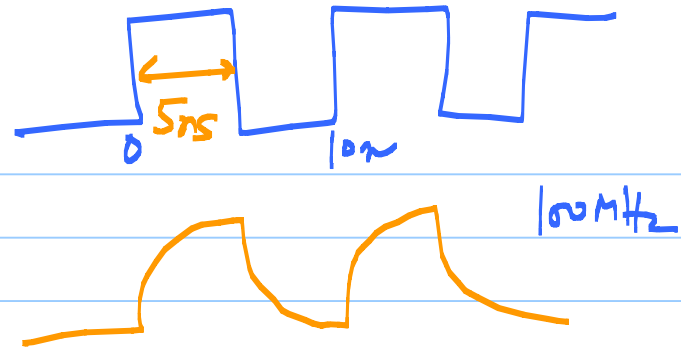
$$f_{um} = \frac{\omega_{um}}{2\pi} = \boxed{1.47 \text{ GHz}}$$



③ Large-signal BW

↳ transient simulations for large signals
AC analysis doesn't help much.

④ Output swing

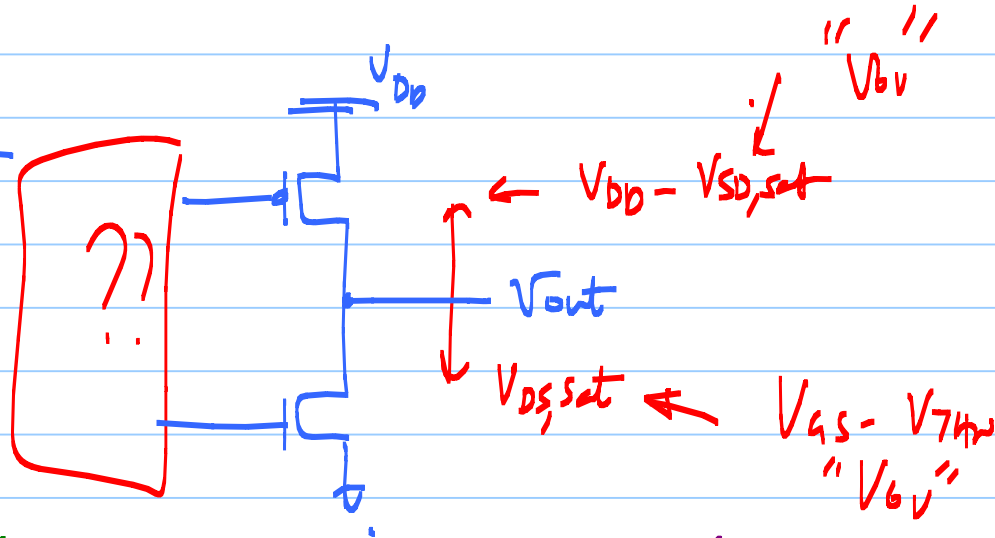


trade-off with
 $V_{ov} \leftarrow f_T$
(Speed)

$$f_T \propto \frac{V_{ov}}{L} \leftarrow$$

⑤ slowing.

Small input


$a_1 u(t)$

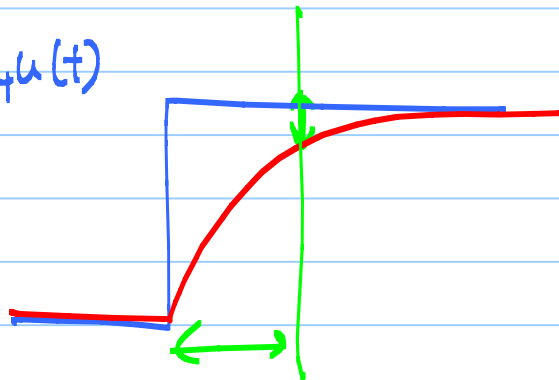

$$\frac{a}{\beta} (1 - e^{-t/T_s})$$

ε_{settling}

$a_2 u(t)$

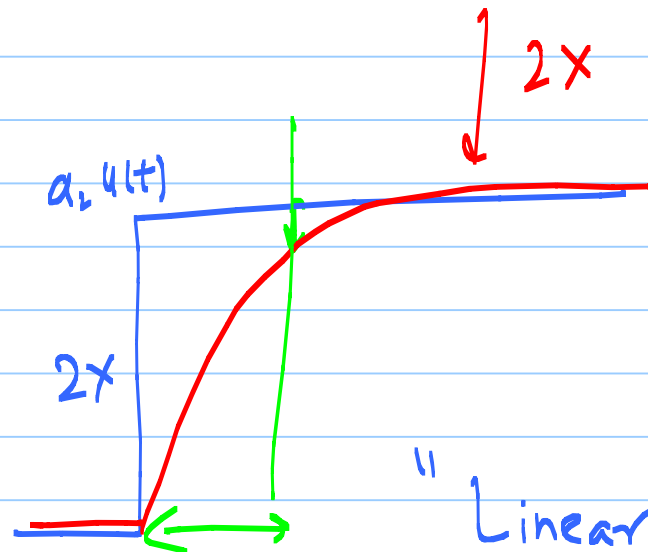



"Linear settling"



↑ slowing


← non-linear settling

$$\beta = 1$$

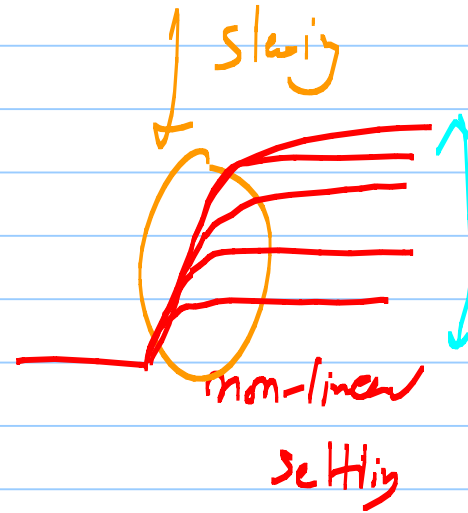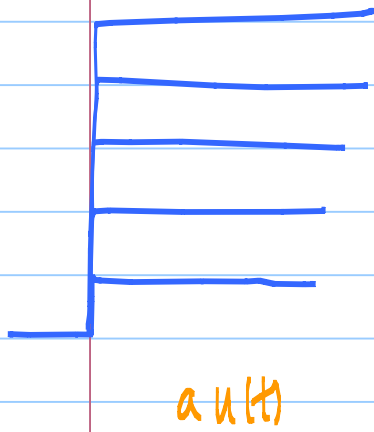

⑨ Noise & offset → ECE 614

⑩ Supply rejection

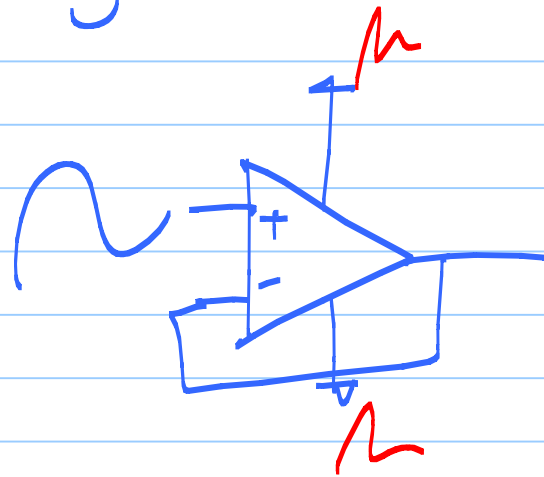


$PSRR^+$
 $PSRR^-$

Stability & Frequency Compensation

Closed-loop Tf




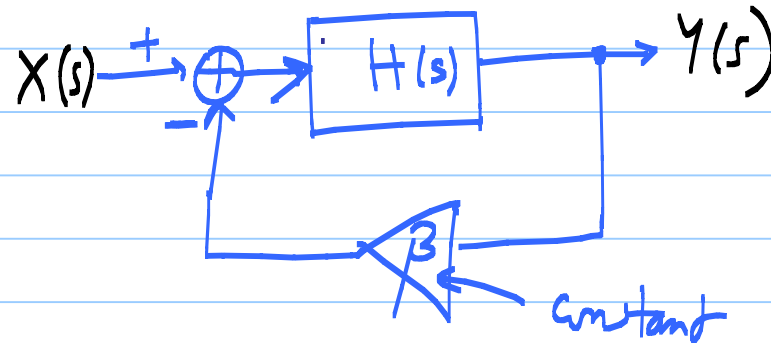
$$\rightarrow \frac{Y}{X}(s) = \frac{H(s)}{1 + \boxed{\beta H(s)}} \leftarrow \text{open-loop Tf}$$






If $\beta H(s=j\omega_1) = -1$ & $A_{CL}(s) = \infty$ $\beta \leq 1$

$\rightarrow$ circuit starts oscillating at ω_1

$$\Rightarrow \text{Here } \begin{cases} |\beta H(j\omega_1)| = 1 \\ \angle \beta H(j\omega_1) = 180^\circ \end{cases} \rightarrow \text{Barkhausen's Criterion}$$

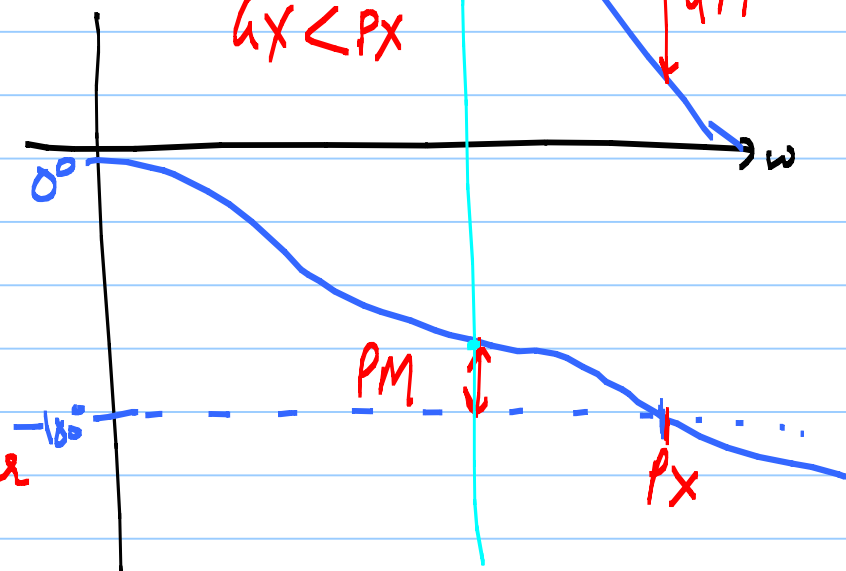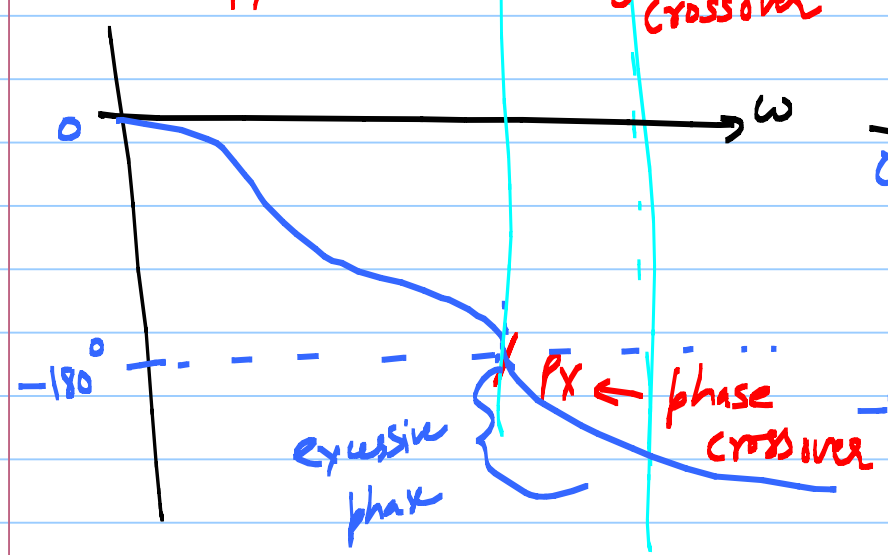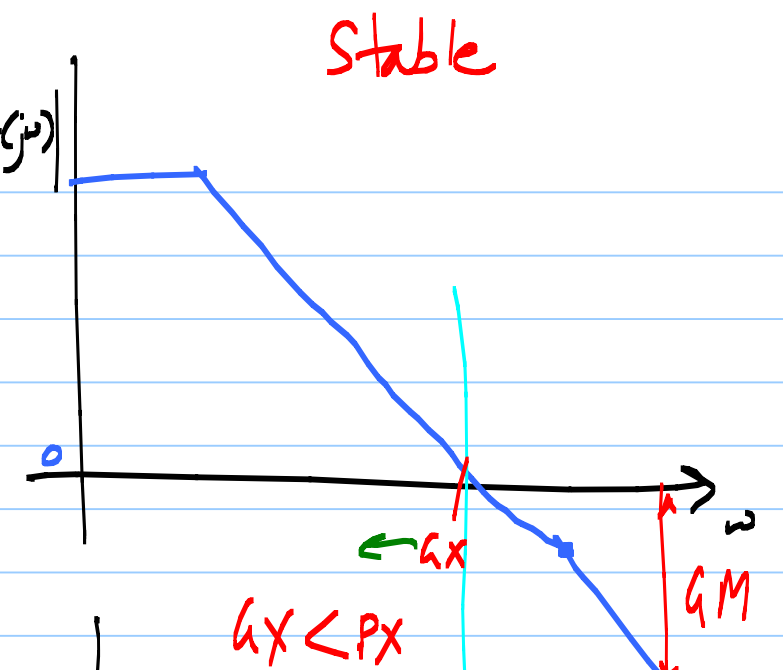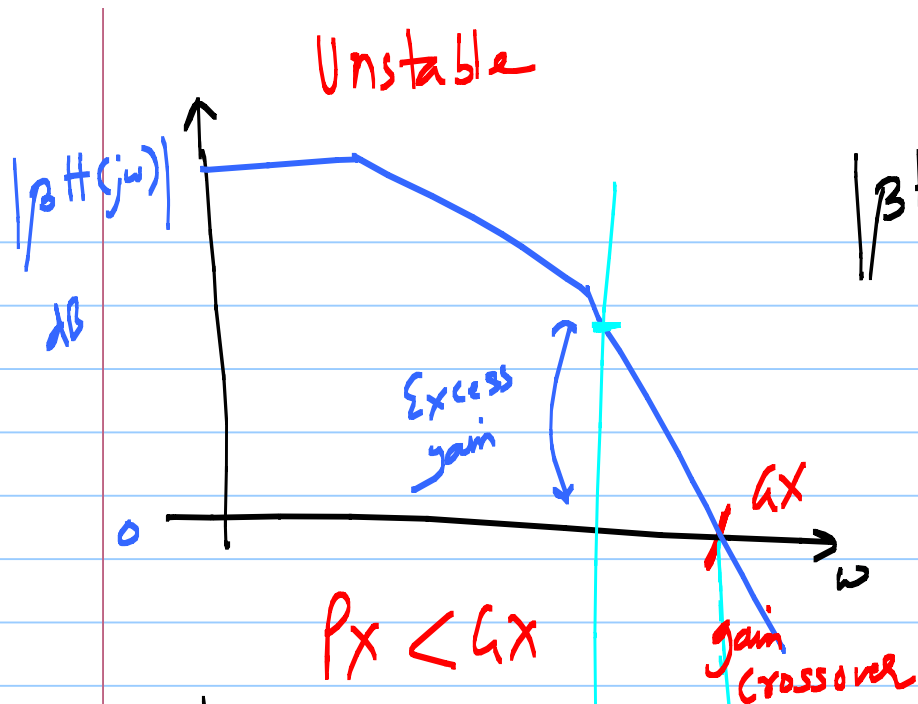

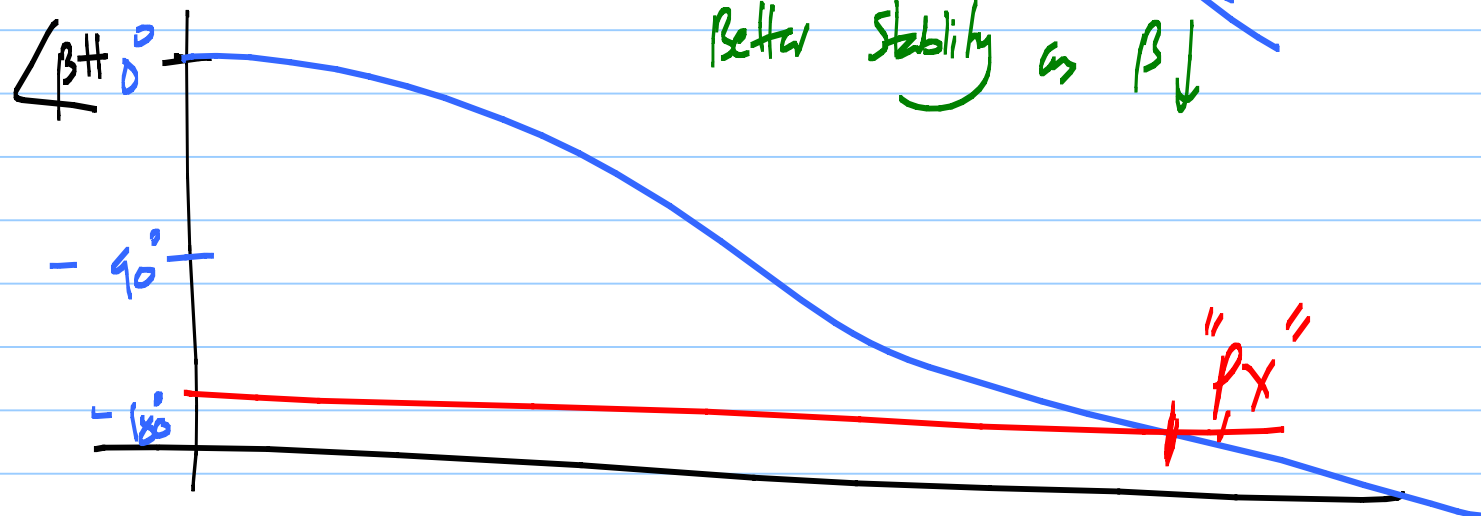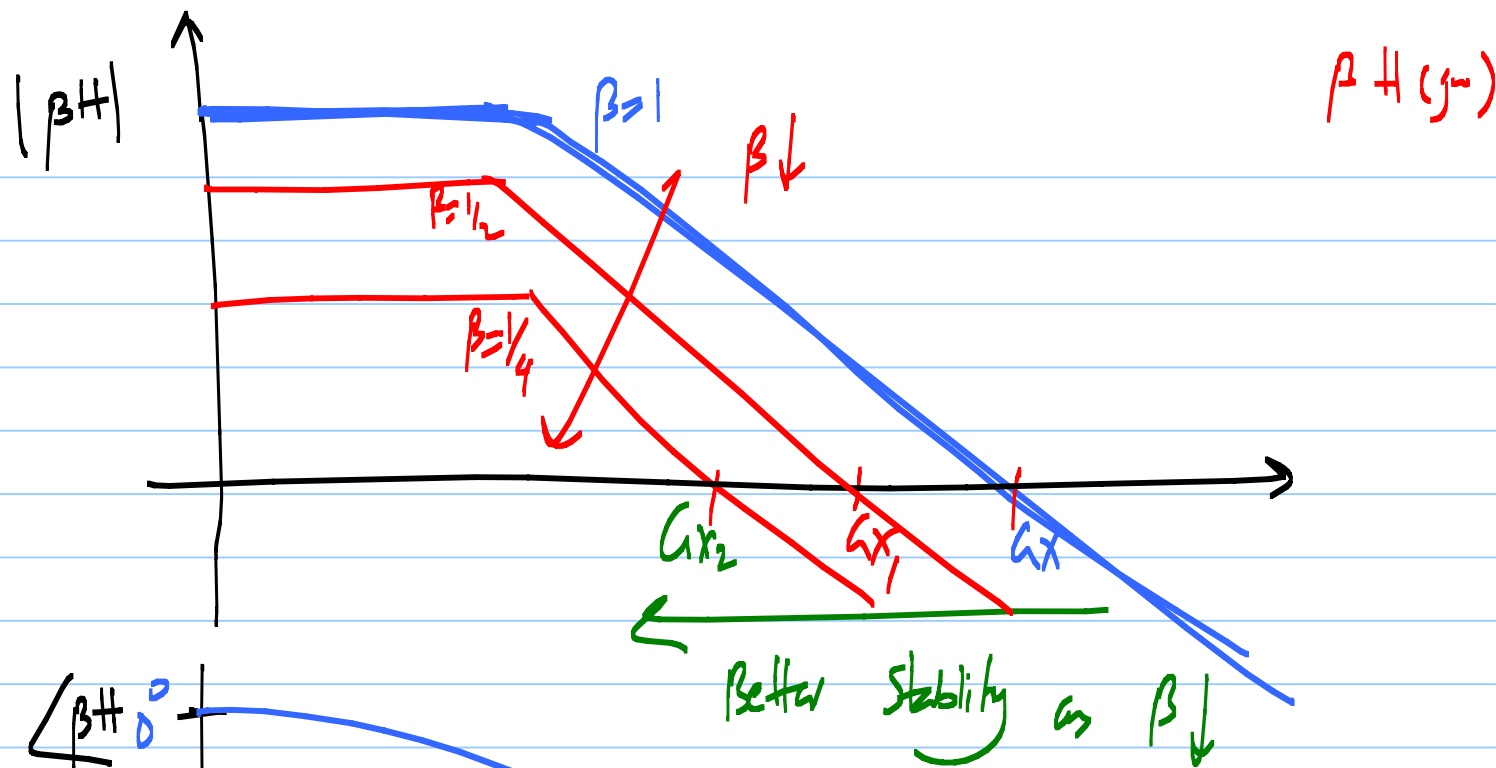

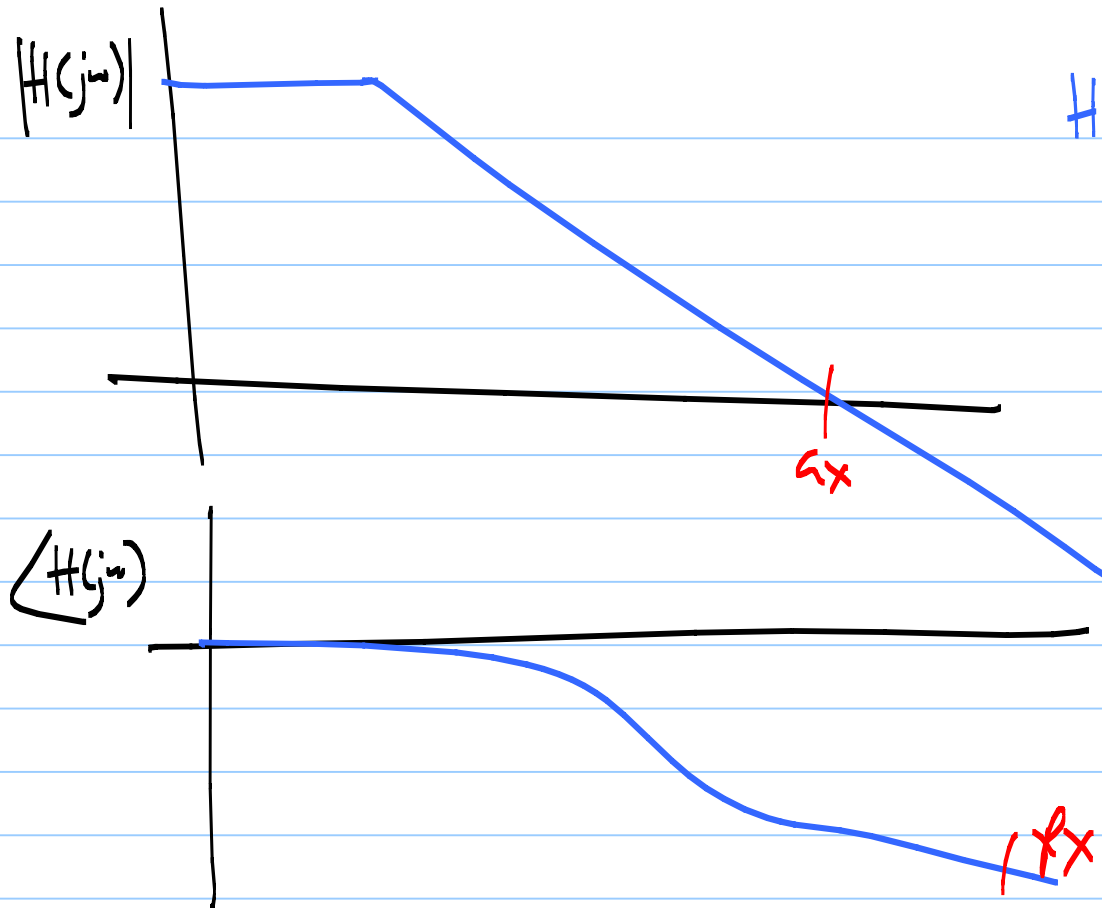

$H(j\omega)$ should have
sufficient
PM $\rightarrow$ GM

$H(j\omega) \leftarrow$ "stable" sufficient PM/CM

$\Rightarrow \beta H(j\omega) \leftarrow$ stable for $\forall \beta \leq 1$

$\Rightarrow \frac{H(j\omega)}{1 + \beta H(j\omega)} \Rightarrow A_c(j\omega) \leftarrow$ is stable