

ECE 511 - Lecture 24


Note Title

4/30/2012

Bandgap References (chapter 25)

BM R

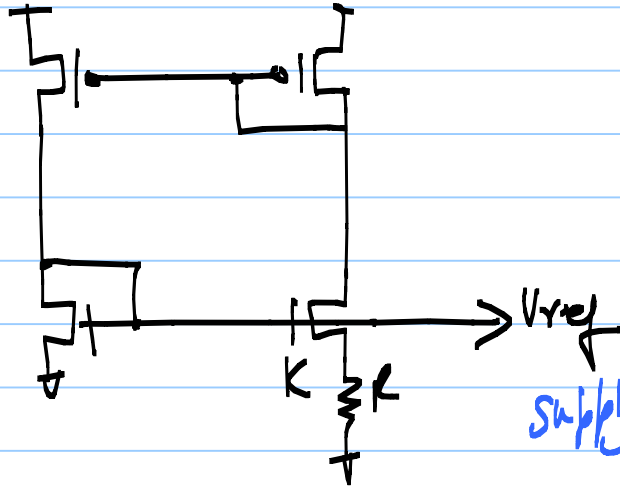Specs $\Rightarrow$ DC sweep
 $\hookrightarrow$ Temperature



$T \uparrow$


$-25^{\circ}\text{C} \rightarrow 100^{\circ}\text{C}$

supply independent reference voltage



$$I_{ref} = \frac{2}{\beta R^2} \left(1 - \frac{1}{\sqrt{K}}\right)^2, \quad V_{ref} = \frac{2}{\beta R} \left(1 - \frac{1}{\sqrt{K}}\right) + V_{THN}$$

$\hookrightarrow$ Not constant with T

Voltage Reference

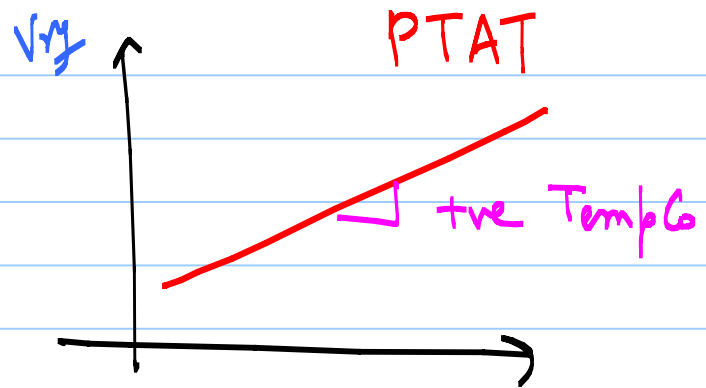

prop. to Absolute Temperature

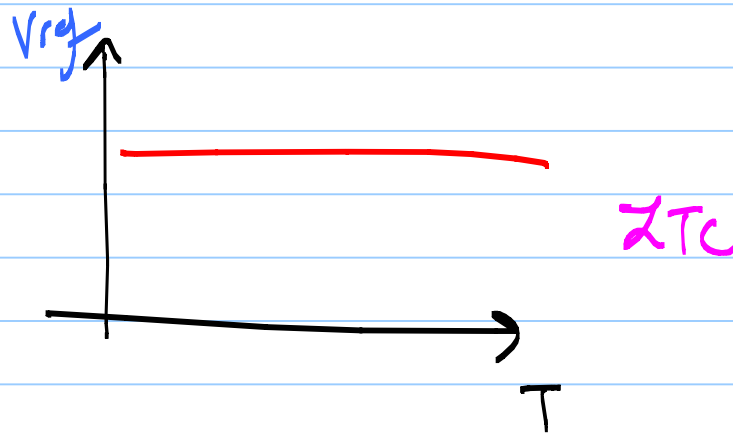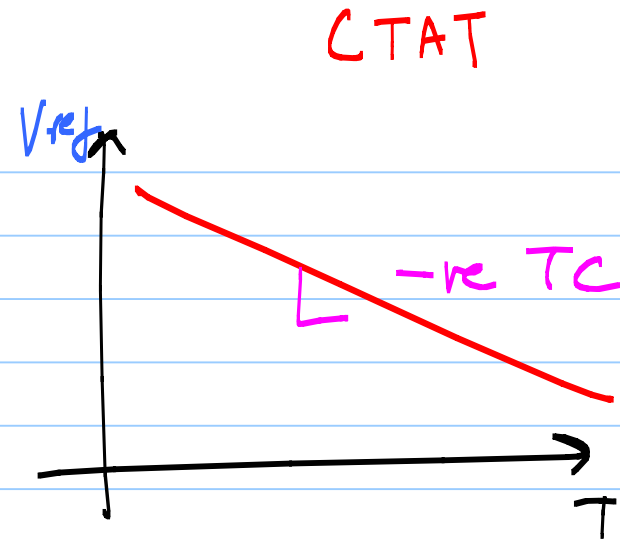

Zero Temp Co $\Rightarrow \frac{\partial V_{ref}}{\partial T} = 0$


$$V_{ref} = \alpha_1 V_1 + \alpha_2 V_2 \quad \begin{array}{l} \swarrow \text{PTAT} \quad \swarrow \text{CTAT} \\ \leftarrow \text{ZTC} \\ \text{Temp. indep Ref} \end{array}$$

Goal: $\frac{\partial V_{ref}}{\partial T} = 0 \Rightarrow \alpha_1 \underbrace{\frac{\partial V_1}{\partial T}} + \alpha_2 \underbrace{\frac{\partial V_2}{\partial T}} = 0$ ZTC

$\alpha_1, \alpha_2 = ?$

$\frac{\partial V_1}{\partial T}, \frac{\partial V_2}{\partial T} \Leftarrow \text{may not be constant}$

① CTAT $\Leftarrow$ -ve T_c Voltage

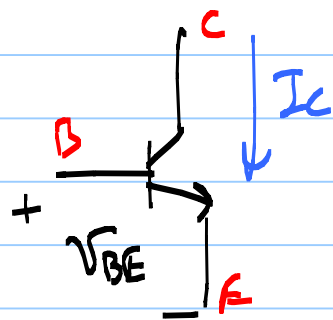

n/pn BJT

$$I_C \approx I_S e^{\frac{V_{BE}}{nV_T}} \rightarrow \textcircled{1}$$

$$V_T \Leftarrow \frac{kT}{q}$$

26 mV @ $T = 300\text{K}$

$$n = 1$$

$$I_S \propto \mu k T n_i^2$$

$$n_i^2 \propto T^3 e^{-E_g/kT}$$

Bandgap
Energy
of Si

$$\mu = \mu_0 T^m, \quad m = -\frac{3}{2}$$

$$I_S = b T^{(4+m)} e^{-E_g/kT} \rightarrow \textcircled{2}$$

@ I_c

$$V_{BE} = V_T \ln\left(\frac{I_c}{I_s}\right)$$

$$\frac{\partial V_{BE}}{\partial T} = \frac{\partial V_T}{\partial T} \ln\left(\frac{I_c}{I_s}\right) - \boxed{\frac{V_T}{I_s} \cdot \frac{\partial I_s}{\partial T}} \rightarrow \textcircled{3}$$


$$\frac{\partial I_s}{\partial T} = \frac{(4+m)}{T} \cdot I_s + I_s \cdot \frac{E_s}{kT^2}$$


$$\Rightarrow \boxed{\frac{V_T}{I_s} \cdot \frac{\partial I_s}{\partial T}} = (4+m) \frac{V_T}{T} + \frac{E_s}{kT^2} \cdot V_T \rightarrow \textcircled{4}$$

|

$$\frac{\partial V_{BE}}{\partial T} = \frac{V_T}{T} \ln\left(\frac{I_C}{I_S}\right) - (4+m) \frac{V_T}{T} - \frac{E_g}{kT^2} \cdot V_T$$
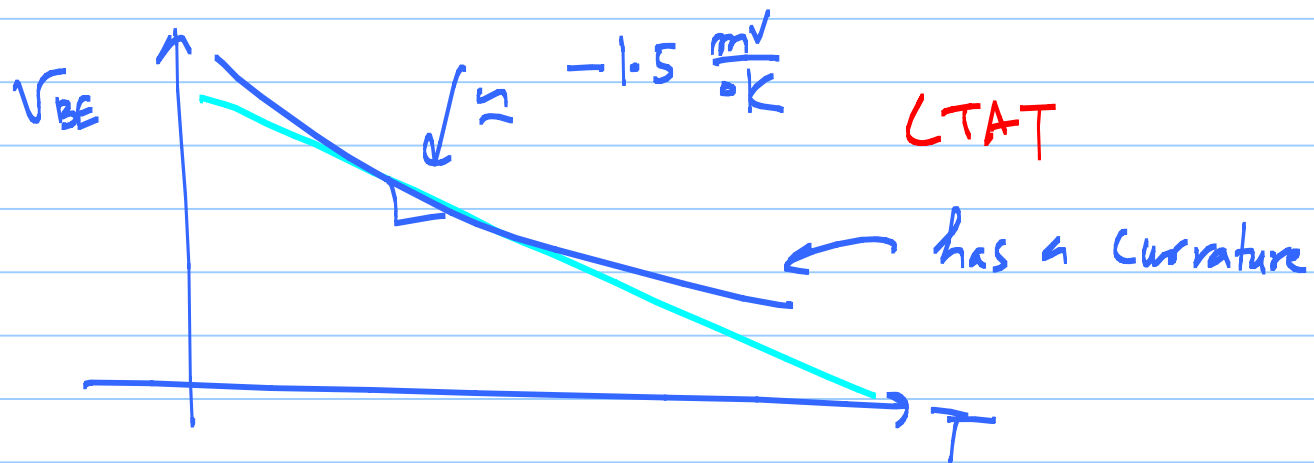
$$\frac{\partial V_{BE}}{\partial T} = \frac{V_{BE} - (4+m)V_T - \frac{E_g}{2}}{T} \rightarrow \textcircled{5}$$



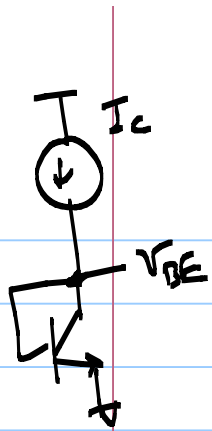

$V_{BE} \Rightarrow$


not a linear CTAT

$\hookrightarrow$ can't make a perfect ZTC at all Temp.



$V_{BE} \leftarrow$ CTAT

② PTAT $\Rightarrow$ +ve TC

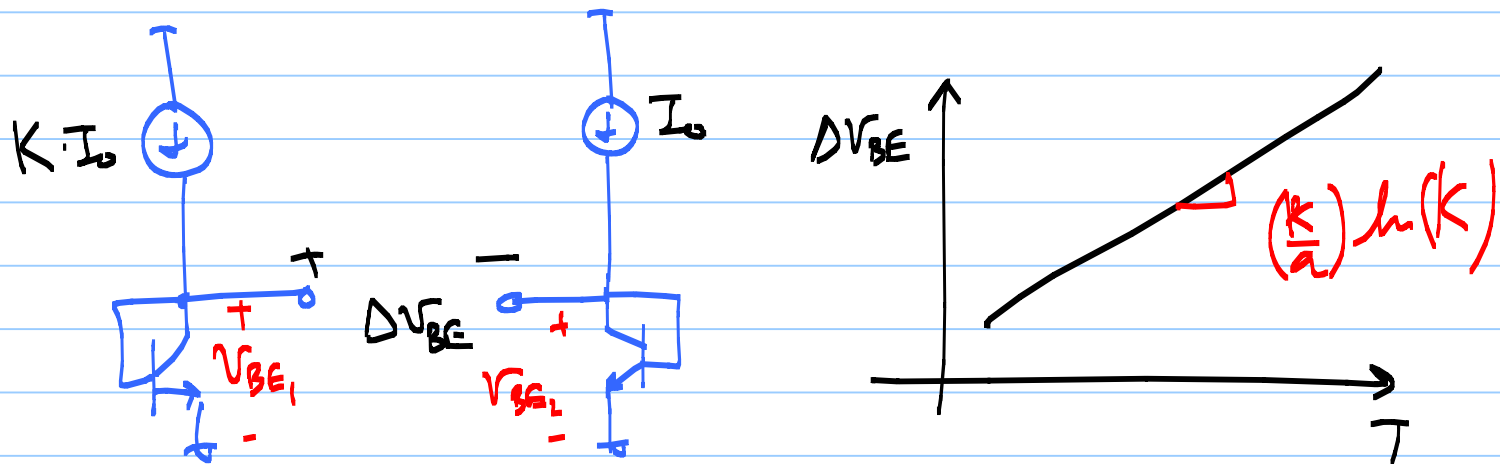

$$\begin{aligned}
 \Delta V_{BE} &= V_{BE1} - V_{BE2} \\
 &= V_T \ln\left(\frac{K I_0}{I_s}\right) - V_T \ln\left(\frac{I_0}{I_s}\right) \\
 &= V_T \ln\left(\frac{K I_0}{\cancel{I_0} I_s}\right) = \boxed{V_T \ln(K)} = \left(\frac{K}{q} \ln k\right) T
 \end{aligned}$$

"Bandgap Reference"

(BGR)

$$\underline{V_{ref}} = \alpha_1 \underbrace{V_{BE}}_{CTAT} + \alpha_2 \underbrace{(V_T \ln K)}_{PTAT}$$

$$\frac{\partial V_{BE}}{\partial T} = -1.5 \frac{mV}{^\circ K}$$

$$\frac{\partial V_T}{\partial T} = \frac{k}{q} = +0.087 \frac{mV}{^\circ K}$$

$$\alpha_1, \alpha_2 = ??$$

$$\frac{\partial V_{ref}}{\partial T} = 0$$

$$\alpha_1 \cdot \frac{\partial V_{BE}}{\partial T} + \alpha_2 \frac{\partial}{\partial T} (V_T \ln K) = 0$$

$$\Rightarrow \alpha_2 \ln(K) = \frac{-\alpha_1 \cdot \frac{\partial V_{BE}}{\partial T}}{k/q}$$

$$= \frac{\alpha_1 \cdot 1.5 \frac{\text{mV}}{\text{K}}}{0.087 \frac{\text{mV}}{\text{K}}}$$

$$\alpha_2 \ln(K) = 17.2 \alpha_1$$


Choose $\alpha_1 = 1$
 $\Rightarrow$

$$\alpha_2 \ln(K) \approx 17.2$$

$$V_{ref} = \alpha_1 V_{BE} + \alpha_2 (V_T \ln K)$$

$$V_{ref} = V_{BE} + 17.2 \times V_T \Rightarrow \frac{\partial V_{ref}}{\partial T} = 0$$


Example #1

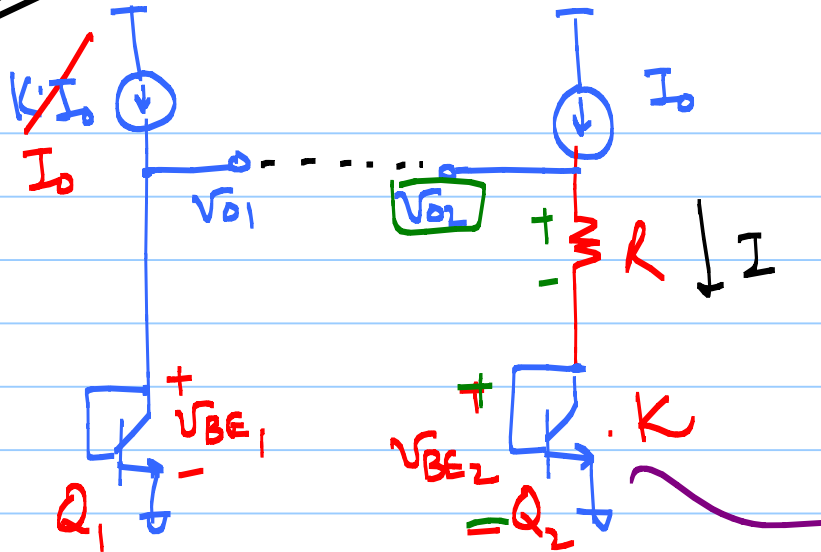

Somehow force $V_{01} = V_{02}$

$$V_{BE1} = I R + V_{BE2}$$
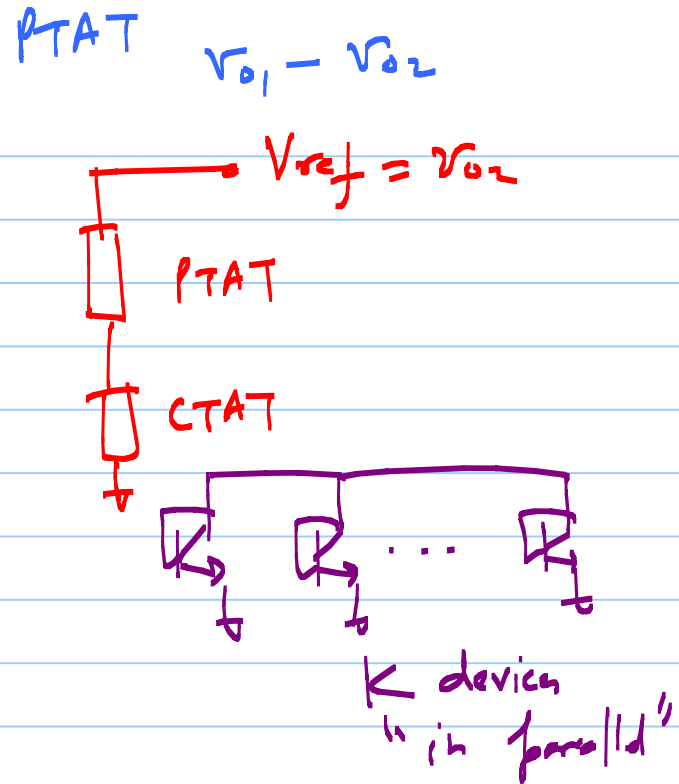
$$I R = V_{BE1} - V_{BE2} = \underline{v_T \ln(K)}$$



K devices
"in parallel"

$$V_{O2} = V_{BE2} + IR$$

$$= \underbrace{V_{BE2}}_{CTAT} + \underbrace{V_T \ln(K)}_{PTAT}$$

for V_{O2} to ZTC reference


$$\ln(K) = 17.2$$

$$K = e^{17.2} = (2.78)^{17.2}$$

$$\boxed{K_2 = 1}$$

"Impractical"

Example #2

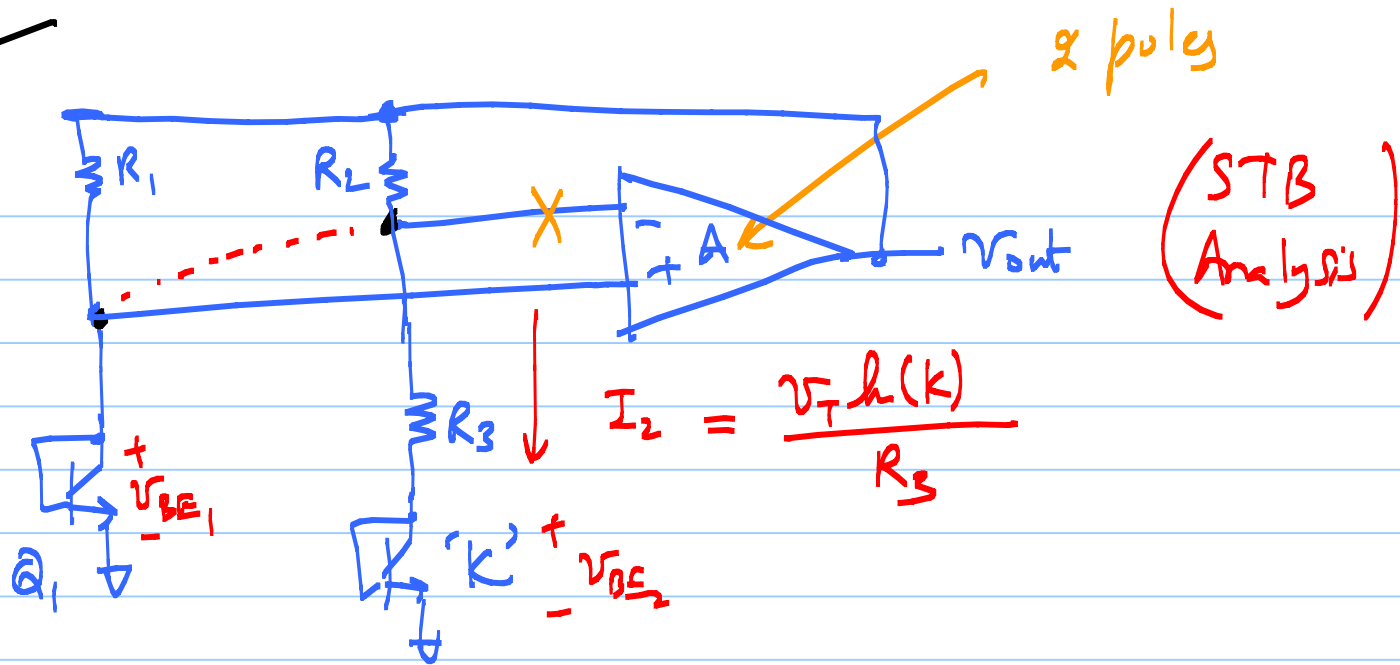

$$V_{out} = V_{BE2} + I_2 \cdot (R_2 + R_3)$$

$$= V_{BE2} + V_T \ln(K) \left[1 + \frac{R_2}{R_3} \right]$$

$\alpha_2 > 1$

$$\text{für } \frac{\partial v_{out}}{\partial T} = 0 \Rightarrow$$

$$L_2 \cdot \ln(K) = 17.2$$

$$\left(1 + \frac{R_2}{R_3}\right) \ln(K) = 17.2$$

$$\frac{R_2}{R_3} = 4 \Rightarrow K = 31$$

* Why Band gap Reference ??

$$V_{REF} = V_{BE} + \boxed{V_T \ln(K)}$$

$$\Rightarrow \frac{\partial V_{REF}}{\partial T} = \frac{\partial V_{BE}}{\partial T} + \frac{V_T}{T} \ln(K) = 0$$

$$\Rightarrow$$

$$\frac{V_{BE} - (4+m)V_T - E_g/2}{T} = -\frac{V_T}{T} \ln(K)$$


$$\Rightarrow V_{REF} = \cancel{V_{BE}'} - \cancel{V_{BE}} + (4+m)V_T + E_g/2$$




$$\boxed{V_{REF} = \frac{E_g}{2} + (4+m)\underline{V_T}}$$

ZTC voltage $\Rightarrow$ Bandgap voltage of the Si ($\frac{E_g}{q}$)
 $\Rightarrow m \& V_T$


$$\text{If } T \rightarrow 0 \Rightarrow V_{REF} \rightarrow \frac{E_g}{q} \Rightarrow 1.12 \text{ V}$$

"Bandgap Reference"

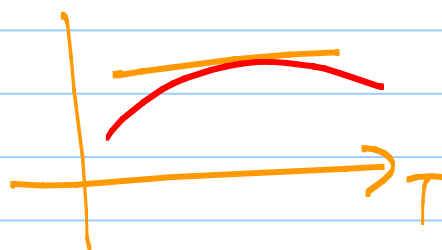

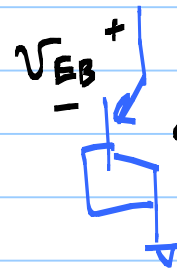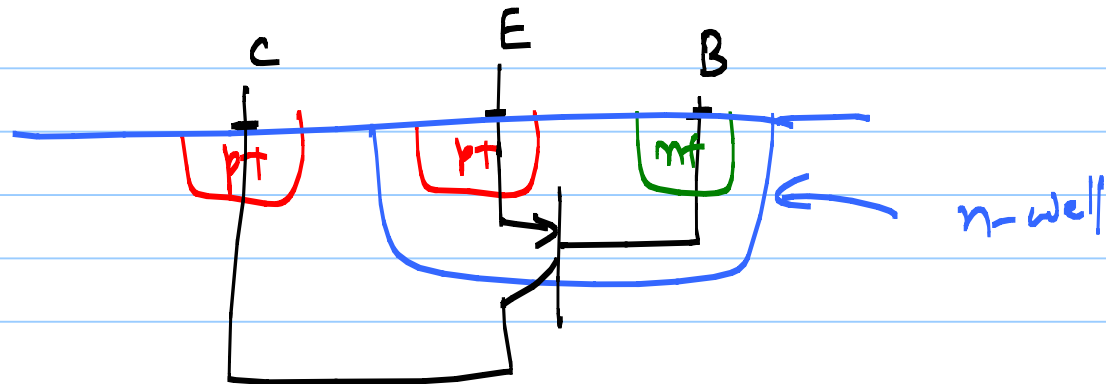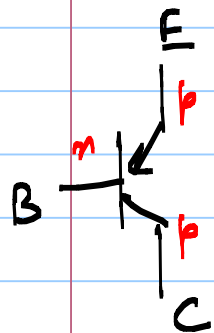

Diode connected β BJT

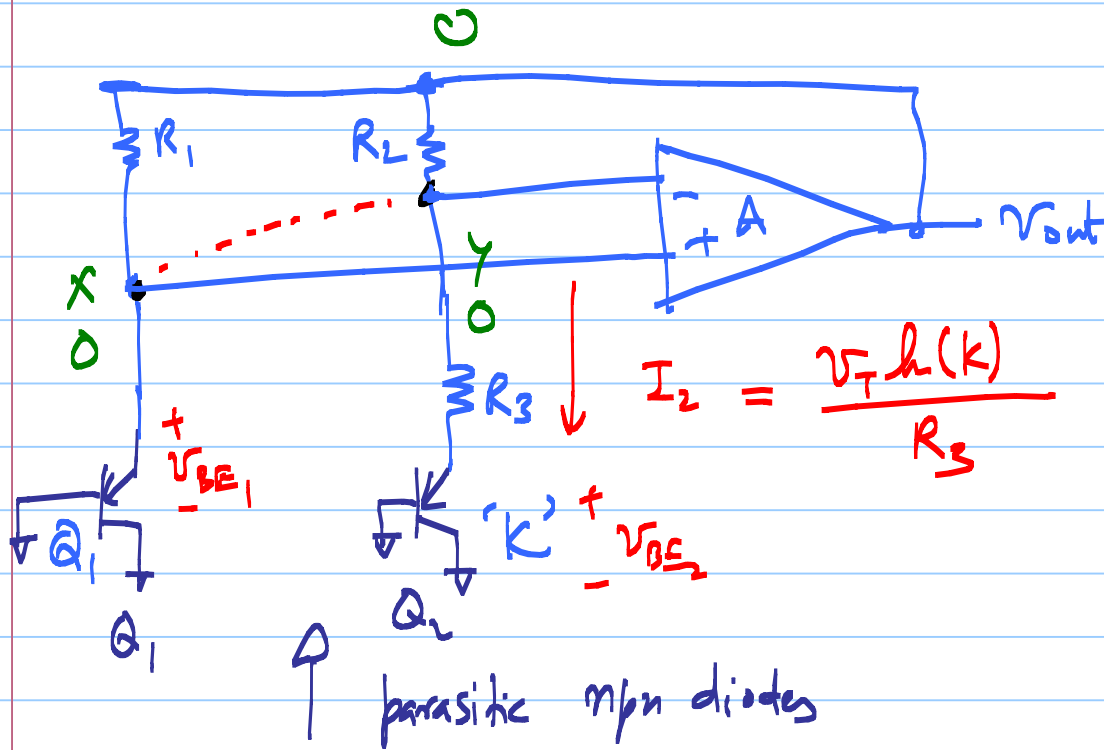

need a
 start up
 circuit

Practical BGR Circuits

