


ECE 511 - Lecture 7

Note Title


2/8/2012

BM12
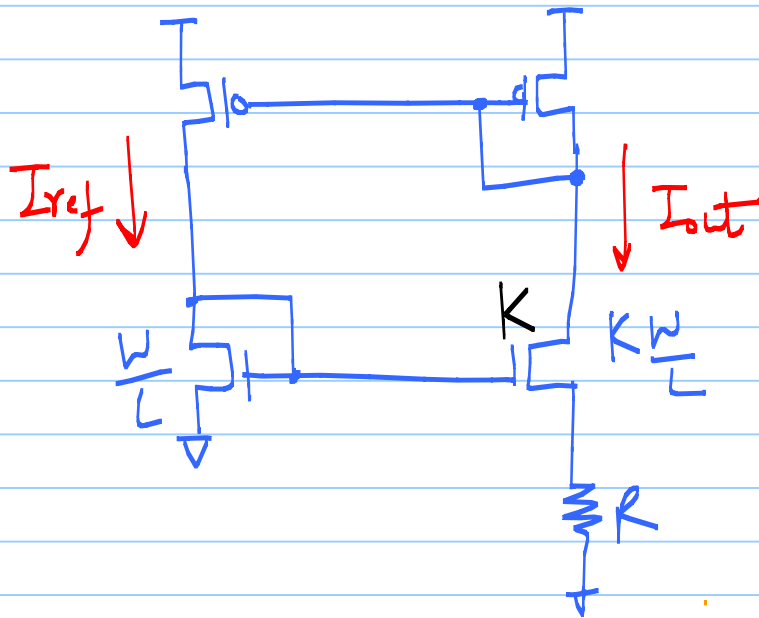
$$I_{out} = I_{ref} = \frac{2}{\beta R^2} \left(1 - \frac{1}{\sqrt{K}}\right)^2$$



Add a diode

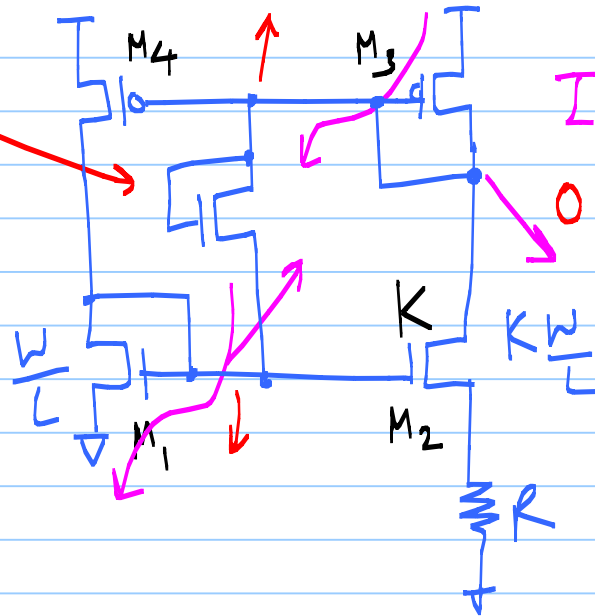

$$I = \frac{2}{\beta R^2} \left(1 - \frac{1}{\sqrt{k}}\right)^2$$

Not a good start-up circuit

1


* BMR uses the feedback



↳ loop gain < 1

↳ fast action

↳ Analysis is skipped.


Short channel BMIR

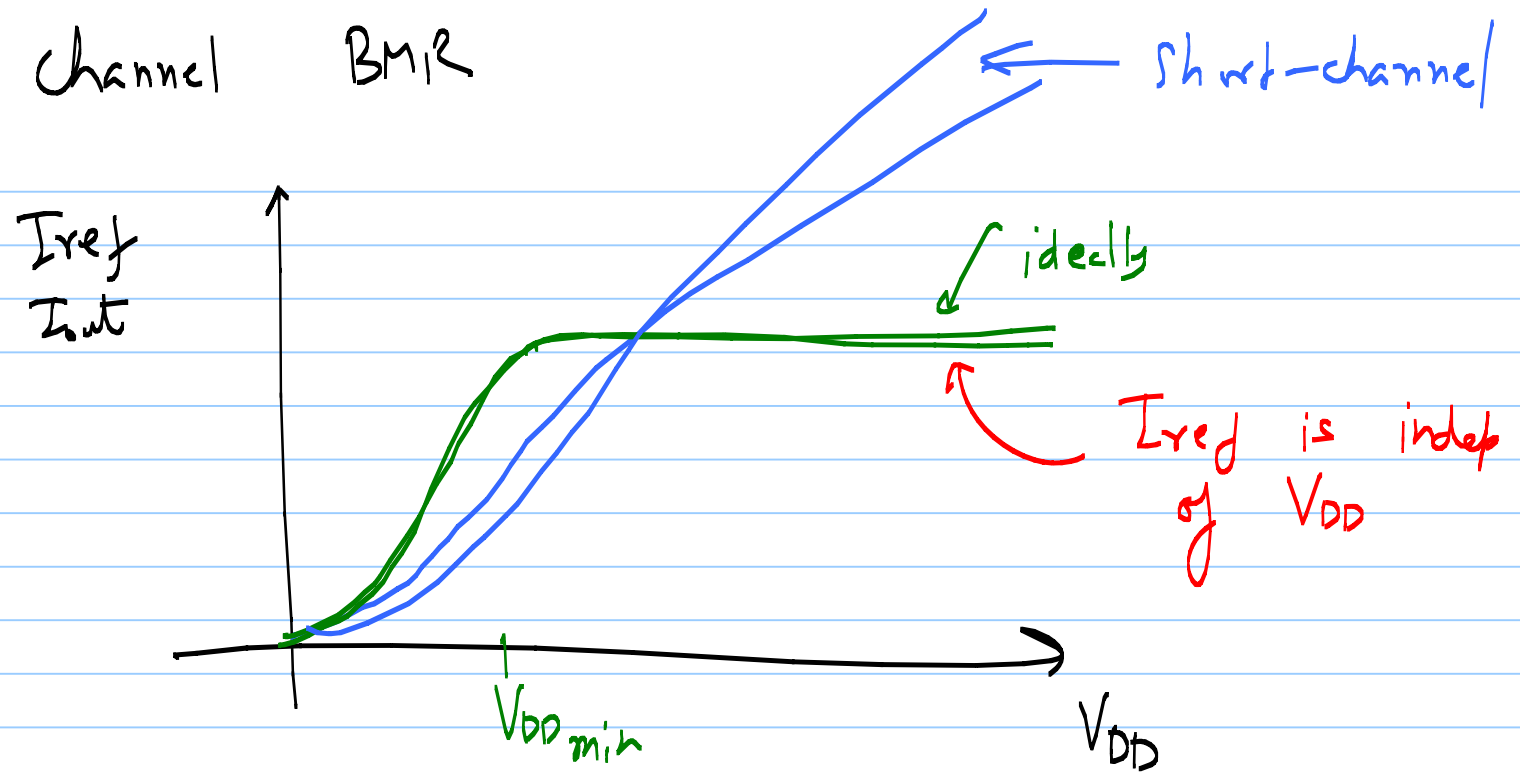

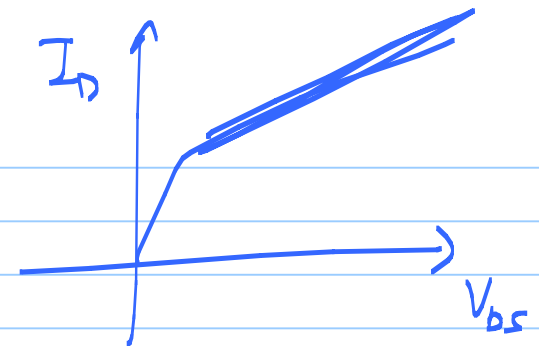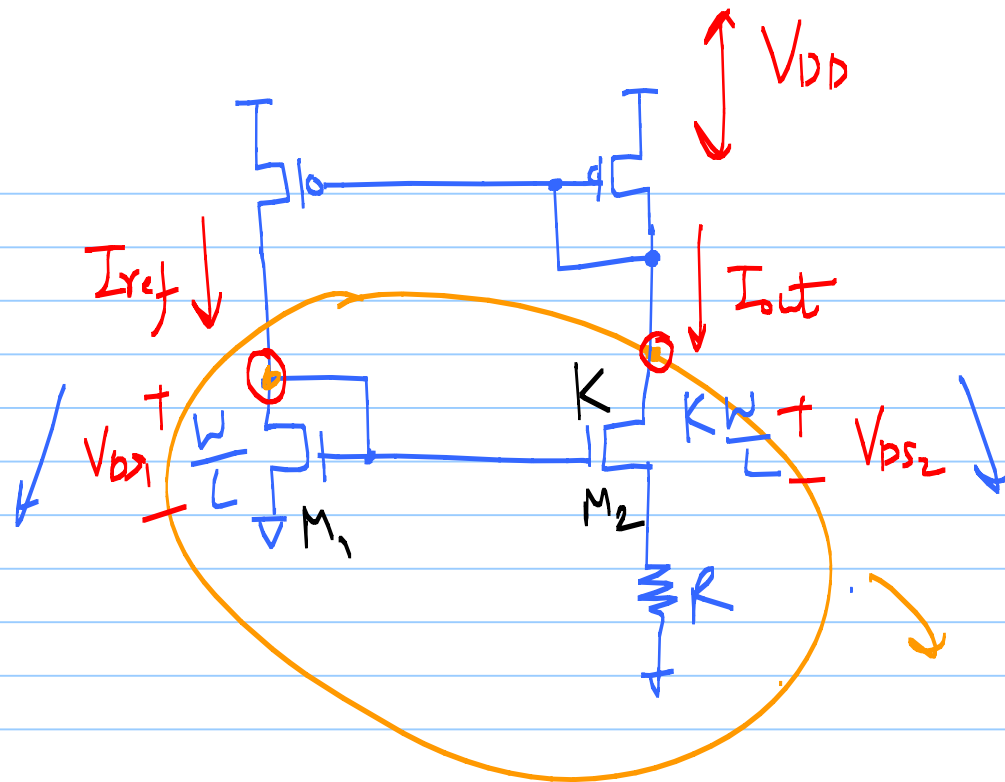

$\lambda \neq 0$
 V_{DS} variation causes
 & I_{ref} & I_{out} mismatch
 & V_{DD} sensitivity

$$V_{reg} = V_{biasn}$$

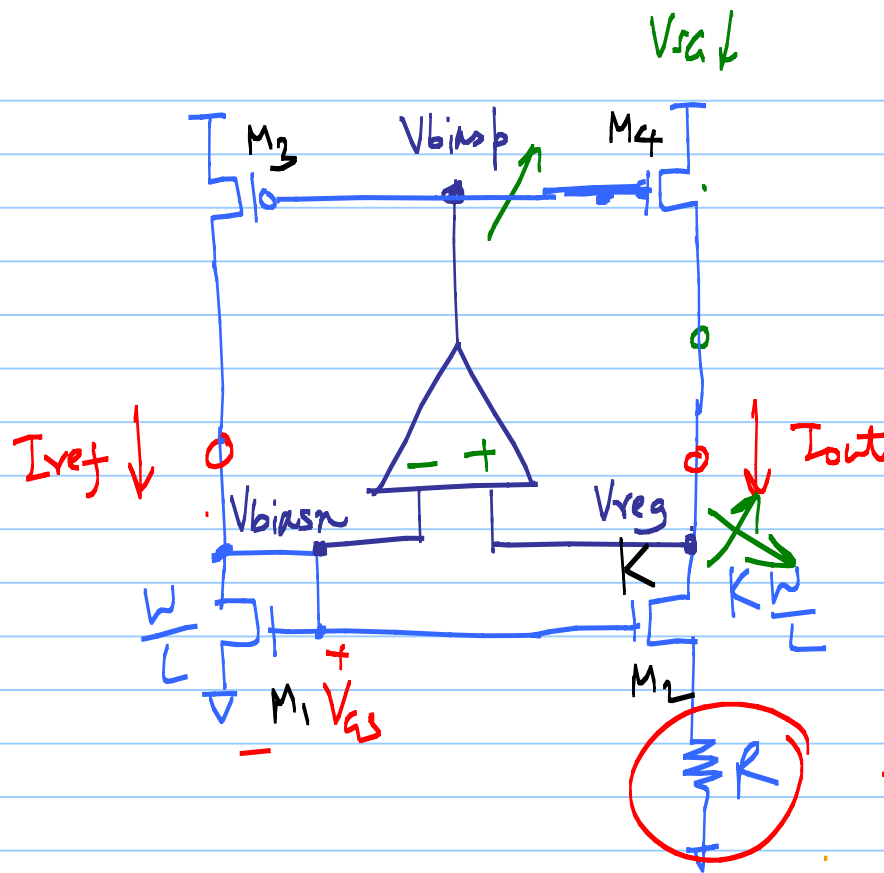


$$V_{biasp} = V_{DD} - V_{sg}$$


$$V_{biasn} = V_{gs}$$



ensure overall
-ve feedback.
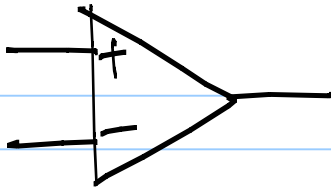
$$I_{ref} \neq \frac{2}{\beta R^2} \left(1 - \frac{1}{\sqrt{k}}\right)^2$$




VCCS
 gain $\Rightarrow A = 10$

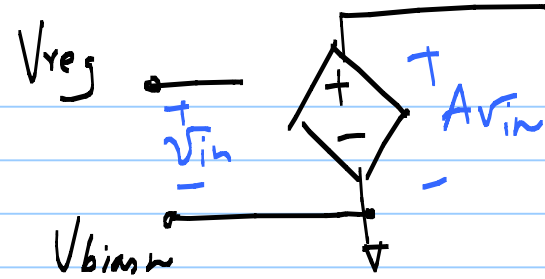

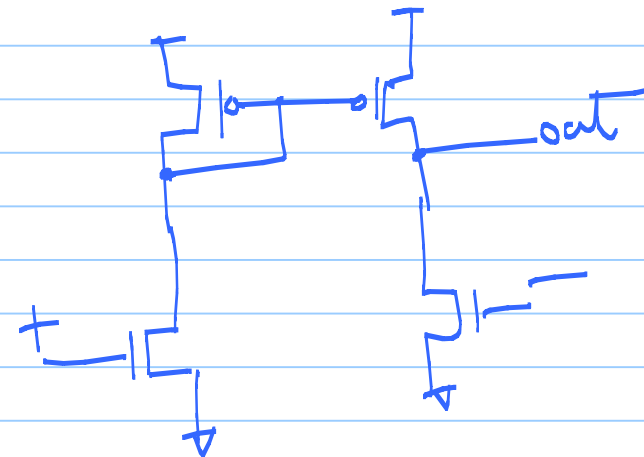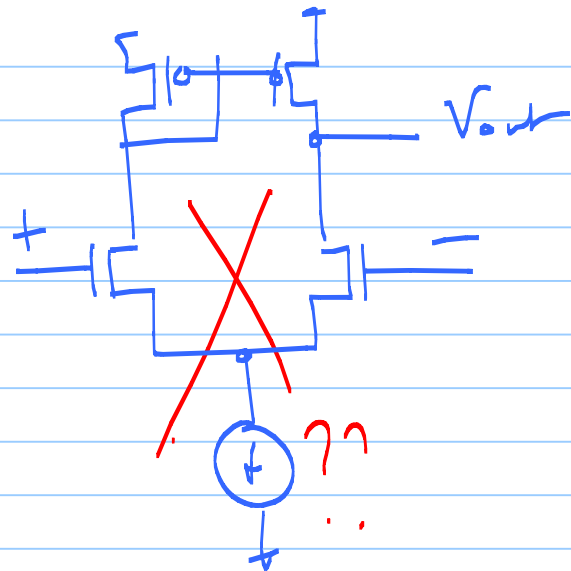

g_m


No precision bias needed.

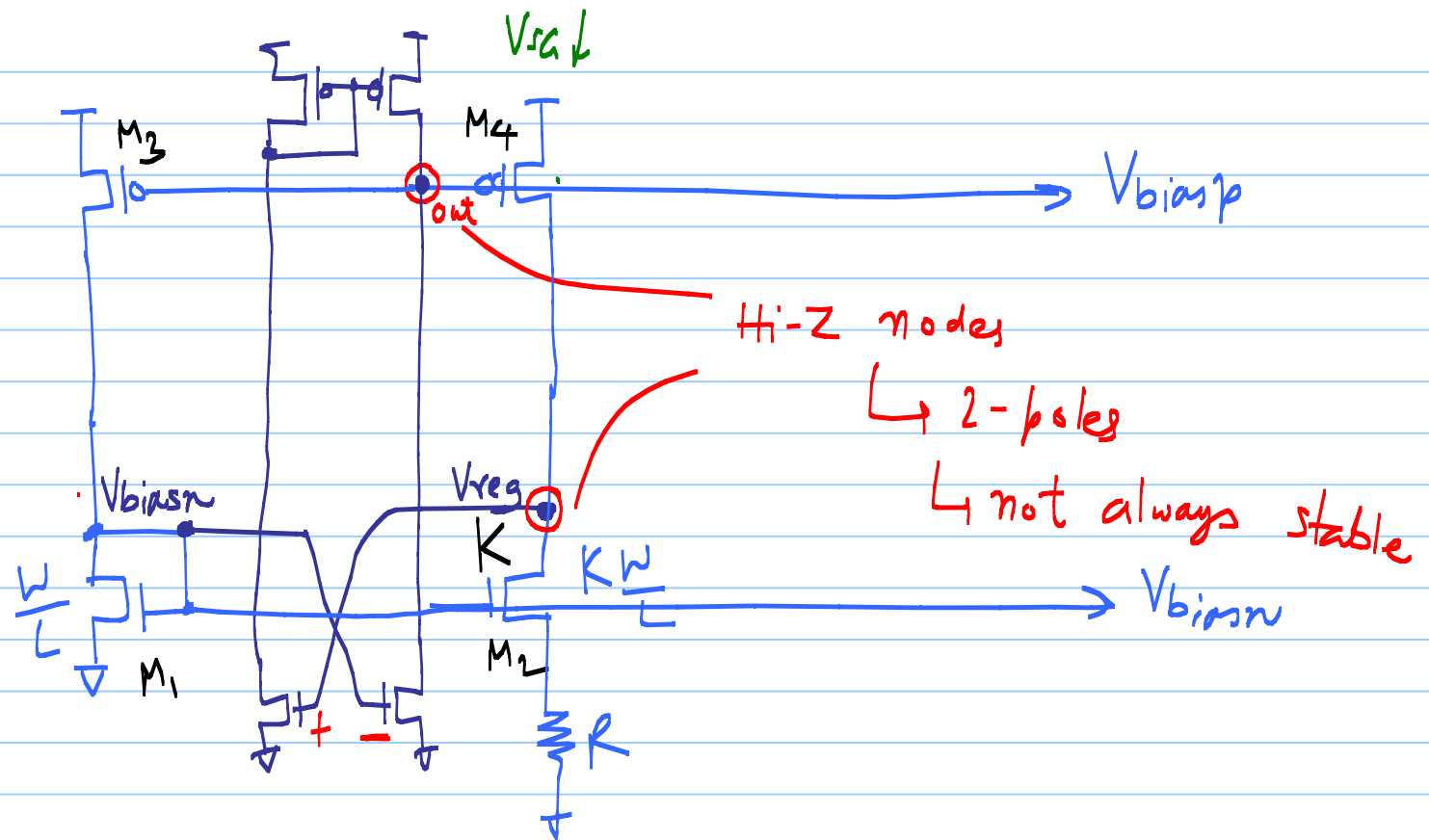

Temp. Coeff for a Resistor

$$TCR = \frac{1}{R} \cdot \left(\frac{\partial R}{\partial T} \right) \approx 1000 \text{ ppm}/^{\circ}\text{C}$$
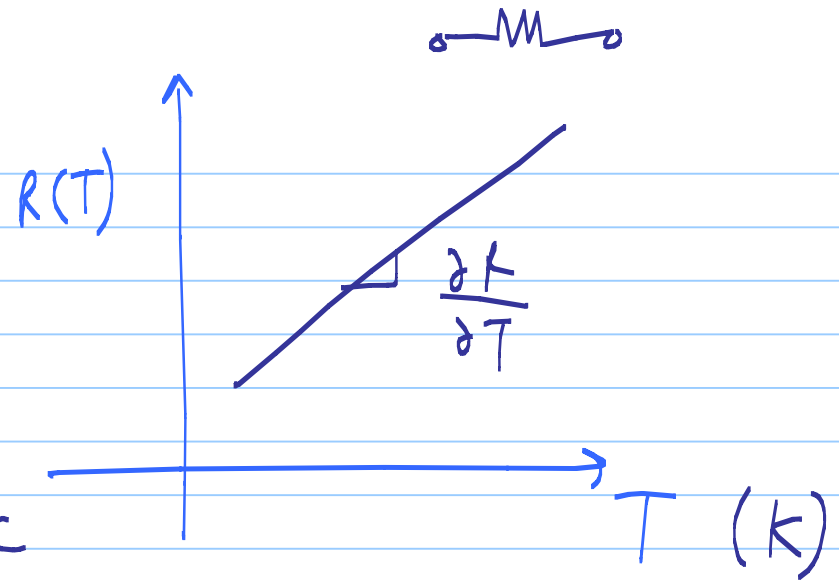
$$TCR_n = -\frac{1.5}{T} = -\frac{1.5}{300} @ 27^{\circ}\text{C}$$



BMR

$$I_{ref} = \frac{2}{k \ln \frac{w}{L}} R^2 \left(1 - \frac{1}{\sqrt{k}}\right)^2$$

$$TC_{BMR} = \frac{\left(\frac{\partial I_{ref}}{\partial T}\right)}{I_{ref}} = -2 \left(\frac{1}{R} \cdot \frac{\partial R}{\partial T}\right) - \frac{1}{k \ln} \cdot \frac{\partial k \ln}{\partial T}$$

$$= -2 \cdot \underline{TC_R} - \underline{TC_{k \ln}}$$

$$= -0.002 + \frac{1.5}{300} \approx 1000 \text{ ppm}/^\circ\text{C} \neq 0$$

$$TC_{I_{ref}} \neq 0$$

Not Temp independent

↳ Bandgap References

(BGR) → Chap-25