

Project Help Session

Note Title

4/21/2012


Table 1: Opamp design specifications.


Parameter	Specified Value
Technology	TSMC 180n CMOS
Supply voltage, V_{DD}	1.8 V
Typical load	$10k\Omega \parallel 1\mu F$
Unit gain frequency (f_{un})	> 100 MHz
Open-loop gain (A_{OL})	> 70 dB
Slew-rate (SR)	> $500 \frac{V}{\mu s}$
Phase margin (ϕ_M)	$\geq 63^\circ$
Power consumption	Minimum possible

faster setting
 $A(s)$

$$SR = 500 \frac{V}{\mu s} = \frac{0.5V}{ms}$$

0.5V
1ns

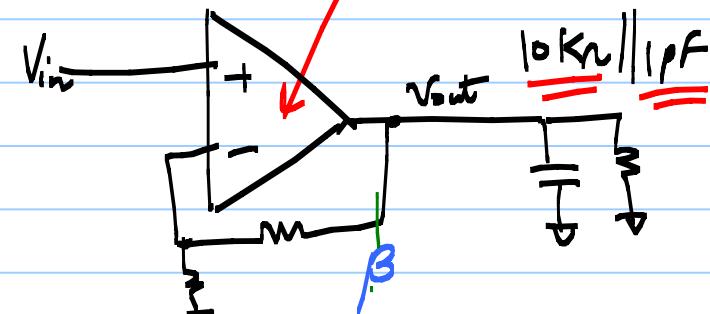

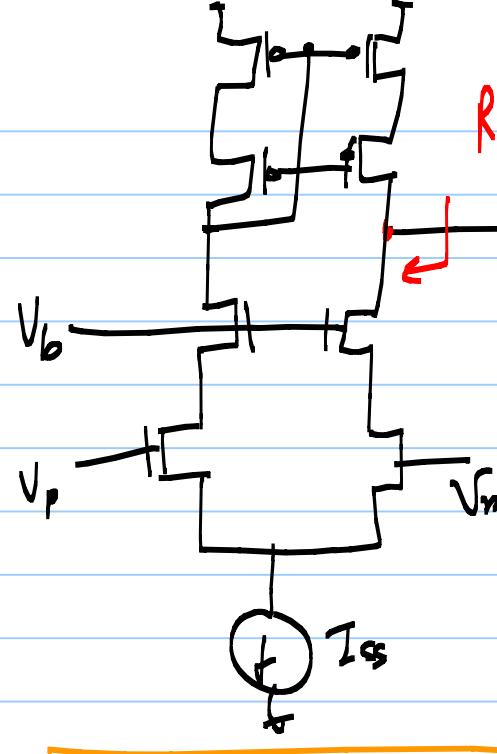

$$I_{M2} \parallel 10k$$

$$R_{out} = R_{p_{cas}} \parallel R_{n_{cas}} \Rightarrow 70 \text{ dB}$$

$$\frac{g_m r_o}{2} = \frac{10^6}{2} \approx 10^5 \text{ } \underline{\underline{10 \text{ dB}}}$$

$$C_L \parallel R_L \Rightarrow 10k$$

$$180_n \Rightarrow g_m r_o \Rightarrow 100$$

$$r_o \Rightarrow 10k$$

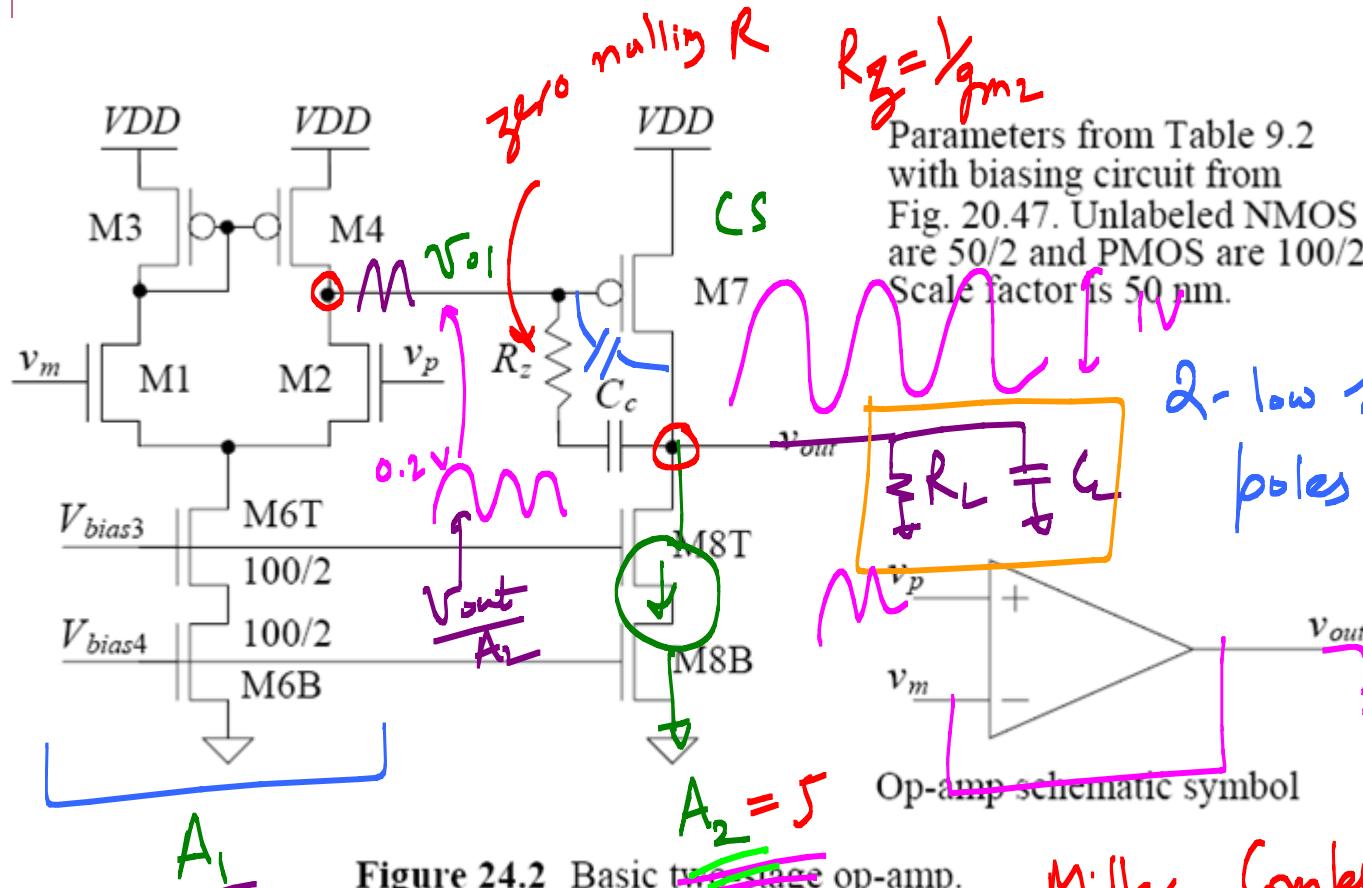


Figure 24.2 Basic two-stage op-amp.


Miller Compensation

$$SR = \frac{I_{SS_2}}{C_L} = \frac{I_{SS_2}}{1\text{pF}} \quad 500 \frac{\text{V}}{\mu\text{s}}$$

$$I_{SS_2} = 500 \times 10^6 \times 10^{-12}$$
$$= 500 \mu\text{A}$$

* Need Class AB 2nd-stage

Output buffer to drive "heavy" loads

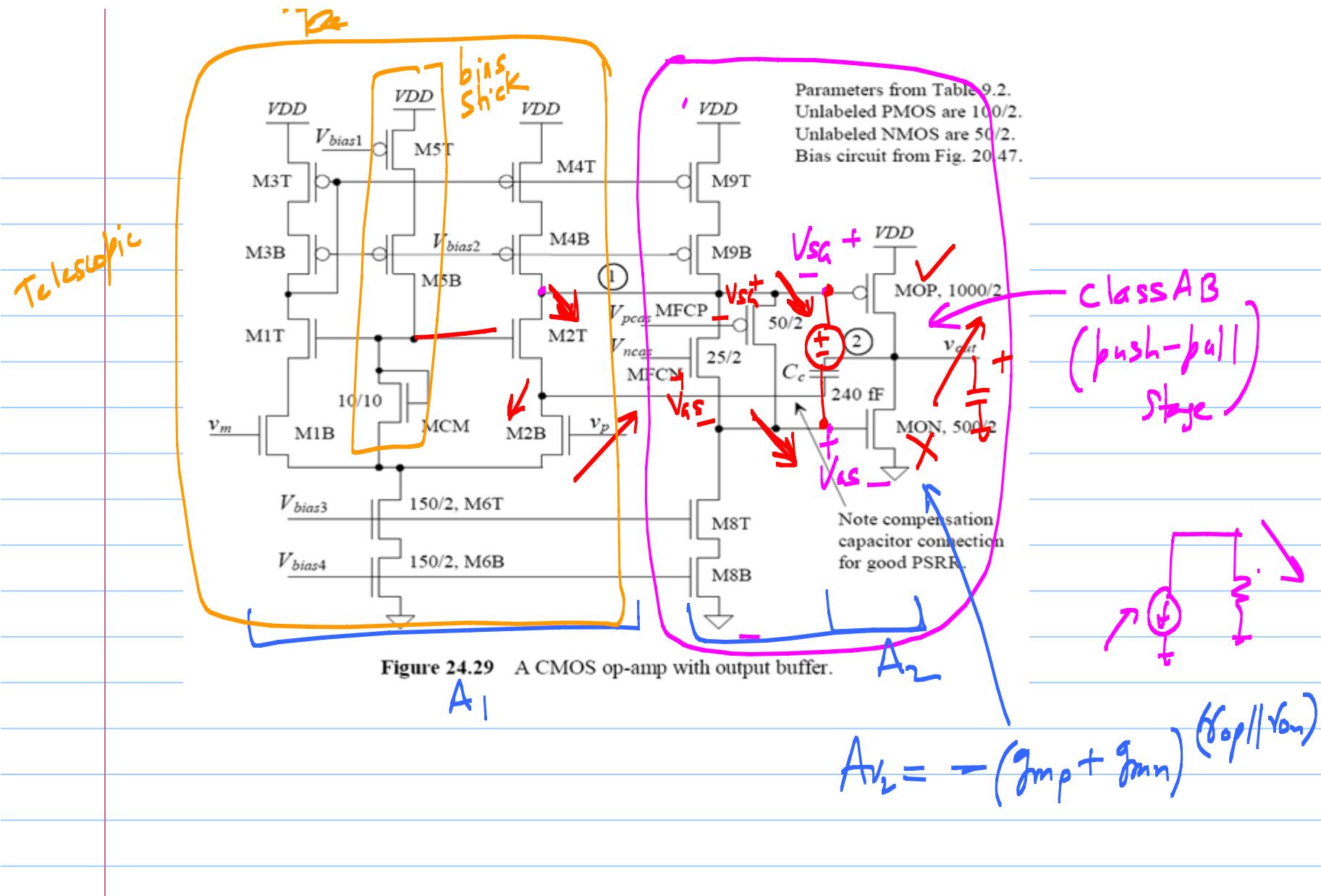

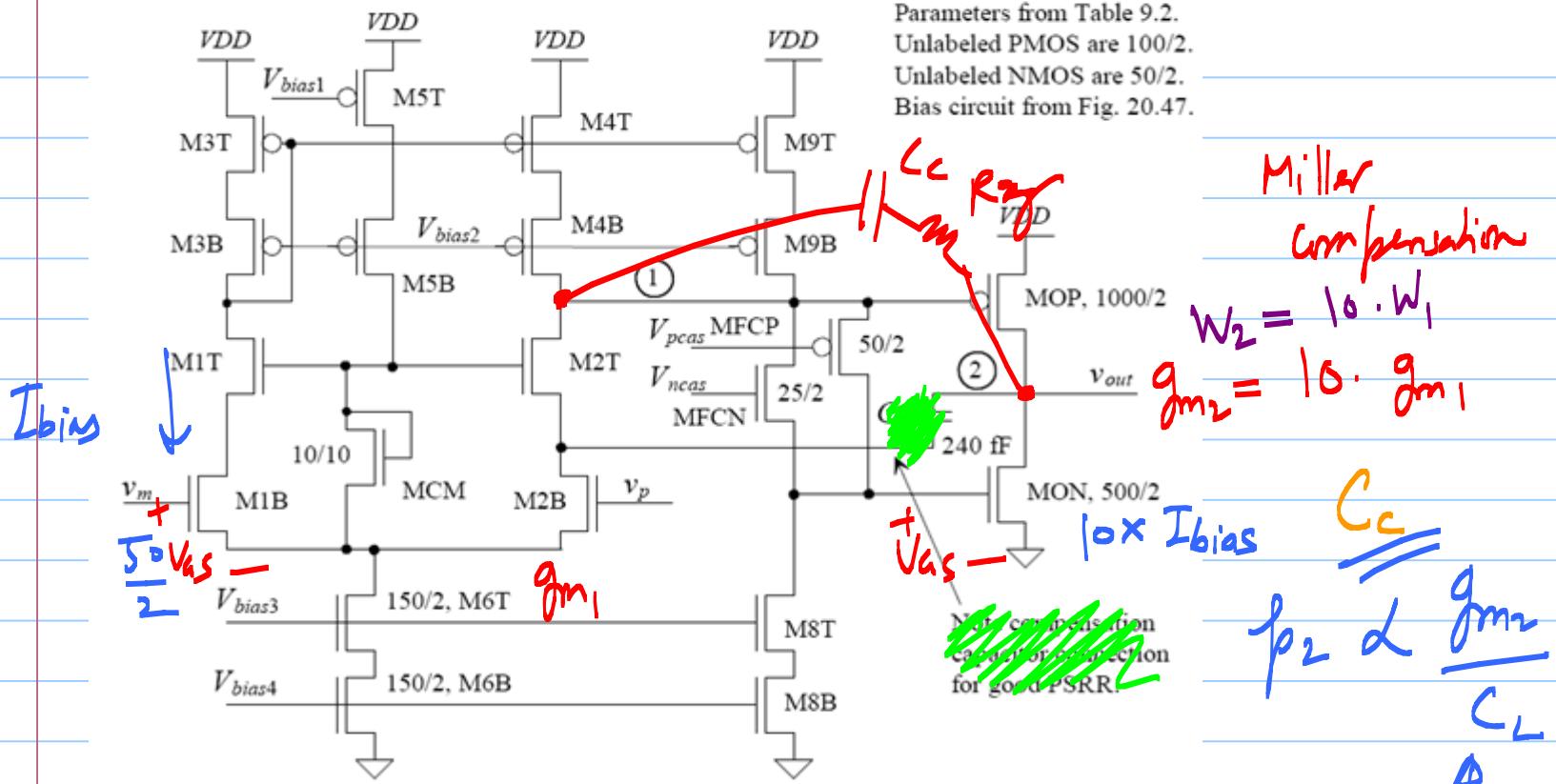


Figure 24.29 A CMOS op-amp with output buffer.

Same V_{AS} \Rightarrow V_{ov} is fixed

$$g_m = \frac{2I_D}{V_{ov}}$$



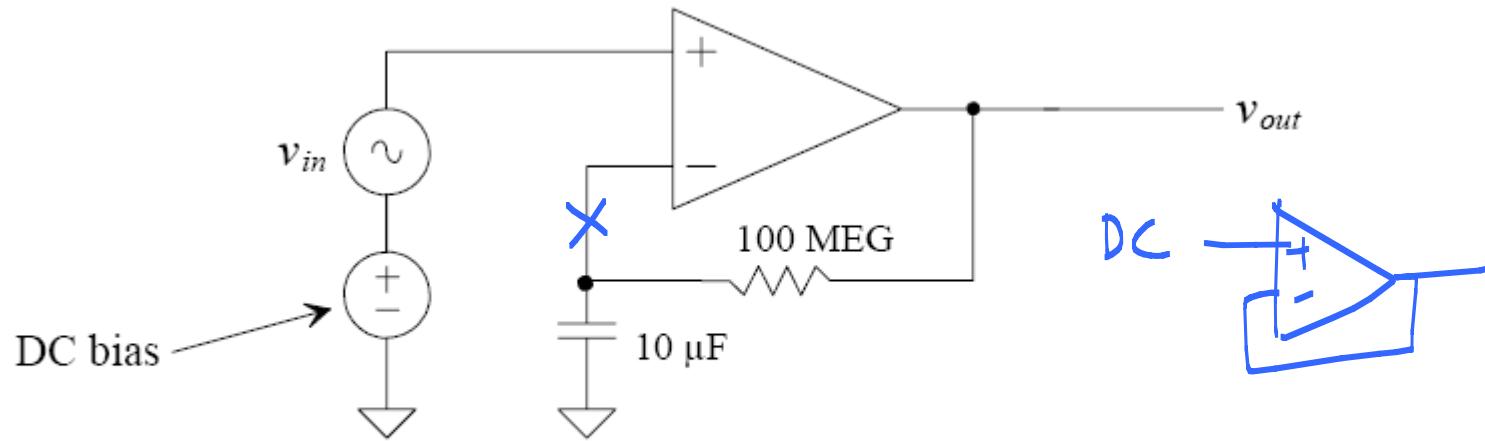


Figure 24.9 Circuit configuration used to simulate open-loop frequency response.

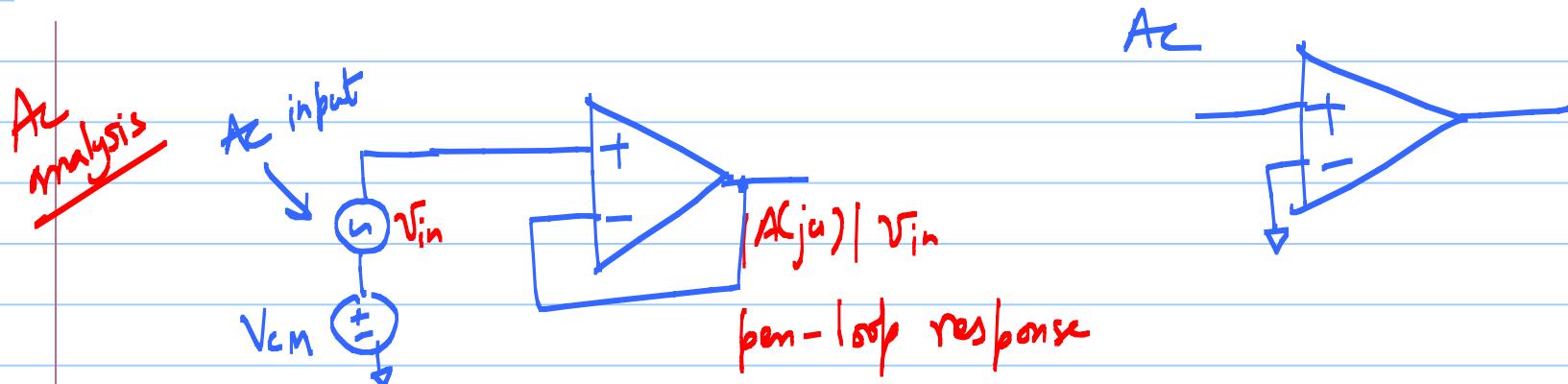


In Spectre

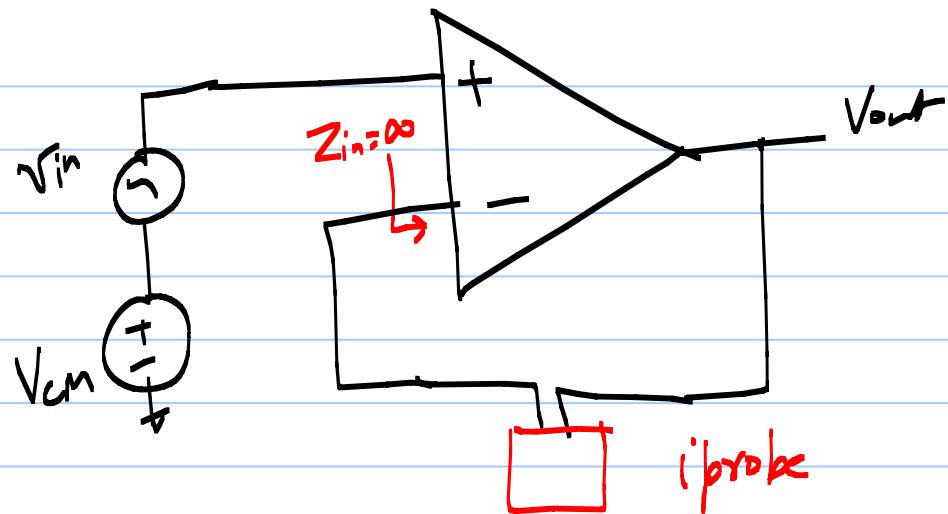


"Stb Analysis"

"Stability"

"Bode plots"

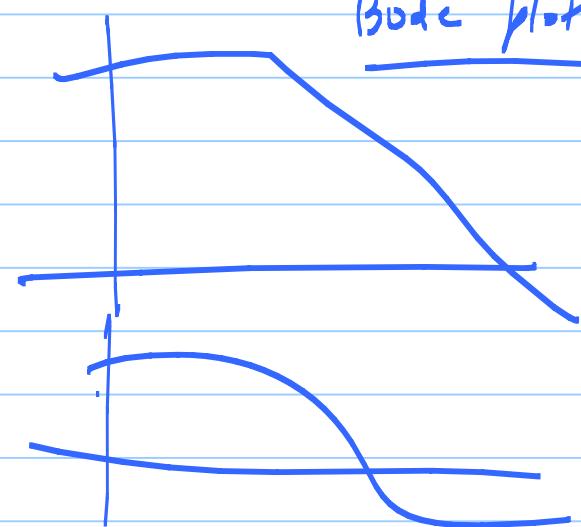

step response

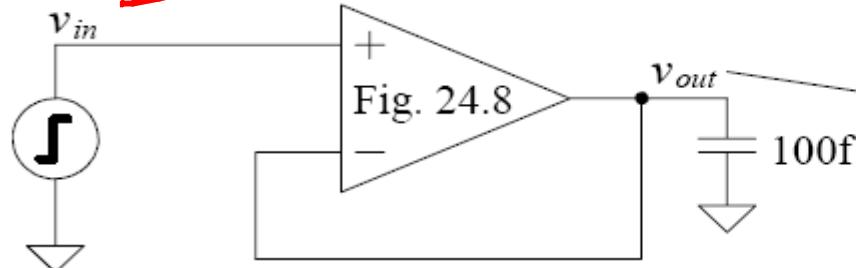

$$C_c = 2.4 \text{ pF}$$

$$R_z = 6.5k$$


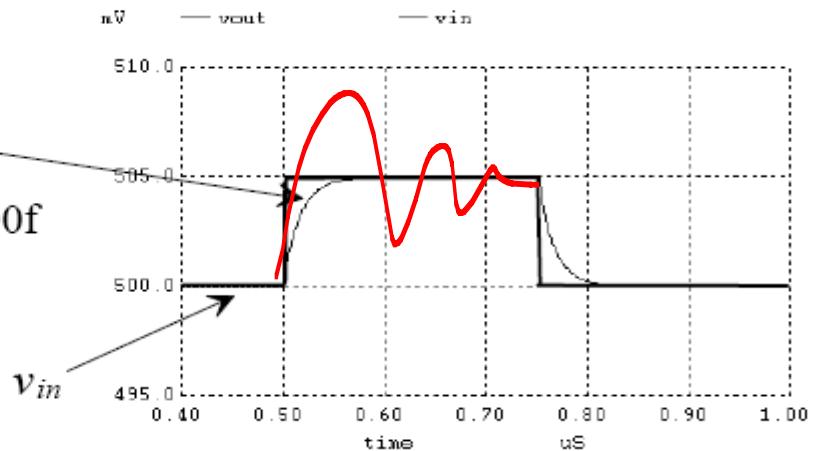


Figure 24.14 Good step response of the op-amp with the zero absent.

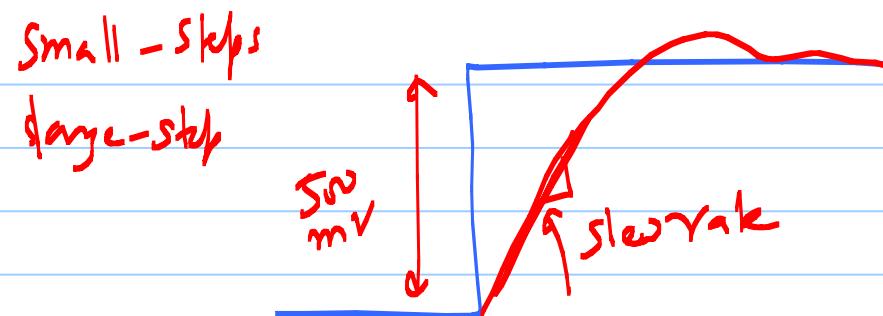

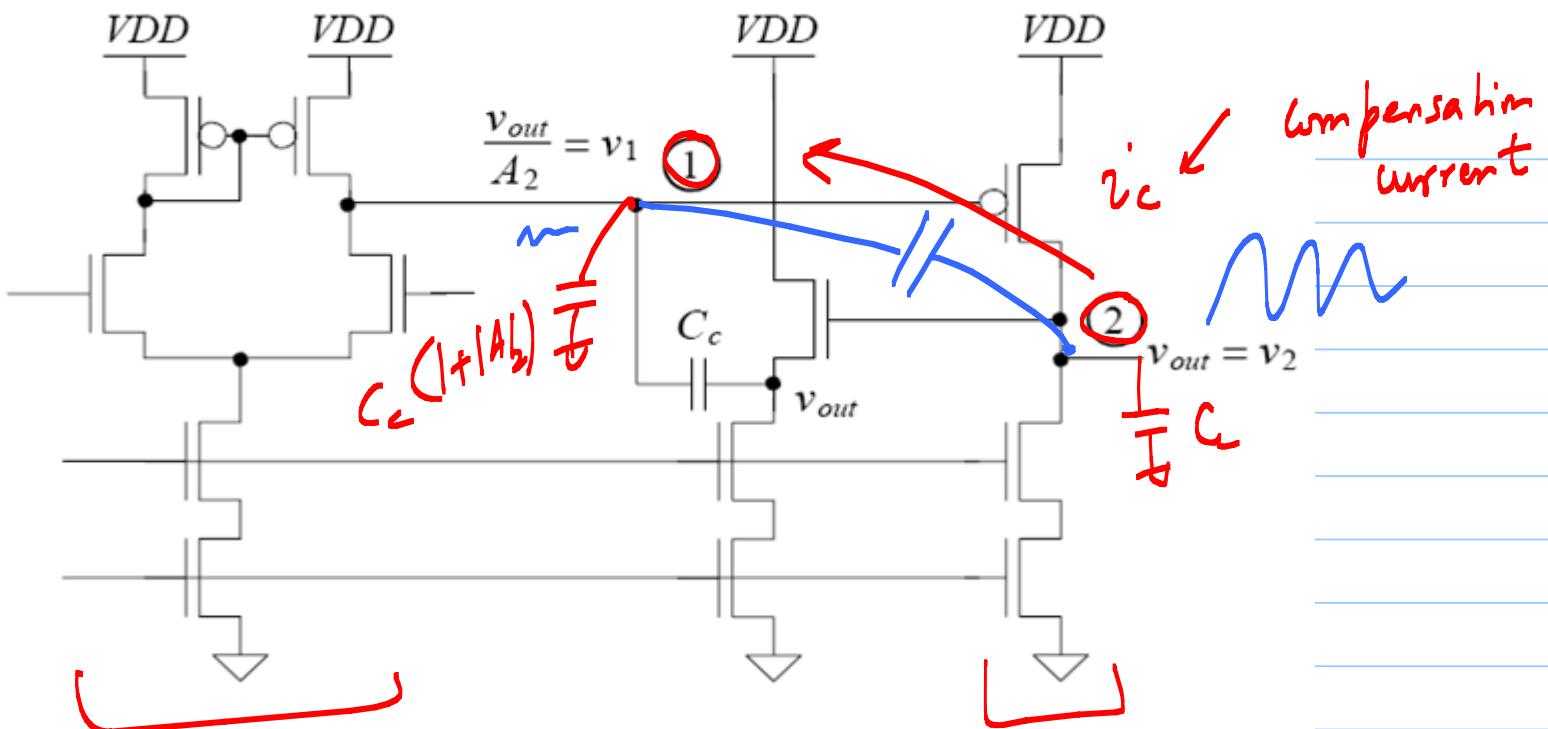


Figure 24.16 Using an amplifier to eliminate forward signal feedthrough via the compensation capacitor.


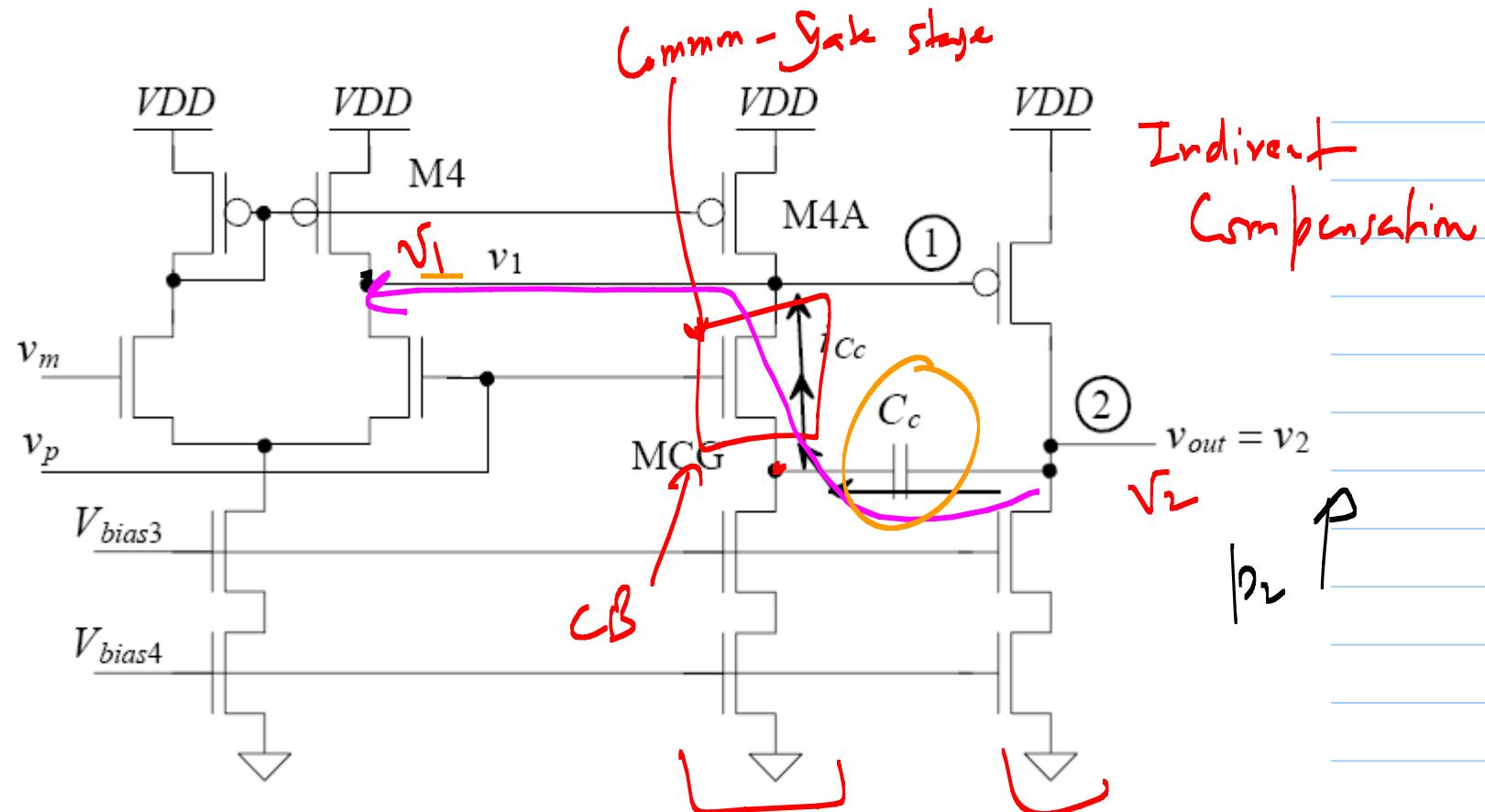


Figure 24.17 Feeding back a current indirectly to avoid the RHP zero.

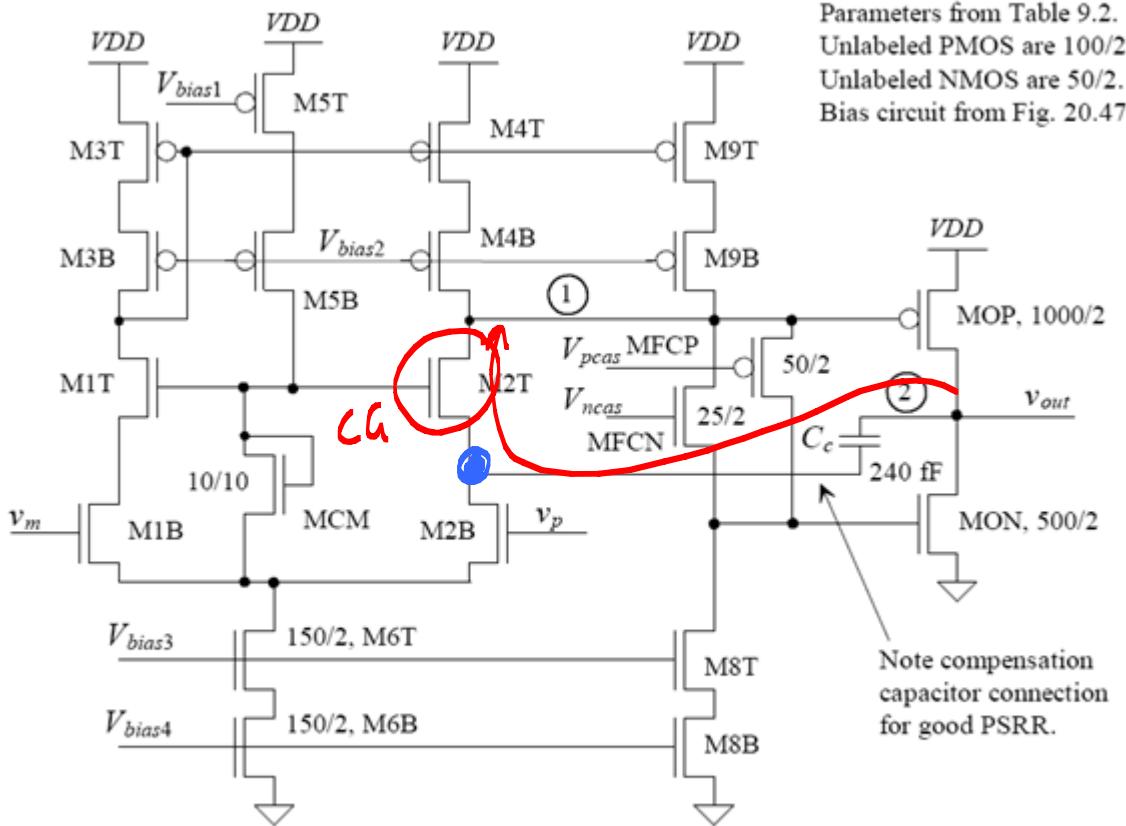

Parameters from Table 9.2.
Unlabeled PMOS are 100/2.
Unlabeled NMOS are 50/2.
Bias circuit from Fig. 20.47.



LHP
zero

$C_c \downarrow$
 $g_m2 \downarrow$

HPS

Figure 24.29 A CMOS op-amp with output buffer.

$$f_2 \leq \lim |A|$$

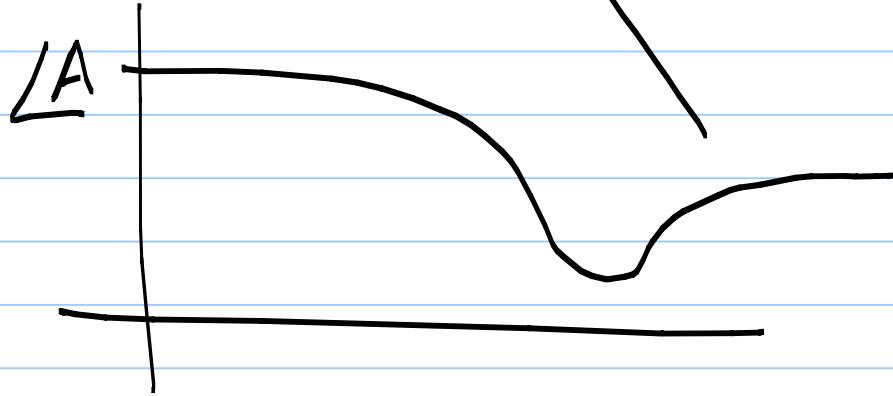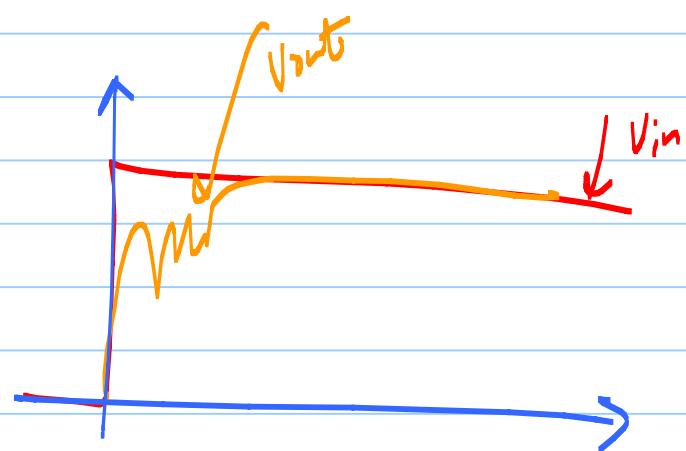

Folded
Card

~~Biassing from Fig. 20.47.
Sizes given in Table 9.2.~~

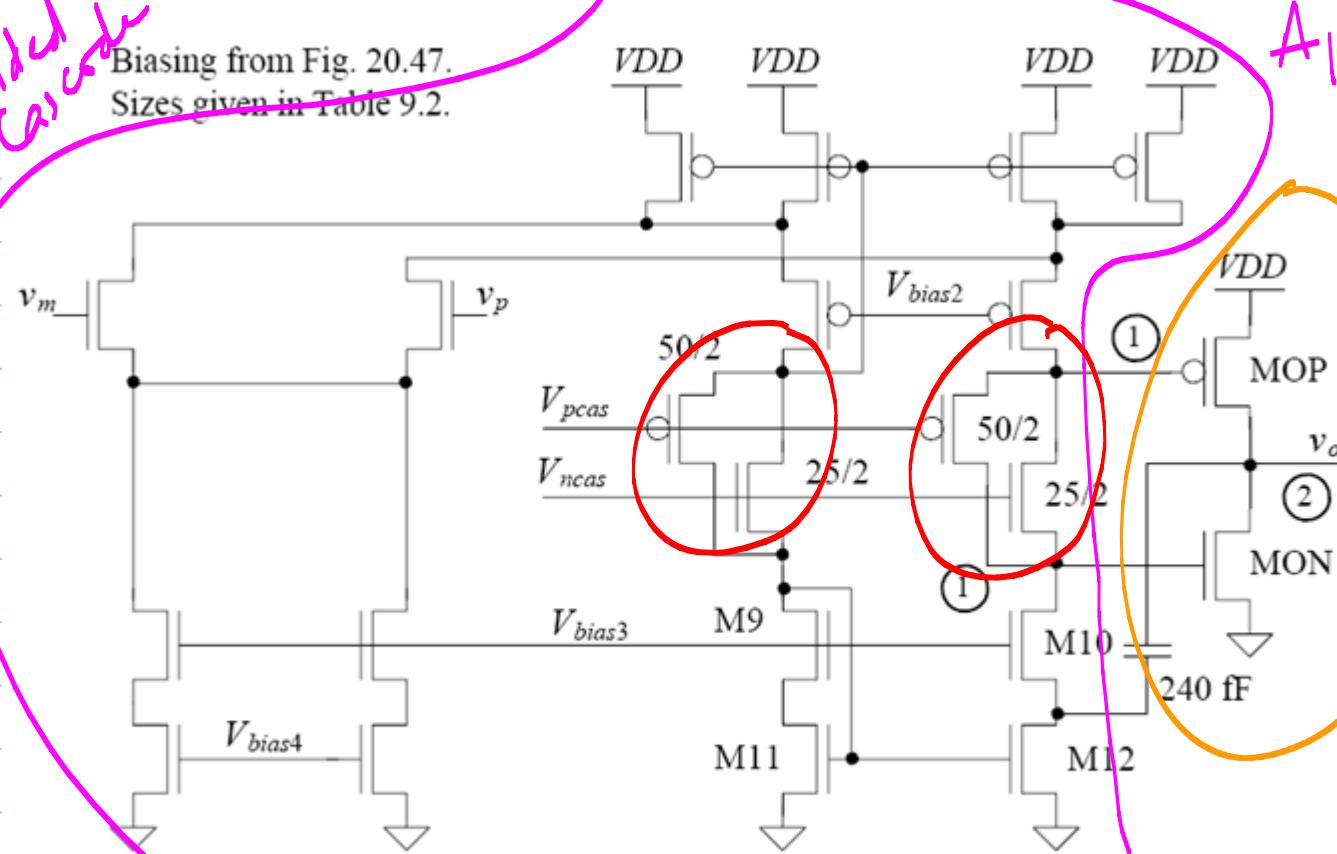


Figure 24.44 Folded-cascode op-amp with class AB output buffer.