
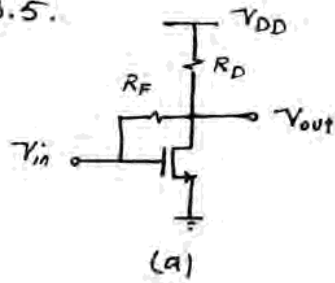


3.5.

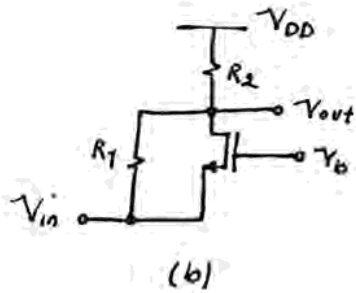


$$\frac{V_o - V_{in}}{R_F} + g_{m1} V_{in} + \frac{V_o}{r_{o1}} + \frac{V_o}{R_D} = 0$$

$$A_V = \frac{V_o}{V_{in}} = - \frac{g_{m1} - 1/R_F}{\frac{1}{R_F} + \frac{1}{r_{o1}} + \frac{1}{R_D}}$$



$$\frac{V_o}{R_2} + (V_o - V_{in}) \left(\frac{1}{R_1} + \frac{1}{r_{o1}} \right) - g_{m1} V_{in} = 0$$
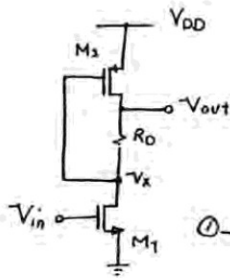
$$\frac{V_o}{V_{in}} = \frac{g_{m1} + \frac{1}{R_1} + \frac{1}{r_{o1}}}{\frac{1}{R_2} + \frac{1}{R_1} + \frac{1}{r_{o1}}}$$



$$\textcircled{1} (g_{m1} V_{in} + \frac{V_x}{r_{o1}}) R_D + V_x = V_{out}, \quad \textcircled{2} (g_{m2} V_x + \frac{V_{out}}{r_{o2}}) = g_{m1} V_{in} + \frac{V_x}{r_{o1}},$$

$$\textcircled{2} \rightarrow V_x (-g_{m2} - \frac{1}{r_{o1}}) = g_{m1} V_{in} + \frac{V_{out}}{r_{o2}} \quad \textcircled{2} \rightarrow V_x = - \frac{g_{m1} V_{in} + \frac{V_{out}}{r_{o2}}}{g_{m2} + \frac{1}{r_{o1}}} \quad \textcircled{3}$$

$$\textcircled{1} \rightarrow g_{m1} R_D V_{in} + (1 + \frac{R_D}{r_{o1}}) V_x = V_o \quad \textcircled{4}$$


(d)

$$\textcircled{3}, \textcircled{4} \rightarrow g_{m1} R_D V_{in} - \frac{(1 + \frac{R_D}{r_{o1}})(g_{m1} V_{in} + \frac{V_{out}}{r_{o2}})}{g_{m2} + \frac{1}{r_{o1}}} = V_{out}$$

$$\left[g_{m1} R_D - \frac{g_{m1} (1 + R_D/r_{o1})}{g_{m2} + \frac{1}{r_{o1}}} \right] V_{in} = \left[1 + \frac{\frac{1}{r_{o2}} (1 + R_D/r_{o1})}{g_{m2} + \frac{1}{r_{o1}}} \right] V_{out}$$

$$\left[g_{m1} R_D (g_{m2} + \frac{1}{r_{o1}}) - g_{m1} (1 + \frac{R_D}{r_{o1}}) \right] V_{in} = \left[g_{m2} + \frac{1}{r_{o1}} + \frac{1}{r_{o2}} (1 + \frac{R_D}{r_{o1}}) \right] V_{out}$$
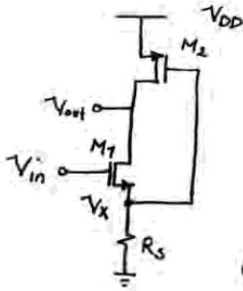
$$\frac{V_{out}}{V_{in}} = \frac{g_{m1} (g_{m2} R_D - 1)}{g_{m2} + \frac{1}{r_{o1}} + \frac{1}{r_{o2}} (1 + \frac{R_D}{r_{o1}})}$$



$$- \left(\frac{V_{out}}{r_{o2}} + g_{m2} V_x \right) = \frac{V_{out} - V_x}{r_{o1}} + g_{m1} (V_{in} - V_x) = \frac{V_x}{R_S} \quad \textcircled{1} \quad \textcircled{2} \quad \textcircled{3}$$


$$\textcircled{1}, \textcircled{3} \rightarrow V_x = - \frac{V_{out}}{r_{o2} (g_{m2} + \frac{1}{R_S})}$$

$$\textcircled{2}, \textcircled{3} \rightarrow \frac{V_{out}}{r_{o1}} + g_{m1} V_{in} = - \frac{V_{out}}{r_{o2} (g_{m2} + \frac{1}{R_S})} \left(\frac{1}{R_S} + g_{m1} + \frac{1}{r_{o1}} \right)$$

(e)

$$\frac{V_{out}}{r_{o1}} \cdot r_{o2} (g_{m2} + \frac{1}{R_S}) + g_{m1} V_{in} \cdot r_{o2} (g_{m2} + \frac{1}{R_S}) = -V_{out} \left(\frac{1}{R_S} + g_{m1} + \frac{1}{r_{o1}} \right)$$
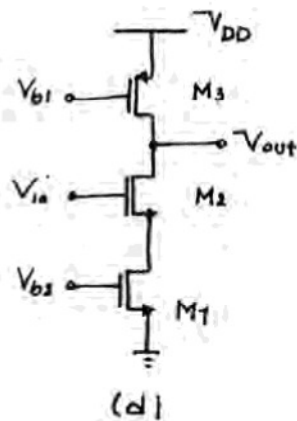
$$\frac{V_{out}}{V_{in}} = - \frac{g_{m1} (g_{m2} + 1/R_S) r_{o2}}{g_{m1} + \frac{1}{R_S} + \frac{1}{r_{o1}} \left[1 + r_{o2} (g_{m2} + \frac{1}{R_S}) \right]}$$




$$G_m = \frac{g_{m2} \cdot r_{o2}}{r_{o1} + \left[(1 + g_{m2} \cdot r_{o1}) r_{o2} \right]}$$

$$R_{out} = r_{o3} \parallel \left[(1 + g_{m2} \cdot r_{o1}) r_{o2} + r_{o1} \right]$$

$$\frac{V_{out}}{V_{in}} = - \frac{g_{m2} \cdot r_{o2} \cdot r_{o3}}{r_{o3} + (1 + g_{m2} \cdot r_{o1}) r_{o2} + r_{o1}}$$

3.6.

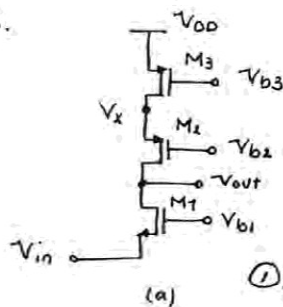


$$\begin{aligned} \textcircled{1} \quad -\frac{V_x}{r_{o3}} &= g_{m2} V_x + \frac{V_x - V_{out}}{r_{o2}} = \frac{V_{out} - V_{in}}{r_{o1}} - g_{m1} V_{in} \\ \textcircled{2} \quad & \\ \textcircled{3} \quad & \end{aligned}$$

$$\textcircled{1}, \textcircled{2} \rightarrow V_x = \frac{V_{out}}{1 + r_{o2} \left(g_{m2} + \frac{1}{r_{o3}} \right)}$$

$$\textcircled{1}, \textcircled{3} \rightarrow \frac{V_{out} - V_{in}}{r_{o1}} - g_{m1} V_{in} = - \frac{V_{out}}{r_{o3} + r_{o2} (1 + g_{m2} \cdot r_{o3})}$$

$$V_{out} \left[\frac{1}{r_{o1}} + \frac{1}{r_{o3} + r_{o2} (1 + g_{m2} \cdot r_{o3})} \right] = \left(g_{m1} + \frac{1}{r_{o1}} \right) V_{in}$$

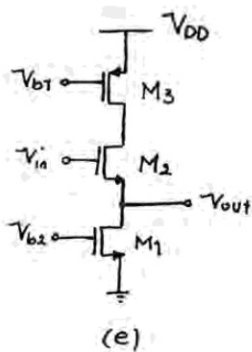
$$\frac{V_{out}}{V_{in}} = \frac{(1 + g_{m1} \cdot r_{o1}) \left[r_{o3} + r_{o2} (1 + g_{m2} \cdot r_{o3}) \right]}{r_{o1} + r_{o3} + r_{o2} (1 + g_{m2} \cdot r_{o3})}$$



resistance seen looking up at the source of M_2

$$R_{in} = \frac{r_{o3} + r_{o2}}{1 + g_{m2} \cdot r_{o2}}$$
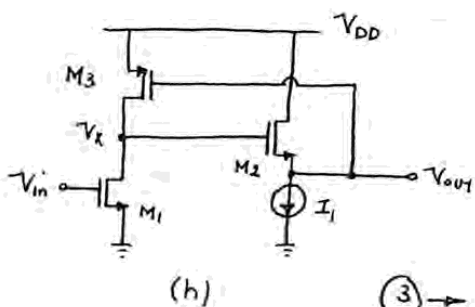
$$\frac{V_{out}}{V_{in}} = \frac{r_{o1}}{r_{o1} + \frac{r_{o3} + r_{o2}}{1 + g_{m2} r_{o2}}} = \frac{r_{o1} (1 + g_{m2} \cdot r_{o2})}{r_{o1} (1 + g_{m2} \cdot r_{o2}) + r_{o2} + r_{o3}}$$



$$\textcircled{1} \quad -\left(\frac{V_x}{r_{o3}} + g_{m3} V_{out}\right) = g_{m1} V_{in} + \frac{V_x}{r_{o1}} \quad \textcircled{2}$$

$$\textcircled{3} \quad -\frac{V_{out}}{r_{o2}} + g_{m2} (V_x - V_{out}) = 0 \quad \text{@ output node}$$

$$\textcircled{3} \rightarrow V_x = \frac{\frac{1}{r_{o2}} + g_{m2}}{g_{m2}} \cdot V_{out} = \frac{1 + g_{m2} r_{o2}}{g_{m2} r_{o2}} V_{out}$$

$$\textcircled{1}, \textcircled{2} \rightarrow -\left[\left(\frac{1}{r_{o3}} + \frac{1}{r_{o1}}\right) \frac{1 + g_{m2} \cdot r_{o2}}{g_{m2} \cdot r_{o2}} + g_{m3}\right] V_{out} = g_{m1} V_{in}$$

$$\frac{V_{out}}{V_{in}} = -\frac{g_{m1} \cdot g_{m2} \cdot r_{o1} \cdot r_{o2} \cdot r_{o3}}{(r_{o1} + r_{o3})(1 + g_{m2} \cdot r_{o2}) + g_{m2} g_{m3} r_{o1} r_{o2} r_{o3}}$$