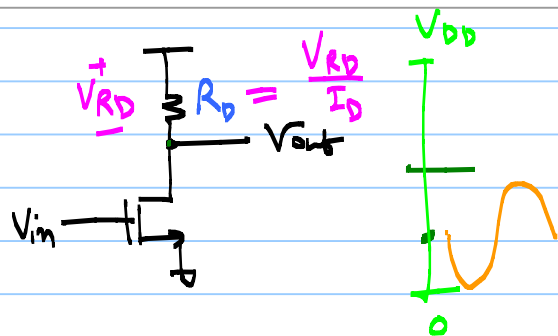


ECE 511 - Lecture 10

Note Title

2/21/2013






$$\begin{aligned}
 A_v &= -g_m R_D \\
 &= -\sqrt{2k_p n \frac{W}{L} I_D} \cdot R_D \\
 &= -\sqrt{2k_p n \frac{W}{L} I_D} \cdot \frac{V_{RD}}{I_D} \\
 &= -\sqrt{2k_p n \frac{W}{L}} \cdot \frac{V_{RD}}{\sqrt{I_D}}
 \end{aligned}$$

* $\frac{W}{L} \uparrow \Rightarrow$ large device cap

* $R_D \uparrow \Rightarrow V_{RD} \uparrow \Rightarrow$ lower swings

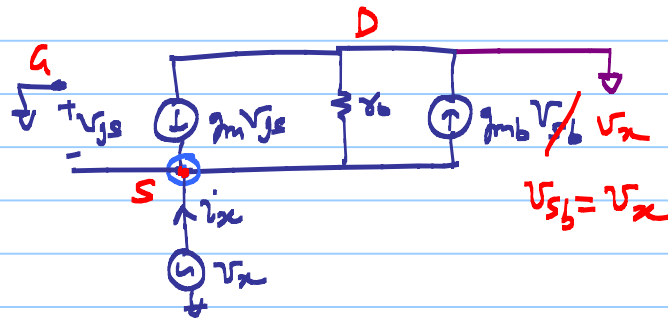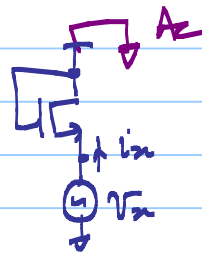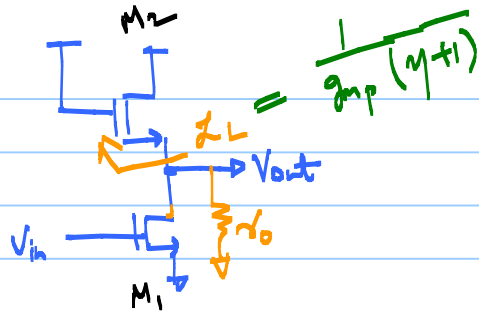* $I_D \downarrow \Rightarrow g_m \downarrow \Rightarrow f_T \downarrow \Rightarrow$ lower speed




$$g_m V_{gs} - g_{mb} V_x - \frac{V_x}{r_o} + i_x = 0$$

$$i_x = V_x \left(\frac{1}{r_o} + g_m + g_{mb} \right)$$

$$\frac{V_x}{i_x} = \frac{1}{g_m + g_{mb} + r_o^{-1}} \approx \frac{1}{g_m + g_{mb}} = \frac{1}{g_m(\gamma+1)}$$

$$r_o \gg \frac{1}{g_m + g_{mb}}$$

$$g_{mb} = \gamma g_m$$

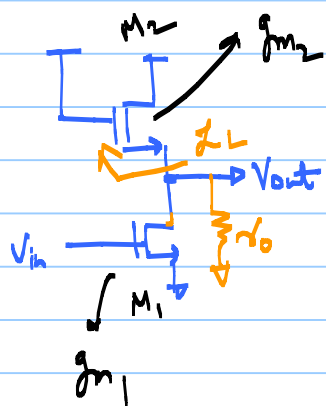


$$A_v = -g_{m1} \frac{1}{g_{m2}(\eta+1)}$$

$$= -\frac{g_{m1}}{g_{m2}} \cdot \frac{1}{\eta+1}$$

$$g_{m2} \ll g_{m1}$$

$$\Rightarrow \left(\frac{W}{L}\right)_2 \ll \left(\frac{W}{L}\right)_1$$

DC Biasing is implied

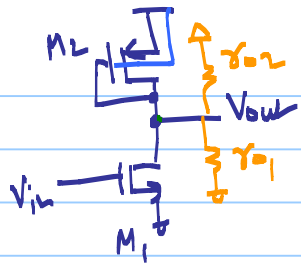


$$A_v = -g_{m1} \cdot r_{O1} \parallel r_{O2} \parallel \frac{1}{g_{m2}}$$


"low gain"

$$\approx -\frac{g_{m1}}{g_{m2}} = -\frac{\sqrt{2\beta_1 I_D}}{\sqrt{2\beta_2 I_D}}$$
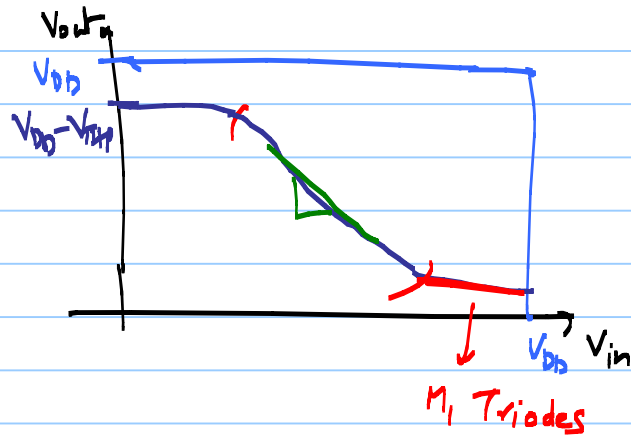
$$= -\frac{\sqrt{(W/L)_1}}{\sqrt{(W/L)_2}} \quad \text{"linear"}$$





* Swing is limited on the output

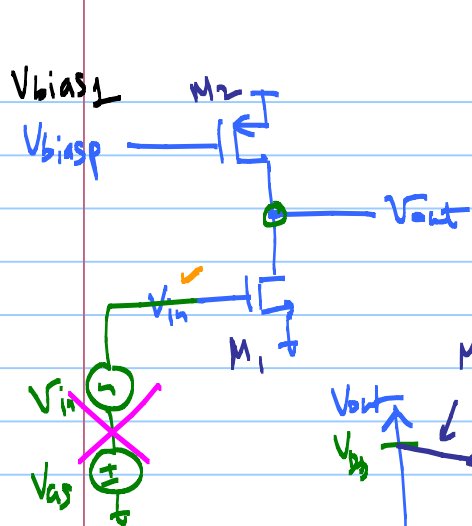


$$A_v = -g_{m1} \cdot (r_{o1} \parallel r_{o2})$$

larger gain

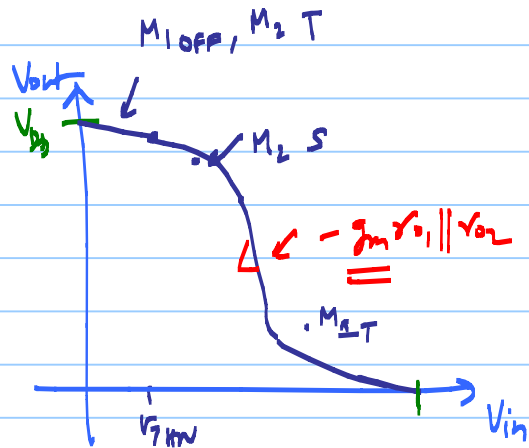
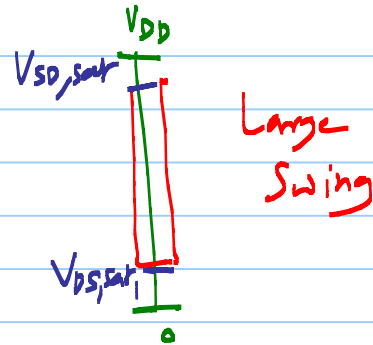
$$\sim g_m r_o \propto \frac{L}{V_{ov}}$$



"Large signal"

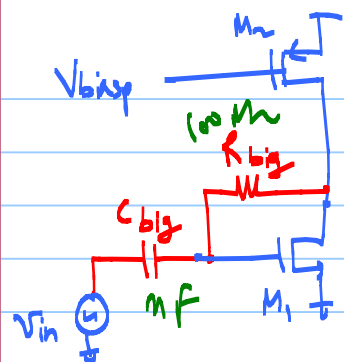

DC picture

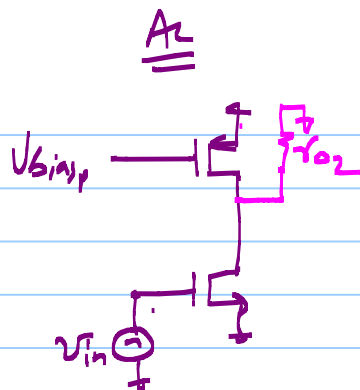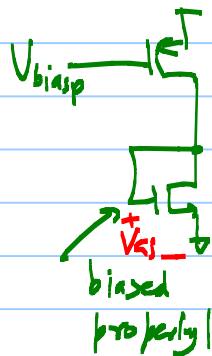

$$A_v = -g_m r_{o1} \parallel r_{o2}$$

↳ non-linearity

$$V_{in} \uparrow \Rightarrow V_{ov} \uparrow \Rightarrow g_m \uparrow$$

$$g_m = f(V_{in})$$


Source - Degeneration



* When all the dropped across R_S

$$i_d \approx \frac{V_{in}}{R_S}$$


$$V_{out} \approx - i_d \cdot R_D =$$
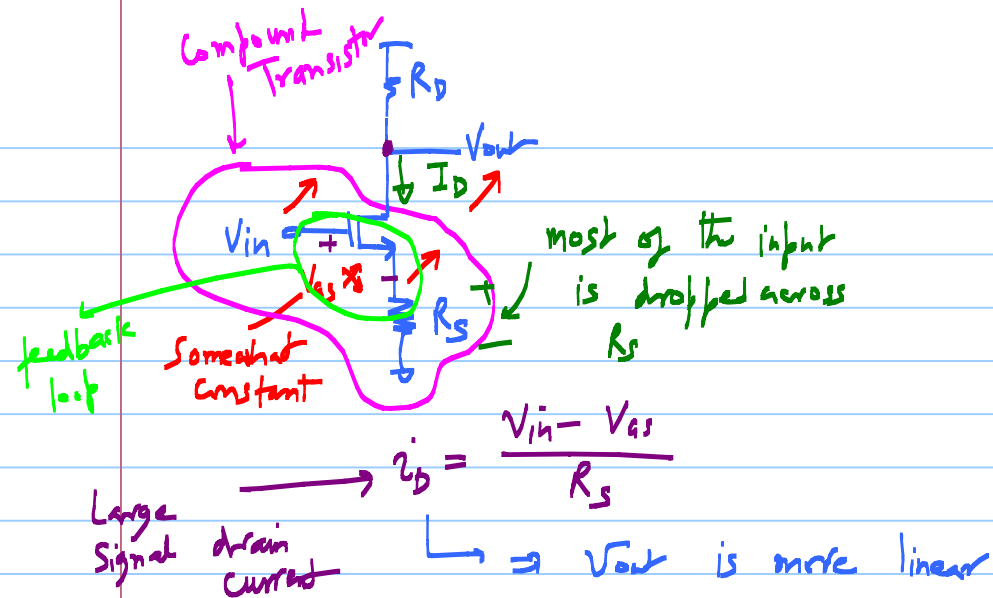
$$\Rightarrow A_v \approx - \frac{R_D}{R_S}$$



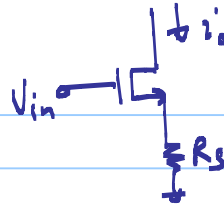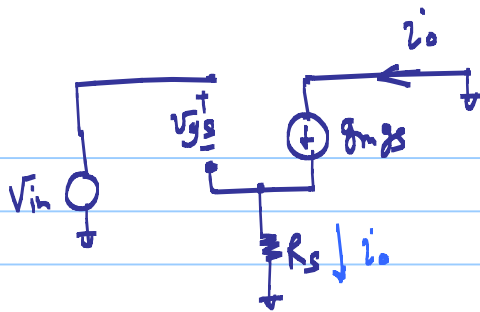
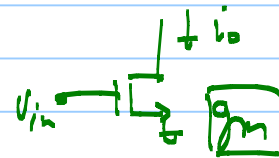
$$\begin{aligned} \gamma &= 0 \\ \lambda &= 0 \end{aligned}$$



$$V_{gs} = V_{in} - i_o R_s \rightarrow (1)$$

$$i_o = g_m V_{gs} \rightarrow (2)$$

$$i_o (1 + g_m R_s) = g_m V_{in}$$

$$\boxed{\frac{i_o}{V_{in}} = \frac{g_m}{1 + g_m R_s} = g_m}$$

transconductance
of the compound device

$$A_v = - g_m R_D$$

$$= - \frac{g_m R_D}{(1 + g_m R_s)}$$

open loop gain

g_m

$$e_{gm} = \frac{g_m}{1 + g_m R_s}$$

large W device
 $\frac{1}{g_m} \ll R_s$

$$\approx \frac{1}{R_s}$$




linear

- (+) higher linearity
- (-) lower gain
- (-) higher noise

with $\lambda \gg 0$

$$e_{gm} = \frac{g_m r_o}{R_s + [1 + (g_m + g_{mb}) R_s] r_o}$$

HW Exercise

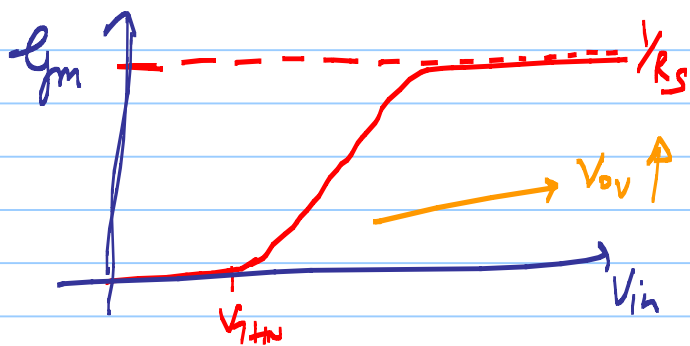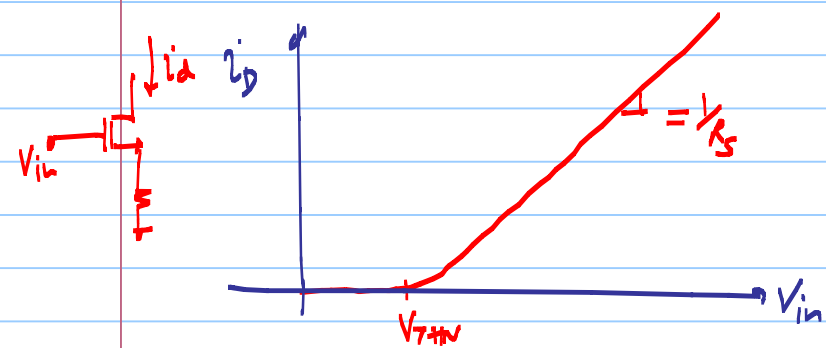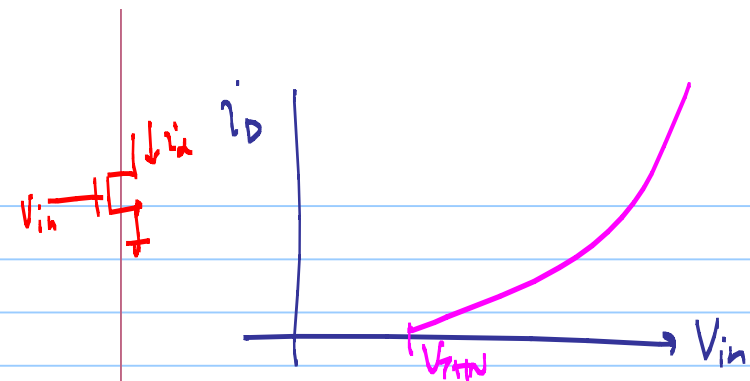

$$i_D = \frac{V_{in} - V_{thn}}{R_S}$$