
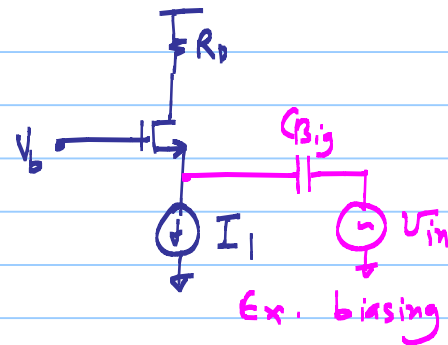
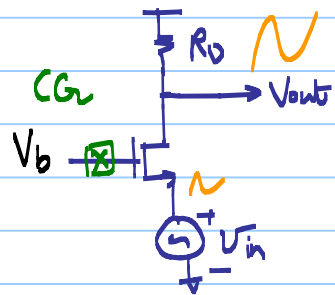




ECE 511 - Lecture 12

Note Title

2/28/2013

Common Gate Stage

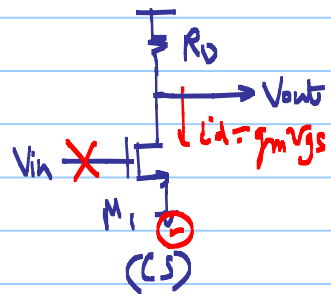

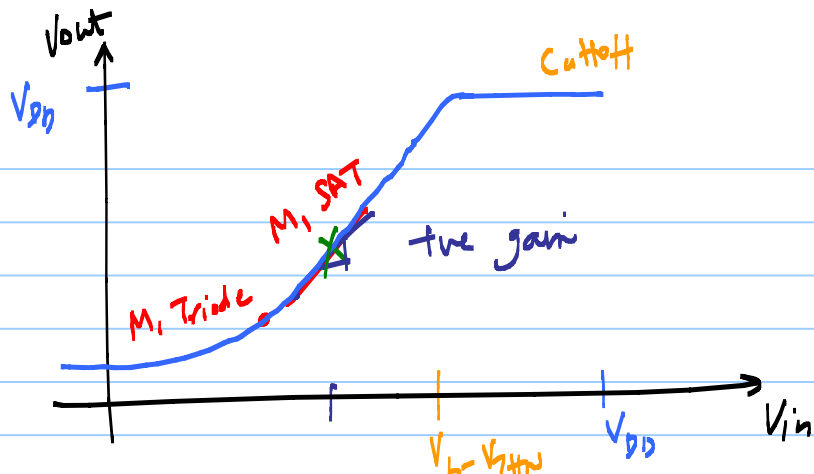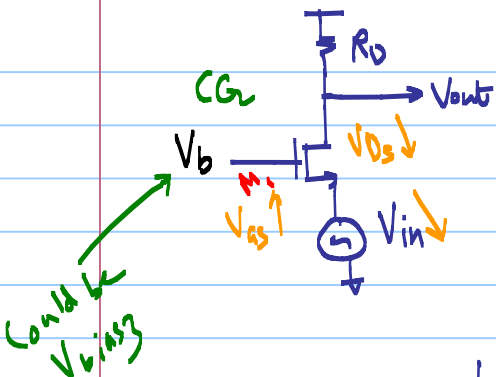

$$V_{out} = f(V_{in})$$

$$A_v = \frac{\partial V_{out}}{\partial V_{in}}$$

$$V_{out} = V_{DD} - \frac{\beta}{2} (V_b - V_{in} - V_{thn})^2 R_D$$


$$A_v = \frac{\partial V_{out}}{\partial V_{in}} = -\frac{\beta}{2} \times 2 (V_b - V_{in} - V_{thn}) \cdot R_D \cdot$$

$$-\frac{\beta}{2} (V_b - V_{in} - V_{thn}) \cdot \frac{\partial V_{thn}}{\partial V_{in}} \cdot R_D$$

$$= \beta (V_b - V_{in} - V_{thn}) \left(1 + \frac{\partial V_{thn}}{\partial V_{gs}} \right) R_D$$

$$= \beta \underbrace{(V_b - V_{in} - V_{thn})}_{V_{gs}} \cdot R_D \cdot (1 + \eta)$$
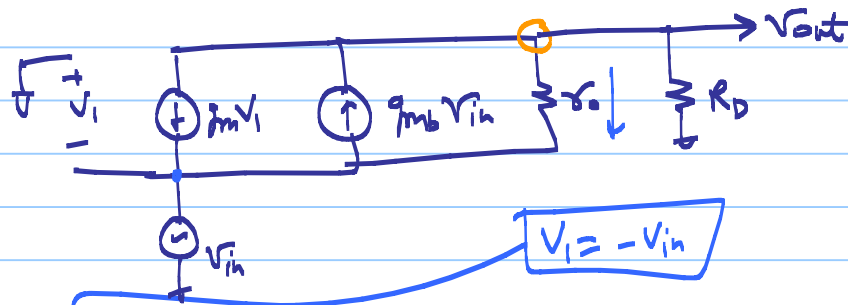
$$A_v = + \underbrace{g_m R_D}_{\text{CS gain}} (M+1)$$



$$-g_m V_1 + g_{m_b} V_{in} - \left(\frac{V_{out} - V_{in}}{r_o} \right) - \frac{V_{out}}{R_D} = 0$$

$$\Rightarrow V_{in} (g_m + g_{m_b}) + \frac{V_{in}}{r_o} = \frac{V_{out}}{r_o \parallel R_D}$$

$$\Rightarrow A_v = \frac{(g_m + g_{m_b}) r_o + 1}{r_o} \times \frac{R_D r_o}{R_D + r_o}$$

$$= \frac{(g_m + g_{m_b}) r_o + 1}{R_D + r_o} \cdot R_D$$

$$\frac{1}{r_o \parallel R_D} = \frac{1}{r_o} + \frac{1}{R_D}$$



$$(g_o + g_D) = g_o + g_D$$

ASIDE

$$\text{For } r_0 \gg R_D \text{ \& } g_m r_0 \gg 1$$

$$\Rightarrow A_v = (g_m + g_{mb}) R_D = \boxed{+ (\gamma + 1) g_m R_D}$$

Input impedance:

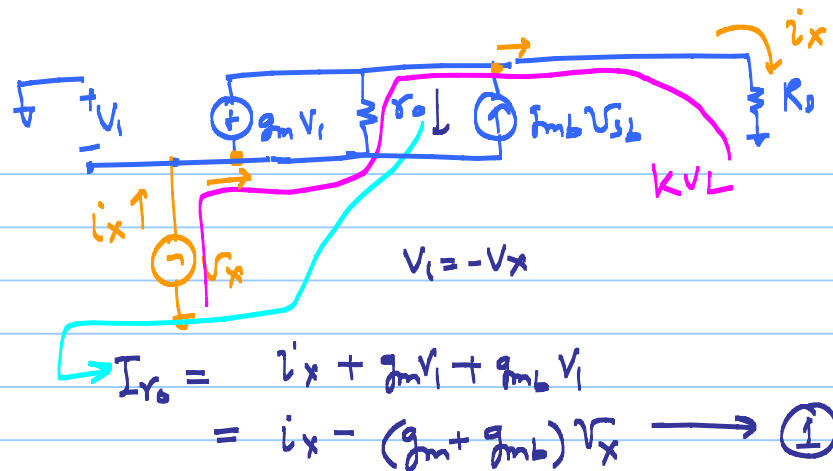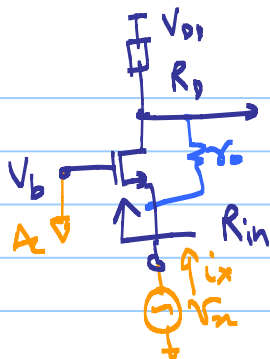

* Adding up the voltages across r_o & R_D

$$R_D i_x + r_o [i_x - (g_m + g_{mb}) V_x] = V_x$$

$$R_{in} = \frac{V_x}{i_x} = \frac{R_D + r_o}{(g_m + g_{mb}) r_o}$$

$$(g_m + g_{mb}) r_o \gg 1$$

$$R_{in} \approx \frac{R_D}{(g_m + g_{mb}) r_o} + \frac{1}{(g_m + g_{mb})}$$

Case I:


$$R_D \ll (g_m + g_{mb}) r_o \quad \approx r_o \text{ or smaller}$$

* R_D can't be a cascoded
CM load

$$R_{in} \approx \frac{1}{g_m + g_{mb}}$$

Case II:


$$R_D = 0$$

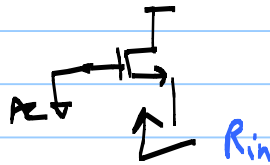

Same case as a SF

$$R_{in} \approx \frac{1}{g_m + g_{mb}}$$

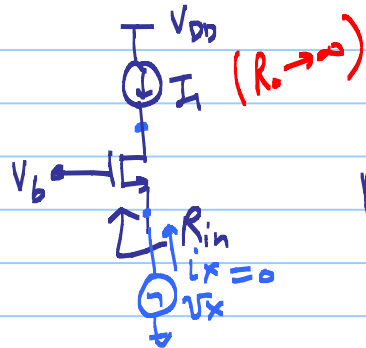Case III: $R_D \rightarrow$ ideal current source





$$R_{in} = \frac{R_D}{(g_m + g_{m6}) r_o} \rightarrow \infty$$

input impedance is large

Case IV $R_D = g_m r_o^2$

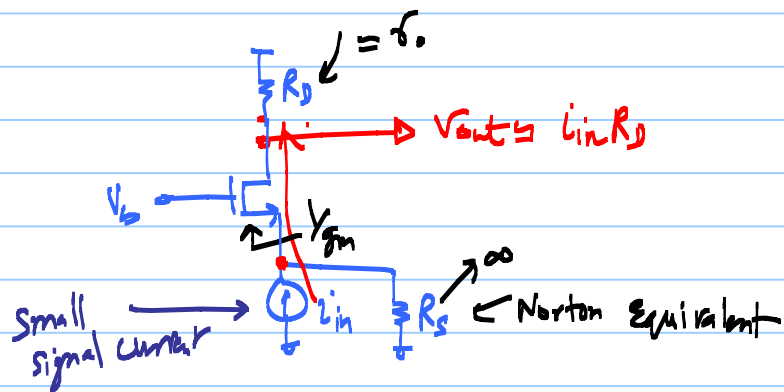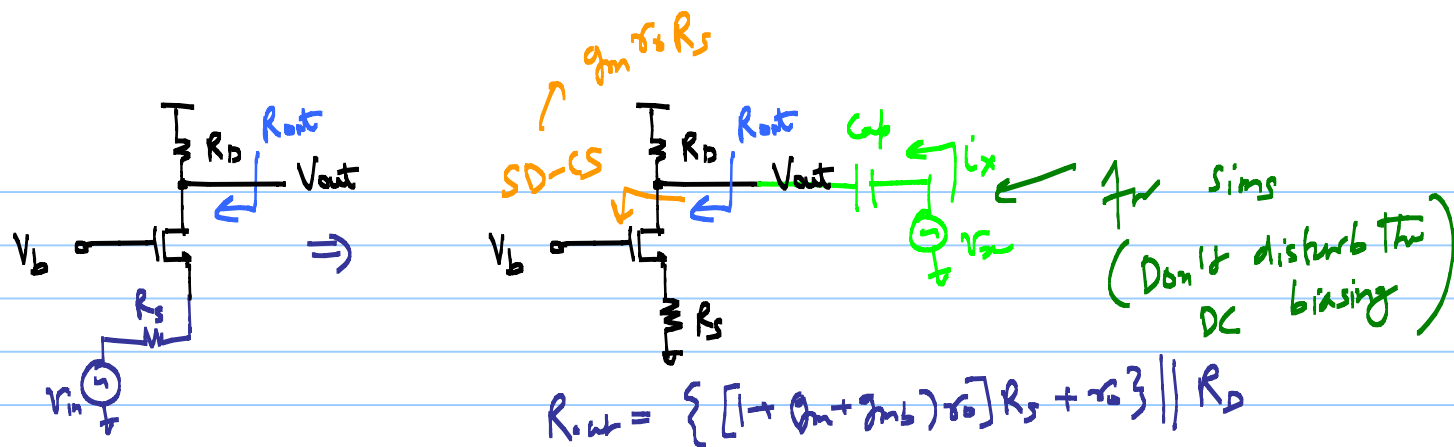
$$R_{in} \leq r_o \leftarrow \text{large}$$



"CG stage makes a good current buffer"

Type	Gain	Z_{in}	Z_{out}	Application
CS	Large	∞	Moderate (≈ 1)	(Voltage) Amplifier
CS + SD	Moderate	∞	High/Moderate	→ Linear amplifier
CD/SF	Low (≤ 1)	∞	Low	→ Voltage Buffer
CC	Medium/High	Low	Moderate/High	→ Current Buffer

Cascode Stage

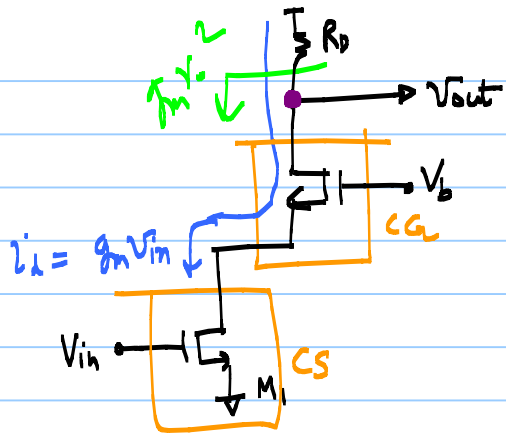

$$\begin{aligned} V_{out} &= -g_m v_{in} (R_D \parallel R_{out}) \\ &= -g_m^2 r_o^2 \\ &= -(g_m r_o)^2 \end{aligned}$$


Lemma: In a linear circuit:
Voltage gain = $-g_m \cdot R_{out}$

where $g_m \rightarrow$ transconductance of the circuit when the output is shorted to ground

$R_{out} \rightarrow$ output resistance of the circuit when the input is set to zero.


Norton Equiv. of the output stage

Proof:

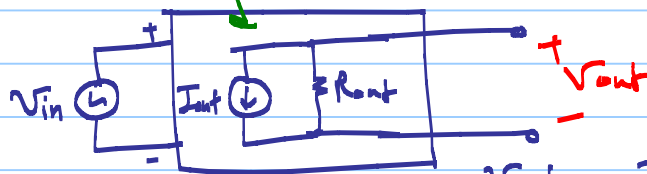



Claim: $V_{out} = -g_m R_{out} \cdot V_{in}$

$$V_{out} = -I_{out} \cdot R_{out}$$

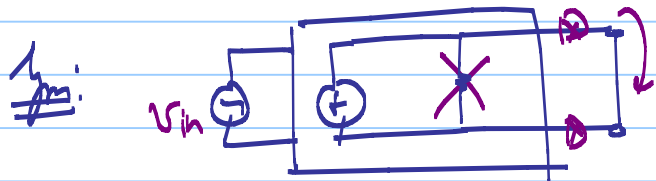


$$I_{sc} = -I_{out}$$
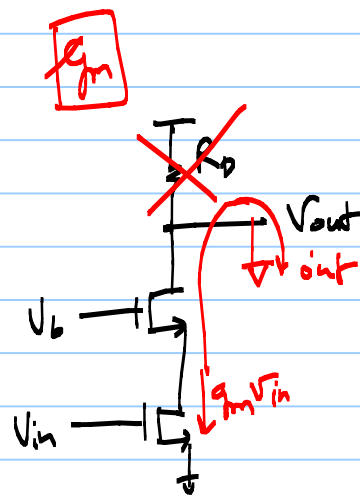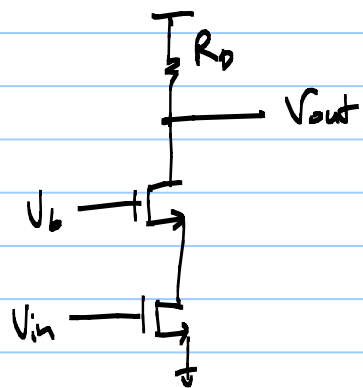
$$\Rightarrow g_m \triangleq \frac{I_{out}}{V_{in}}$$



$$i_{out} = g_m V_{in}$$

R_{out}

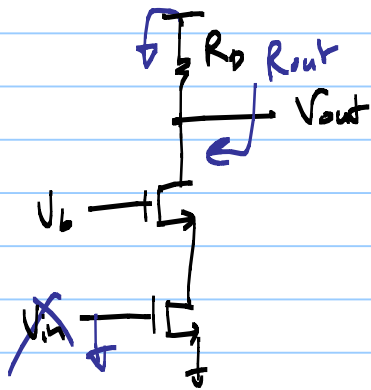

$$(R_D \parallel g_{m2} r_{o2})$$

$$R_D \gg g_{m1} r_{o1}^2$$

$$A_v = - g_{m1} (R_D \parallel g_{m2} r_{o2})$$

$$\approx - (g_{m1} r_{o1})^2$$