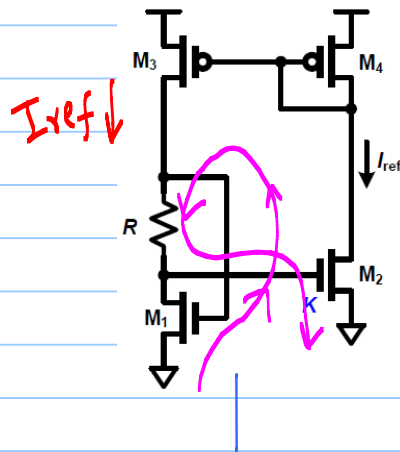


# 'ECE 511 - Lecture 14

Note Title

3/7/2013




$$\lambda = 0$$

$$V_{gs1} - I_{ref} R = V_{gs2}$$

$$\sqrt{\frac{2 I_{ref}}{W/L}} + \cancel{V_{thn}} - I_{ref} R = \sqrt{\frac{2 I_{ref}}{kW/L}} + \cancel{V_{thn}}$$
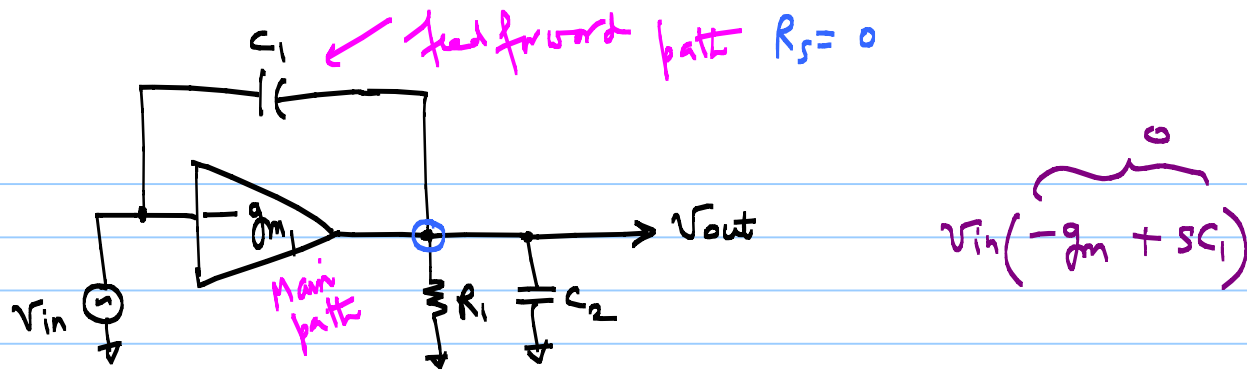
$$\sqrt{\frac{2 I_{ref}}{W/L}} \left( 1 - \frac{1}{\sqrt{k}} \right) = I_{ref} \cdot R$$



$$\boxed{-g_{m1}V_{in}} - \frac{V_{out}}{sC_2} - \frac{V_{out}}{R_1} - \frac{(V_{out} - V_{in})}{\boxed{1/sC_1}} = 0$$

$$\Rightarrow (-g_{m1} + sC_1)V_{in} = V_{out}\left[\frac{1}{R_1} + sC_2 + sC_1\right]$$



$$\Rightarrow \frac{V_{out}}{V_{in}}(s) = \frac{-(g_{m1} - sC_1)}{\frac{1}{R_1} + s(C_1 + C_2)}$$

$$A_v = -g_{m1}R_1$$

$$\omega_z = +g_{m1}/C_1 \quad \text{"RHP"}$$


$$\omega_p = \frac{1}{R_1(C_1 + C_2)}$$

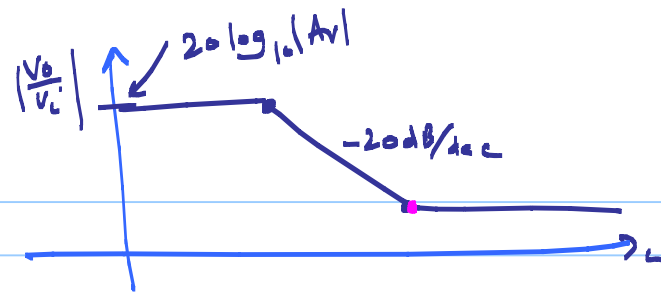
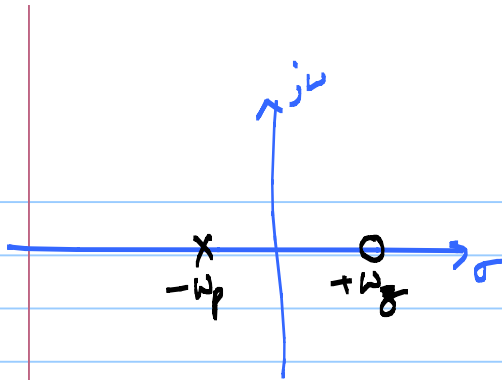
$$= -g_{m1}R_1 \cdot \frac{\left(1 - \frac{sC_1}{g_{m1}}\right)}{1 + sR_1(C_1 + C_2)} = \boxed{A_v \frac{(1 - s/\omega_z)}{(1 + s/\omega_p)}}$$



$$\angle \frac{V_o}{V_i} = -\tan^{-1}\left(\frac{\omega}{\omega_z}\right) - \tan^{-1}\left(\frac{\omega}{\omega_p}\right)$$



RHF zero looks like  
~ pole

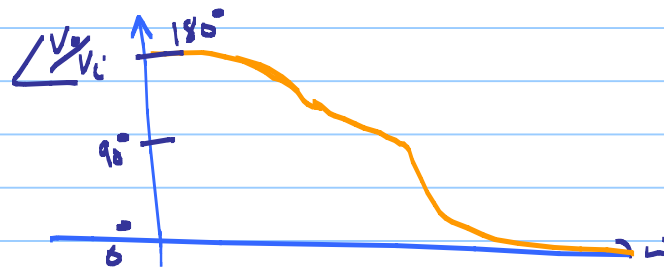

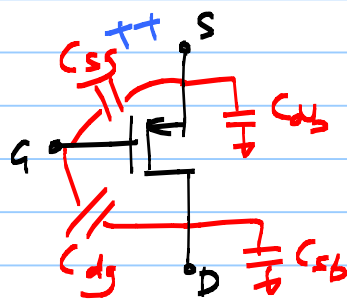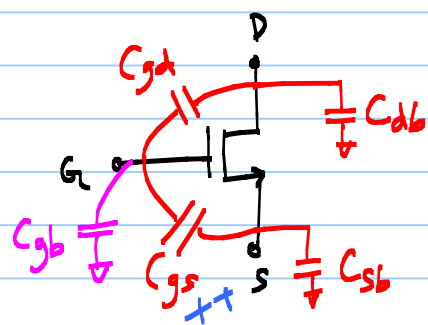


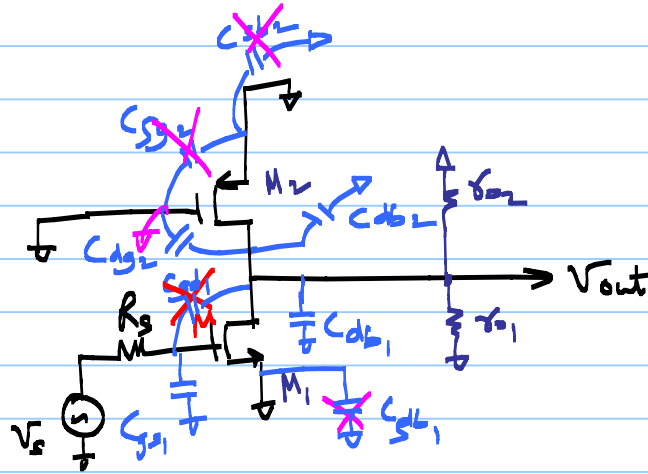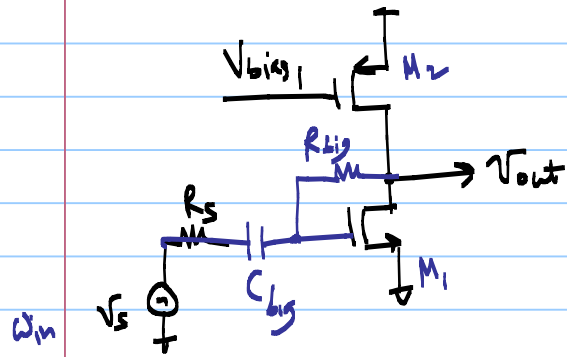
# CS Stage

$$\omega_{in} \gg \frac{1}{R_{bi} C_{bi}}$$



Using Miller's Appx.

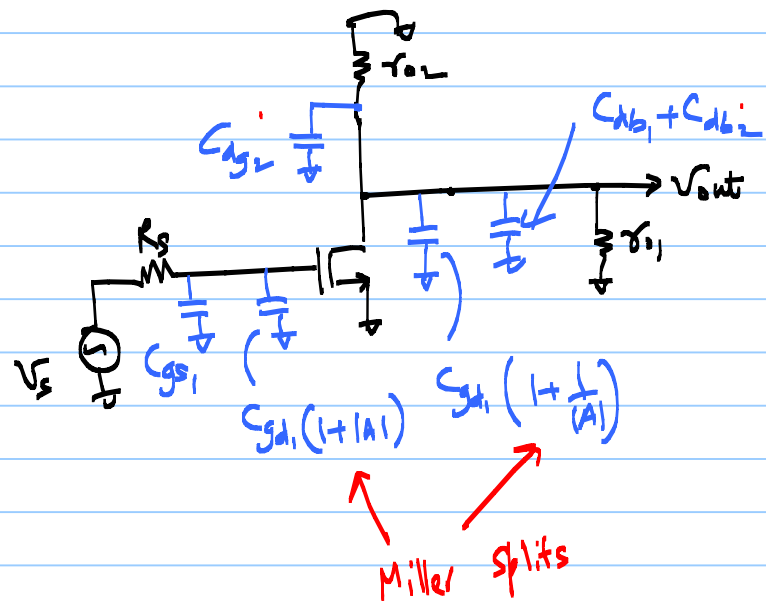

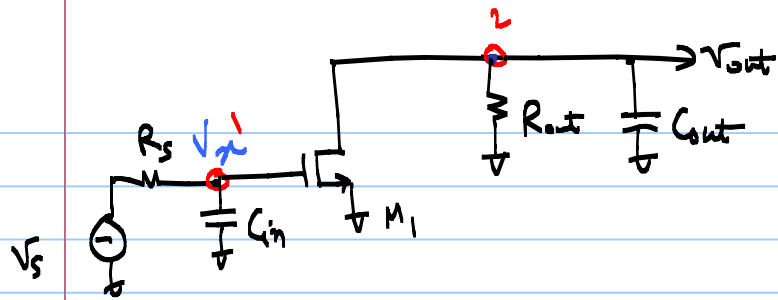

Small signal  $R$  &  $C$ 's

$$R_{out} = r_{o1} \parallel r_{o2}$$

$$C_{in} = C_{gs1} + C_{gd1}(1 + |A|)$$

$$C_{out} = C_{gd1}\left(1 + \frac{1}{|A|}\right) + C_{ab}$$

$$A = -g_{m1} R_{out}$$

$$\omega_{in} = \frac{1}{R_s C_{in}} = \frac{1}{R_s [C_{gs1} + (1 + |A|) C_{gd1}]} \quad \checkmark$$

$$\omega_{out} = \frac{1}{R_{out} C_{out}} = \frac{1}{(r_{o1} \parallel r_{o2}) [C_{gd1} + C_{ab}]} \quad \checkmark$$

$$\omega_z = \frac{g_{m1}}{C_{gd1}} \quad \text{RHP zero}$$


$$\frac{v_{out}}{v_{in}}(s) = \frac{A_v \left(1 - \frac{s}{\omega_z}\right)}{(1 + s/\omega_{in})(1 + s/\omega_{out})}$$

← Miller misses this zero!

Draw the equivalent circuit

$$R_o = r_{o1} || r_{o2}$$

$$C_o = C_{d1} + C_{d2}$$

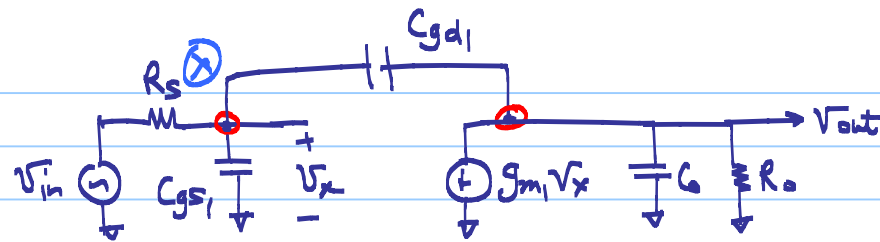

$$\textcircled{1} \Rightarrow \frac{V_x - V_{in}}{R_s} + V_x C_{gs} s + (V_x - V_{out}) C_{gd1} s = 0$$

$$\textcircled{2} \Rightarrow (V_{out} - V_x) C_{gd1} s + g_{m1} V_x + V_{out} \left( \frac{1}{R_o} + s C_o \right) = 0$$

Solve for  $V_x$  & substitute in  $\textcircled{1}$

$$V_x = - \frac{V_{out} (C_{gd1} s + \frac{1}{R_o} + C_o s)}{g_{m1} - s C_{gd1}}$$

$$\frac{V_{out}}{V_{in}}(s) = \frac{(C_{gd1}s - g_{m1})R_o}{R_s R_o \xi s^2 + \underbrace{[R_s(1 + g_{m1}R_o)C_{gd1} + R_s C_{gs1} + R_o(C_{gd1} + C_{db})]}_{\xi} s + 1}$$

$\xi \rightarrow z_{ci}$

$\xi = C_{gs1}C_{gd1} + C_{gs1}C_o + C_{gd1}C_o \rightarrow \frac{1}{\omega_{p1}}$


2<sup>nd</sup>-order TF  $\Rightarrow$  2 nodes interacting from  $g_{d1}$

$$N^r = (sC_{gd1} - g_{m1})R_o = \underbrace{-g_{m1}R_o}_{A_v} \left(1 - \frac{s}{\omega_z}\right)$$

$\frac{g_{m1}}{C_{gd1}}$

$$D(s) = \frac{s^2}{\omega_n^2} + 2\zeta \frac{s}{\omega_n} + 1$$

Dr

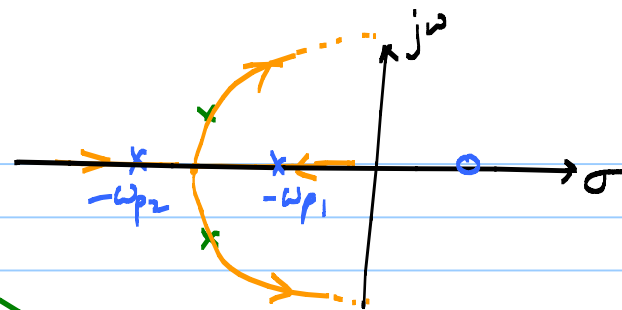

if we have  $|\omega_{p1}| \ll |\omega_{p2}|$

$$D(s) = \left(\frac{s}{\omega_{p1}} + 1\right) \left(\frac{s}{\omega_{p2}} + 1\right)$$

$$= \frac{s^2}{\omega_{p1}\omega_{p2}} + \left(\frac{1}{\omega_{p1}} + \frac{1}{\omega_{p2}}\right)s + 1$$

$$\approx \frac{s^2}{\omega_{p1}\omega_{p2}} + \boxed{\frac{1}{\omega_{p1}}}s + 1$$

coeff<sup>n</sup> of 's'

$$\omega_{p1} = \frac{1}{\underbrace{R_s(1 + g_{m1}R_o)}_{\text{Miller input cap}} C_{gd1} + R_s C_{g_{a1}} + \underbrace{R_o(C_{gd1} + C_o)}_{\text{Extra term}}}$$