

ECE 511 - Lecture 15

Note Title

3/14/2013

$$\omega_{p1} \ll \omega_{p2}$$

$$\omega_{p1} = \frac{1}{R_s [1 + g_m R_o] C_{gd1} + R_s C_{gs1} + R_o (C_{gd1} + C_o)}$$

$$\text{coeff}^n \text{ of } s^2 \Rightarrow \frac{1}{\omega_{p1} \omega_{p2}}$$

$$\Rightarrow \omega_{p2} = \frac{1}{\omega_{p1}} \times \frac{1}{R_s R_o} \quad \text{coeff of } s^2 \text{ in } D(s)$$

$$= \frac{1}{\omega_{p1}} \times \frac{1}{R_s R_o [C_{gs1} C_{gd1} + C_{gs1} C_o + C_{gd1} C_o]}$$

$$= \frac{R_s (1 + g_m R_o) C_{gd1} + R_s C_{gs1} + R_o (C_{gd1} + C_o)}{R_s R_o [C_{gs1} C_{gd1} + C_{gs1} C_o + C_{gd1} C_o]}$$

$$* \quad \underline{C_{gs1}} \gg (1 + g_m R_o) \underline{C_{gd1}} + \frac{R_o}{R_s} \underline{(C_{gd1} + C_o)}$$

$$\omega_{p2} \approx \frac{1}{R_o (C_{gd1} + C_o)}$$

← same as ω_{out}



only valid when C_{gs1} dominates the response

$$\frac{V_{out}}{V_{in}}(s) = \frac{A_v (1 - s/\omega_z)}{(1 + \frac{s}{\omega_{p1}})(1 + \frac{s}{\omega_{p2}})}$$

← RHP zero

zero:
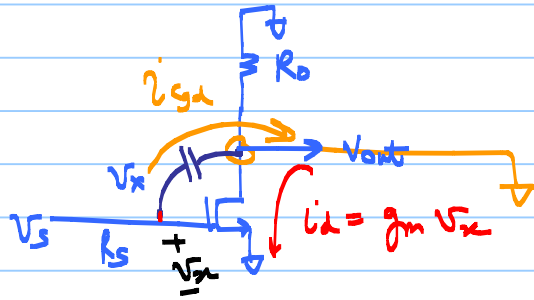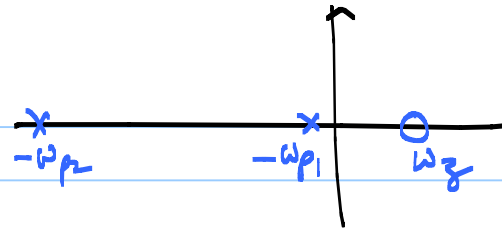
$$\omega_z = \frac{g_m}{C_{gd1}} \longrightarrow RHP$$



@ high frequencies, the feedforward path current adds to the main path in the opposite phase.


@ $\omega = \omega_z \Rightarrow$

$$i_{C_{gd1}} + i_d = 0$$

$$v_x s C_{gd1} - g_m v_x = 0$$

$$\boxed{\omega_z = \frac{g_m}{C_{gd1}}}$$

—

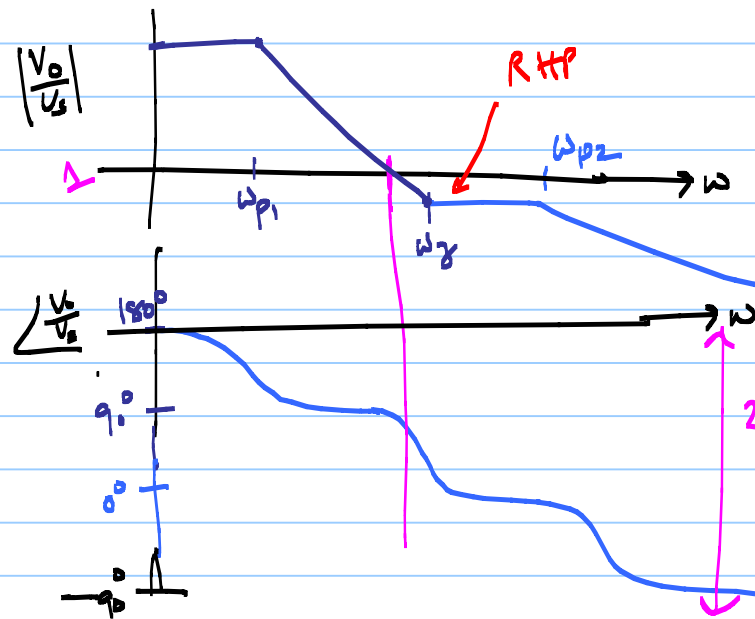

$$\angle = 180^\circ - \tan^{-1}\left(\frac{\omega}{\omega_p}\right) - \tan^{-1}\left(\frac{\omega}{\omega_z}\right) - \tan^{-1}\left(\frac{\omega}{\omega_{p2}}\right)$$

"RHP zero degrades phase"

$$\omega_z = +\frac{g_{m1}}{C_c} \quad @ \text{ RHP}$$

$$C_{gd1} \rightarrow C_c$$

$$A_v = -g_m R_o$$



$$\omega_{p1} = \frac{1}{R_s [(1+|A_v|)C_c + C_{gs1}] + R_o(C_c + C_o)}$$

$$\omega_{p2} = \frac{R_s(1+|A_v|)C_c + R_s C_{gs1} + R_o(C_c + C_o)}{R_s R_o [C_{gs1} C_c + C_{gs1} C_o + C_c C_o]}$$

+ $C_c = 0$ & large C_o $< C_{gs1}$

$$\omega_{p1} \approx \frac{1}{R_s C_{gs1} + R_o C_o}$$
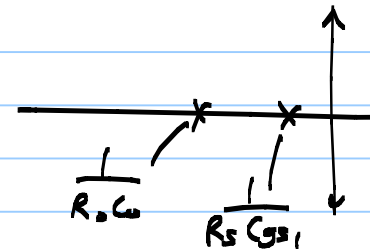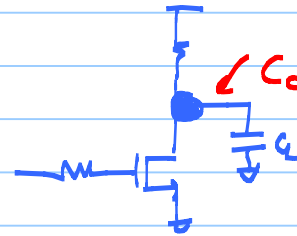
$$\omega_{p2} \approx \frac{\cancel{R_s C_{gs1}} + \cancel{R_o C_o}}{\cancel{R_s R_o} \cancel{C_{gs1} C_o}} \approx \frac{1}{R_o C_o}$$



* Increase C_c :

Consider when $C_c \gg C_{gs1}$

$$\omega_{p1} = \frac{1}{R_s(1 + |A_v|)C_c + R_o(C_c + C_o)}$$

$$\omega_{p2} = \frac{R_s(1 + |A_v|)C_c + \cancel{R_o(C_c + C_o)}}{R_s R_o C_c [C_o + C_{gs1}]}$$

$|A_v| \gg 1$

$$\approx \frac{\cancel{R_s}(1 + g_{m1}R_o)\cancel{C_c}}{\cancel{R_s} R_o(C_o + C_{gs1})\cancel{C_c}}$$

$$\approx \frac{g_{m1} R_o}{R_o(C_o + C_{gs1})}$$

$$\approx \boxed{\frac{g_{m1}}{C_o + C_{gs1}}}$$



	$C_c = 0$	Typical case $C_c \gg C_{gs1} \leftarrow C_c \approx C_0$
ω_{p1}	$\approx \frac{1}{R_s C_{gs1} + R_o C_0}$	$= \frac{1}{R_s (1 + A) C_c + R_o [C_c + C_0]}$ ω_{p1} is smaller
ω_{p2}	$\approx \frac{1}{R_o C_0}$	$\approx \frac{g_{m1}}{C_c + C_{gs1}} \approx \frac{g_{m1}}{C_0} = g_{m1} R_o \left(\frac{1}{R_o C_0} \right)$ ω_{p2} is increased by $(g_{m1} R_o) \Rightarrow$ a large value
ω_z	$\frac{g_{m1}}{C_{gs1}}$	$\frac{g_{m1}}{C_c} \downarrow$

$C_c \uparrow$


"Pole splitting"

$\Rightarrow$


Miller
compensation

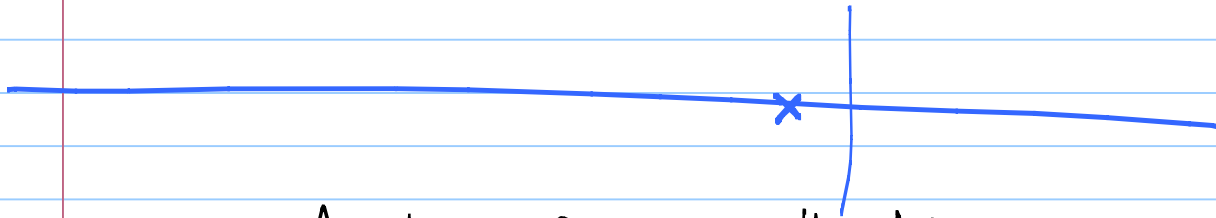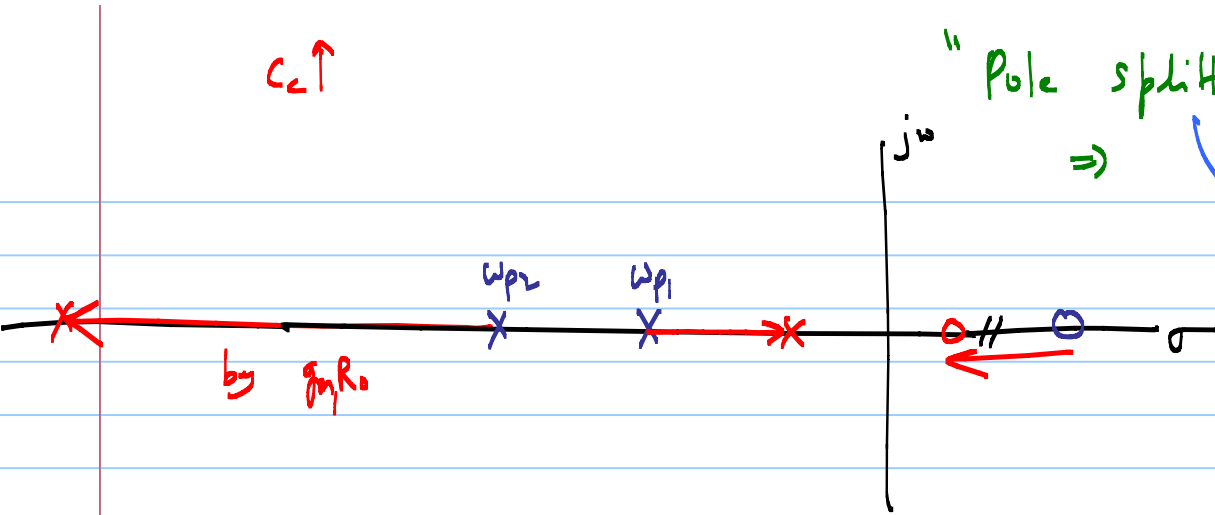

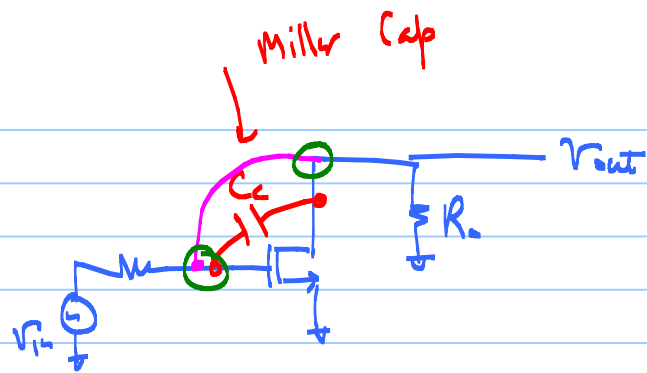
A Large C_c splits the poles into a
dominant pole ω_{p1}
non-dominant pole ω_{p2}



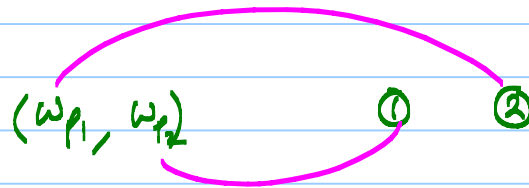
$$\omega_{p2} \approx \frac{g_{m1}}{C_o}$$



Miller Cap

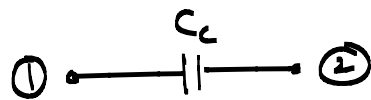
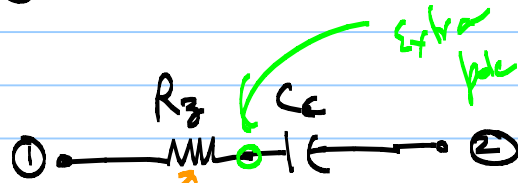
$$\omega_z = \frac{g_{m1}}{C_c} \quad @ RHP$$




$$\omega_z' = \frac{1}{C_c \left(\frac{1}{g_{m1}} - R_z \right)}$$


zero nulling
Resistor

$$R_z < \frac{1}{g_m} \rightarrow RHP$$

$$R_z = \frac{1}{g_m} \rightarrow \infty$$

$$R_z > \frac{1}{g_m} \rightarrow LHP$$

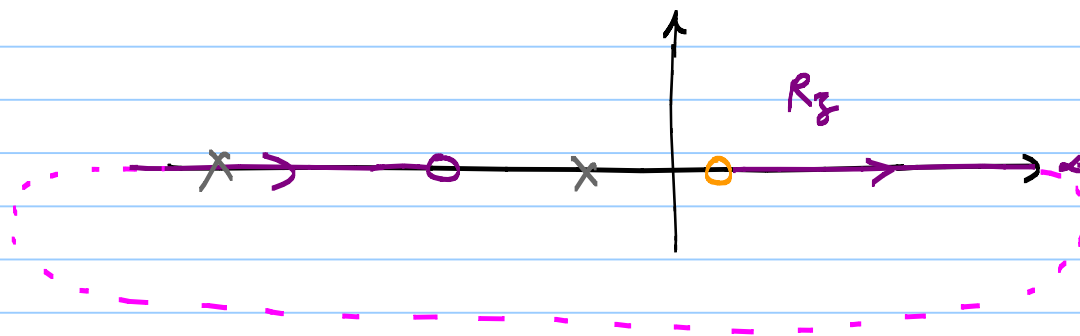

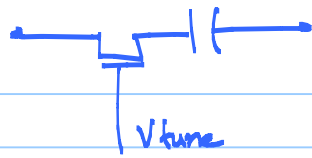

"Generic 2 node Amplifier Model"

