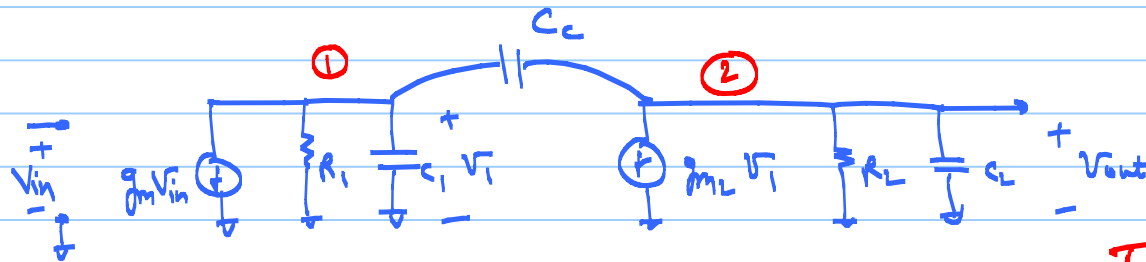


ECE 511 - Lecture 16

Note Title

3/19/2013



$$A_v = g_{m1} R_1 g_{m2} R_L$$

$$\omega_{un} \approx \frac{g_{m1}}{C_c}$$

$$\omega_{p1} = \frac{1}{R_L (C_2 + C_c) + R_1 (C_1 + C_c (1 + g_{m2} R_L))}$$

$$\approx \frac{1}{g_{m1} R_L R_1 C_c}$$

$$\omega_{p2} \approx \frac{g_{m2} C_c}{C_c C_1 + C_1 C_2 + C_c C_2} \propto \frac{g_{m2}}{C_2} \text{ for } C_c \approx C_2 \gg C_1$$


$$\omega_z = \frac{g_{m2}}{C_c} @ \text{RHP}$$

$$A_v(s) = \frac{A_{v0} (1 - s/\omega_z)}{(1 + s/\omega_{p1})(1 + s/\omega_{p2})}$$

if $\omega_{p1} \ll \omega_{p2} \Rightarrow \omega_{p1} \Rightarrow \text{dominant pole}$
 ω_z is also far out

$$A_v(s) \approx \frac{A_{v0}}{(1 + s/\omega_{p1})}$$
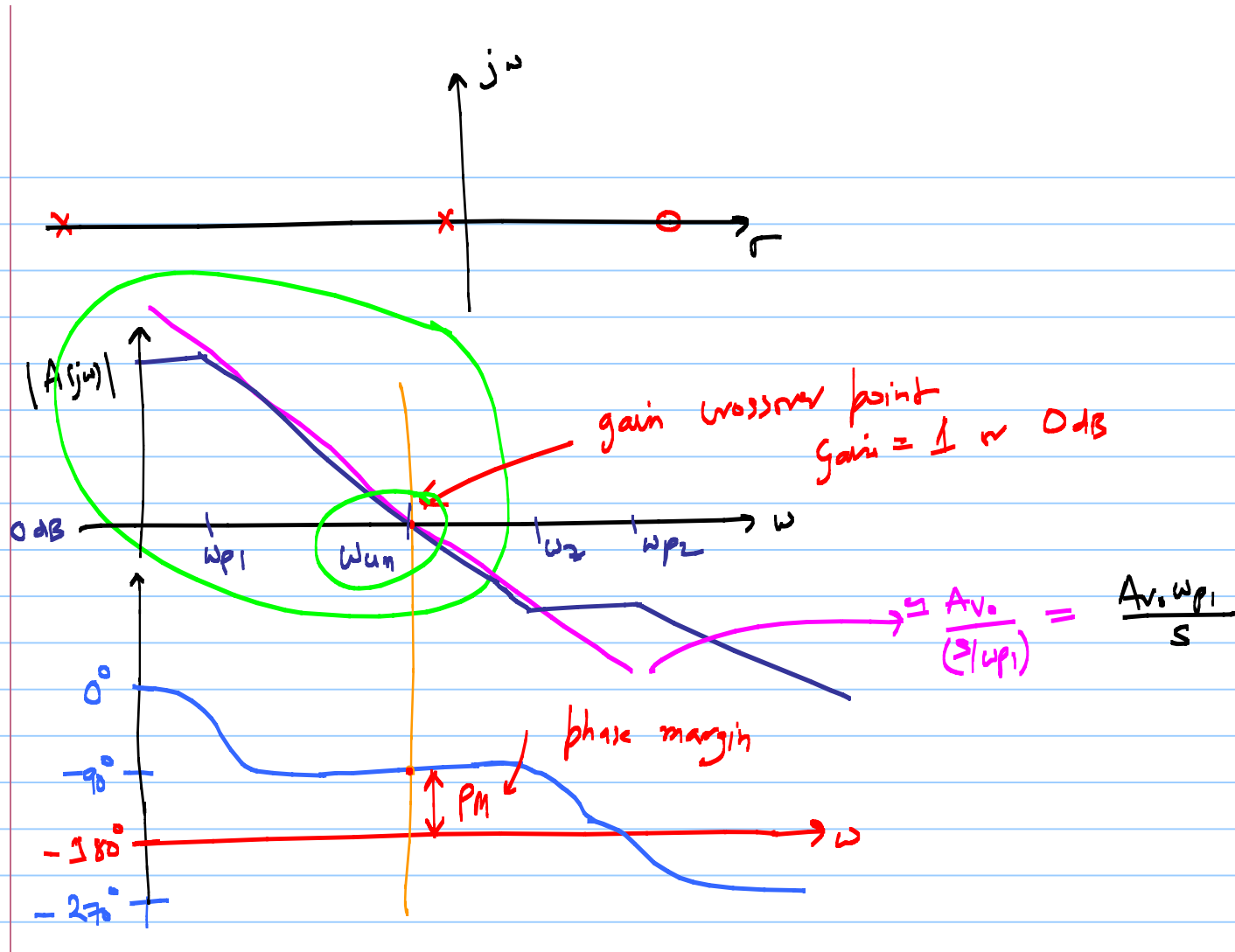
$$\omega_{3dB} = \frac{1}{g_{m2} R_2 R_1 C_c}$$



Deriving ω_{un}

$$A_v(s) = \frac{A_{v0}}{1 + s/\omega_{p1}}$$

$$|A_v(j\omega)| = \frac{|A_{v0}|}{\left(1 + \frac{\omega^2}{\omega_{p1}^2}\right)^{1/2}}$$

$$\text{for } \frac{\omega}{\omega_{p1}} \gg 1$$

$$1 + \left(\frac{\omega}{\omega_{p1}}\right)^2 \approx \left(\frac{\omega}{\omega_{p1}}\right)^2$$

$$\approx \frac{A_{v0} \omega_{p1}}{s} = \frac{\omega_{un}}{s}$$

$$\text{because @ } s = \omega_{un}, \quad \left| \frac{\omega_{un}}{s} \right| = 1$$

$$\Rightarrow \omega_{un} = A_{v0} \cdot \omega_{p1} = \cancel{g_{m1} R_1} \cancel{g_{m2} R_2} \cdot \frac{1}{\cancel{g_{m2} R_2} \cancel{R_1} C_c} = \frac{g_{m1}}{C_c}$$

$$\omega_{um} = \frac{g_{m1}}{C_c}$$

⇒ What is ω_{um} ?



$$\omega_{um} = A_{v0} \cdot \omega_{p1}$$

$$= A_{v0} \cdot \omega_{3dB} = \text{Gain-Bandwidth product}$$

"Ex. 21.6 to 21.10
for pole splitting"

Source follower frequency Response

$$\gamma = \lambda = 0$$

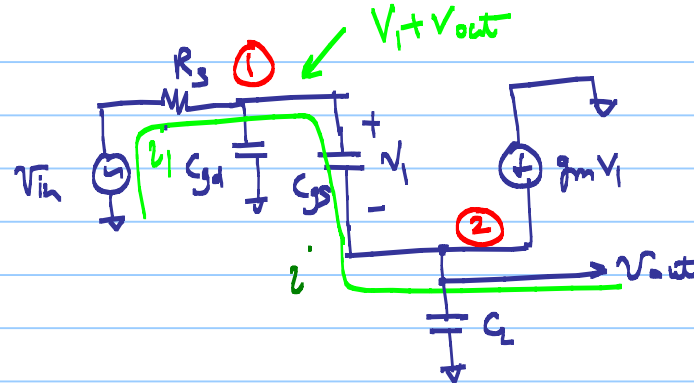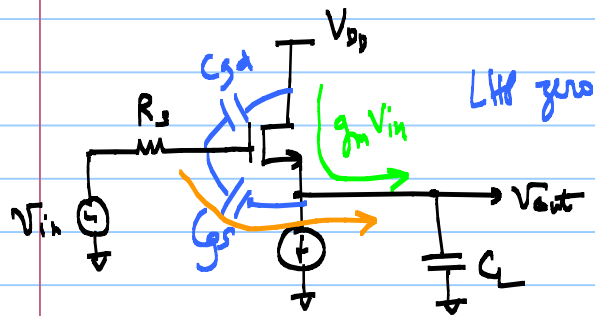

KCL @ node 2

$$V_1 C_{gs} s + g_m V_1 = V_{out} \cdot s C_L$$

$$\Rightarrow V_1 = \frac{s C_L}{g_m + s C_{gs}} \cdot V_{out}$$

* KVL beginning from V_{in} plug-in V_1

$$V_{in} = R_S [V_1 s C_{gs} + (V_1 + V_{out}) C_{gd} s] + V_1 + V_{out}$$

KCL @ node 1

$$\frac{V_1}{1/s C_{gs}} + \frac{(V_1 + V_{out})}{1/s C_{gd}} - i_1 = 0$$

$$i_1 = s C_{gs} V_1 + (V_1 + V_{out}) s C_{gd}$$

$$\frac{V_{out}}{V_{in}}(s) = \frac{(g_m + g_s s)}{R_s [C_{gs} C_L + C_{gs} G_d + G_d C_L] s^2 + [g_m R_s (G_d + C_L + C_{gs})] s + g_m}$$

$$\text{LHP zero} \Rightarrow \omega_z = \frac{g_m}{C_{gs}} \quad \left| \quad s_z = -\frac{g_m}{C_{gs}} \right.$$

Assuming $|\omega_p| < |\omega_z|$


$$\begin{aligned} \omega_{p1} &= \frac{g_m}{g_m R_s G_d + C_L + C_{gs}} \\ &= \frac{1}{R_s G_d + \frac{C_L + C_{gs}}{g_m}} \end{aligned}$$

if $R_s G_d$ is small

$$\omega_{p1} \approx \frac{g_m}{C_L + C_{gs}}$$

Input impedance of SF

@ low frequency $g_{mb} \gg |sC_L|$

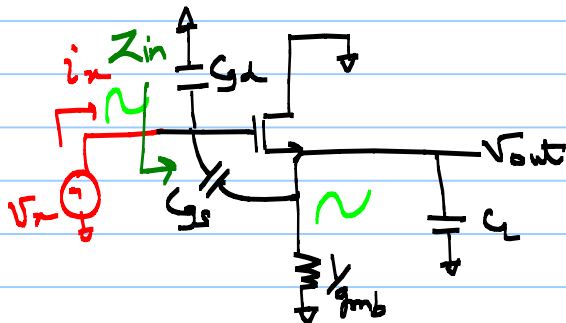

$$Z_{in} \approx \frac{1}{sC_{gs}} \left(1 + \frac{g_m}{g_{mb}} \right) + \frac{1}{g_{mb}}$$

$$= \frac{1}{s \frac{C_{gs}}{\left(1 + \frac{g_m}{g_{mb}} \right)}} + \frac{1}{g_{mb}}$$

* input cap is a fraction
of C_{gs}


@ higher frequencies
 $g_{mb} \ll (sC_L)$

$$Z_{in1} = \frac{1}{sG_D} + \frac{1}{sC_L} + \frac{g_m}{G_D C_L s^2}$$

$$Z_{in1}(j\omega) = \underbrace{\frac{1}{j\omega} \left[\frac{1}{G_D} + \frac{1}{C_L} \right]}_{\text{Capacitance}} - \underbrace{\frac{g_m}{G_D C_L \omega^2}}_{\text{negative resistance}}$$




$$\text{Re}(Z_{in}) = -\frac{g_m}{G_D C_L \omega^2} \quad \leftarrow \text{useful in oscillators}$$



$$\omega_0 = \frac{1}{\sqrt{L_C}}$$

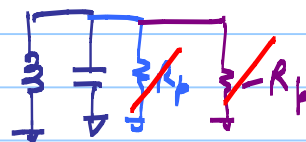

output impedance

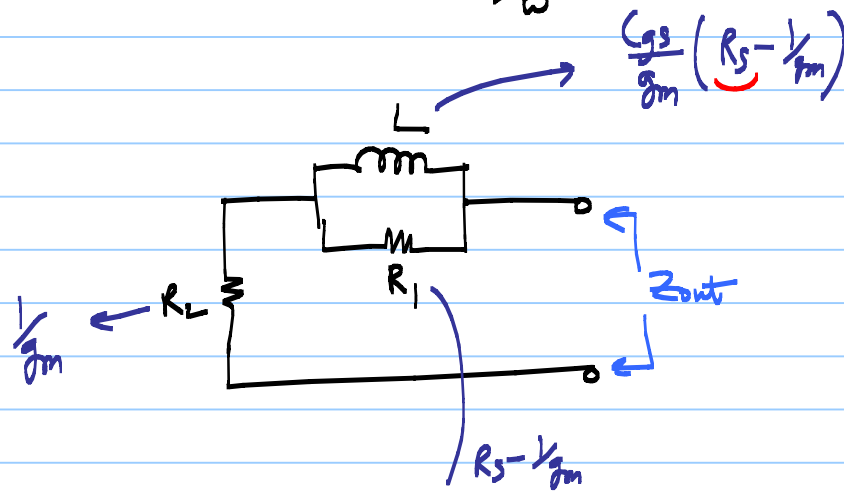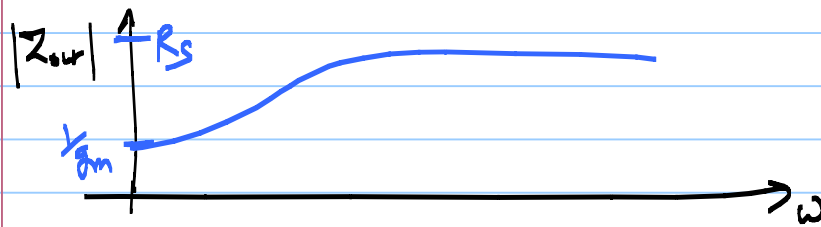
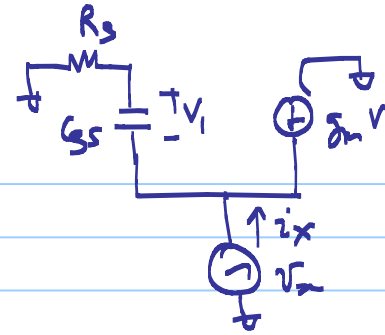
$$Z_{out} = \frac{R_S G_S S + 1}{g_m + S G_S}$$



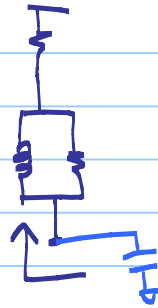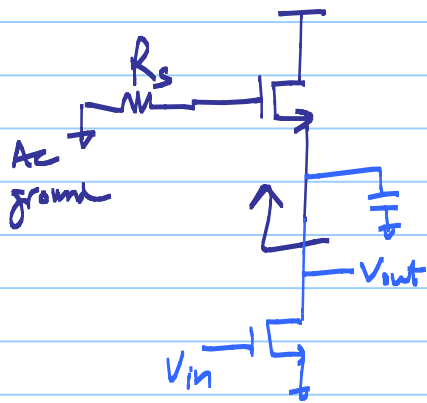


inductive load

(active inductive load)

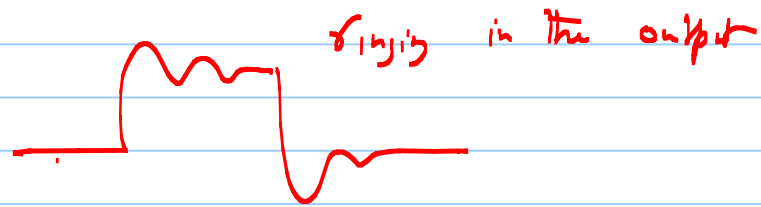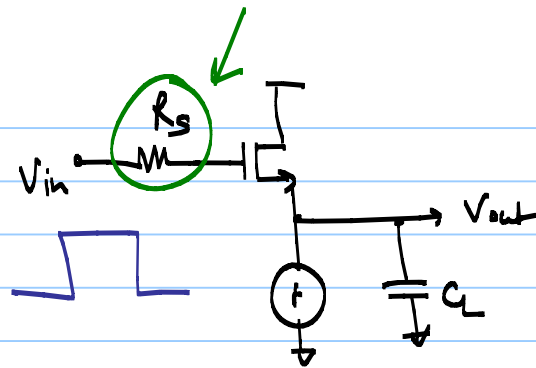


* If the SF is driven by a large R_S
 ↳ Substantial inductive peaking

Common Gate Frequency Response

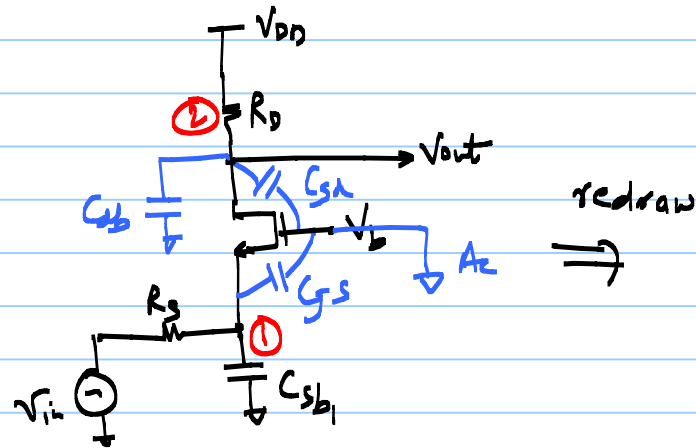

redraw $\Rightarrow$

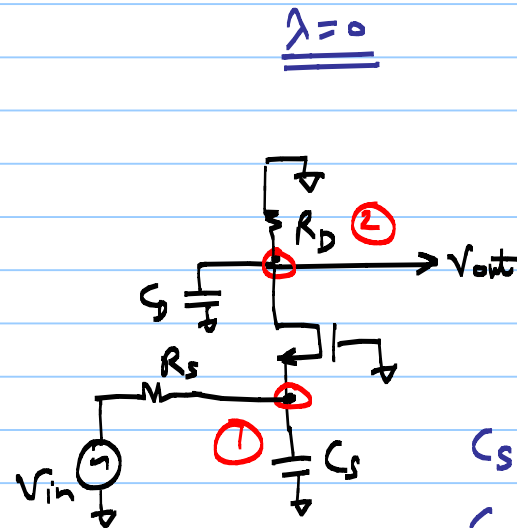

$$C_s = g_m + C_{sb}$$

$$C_D = C_{gd1} + C_{db}$$


@ node-1

$$\omega_{p1} = \frac{1}{\left(R_s \parallel \frac{1}{g_m + g_{ds}} \right) C_s}$$

@ node-2

$$\omega_{p2} = \frac{1}{R_D C_D}$$
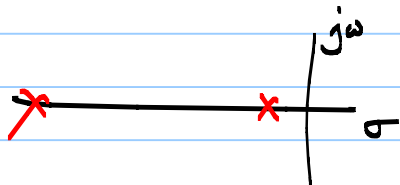
$$\frac{V_{out}}{V_{in}}(s) = \frac{(g_m + g_{m2}) R_D}{1 + (g_m + g_{m2}) R_S} \cdot \frac{1}{(1 + s\tau_{p1})(1 + s\tau_{p2})}$$



* No miller $C_p \Rightarrow$ potentially wideband response

$\hookrightarrow$ low-impedance input $\rightarrow$ Current Buffer.

$\Rightarrow$ Transimpedance amplifier

