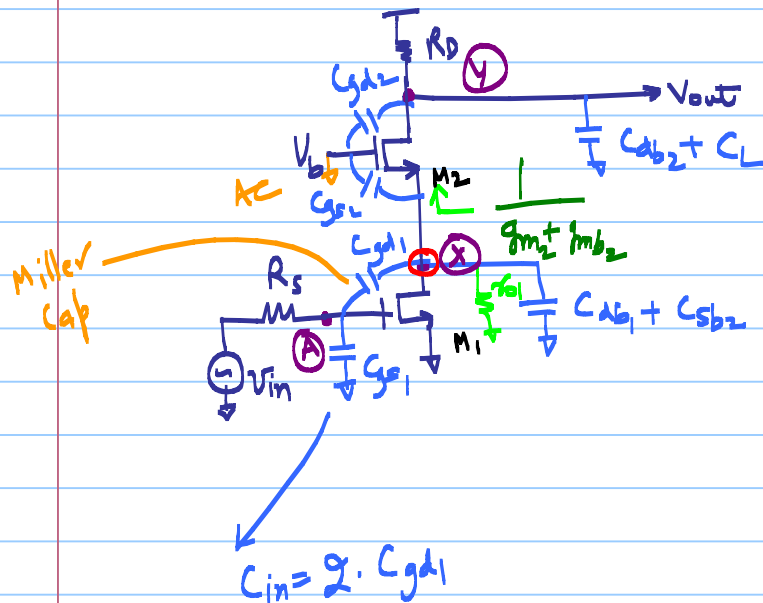


ECE 511 - Lecture 17

Note Title

3/21/2013



Miller effect is less significant in cascode amplifiers than a CS stage

Cascode Amplifier

$$A_v = -g_{m1} \cdot \left(R_D \parallel \underbrace{g_{m2} r_{o2} r_{o1}}_{g_m r_o^2} \right)$$

Miller effect of C_{gd1}

* gain from A to X

(Assume $R_D \ll r_o$)

$$A_{A \rightarrow X} = -g_{m1} \cdot \frac{1}{g_{m2} + g_{m3b}}$$

$$= -1$$

$$M_1 \stackrel{D}{=} M_2$$

$\beta = 0$

Pole @ A:

$$\omega_{pk} = \frac{1}{R_s [C_{gs1} + (1 + \frac{g_{m1}}{g_{m2} + g_{mb2}}) C_{gd1}]}$$


$|A_v|$ for $A \rightarrow X$

Pole @ X:

$$\omega_{px} = \frac{1}{R_x \cdot C_x} = \frac{(g_{m2} + g_{mb2})}{2C_{gd1} + C_{db1} + C_{sb2} + C_{gs2} + (1 + \frac{1}{|A_v|})C_c}$$

Pole @ Y:
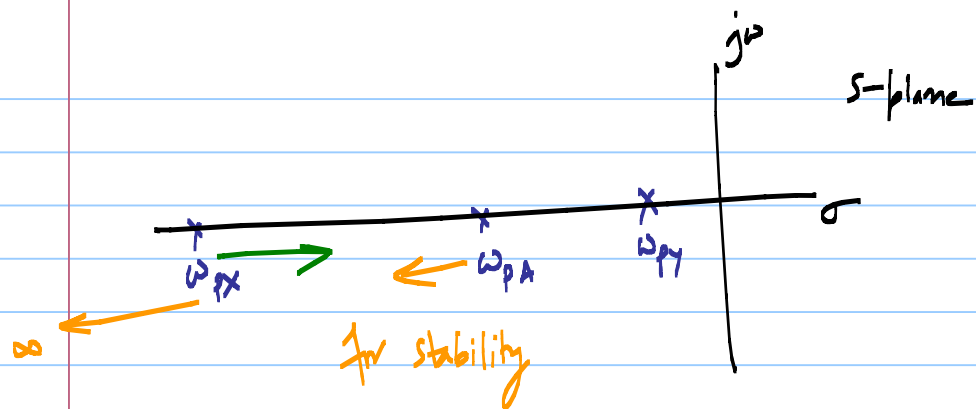
$$\omega_{py} = \frac{1}{R_D (C_{db2} + C_{k2} + C_L)}$$



* What if R_D is replaced by a cascode current source load.

$$A_v = -g_{m1} \left[(g_{m1} r_{o1})_n \parallel (g_{m1} r_{o1})_p \right] \leftarrow \text{higher DC gain}$$

$$\Rightarrow \text{impedance at node 'x'} \Rightarrow r_{o1} \parallel \left[\frac{R_D}{(g_{m1} r_{o1})_n} \right]$$


$$\hookrightarrow \text{pole at 'x' moves closer} \quad = r_{o1} \parallel \frac{(g_{m1} r_{o1})_p}{(g_{m1} r_{o1})_n} \approx \frac{r_{o1}}{2}$$

$$\frac{1}{g_{m2}} \rightarrow \frac{r_{o1}}{2}$$

* But, in practice this pole doesn't degrade stability much.


Differential Amplifier :

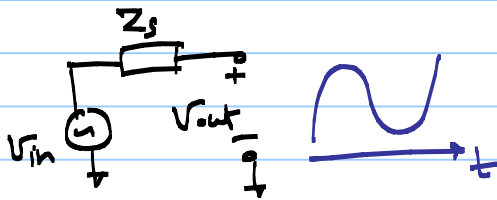- * Single-ended signal is defined as one that is measured wrt. a fixed potential $\rightarrow$ usually ground



- * A differential signal is defined as one measured between two nodes that have equal and opposite signal excursions around a fixed potential

$$V_{out} = V_{o1} - V_{o2}$$

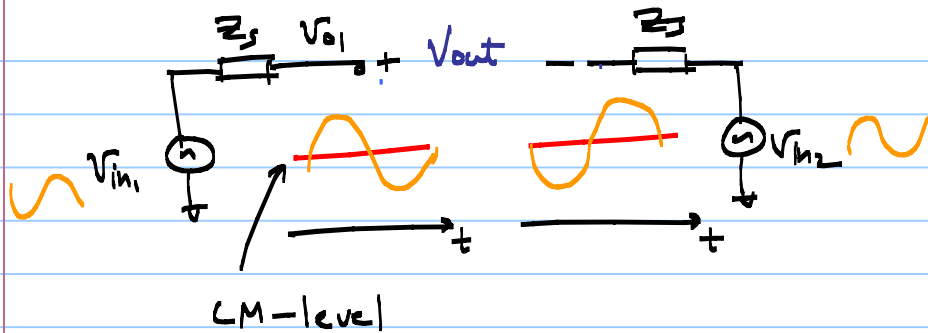



The center potential in differential signaling is called the "common-mode" level

Common mode $\rightarrow V_{cm} = \frac{V_{o1} + V_{o2}}{2}$ $\xrightarrow{t}$ V_{cm}




Differential $\rightarrow V_d = (V_{o1} - V_{o2})$ $\xrightarrow{t}$

Advantages:

①

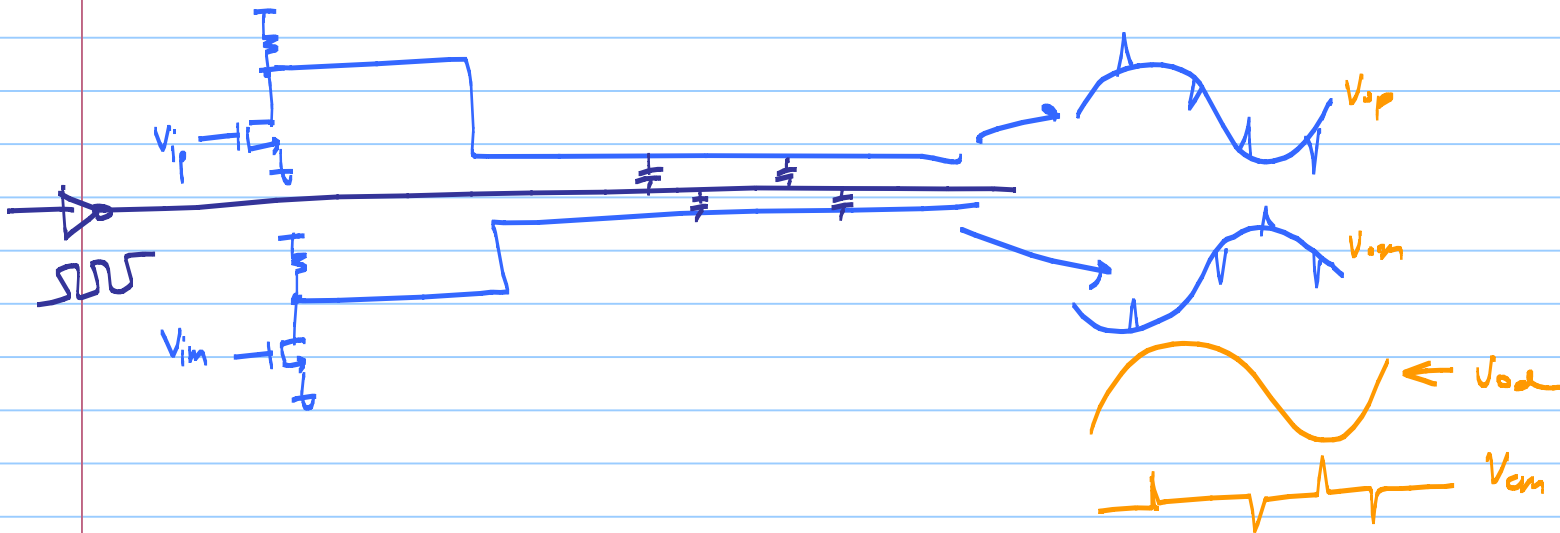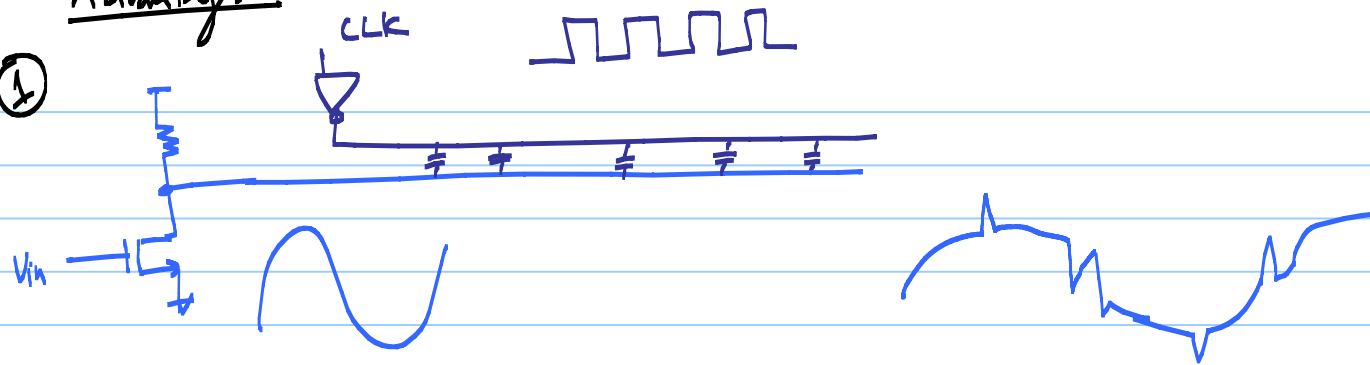

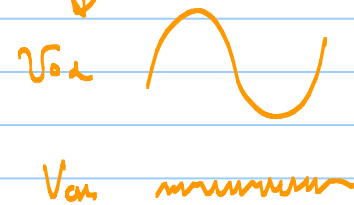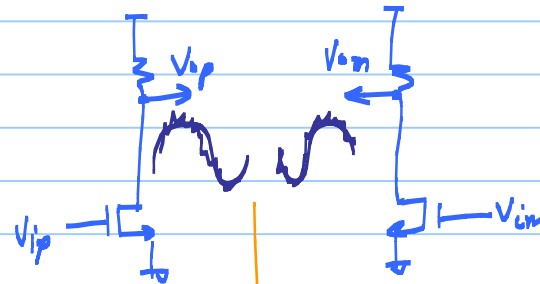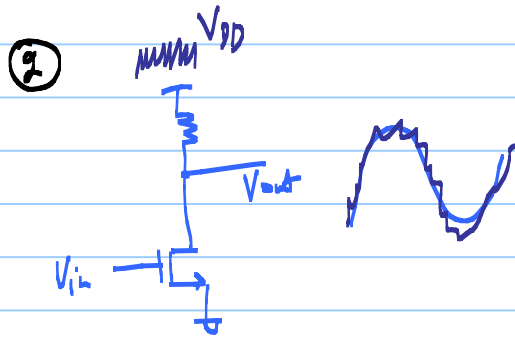⇒ Differential signalling rejects "common-mode noise".






Better "PSRR"
power supply rejection

③ Simple biasing


(-) 2x Area
↳ not an issue

Basic Diff-pair

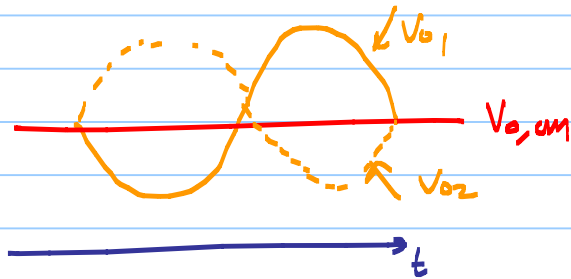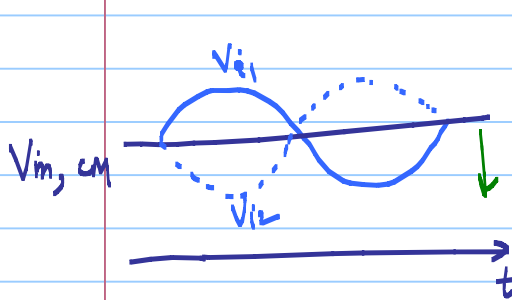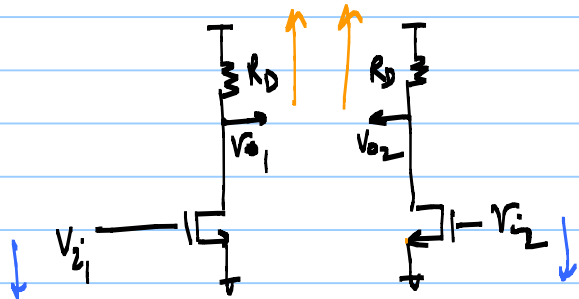2 - identical SF signal paths to
process both phases




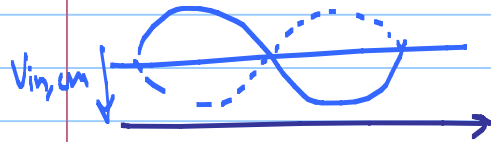* What if $V_{in, cm}$ is not well defined



Bad $\Rightarrow$ bias current in both the halves are dependent
on $V_{in,cm}$.

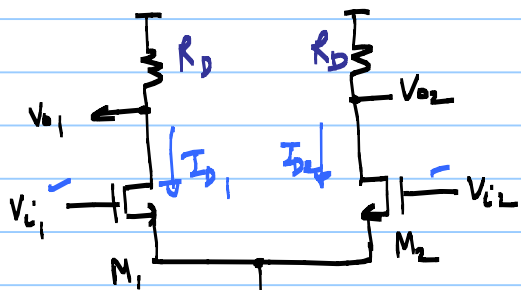
$\hookrightarrow$ Need the diff-pair bias current to be
independent of the input CM-level.



tail
current source

In DC picture

$$I_{D1} = I_{D2} = \frac{I_{SS}}{2}$$

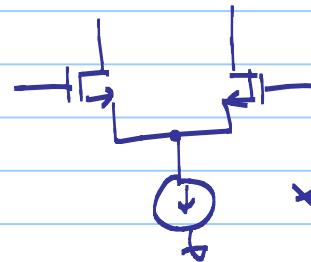

* Basic
Differential
pair


$$I_{SS} = I_{D1} + I_{D2}$$

independent of $V_{in,cm}$

* If $V_{i1} = V_{i2} = V_{in,cm} \Rightarrow$ bias current in each device = $\left(\frac{I_{SS}}{2}\right)$

$$V_{out,cm} = V_{DD} - \left(\frac{I_{SS}}{2}\right) R_D$$

* DC biasing is simplified

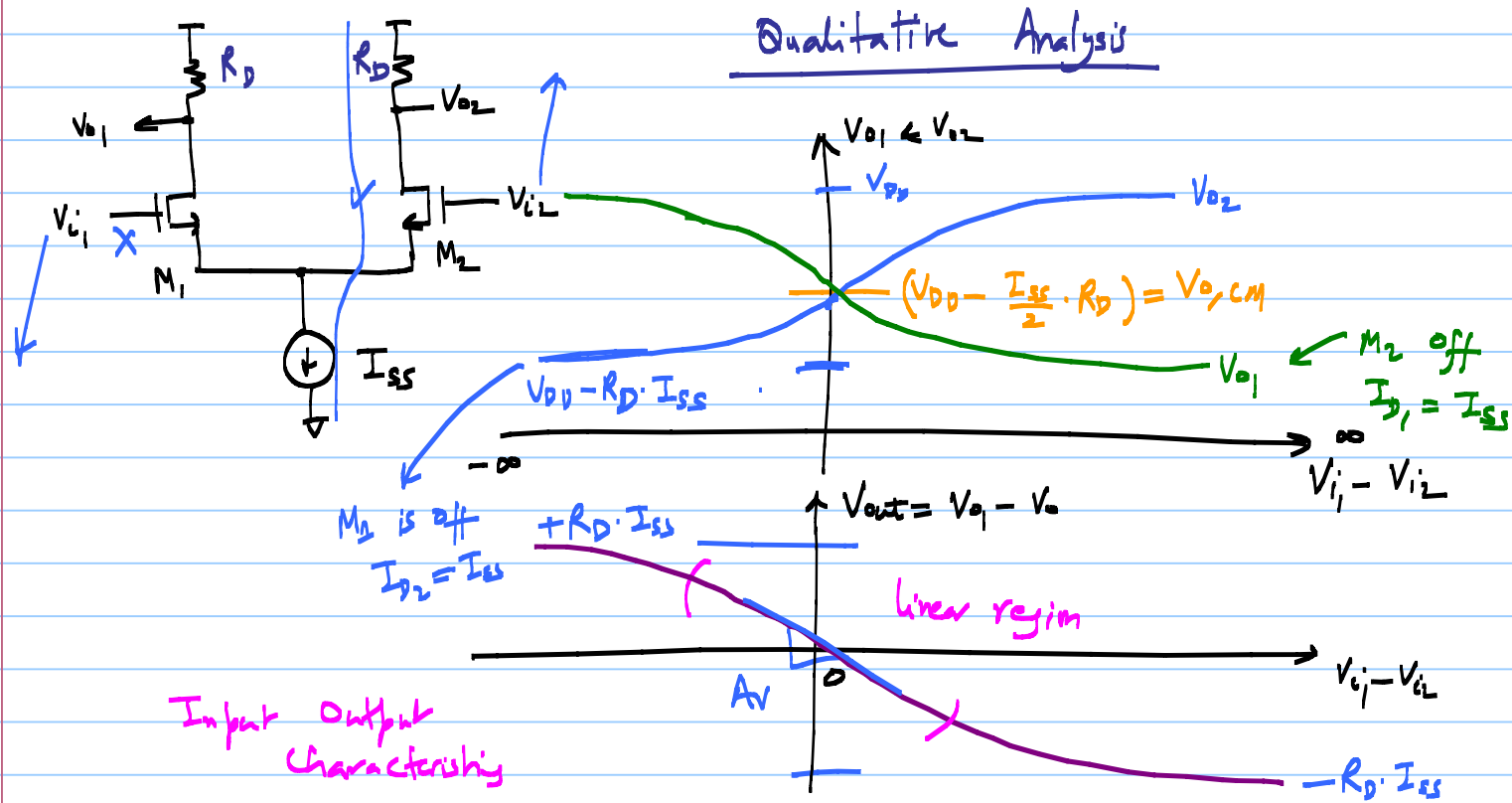

* small signal gain $A_v = \frac{d(V_{o1} - V_{o2})}{d(V_{i1} - V_{i2})}$

Comm-mode behavior of the circuit