




ECE 511- Lecture 18

Note Title

4/2/2013


Common-mode behavior of diff-pair

($\lambda = 0$)

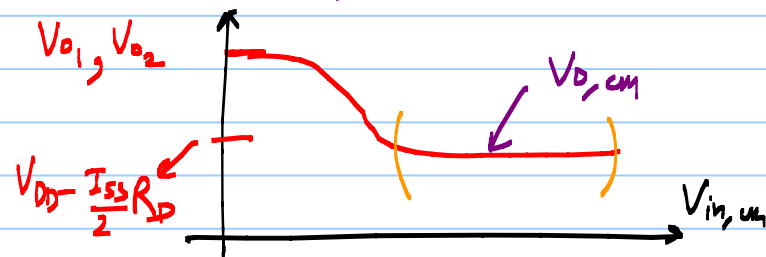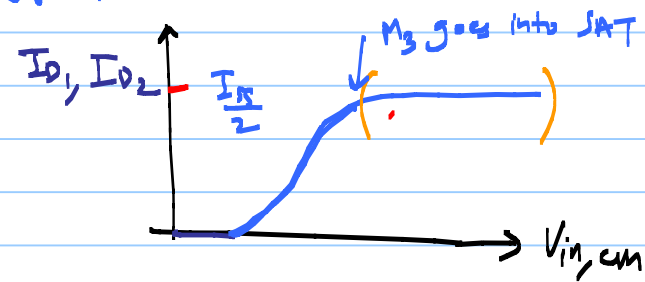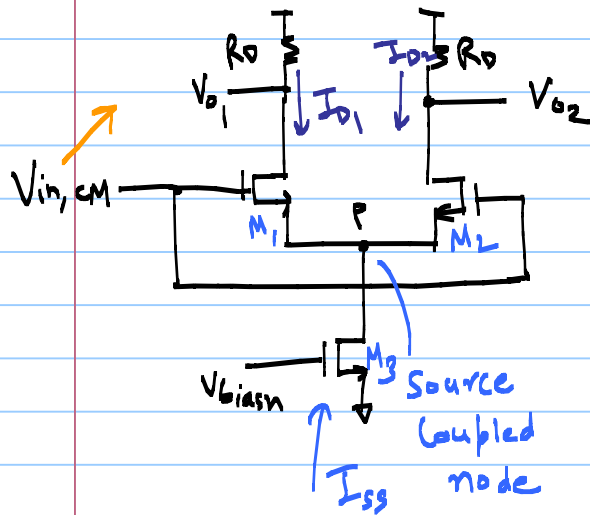

Ⓐ $V_{in,cm} = 0,$

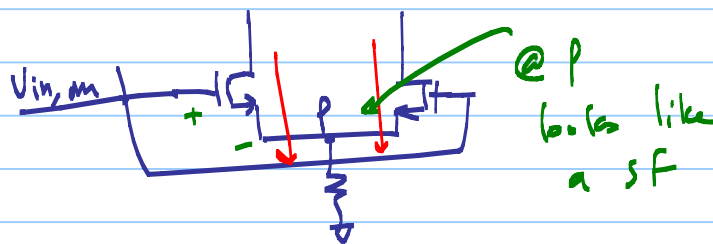Ⓑ $V_{in,cm} > V_{THN},$ $M_1 \& M_2$ turn on in saturation
 $M_3 \rightarrow$ Triode



$V_{in} \rightarrow$ $\downarrow = i = G_m V_{in}$
 $2x$
 R


Ⓒ $V_{in,cm} \geq V_{AS1} + V_{DS,sat3}$

Ⓓ $M_{1,2}$ enter into triode


$V_{in,cm} > V_{out} + V_{THN}$
 $\uparrow = (V_{DD} - \frac{R_D I_{SS}}{2}) + V_{THN}$

✓ sets an upper limit on input CM-level
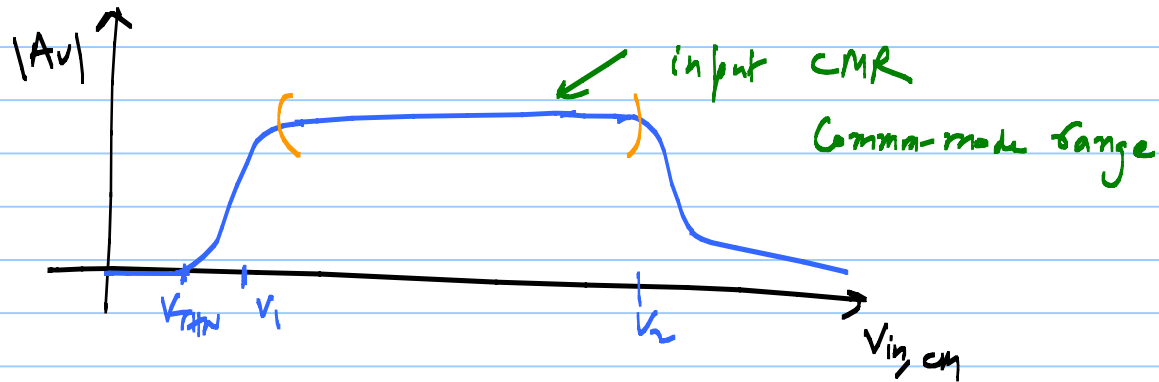
$$V_{in,cm} \in \left[\underbrace{V_{GS1} + V_{DS,sat3}}_{V_1}, \underbrace{V_{DD} - \frac{I_D R_{SS}}{2} + V_{THN}}_{V_2} \right]$$



MICS bands

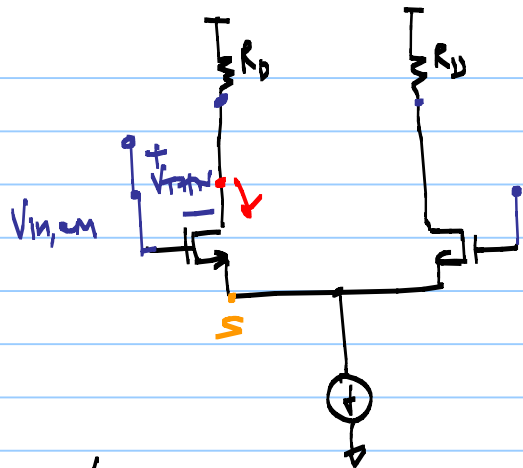

How large can be the output voltage swing?


* Can go as high as V_{DD}

but lower limit is $V_{in,cm} - V_{THN}$

$$V_{out} \in [V_{in,cm} - V_{THN}, V_{DD}]$$



↑
don't want really high $V_{in,cm}$

* $V_D > V_G - V_{THN}$

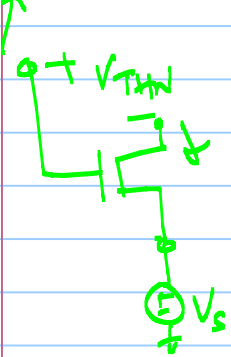

Large Signal behavior:
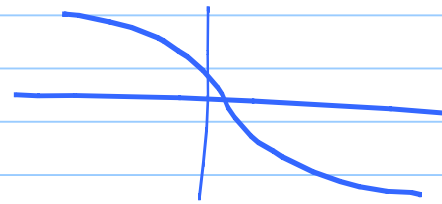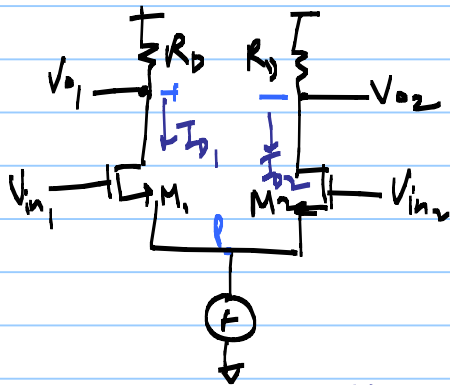
$$V_{out} = V_{o1} - V_{o2} = f(V_{in1} - V_{in2})$$



$$V_{o1} - V_{o2} = (I_{D1} - I_{D2}) R_D \longrightarrow \textcircled{1}$$

$$V_{in1} - V_{in2} = V_{GS1} - V_{GS2}$$

$$= \left(\sqrt{\frac{2I_{D1}}{\beta}} + V_{THN} \right) - \left(\sqrt{\frac{2I_{D2}}{\beta}} + V_{THN} \right)$$

$$V_{in_1} - V_{in_2} = \sqrt{\frac{2}{\beta}} (\sqrt{I_{D_1}} - \sqrt{I_{D_2}}) \quad \therefore I_{SS} = I_{D_1} + I_{D_2}$$

$$(V_{in_1} - V_{in_2})^2 = \frac{2}{\beta} \left(I_{SS} - 2\sqrt{I_{D_1}I_{D_2}} \right)$$

$$\Rightarrow \frac{\beta}{2} (V_{in_1} - V_{in_2})^2 - I_{SS} = -2\sqrt{I_{D_1}I_{D_2}}$$


$\Rightarrow$ square both the sides again & use the identity


$$4I_{D_1}I_{D_2} = (I_{D_1} + I_{D_2})^2 - (I_{D_1} - I_{D_2})^2$$

$$I_{D_1} - I_{D_2} = \frac{\beta}{2} (V_{in_1} - V_{in_2}) \sqrt{\frac{4I_{SS}}{\beta} - (V_{in_1} - V_{in_2})^2}$$

$$V_{o1} - V_{o2} = V_{out} = \left[-\frac{\beta R_D}{2} (V_{in1} - V_{in2}) \right] \sqrt{\frac{4I_{SS}}{\beta} - (V_{in1} - V_{in2})^2}$$

$$x \sqrt{\frac{4I_{SS}}{\beta} - x^2}$$

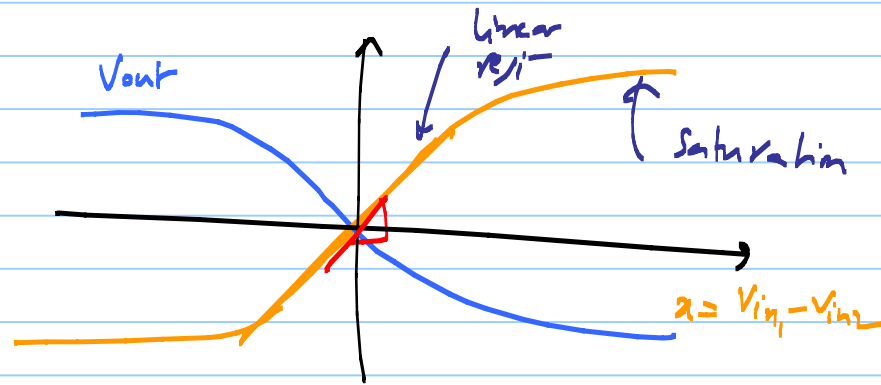

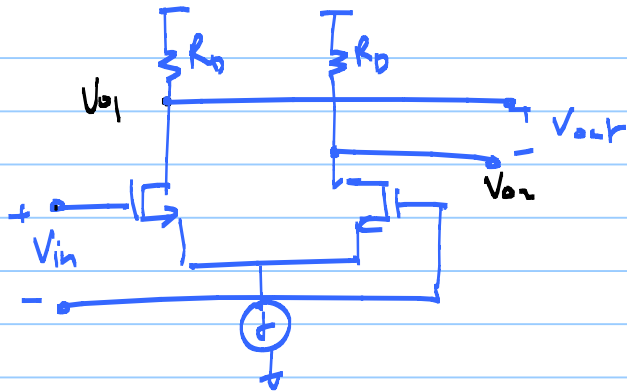


$$A_v = -g_m R_D$$

$$\begin{aligned}
 V_{O1} - V_{O2} = V_{out} &= -\frac{\beta R_D}{2} \underbrace{(V_{in1} - V_{in2})}_{V_{in}} \sqrt{\frac{4I_{SS}}{\beta} - \cancel{(V_{in1} - V_{in2})^2}} \\
 &= -\frac{\beta}{2} R_D V_{in} \cdot 2 \sqrt{\frac{I_{SS}}{\beta}} \\
 &= -\sqrt{\beta I_{SS}} \cdot R_D \cdot V_{in}
 \end{aligned}$$

$$= - \underbrace{\sqrt{2\beta I_D}}_{g_m} \cdot R_D \cdot V_{in}$$


$$= - g_m R_D V_{in}$$

$$\Rightarrow \boxed{A_v = - g_m R_D}$$

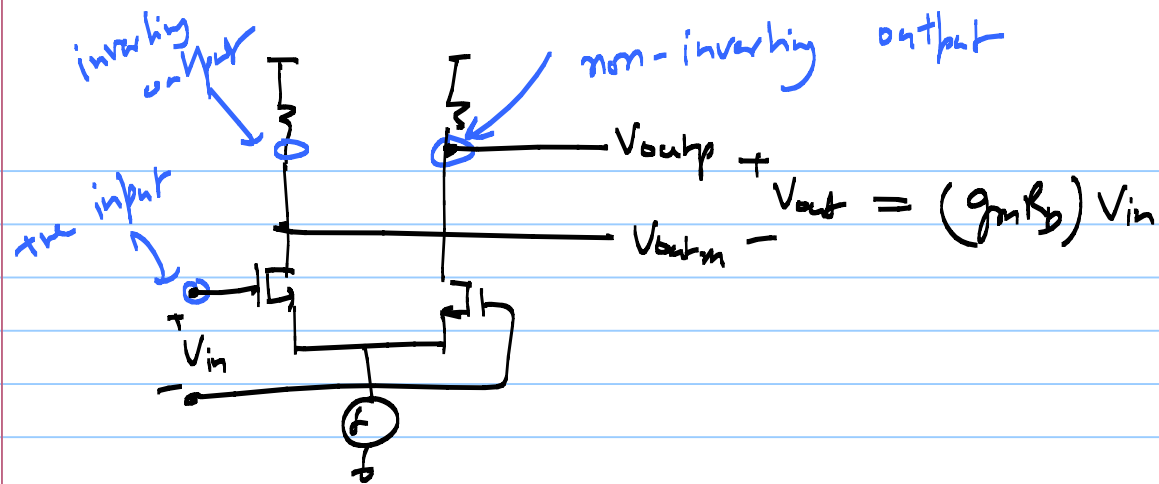

Half-Circuit Analysis / Method

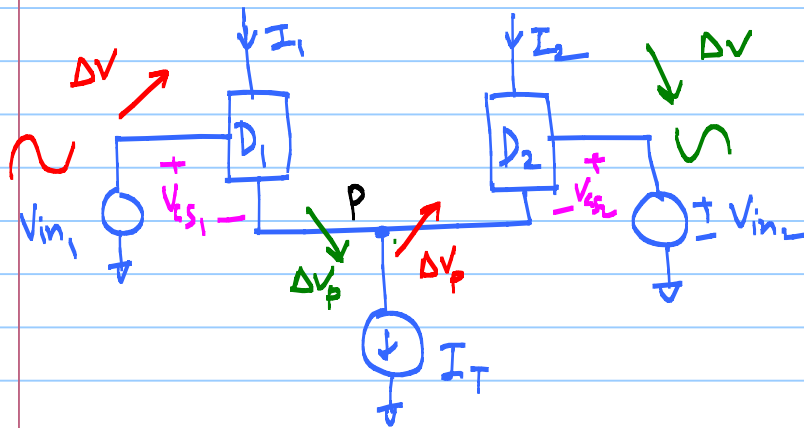
" D_1 & D_2 are identical linear circuits"



$$V_p = V_{in,cm} - V_{ds1,2}$$


$\Rightarrow$ by superposition
 V_p is constant
 $\hookrightarrow V_p$ is AC ground

Symmetry

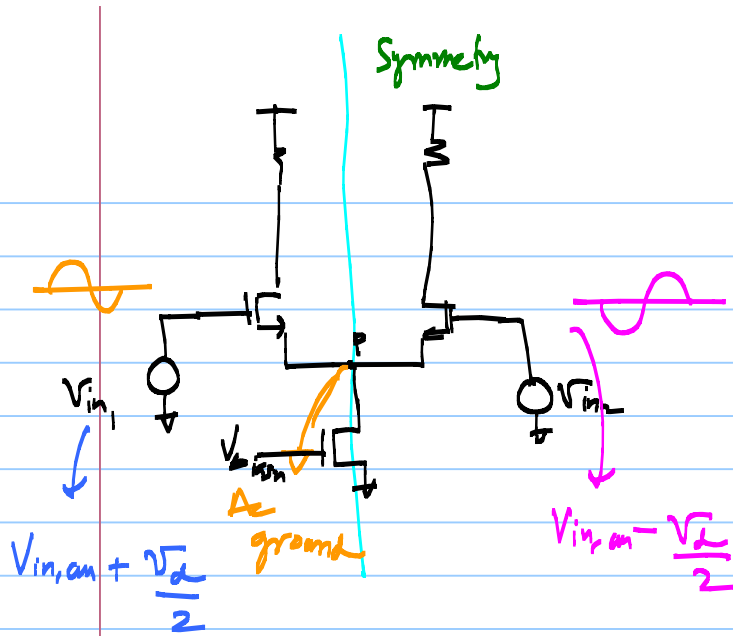

AC picture

decomposes into two half circuits

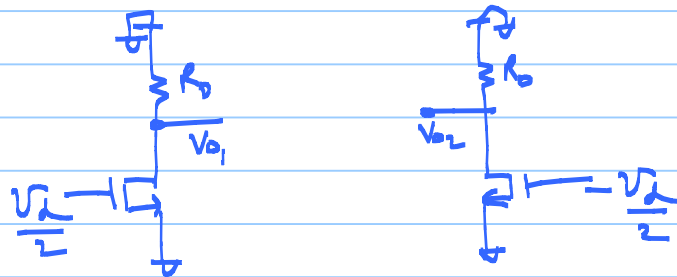

$$V_{o1} = -g_m R_D \frac{V_d}{2}$$


$$V_{o2} = g_m R_D \frac{V_d}{2}$$

$$V_{out} = V_{o1} - V_{o2} = -g_m R_D V_d$$

$$A_v = -g_m R_D$$

* What if the inputs are not FD, but single-ended.

Caveat: Can't apply the theorem yet!

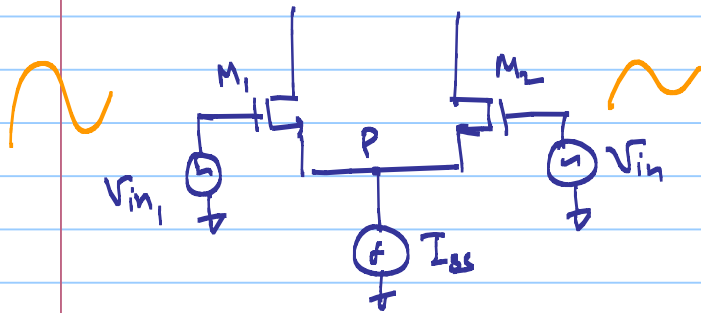


$$V_{in1} = \frac{(V_{in1} - V_{in2})}{2} + \frac{(V_{in1} + V_{in2})}{2}$$

$$V_{in2} = \frac{(V_{in2} - V_{in1})}{2} + \frac{(V_{in1} + V_{in2})}{2}$$

$$f(x) = f_{\text{odd}}(x) + f_{\text{even}}(x)$$



$$\frac{f(x) - f(-x)}{2}$$

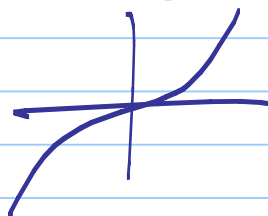

$$\frac{f(x) + f(-x)}{2}$$

