

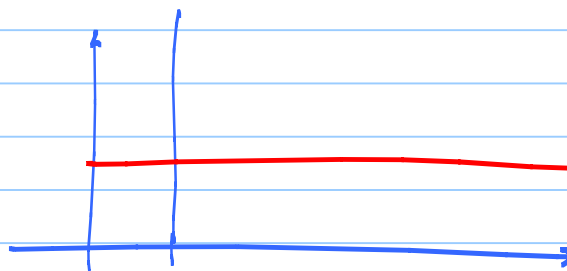
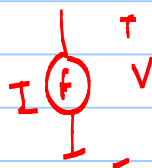
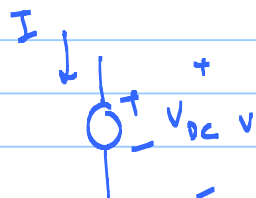
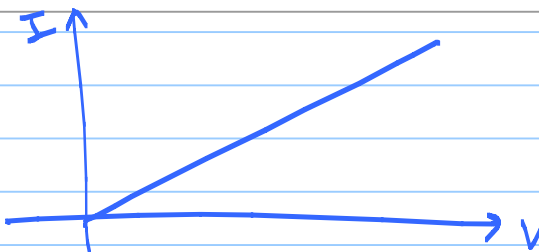
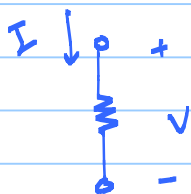


ECE 511 - Lecture 1






Note Title

1/22/2013

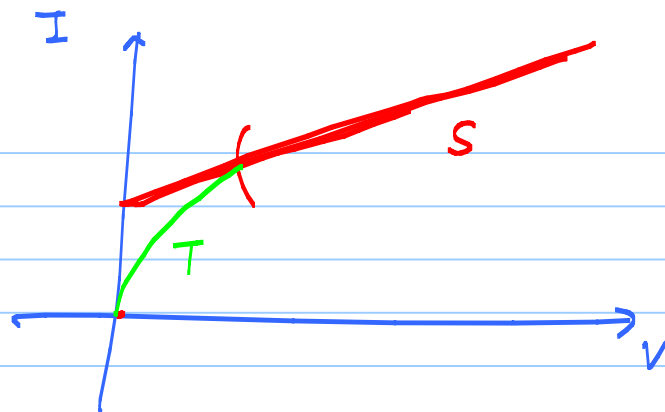

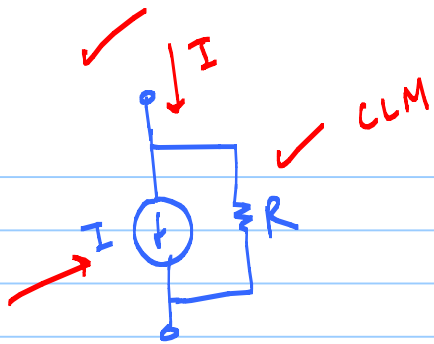

Square Law Equations

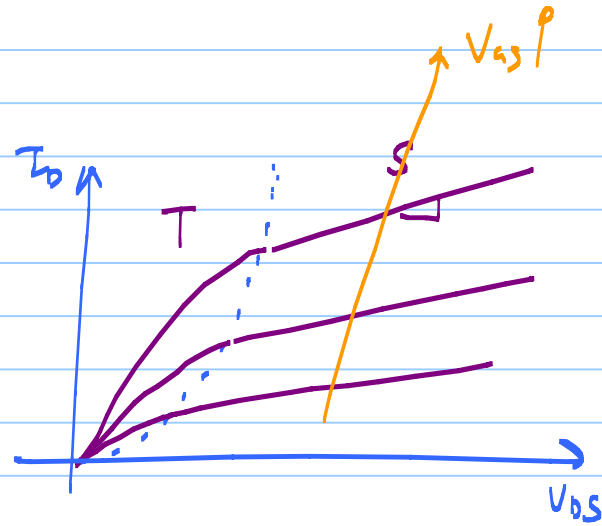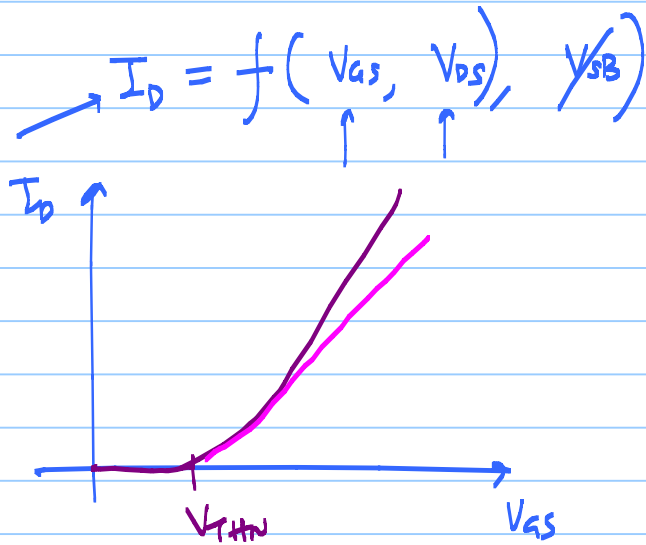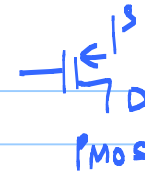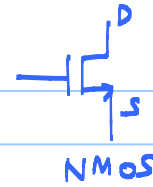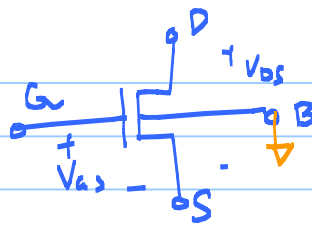


for Saturation V_r

$$V_{DS} \geq V_{DS,sat} = V_{GS} - V_{THN}$$

$$I_D = \begin{cases} 0, & \text{Cutoff} \\ \mu_n C_{ox} \frac{W}{L} \left[(V_{GS} - V_{THN}) V_{DS} - \frac{V_{DS}^2}{2} \right] & \text{Triode} \quad (V_{DS} < V_{GS} - V_{THN}) \\ \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{THN})^2 (1 + \lambda (V_{DS} - V_{DS,sat})) & \text{Sat} \quad (V_{DS} > V_{GS} - V_{THN}) \end{cases}$$



$$V_{ov} = V_{GS} - V_{THN} \stackrel{D}{=} V_{DS, sat}$$

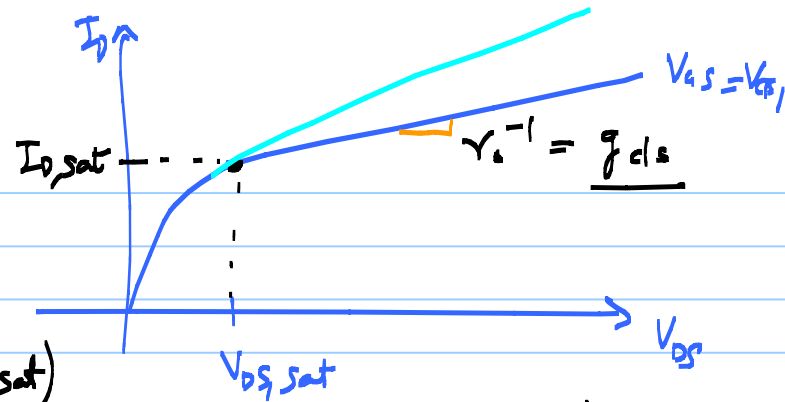$\left(\frac{w}{L}\right) \leftarrow$ Aspect ratio
"slenderness"



$$I_D = I_{D,sat} + I_{D,sat} \cdot \lambda (V_{GS} - V_{GS,sat})$$
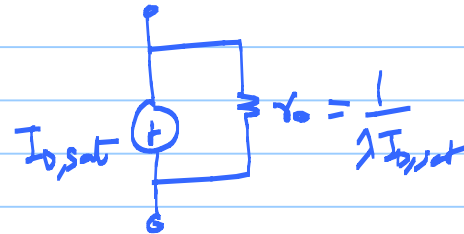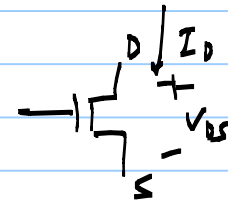
$$r_o = \left(\frac{\partial I_D}{\partial V_{GS}} \right)^{-1} = \frac{1}{\lambda I_{D,sat}}$$



intrinsic
gain
↓
 $g_m r_o$

in triode:

$$I_D = k_p \frac{W}{L} \left[(V_{GS} - V_{TH}) V_{DS} - \frac{V_{DS}^2}{2} \right]$$




$$R_{ch} = \left[\frac{\partial I_D}{\partial V_{DS}} \right]^{-1} = \frac{1}{k_p \frac{W}{L} [V_{GS} - V_{TH} - \underline{V_{DS}}]}$$


V_{GS} controlled
variable resistance

$$V_{DS} \ll V_{GS} - V_{TH}$$


$$R_{ch} \approx \frac{1}{k_p \frac{W}{L} (V_{GS} - V_{TH})}$$

Deep Triode

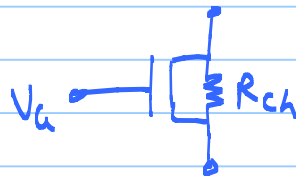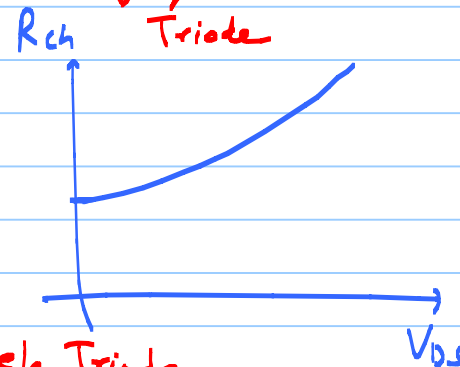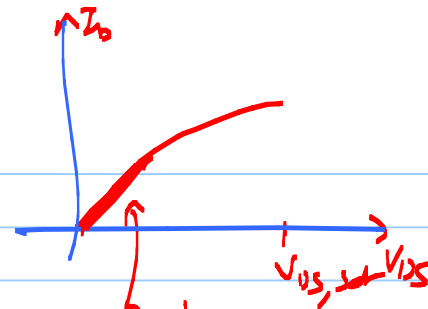

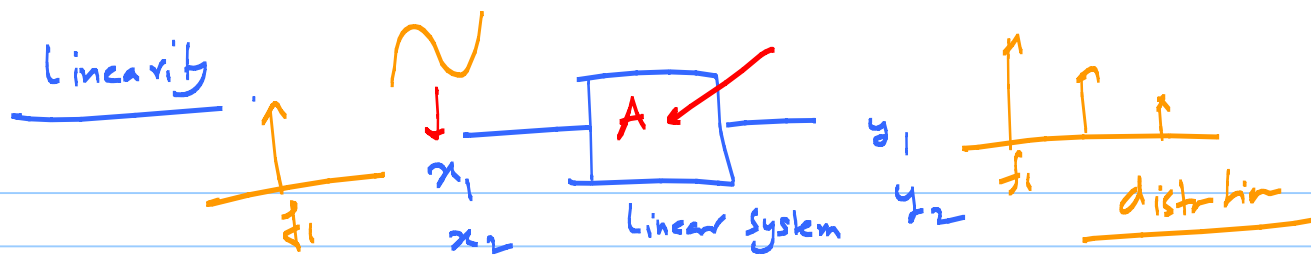

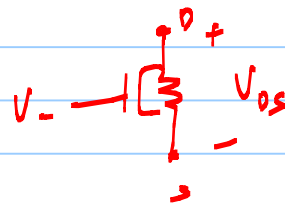
$$y = \alpha_1 x_1 + \alpha_2 x_2 \Rightarrow \alpha_1 y_1 + \alpha_2 y_2$$



$$R_{ch} = f(V_{os})$$

Diode Connected MOSFET

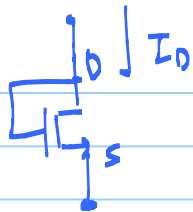


$$V_{DS} = V_{GS} \\ \geq V_{GS} - V_{THN}$$





Always in saturation





$$I_D = f(V_{GS})$$

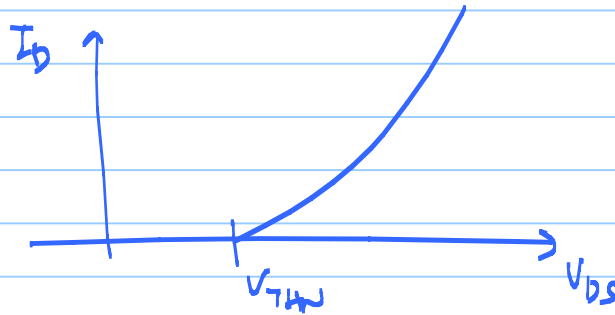


Intuition

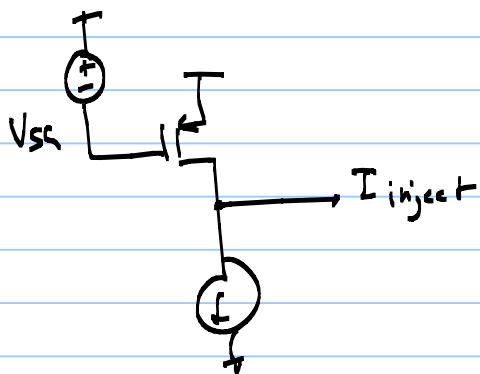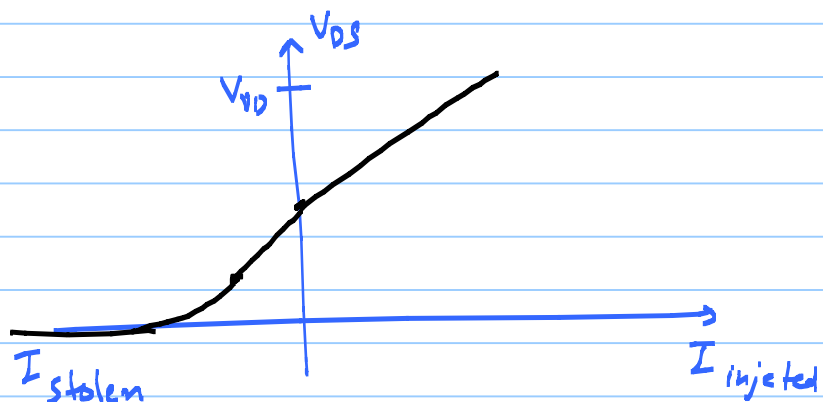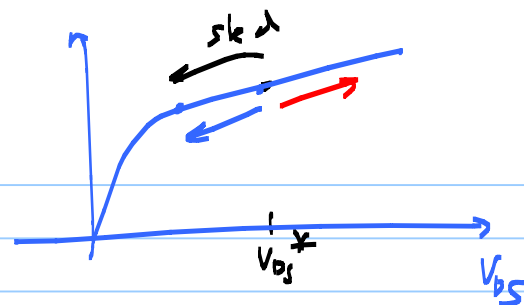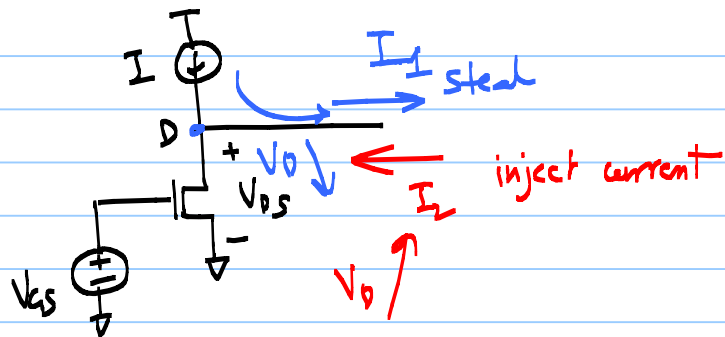


Small-signal behavior

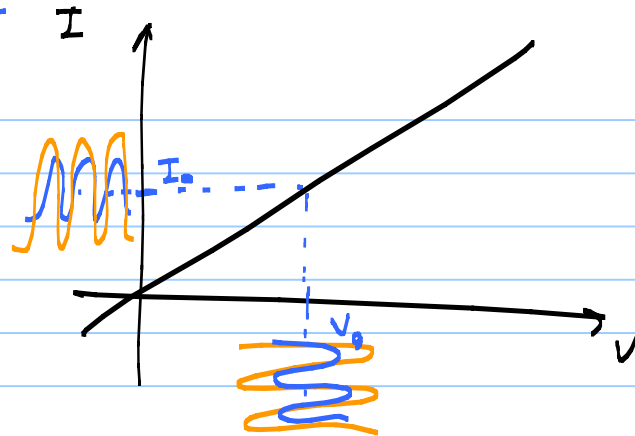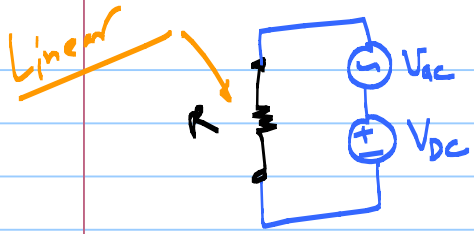

Non-linear Device

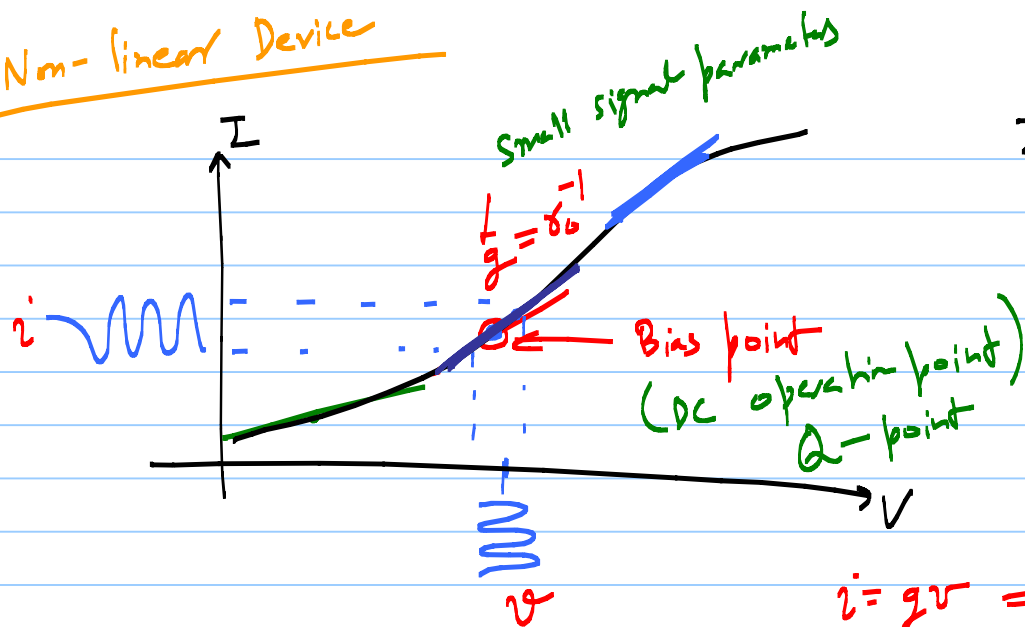

$$I = f(V)$$

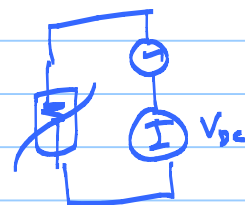

$$i = g v = \frac{v}{r_o}$$

$x = x_1$

$$I = f(v)$$

Taylor series expansion around
 $V = V_0$

$$= f(v_0) + \frac{f'(v_0)}{1!} \underbrace{(v-v_0)}_v + \frac{f''(v_0)}{2!} \underbrace{(v-v_0)^2}_{v^2} + \frac{f'''(v_0)}{3!} \underbrace{(v-v_0)^3}_{v^3} + \dots$$

$$V = V_0 + v$$

$$I = \underbrace{f(v_0)}_{I_0} + f'(v_0) \cdot v + \frac{f''(v_0)}{2!} \cdot v^2 + \frac{f'''(v_0)}{3!} \cdot v^3 + \dots$$

$$v = I - I_0 = \alpha_1 v + \alpha_2 v^2 + \alpha_3 v^3 + \dots$$

$$f'(v_0) = g$$

$v \uparrow$

for small v

$$z = g_1 v$$

v is larger

$$z = g_1 v + g_2 v^2 + g_3 v^3 + \dots$$

harmonic distortion