
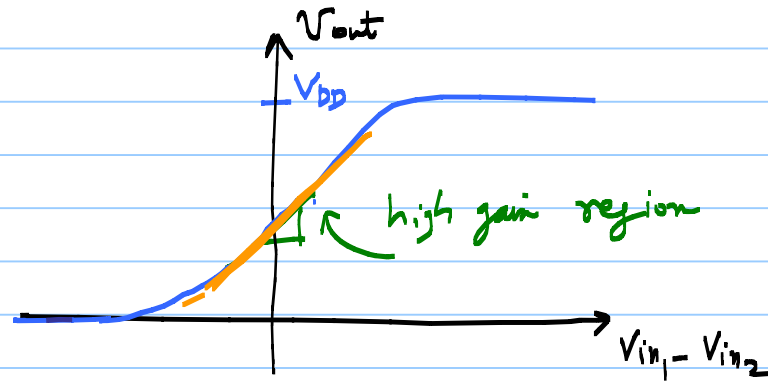


ECE 511 - Lecture 20

Note Title

4/9/2013

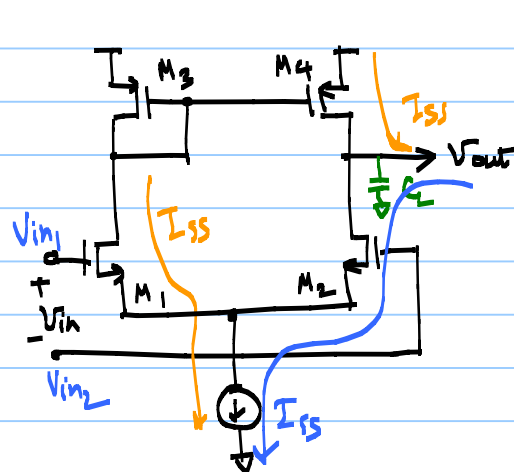


($V_{in,cm}$) Input CMR $\leftarrow [V_{GGS1} + V_{DS1}, V_{DD} - V_{SGS} + V_{THN}]$

output range

$\rightarrow V_{out} \geq V_{in,cm} - V_{THN}$

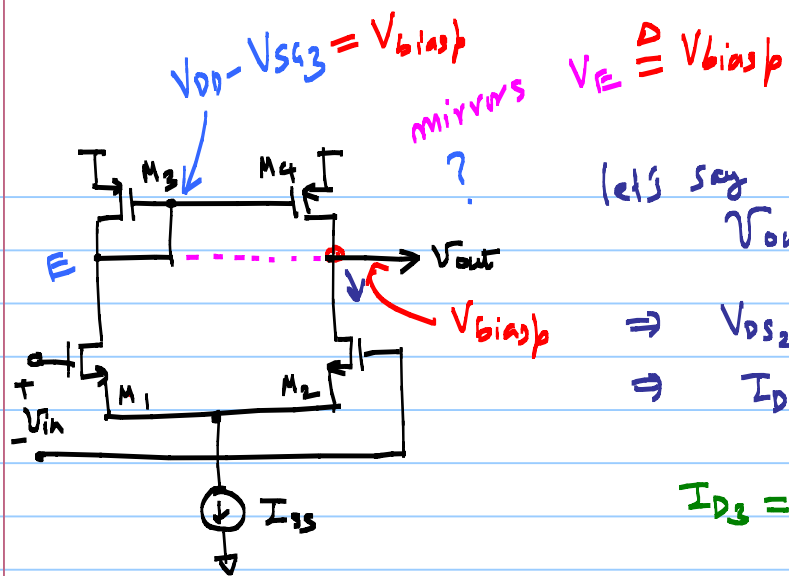↓
Voltage reqd. to
keep I_{SS} in saturation



let's say
 $V_{out} < V_E$

$$\Rightarrow V_{DS2} < V_{DS1}$$

$$\Rightarrow I_{D1} > I_{D2}$$

$$I_{D1} > \frac{I_{cs}}{2}$$

①

$$I_{D3} = I_{D1}$$

$$\therefore V_{SD4} > V_{SD3} \Rightarrow$$




$$I_{D4} > I_{D3}$$

$$I_{D4} > \frac{I_{cs}}{2} \Rightarrow I_{D2} > \frac{I_{cs}}{2}$$


$$\Rightarrow I_{D1} = I_{D2}$$

Contradiction

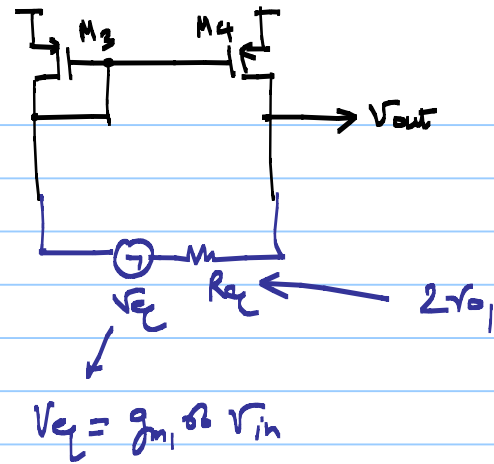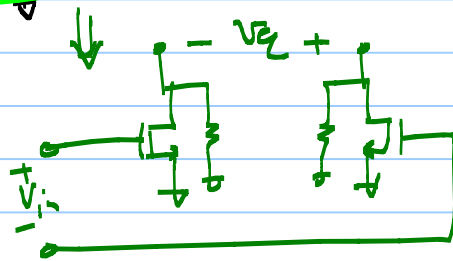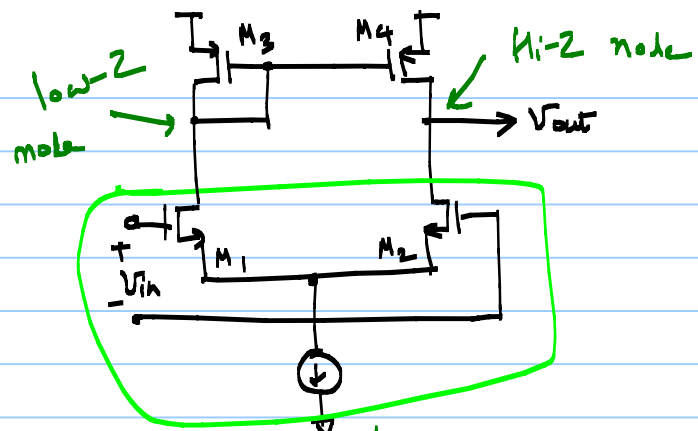$\Rightarrow V_{out}$ DC-level is well defined $\triangleq V_{biasp}$



"Handwaving Method" AC, DM circuit

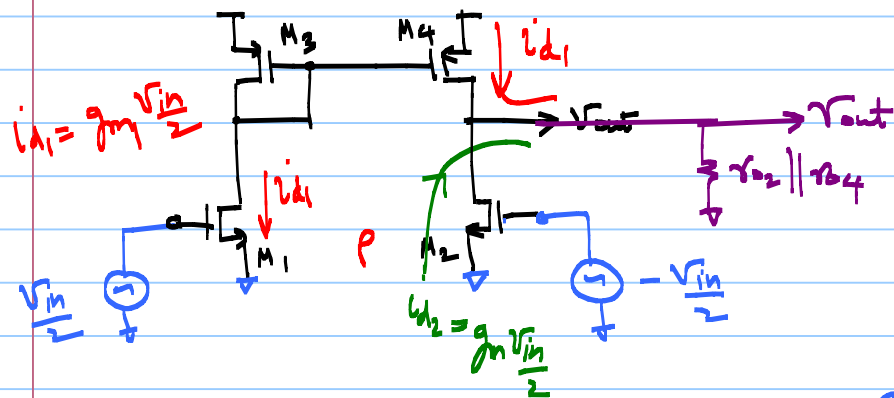


$$A_{v, DM} = g_{m1,2} (r_{o2} || r_{o4})$$

$$v_{out} = (i_{d1} + i_{d2}) (r_{o2} || r_{o4})$$


$$\Rightarrow \frac{v_{out}}{v_{in}} = g_{m1,2} (r_{o2} || r_{o4})$$

2x gain due to the current mirror

$$g_{m1,2} = g_{m1} = g_{m2}$$

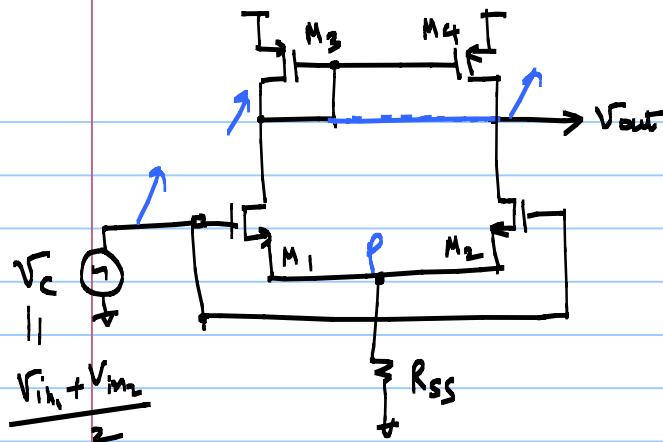

AC, CM equivalent circuit

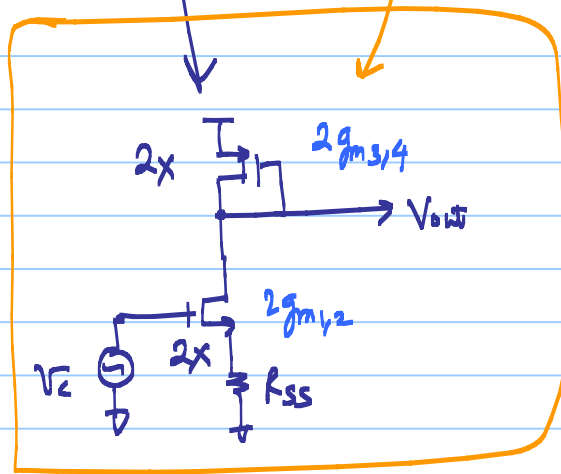

$$A_{v,cm} = -g_m \cdot \left(R_{out} \parallel \frac{1}{2g_{m3,4}} \right)$$


$$\approx -\frac{1}{1 + 2g_{m1,2}R_{ss}} \cdot \frac{g_{m1,2}}{g_{m3,4}} \rightarrow (2g_{m1,2} \cdot \frac{r_{o1,2}}{2}) R_{ss}$$

$$A_{v,cm} \approx -\frac{1}{2g_{m3,4}R_{ss}}$$


$$CMRR = \left| \frac{A_{v,DM}}{A_{v,CM}} \right| = g_{m1,2} (r_{o1,2} || r_{o3,4}) \cdot 2 g_{m3,4} R_{SS}$$

Diffamp Frequency Response

Differential Mode Circuit

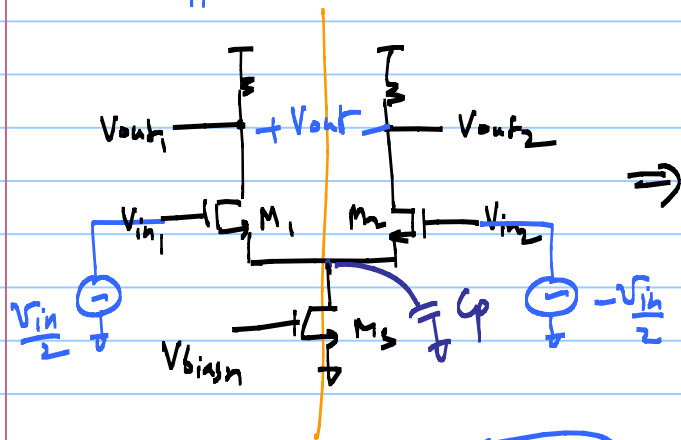


DM Half Circuit

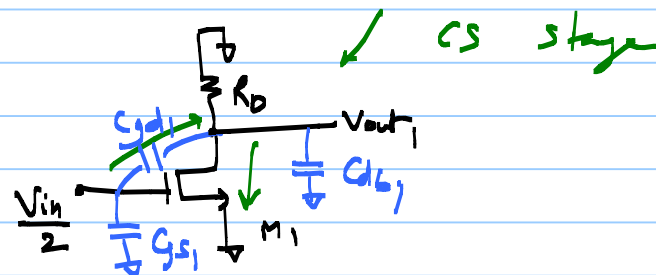

$$\frac{V_{out1} - V_{out2}}{V_{in1} - V_{in2}}(s) = - \frac{A_{vi} (1 - s/\omega_z)}{(1 + s/\omega_{p1})} \quad g_m R_D$$

$$\omega_{p1} = \frac{1}{(R_D \parallel R_o) C_L}, \quad \omega_z = \frac{g_{m1,2}}{C_{s1,2}}$$


CM picture

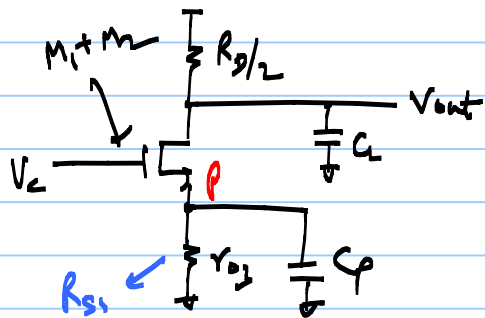


$$A_{r,cm}(s) = - \frac{\frac{R_D}{2} \parallel \frac{1}{sC_L}}{\frac{1}{2g_{m1,2}} + (r_{o3} \parallel \frac{1}{sC_P})}$$

@ high frequencies

CMKT degrades

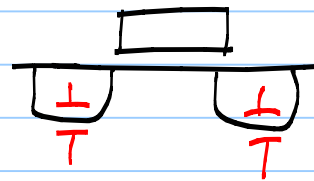

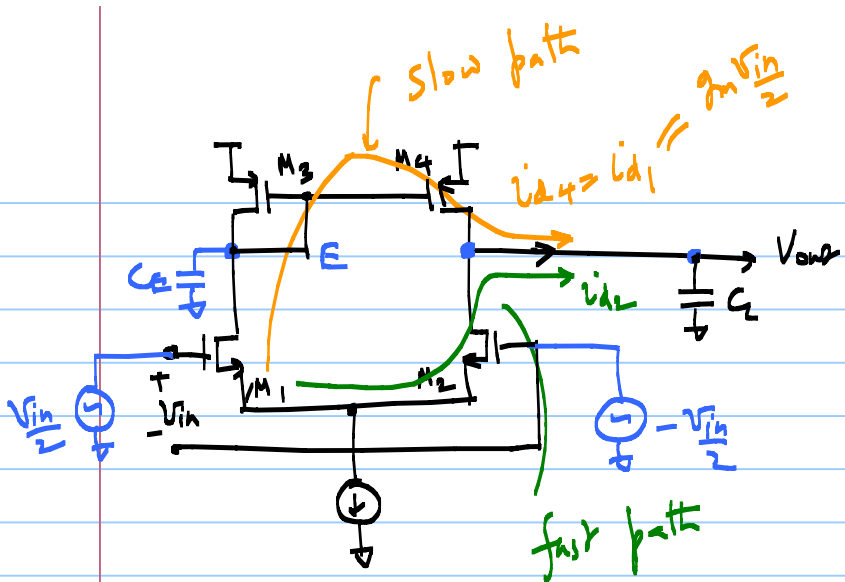

$$i_{d4} = i_{d1} = g_m \frac{V_{in}}{2}$$

$$i_{d2} = g_m \frac{V_{in}}{2}$$



$$C_E = C_{GS3} + C_{GS4} + C_{db3} + C_{db4} + \text{Miller caps from } C_{d1} \text{ \& } C_{d4}$$

* Sum of two frequency responses

$$\omega_{p1} \approx \frac{1}{(r_{o2} || r_{o4}) C_L}$$

$$\omega_{p2} \approx \frac{g_{m3}}{C_E} \approx \frac{g_{m3}}{3C_{SS}} \approx \frac{\omega_T}{3}$$



"Mirror pole" @ high frequency

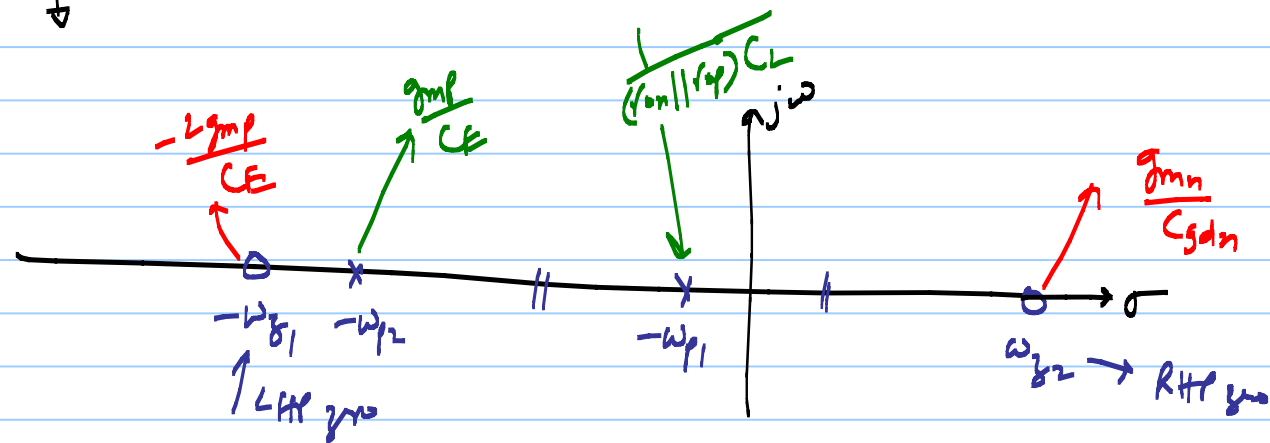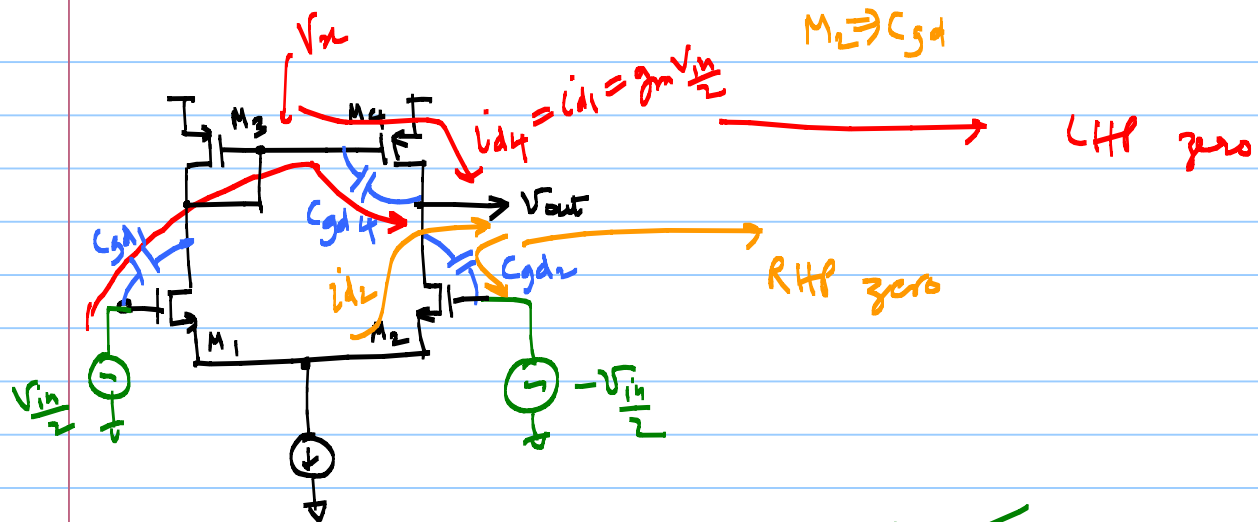

Operational Amplifiers (Opamps)


* integral block in any Mixed-Signal

* Opamp $\Rightarrow$ high gain VCVS

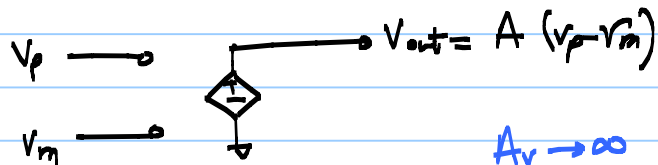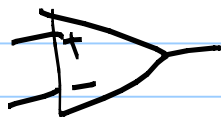

$$\left. \begin{array}{l} A_v \rightarrow \infty \\ Z_{in} \rightarrow \infty \\ Z_{out} \rightarrow 0 \end{array} \right\} \text{VCVS}$$

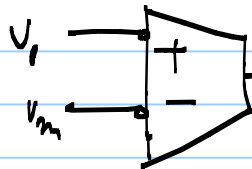* OTA (op. transconductance Amplifier) $\Rightarrow$ high g_m VCCS



$$i_{out} = g_m (V_p - V_m)$$

$$\left. \begin{array}{l} Z_{in} \rightarrow \infty \\ g_m \rightarrow \infty \\ Z_{out} \rightarrow \infty \end{array} \right\}$$

