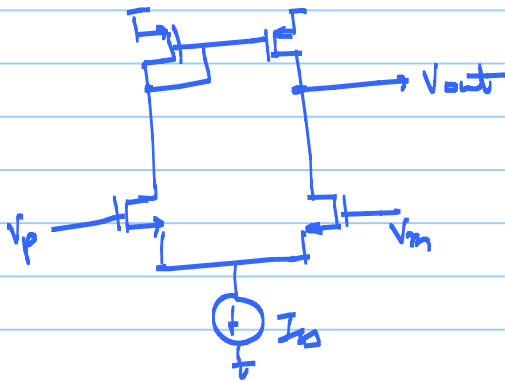



ECE 511- Lecture 21

Note Title

4/11/2013



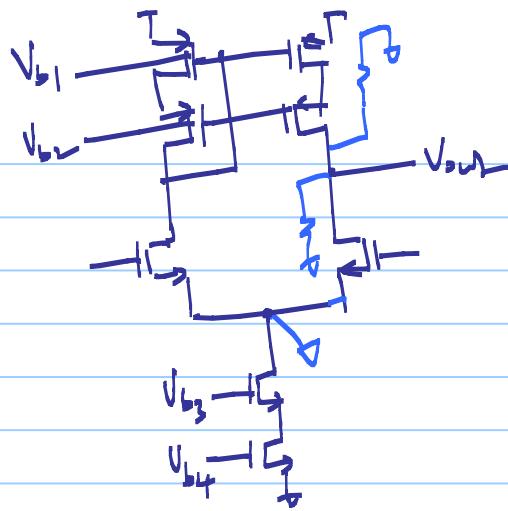
$$A_{v,DM} = g_m \cdot (r_{op} \parallel r_{on}) \approx g_m r_o$$



$$A_{v,om} = g_{m1} \cdot (r_{on} \parallel (g_{m2} r_{o2} \tilde{r}))$$

$$\approx g_{m1} r_{on}$$


Telescopic Amplifier

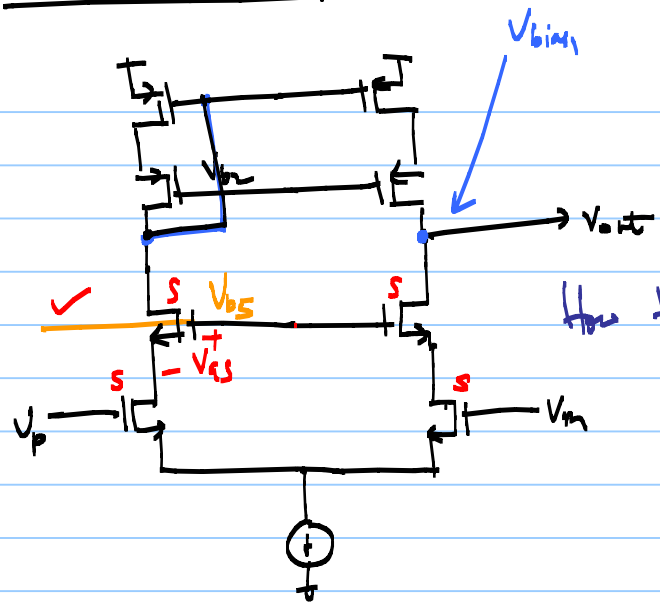


How to generate V_{b5} ?


"Telescope"

"Replica Biasing"

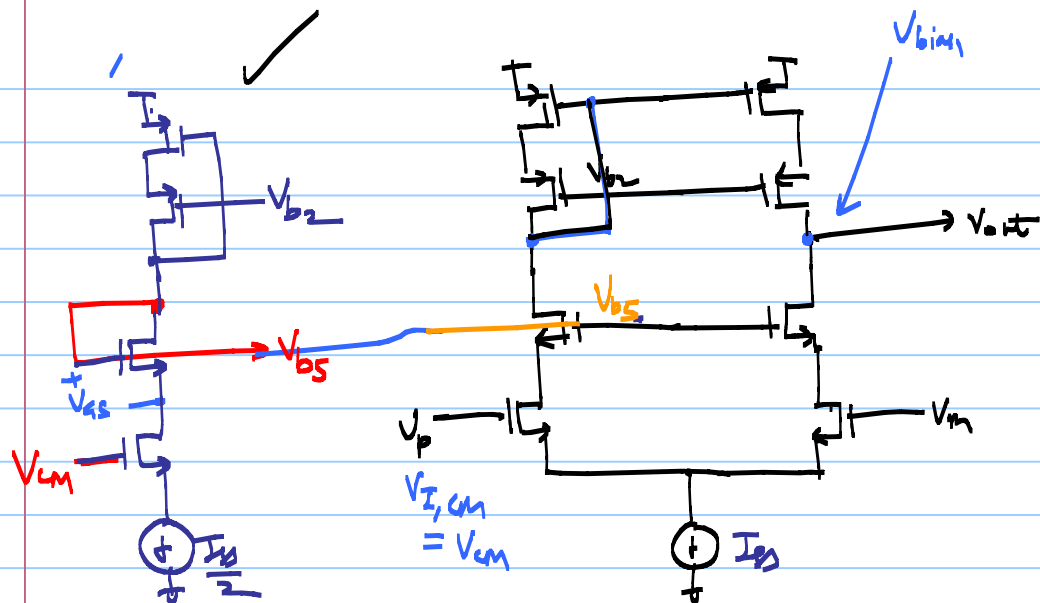

(conceptual)

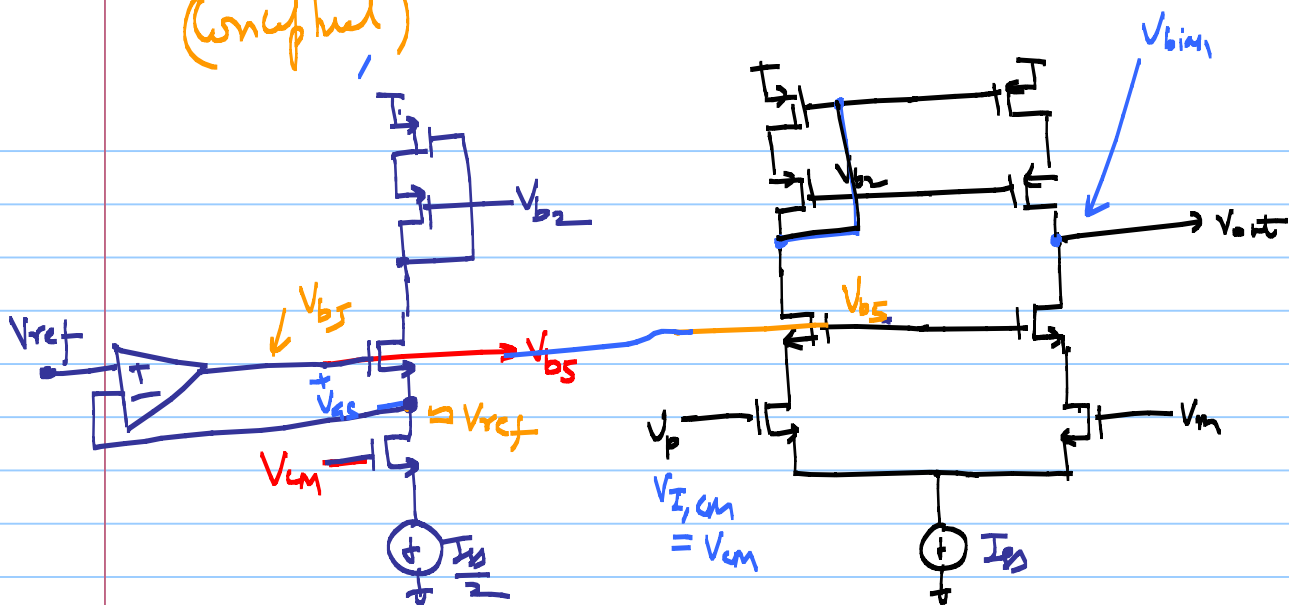


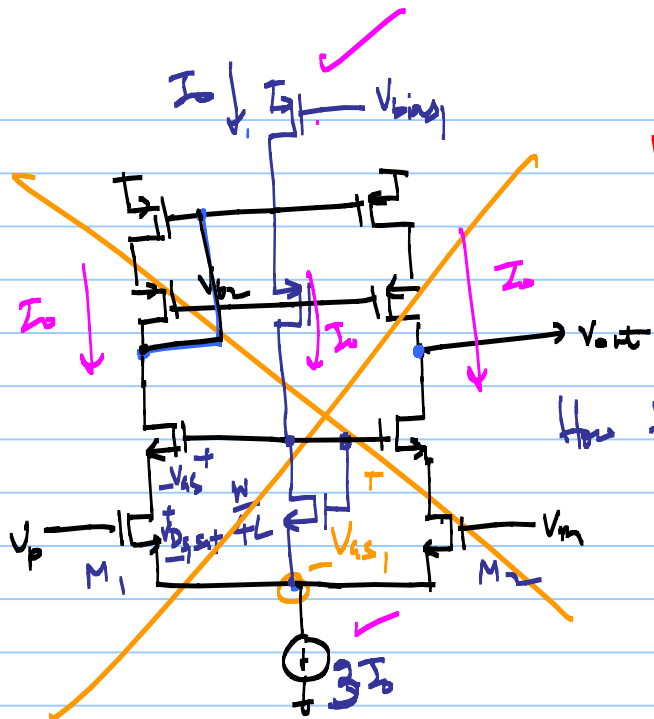

"Bias Stick disturbs biasing of the diff-pair"

How to generate V_{b5} ?
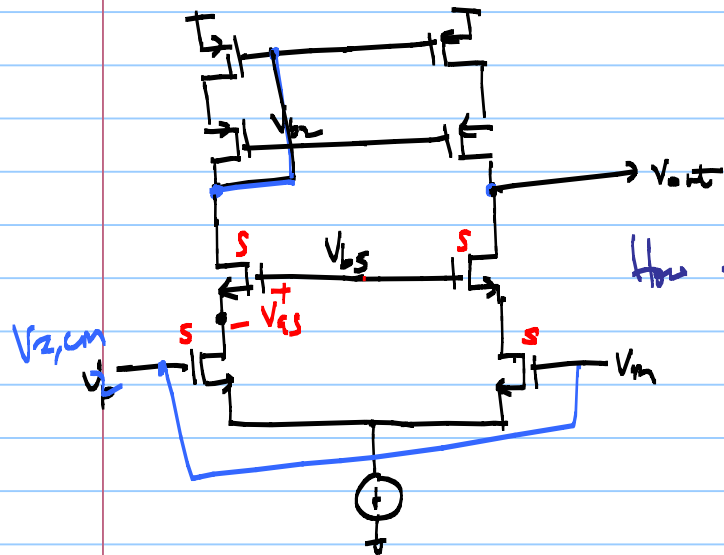
$$A_v = g_{m1} \cdot (R_{D1} \parallel R_{D2})$$



How to generate V_{DS} ?

$$V_{in,cm} \geq V_{DS} + V_{GS} = V_{GS} + 2V_{DS,sat} = 3V_{DS,sat} + V_{THN}$$


$$V_{in,cm} \leq V_{DD} - \underbrace{V_{SG} - V_{DS,sat}}_{\text{orange box}} + V_{THN}$$

"input CMR is limited"

Opamp performance Metrics


① gain

ideal opamp, A , ✓ DC gain
(no pole)

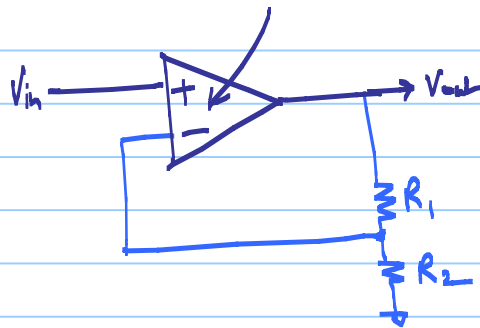


$$\beta = \frac{R_2}{R_1 + R_2}$$

$$L = A\beta$$

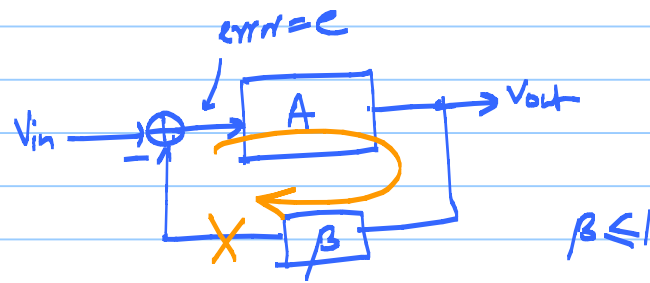

Loop-gain $L = A\beta$

Aside (Ideal opamp)

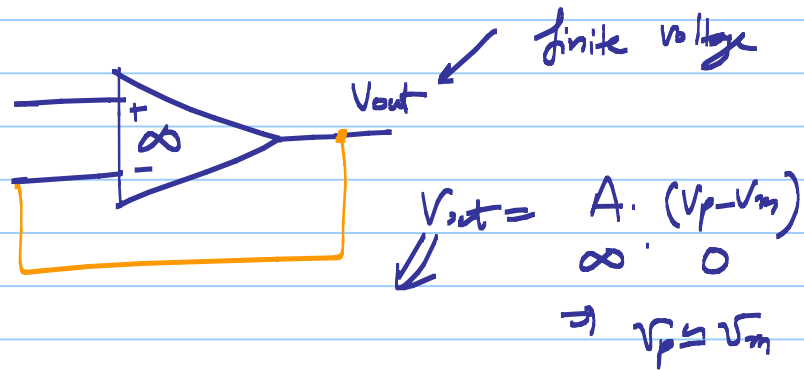

$$GBW = \text{gain} \times BW = \text{constant}$$

$$H_{cl} = \frac{V_{out}}{V_{in}} = \frac{A}{1+L} = \frac{A}{1+A\beta} \leftarrow$$

$\frac{G}{1+G+H}$
from controls

$$= \frac{1}{\frac{1}{A} + \beta}$$

if $A \rightarrow \infty$

$\approx \frac{1}{\beta} \rightarrow$ ideal closed-loop gain

$$\frac{R_1 + R_2}{R_2} = 1 + \frac{R_1}{R_2}$$

$$= \frac{1}{\beta} \cdot \frac{A\beta}{1+A\beta}$$

$$= \frac{1}{\beta} \cdot \frac{1}{1 + \frac{1}{A\beta}}$$

$$= \frac{1}{\beta} \cdot \left(1 + \frac{1}{A\beta}\right)^{-1}$$

$$= \frac{1}{\beta} \left(1 - \frac{1}{A\beta}\right)$$

$$|x| \ll 1$$

$$(1+x)^{-1} \approx 1-x$$

$$\rightarrow = 1 - x + \cancel{\frac{x^2}{2}} - \cancel{\frac{x^3}{3}} + \cancel{\frac{x^4}{4}}$$

$$\frac{V_{out}}{V_{in}} = \underbrace{\left(\frac{1}{\beta}\right)}_{\text{ideal closed-loop gain}} \left(1 - \underbrace{\frac{1}{A\beta}}_{\text{Error} \Rightarrow \epsilon}\right) \quad \text{relative gain error}$$

for $\epsilon \rightarrow 0$
 $A\beta \gg 1$


$$\epsilon = \frac{1}{A\beta} \quad \text{for } \frac{1}{\beta} = 10$$

for $\epsilon < 1\% \Rightarrow A > 1000 = 60 \text{ dB}$

↑ gain error

A sets the precision requirements

② Small-signal BW

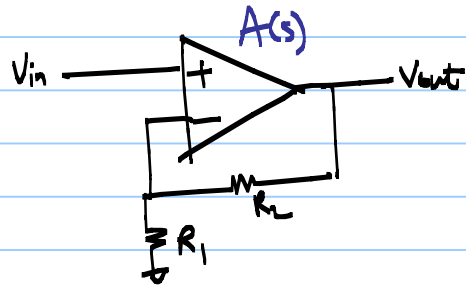

$$A(s) = \frac{A_0}{\left(1 + \frac{s}{\omega_0}\right)} \rightarrow \text{dominant pole model}$$

$$\text{Loop gain} = \beta A(s) = \frac{A_0 \beta}{1 + \frac{s}{\omega_0}}$$

$$A_{CL}(s) = \frac{V_{out}}{V_{in}}(s) = \frac{A(s)}{1 + L(s)} =$$

$$= \frac{\frac{A_0}{\left(1 + \frac{s}{\omega_0}\right)}}{1 + \frac{A_0 \beta}{\left(1 + \frac{s}{\omega_0}\right)}} = \frac{A_0}{1 + \frac{s}{\omega_0} + \beta A_0}$$

$$= \frac{A_0}{(1+\beta A_0) + \frac{s}{\omega_0}} = \left(\frac{A_0}{1+\beta A_0} \right) \cdot \frac{1}{1 + \frac{s}{\omega_0(1+\beta A_0)}}$$

$$= A_{CL} \cdot \frac{1}{\left(1 + \frac{s}{\omega_{3dB}}\right)}$$


$$-3dB \text{ BW} = \omega_{3dB} = \omega_0(1+\beta A_0)$$

$$\begin{aligned} &\leq \omega_0 \beta A_0 \\ &= \beta (A_0 \omega_0) \\ &= \beta \cdot \omega_{un} \end{aligned}$$

$$\omega_{3dB} = \beta \cdot \omega_{un}$$


$$\Rightarrow \omega_{un} = \frac{1}{\beta} \cdot \omega_{3dB} = A_{CL} \cdot \omega_{3dB}$$
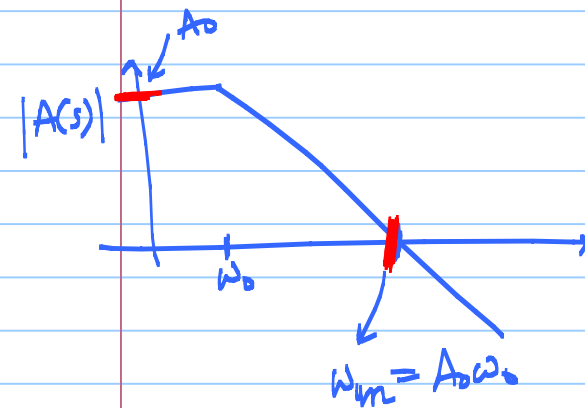
$$\boxed{\omega_{un} = \text{Gain} \times \text{BW}} \quad \text{Trade-off}$$




$$\boxed{\omega_{2+3} \cdot A_{OL} = \omega_{un}}$$

Exactly true for dominant-pole opamp

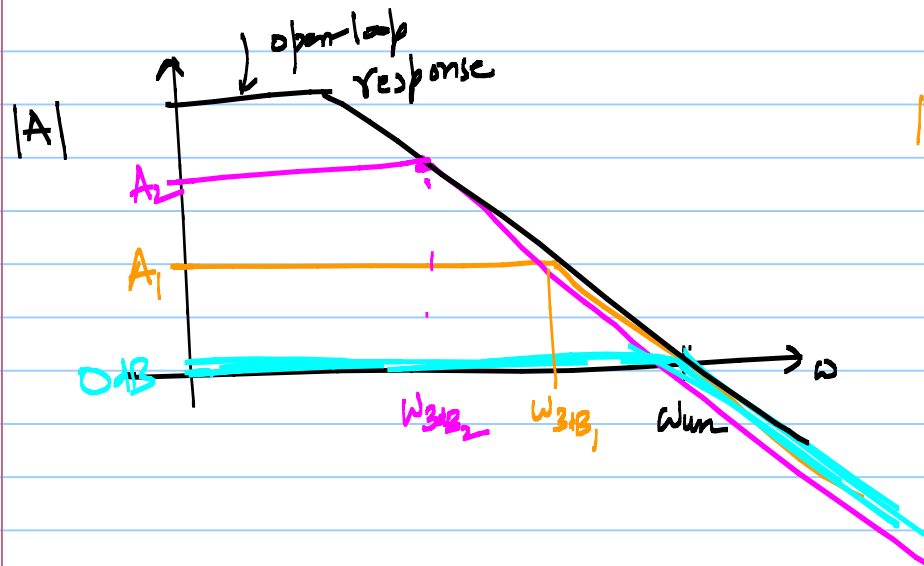


$$\beta < \frac{1}{2}$$
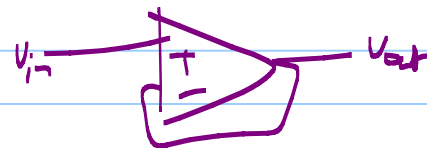
$$\beta = 1 \Rightarrow \omega_{2+3} = \omega_{un}$$



$$A_{CL}(s) \Rightarrow \frac{1}{\beta} \cdot \frac{1}{1 + s/\omega_{3dB}} \quad \tau = \frac{1}{\omega_{3dB}}$$
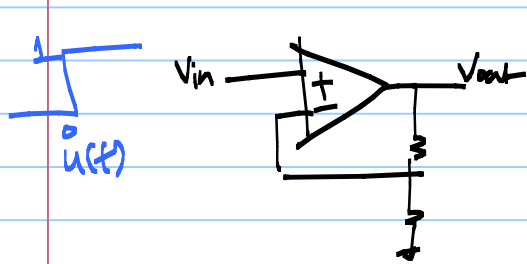
$$v_{out}(t) = \frac{1}{\beta} \cdot (1 - e^{-t/\tau}) u(t)$$



* Settling accuracy

$$v_{out} = \frac{1}{\beta} (1 - e^{-t/\tau}), \quad \text{allow } T_1 \text{ to settle}$$

$$\text{settling error} = e^{-T_1/\tau}$$

for 1% settling accuracy

$$1 - e^{-T_1/\tau} = 0.99$$

$$\Rightarrow T_1 = 4.62 \approx 5\tau$$

with a gain of 10

Ex. for 1% settling τ of 5ns $\Rightarrow \tau = 1.09 \text{ ns} \approx 1 \text{ ns}$

$$\omega_{3dB} = \frac{1}{\tau} = 1 \text{ G rad/s}$$

$$\text{Gain} = \frac{1}{\beta} = 10 \Rightarrow \omega_{un} = 10 \times \omega_{3dB}$$

$$\omega_{un} = 10 \times 10^9$$

$$f_{un} = \frac{\omega_{un}}{2\pi} = 1.47 \text{ GHz}$$