

ECE 511 - Lecture 22

Note Title

4/16/2013


* Slewiness

$$A_{cl} = \frac{A_v}{1 + A_v} \rightarrow 1$$



small signal TF

$$A_{cl}(s) = \frac{1}{1 + \frac{s}{\omega_{3dB}}}$$

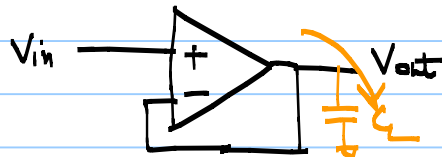
$$\omega_{3dB} = \frac{\omega_{um}}{A_{cl}}$$




linear response

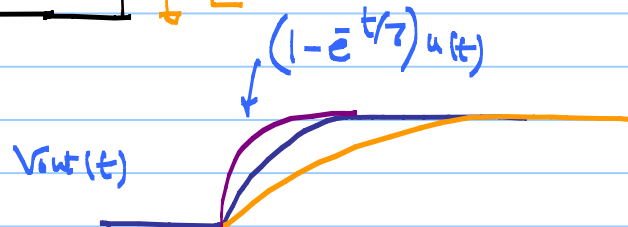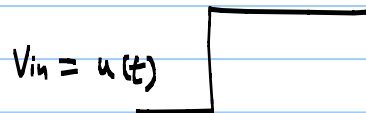


$$i_L = C_L \frac{dV_{out}}{dt}$$

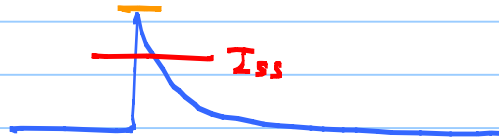

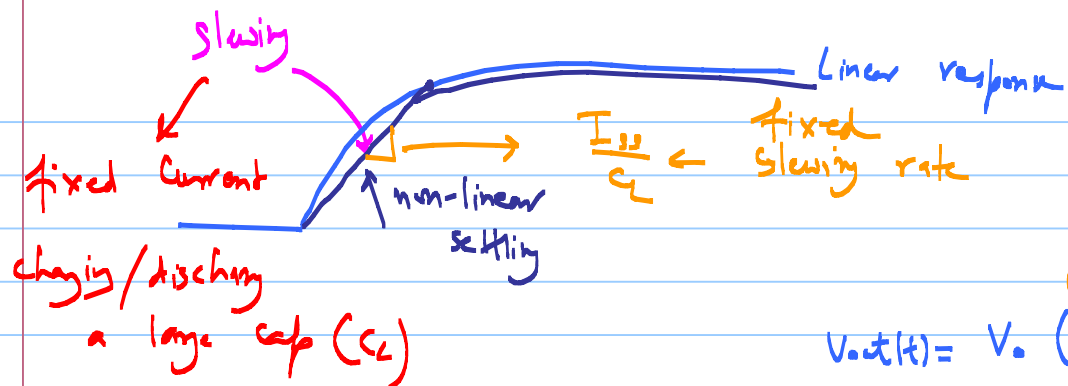


$$V_{out}(t) = V_o \left(1 - e^{-\frac{(1-\epsilon)t}{T_1}} \right)$$

error


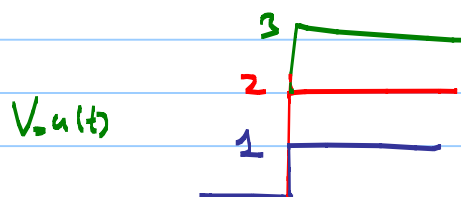


Linear settling

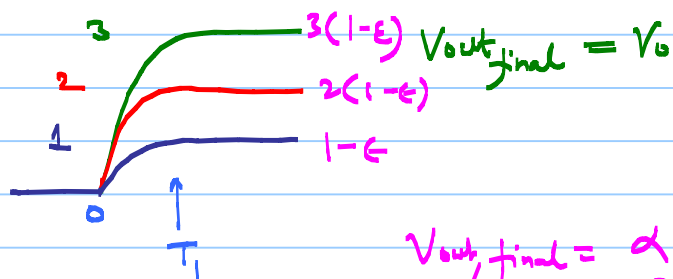

$$V_{out, final} = \alpha V_o$$

constant

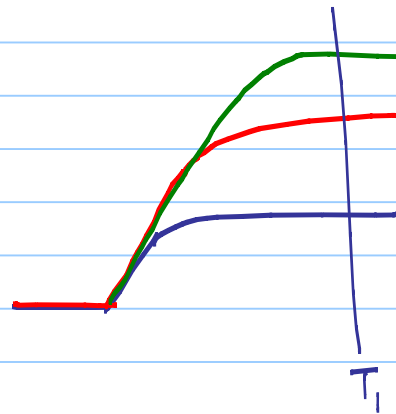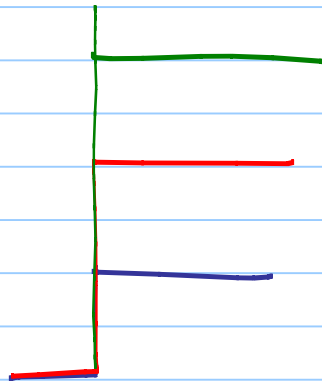


The settled values are not proportional

with different input step height

the final output is not "linear"

$V_{out, final}$

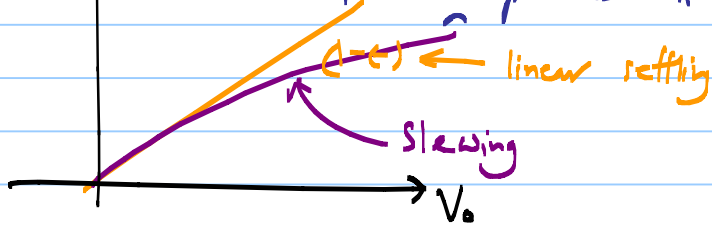

"non-linearity"

④ Output swing

↳ trades off with device size, V_{ov} , current & speed

SNR trade off

→ Use FD circuit

$S \rightarrow 6\text{dB}$

$N \rightarrow 3\text{dB}$

SNR 3dB gain

⑤ Linearity

① FD circuits → eliminate even-order harmonics



$$f_{\text{odd}}(x) = \frac{f\left(\overset{V_{in}}{x}\right) - f\left(\overset{-V_{in}}{-x}\right)}{2}$$

② Use large open-loop gain $\Rightarrow$ reduces non-linearity

* Noise & offset $\rightarrow$ ECE 614

* Supply noise rejection $\rightarrow$ FD circuits


U_{GB}

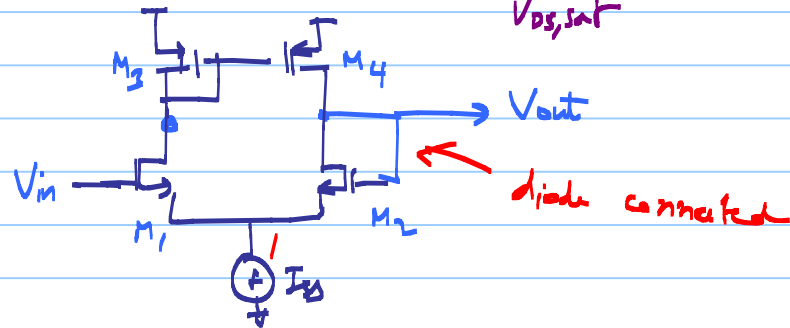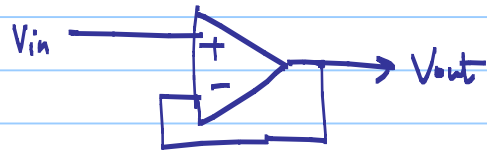

$$\begin{aligned} V_{DD} &= 3V \\ V_{THN,p} &= 0.7V \\ V_{ov} &= 0.3V \\ V_{DS,sat} & \end{aligned}$$

* Input CMR

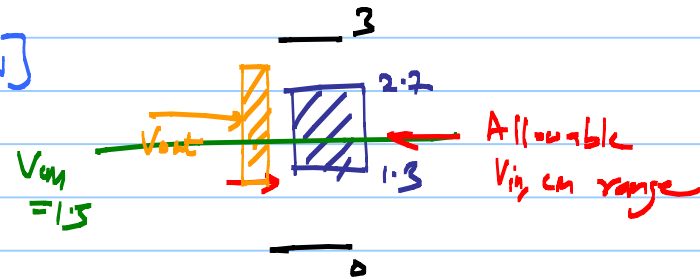
$$\begin{aligned} V_{in,cm} &\in [V_{GS} + V_{DS,sat}, V_{DD} - V_{GS} + V_{THN}] \\ &= [1.3, 2.7V] \end{aligned}$$



$$R_{o,CL} = \frac{R_{o,OL}}{1 + \text{loop gain}} = \frac{\cancel{r_{op} \parallel r_{on}}}{1 + g_m(\cancel{r_{op} \parallel r_{on}})} \approx \frac{1}{g_m}$$

⇒ low output impedance

∴ loop gain is also large

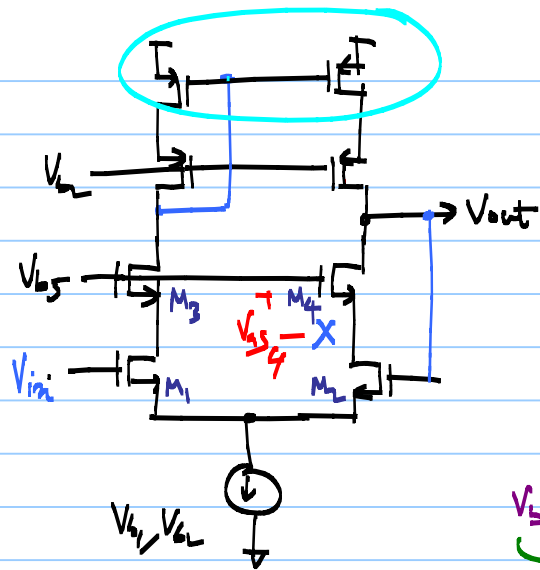

* M_2 & $M_4 \rightarrow \text{SAT}$

$$V_{out} \leq V_{a2} + V_{THN} \quad \text{--- (1)} \quad : M_2 \text{ SAT}$$

$$V_{out} \geq V_{b5} - V_{THN} \quad \text{--- (2)} \quad : M_4 \text{ SAT}$$

$$V_{a2} = V_{b5} - V_{a54} \rightarrow \text{--- (3)}$$

$$\underbrace{V_{b5} - V_{THN}}_{V_{min}} \leq V_{out} \leq \underbrace{V_{b5} - V_{a54} + V_{THN}}_{V_{max}}$$

allowed

output range: $V_{max} - V_{min} = 2V_{THN} - V_{a54}$


$$\approx \underbrace{V_{THN} - V_{ov4}}_{\text{very small range}}$$

very small range

* Can't make a UCB with a single-stage Telescopic opamp



(-) limited output swing

(+) difficulty in sharing input & output

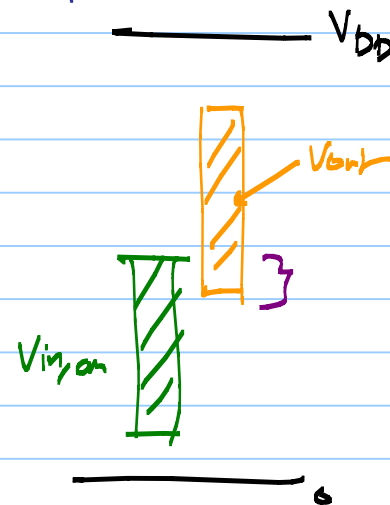

Folded Cascode Amplifiers

NMOS Cascode

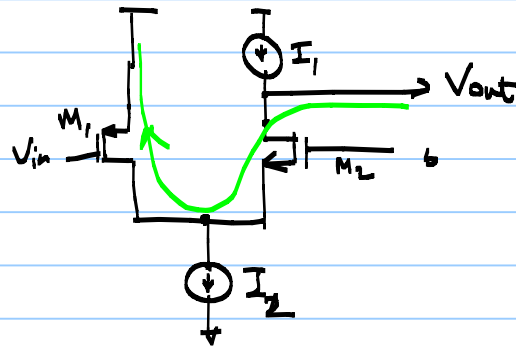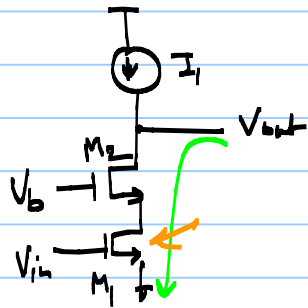


$$I_2 > I_1$$


Gain: $A = -g_{m1} \cdot R_{out}$

(+) FC doesn't "stack" the cascode transistor on top of the input device.

↳ helps with headroom issues

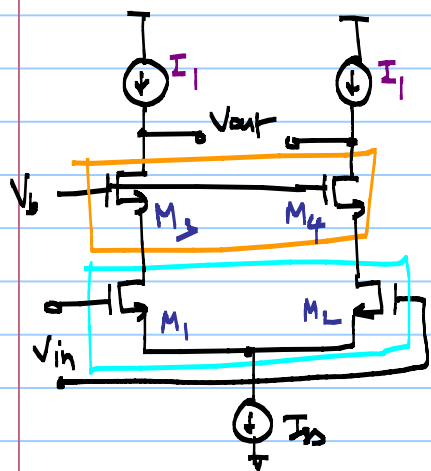
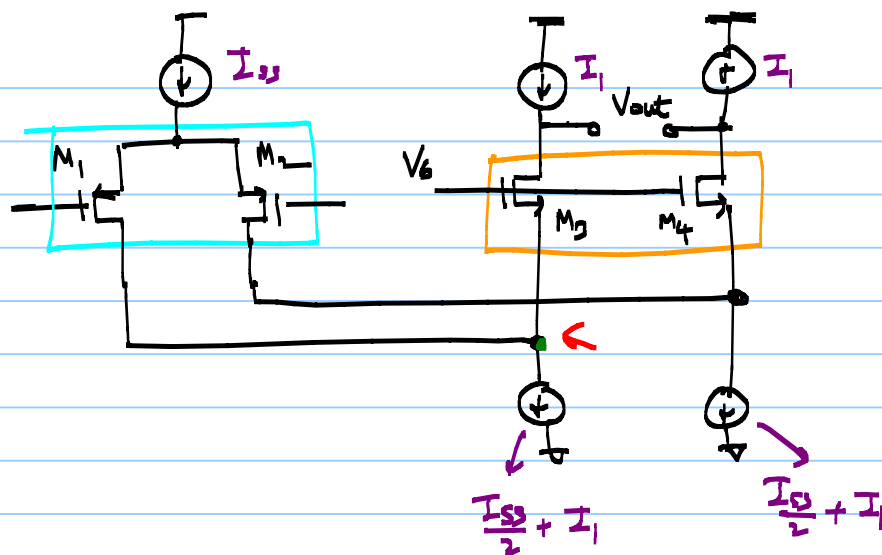
$$V_{cm,in} \leq V_b - V_{GS} + V_{THN}$$




to keep M_1 & M_2 is SAT

$$V_{cm,in} \geq \underbrace{V_b - V_{GS}} - V_{THN}$$


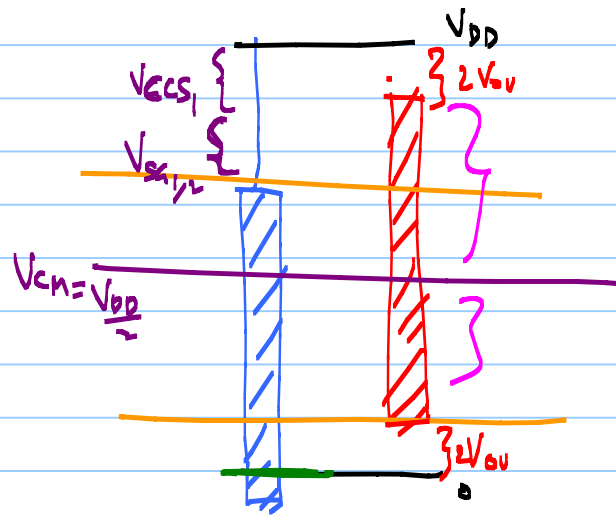
$$V_{in,cm} \geq V_{DS,sat5} - V_{TH1} < 0$$



* Easily short input & output

* Wide input CMR

* PMOS input CMR includes GND rail

* NMOS input CMR includes the V_{DD} rail

* Consumes $2 \times$ bias current $\rightarrow$ higher power consumption than telescopic

