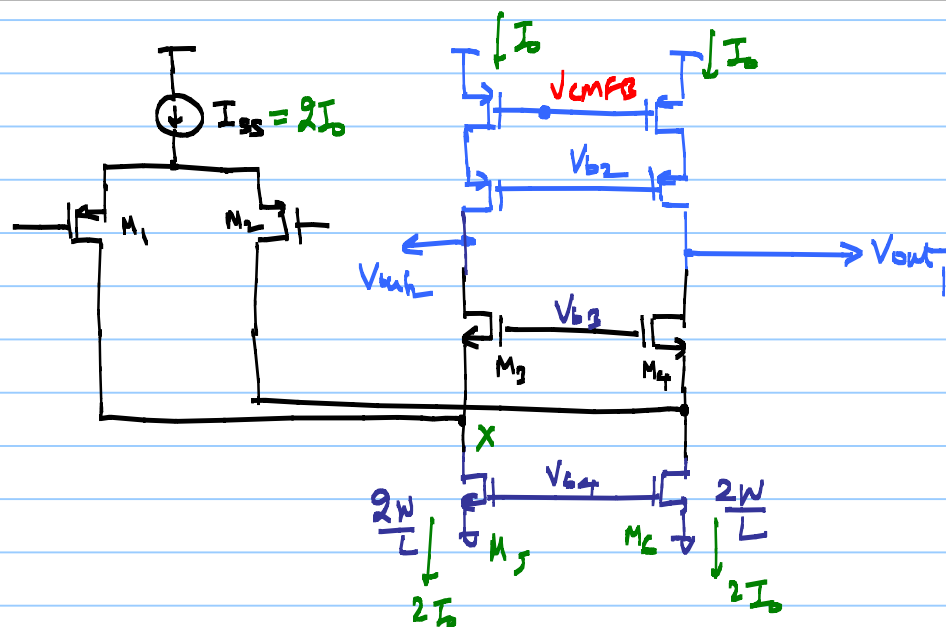



ECE 511 — Lecture 23

Note Title


4/18/2013



"DM Az picture"

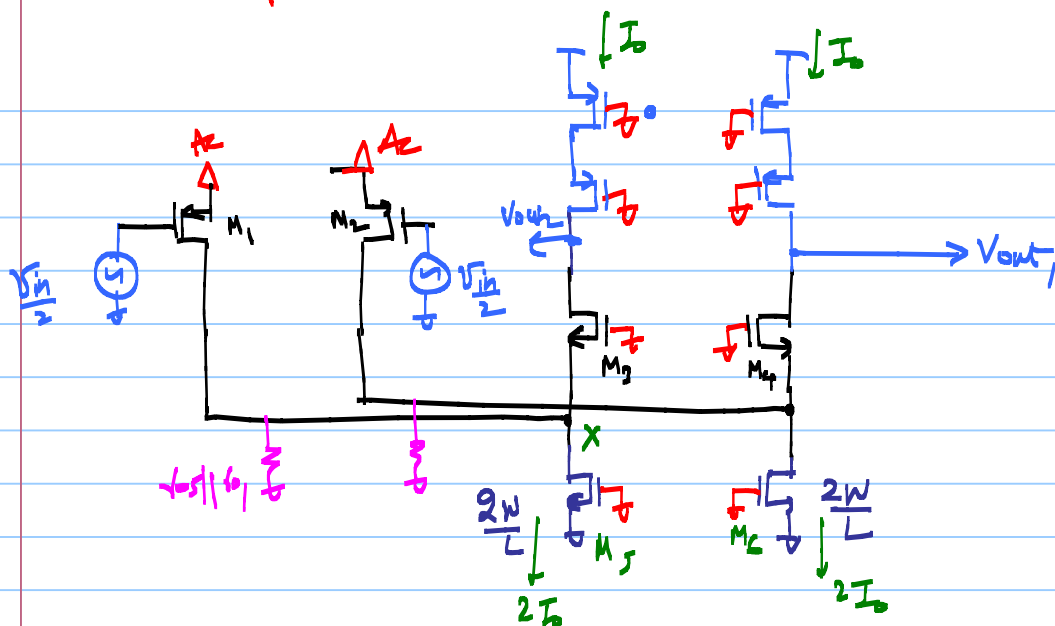

DM

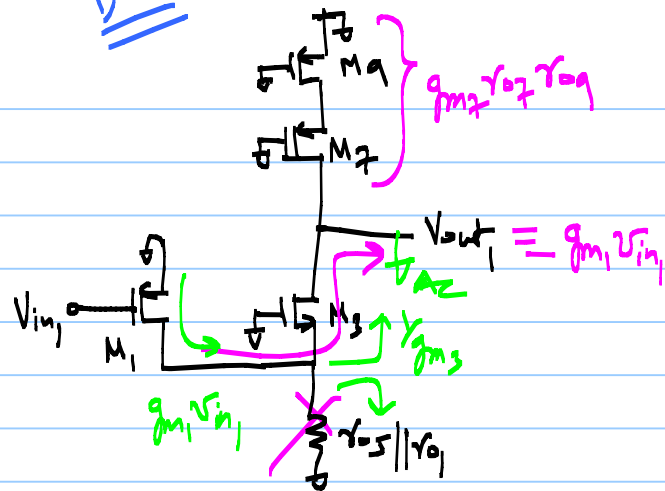


"Lemma"

$$A_v = -g_m \cdot R_{out}$$

g_m
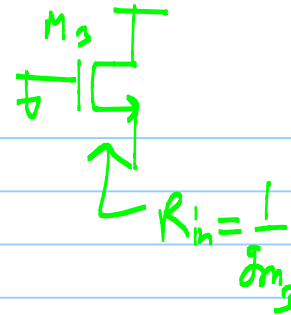
$$(g_{m1} r_{O2} r_{O9}) \parallel (g_{m3} r_{O3} (r_{O5} \parallel r_{O1}))$$



$$A_{v, DM} = -g_{m1} \cdot (g_{m2} r_{O2} r_{O9}) \parallel (g_{m3} r_{O3} (r_{O5} \parallel r_{O1}))$$


$$\approx -g_{mp} \cdot \boxed{g_{mp} r_{Op}^2} \parallel \boxed{g_{mn} \cdot \frac{r_{On} L}{2}}$$

Telescopic gain


$$A_T = -g_{mn} \cdot (R_{ocsp} \parallel R_{ocsn})$$

$$= -g_{mp} \cdot (R_{ocsp}) \parallel \left(\frac{R_{ocsn}}{2} \right) \checkmark$$

= 2-3 x lower than the Telescopic

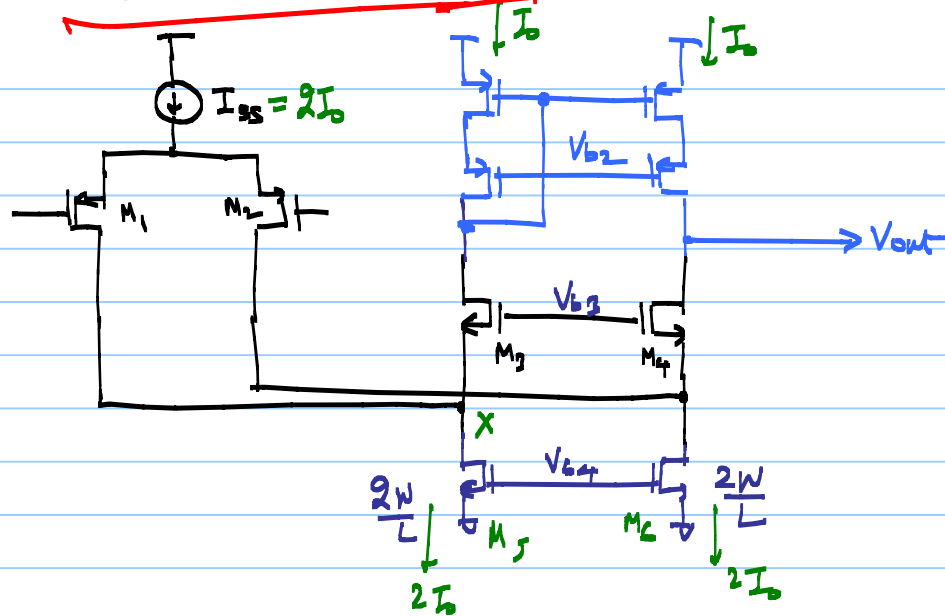


A2 picture


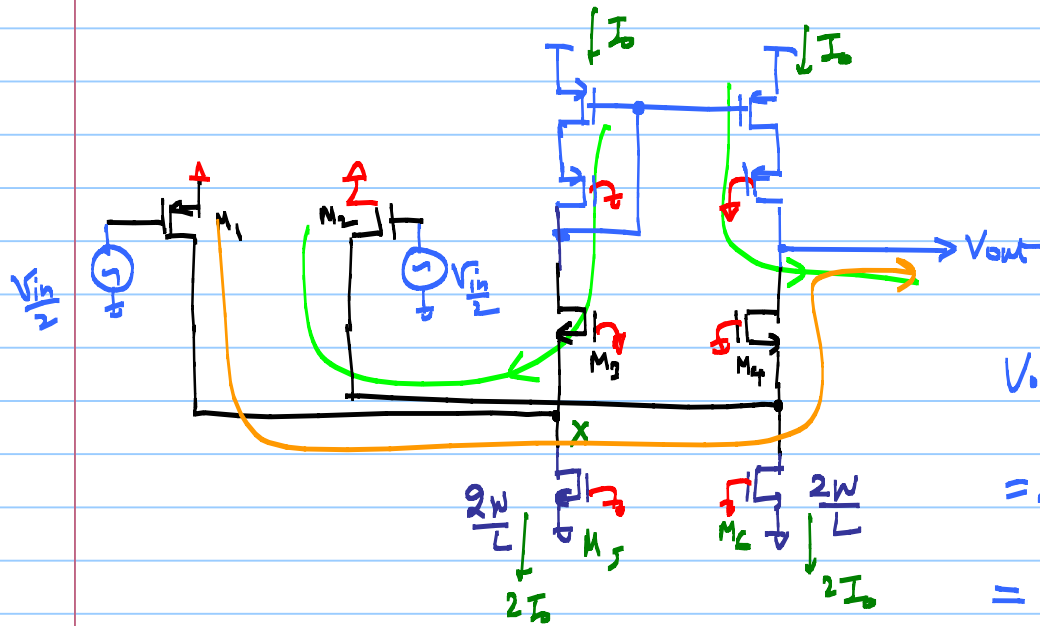


$$\begin{aligned}
 V_{out} &= 2 i_{d1} \cdot R_{out} \\
 &= 2 \times (\text{gaining the half circuit}) \\
 &= -g_{mp} \cdot (R_{o\text{casp}}) \parallel \left(\frac{R_{o\text{casp}}}{2} \right)
 \end{aligned}$$

AC CM Picture

"Fold the circuit"

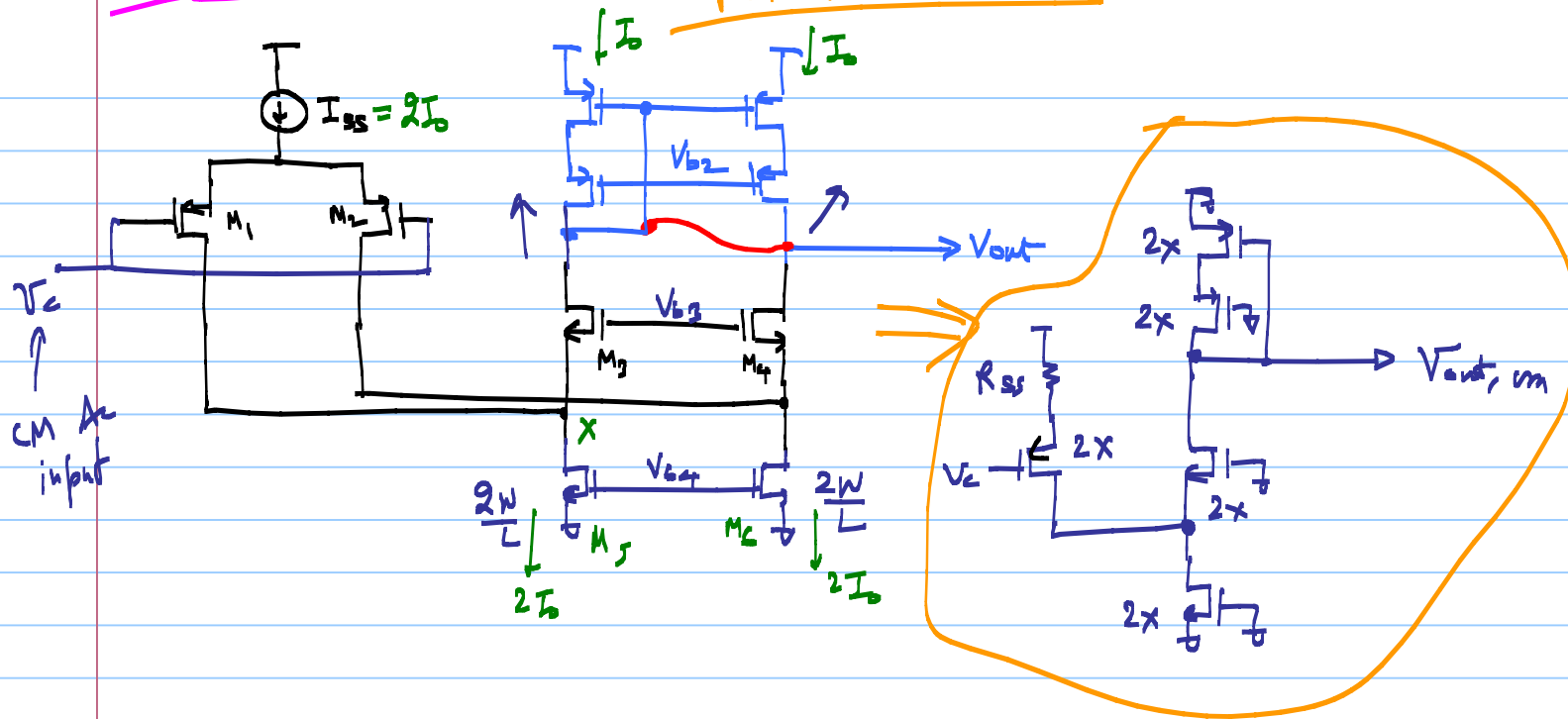

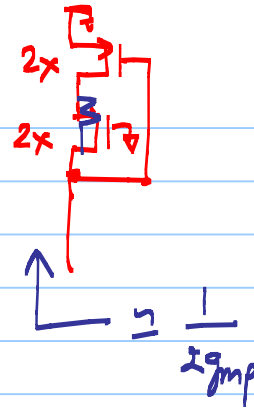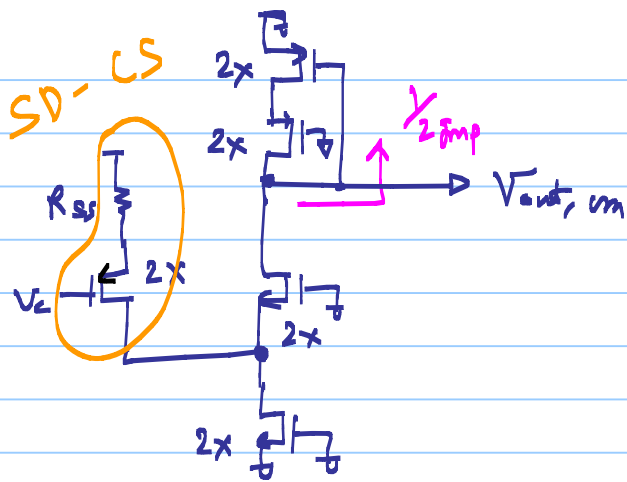

"Lemma"

$$A_{v, cm} = -g_{m1} \cdot R_{out}$$

$\frac{2g_{m1}}{1 + 2g_{m1}R_{SD}}$

$\frac{1}{2g_{mp}}$


$$CMRR = \frac{A_{v, DM}}{A_{v, cm}}$$

for single-ended FE


$$A_{v,DM} = g_{mp} \cdot (R_{ocsp}) \parallel \left(\frac{R_{ocun}}{2} \right)$$

$$A_{v,cm} = \frac{\cancel{2g_m}}{1 + 2g_{m1}R_{S1}} \cdot \frac{1}{\cancel{2g_m}} \approx \frac{1}{1 + 2g_{mp}R_{S2}}$$
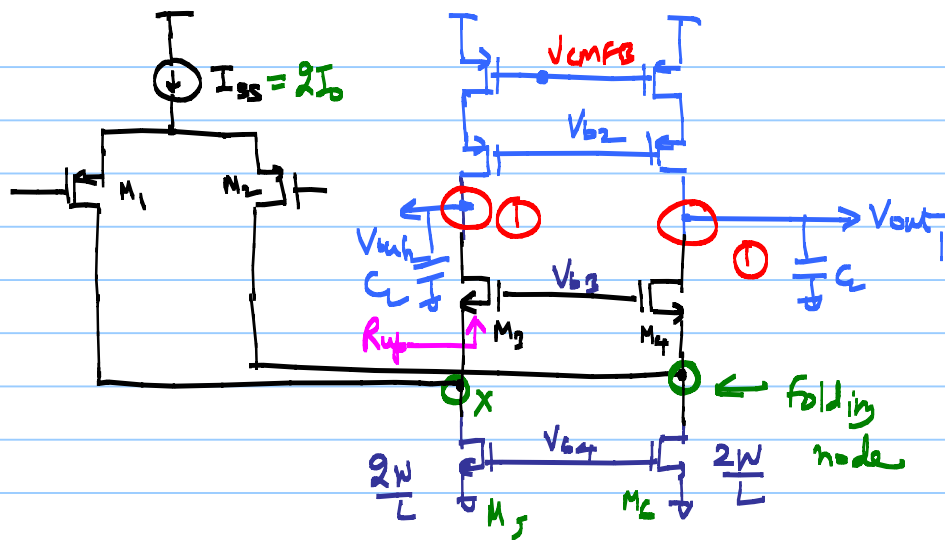
$$CMRR = \frac{A_{v,DM}}{A_{v,cm}} = (1 + 2g_{mp}R_{S2}) \cdot g_{mp} \cdot \left[(g_{m1}r_{op}^2) \parallel \left(\frac{g_{m2}r_{on}}{2} \right) \right]$$



$$\omega_{p1} = \frac{1}{R_{out} C_L}$$

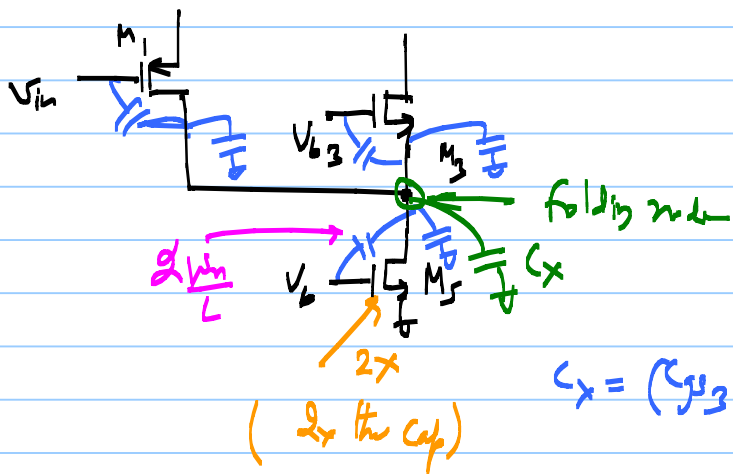

$$C_x = (C_{gs3} + C_{sb3}) + (C_{db1} + C_{d1}) + (C_{ds5} + C_{db5})$$

$$R_x = r_{o1} \parallel r_{o5} \parallel R_{up}$$


$$\approx \frac{r_o}{3}$$

$$\omega_{p1} \approx \frac{1}{R_x C_x}$$

$$R_D \leftarrow g_{mp} r_o^2$$

$$R_{up} \approx r_o$$

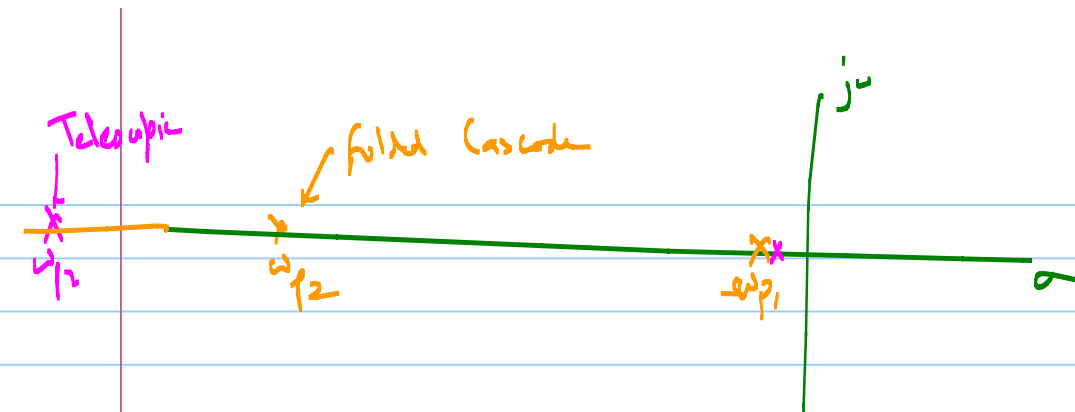
$$= \frac{1}{g_m} \text{ only if } R_D \leq r_o$$



$$A_v \downarrow \quad 2-3x$$

Stability is impaired due to ω_{p2}

(+ +) Headroom

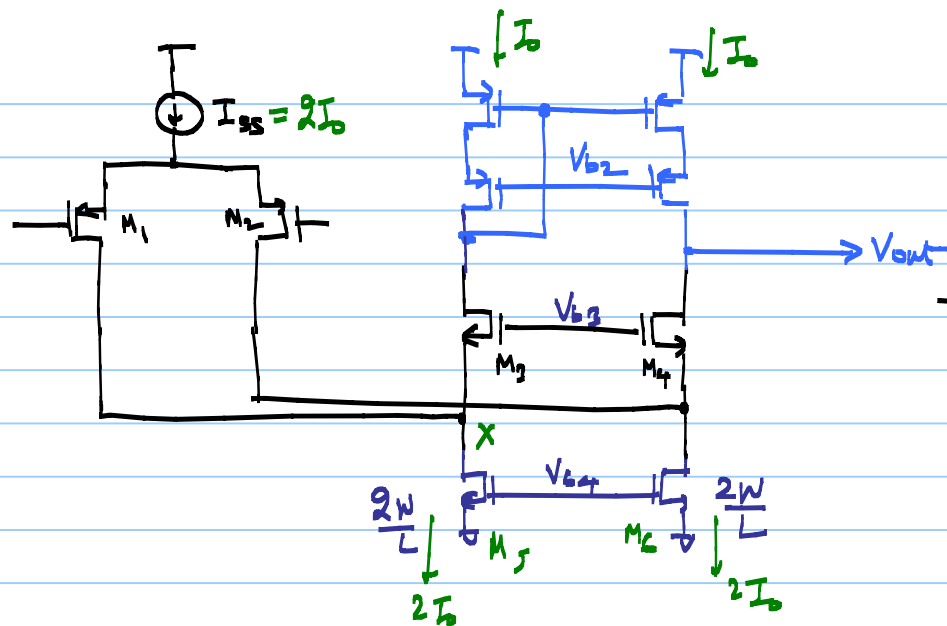


Input
CMR

PMOS input $\Rightarrow I_{SS}$


NMOS input $\Rightarrow V_{DD}$

"Combine for rail-rail

Input CMR"

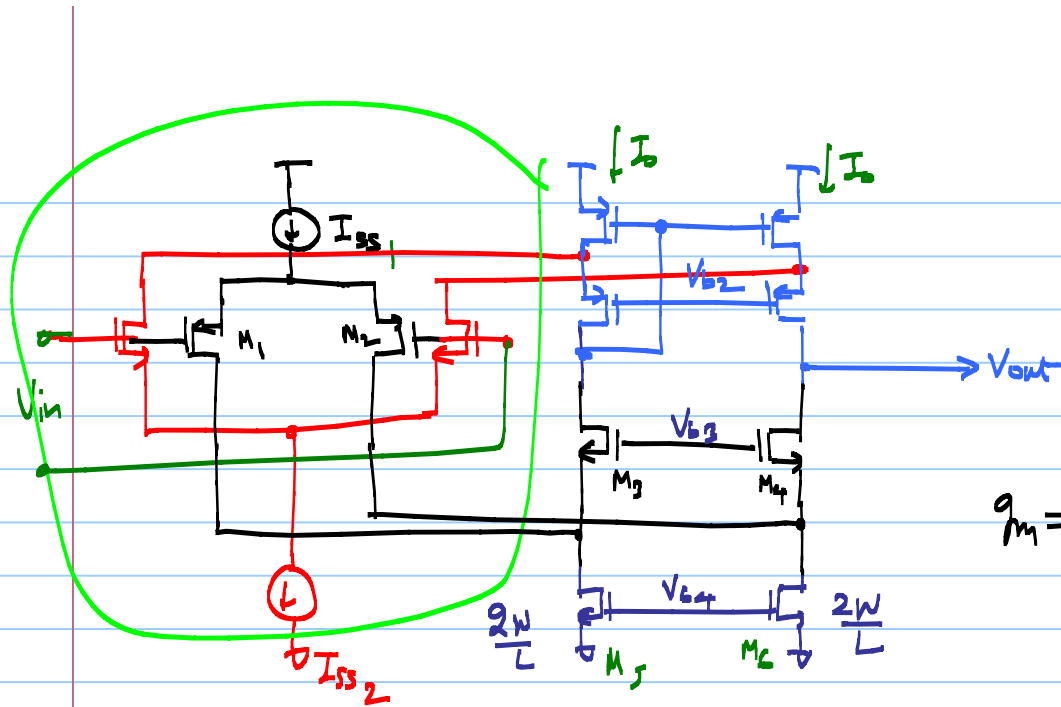

$$g_m = g_{m1} + g_{m2}$$

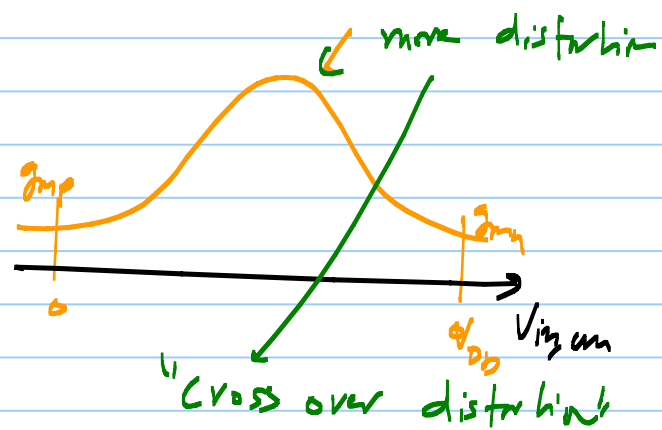


Two-stage opamps

* Issues with single-ended opamp


(-) $\rightarrow$ gain is limited by $T_{in} \cdot R_{out}$

heavy load $\rightarrow$ Big C
Small R

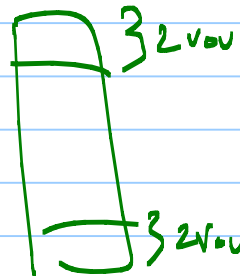(-) $\rightarrow$ output swing is limited by cascode output




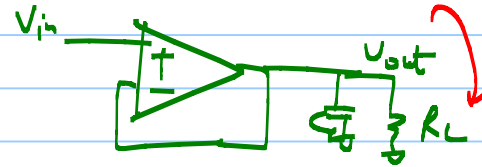(+) Large gain if unloaded $\leftarrow$ Cascoding (T_{e1} , F_2)




$$i_L = C \frac{dV_{out}}{dt}$$

$$i_L = \frac{V_{out}}{R_L}$$

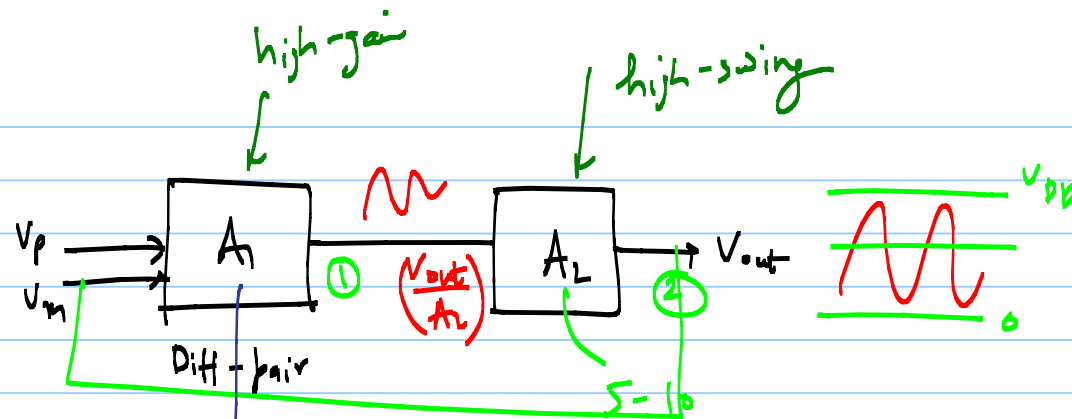


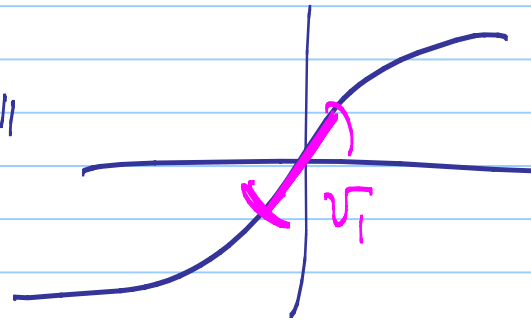output excursions are small
 $\rightarrow$ low-distortion



$\rightarrow$ Two-stage opamps provide
 much higher linearity.

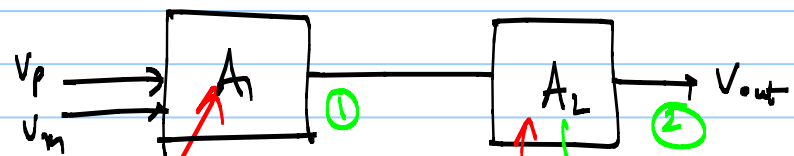$\rightarrow$ Second stage could be
 slightly non-linear



Diff-pair


FL

Teleskopie

Class A ✓

~~B~~

AB ✓

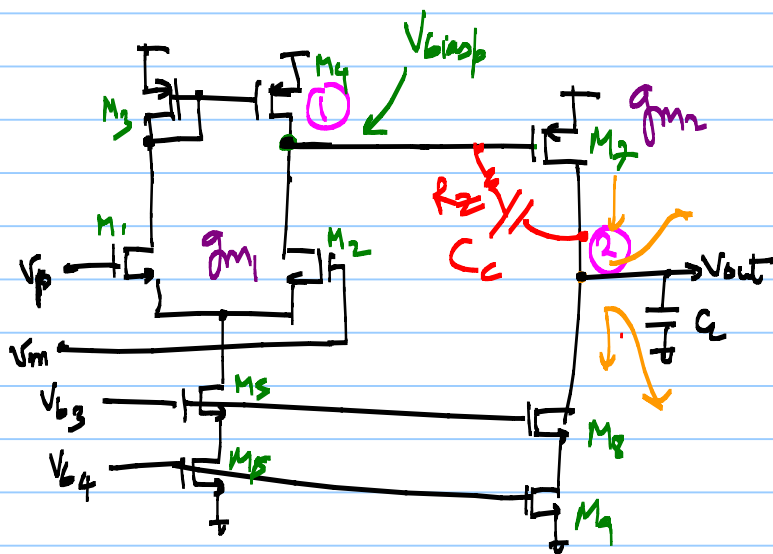

$$\omega_{p1} = \frac{1}{g_{m2} R_2 R_1 C_c}$$

$$\omega_{p2} \approx \frac{g_{m2}}{C_L}$$

$$\omega_{un} \approx \frac{g_{m1}}{C_c}$$