

Lecture 27

Note Title

5/7/2013


$$SR = \frac{I_{ss}}{C_c} = 500 \frac{V}{\mu s} = \frac{100 \mu}{C_c}$$

$$\Rightarrow C_c = \frac{100 \times 10^{-6} \times 10^{-6}}{500}$$


$$= \underline{0.2 \text{ pF}}$$



$$FOM_1 = \frac{f_{un} \cdot A_{OL}}{\text{power}}$$
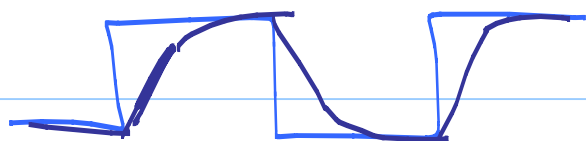
$$FOM_2 = \frac{SR \cdot A_{OL}}{\text{power}}$$



$$g_m r_o = 10$$

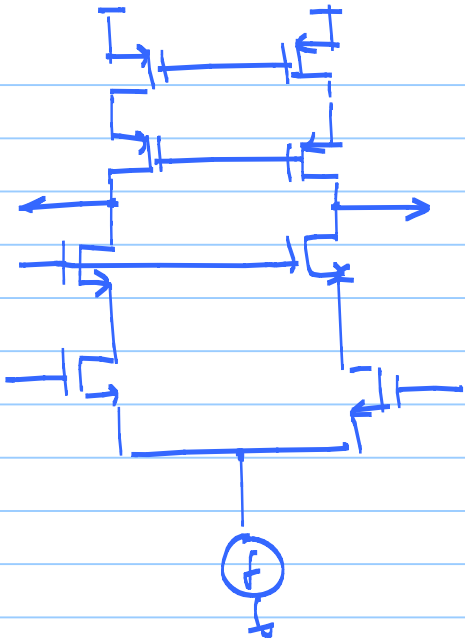


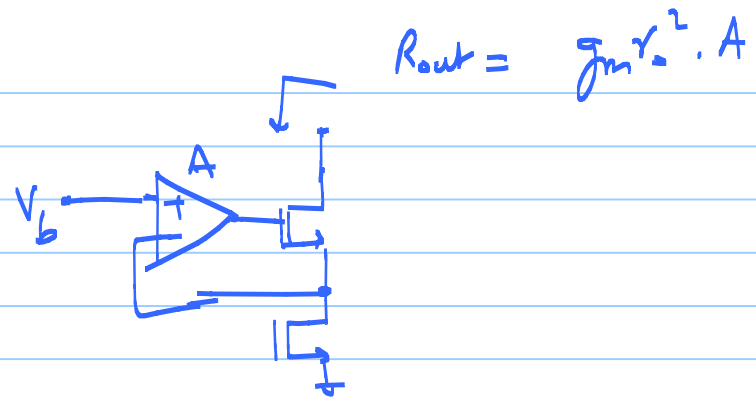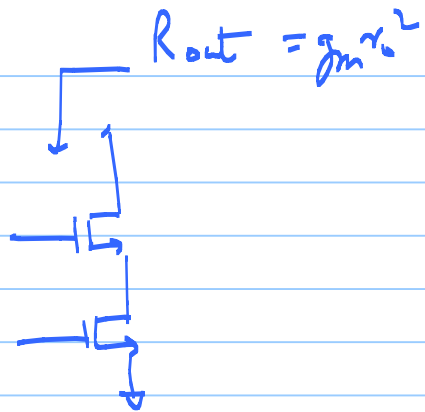


"Gain-Boosting"

nan-cmos

$\leq 90\text{nm}$

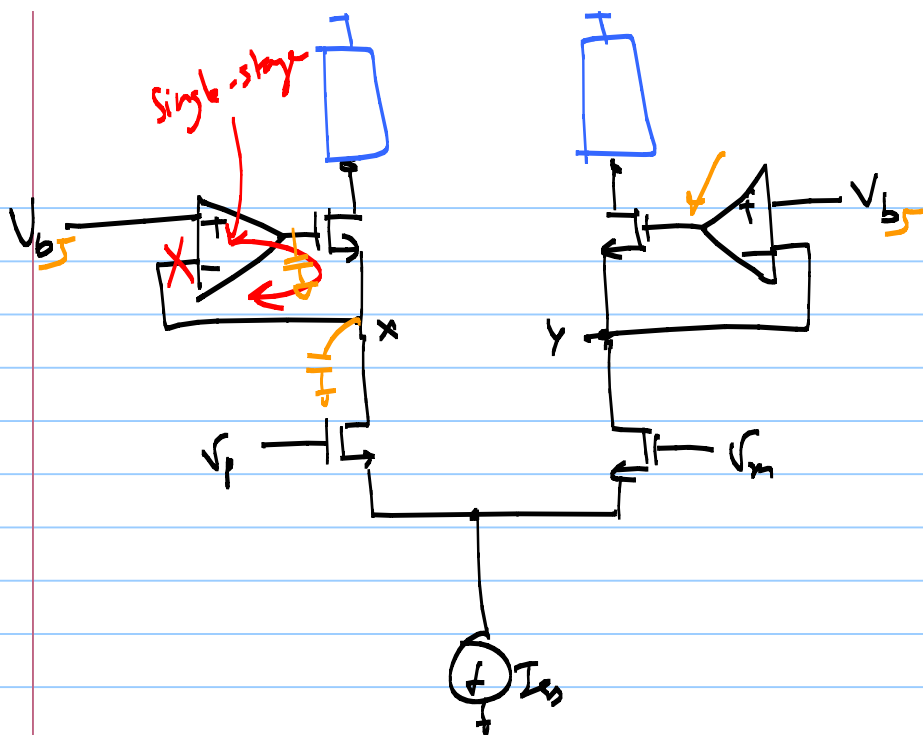

$$A_v = -g_m R_{out}$$

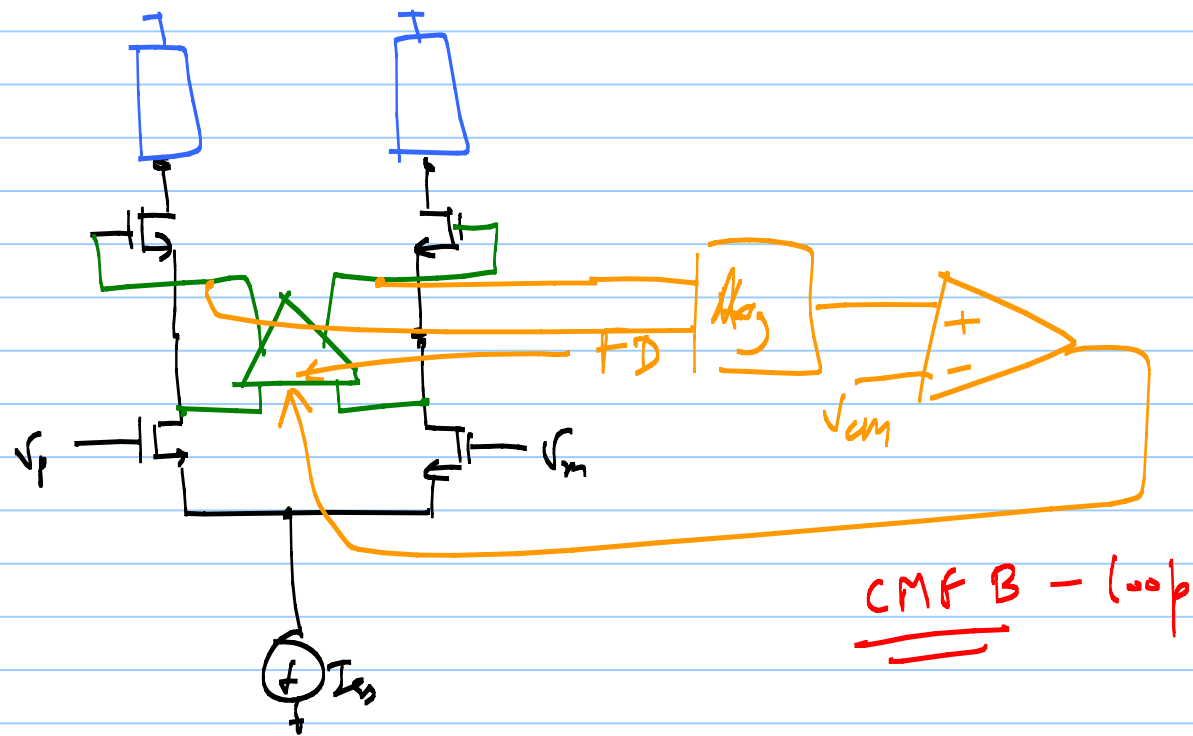

$0^{\circ} - 60^{\circ}\text{C}$

Temp co.


R _m

$$R(T) = R(T_0) \left[1 + TC_R \left(\frac{T - T_0}{T_0} \right) \right]$$

$$TC_R = \frac{1}{R} \frac{\partial R}{\partial T}$$

"Temperature Coefficient"

BMR

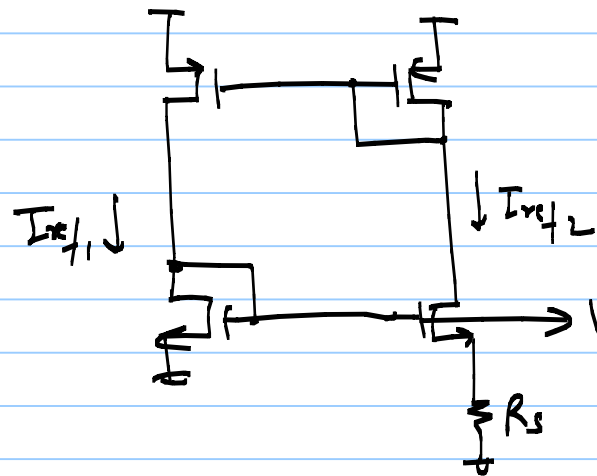

$$V_{ref} = \frac{2}{R_s k_p \cdot \frac{W}{L}} \left(1 - \frac{1}{\sqrt{K}} \right) + V_{THN}$$

$$\frac{\partial V_{ref}}{\partial T} = \left(\frac{\partial V_{THN}}{\partial T} \right) - \frac{2}{R_s k_p \cdot \frac{W}{L}} \left(1 - \frac{1}{\sqrt{K}} \right) \left(\frac{1}{R} \cdot \frac{\partial R}{\partial T} + \frac{1}{k_p} \cdot \frac{\partial k_p}{\partial T} \right)$$

$\neq 0$




$-\frac{1.5}{T}$

$\mu_n C_{ox}$

Select an R such that $\frac{\partial V_{ref}}{\partial T} = 0$ $\downarrow$ for temp co.
 ZTC

$$R = \frac{2}{\frac{\partial V_{ref}}{\partial T} \cdot k \ln \frac{W}{C}} \left(1 - \frac{1}{\sqrt{K}} \right) \left[\frac{1}{R} \cdot \frac{\partial R}{\partial T} - \frac{1.5}{T} \right]$$

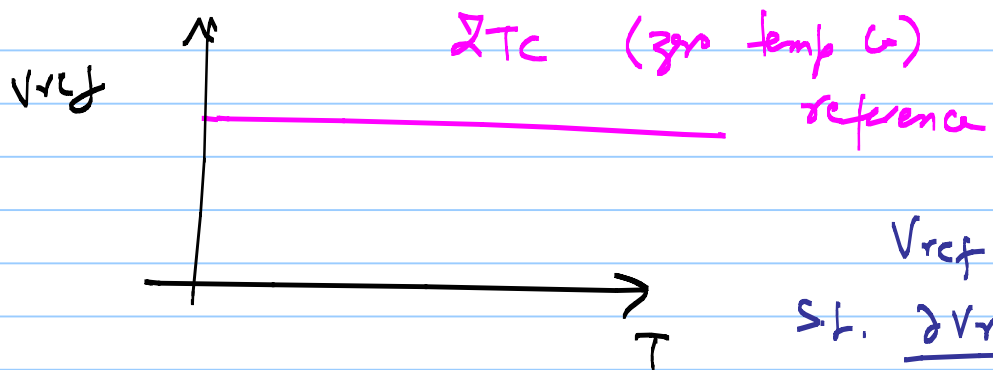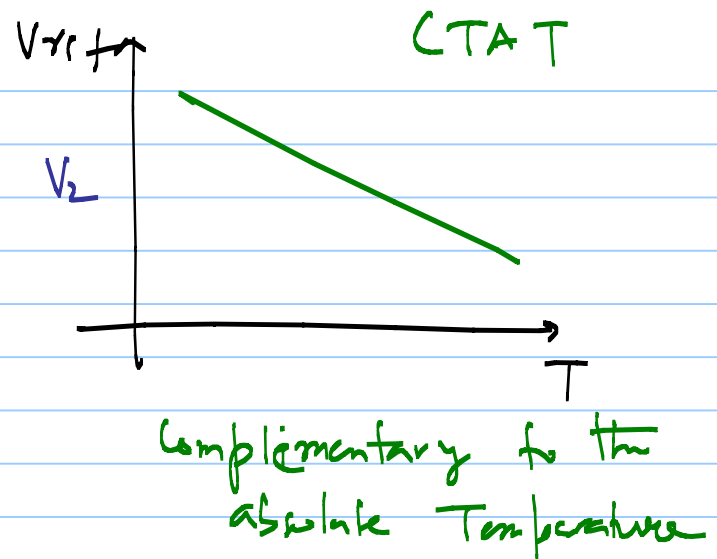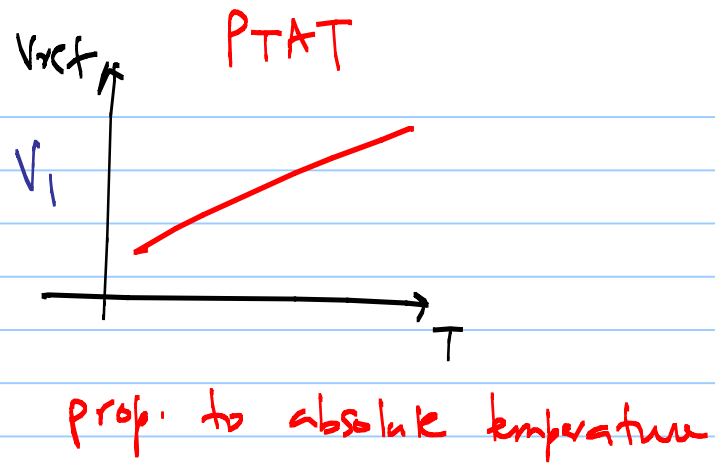
$\rightarrow$ impractical to make BMR
 with ZTC




$$V_{ref} = \alpha_1 V_1 + \alpha_2 V_2$$

s.t. $\frac{\partial V_{ref}}{\partial T} = 0 \approx \boxed{\alpha_1 \frac{\partial V_1}{\partial T} + \alpha_2 \frac{\partial V_2}{\partial T} = 0}$

⊛ CTAT $\Rightarrow$ -ve Temp Co

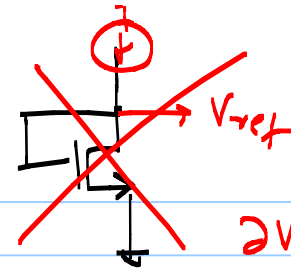

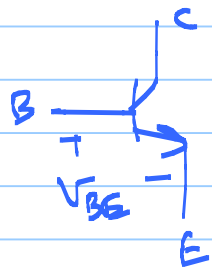
$$\frac{\partial V_{TH}}{\partial T} \leq 0$$



$$I_c = I_s e^{\frac{V_{BE}}{V_T}}$$

$$V_T = \frac{kT}{q} = 26 \text{ mV}$$

@ T = 300K

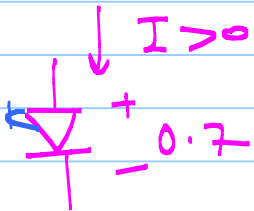

$$I_s \propto \mu k T n_i^2$$

$$\mu \propto \mu_0 T^m, \quad m = -\frac{3}{2}$$

$$n_i^2 \propto T^3 \cdot e^{-E_g/kT}$$

Bandgap

$E_g \rightarrow 1.12 \text{ eV}$

$$V_{BE} = V_T \ln \left(\frac{I_c}{I_s} \right)$$

$$I_s = b T^{(4+m)} \cdot e^{-E_g/kT}$$

②

* Compute the TC of V_{BE}

$$\frac{\partial V_{BE}}{\partial T} = \frac{\partial V_T}{\partial T} \cdot \ln\left(\frac{I_C}{I_s}\right) - \frac{V_T}{I_s} \cdot \left(\frac{\partial I_s}{\partial T}\right)$$

③

$$\begin{aligned} \frac{\partial I_s}{\partial T} &= \frac{(4+m)}{T} b T^{4+m} \cdot e^{-E_g/kT} + b T^{4+m} e^{-E_g/kT} \cdot \frac{E_g}{kT^2} \\ &= \frac{(4+m)}{T} \cdot I_s + I_s \cdot \frac{E_g}{kT^2} \end{aligned}$$

$$\frac{\partial V_T}{\partial I_s} \cdot \frac{\partial I_s}{\partial T} = (4+m) \frac{V_T}{T} + \frac{E_g}{kT^2} \cdot V_T$$

$$\Rightarrow \frac{\partial V_{BE}}{\partial T} = \frac{V_T}{T} \ln \left(\frac{I_c}{I_s} \right) - (4+m) \frac{V_T}{T} - \frac{E_g}{kT^2} \cdot V_T$$

$$\boxed{\frac{\partial V_{BE}}{\partial T} = \frac{V_{BE} - (4+m)V_T - E_g/q}{T}}$$


$$q = 1.6 \times 10^{-19} \text{ C}$$

* $\frac{\partial V_{BE}}{\partial T}$ depends upon V_{BE} itself besides the temperature

* with $V_{BE} = 0.75V$, $T = 300K$

$$\boxed{\frac{\partial V_{BE}}{\partial T} \approx -1.5 \frac{mV}{^{\circ}K}}$$


* V_{BE} is not a linear CTAT

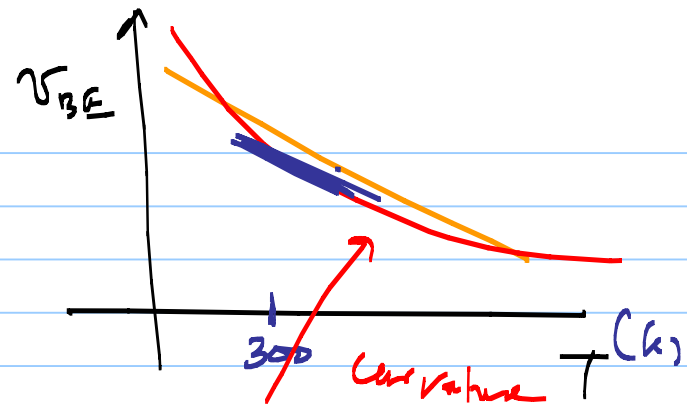

② PTAT

npn BJT's

diode connected

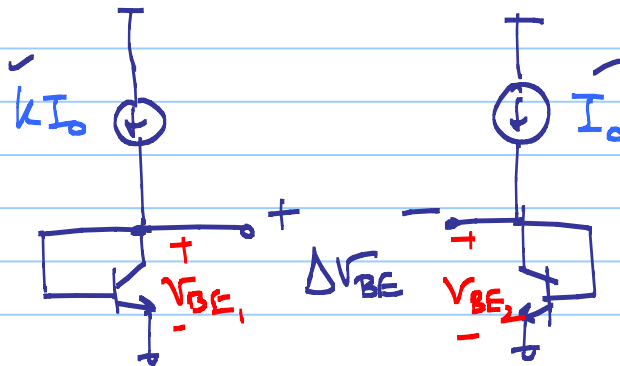

$$\Delta V_{BE} = V_{BE1} - V_{BE2}$$

$$= V_T \ln \left(\frac{kI_0}{I_s} \right) - V_T \ln \left(\frac{I_0}{I_s} \right)$$


$$= V_T \ln(k)$$



$$\Delta V_{BE} = V_T \ln(k)$$

$$\frac{\partial V_{BE}}{\partial T} = \frac{k}{q} \ln(k) > 0$$

independent of I_c .

linear PTAT

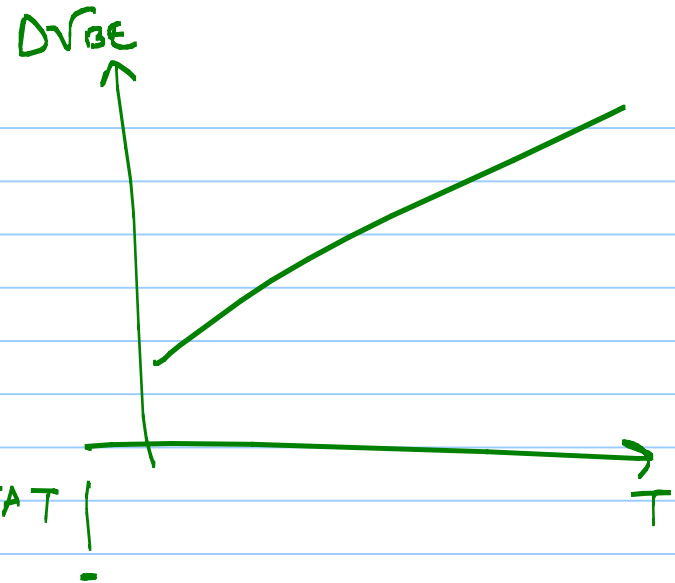

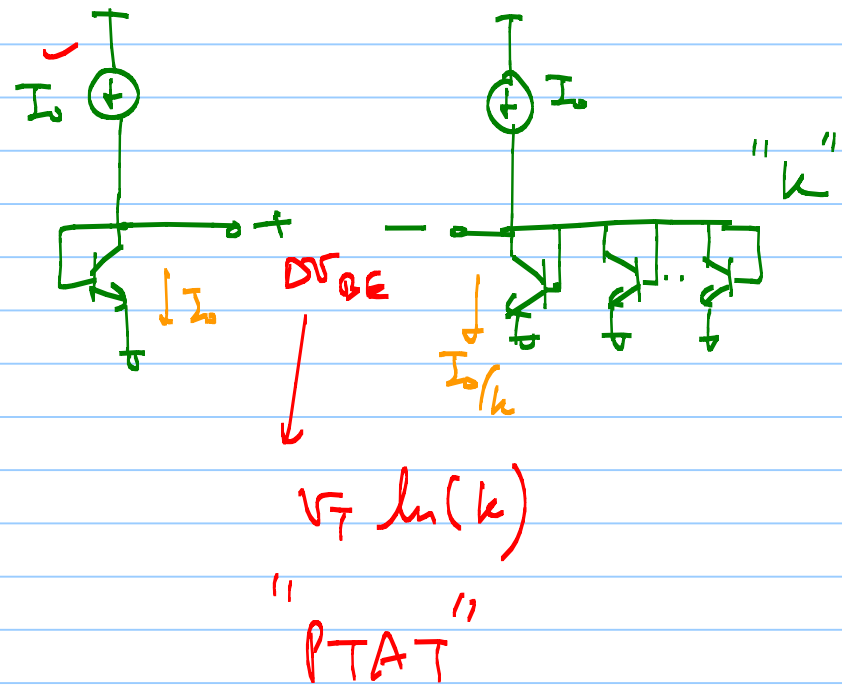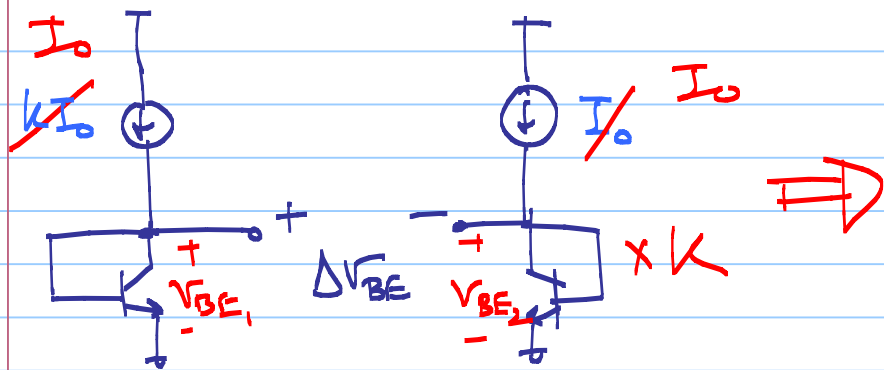

$V_T \ln(k)$

"PTAT"

Bandgap Reference $\Rightarrow \alpha_1 \cdot \text{CTAT} + \alpha_2 \cdot \text{PTAT} \Rightarrow \text{ZTC}$

$$V_{\text{ref}} = \alpha_1 \overbrace{V_{\text{BE}}}^{\Delta V_{\text{BE}}} + \alpha_2 \overbrace{\left(V_T \ln(k) \right)}^{\Delta V_{\text{BE}}}$$

* How do we choose α_1 & α_2 ?

$$\frac{\partial V_{\text{ref}}}{\partial T} = 0 \Rightarrow \alpha_1 \cdot \frac{\partial V_{\text{BE}}}{\partial T} + \alpha_2 \cdot \left(\frac{k}{q} \ln k \right) = 0$$

Boltzmann $\downarrow$ ratio of diodes

$$\alpha_2 \ln k = \frac{-\alpha_1 \cdot \frac{\partial V_{\text{BE}}}{\partial T}}{k/q}$$

$\frac{\partial V_{\text{BE}}}{\partial T} \rightarrow -1.5 \frac{\text{mV}}{^\circ\text{K}}$
 $k/q \rightarrow \frac{\partial V_T}{\partial T} = 0.087 \frac{\text{mV}}{^\circ\text{K}}$

$$\alpha_2 \ln(h) = \alpha_1 \cdot \frac{1.5 \frac{\text{mV}}{h}}{0.087 \frac{\text{mV}}{h}}$$

$$\boxed{\alpha_2 \ln(h) = \alpha_1 \times 17.2}$$

Arbitrarily choose $\alpha_1 = 1$

$$\Rightarrow \alpha_2 \ln(h) = 17.2$$

$$\Rightarrow \boxed{V_{REF} = V_{BE} + 17.2 \cdot V_T}$$

$$= 0.75V + 17.2 \times 26 \text{ mV}$$

$$\Rightarrow 1.2V$$

