

ECE 511- Lecture 3

$$\lambda = 0$$

Note Title

1/29/2013

AC analysis:

① Draw the DC "picture"

↳ short AC voltage
open AC currents

Solve for the bias points

② Use DC operating point, to find small-signal params

↳ g_m , r_o , g_{m_b} , $\dots$

"LINEARIZATION"

③ Draw the AC picture

↳ replace devices by their small-signal models


↳ short DC voltage sources

↳ open DC current sources

Solve for AC values

Final results $\Rightarrow$ superposition of DC & AC values

Ex 9.5

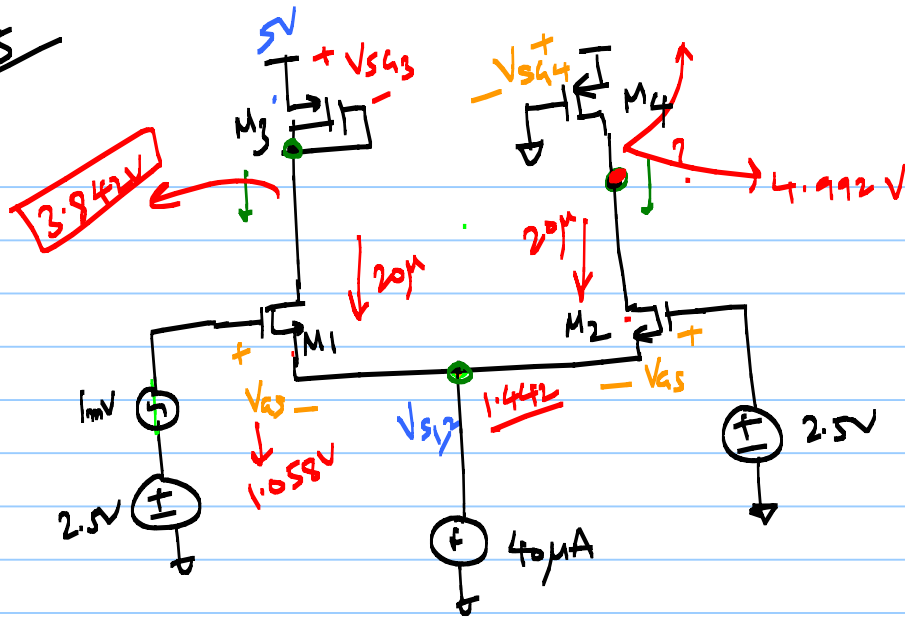

All NMOS $\rightarrow \frac{10}{2}$

$$A_{II} \text{ PMOS} \rightarrow \frac{3-}{2}$$

Table 6.2

$$V_{DD} = 5V$$
$$V_{THN} = 0.9$$
$$K_{P_n} = \frac{120 \mu A}{\sqrt{2}}$$
$$V_{THP} = 0.9$$
$$K_{fp} = 4 \frac{\mu \Delta}{v}$$

* Find all the voltages & currents

Solve DC picture:

* M_1 & M_2 are in saturation

$$V_{GS1} = V_{GS2} = \sqrt{\frac{2I_D}{K P_n \frac{W}{L}}} + V_{THN} = \sqrt{\frac{2 \times 20 \mu}{120 \mu \cdot \frac{10}{2}}} + 0.8$$

$$= 1.058 \text{ V}$$

$$V_{s,2} = 2.5 - 1.058 = \boxed{1.442}$$

Since $M_3 \Rightarrow \text{SAT}$

$$\Rightarrow V_{S43} = \sqrt{\frac{2 \cdot 20}{40} \cdot \frac{2}{30} + 0.9} = 1.158 \text{ V}$$

$$V_{D1} = V_{D3} = \boxed{3.842 \text{ V}}$$

Is M_1 really in SAT? **Yes**

$$V_{DS1} = 3.842 \text{ V} - 1.442 = 2.4 \text{ V}$$

$$V_{DS,sat1} = V_{GS1} - V_{THN1} = 1.058 - 0.8 = 258 \text{ mV}$$

* Assume $M_4 \Rightarrow \text{Triode}$ (initial guess)

$$V_{S44} = 5 \text{ V} \quad \text{Confirmed}$$

$$\text{for saturation} \Rightarrow V_{SD} \geq V_{SG} - V_{THP}$$

$$\cancel{V_S} - V_D \geq \cancel{V_S} - V_G - V_{THP}$$

$$V_{G4} \geq V_D - V_{THP}$$

V_D

$$\Rightarrow \underline{V_D \leq 0.7 \text{ V}}$$

$$20\mu = \frac{30}{2} \times \frac{40\mu A}{V} \cdot \left[(5-0.9)V_{SD} - \frac{V_{SD}^2}{2} \right]$$

↑ Quadratic

$$V_{SD} = 8.13 mV$$

$$V_{D4} = 4.992 V$$

$$x = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

②

M_4

$$R_{ch4} = \frac{1}{K_P \frac{W}{L} (V_{GS} - V_{thn})} = 407 \Omega$$

Deep Triode

M_1, M_2

$\Rightarrow$

$$g_{m1} = g_{m2} = \sqrt{2 \beta_n I_D} = 150 \frac{\mu A}{V}$$


20 μA

M_3

$\Rightarrow$

$$g_{m3} = \sqrt{2 \beta I_D} = 150 \frac{\mu A}{V} \Rightarrow R = \frac{1}{g_m} = 6.67 k\Omega$$
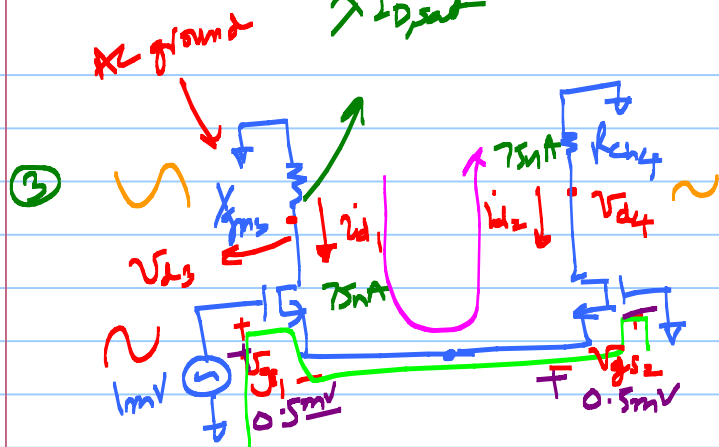
$$r_o = \frac{1}{\lambda I_{D,sat}} = \infty$$



$$-1mV + V_{gs1} - V_{gs2} = 0$$

$$V_{gs1} = V_{gs2} = \frac{1mV}{2} = 0.5mV$$

$$i_{d1} = g_m V_{gs1} = 0.5mV \times 150\mu = 75nA$$

$$i_{d2} = -75nA$$

KCL @ $V_{s1,2}$

$$i_{d1} + i_{d2} = 0$$

$$i_{d2} = -i_{d1}$$

$$V_{gs2} = -V_{gs1}$$

$$i_{d1} + i_{d2} = 0$$

$$g_{m1} \cdot V_{gs1} + g_{m2} \cdot V_{gs2} = 0$$

$$\Rightarrow V_{gs2} = -V_{gs1}$$

$$V_{d1} = V_{d3} = -i_{d1} \cdot \frac{1}{g_{m3}} = 0.5 \text{ mV}$$

$$V_{d2} = V_{d4} = -i_{d4} \cdot R_{ch4} = 0.03 \text{ mV}$$

$$\begin{aligned} V_{D1,3} &= V_{D1,3} + V_{d1,3} \\ &= 3.942 - \underbrace{0.5 \times 10^{-3} \sin(\omega t)}_{A_2} \end{aligned}$$

$$V_{D2,4} = 4.992 + \underbrace{0.03 \times 10^{-3} \sin(\omega t)}_{A_2}$$

$$i_{d1} = I_{D1} + i_{d1}$$

$$i_{d2} = I_{D2} + i_{d2}$$



• A₂

• from

Long-channel g_m, r_o
from Chap 6 $\Rightarrow$

$$\lambda \propto \frac{1}{L}$$

$$r_o = \frac{1}{\lambda I_{D,sat}} \propto \frac{L^2}{V_{DS,sat}^2}$$

$$r_o \propto \frac{L^2}{V_{OV}^2}$$

$$L \uparrow \Rightarrow r_o \uparrow$$
$$V_{OV} \downarrow \Rightarrow r_o \uparrow$$


$$g_m = \beta V_{OV} \propto \frac{V_{OV}}{L}$$

$$g_m r_o$$

max
open loop gain from a transistor

$$I_{D,sat} = \frac{K_n}{2} \cdot \frac{W}{L} \cdot V_{DS,sat}^2$$


$$V_{OV} = V_{GS} - V_{THN}$$

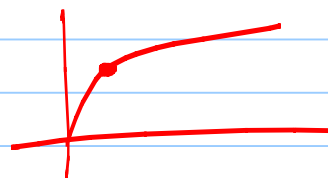

MOSFET Transition frequency (f_T)


SAT

As picture

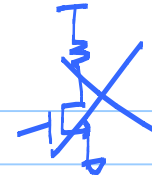

Current gain

$$@ f = f_T = \left| \frac{i_d}{i_g} \right| = 1$$

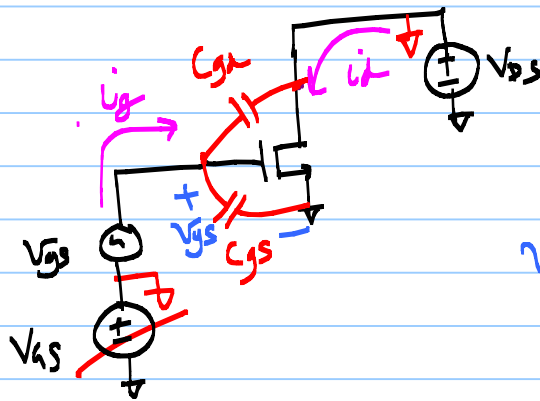


$$V_{gs} = \frac{i_g}{s(C_{gd} + C_{gs})} \longrightarrow \textcircled{1}$$

$$i_d = g_m V_{gs}$$

$$\Rightarrow i_d = \frac{g_m i_g}{s(C_{gd} + C_{gs})}$$

$$\frac{i_d}{i_g} = \frac{g_m}{s(C_{gd} + C_{gs})}$$

$$\left| \frac{i\omega}{i\omega} \right| = \frac{g_m}{2\pi f (C_{gd} + C_{gs})} = 1$$

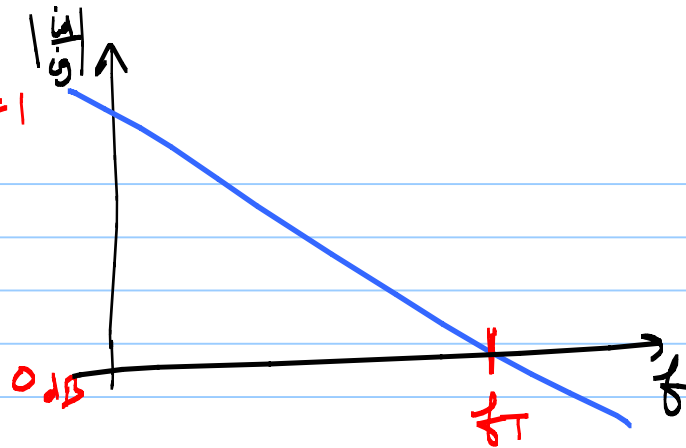

$$\Rightarrow f_T = \frac{g_m}{2\pi (C_{gs} + C_{gd})}$$

ignore junction caps


⇒ more inhibition on f_T

In sat

$$C_{gs} = \frac{2}{3} W L C_{ox}$$

$$C_{gt} = C_{gdo} \cdot W$$

$$C_{gs} \gg C_{gt}$$

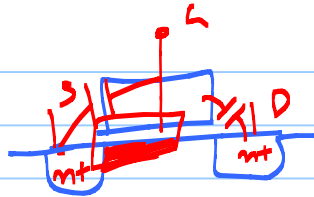

RF Aside
 $f_{max} > f_T$



$$f_T = \frac{g_m}{2\pi C_{gs}} = \frac{3\mu_n (V_{GS} - V_{THN})}{4\pi L^2 C_{ox}} = \frac{3\mu_n}{4\pi} \cdot \frac{V_{ov}}{L^2}$$

Long
channel
CMOS
process

$$f_T \propto \frac{V_{ov}}{L^2}$$

fastest operation

$$L = L_{min}$$

$$V_{ov} \uparrow$$

moderate speed $V_{ov} \leq 2-5\% \cdot V_{DD}$

high speed $V_{ov} > 5\% \cdot V_{DD}$