
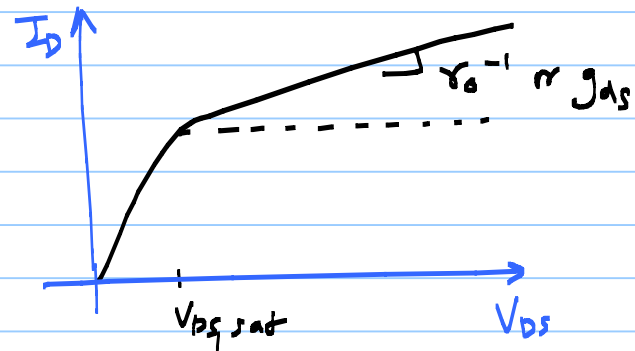




ECE 511 - Lecture 7

Note Title


2/12/2013

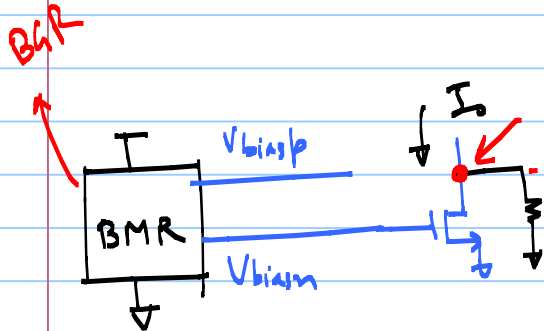

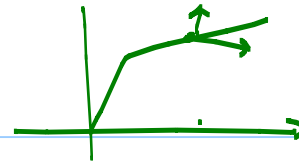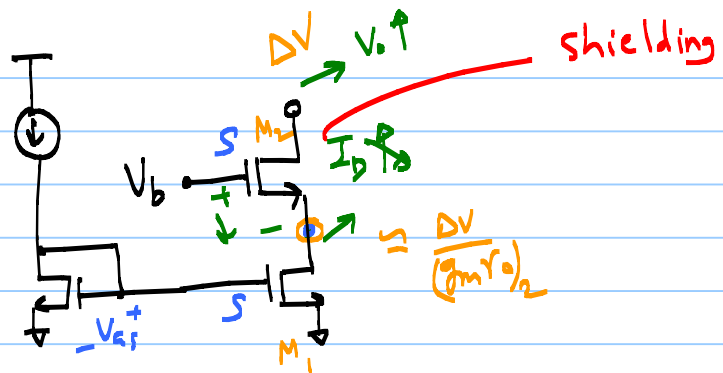* hold the V_{DS} of the current mirror device to be more constant





x How to set V_b ?

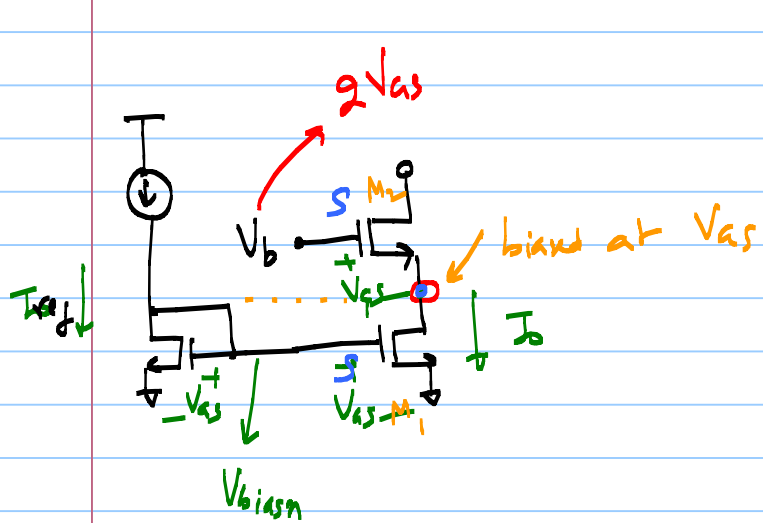

$$V_b = 2V_{as}$$

I_o mirrors I_{ref} closely.

$$I_o \triangleq I_{ref}$$

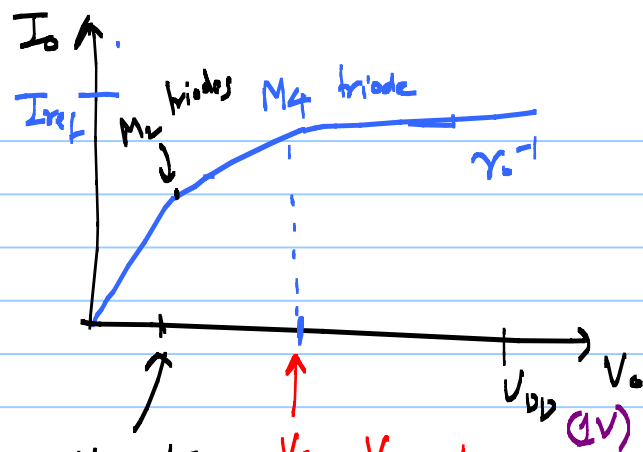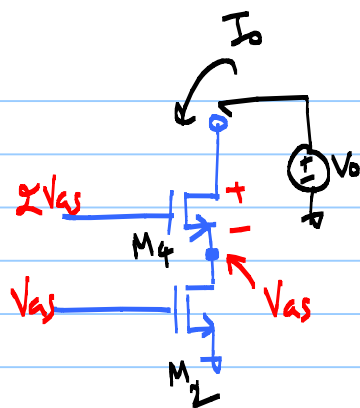

$V_{DS,sat}$
(70mV)

$V_{GS} + V_{DS,sat}$

$V_{TH} + 2V_{DS,sat}$
280m 140m


420m

voltage headroom

(580m)

reduced swings for the CM



"Cascode Current Mirror"

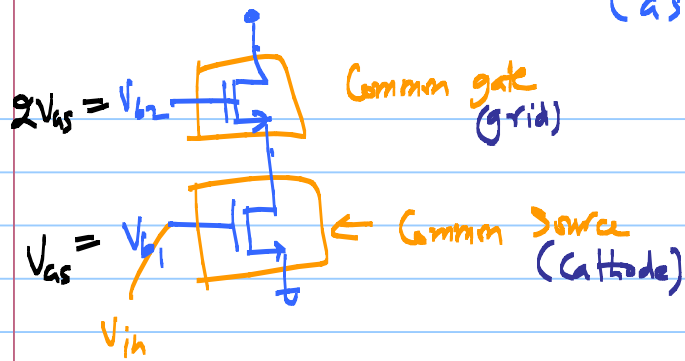


cascode of common cathode and common grid amplifier

CASCODE

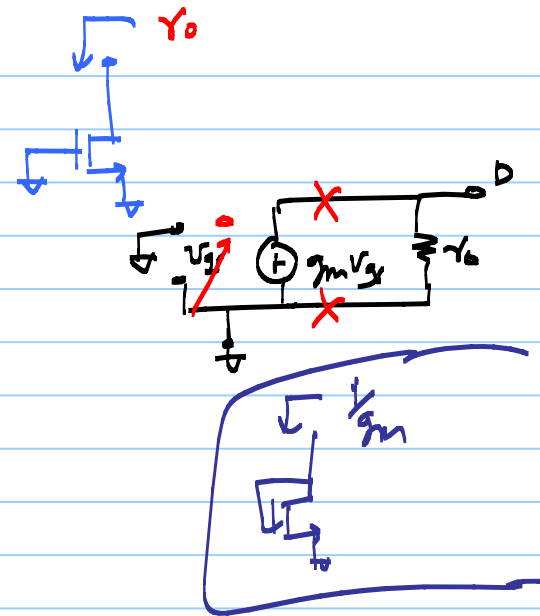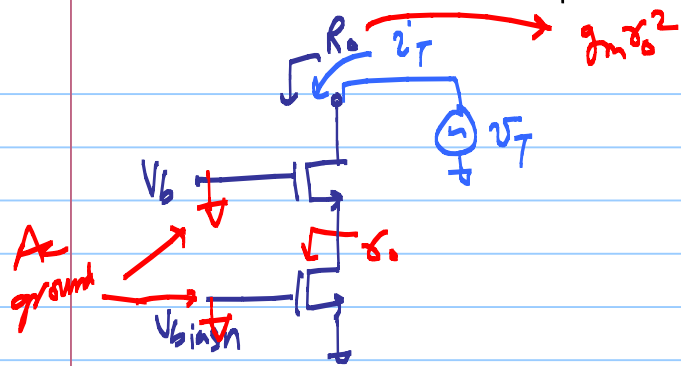* What is R_{out} for the cascode current mirror?



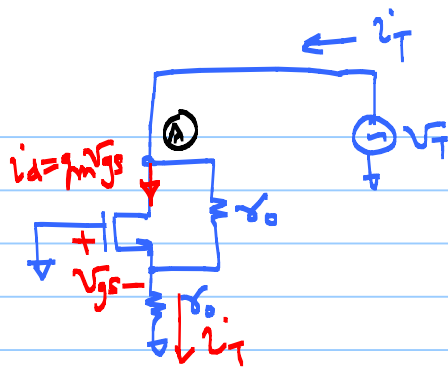

$$\text{KVL: } v_{gs} + i_T r_o = 0$$

$$\Rightarrow v_{gs} = -i_T r_o \rightarrow \textcircled{1}$$

KCL @ (A):

$$i_T - g_m v_{gs} - \frac{(v_T - (-v_{gs}))}{r_o} = 0 \rightarrow \textcircled{2}$$

Eliminate v_{gs}

$$\Rightarrow i_T + g_m r_o i_T - \frac{v_T}{r_o} + i_T = 0$$


$$\Rightarrow \frac{v_T}{r_o} = i_T (2 + g_m r_o)$$

$$R_o = \frac{v_T}{i_T} = (2 + g_m r_o) r_o = 2r_o + g_m r_o^2$$



$$R_{ncas} \approx \boxed{g_m r_o^2} = (g_m r_o) \cdot r_o$$

if $g_m r_o \gg 1$
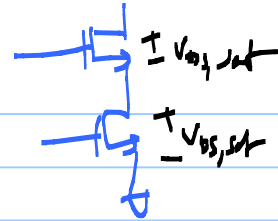
$$V_o \geq 2V_{DS,sat} + \underline{\underline{V_{THN}}}$$



Wide Swing Cascode CM

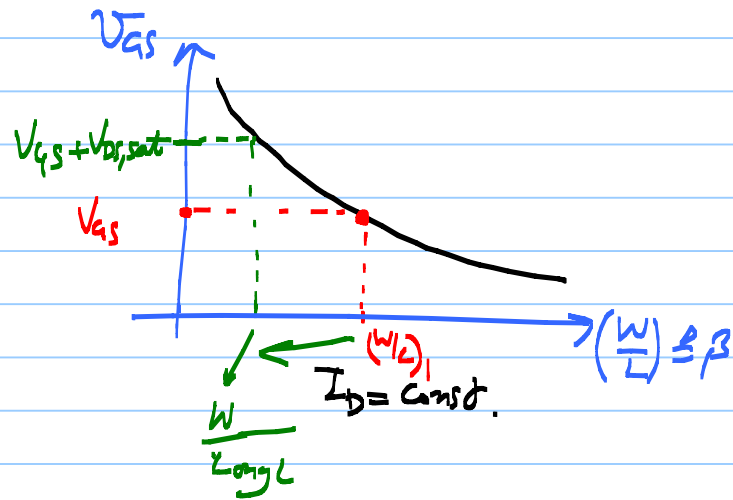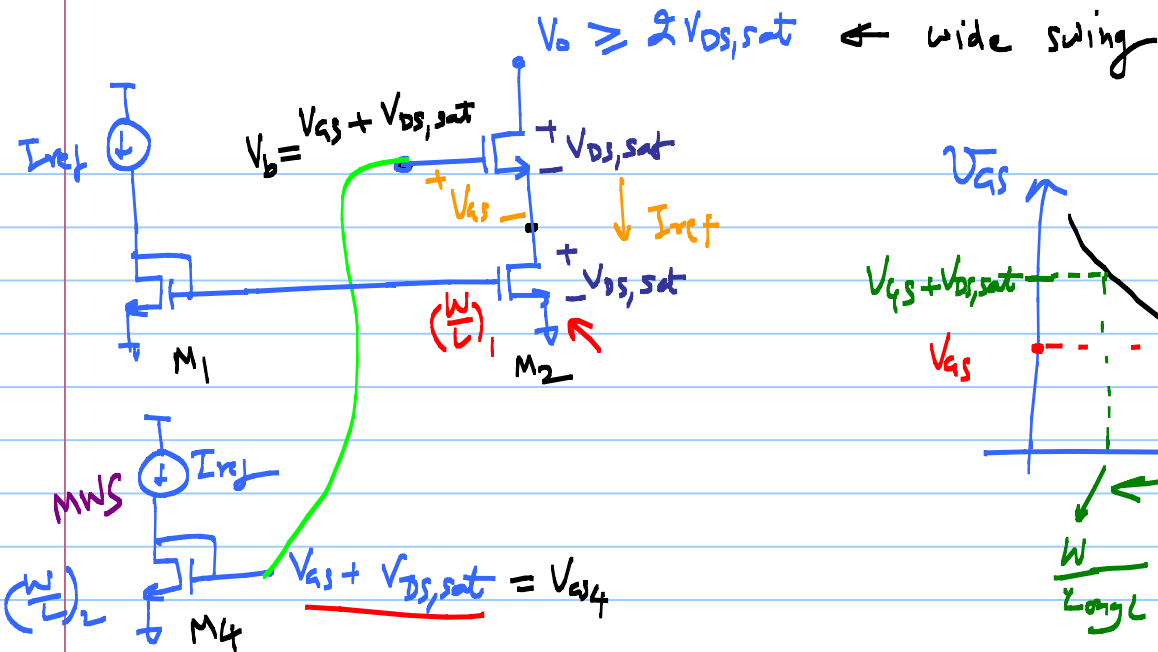

$$\underline{V_{GS4}} = 2V_{DS,sat} + V_{THN} = \sqrt{\frac{2I_{ref}}{\beta_4}} + V_{THN}$$




$$2 \left(\sqrt{\frac{2I_{ref}}{\beta_2}} \right) = \sqrt{\frac{2I_{ref}}{\beta_4}}$$

$$\Rightarrow 2\sqrt{\beta_4} = \sqrt{\beta_2}$$


$$\beta_4 = \frac{\beta_2}{4}$$

$$\Rightarrow \left(\frac{W}{L} \right)_4 = \frac{W}{4L}$$

$$V_o \in [2V_{DS,sat}, V_{DD}]$$

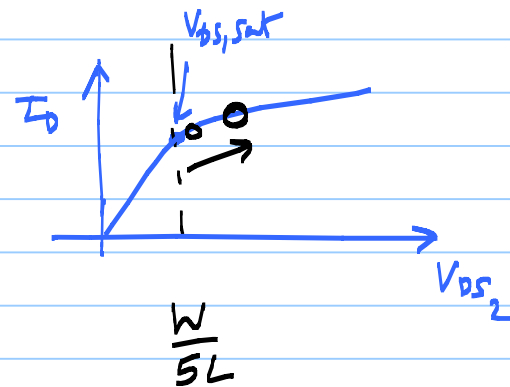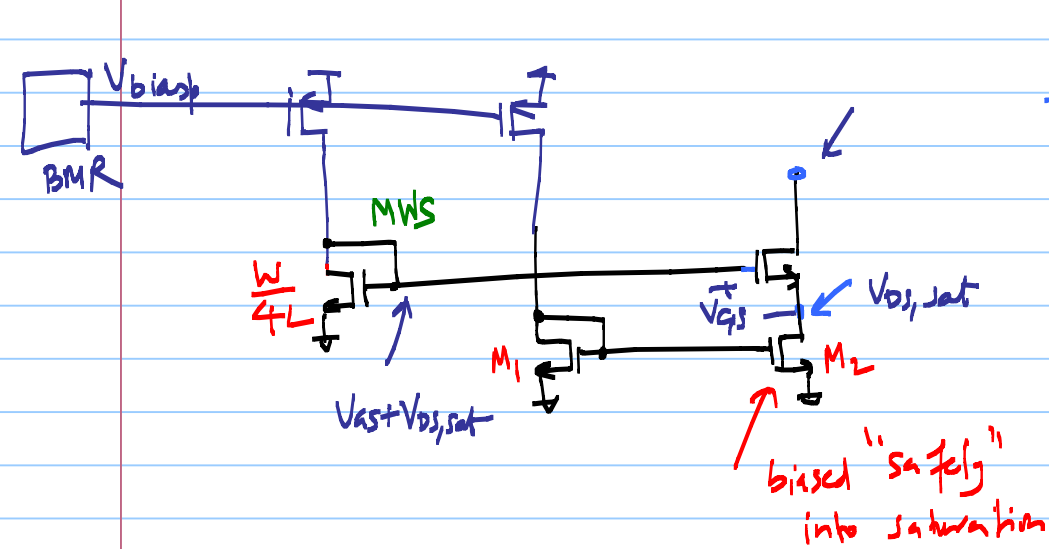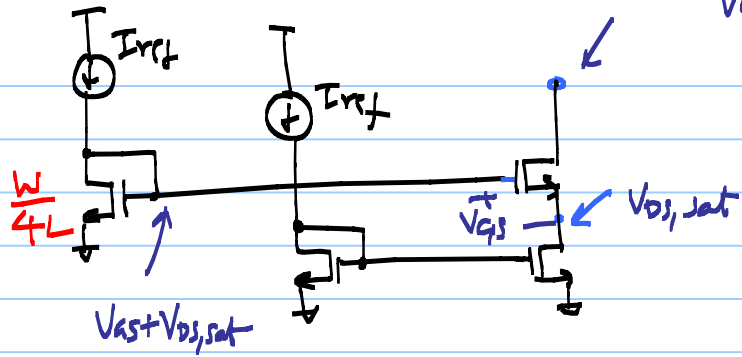

Somn $\rightarrow \frac{W}{25L}$

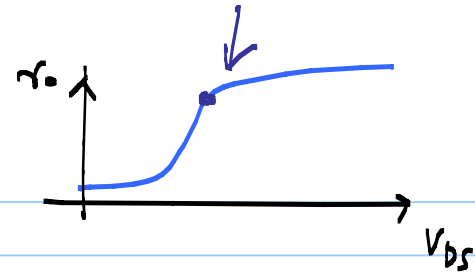

"Replica Biasing"

Fig 20.38

