

# Homework 6

ECE 5/411 – CMOS Analog IC Design (Spring 2014)

Due on Tuesday, April 1, 2014.

**Note:**

1. Use Cadence schematic capture, layout and Spectre simulation tools, available on the AMS servers for the homework problems.

**Problem 1:** Assuming all transistors are in saturation, find expressions for small-signal voltage gain ( $A_v = G_m R_{out}$ ),  $R_{in}$  and  $R_{out}$  for each of the circuits shown below. Use variables  $g_{m1}$ ,  $r_{o1}$ ,  $g_{m2}$ ,  $r_{o2}$ , etc. Assume that  $r_o = \infty$ , unless you must have a finite value.

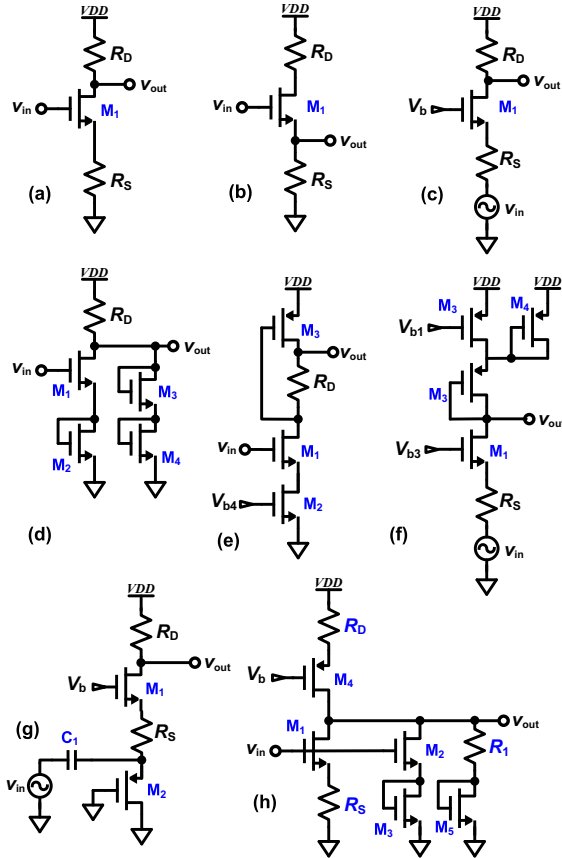


Figure 1

**Problem 2:** The NMOS in the figure below has  $V_{THN} = 0.7V$ , and  $KP_n = 500\mu A/V^2$ . The drain current in the device is 1mA.

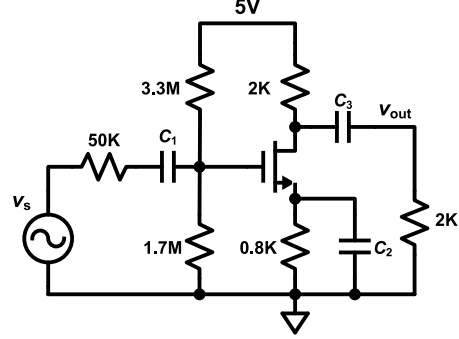


Figure 2

- Determine the small signal gain from  $v_s$  to  $v_{out}$ .
- Determine the  $W/L$  for the device and the DC operating points  $V_{GS}$  and  $V_{DS}$ .
- The lowest frequency in  $v_s$  is  $\omega_{in} = 100\text{rad/s}$ . Determine the minimum values of  $C_1$ ,  $C_2$  and  $C_3$  required so that the frequencies associated with their charging/discharging is at least 10 times smaller than  $\omega_{in}$ .
- The supply voltage is changed to 5.5. Determine the small signal gain of the amplifier.

**Problem 3:** For the amplifier shown in the figure below:

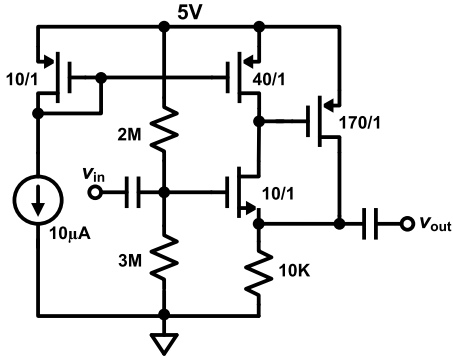


Figure 3

$$V_{THN} = 0.7V, \text{ and } KP_n = 200 \frac{\mu A}{V^2}$$

$$V_{THP} = 0.8V, \text{ and } KP_p = 50 \frac{\mu A}{V^2}$$

$$\gamma = 0$$

- Determine the operating points of all the devices in the circuit. For this part, neglect channel length modulation ( $\lambda = 0$ ).
- All transistors in the circuit have finite  $r_o$ , such that for any transistor  $g_m r_o = 100$ . Draw the small signal equivalent circuit of the amplifier, and determine the small signal gain ( $\frac{v_{out}}{v_{in}}$ ). Also determine the input and output resistances of the amplifier (Perform low-frequency analysis only).